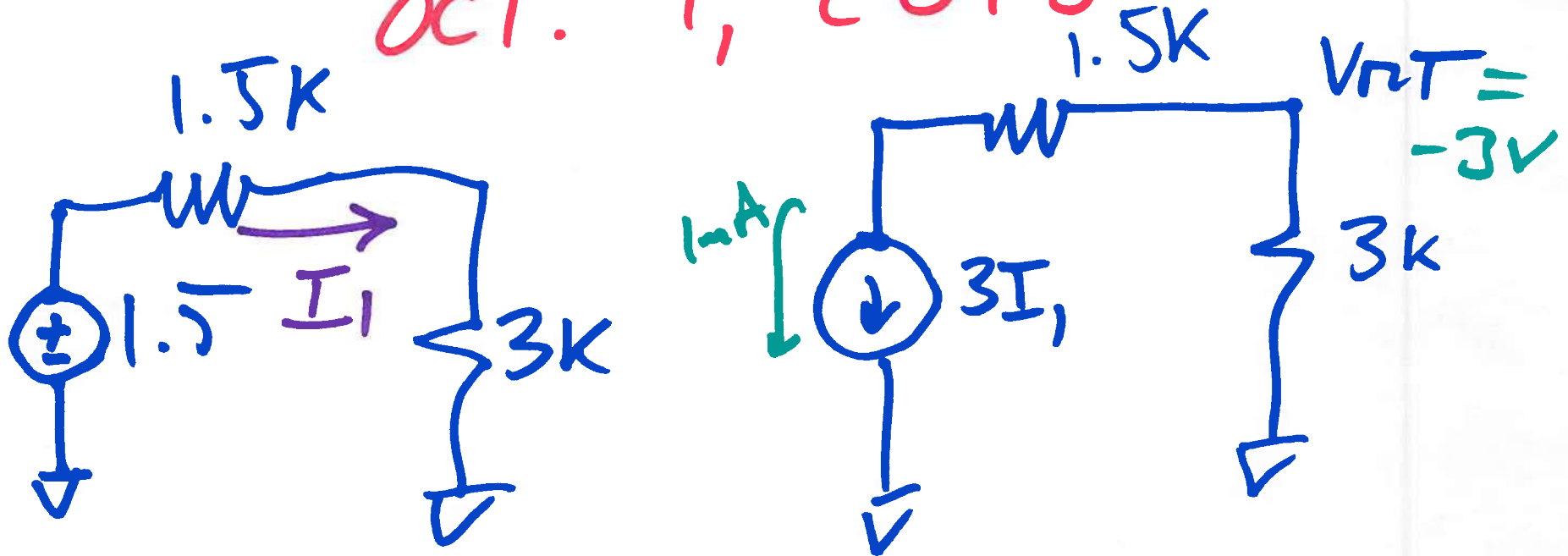


EE 220 circuits 1


Lecture 11

Oct. 1, 2018




$$I_1 = \frac{1.5}{4.5k} = \frac{1}{3}\mu A$$


11

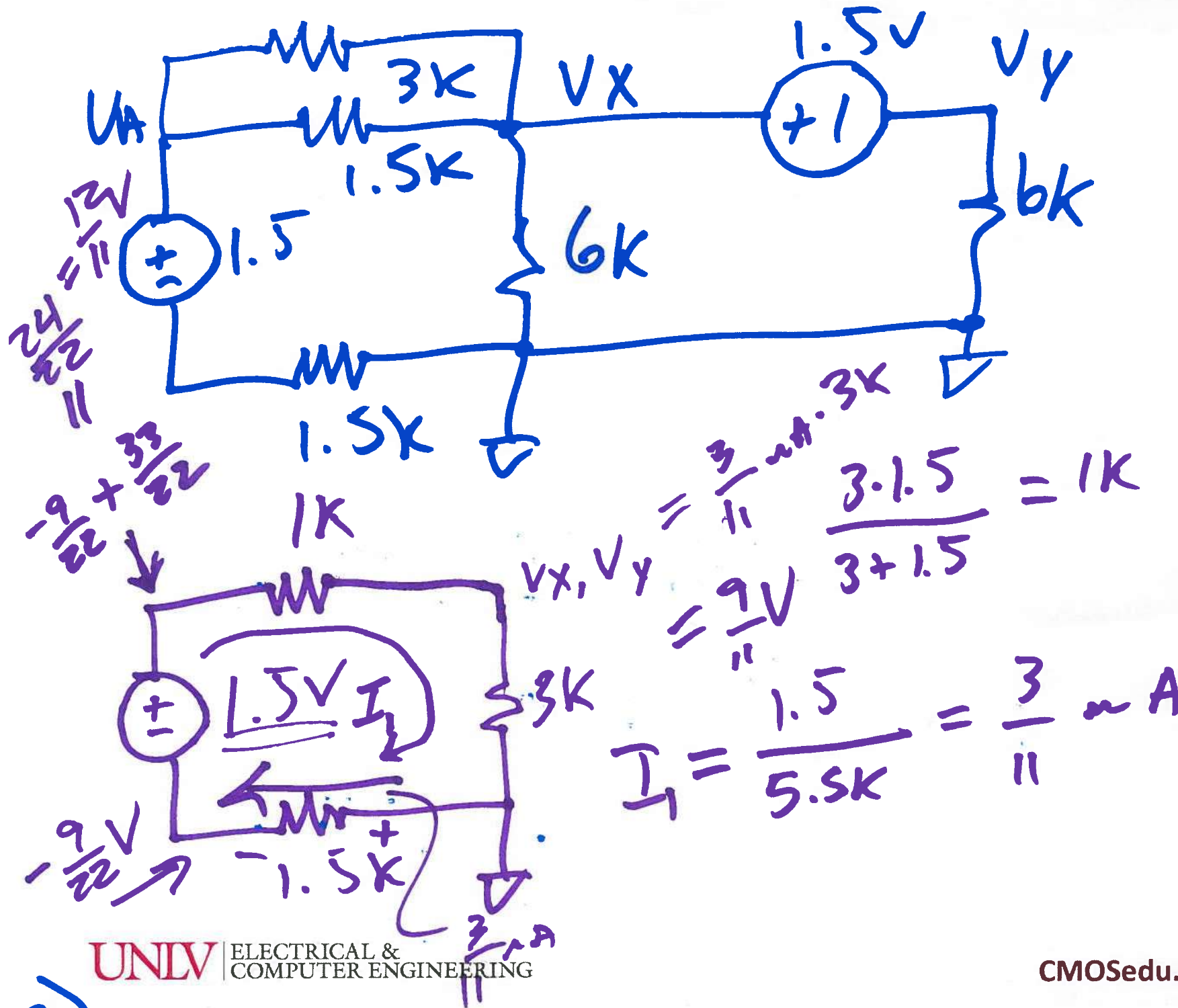

2)

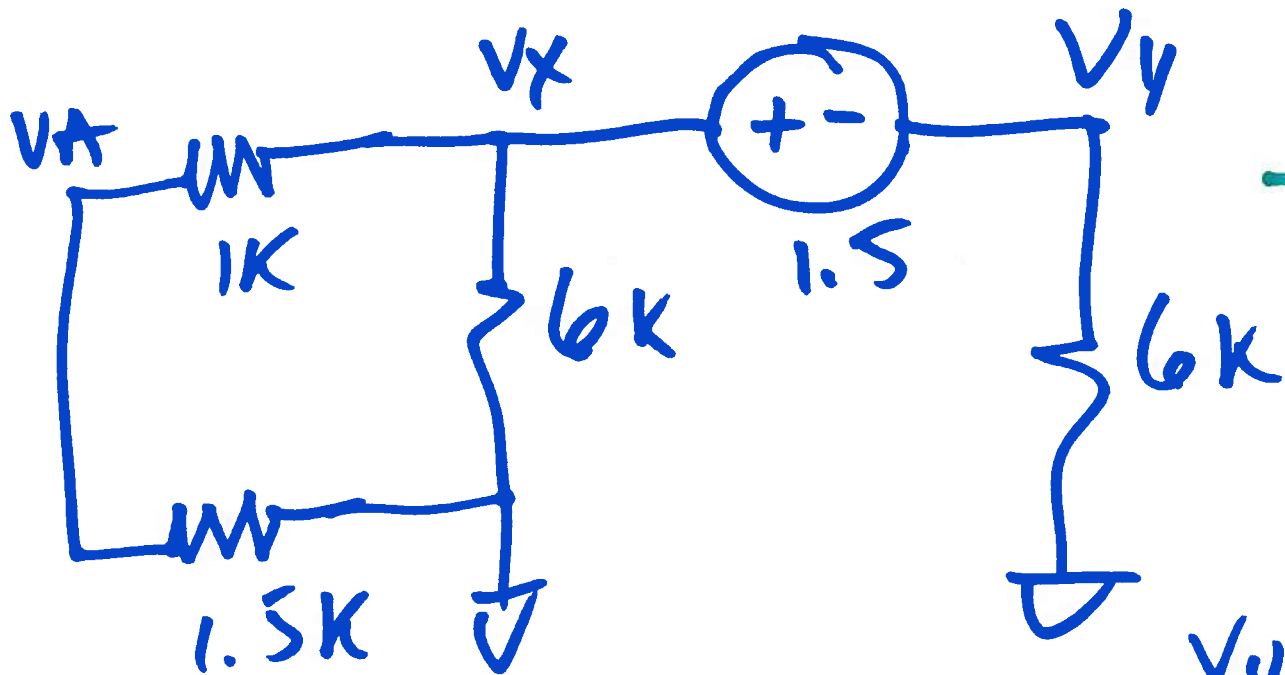

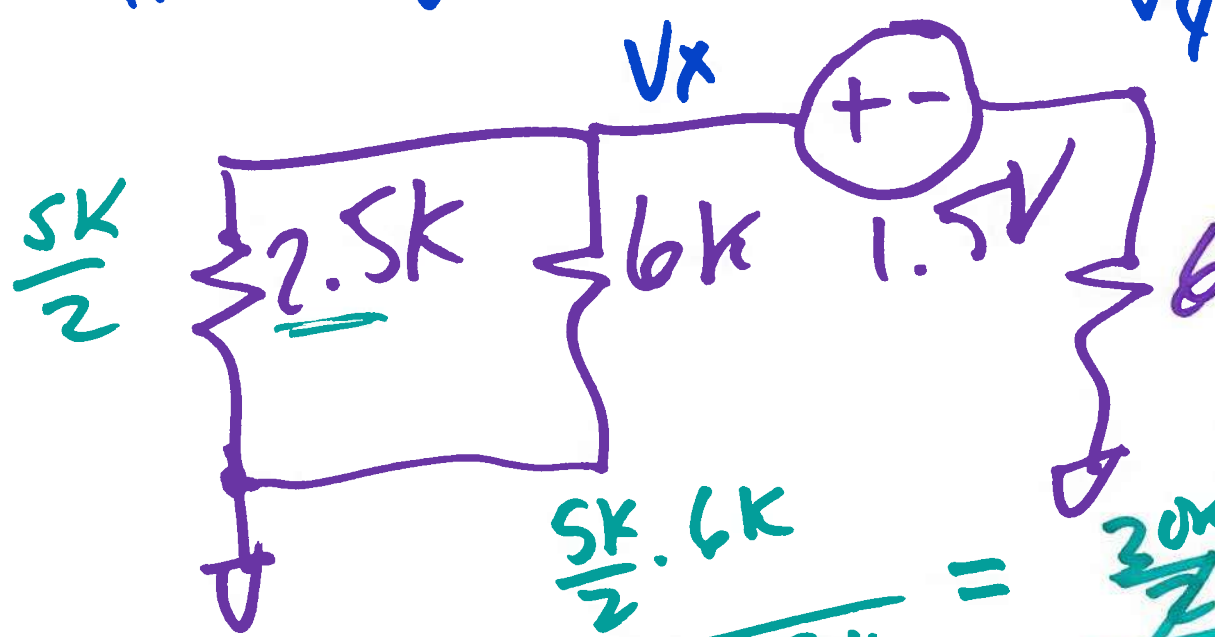
$$\frac{\frac{5k}{2} \cdot 6k}{\frac{5k}{2} + \frac{12k}{2}} = \frac{\frac{30k^2}{2}}{\frac{17k}{2}} = 15k$$



$$\frac{\frac{5k}{2} \cdot 6k}{\frac{5k}{2} + \frac{12k}{2}} = \frac{\frac{30k^2}{2}}{\frac{17k}{2}} = \frac{30k}{17}$$

$\frac{30k}{17}$
 $\frac{30k}{17} \cdot \frac{6k}{6k + \frac{30k}{17}} = \frac{30k}{17} \cdot \frac{6k}{\frac{102k + 30k}{17}} = \frac{30k}{17} \cdot \frac{6k}{\frac{132k}{17}} = \frac{30k}{17} \cdot \frac{6k \cdot 17}{132k} = \frac{30k \cdot 6k}{132k} = \frac{180k^2}{132k} = \frac{15k}{11}$


3)

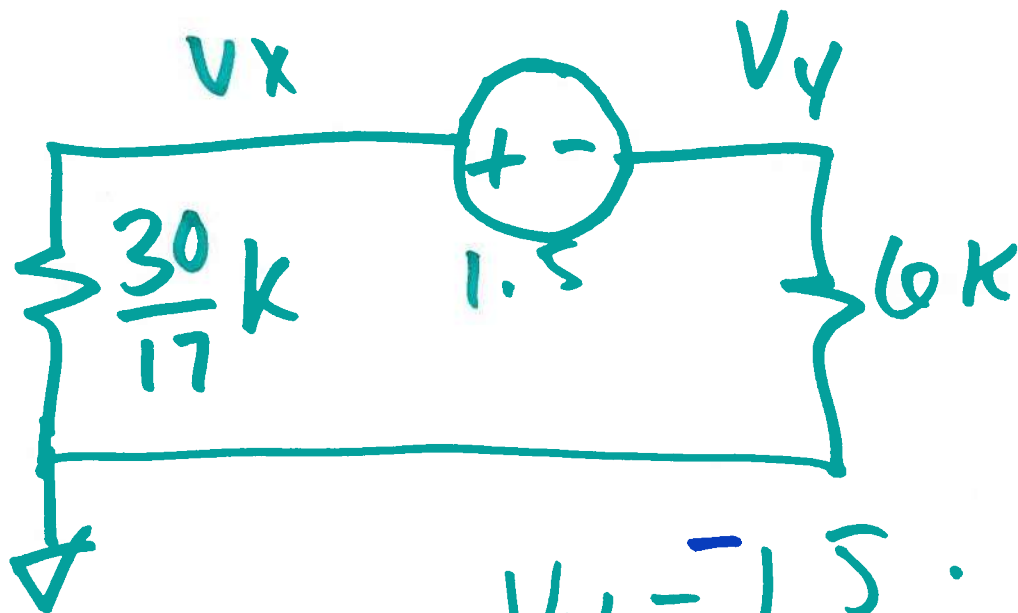

$$V_y = 1.5 \cdot \frac{6k}{6k + \frac{30}{17}k}$$

$$V_x = V_y + 1.5$$

4)

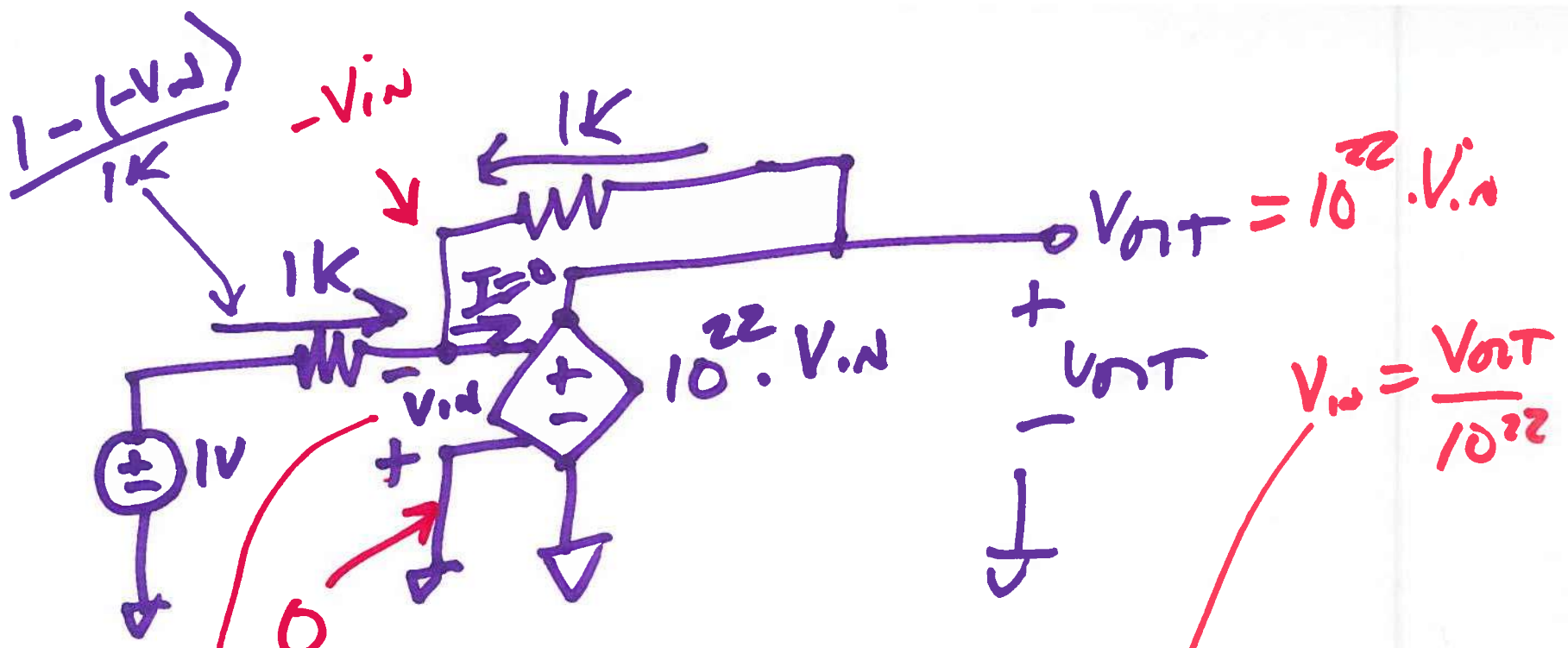

$V_{out} = -1V$

$0 - (-V_{id}) = V_{id}$

$\frac{1 - (-V_{in})}{1k} + \frac{V_{out} - (-V_{in})}{1k} = 0$

$-1 = V_{out} \left(1 + \frac{2}{10^{22}}\right)$


$1 + V_{in} + V_{out} + V_{in} = 0$
 $1 + 2V_{in} + V_{out} = 0$
 $1 + \frac{2V_{out}}{10^{22}} + V_{out} = 0$



1) Determine
+ (non-inverting)
Voltage

2) $V_+ = V_-$
3) KCL AT
inverting input

op-amp
operational Amplifier

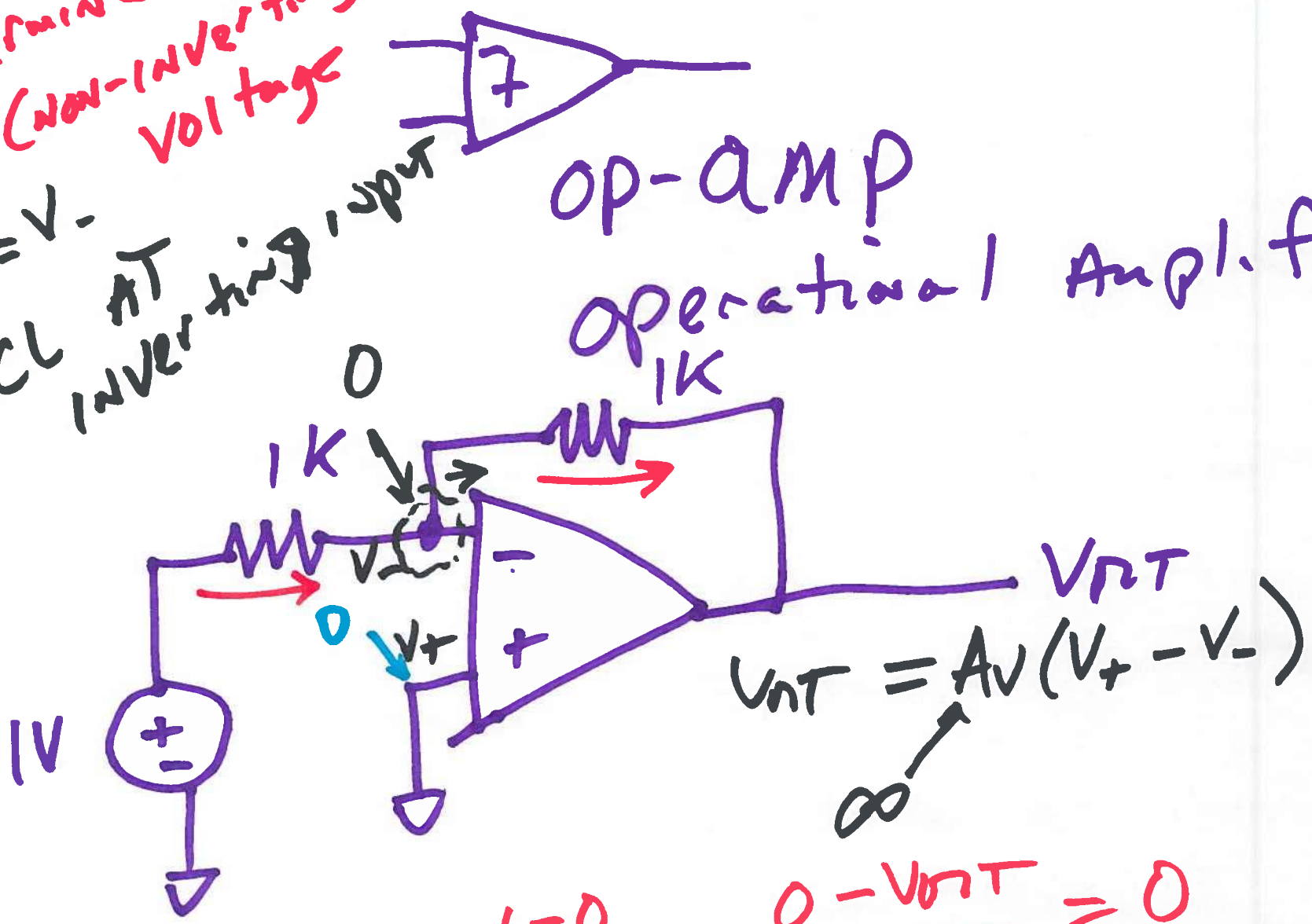

$$V_{out} = A_V (V_+ - V_-)$$

∞

$$\frac{1-0}{1k} - \frac{0 - V_{out}}{1k} = 0$$

$$V_{out} = -1V$$

6)

