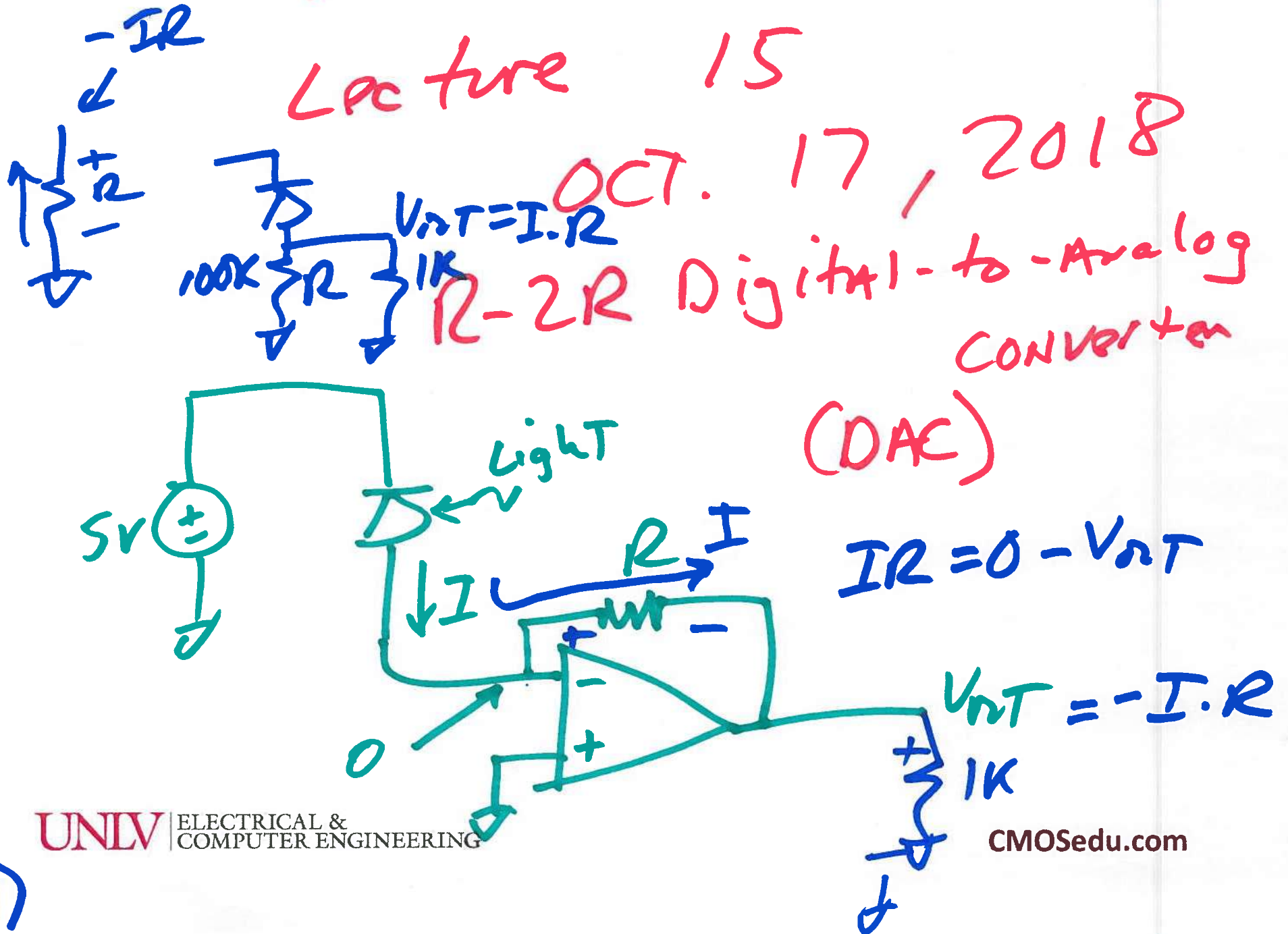


# EE 220 Circuits 1

## Lecture 15


OCT. 17, 2018

### R-2R Digital-to-Analog Converter (DAC)



1)

# Capacitors

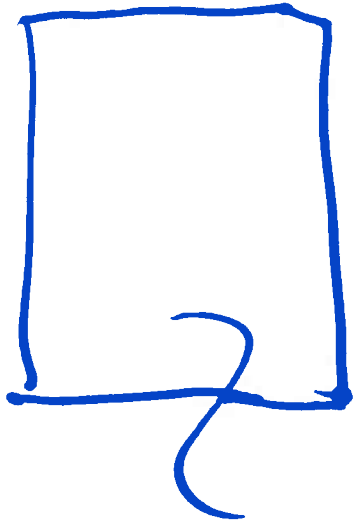


$$\frac{\epsilon \cdot A}{t} = C$$

↑  
FARADS

Capacitive touch

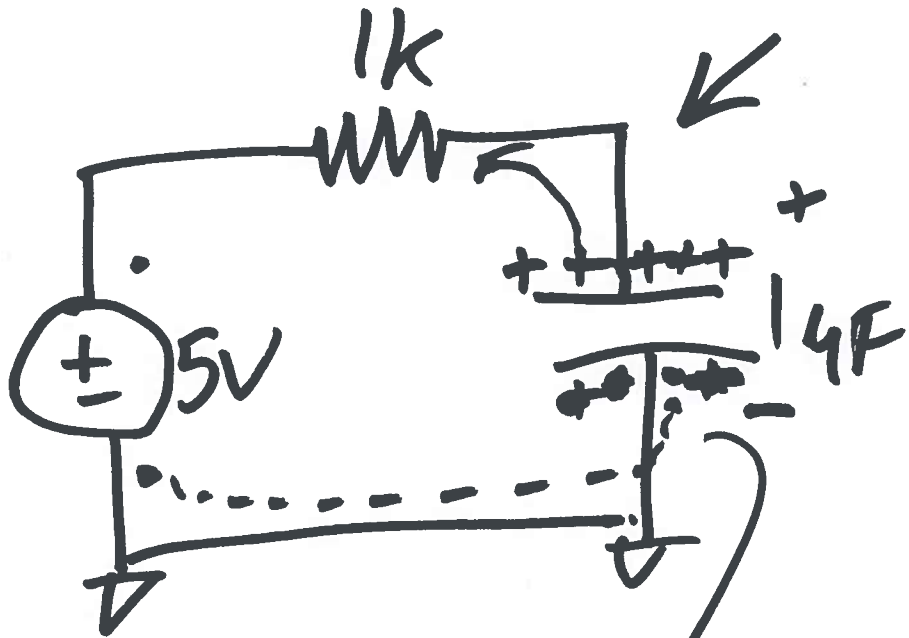- 1  $\mu$ F =  $10^{-6}$  F (Micro)
- 1 nF =  $10^{-9}$  F
- 1 pF =  $10^{-12}$  F (Nano)
- 1 fF =  $10^{-15}$  F (Pico)
- 1 aF =  $10^{-18}$  F (Femto)



CURRENT flows  
IN a CAP  
is displacement  
current




$$Q = C \cdot V$$

↑ capacitance (FARADS) ← voltage

$$Q = 14F \cdot 5V = 54C$$

$$CV = Q$$


Replacing  
R w a capacitor

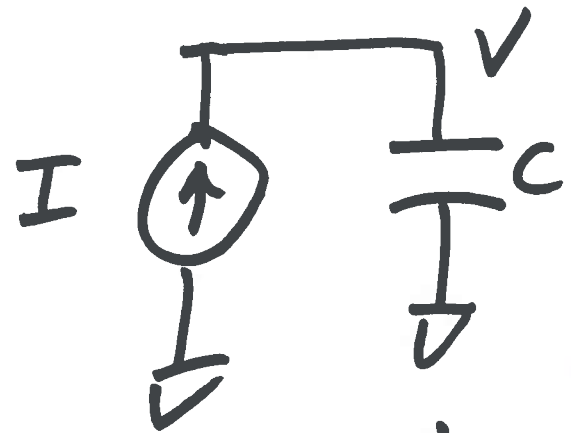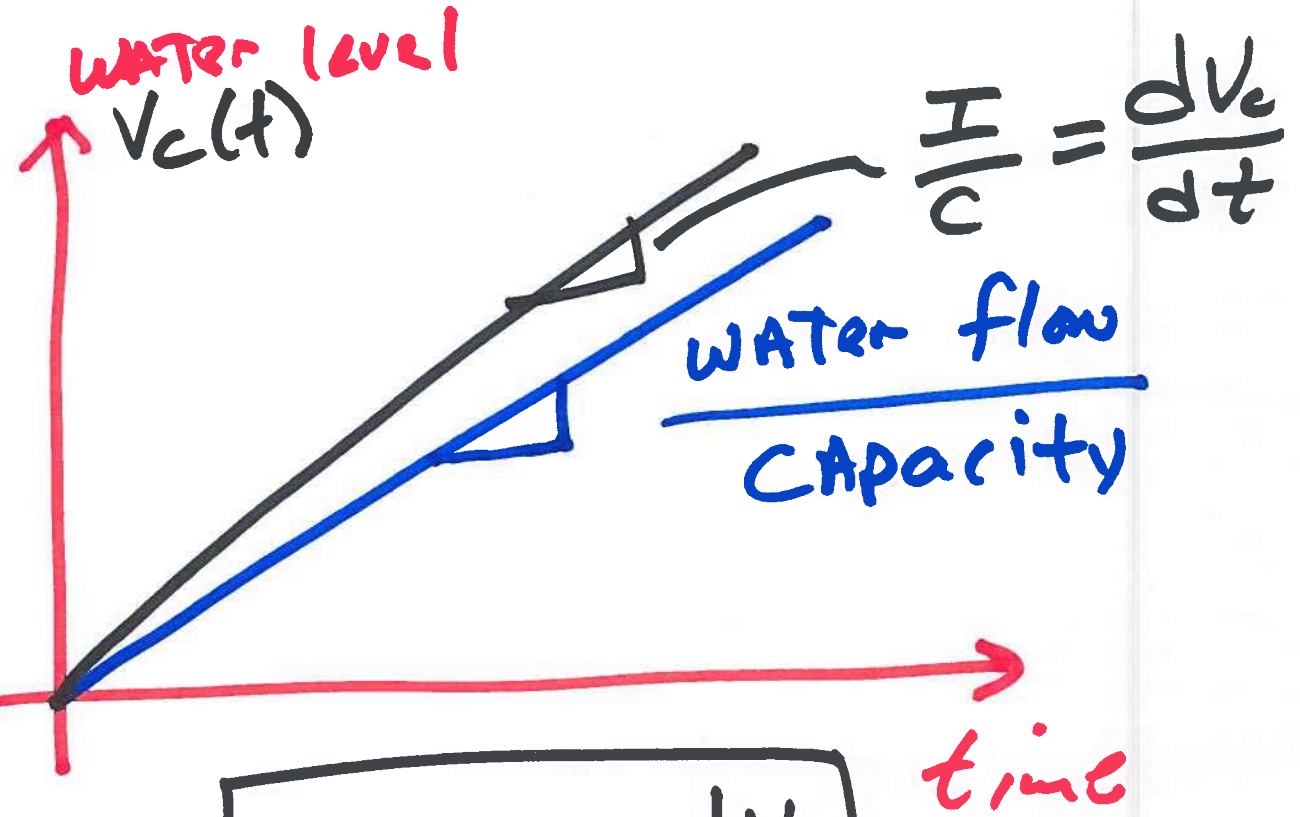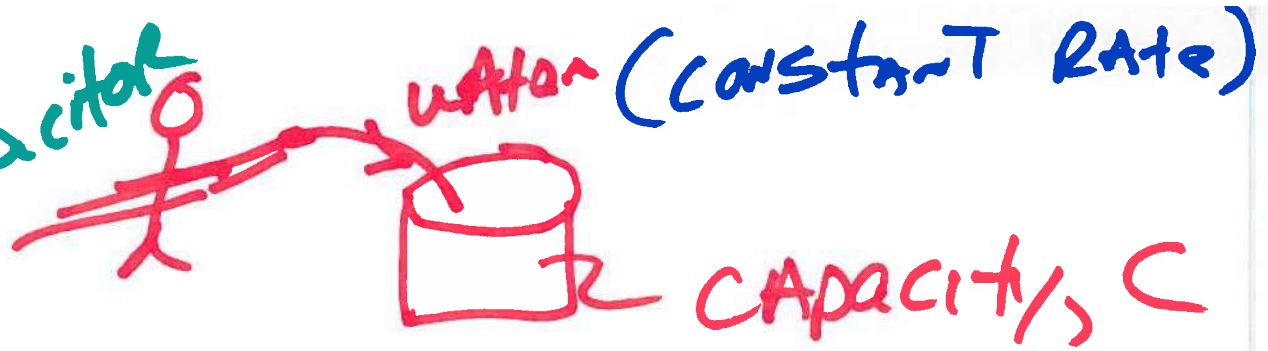

$$V_c = \frac{1}{C} \int_0^t I \cdot dt$$

$$I = C \cdot \frac{dV_c}{dt}$$

4)

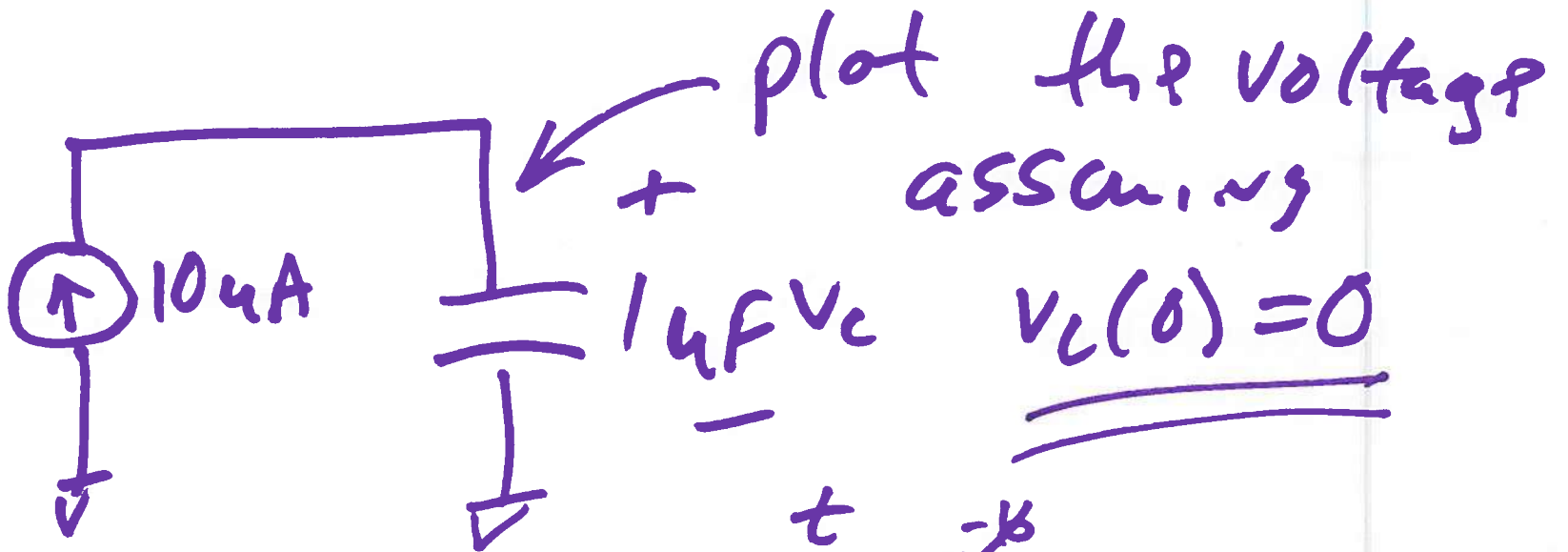


$$V = \frac{1}{C} \int i \cdot dt$$

$$V_c(t) = \frac{1}{10^{-6}} \int_0^{t \cdot 10^{-6}} 10\mu\text{A} \cdot dt$$

$$i = C \frac{dv}{dt}$$

$$C \frac{dv}{dt} = \frac{i}{C} \Rightarrow \frac{dv}{dt}$$

$$V_c(t) = 10 \cdot t \text{ volts}$$

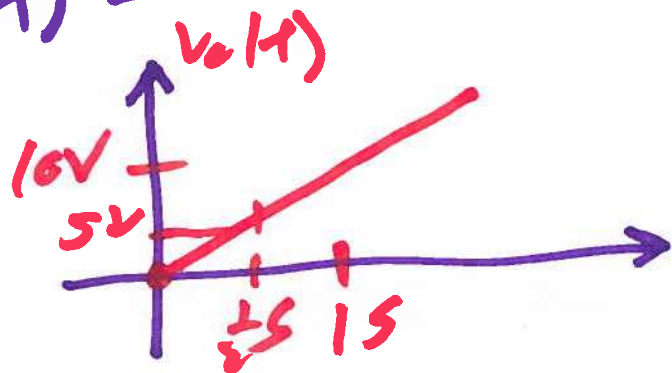

5)


$$CV = Q \leftarrow$$

$$I = C \frac{dv_c}{dt}$$


$$Q = 5 \cdot 14F$$

$$= 54C$$
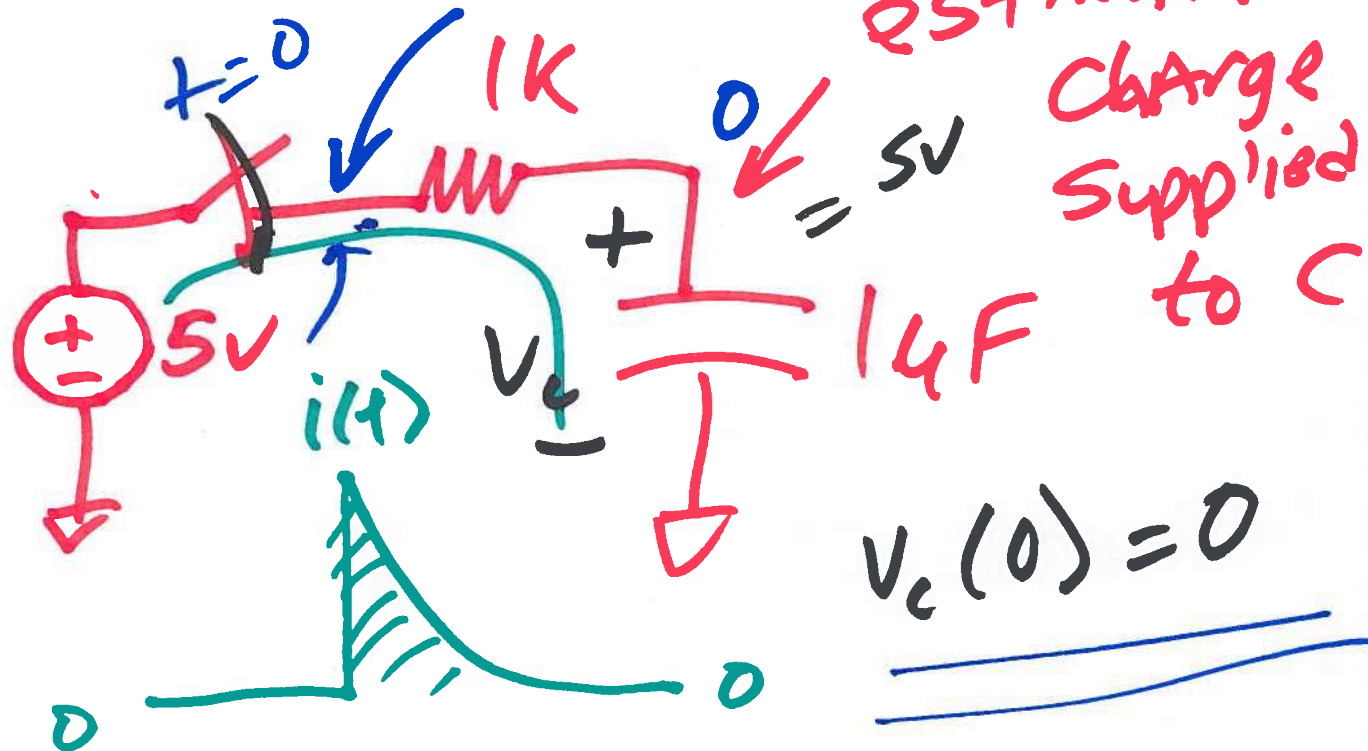
$$v_c = \frac{1}{C} \int_0^t I \cdot dt$$



b)

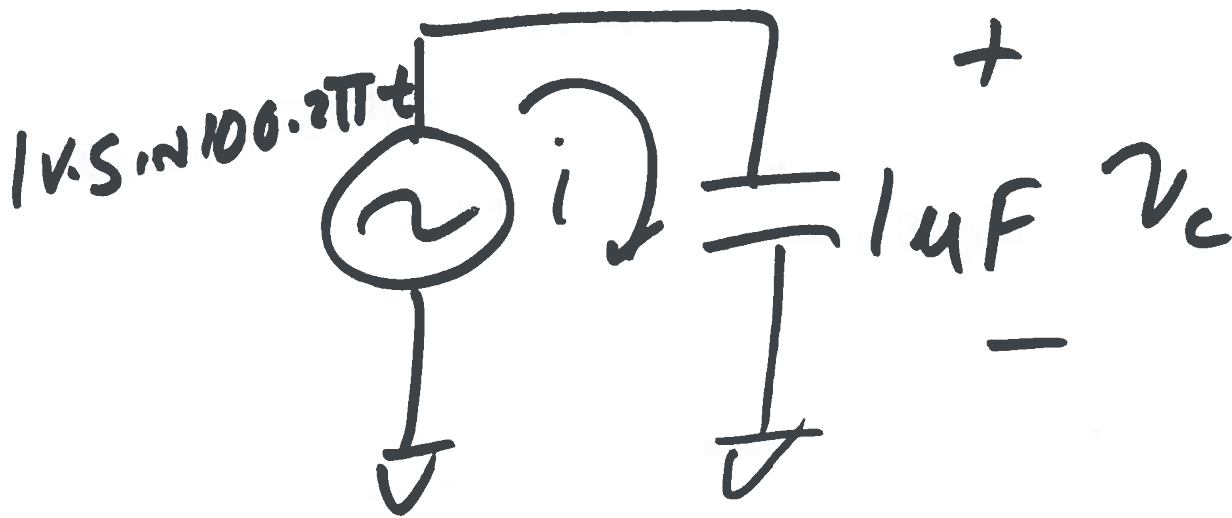

$$\frac{10^{-6}}{10^2} = 10^{-8}$$

$$\frac{1}{2\pi} = .159$$

$$.159 \cdot 10^{-8}$$

$$V_c(t) = 1 \cdot \sin(2\pi 100 \cdot t) \quad 15.9 \cdot 10^{-8}$$

$$15.9 \mu A$$

$$i = 1 \mu F \cdot \frac{d \sin 2\pi 100 \cdot t}{dt}$$

$$6.28 \cdot 10^2 \cdot 10^{-6}$$

$$6.28 \cdot 10^{-4}$$

$$628 \mu A$$

$$i = 10^{-6} \cdot \cos 2\pi \cdot 100 \cdot t$$

$$\frac{10^{-6}}{2\pi}$$

7)