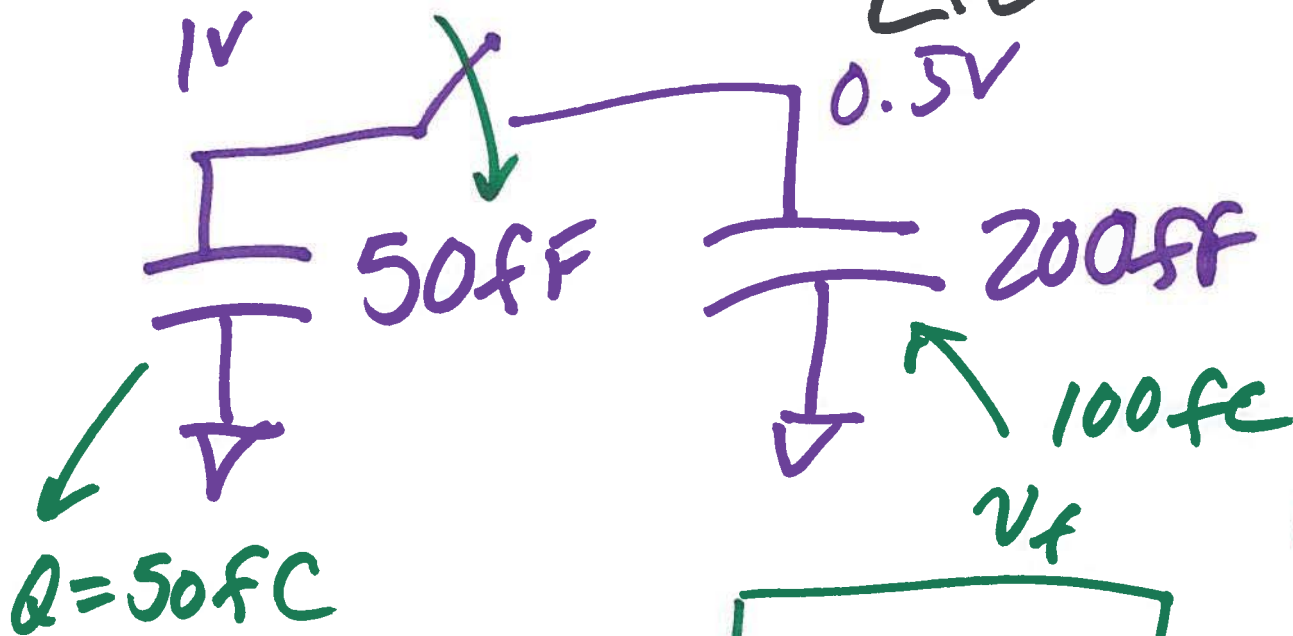


$$CV = Q$$

EE 220 Circuits 1

NOV. 19, 2018

Lecture 23



$$150fF = V_f 250fF$$

$$V_f = \left(\frac{250}{150} \right)^{-1} \left(\frac{5}{3} \right)^{-1}$$

$$\frac{3}{5} = 0.6$$

1)

$$E = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \cdot 50 \text{ fF} \cdot 1^2 + \frac{1}{2} 200 \text{ fF} \cdot 0.5^2$$


$$= 25 \text{ fJ} + 25 \text{ fJ}$$

$$E_{\text{TOTAL}} = 50 \text{ fJ} \leftarrow$$

$$E_{\text{final}} = \frac{1}{2} 250 \text{ fF} \cdot 0.6^2 \text{ (final)}$$

$$= 125 \cdot .36$$

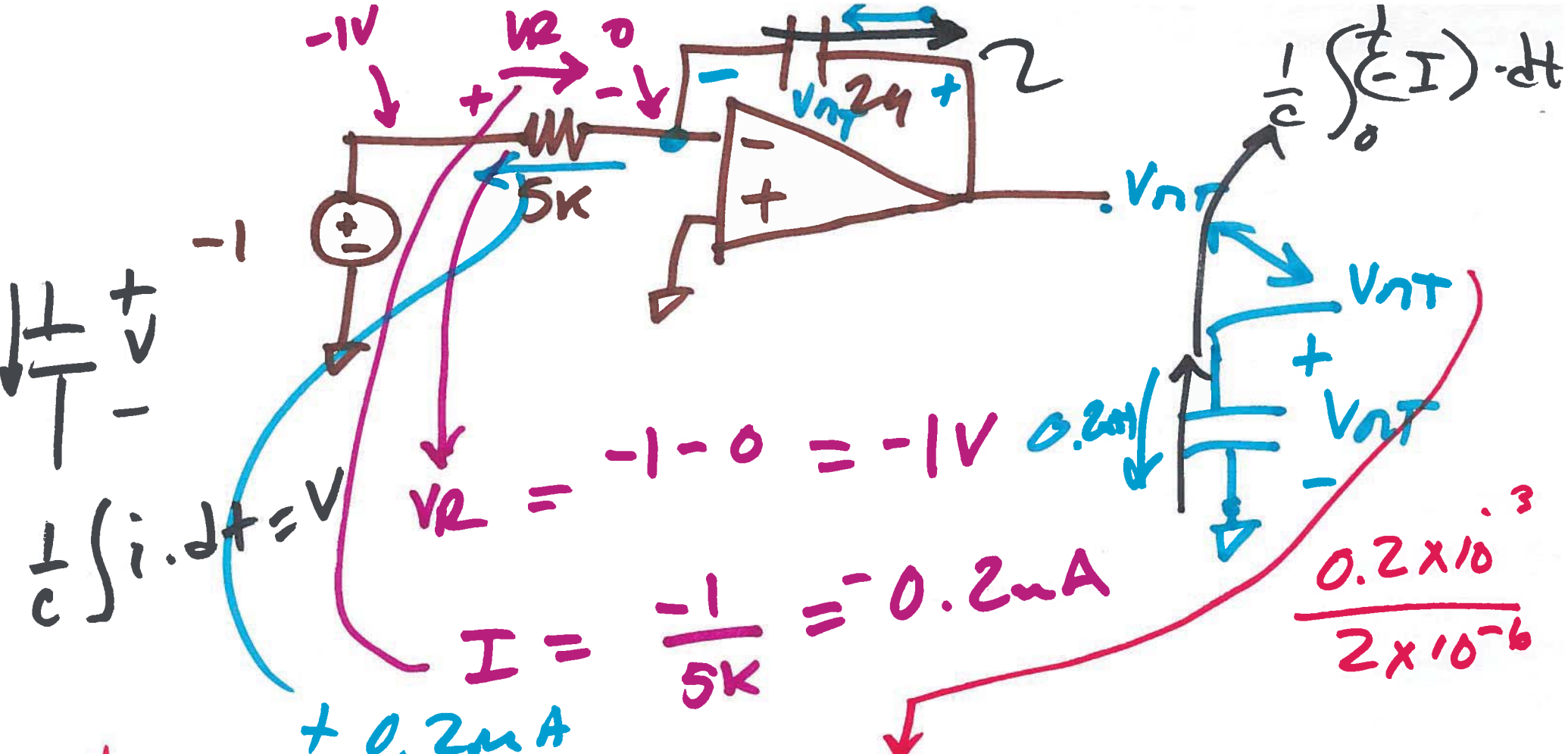
$$= \underline{\underline{45 \text{ fJ}}}$$



$$V_{out} = \frac{1}{C} \int_0^t I \cdot dt = \frac{1}{C} 0.2\mu A \cdot t$$


$$= 1000 t$$

3)

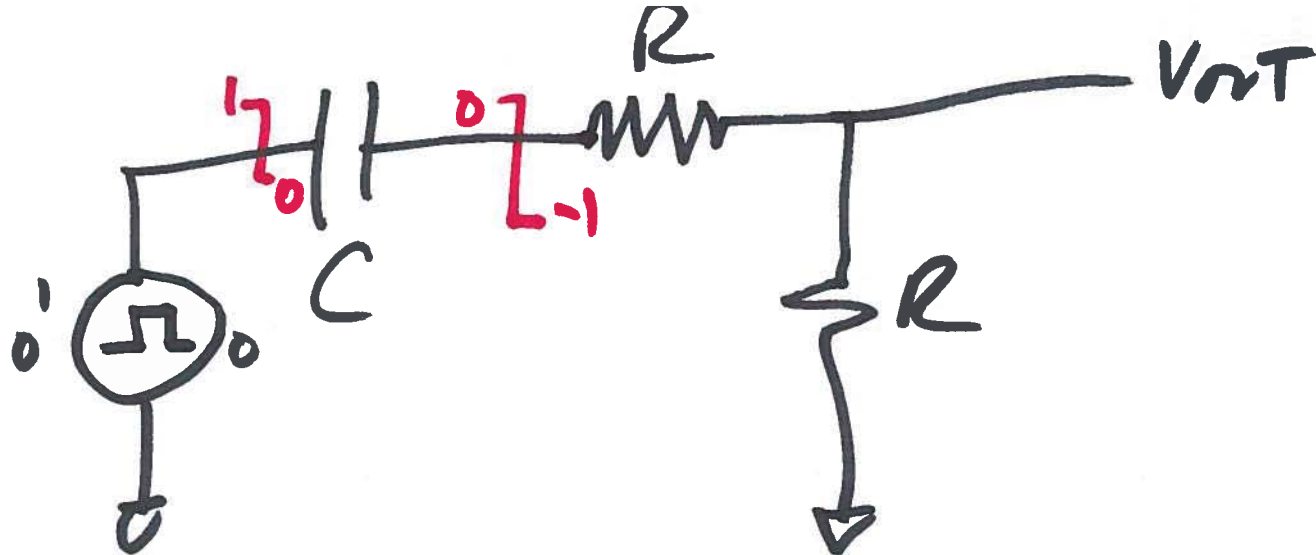


$T \gg RC$

$\tau = 2R \cdot C$

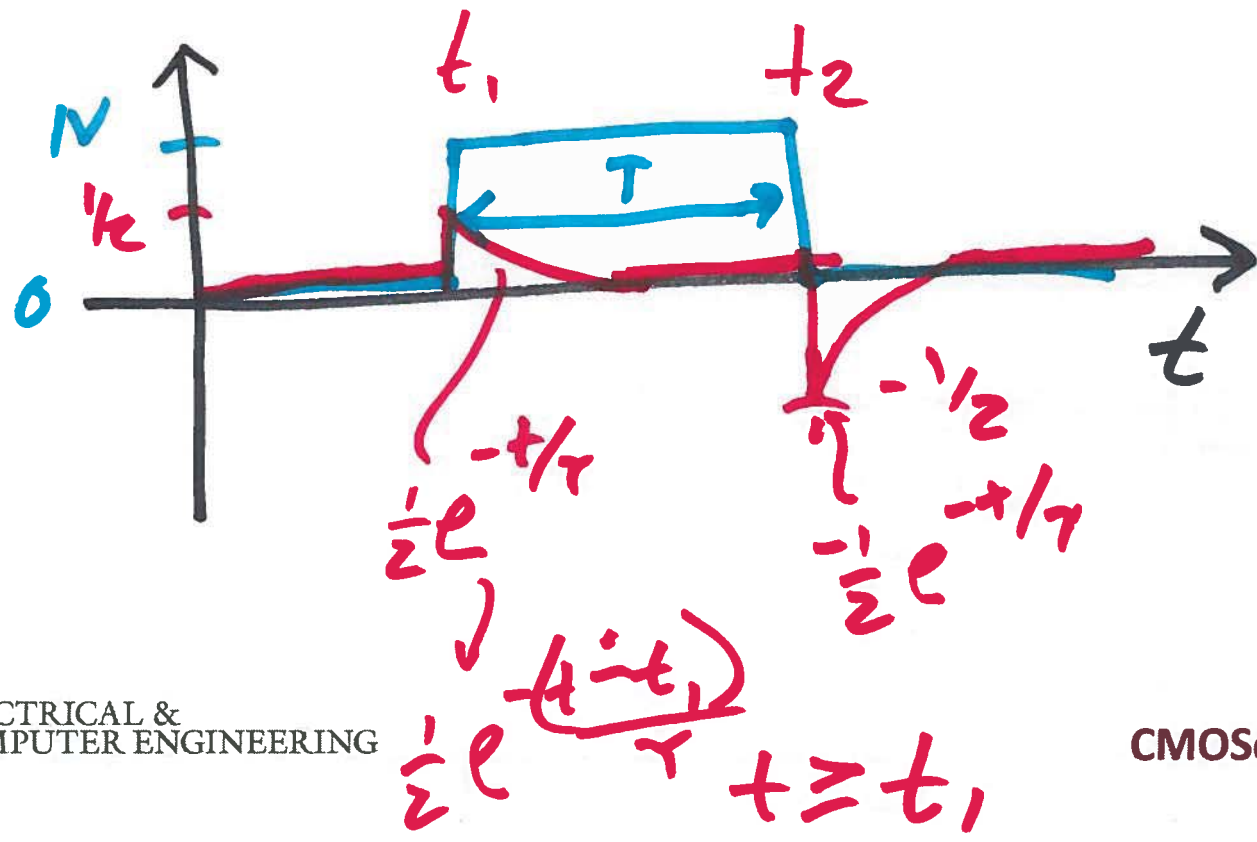


4)

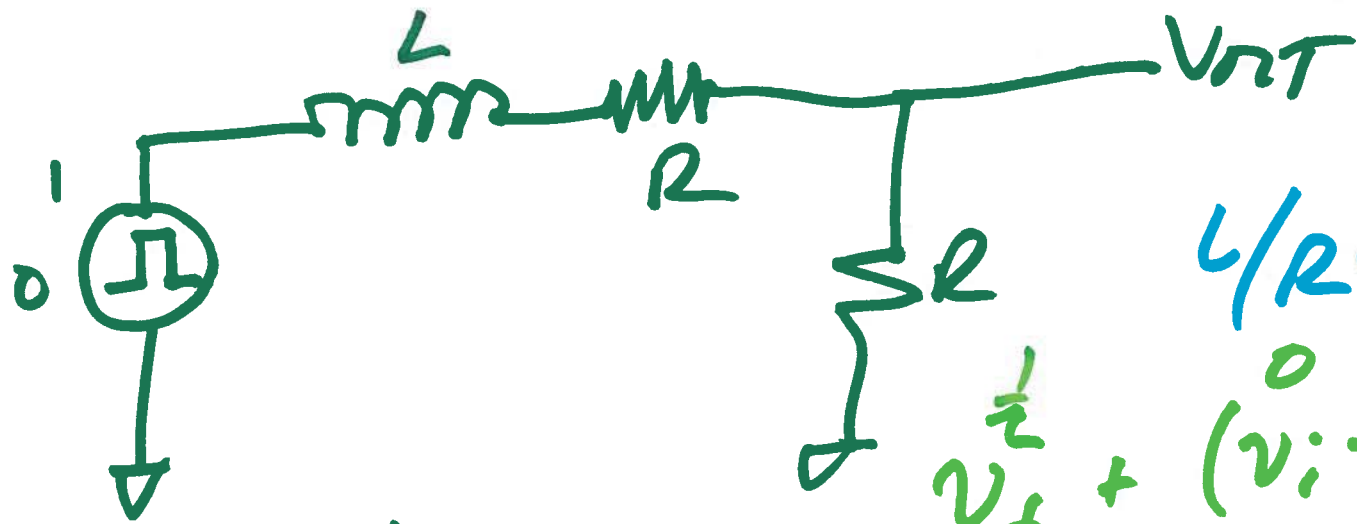

$$L/R \cdot 2 = \tau$$

$$v_f + (v_i - v_f)e^{-t/\tau}$$

$$T \gg \frac{L}{2R}$$

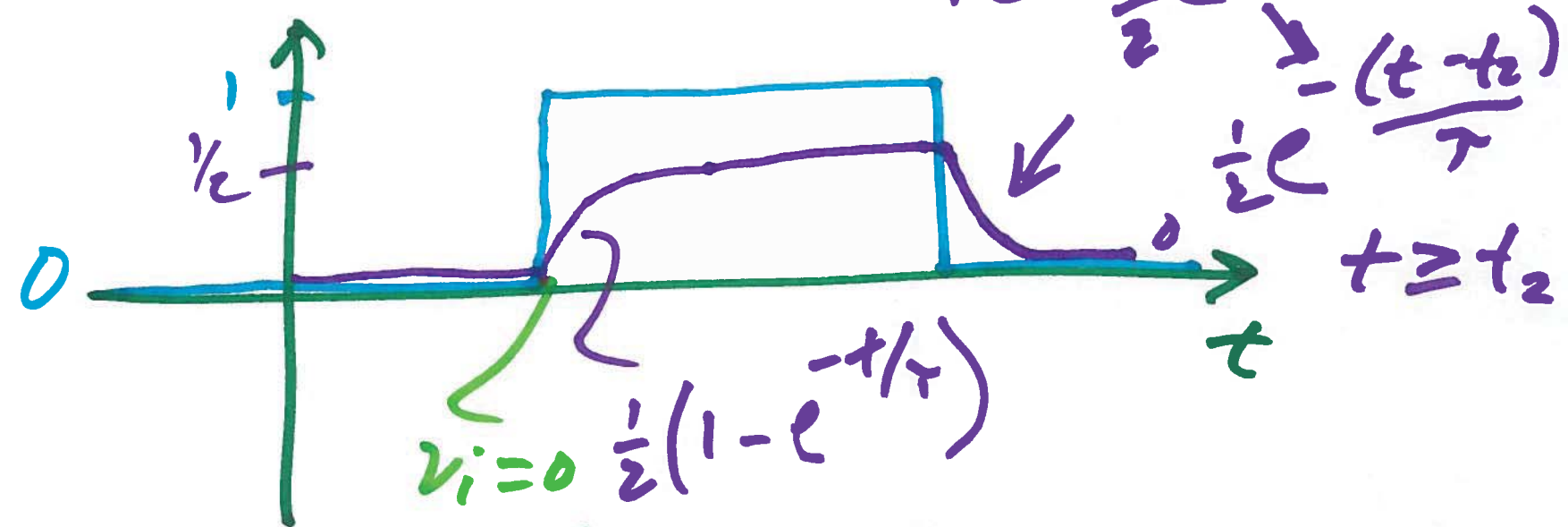


$$v_i = 0 \quad \frac{1}{2}(1 - e^{-t/\tau})$$


$$v_f = \frac{L}{2}$$

5)

Root Mean Square (RMS)

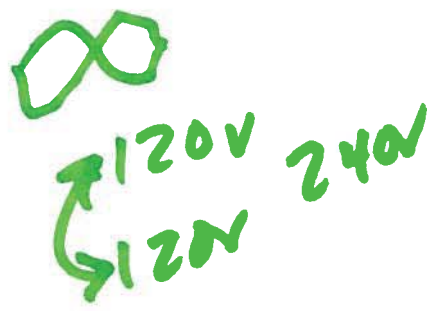

→ 120V
→ ± 5%
114 → 126V

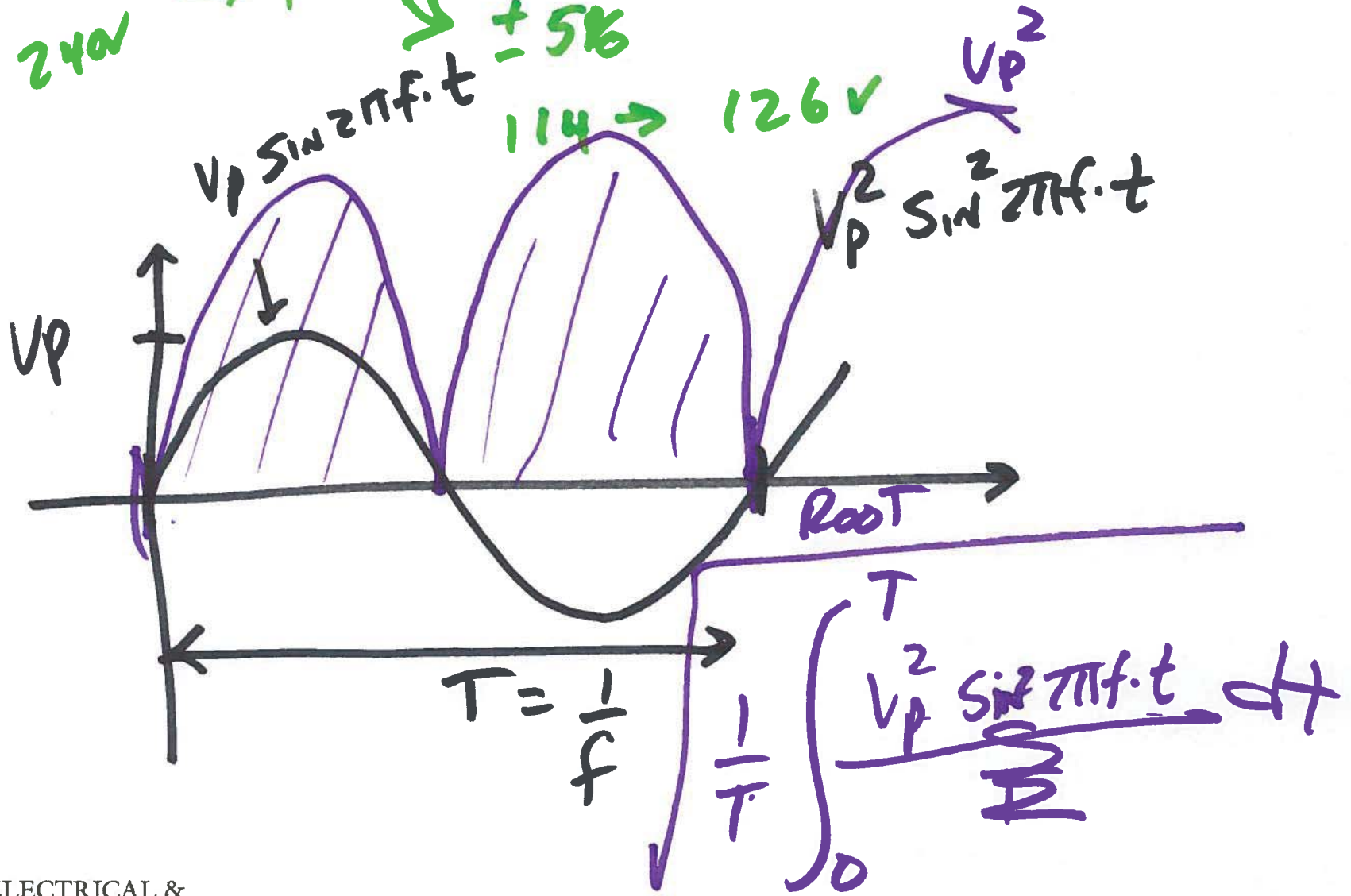

6)

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T V_P^2 \sin^2 2\pi f t \cdot dt}$$

$$= \sqrt{\frac{V_P^2}{2T} \int_0^T (1 - \cos 4\pi f t) dt}$$

$V_P = \sqrt{2} \cdot V_{RMS}$
 $= \sqrt{2} \cdot 120V$
 $\approx 170V$

peak-to-peak


$$= \sqrt{\frac{V_P^2}{2T} \left[\int_0^T dt - \int_0^T \cos 4\pi f t \cdot dt \right]}$$



$f = \frac{1}{T}$


$$V_{RMS} = \frac{V_P}{\sqrt{2}}$$

1)

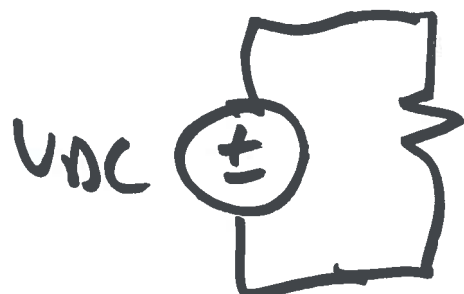

$$P_R = \frac{V_{DC}^2}{R} = I^2 R$$

$$I = \frac{V_{DC}}{R}$$

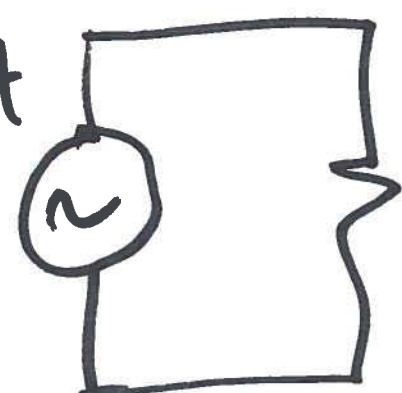

$$R, P_R = \frac{V_{RMS}^2}{R}$$

$$V_{RMS} = \frac{V_P}{\sqrt{2}}$$

$$\frac{1}{T} \int_0^T V_{DC}^2 \cdot dt = V_{DC}^2$$

$$\sqrt{\cancel{\frac{1}{T}} \cdot \cancel{\int_0^T} \cdot V_{DC}^2} = V_{DC}$$

9)