
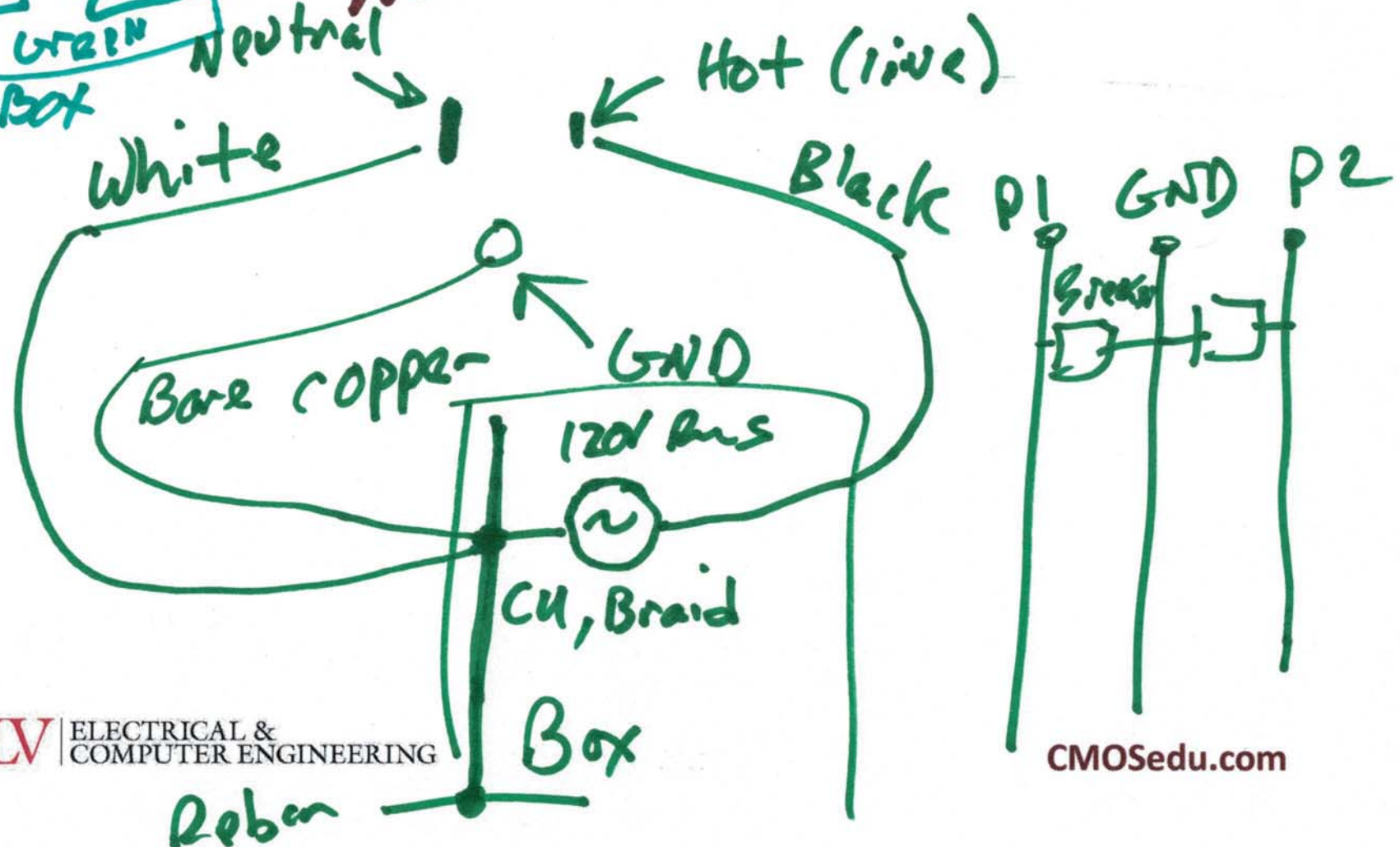





# EE 220 circuits 1

+240  
Lecture 25


NOV. 26, 2018

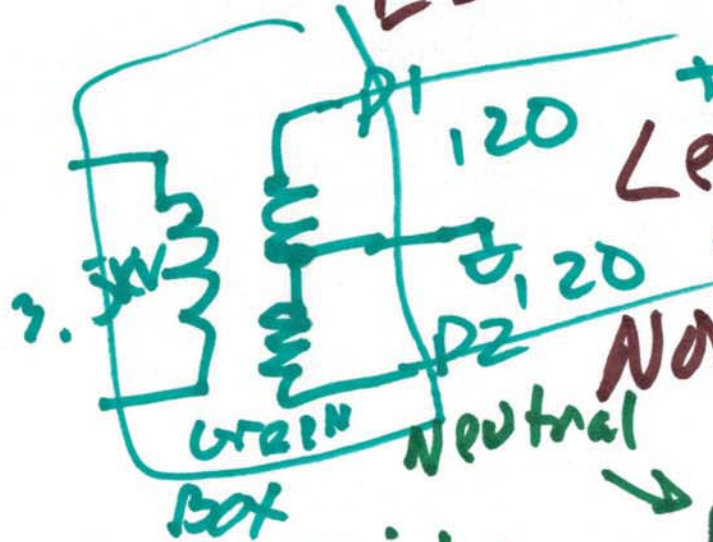

1)

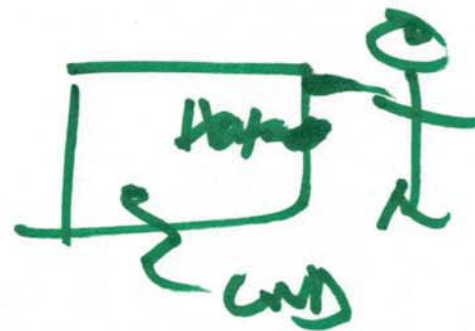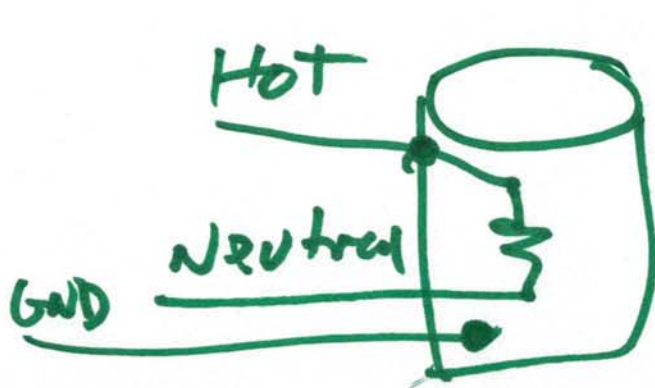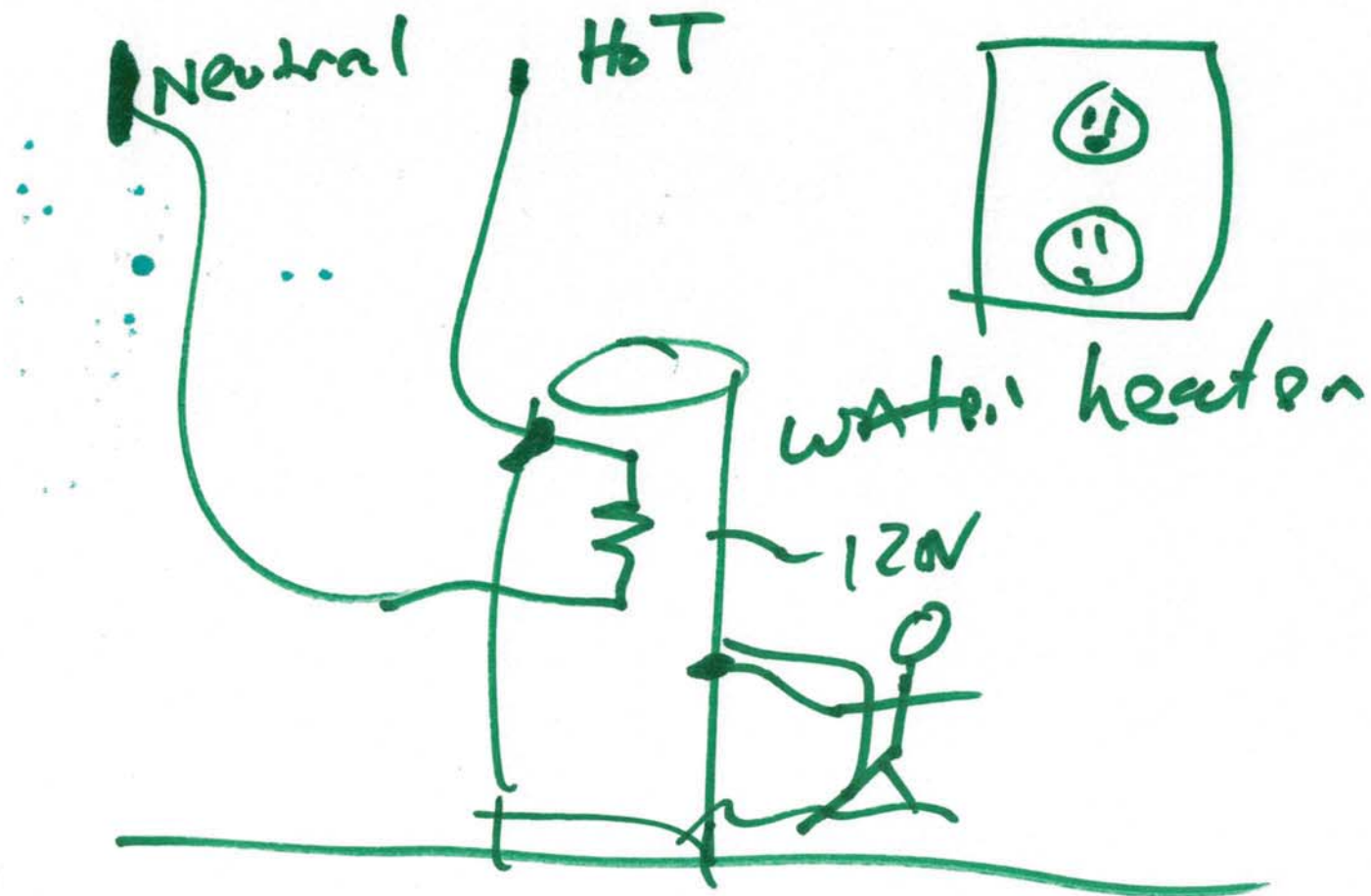


2)

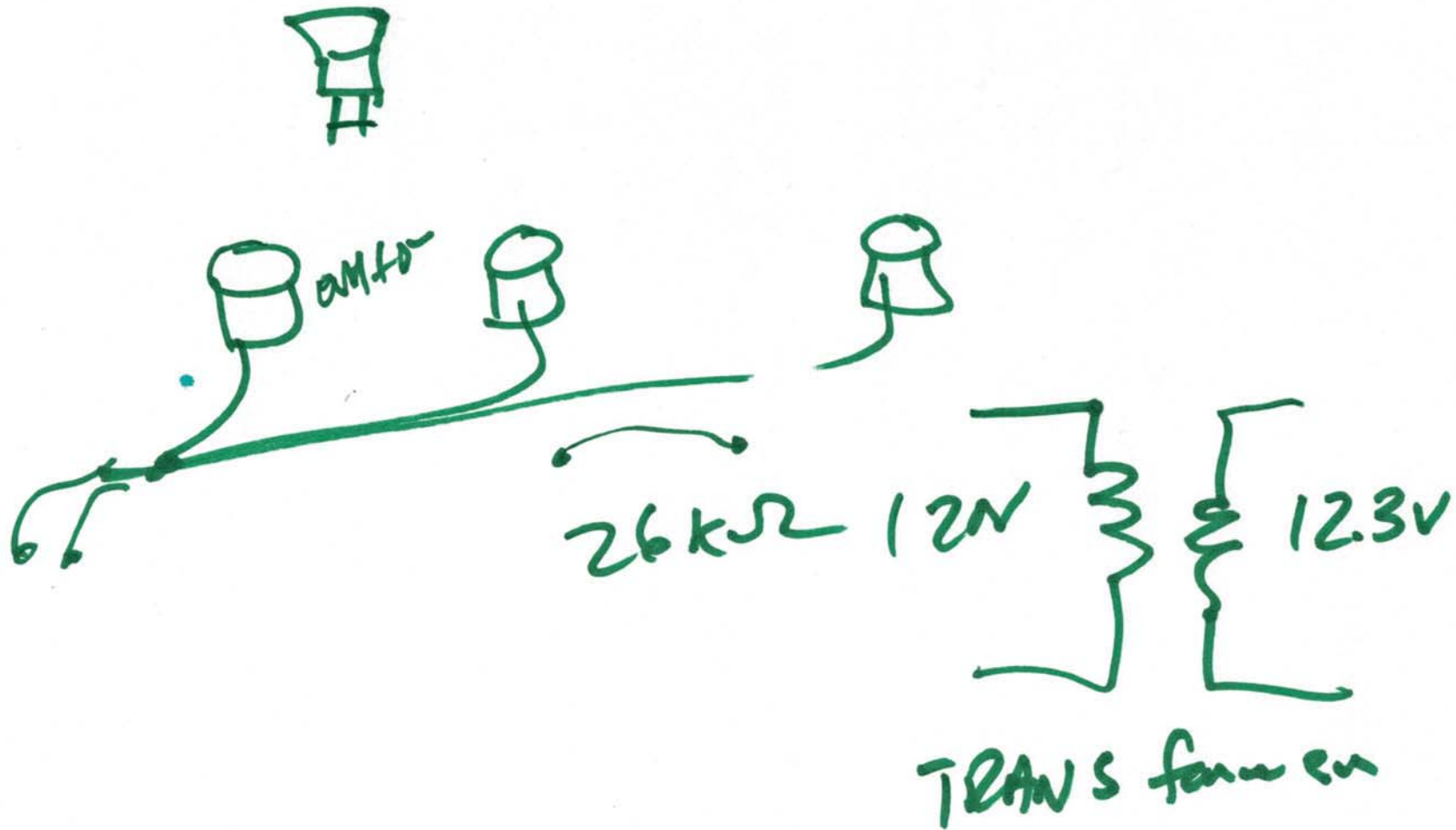

3)

# frequency response

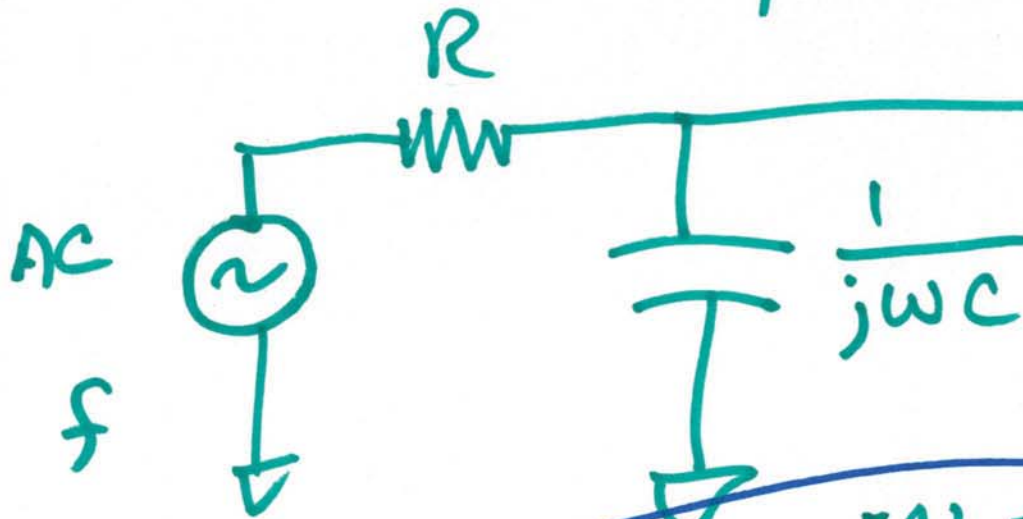

$$V_{out} = V_{in} \cdot \frac{1}{j\omega C}$$

$$\frac{1}{j\omega C} + R$$

$$\frac{1 + j\omega R C}{1 + j\omega R C}$$

$$\left\{ \frac{V_{out}}{V_{in}} \right\} =$$

$$\frac{1 + j\omega R C}{\sqrt{1^2 + \omega^2 R^2 C^2}}$$

$$\Rightarrow \left| \frac{V_{out}}{V_{in}} \right| =$$

$$\frac{1}{\sqrt{1 + \left(\frac{f}{x}\right)^2}}$$

LO  
 $\angle \tan^{-1} 2\pi f R C$  transfer function

$$20 \log \frac{1}{\sqrt{2}} = 20 \log .707 =$$

$$\angle \tan^{-1} 2\pi f R C - 3dB$$

$$x = \frac{1}{2\pi R C}$$

4)


$$y\text{-Axis in dB} = 20 \log \frac{v_{out}}{v_{in}}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = -7 \text{ dB} \quad f = 2 \text{ kHz}$$

$$\angle \frac{v_{out}}{v_{in}} = -15^\circ$$

$$v_{in} = 1$$
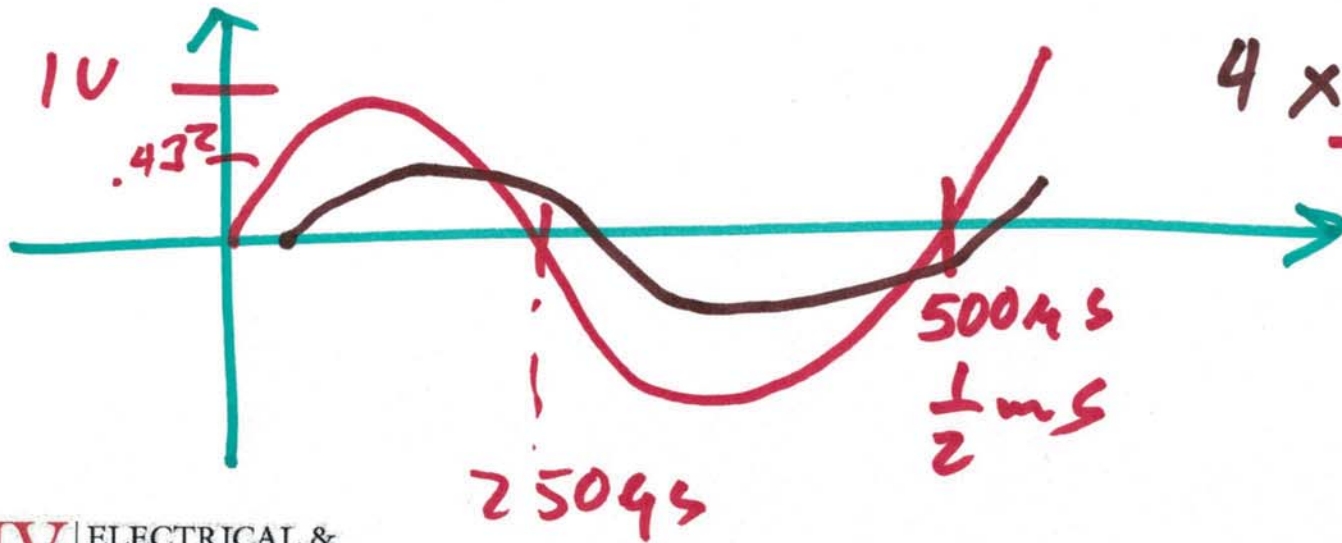
$$v_{in} = 1 \quad -7 = 20 \log \frac{v_{out}}{1}, \quad v_{out} = 1 \cdot 10^{-7/20}$$



$$4 \times .446 = .360$$

$$-15^\circ = \frac{t_d}{500 \text{ ns}}$$

$$t_d = 20.83 \text{ ns}$$

$$\times 4$$

5)