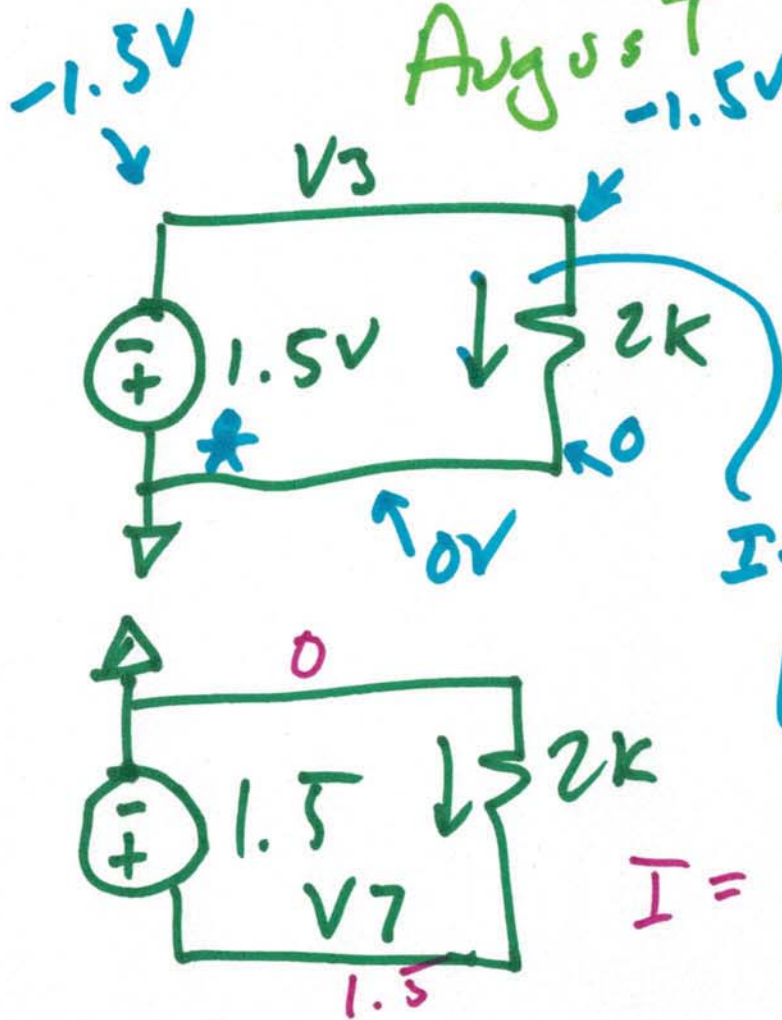


EE 220 Circuits 1

August 29, 2018
Lecture 2




$$I = \frac{-1.5 - 0}{2k} = \frac{V_1 - V_2}{R}$$

$$\boxed{I = -750\mu A}$$

$$I = \frac{0 - 1.5}{2k} = \underline{\underline{-750\mu A}}$$

1)

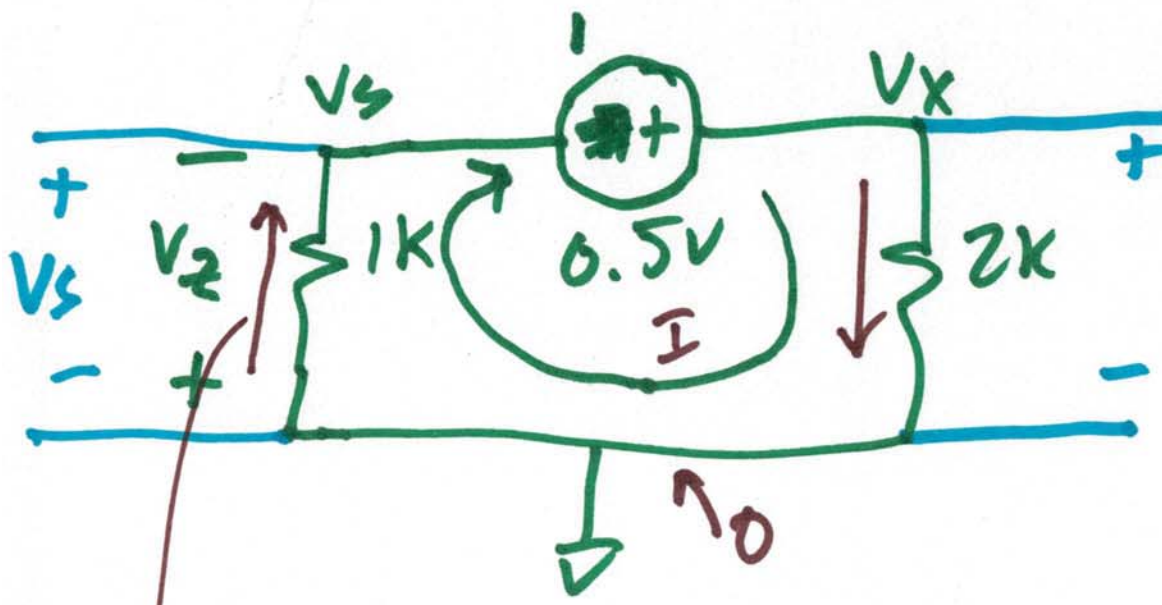

$$0.5 = V_x - V_s$$

$$I = \frac{V_x - 0}{2k}$$

$$V_x = I \cdot 2k$$

$$V_s = -I \cdot 1k$$

$$V_2 = 0 - V_s = -V_s$$

$$I = \frac{0 - V_s}{1k} = -\frac{V_s}{1k}$$

$$V_x = .166mA \cdot 2k = 333mV$$


$$V_s = -167mV = -.166mA \cdot 1k$$

$$0.5 = I \cdot 2k - (-I \cdot 1k)$$

$$I = \frac{0.5}{3k} = \frac{1}{6}mA = .1667mA$$

2)

Voltage divider

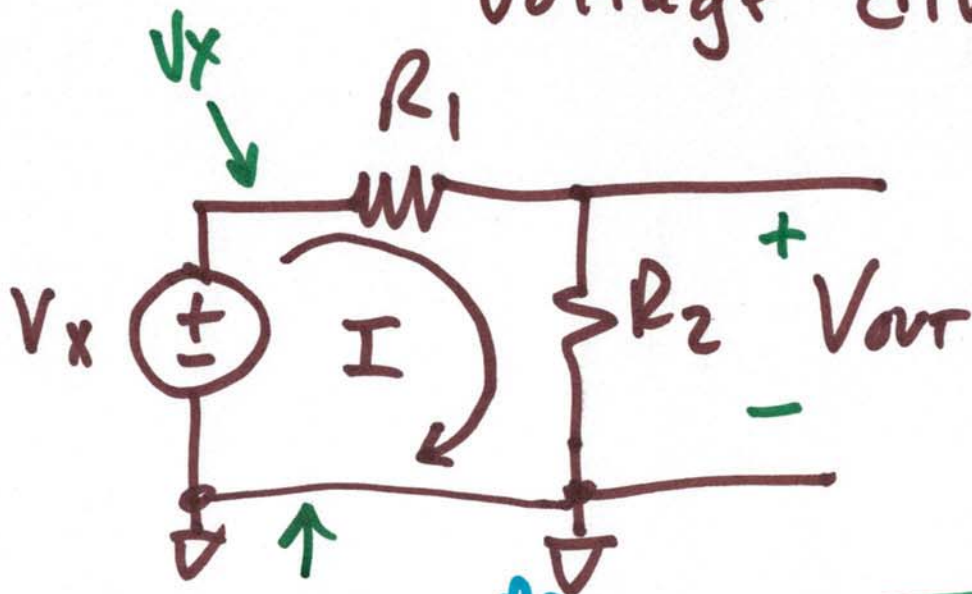


$$I = \frac{V_x - 0}{R_1 + R_2}$$

$$V_{out} = I \cdot R_2$$

$$V_{out} = V_x \cdot \frac{R_2}{R_1 + R_2}$$

Voltage divider equation

$$= V_{in} \cdot \frac{R_0}{R_0 + R_1}$$

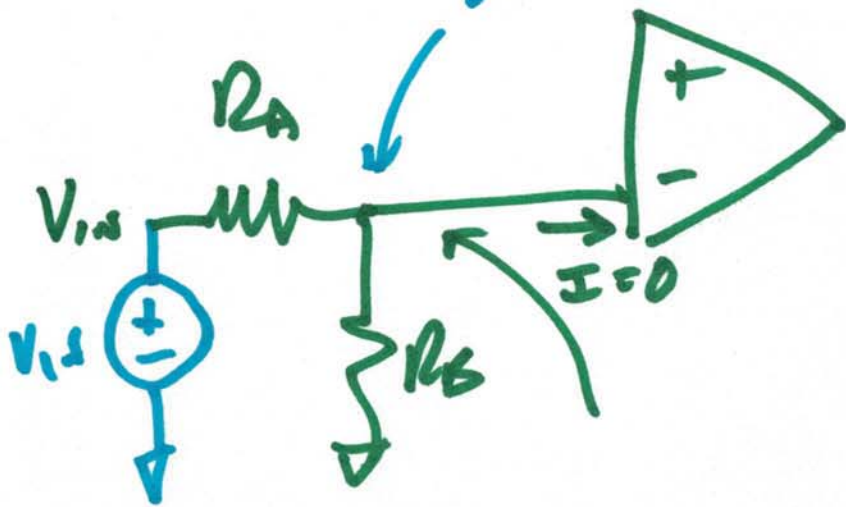


3)

Resistors in Series



$$B = \frac{X_1 \cdot X_2}{X_1 + X_2}$$

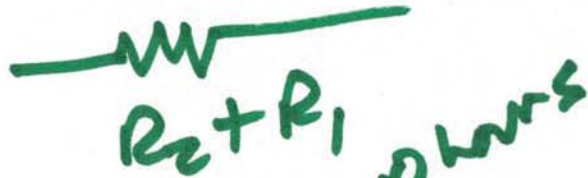

$$\frac{1 \text{ pol}}{20 X_1} + \frac{1 \text{ pol}}{10 X_2} = \frac{1}{B}$$



$$\frac{1 + 2}{20} = \frac{1}{B}$$


$$B = \frac{20}{3} = 6.67 \text{ Hg}$$

$$R = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

CMOSedu.com

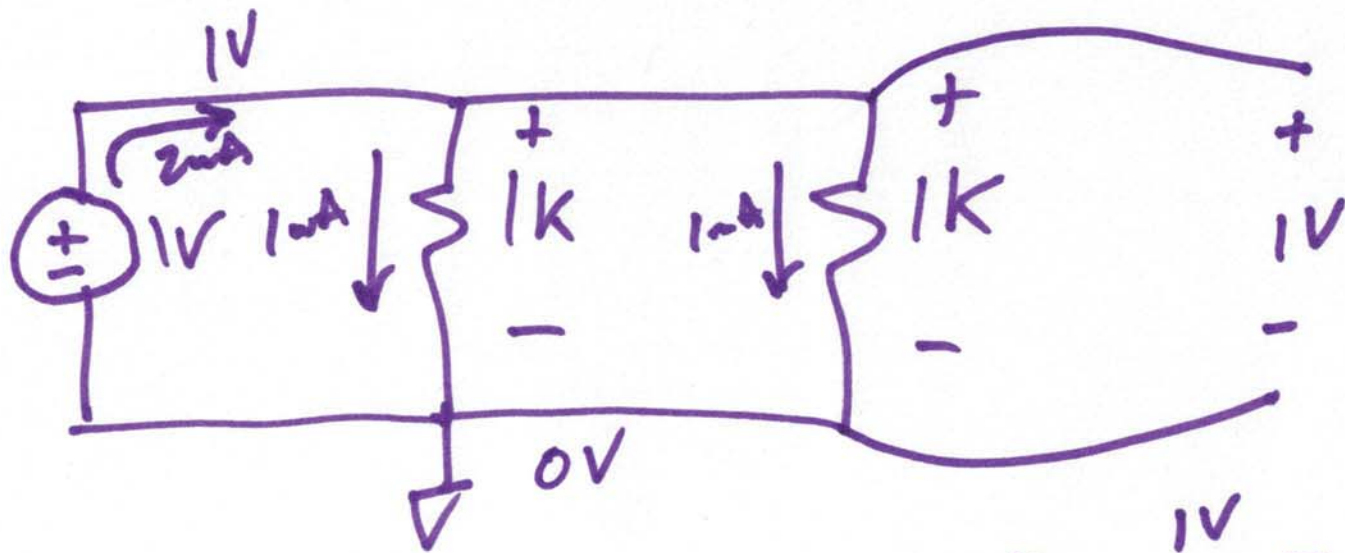


$$\frac{R_1 \cdot R_2}{R_1 + R_2} = R_{EQ} = 1k \parallel 1k = \frac{1k \cdot 1k}{1k + 1k} \quad \frac{1V}{1k} = 1mA$$


$$= 500\Omega$$

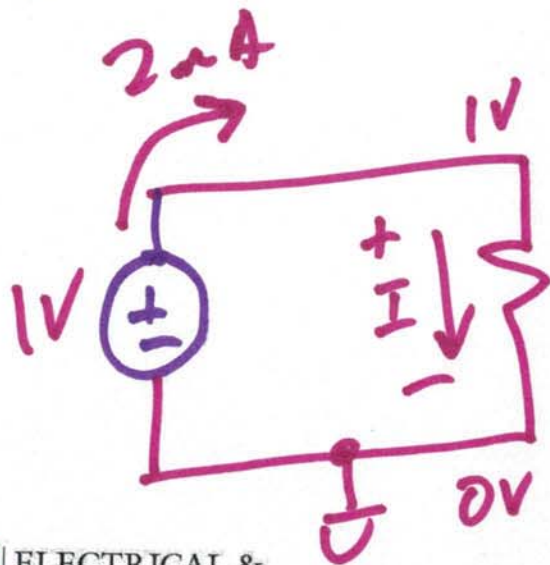

$$I = \frac{1 - 0}{500} = 2mA$$

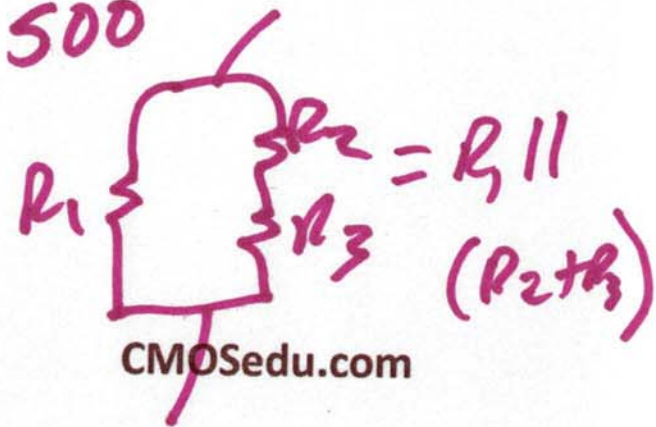

CURRENT divider

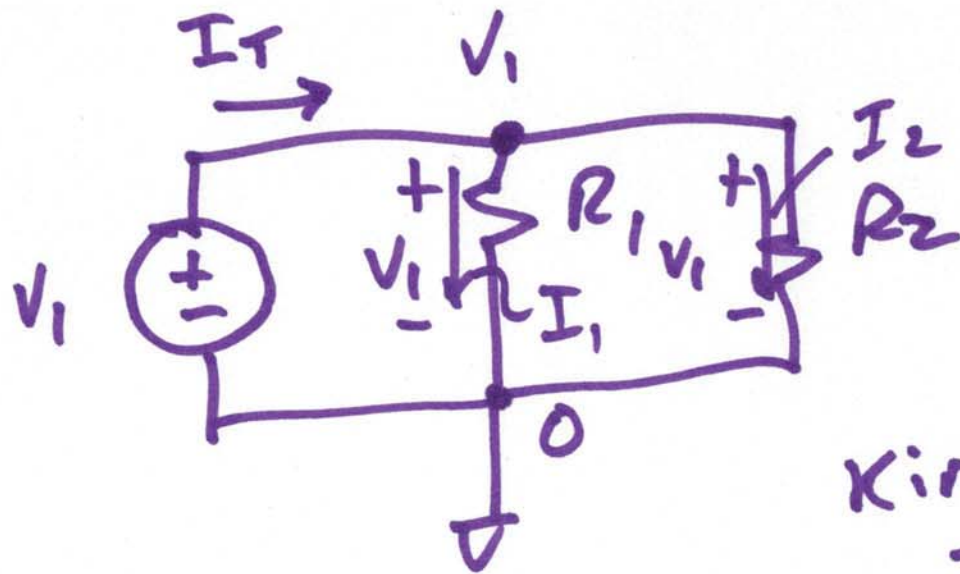

$$I_1 = \frac{V_1 - 0}{R_1}$$

$$I_2 = \frac{V_1 - 0}{R_2}$$

Kirchoff's current law

$$I_T = I_1 + I_2$$


$$I_2 = I_T - I_1$$

$$\frac{V_1}{R_2} = \frac{V_1}{R_1 \parallel R_2} - \frac{V_1}{R_1}$$

$$= \frac{V_1}{R_1 \parallel R_2}$$

$$R_1 \parallel R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2}$$
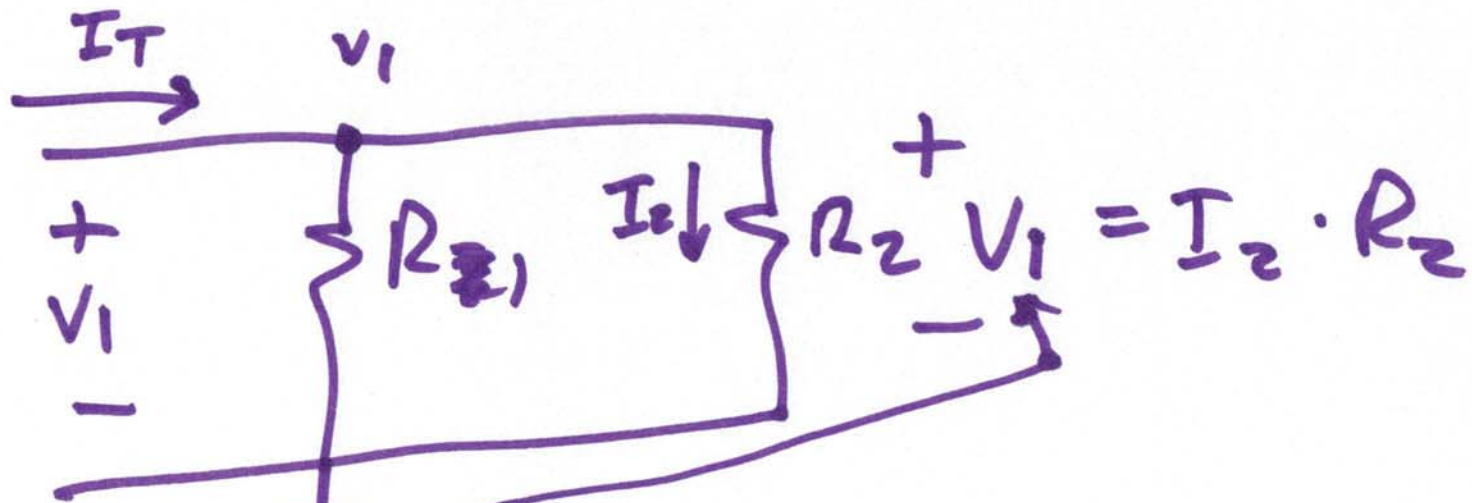
$$I_2 = I_T \cdot \frac{R_1}{R_1 + R_2}$$




$$V_1 = I_T \cdot \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$I_2 = I_T \cdot \frac{R_1}{R_1 + R_2}$$

current divider

1)

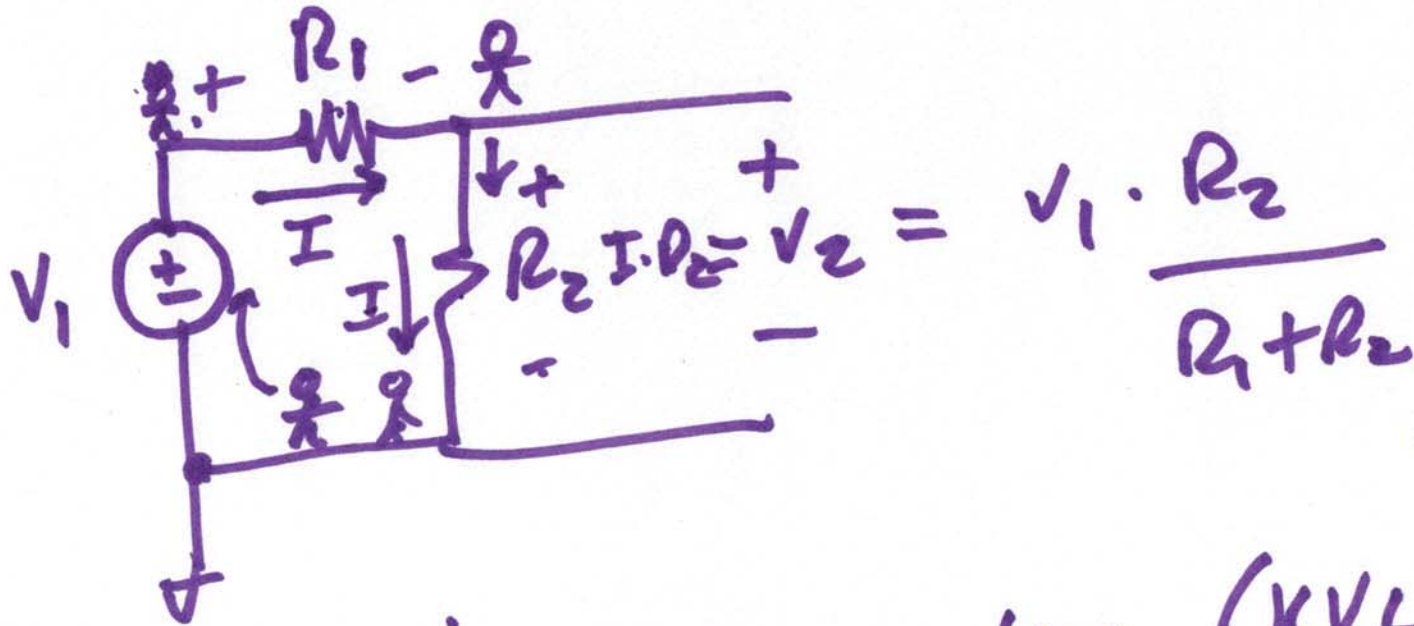

Kirchoff's voltage law (KVL)

$$V_1 - I \cdot R_1 - I \cdot R_2 = 0$$

$$V_1 = I \cdot (R_1 + R_2)$$

$$V_2 = I \cdot R_2$$

$$V_2 = V_1 \cdot \frac{R_2}{R_1 + R_2}$$