


EE 220

Circuits 1

Lecture 6

Sept. 14, 2018

$$3kI_1 + 1kI_2 + 1.5 = 0$$

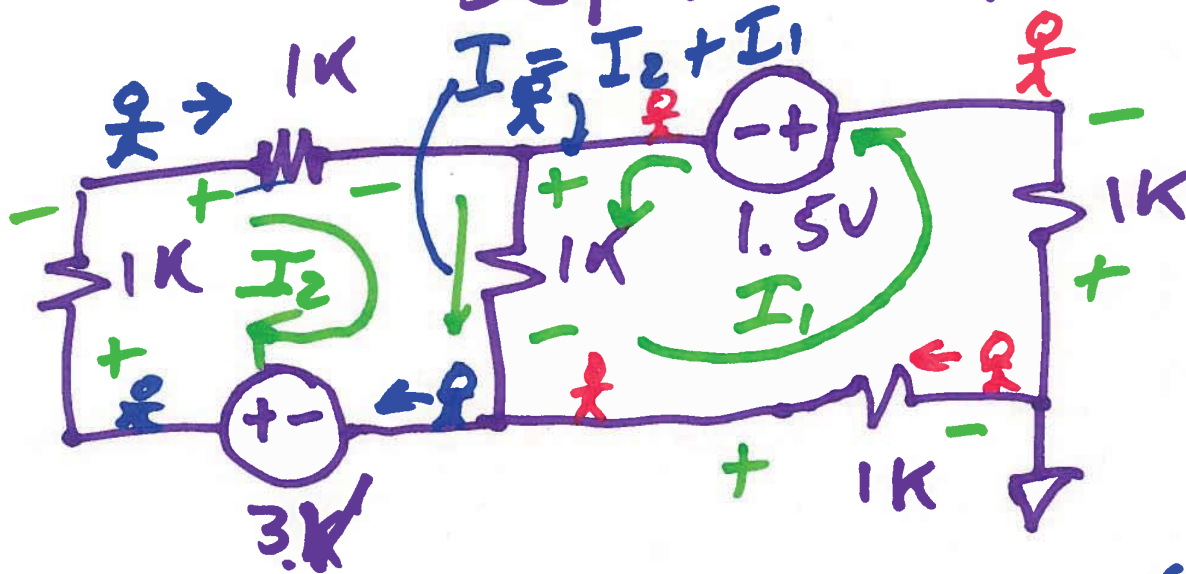

$$I_1 \cdot 1k + (I_2 + I_1)1k + 1.5 + I_1 \cdot 1k = 0$$

$$0 = -I_2 \cdot 1k - 1k(I_2 + I_1) + 3 - 1k \cdot I_2$$

$$0 = -3kI_2 + 3 - 1kI_1 \quad \text{CMOSedu.com}$$

1)

$$I_1 = -3I_2 + 3 \text{ mA}$$


$$\downarrow$$
$$3kI_1 + 1kI_2 + 1.5 = 0$$

$$-9kI_2 + 9V + 1kI_2 + 1.5 = 0$$

$$-8kI_2 = -10.5$$

$$I_2 = \frac{10.5}{8k}$$
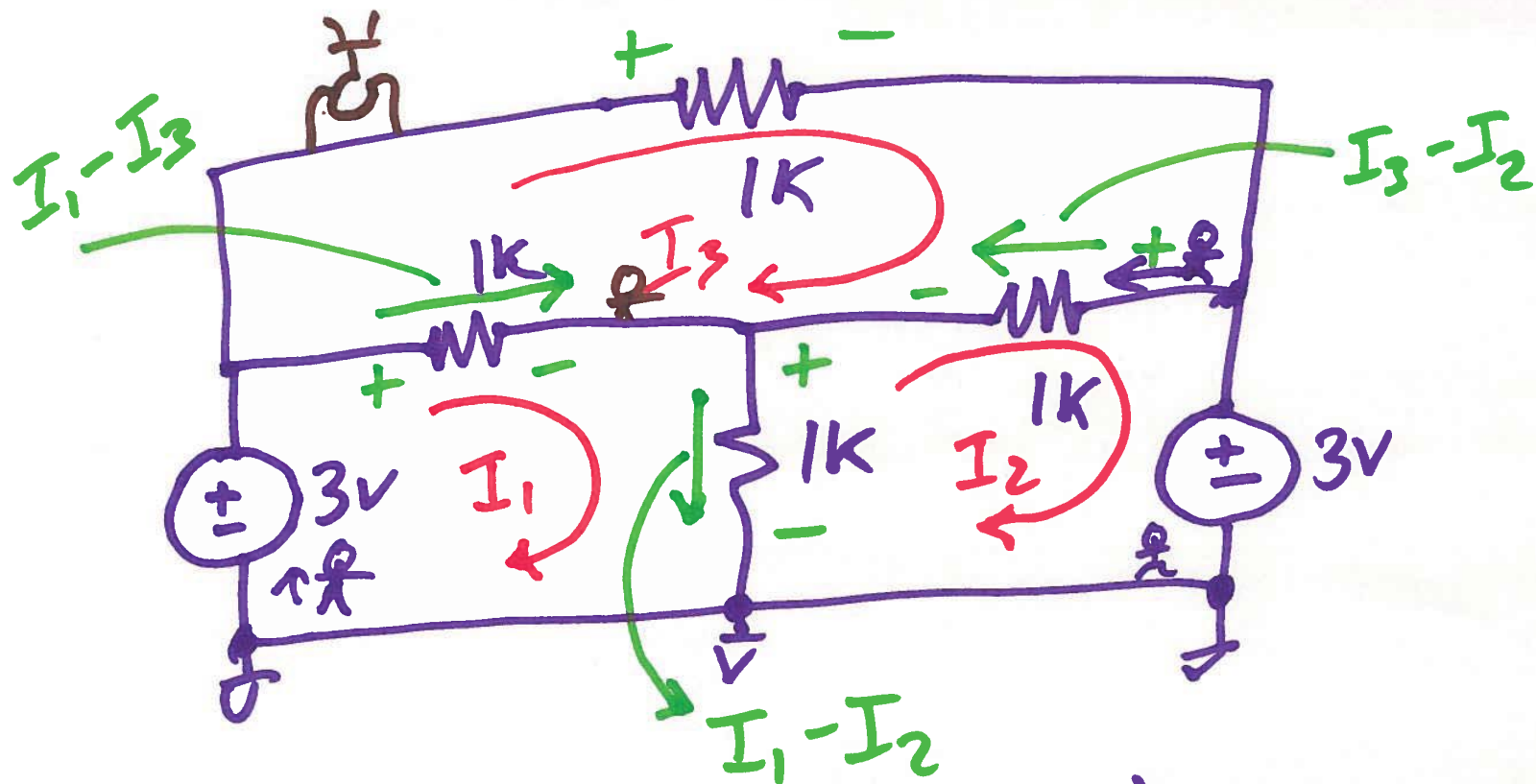
$$I_1 = \frac{-31.5}{8k} + 3 \text{ mA}$$



$$3 - 1k(I_1 - I_3) - 1k(I_1 - I_2) = 0$$

$$3 - 1k(I_3 - I_2) - 1k(I_1 - I_2) = 0$$

$$-1k \cdot I_3 - 1k(I_3 - I_2) + 1k(I_1 - I_3) = 0$$

$$-3I_3 + I_2 + I_1 = 0$$

$$3\text{mA} - 2I_1 + I_2 + I_3 = 0$$

$$3\text{mA} - I_1 + 2I_2 - I_3 = 0$$

$$I_1 + I_2 - 3I_3 = 0$$

$$I_1 = 3I_3 - I_2$$

$$3\text{mA} + 3I_2 - 5I_3 = 0$$

$$-(3\text{mA} + 3I_2 - 4I_3 = 0)$$

$$-I_3 = 0$$

$$\boxed{I_3 = 0}$$


$$3\text{mA} - I_1 - 2I_1 = 0$$

$$\boxed{I_1 = 1\text{mA}}$$

$$I_1 = I_2 =$$

$$\boxed{I_2 = -1\text{mA}}$$

THEVENIN'S THEOREM

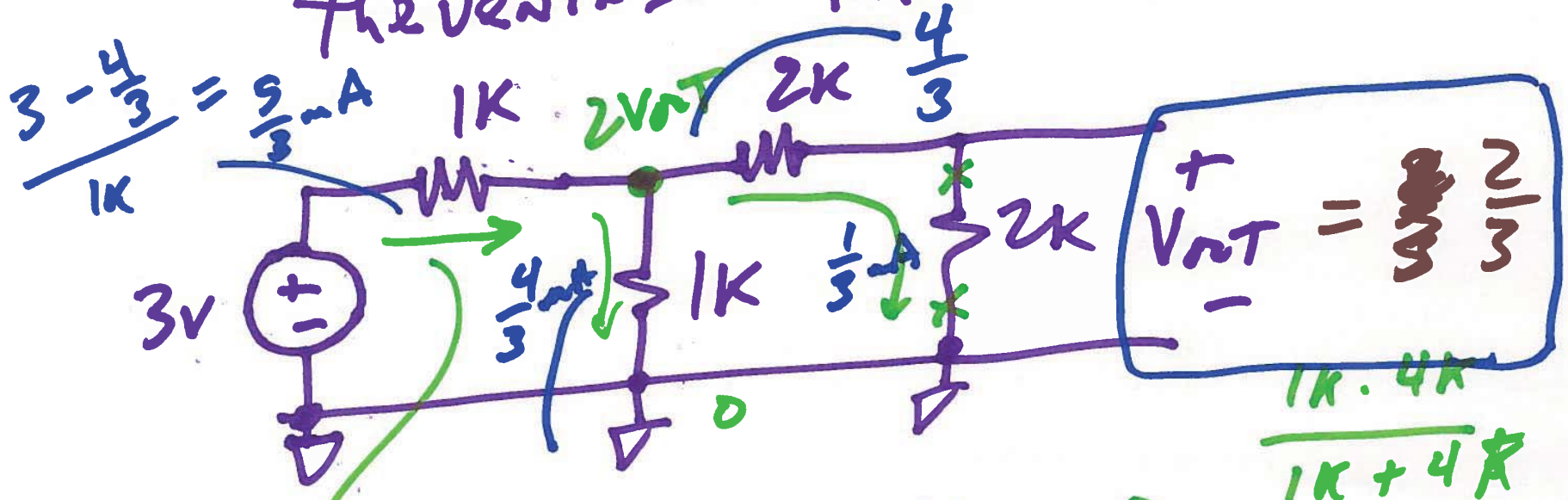

$$\frac{3 - 2V_{th}}{1\text{k}} = \frac{2V_{th} - 0}{1\text{k} \parallel 4\text{k}} = 800\Omega$$


$$3 - 2V_{th} = \frac{1,000}{800} (2V_{th})$$

$$\frac{2}{3} = \frac{2 \cdot 15}{3 \cdot 15}$$


$$3 - 2V_{th} = 2.5V_{th}$$

$$V_{th} = \frac{3}{4.5} = \frac{3 \cdot 10}{45} = \frac{30}{45} = \frac{2}{3}$$


5)

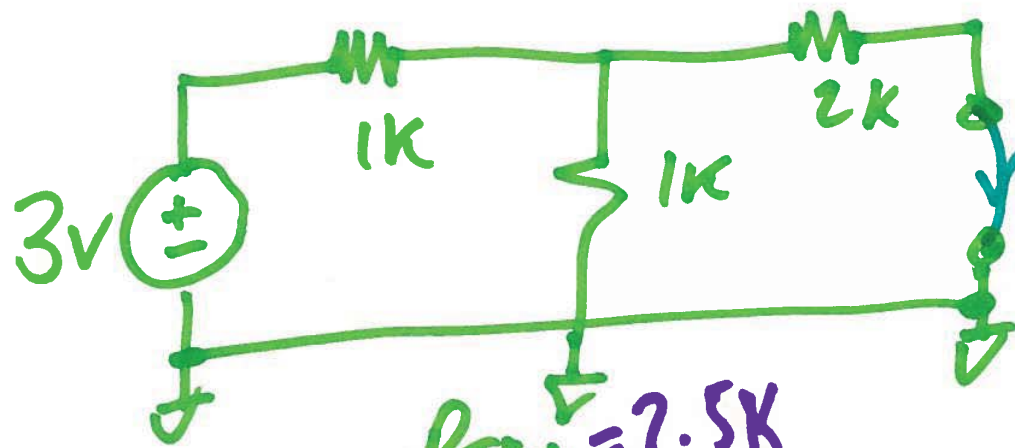

$R_{TH} = 2.5k$

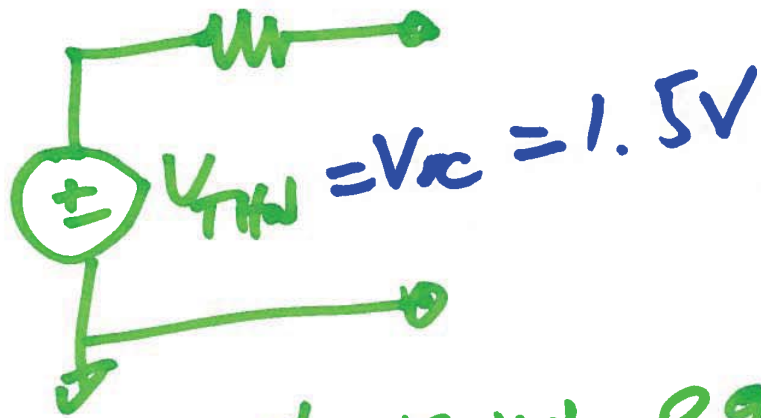


Thevenin equivalent!

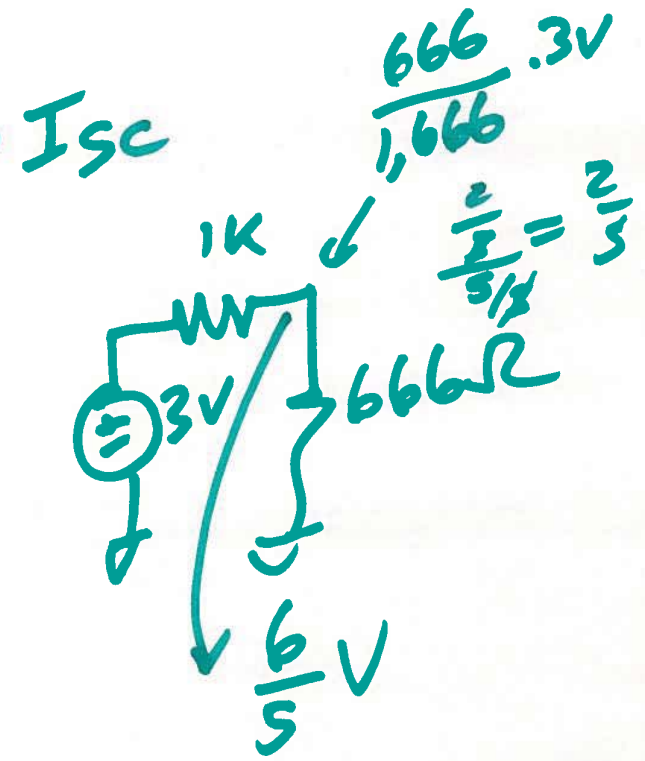

$$I_{sc} = \frac{6/5}{666} = \frac{6/5}{\frac{2}{3}k} = \frac{9}{5} \mu A$$

b)

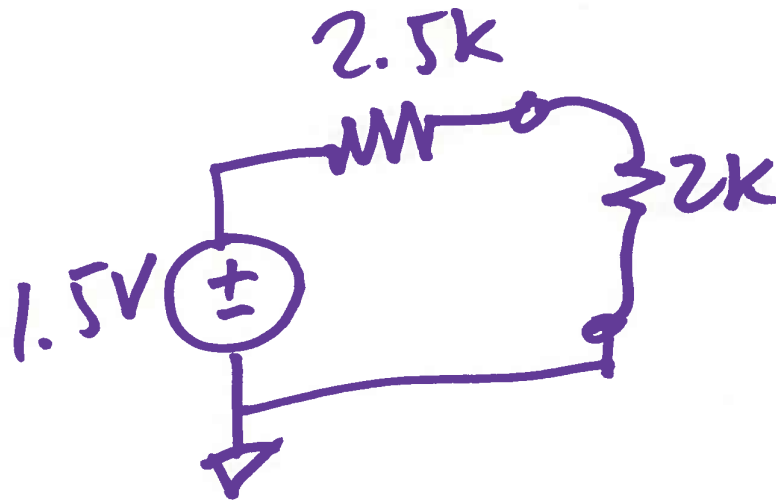


$$V_{th} = 1.5 \cdot \frac{2k}{2k + \frac{5k}{2}}$$

$$= 1.5 \cdot \frac{4}{9}$$

$$= \frac{3}{2}$$

NOYTON EQUIVALENT

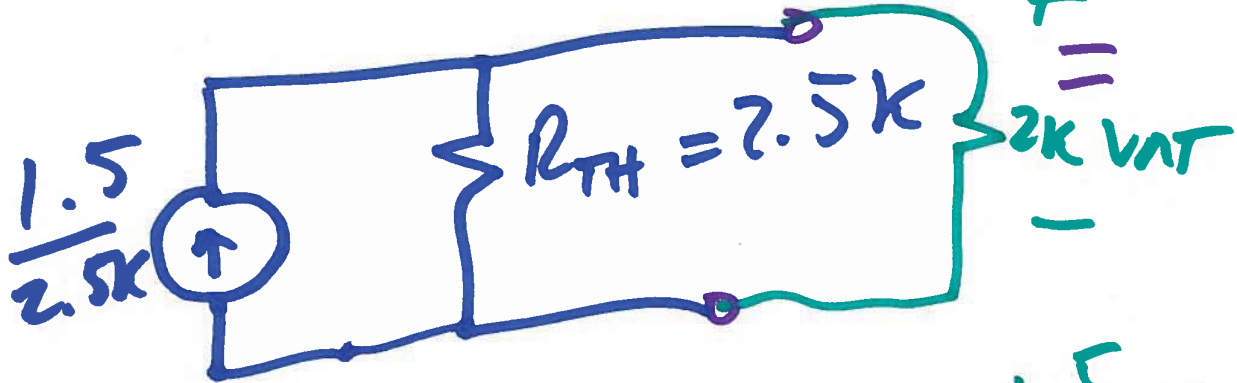

$$V_{th} = \frac{1.5}{2.5k} \cdot \frac{2k \cdot 2.5k}{2k + 2.5k}$$

$$= \frac{12}{18} = \frac{2}{3} V$$

7)