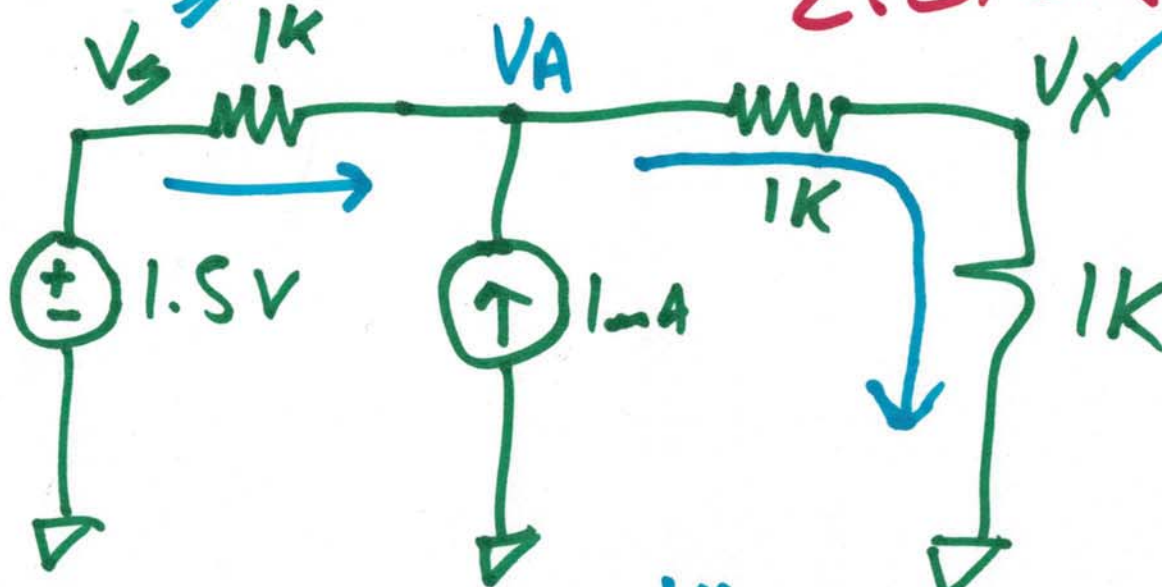


EE 220 circuits 2

Sept. 14, 2018

Lecture 7

find V_X



$$= \frac{1k \cdot V_A}{1k + 1k}$$

$$1.5 - V_A + 1mA$$

$$= \frac{V_A - 0}{2k}$$


$$= \frac{V_A - V_X}{1k}$$

$$3 - 2V_A + 2V = V_A$$

$$5V = 3V_A \quad V_X = \frac{V_A}{2}$$

$$V_A = \frac{5}{3} V$$


$$V_X = \frac{5}{6} V$$

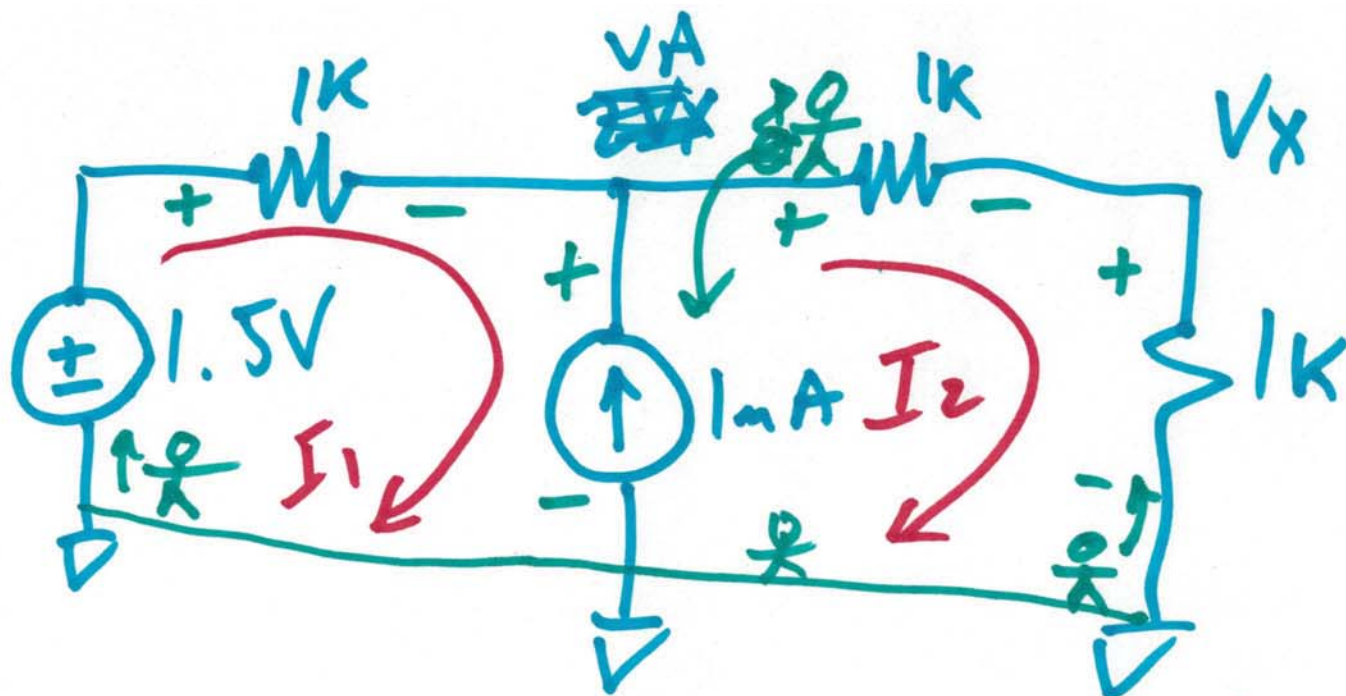

$$1\text{mA} = I_2 - I_1 \quad (1)$$

$$1.5 - 1kI_1 - V_A = 0 \quad (2)$$

$$1kI_2 + 1kI_2 - V_A = 0 \quad (3)$$

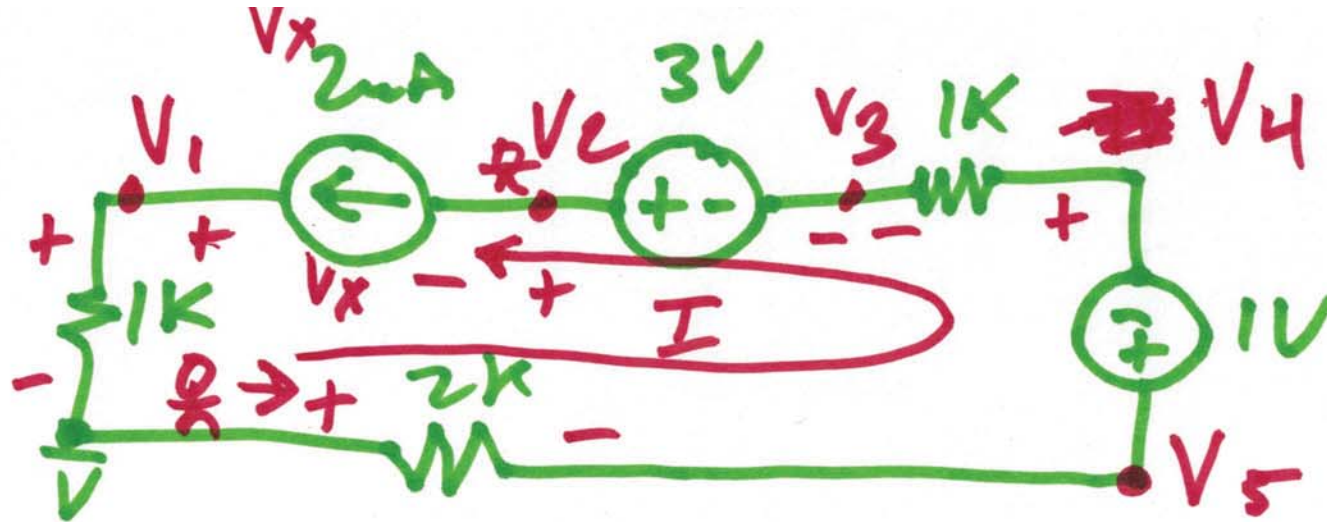

$$V_5 - V_4 = 1$$


$$V_2 - V_5 = 3$$

$$-2k \cdot I - 1V - 1k \cdot I + 3V + (V_1 - V_2) - 1k \cdot I = 0$$

$$I = 2\mu A$$


- V_1 V_2 V_3 V_4 I
 V_5

57

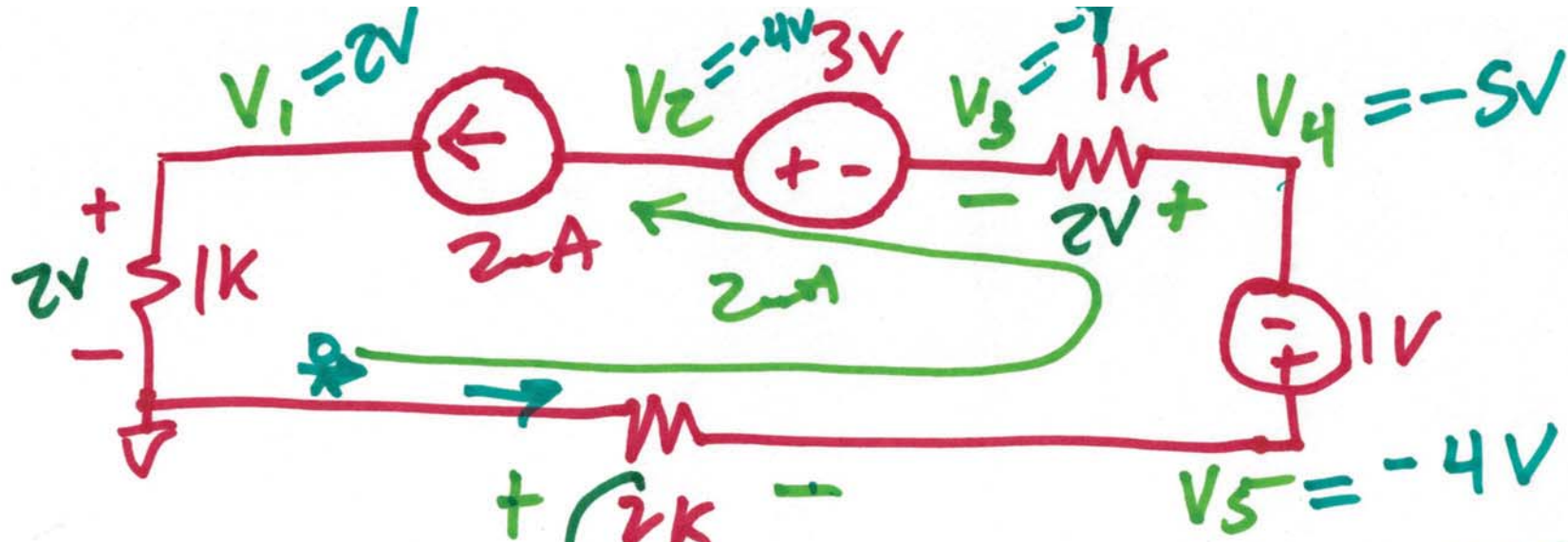


$I = 2mA$

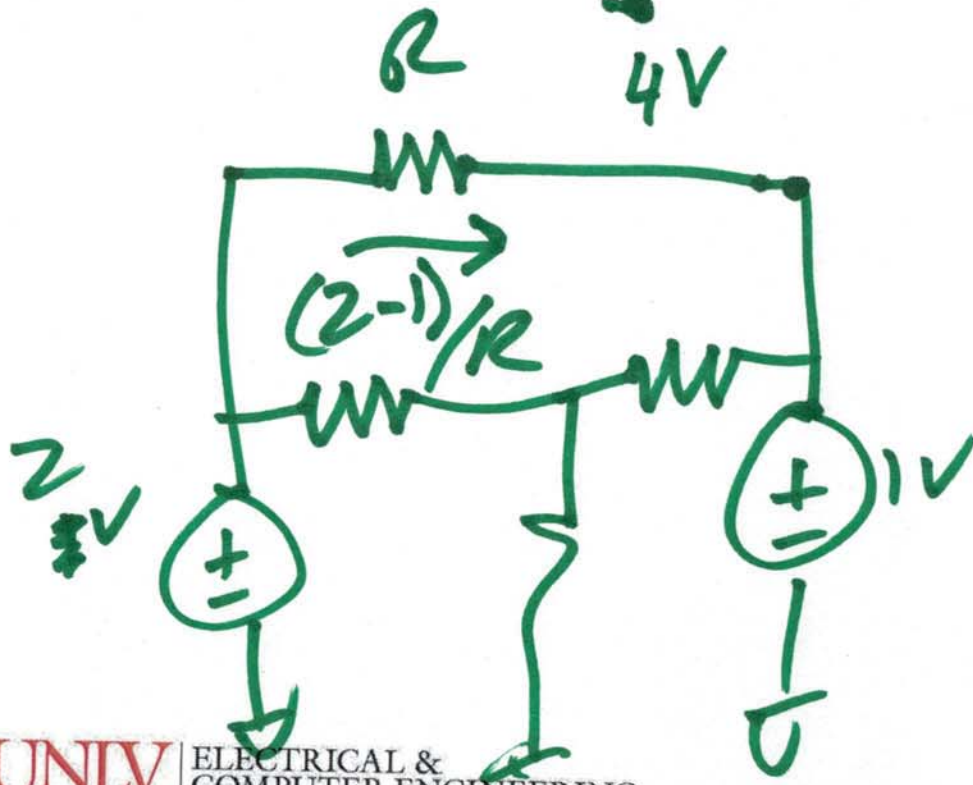- $V_1 = 2V$
- $V_2 = -4V$
- $V_3 = -7V$
- $V_4 = -5V$
- $V_5 = -4V$





4)

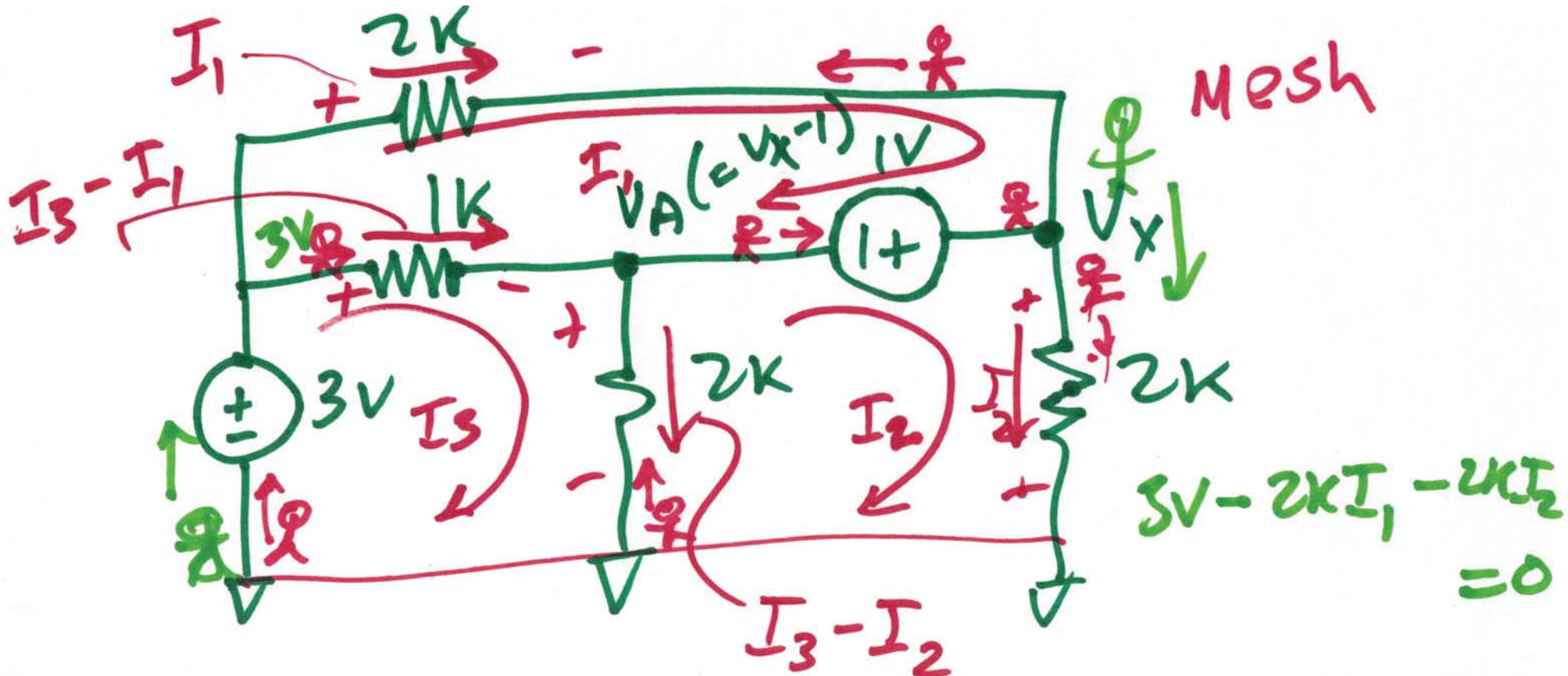


$$3V - 1k(I_3 - I_1) - 2k(I_3 - I_2) = 0$$

$$-2k(I_2) + 2k(I_3 - I_2) + 1V = 0$$


$$2kI_1 - 1k(I_3 - I_1) + 1V = 0$$

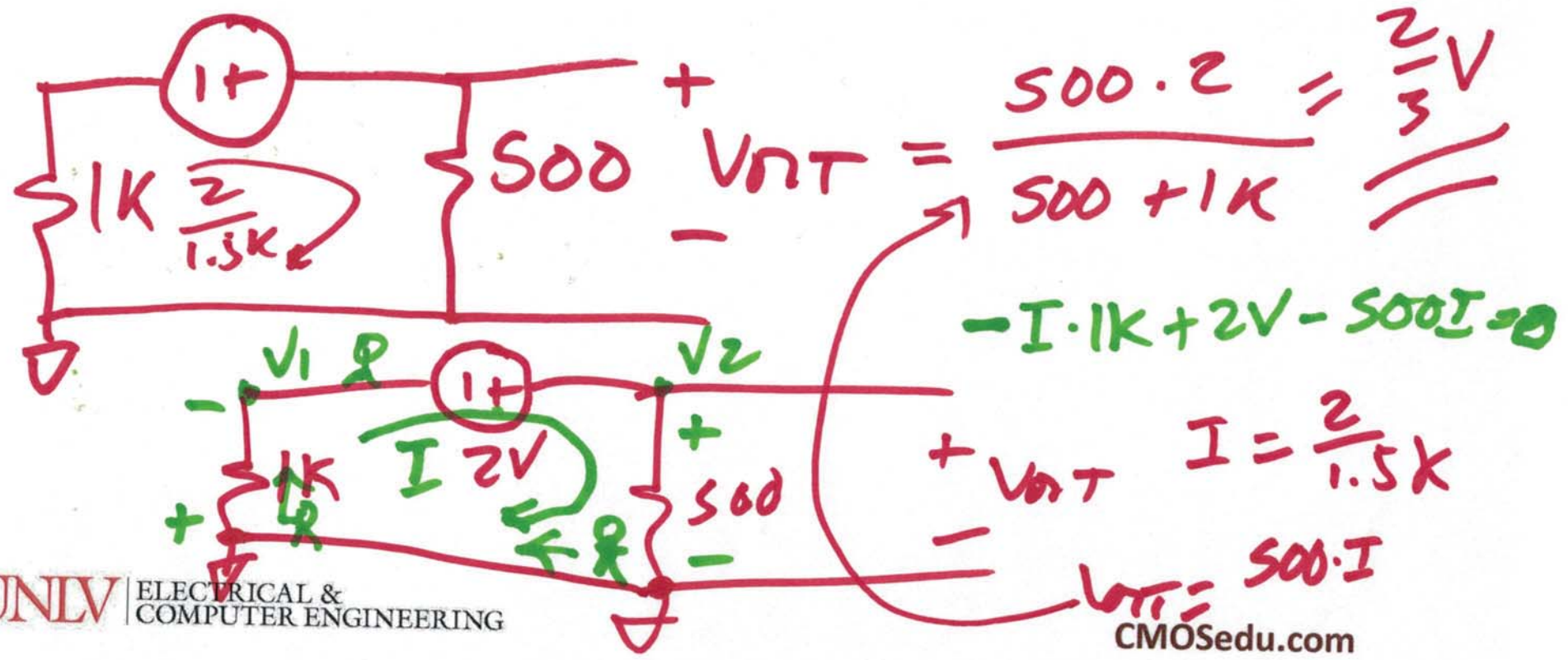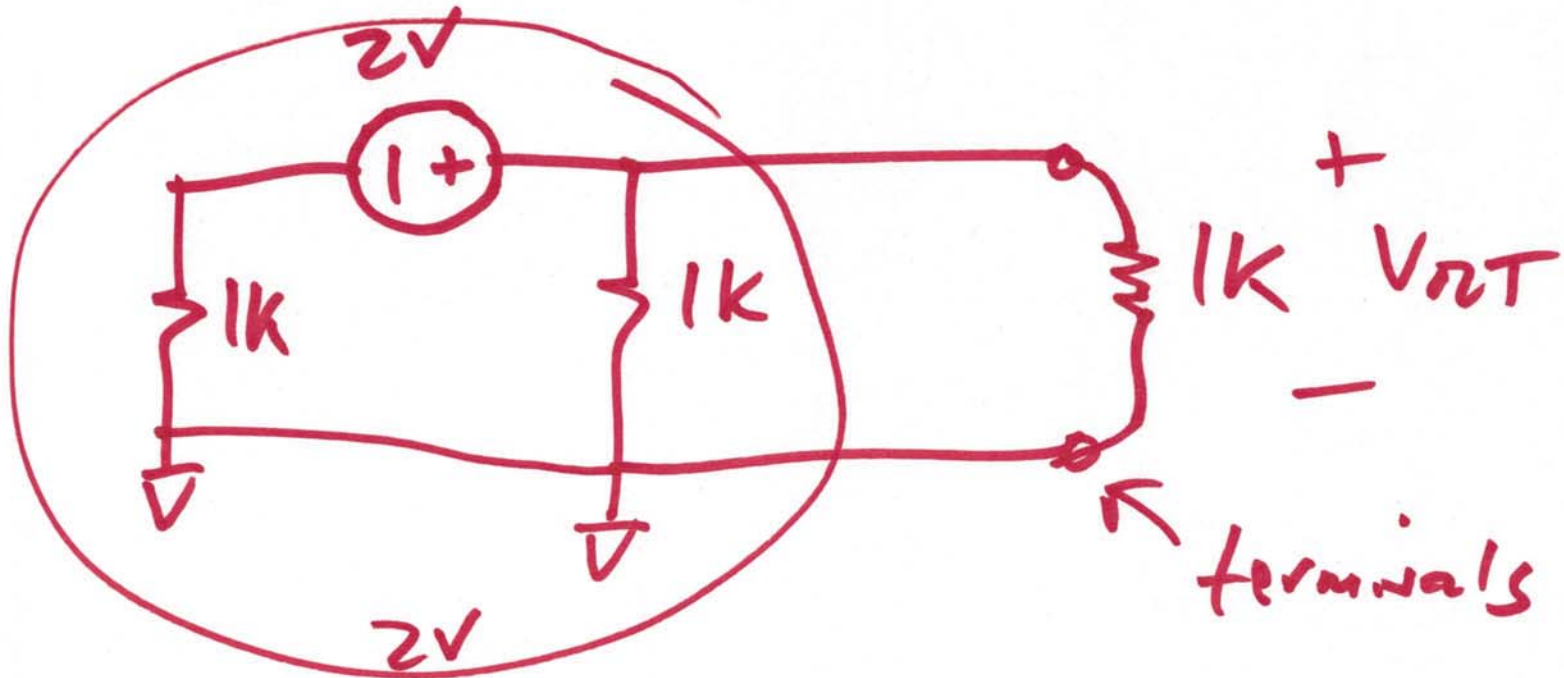

b)

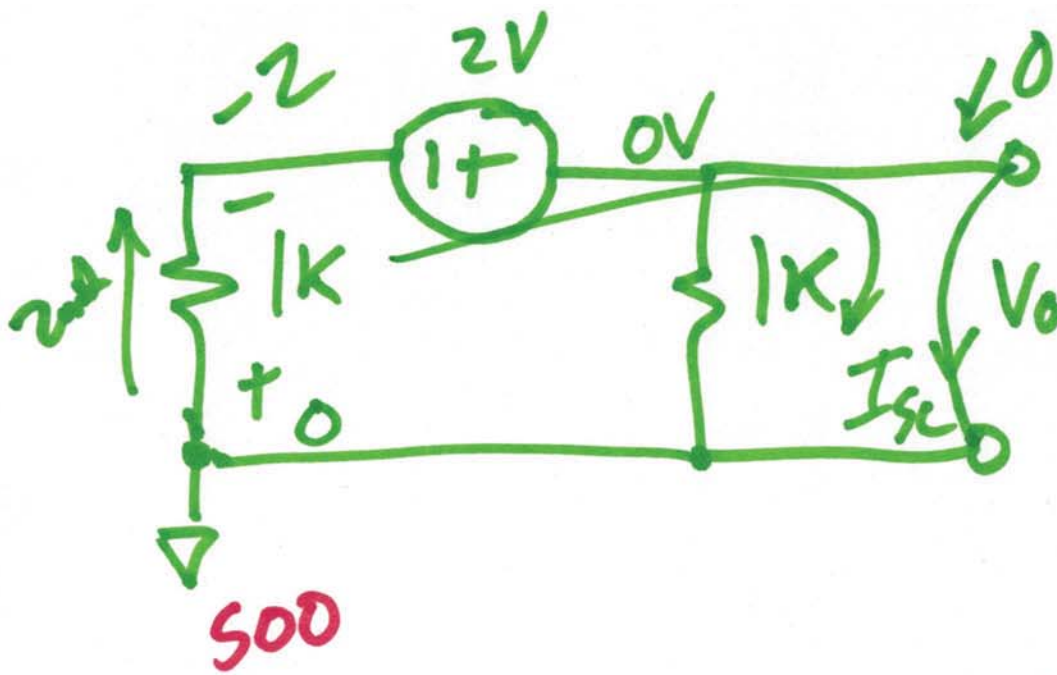

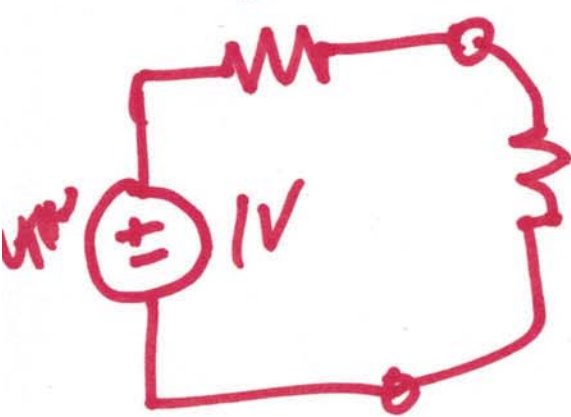
$V_{oc} = 1V = V_{TH}$
 $R_{TH} = 500\Omega$
 $I_{sc} = 2mA$



$V_{TH} = \frac{1V}{2mA} = \frac{V_{oc}}{I_{sc}} = 500\Omega$
 $V_{OUT} = \frac{2}{3}V$

Thevenin equivalent circuit




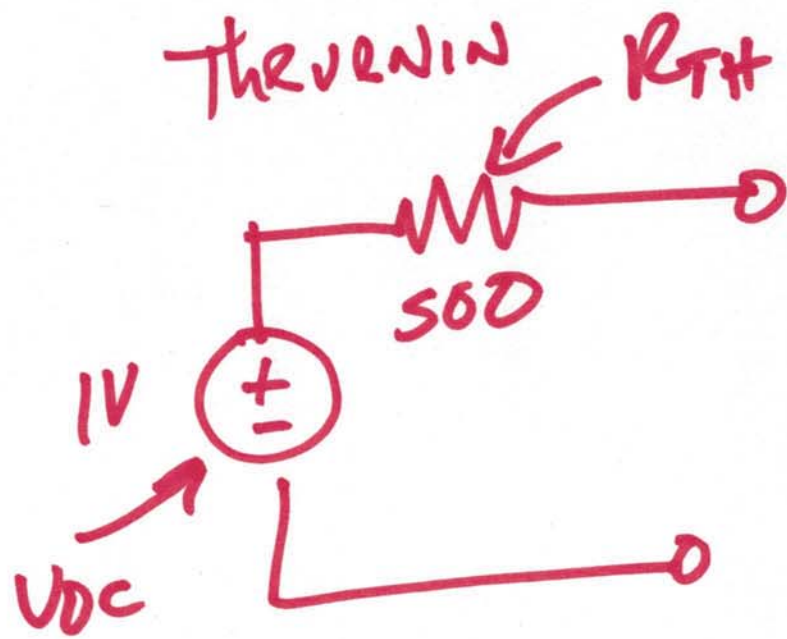

$$= 2\mu\text{A} \cdot 333\Omega = .666\text{V}$$

$$V_{NT} = 2\mu\text{A} \cdot 1\text{k} \parallel 500$$

NORTON

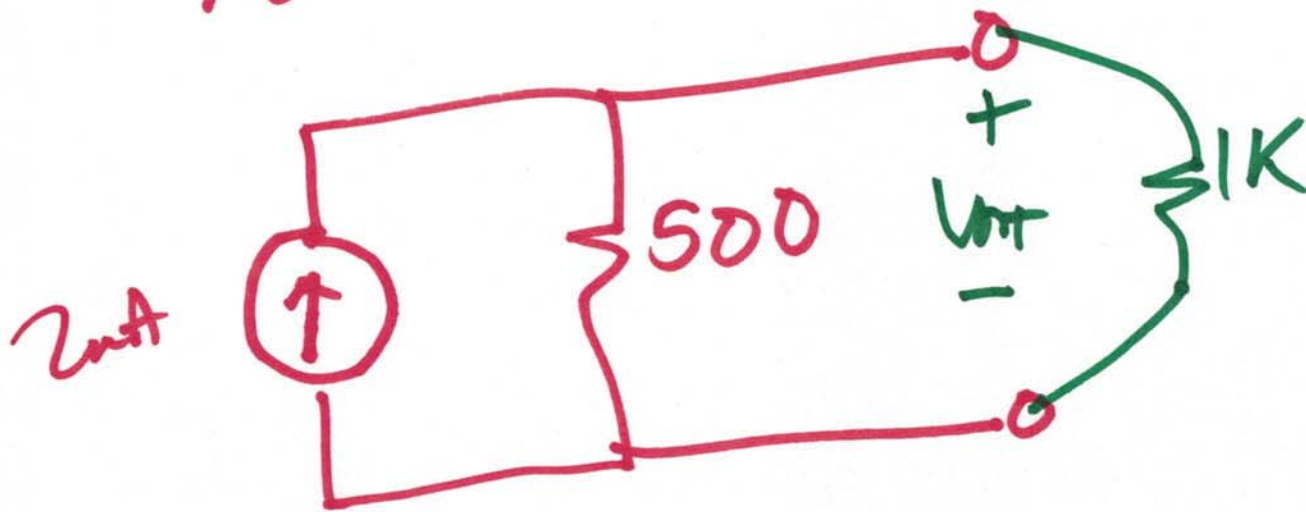

$$\frac{1,000 \cdot 500}{1,000 + 500}$$

$$\frac{500,000}{1,500} = \frac{1000}{3}$$

$$= 333\Omega$$

8)