
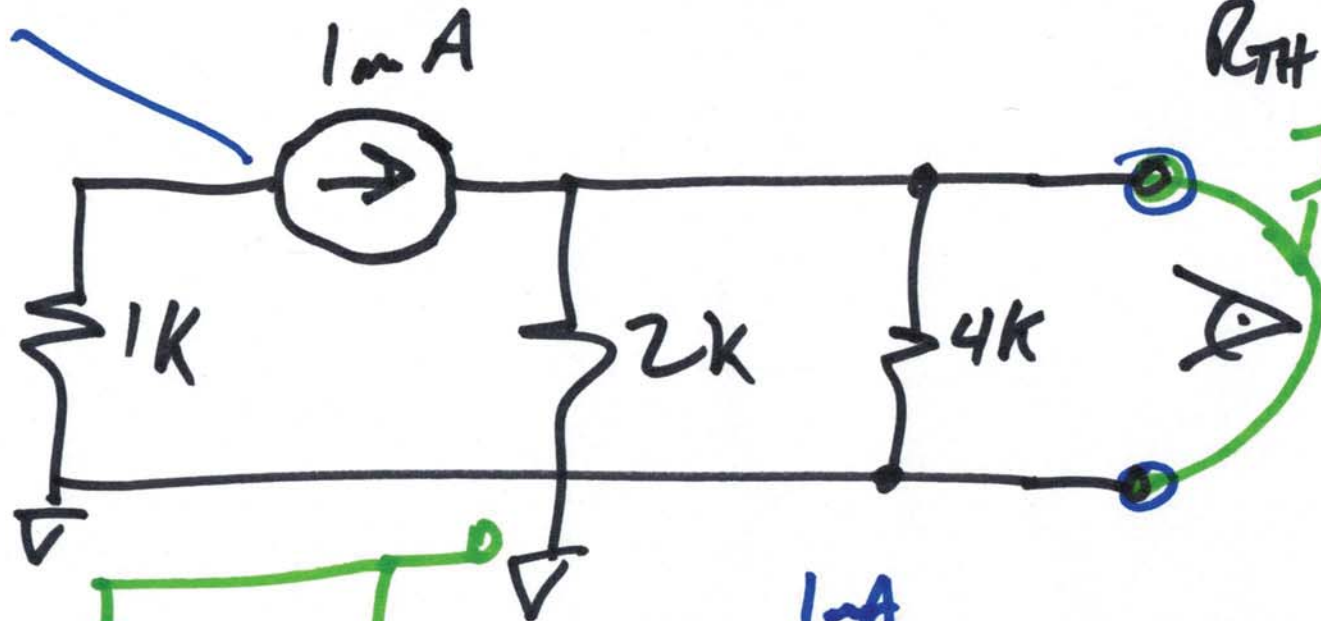


Lecture 8

Sept. 19, 2018



EE 220

Circuits 1

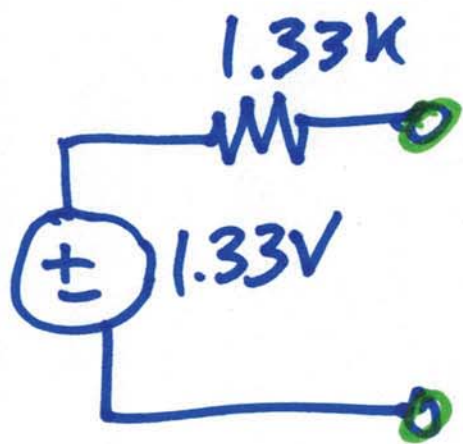


$$R_{TH} = \frac{2k \cdot 4k}{2k + 4k}$$

$$I_{sc} = 1mA = \frac{8k}{6} = 1.33k$$

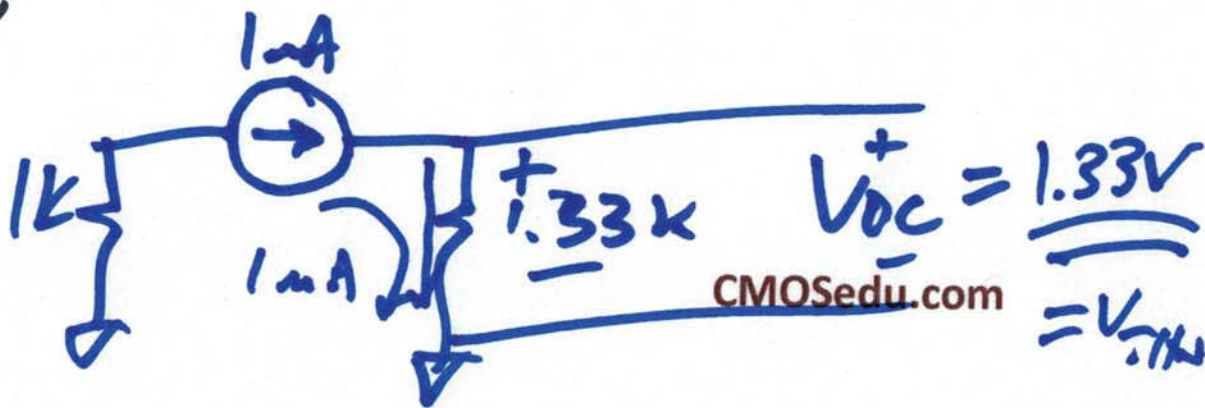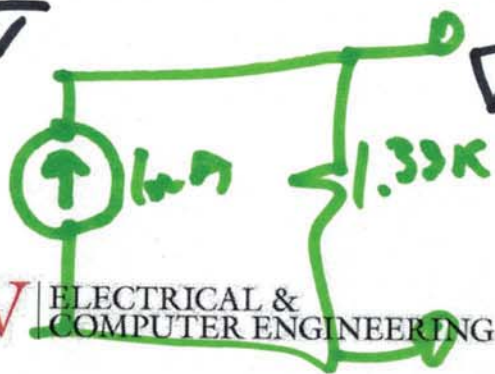

$$V_{oc} = 1.33V = V_{TH}$$

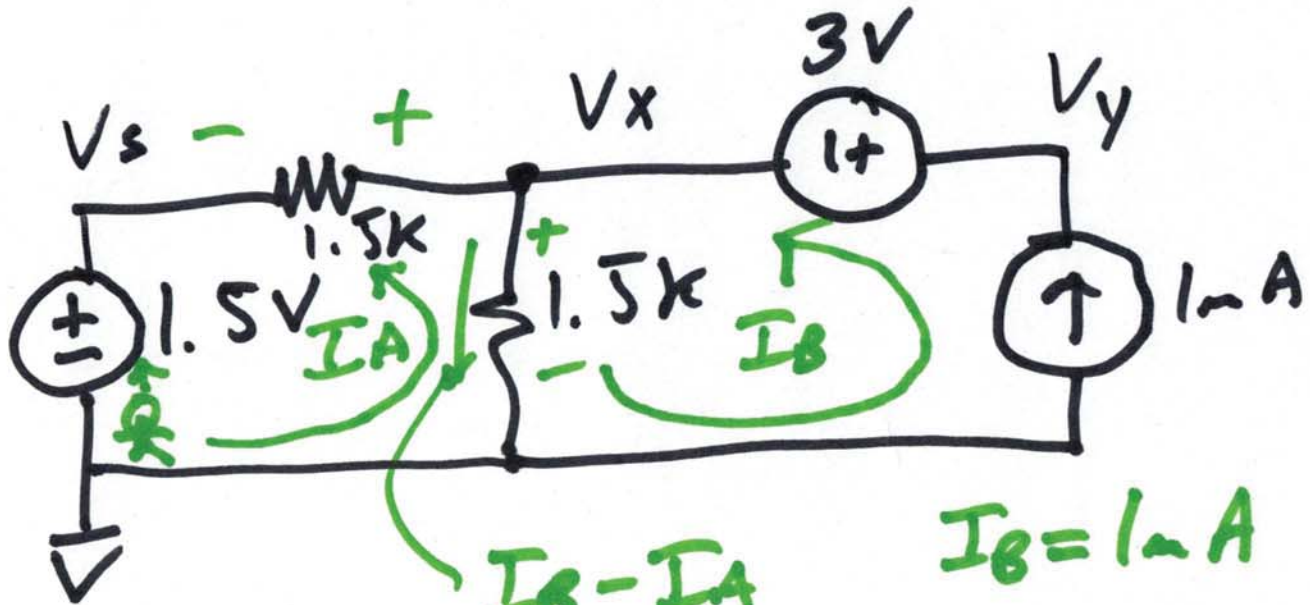

$I_B - I_A$ $I_B = 1\text{mA}$


$$1.5\text{V} + 1.5\text{k} \cdot I_A - 1.5\text{k} (1\text{mA} - I_A) = 0$$

$$1.5 + 1.5\text{k} I_A - 1.5 + 1.5\text{k} I_A = 0$$

$$\boxed{I_A = 0}$$

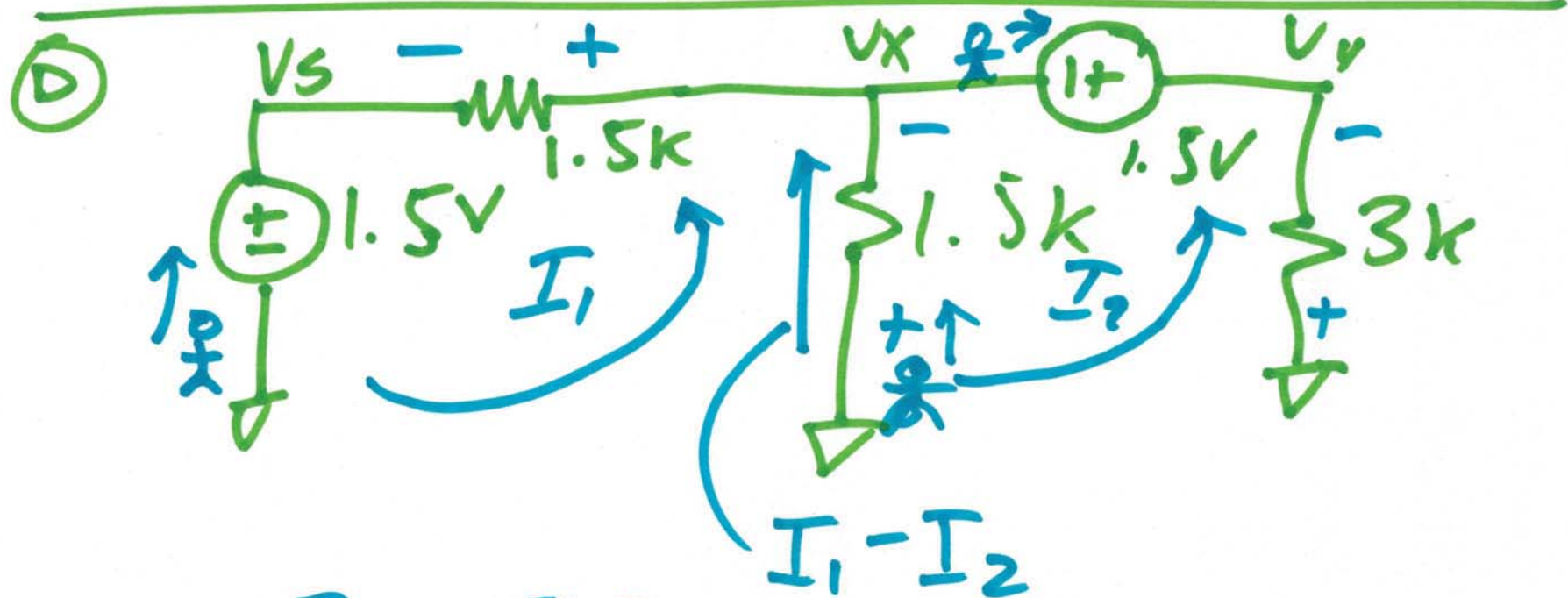
2)

$$\textcircled{C} \quad \frac{1.5 - V_x}{1.5k} + \frac{1.5 - V_x}{1.5k} = \frac{V_x}{3k}$$



$$1.5 + 1.5kI_1 + 1.5k(I_1 - I_2) = 0$$

$$1.5 + 3kI_2 - 1.5k(I_1 - I_2) = 0$$

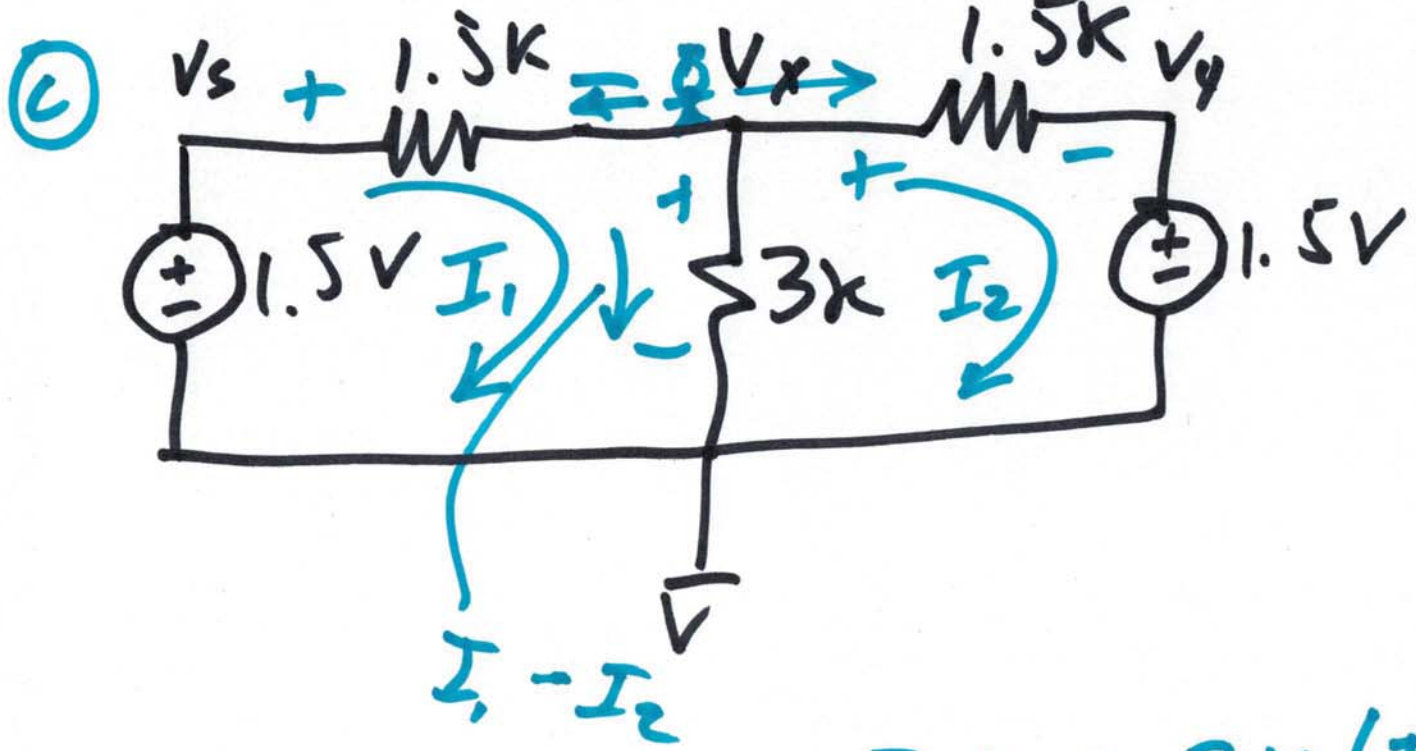


$$1.5k \cdot I_1 - 1.5V + 3k(I_1 - I_2) = 0$$

$$-(-1.5k I_2 - 1.5V + 3k(I_1 - I_2)) = 0$$

~~3kI~~

4)

4.54

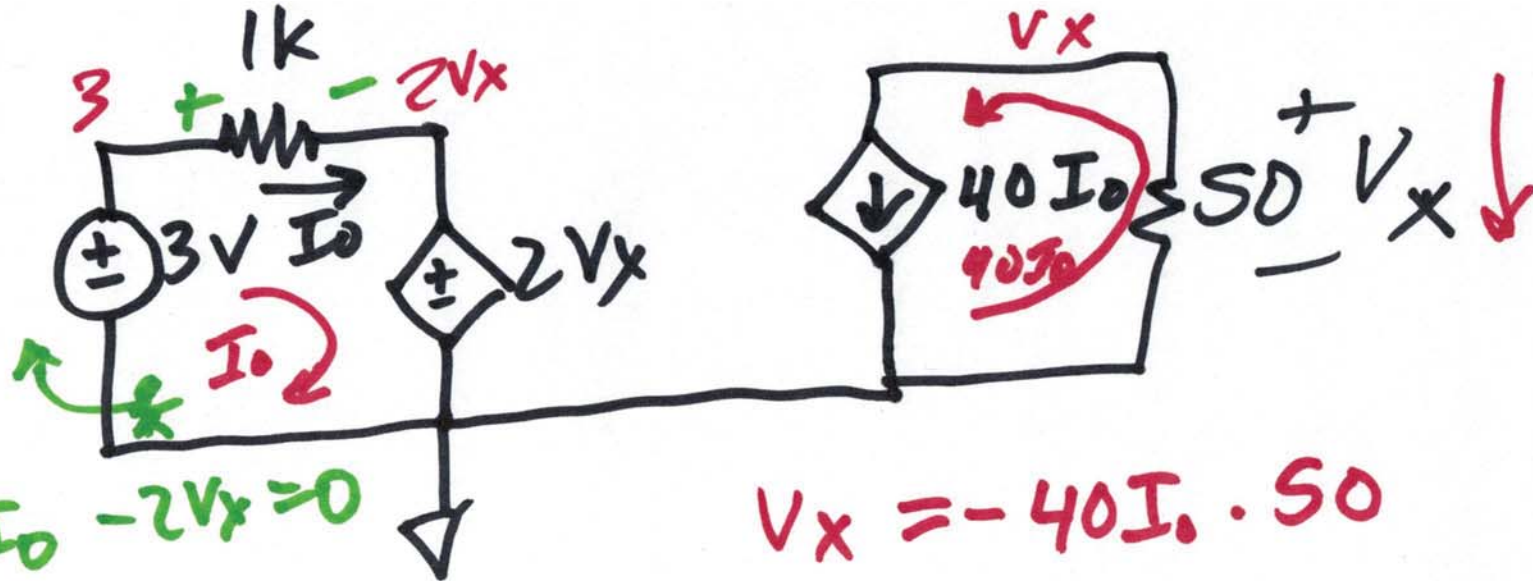

$$3 - 1kI_0 - 2V_x = 0$$

$$V_x = -40I_0 \cdot 50$$

$$V_x = -2kI_0$$

$$\frac{3 - 2V_x}{1k} = I_0$$

$$V_x = +2V$$

$$3 + 4kI_0 = 1kI_0$$

$$3kI_0 = -3$$

$$I_0 = -1\mu A$$

