


EE 220


Circuits 1

Lecture 9


September 24, 2018

Source transformation

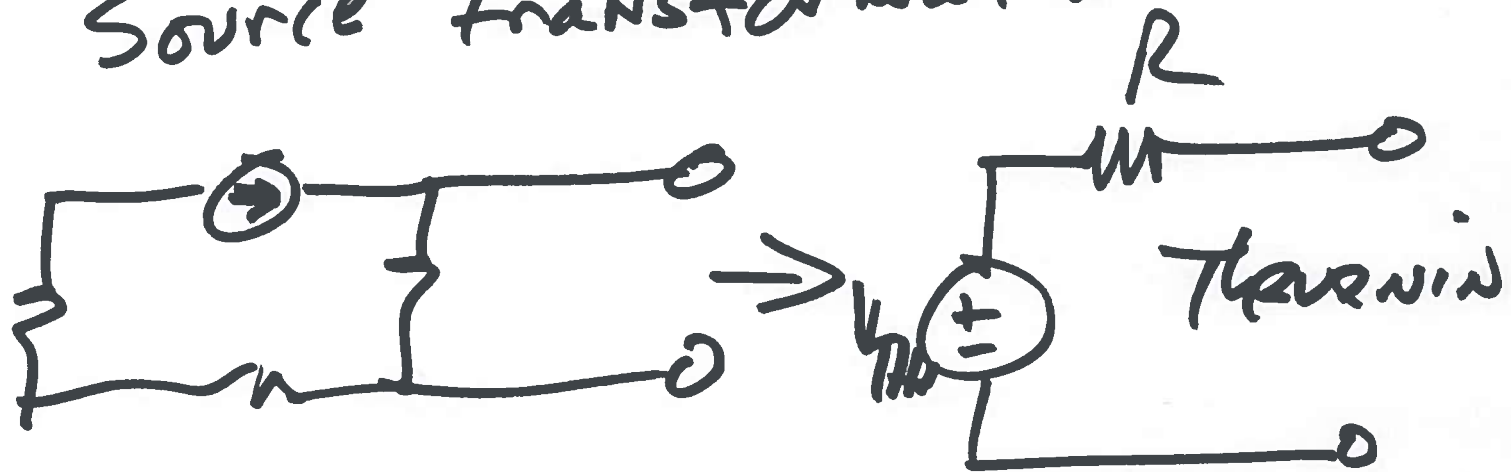

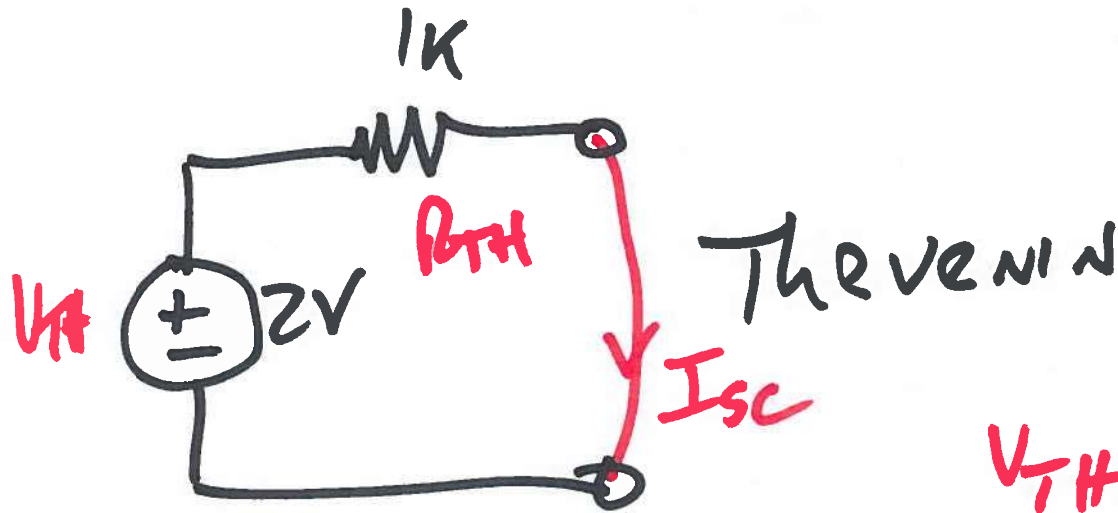


$$V_{TH} = I_{sc} \cdot R_{TH}$$

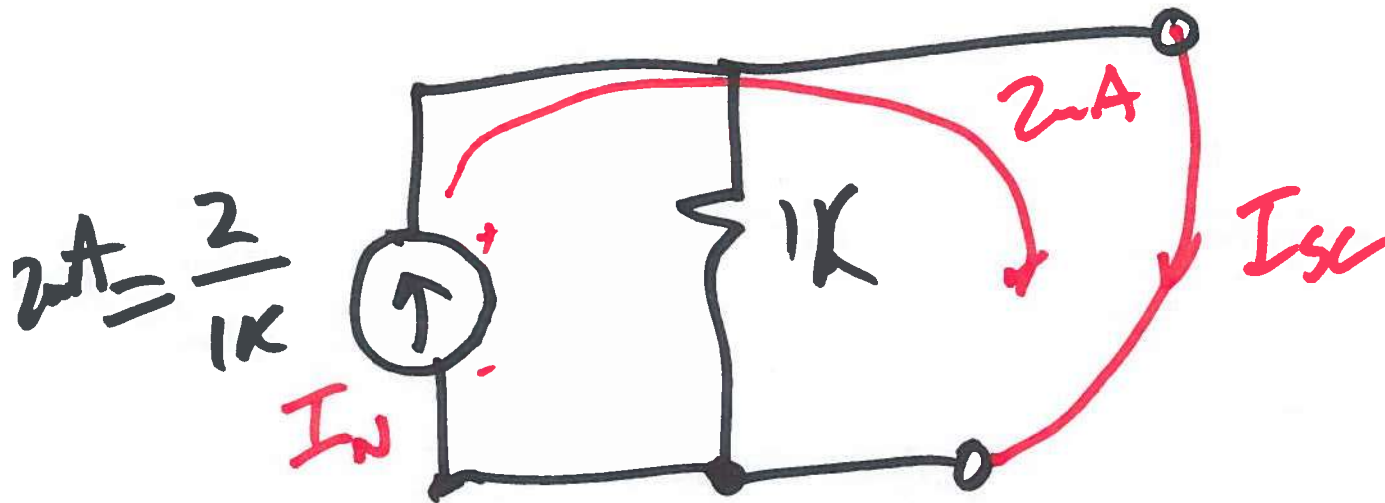


2)

"super node"

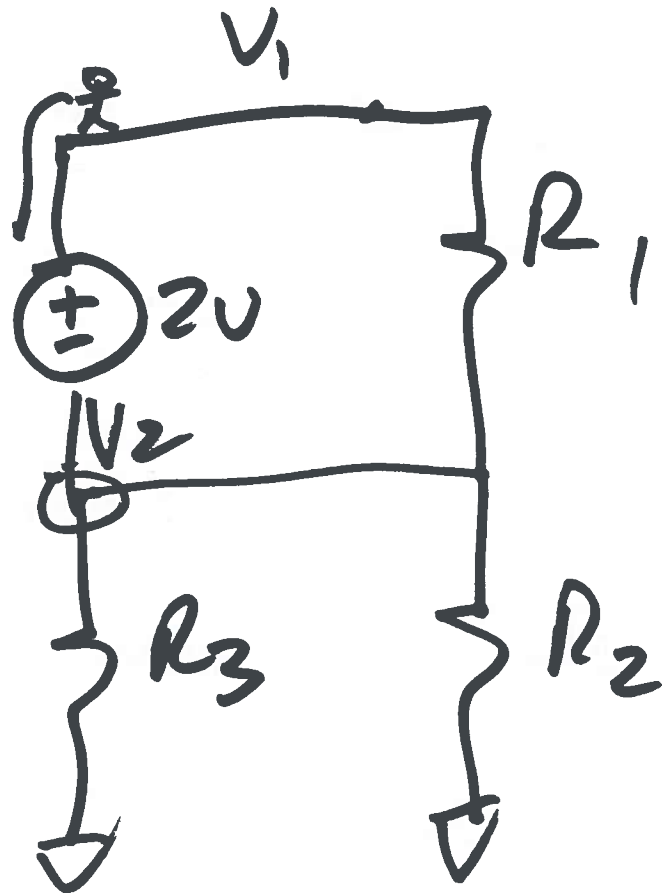

$$V_2 = V_1 - 2V$$

Super mesh

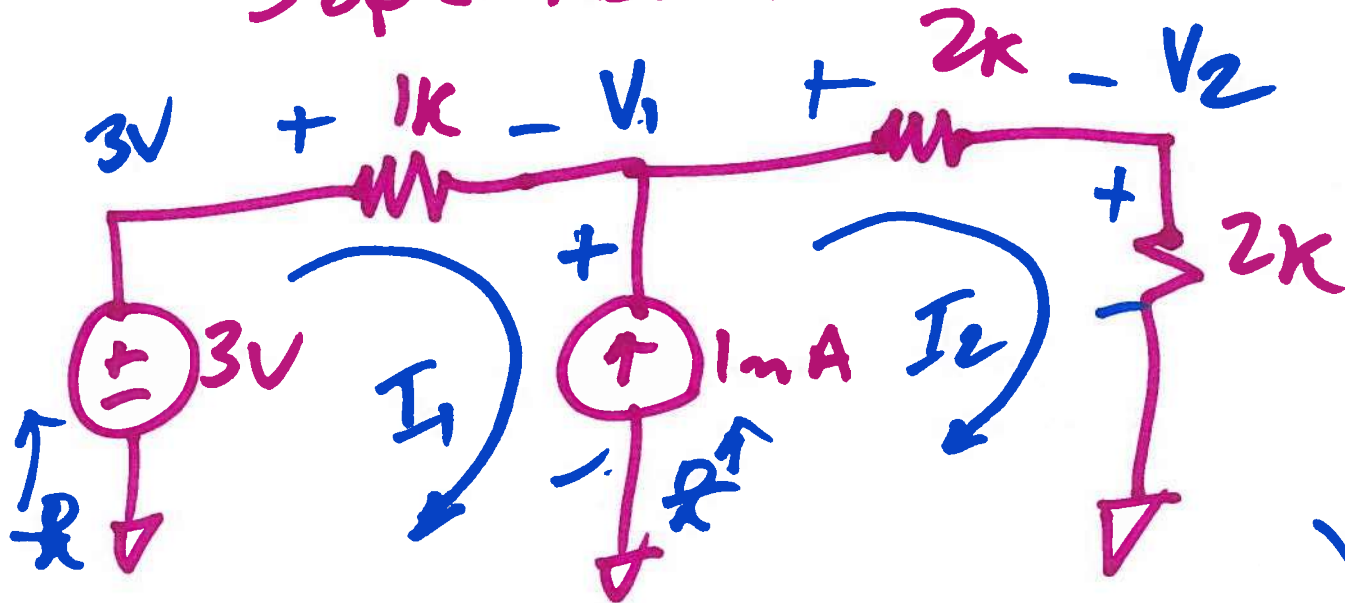

Mesh analysis

$$1\text{mA} = I_2 - I_1 \quad (1)$$


$$3 - 1\text{k} \cdot I_1 - V_1 = 0 \quad (2)$$

$$V_1 - 2\text{k}I_2 - 2\text{k}I_2 = 0 \quad (3)$$

Supermesh

$$1\text{mA} = I_2 - I_1$$
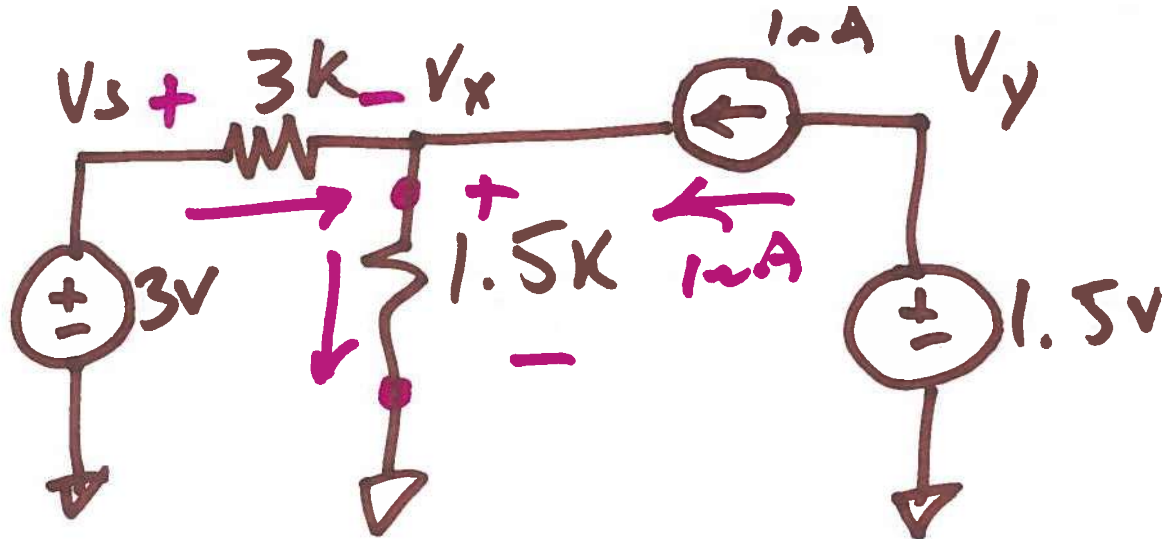
$$3 - 1\text{k}I_1 - 2\text{k}I_2 - 2\text{k}I_2 = 0$$




$$\frac{3 - V_x}{3k} - \frac{V_x}{1.5k} + 1mA = 0$$

$$3 - V_x - 2V_x + 3V = 0$$

$$6 = 3V_x$$

$V_x = 2V$

5)

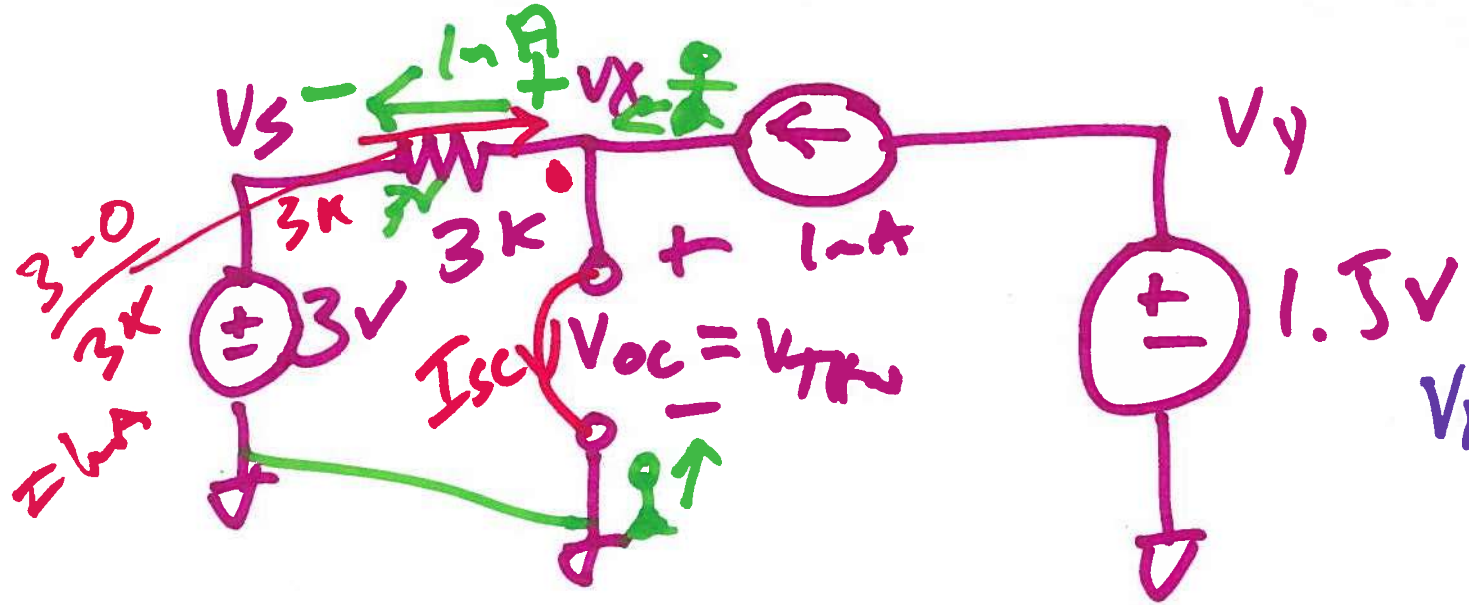

$$\frac{V_{Th}}{I_{Th}} = \frac{V_{oc}}{I_{sc}} = R_{Th}$$



$$V_X = 2mA \cdot 3k \parallel 1.5k$$

$$\frac{3 \cdot 1.5}{3 + 1.5} = \frac{4.5}{4.5}$$


$$= 1k$$

$$\underline{\underline{V_X = 2V}}$$


$$3k - 3V - 3 + V_{Th} = 0$$

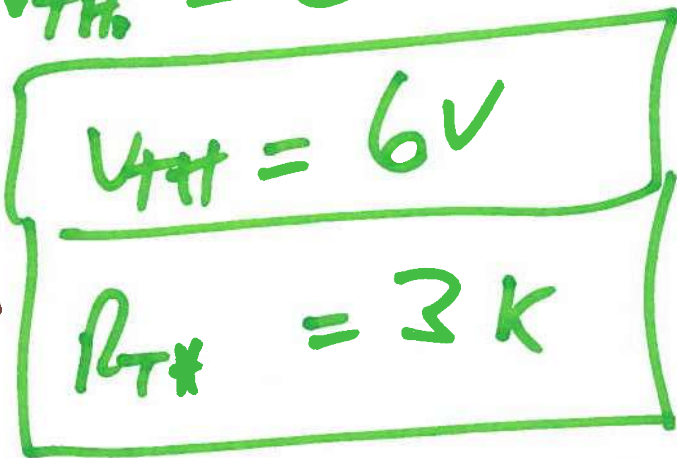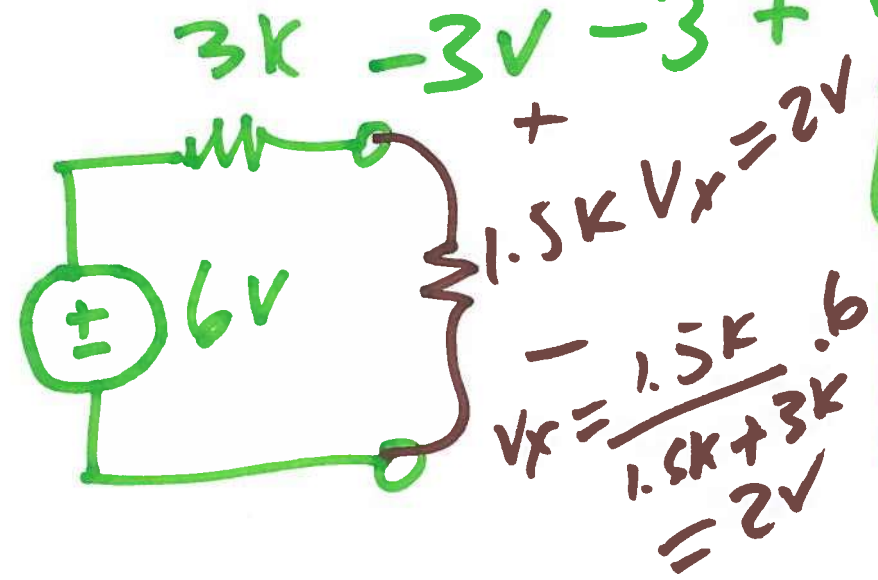
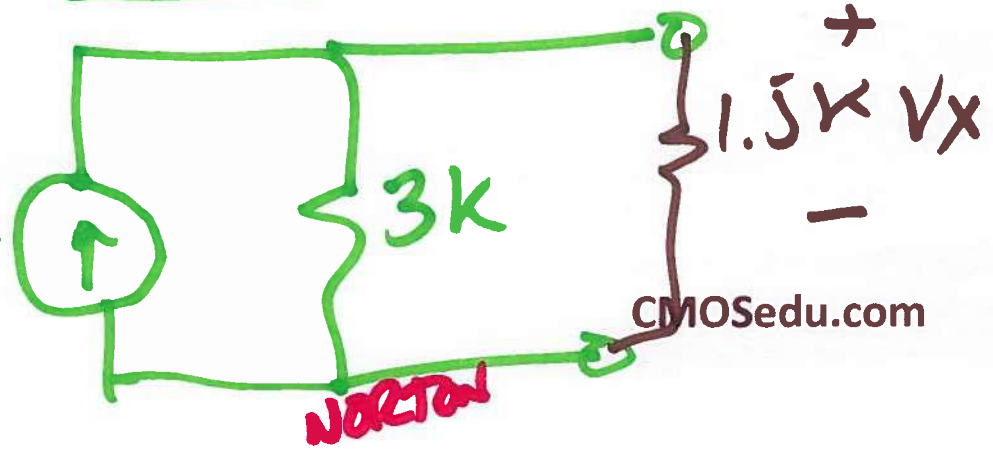
$$\underline{\underline{2mA}} = \frac{6}{3k}$$



6)

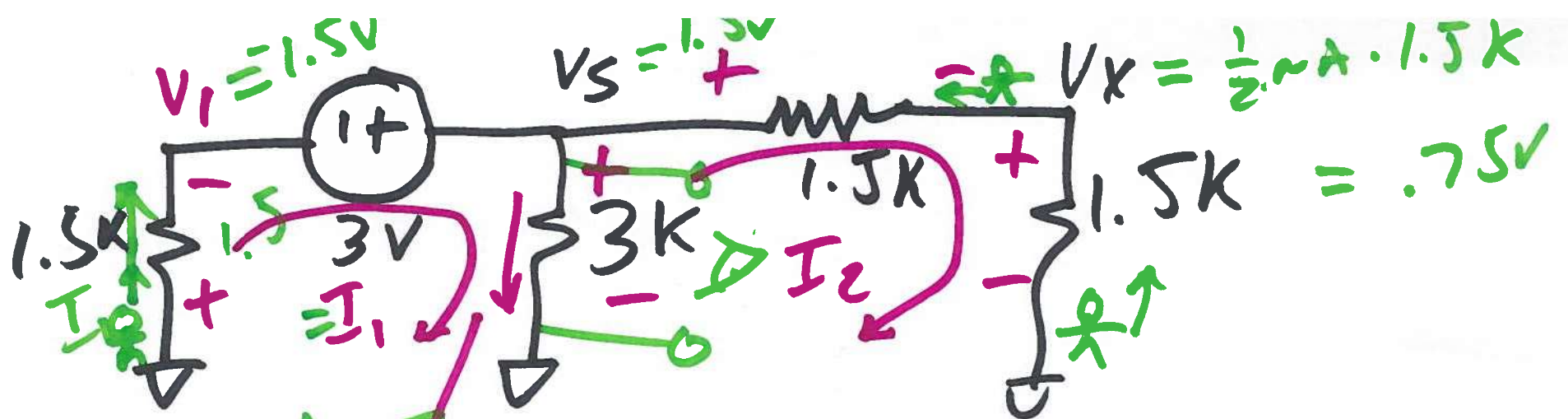

$4I_2 = 2\mu A$
 $I_2 = \frac{1}{2} \mu A$
 $I_1 - I_2$

$-1.5k I_1 + 3V - 3k(I_1 - I_2) = 0$
 $6I_2 - 2I_2 = 2\mu A$
 $1.5k I_2 - 3k(I_1 - I_2) + 1.5k I_2 = 0$

$3I_1 - 2I_2 = 2\mu A$
 $\leftarrow I_1 - 2\mu A + 2I_1 - 2I_2 = 0$


$4I_2 - 2I_1 = 0$
 $\leftarrow I_2 - 2I_1 + 2I_2 + I_2 = 0$

$2I_1 = 4I_2$

$I_1 = 2I_2$

$I_1 = 1\mu A$

1)

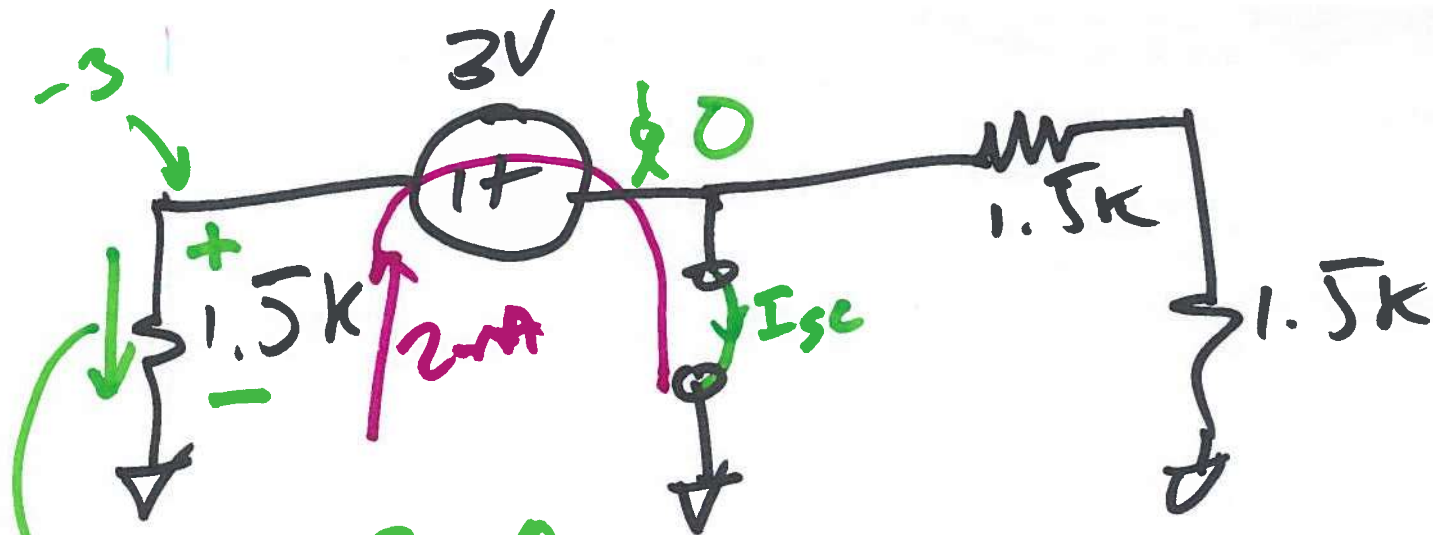


$$I = \frac{-3 - 0}{1.5k} = -2mA$$

$$R_{TH} = 1.5k \parallel 3k$$

$$R_{TH} = 1k$$

$$I_{sc} = 2mA = I_0$$



$$V_{TH} = 2mA \cdot 1k = 2V$$

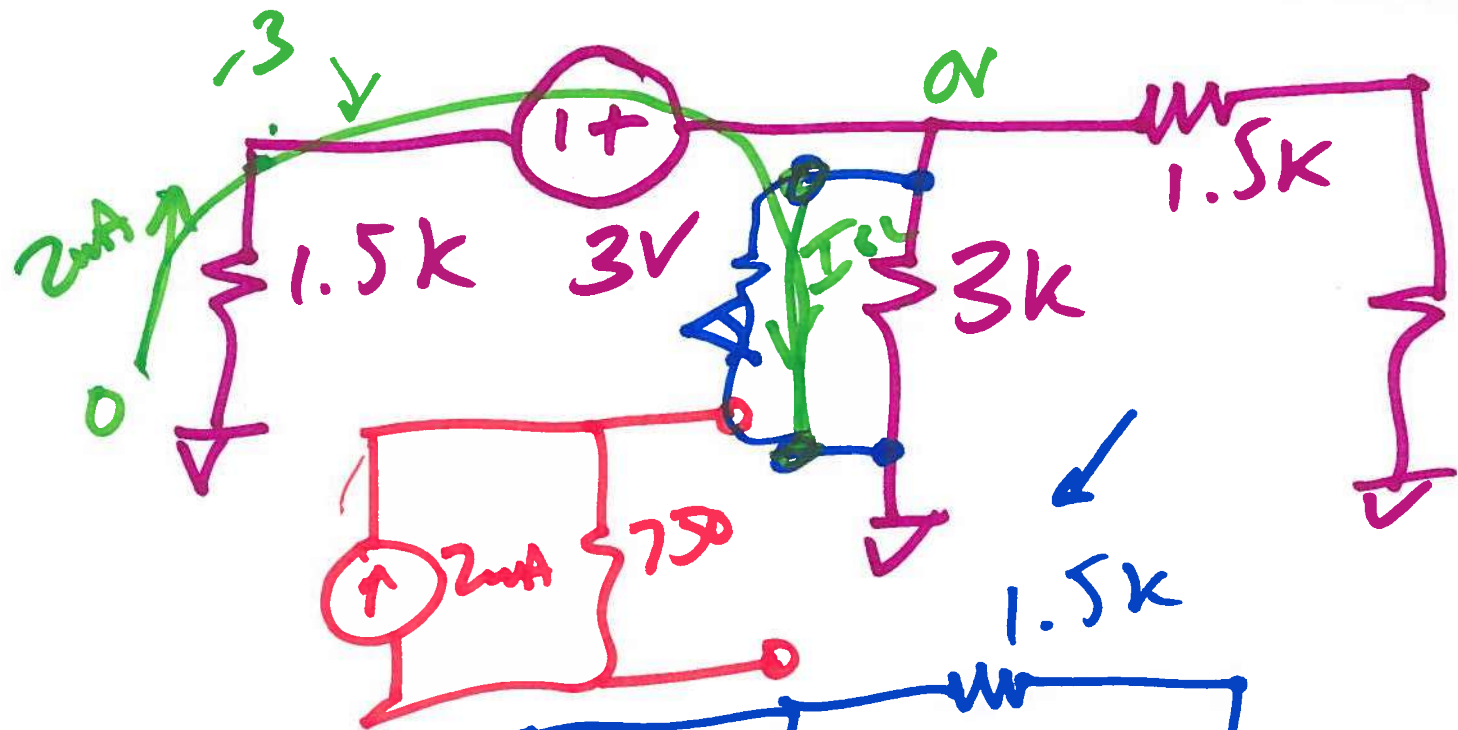

$$V_{TH} = 1.5V = 2\mu A \cdot 750$$

$$I_{sc} = I_D = 2\mu A$$

$$R_{TH} = 750 \Omega$$

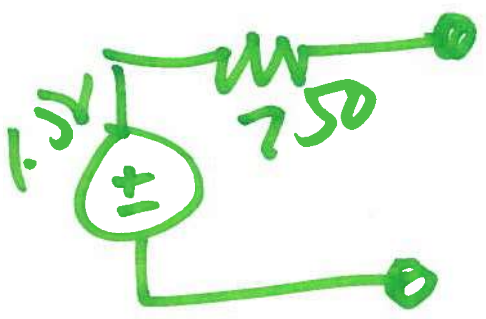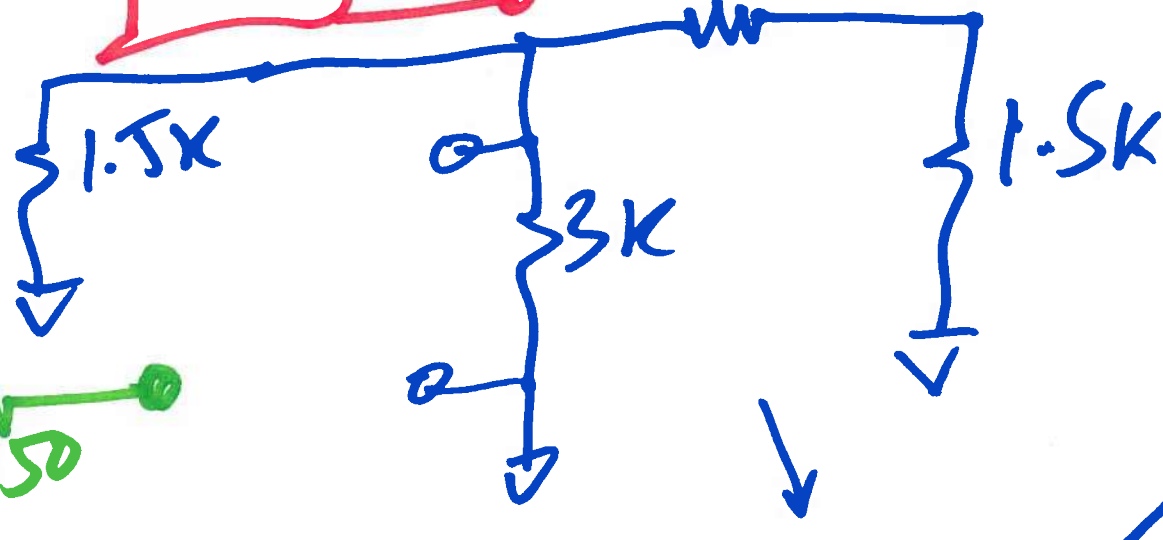

a)