
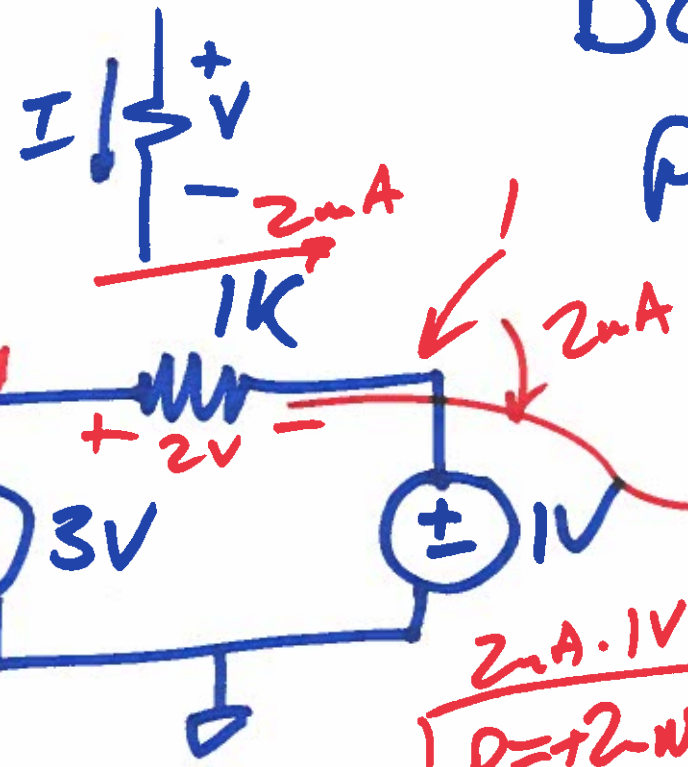


EE 220 Circuits 1

OCT. 2, 2019

Lecture 11

DC CKTS

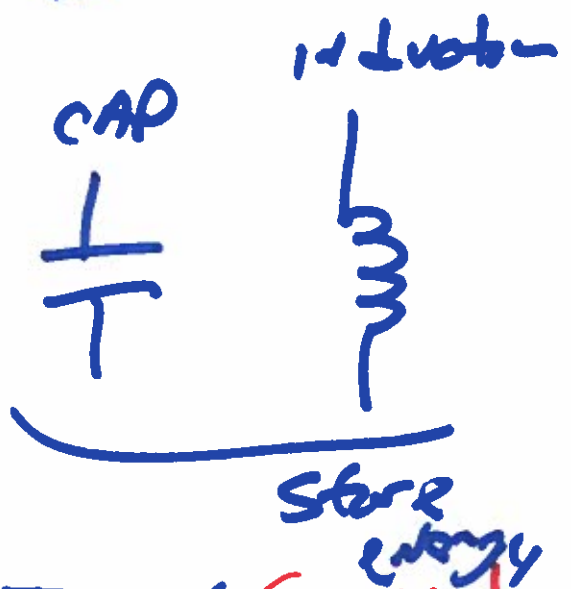

Power = $I \cdot V$ (Watts)

$V = IR, I = \frac{V}{R}$

$P = \frac{V^2}{R} = I^2 R$



Power = $2V \cdot 2mA = 4mW$

$2mA \cdot 1V$
 $P = +2mW$



Watts = $\frac{joules}{s}$

-6mW

1)

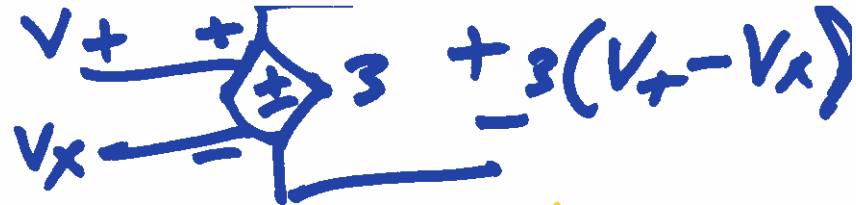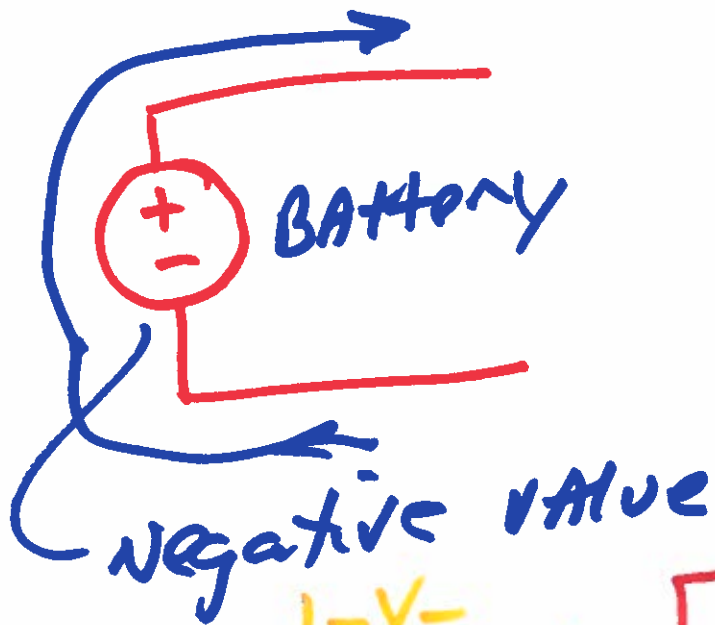
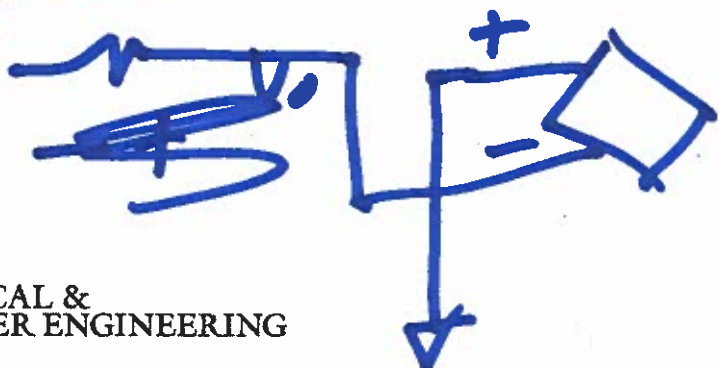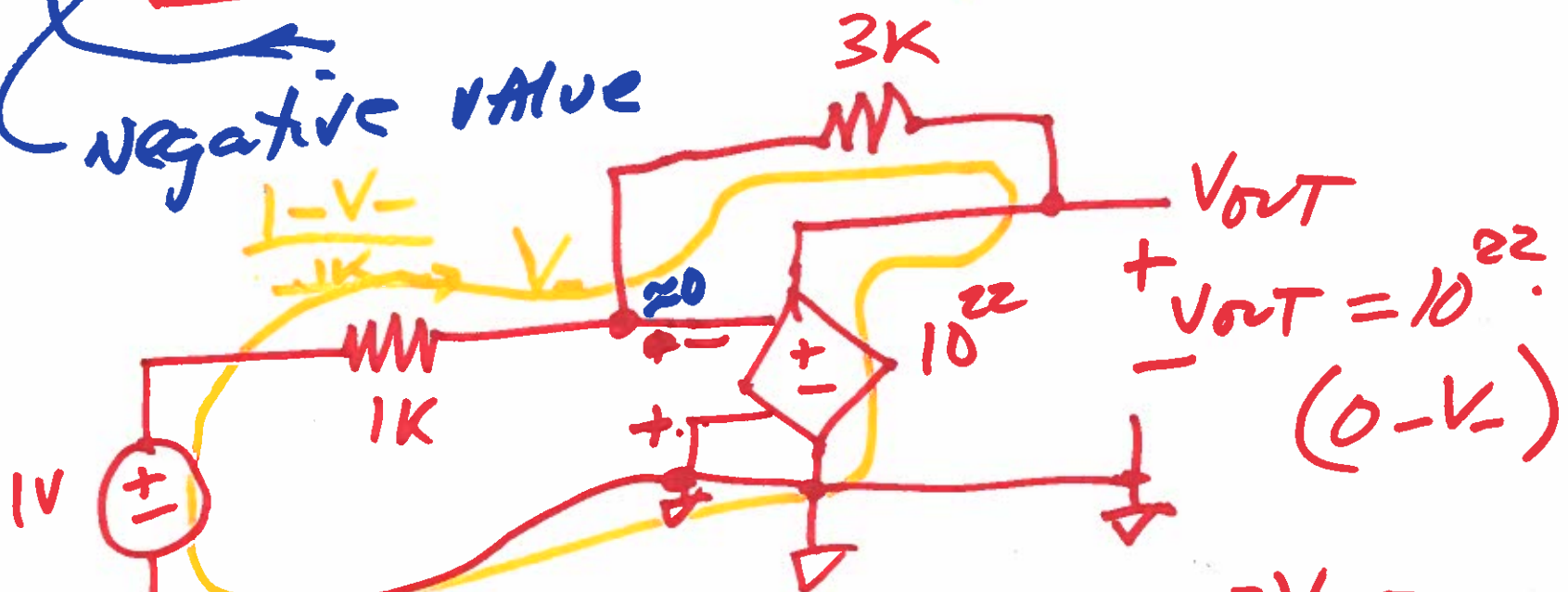
$$(1 - V_-) / 1K = \frac{V_- - V_{out}}{3K}$$



$$V_- = \frac{-V_{out}}{10^{22}}$$

$$V_- = \frac{3}{10^{22}} \approx 0$$

2)

$$(1 - V_-)3 = V_- - V_{out}$$


$$V_- = -\frac{V_{out}}{10^{22}}$$

$$3 + \frac{3V_{out}}{10^{22}} = -\frac{V_{out}}{10^{22}} - V_{out}$$

$$3 = -\frac{4V_{out}}{10^{22}} - V_{out}$$

$$V_{out} \approx -3$$

INVERTING INPUT OF OP-AMP

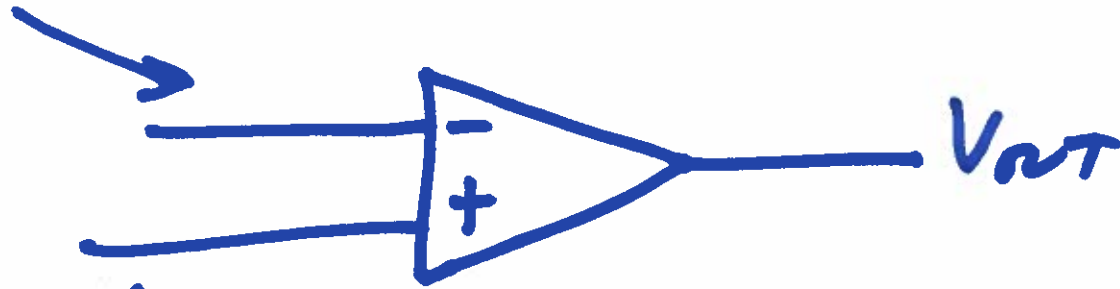


NON-INVERTING INPUT

$$\frac{V_- - V_{OUT}}{R_F}$$

$$V_{OUT} = A_{OL} (V_+ - V_-)$$

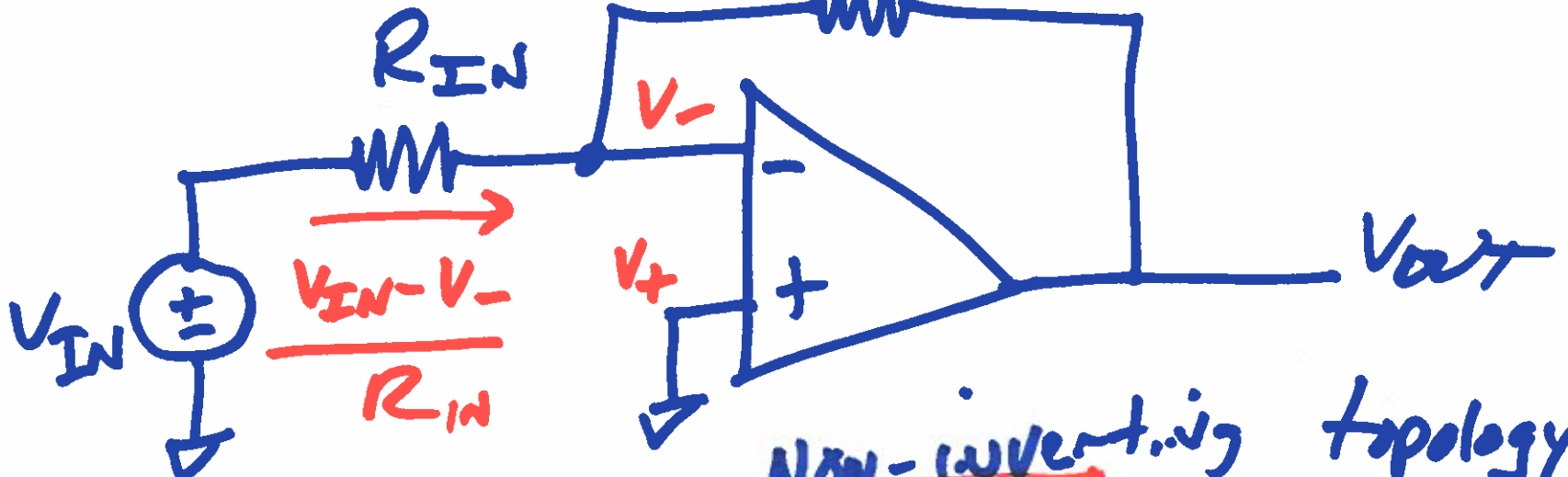ideal op-amp
 $A_{OL} \rightarrow \infty$



Non-inverting topology

$$\frac{V_{OUT}}{V_{IN}} = -\frac{R_F}{R_{IN}}$$

4)

$$\frac{V_{IN} - V_-}{R_{IN}} = \frac{V_- - V_{OUT}}{R_F}$$

$$V_- = -\frac{V_{OUT}}{A_{OL}}$$

$$\frac{R_F}{R_{IN}} \left(V_{IN} + \frac{V_{OUT}}{A_{OL}} \right) = \frac{-V_{OUT}}{A_{OL}} - V_{OUT}$$

$$\lim_{A_{OL} \rightarrow \infty} \frac{R_F}{R_{IN}} \cdot V_{IN} = V_{OUT} \left(\frac{-R_F}{R_{IN} A_{OL}} - \frac{1}{A_{OL}} \right)$$

$$V_{OUT} = -\frac{R_F}{R_{IN}} \cdot V_{IN}$$


$$\frac{V_{OUT}}{V_{IN}} = -\frac{R_F}{R_{IN}}$$

0-5V
-5-5

5)

NON-INVERTING topology


1) find voltage on "+" terminal

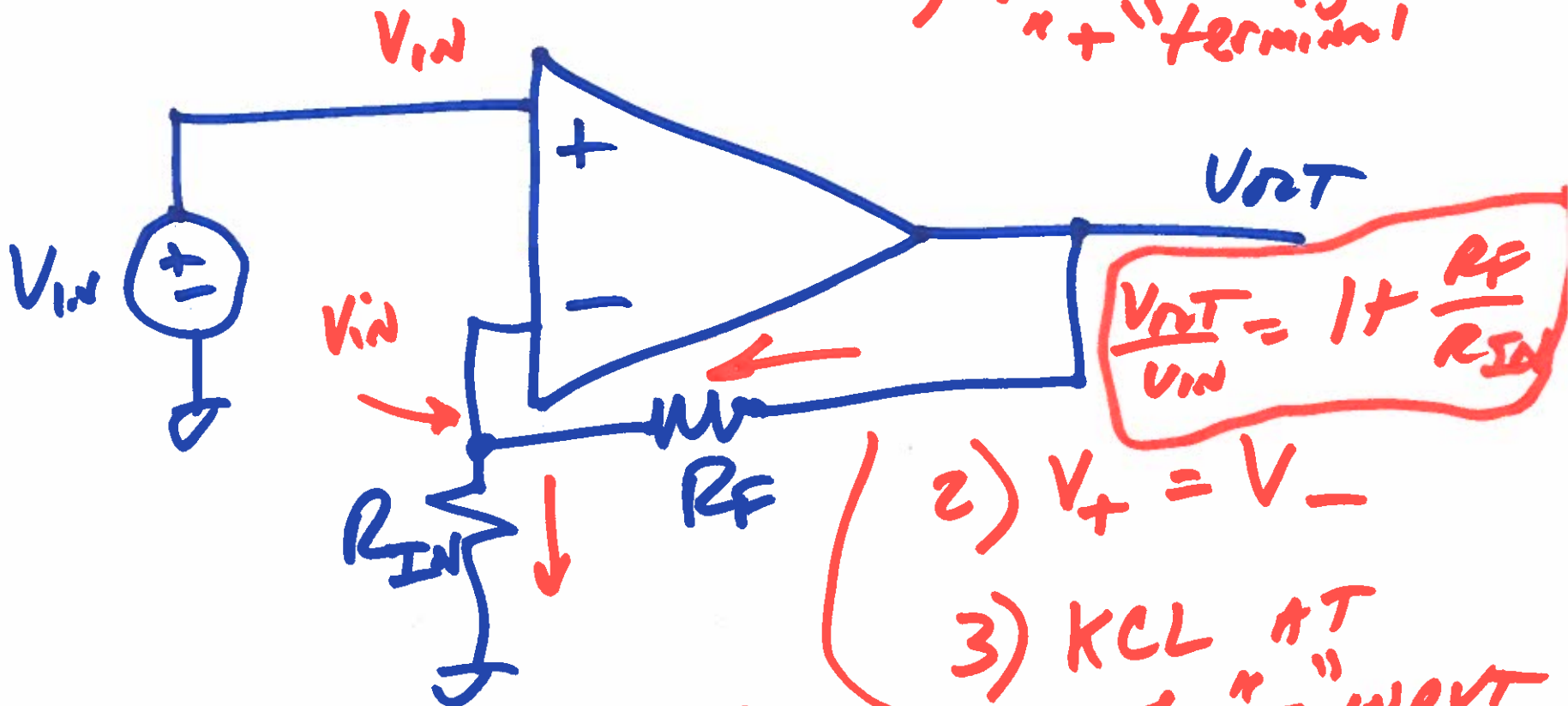

$$\frac{V_{in}}{R_{in}} = \frac{V_{out} - V_{in}}{R_f}, \quad V_{in} \left(\frac{1}{R_{in}} + \frac{1}{R_f} \right) = \frac{V_{out}}{R_f}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_f + R_{in}}{R_{in}} = 1 + \frac{R_f}{R_{in}}$$

b)

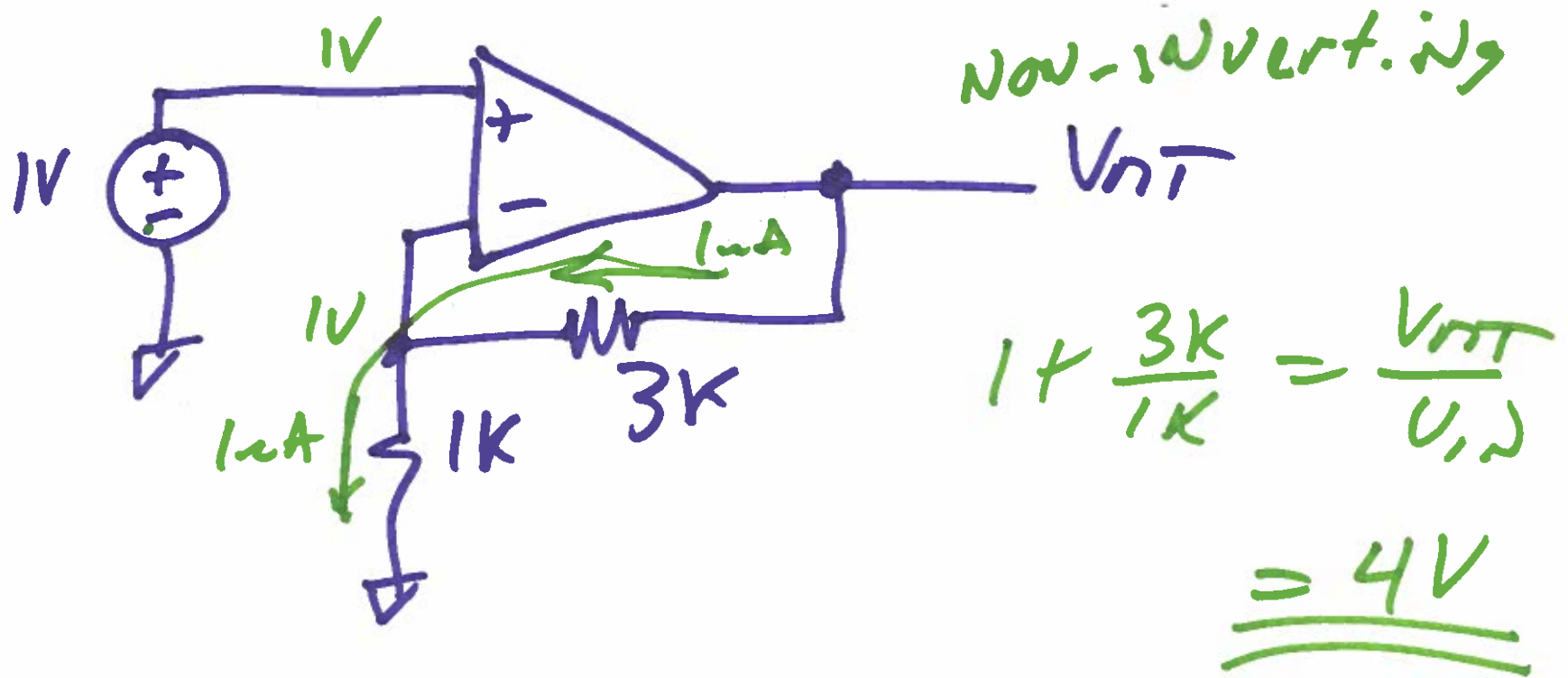

$$\frac{V_{out} - 1}{3k} = \frac{1}{1k}$$

$$V_{out} - 1 = 3$$

$V_{out} = 4V$

7)