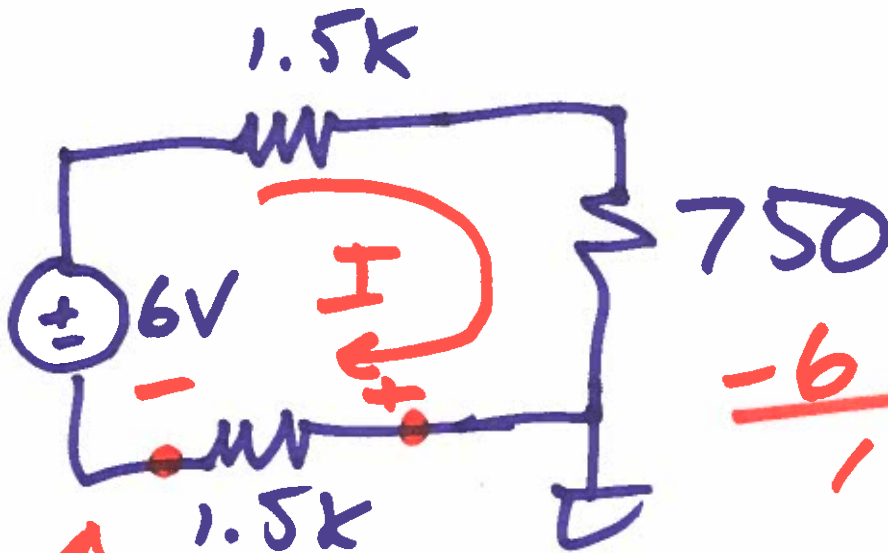


EE 220 Circuits 1

Lecture 12

OCT. 7, 2019






$$I = \frac{6}{1.5k + 750 + 1.5k}$$

$$\frac{-6 \cdot 6 \cdot 250}{15 \cdot 250} - \frac{6 \cdot 3 \cdot 500}{8 \cdot 500}$$

$$V_b = -1.5k \cdot I = \frac{-6 \cdot 1.5k}{1.5k + 750 + 1.5k}$$


$$V_b = -\frac{36}{15} = -\frac{12}{5} = \boxed{-2.4V}$$

1)

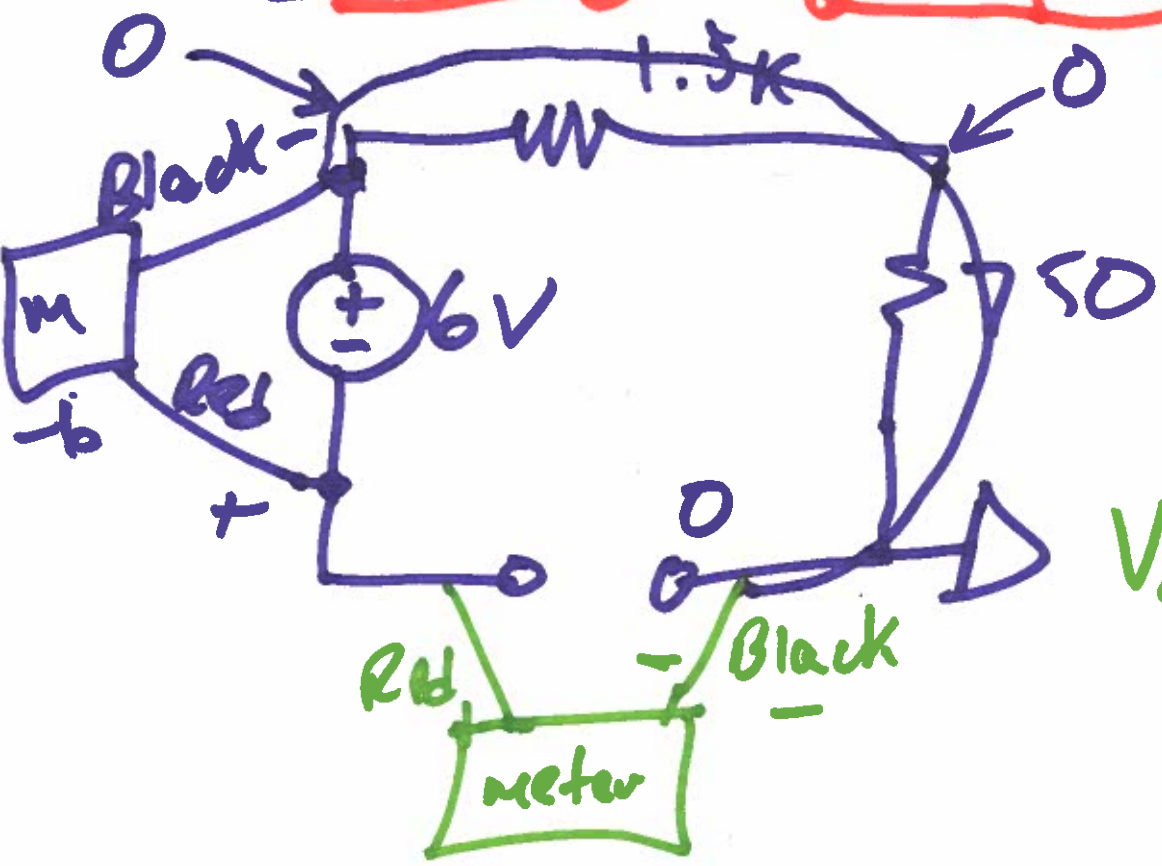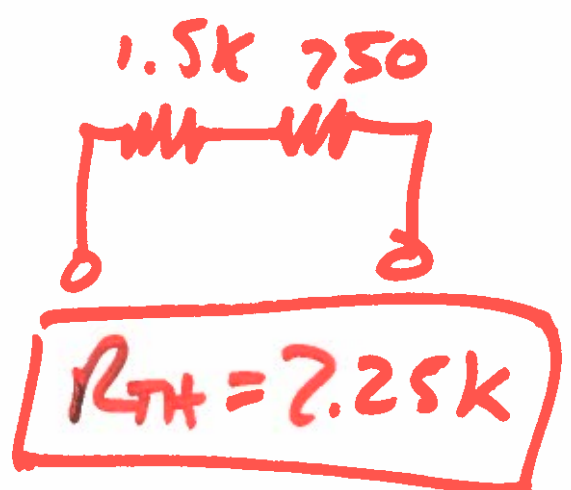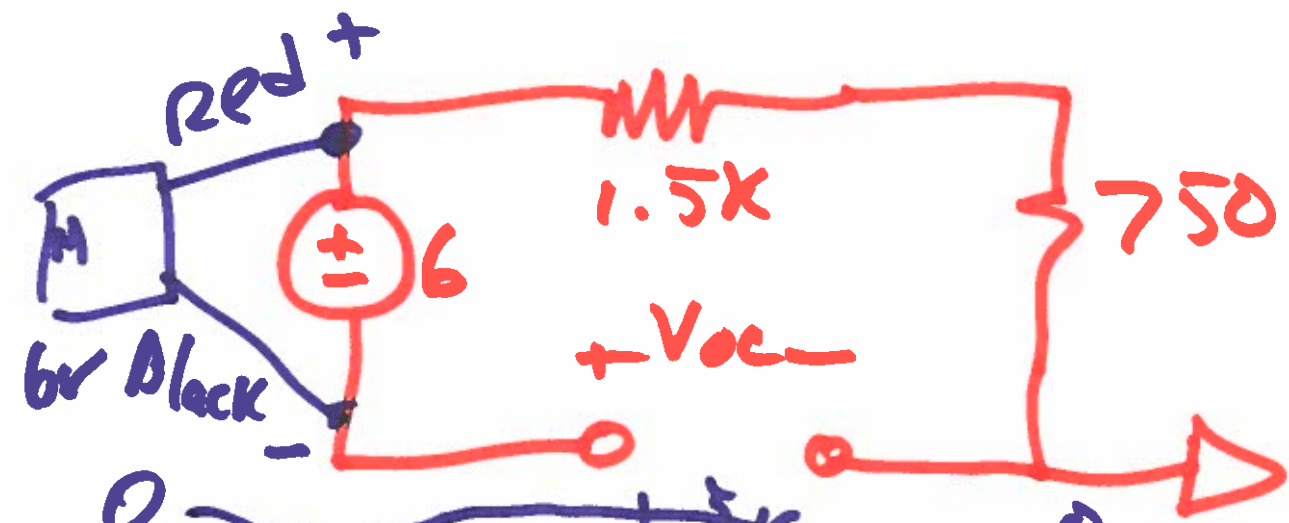

$$V_{oc} = -6V = V_{TH}$$


2)

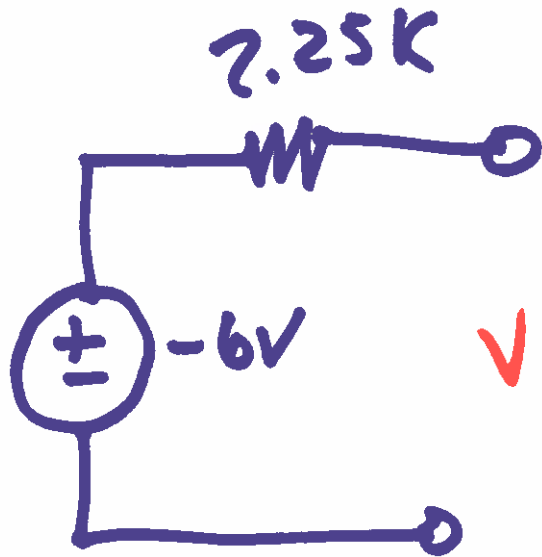


$$V_b = \frac{-6}{2.25k + 1.5k} \cdot 1.5k$$

I

$V_b = -2.4V$

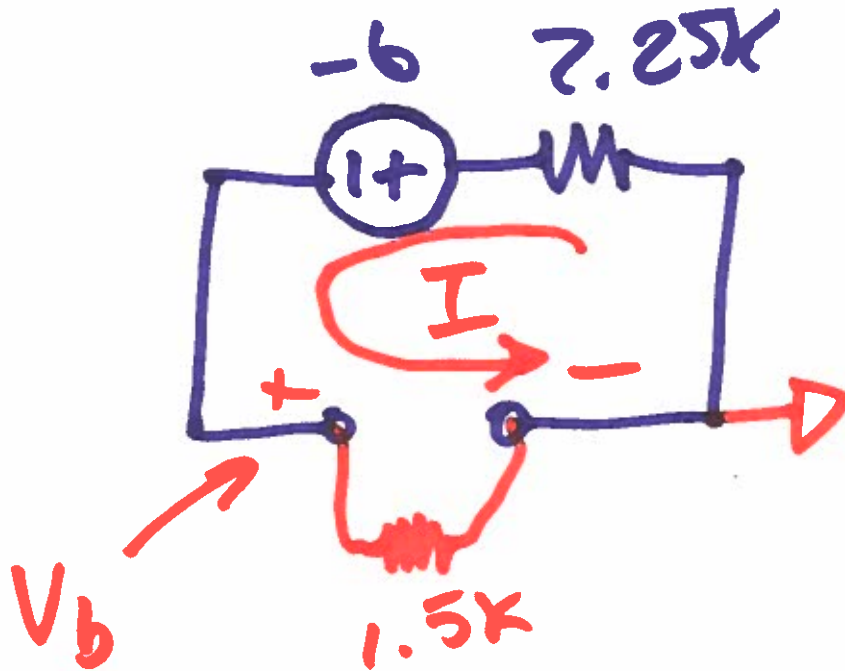

3)

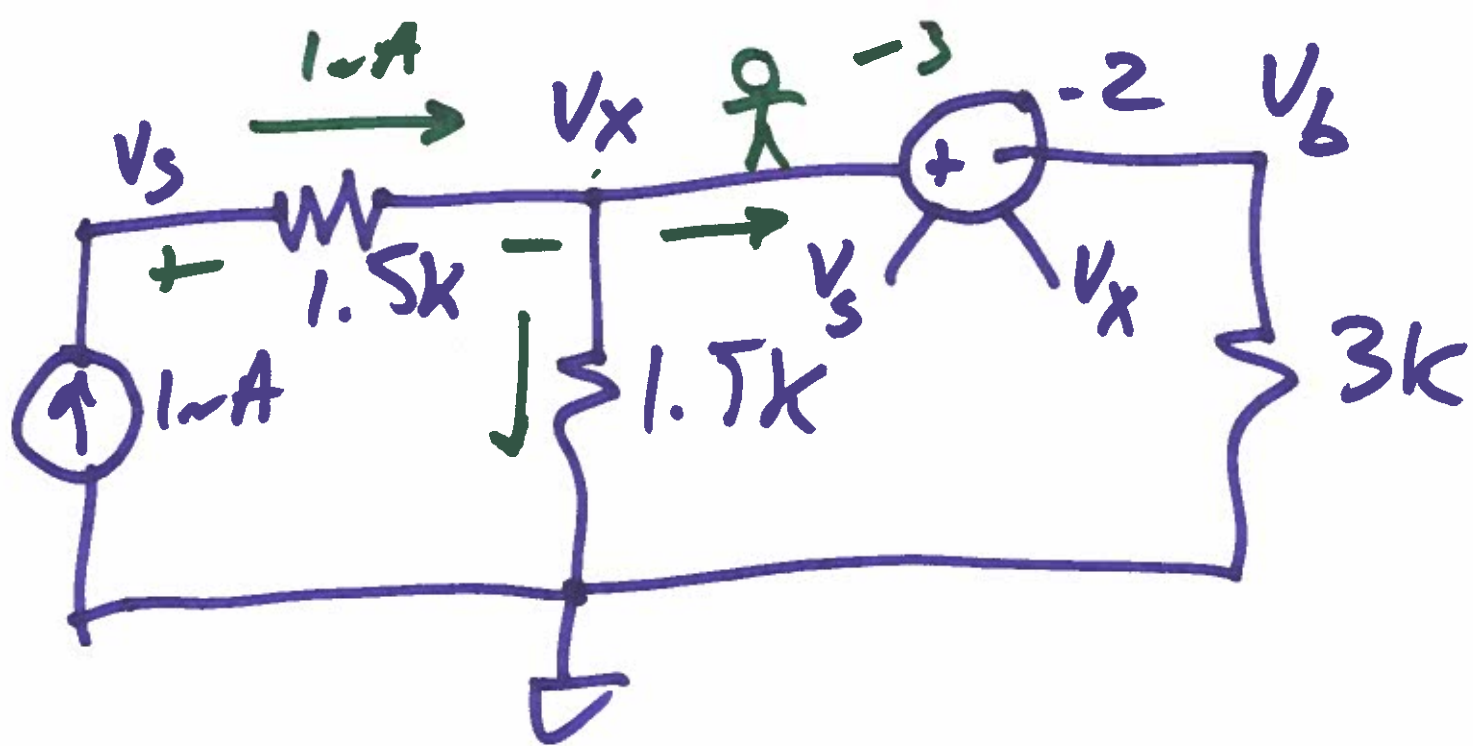


$$V_s - V_x = 1.5V$$

$$V_x - (-2)1.5 = V_b$$

$$\frac{V_b}{3k} + \frac{V_x}{1.5k} = 1mA$$

NON-INVERTING

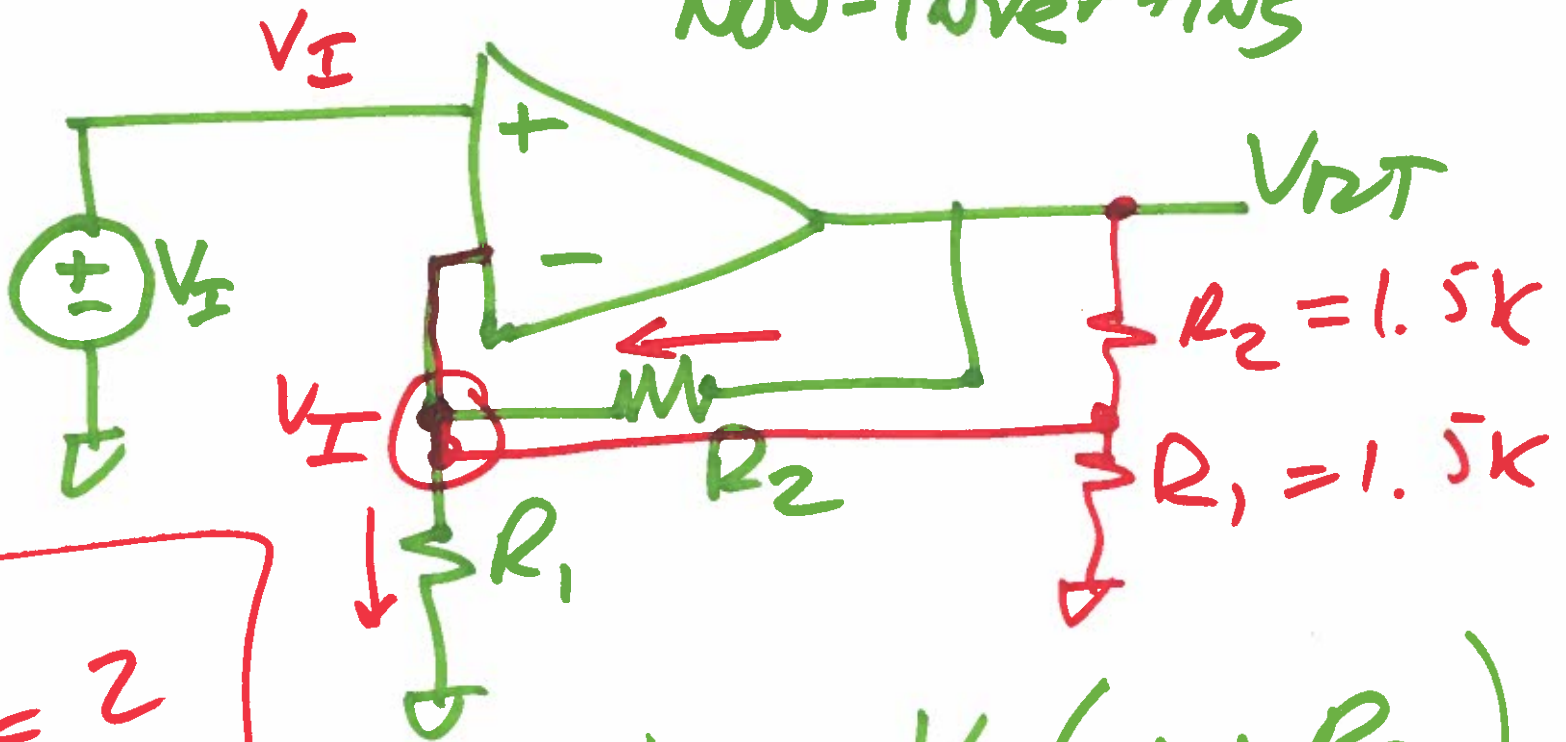

$$\frac{V_{OUT}}{V_{IN}} = 2$$


$$V_{OUT} = V_{IN} \left(1 + \frac{R_2}{R_1} \right)$$

$$\frac{V_{IN}}{R_1} = \frac{V_{OUT} - V_{IN}}{R_2},$$

$$V_{IN} \cdot \frac{R_2}{R_1} = V_{OUT} - V_{IN}$$

$$V_{OUT} = V_{IN} \left(1 + \frac{R_2}{R_1} \right)$$


$$V_{out} = 2V_{in}$$

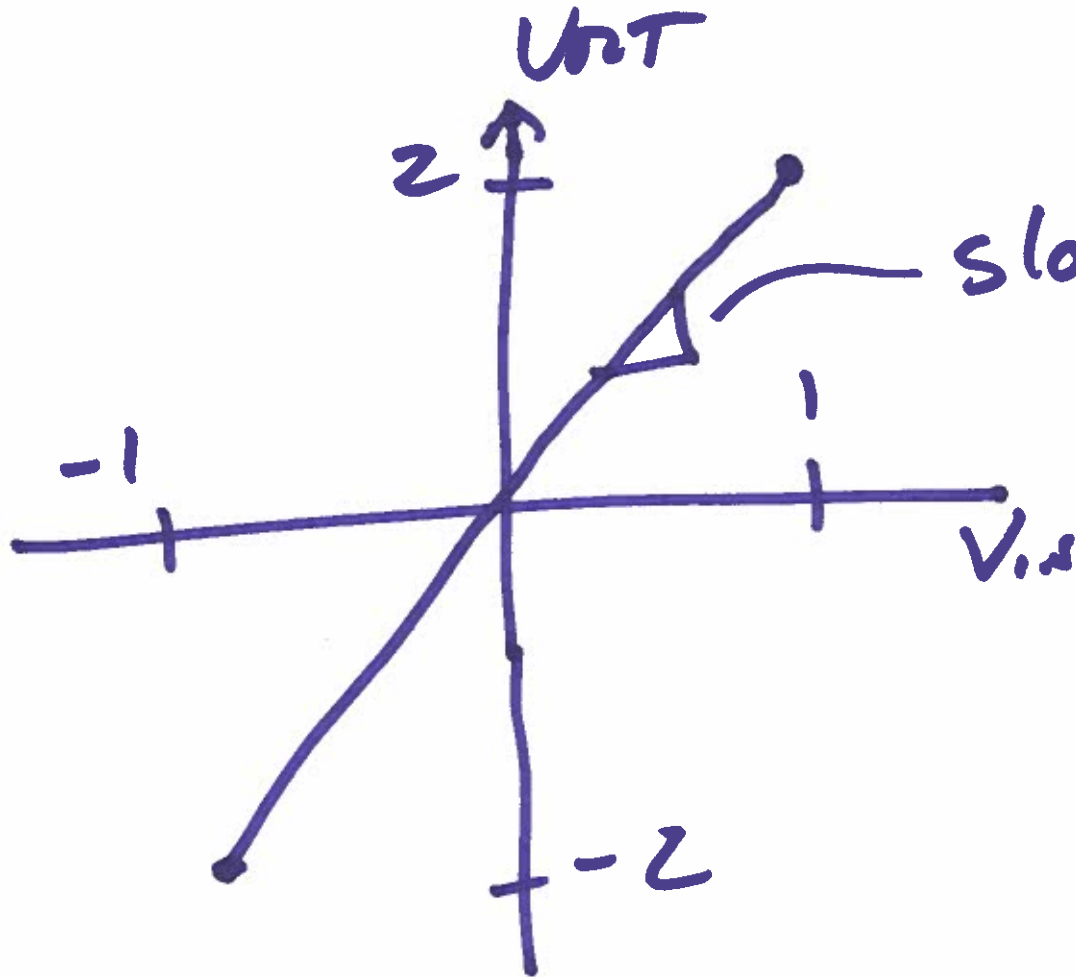


slope is the gain

$$\text{gain} = \frac{V_{out}}{V_{in}} = 2$$

b)

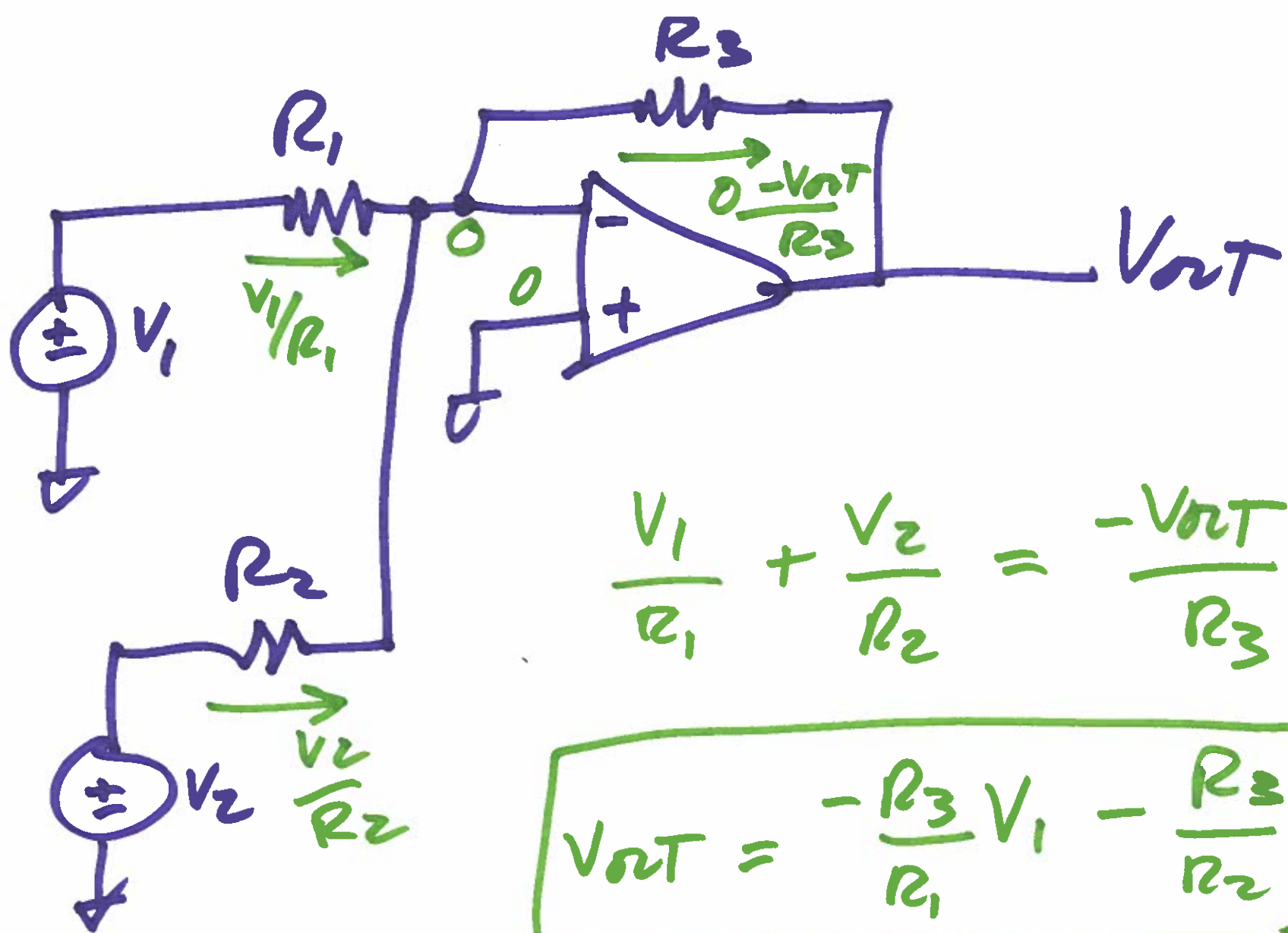

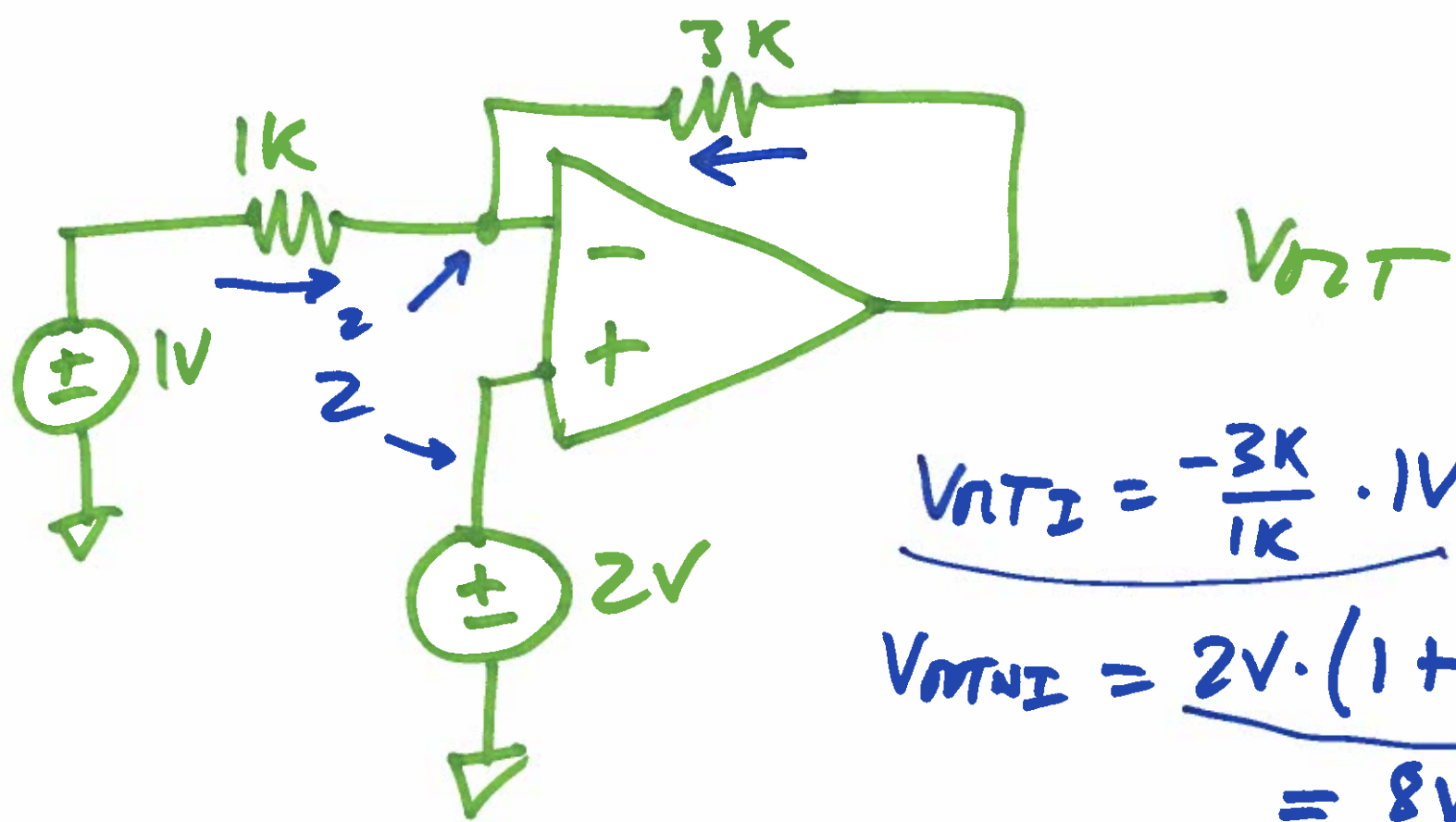

$$V_{out1} = \frac{-3k}{1k} \cdot 1V = -3$$


$$V_{out2} = \frac{2V \cdot \left(1 + \frac{3k}{1k}\right)}{=} = 8V$$

$$\frac{1-2}{1k} + \frac{V_{out} - 2}{3k} = 0 \quad V_{out} = 8 - 3 = 5V$$

$$2 - V_{out} = -3V$$

$V_{out} = 5V$


8)

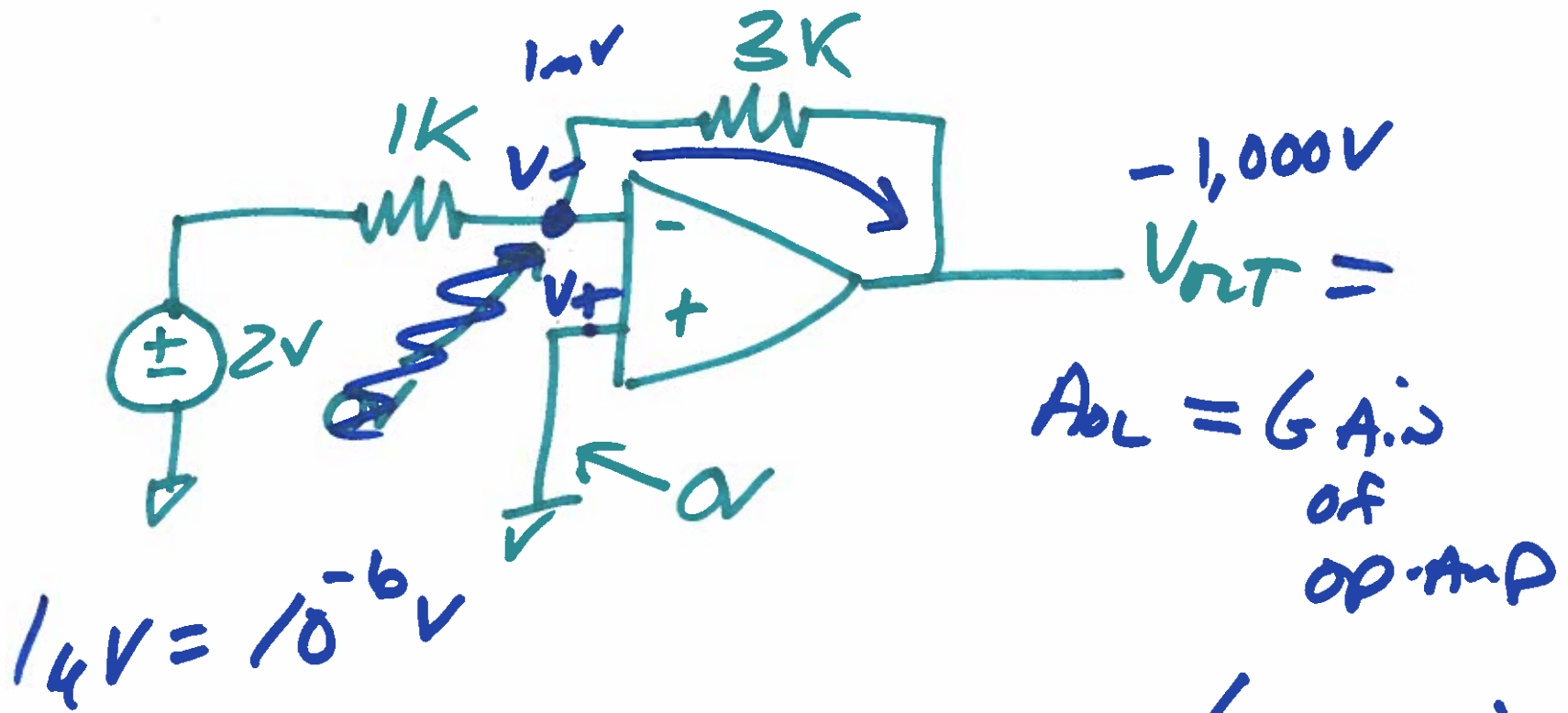

$$V_{OUT} = A_{OL} (V_+ - V_-)$$

$$-1,000V = -10^3 = 10^6 (0 - 1\mu V - 10^{-3})$$

9)

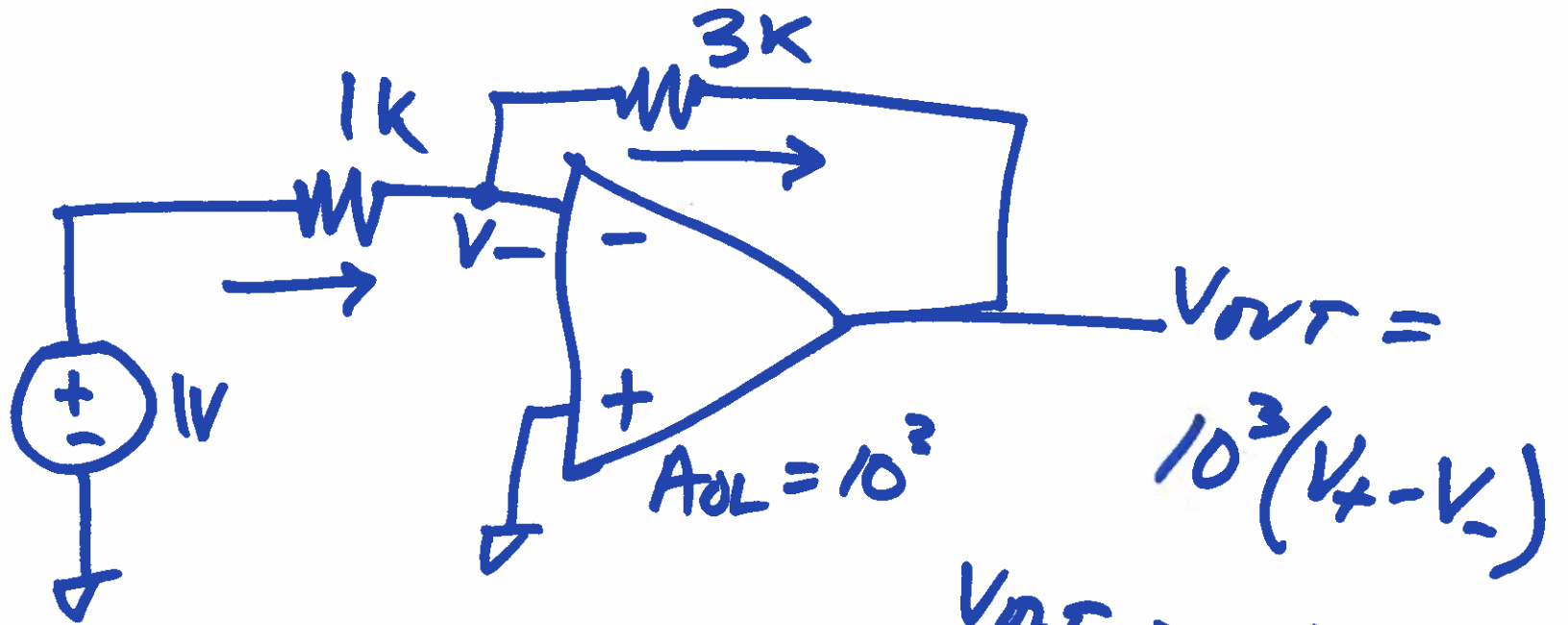

$$V_{OUT} = \frac{-3}{1.004} \quad | \quad -V_- = \frac{V_- - V_{OUT}}{3k}$$

$$V_{OUT} = -V_- \cdot 10^3 \quad | \quad V_- = \frac{-V_{OUT}}{10^3}$$

$$3 = V_{OUT} \left(\frac{3}{10^3} + \frac{1}{10^3} + 1 \right) + \frac{V_{OUT}}{10^3} = \frac{1}{3} \left(\frac{-V_{OUT}}{10^3} - V_{OUT} \right)$$

$$1 + .001 + .003$$

$$3 + \frac{V_{OUT} \cdot 3}{10^3} = \frac{-V_{OUT}}{10^3} - V_{OUT}$$

10)