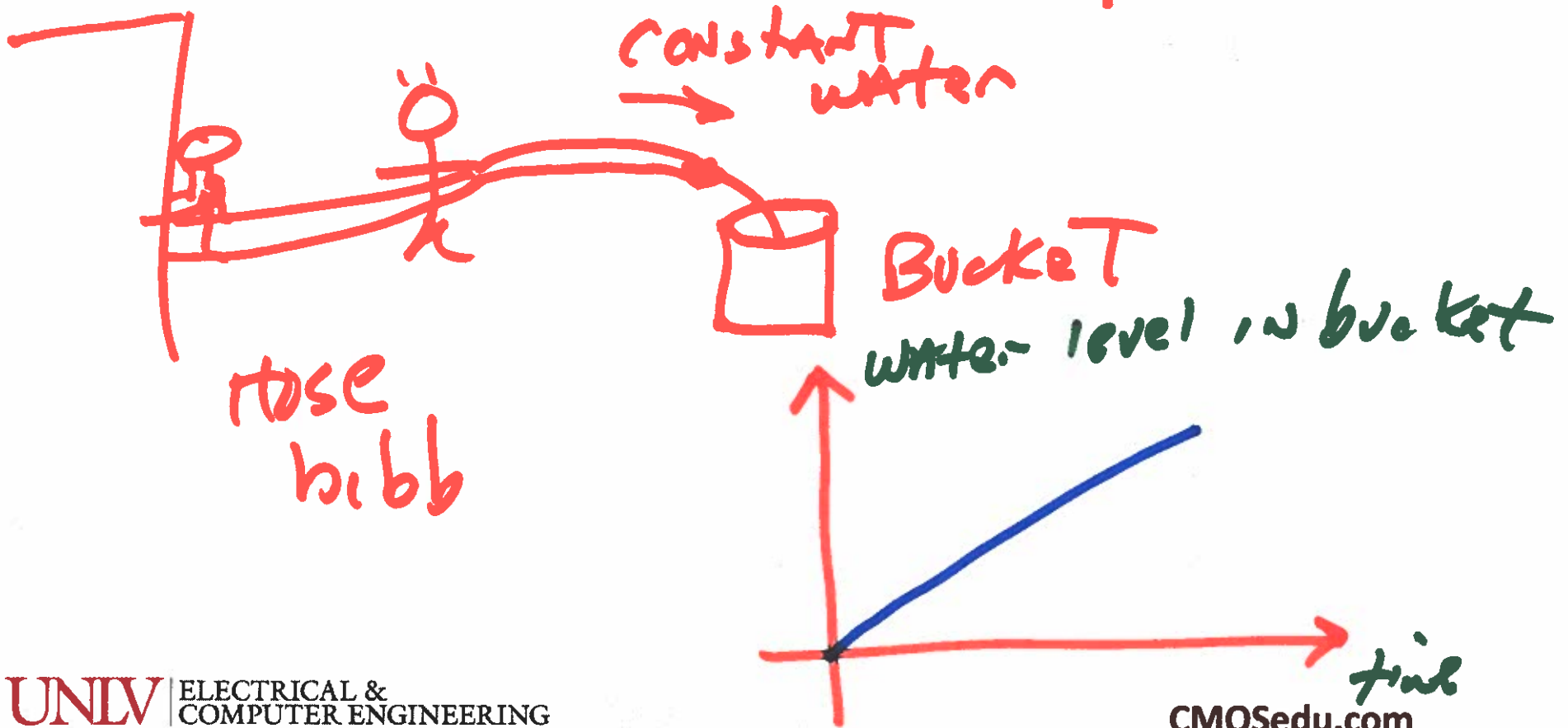


# EE 220 Circuits 1

## Lecture 184


OCT. 16, 2019

### Capacitors



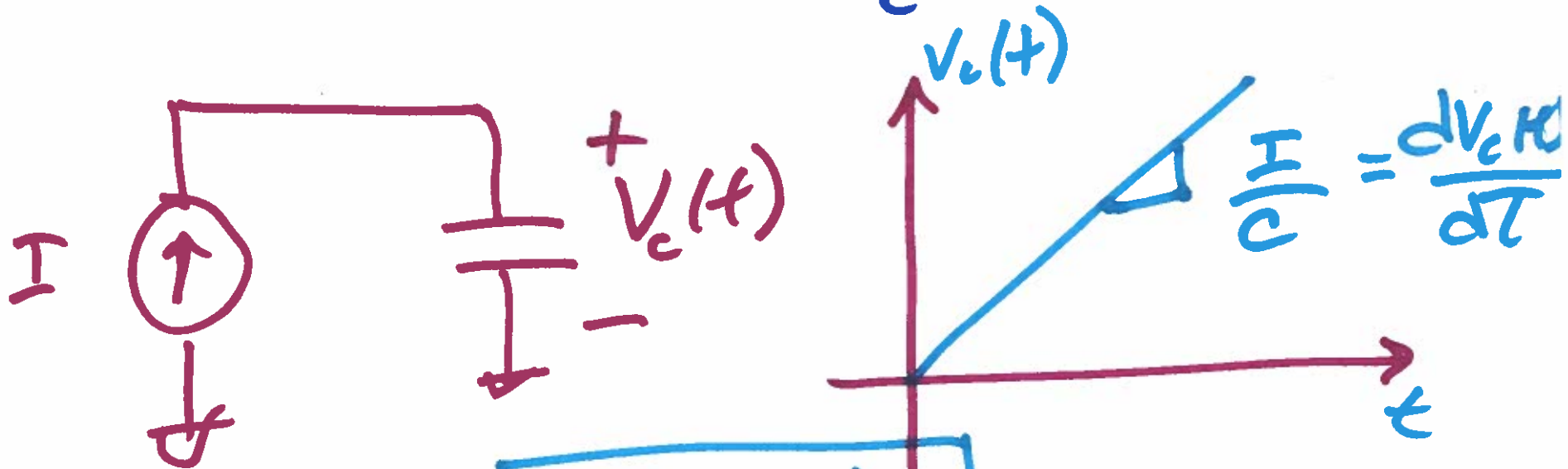1)

$\epsilon$  dielectric constant  $\rightarrow$  CAPACITOR (CAP)  
 $A = \text{Area of the plates}$   
 $C = \epsilon \cdot \frac{A}{t}$  (FARADS)




$$I = C \frac{dV_c}{dt}$$

Capacitance = Charge · Voltage


$$C = Q \cdot V \leftarrow$$

Coulombs

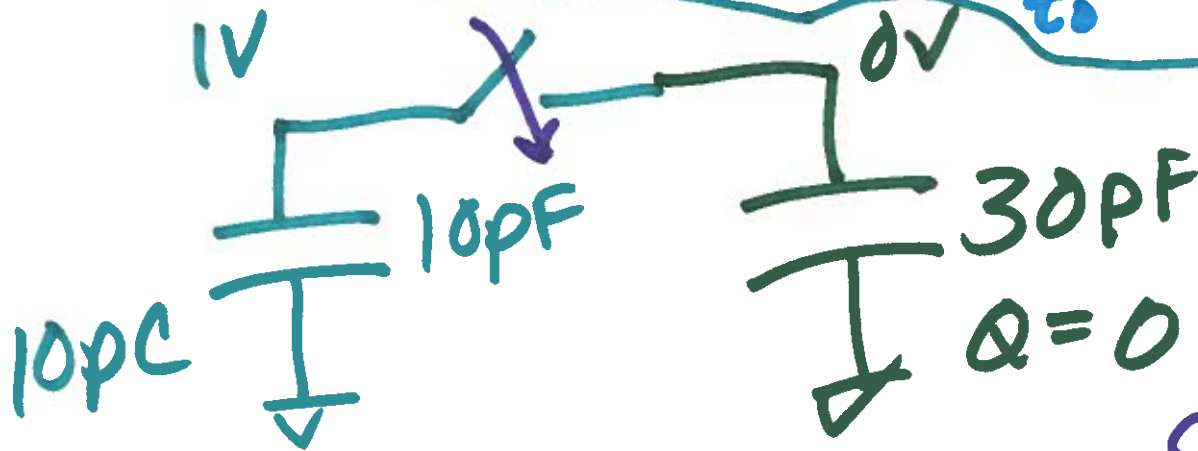
$$V_c(t) = \frac{1}{C} \int_{t_0}^t i(t) \cdot dt + V_c(t_0)$$



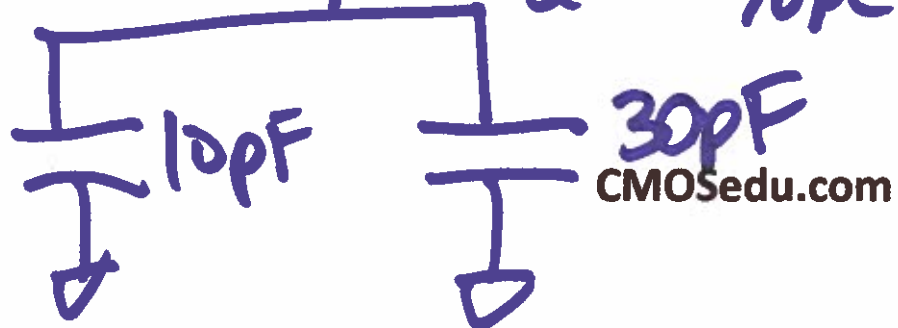
$$V_f = \frac{C}{Q} = \frac{40pF}{10pC} = 4V$$




3)

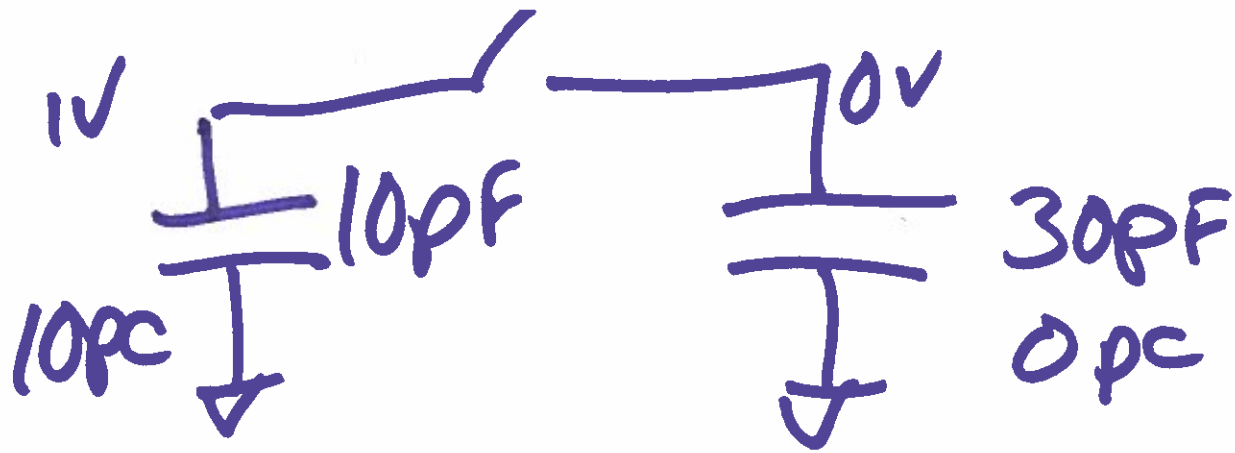
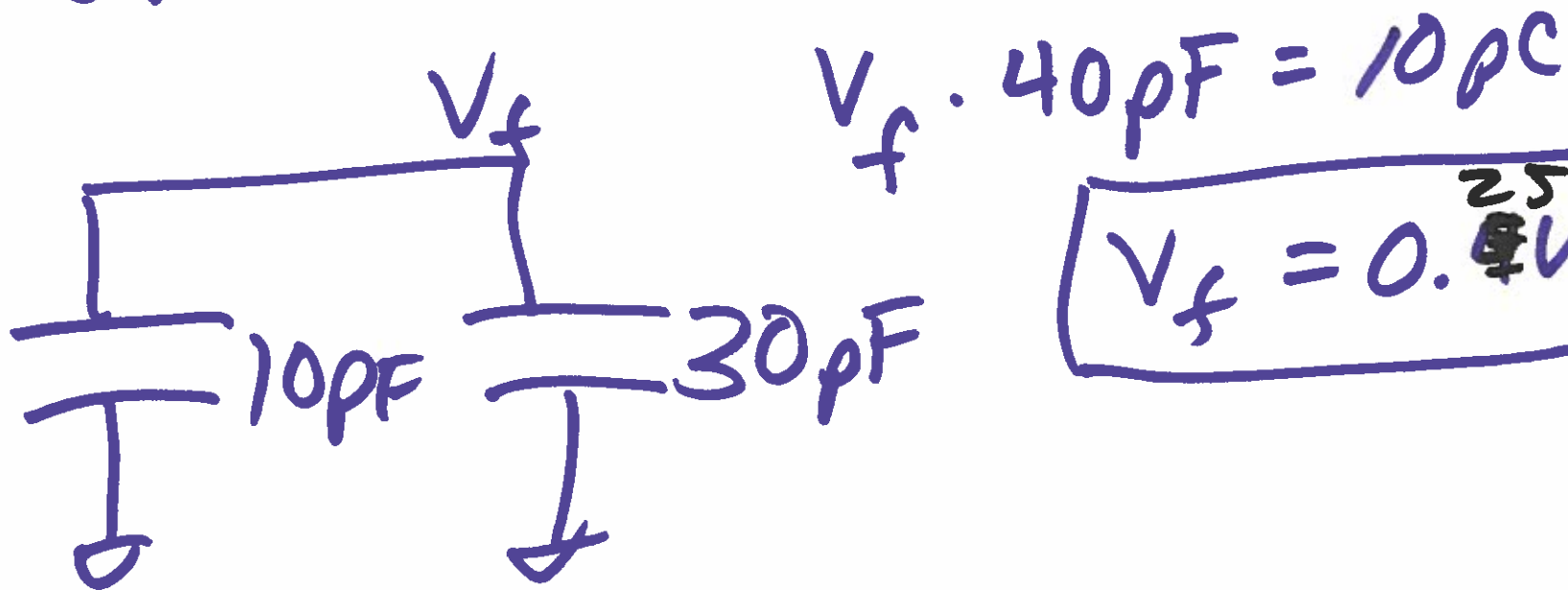
$$Q_{\text{before}} = 10pC + 0pC = 10pC$$



4)

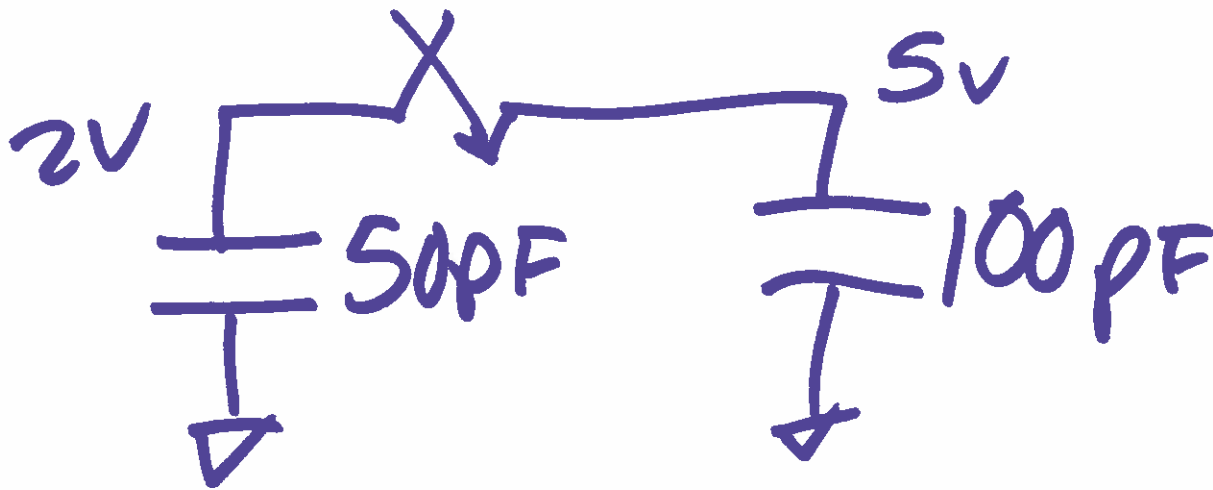

$$P = 10^{-12}$$

$$N = 10^{-9}$$

$$f = 10^{-15}$$

$$y = 10^{-6}$$

$$\underbrace{2 \cdot 50 \text{ pF} + 5 \cdot 100 \text{ pF}}_{\text{Before}} = \underbrace{V_f (150 \text{ pF})}_{\text{Charge after}}$$


$$V_f = \frac{600}{150} = \boxed{4 \text{ V} = V_f}$$

5)


$$I = C \frac{dV}{dt}$$

$$I = 14F \cdot \frac{1}{14} = 1A$$

$$I = 14F \cdot \frac{-2V}{14} = -2A$$

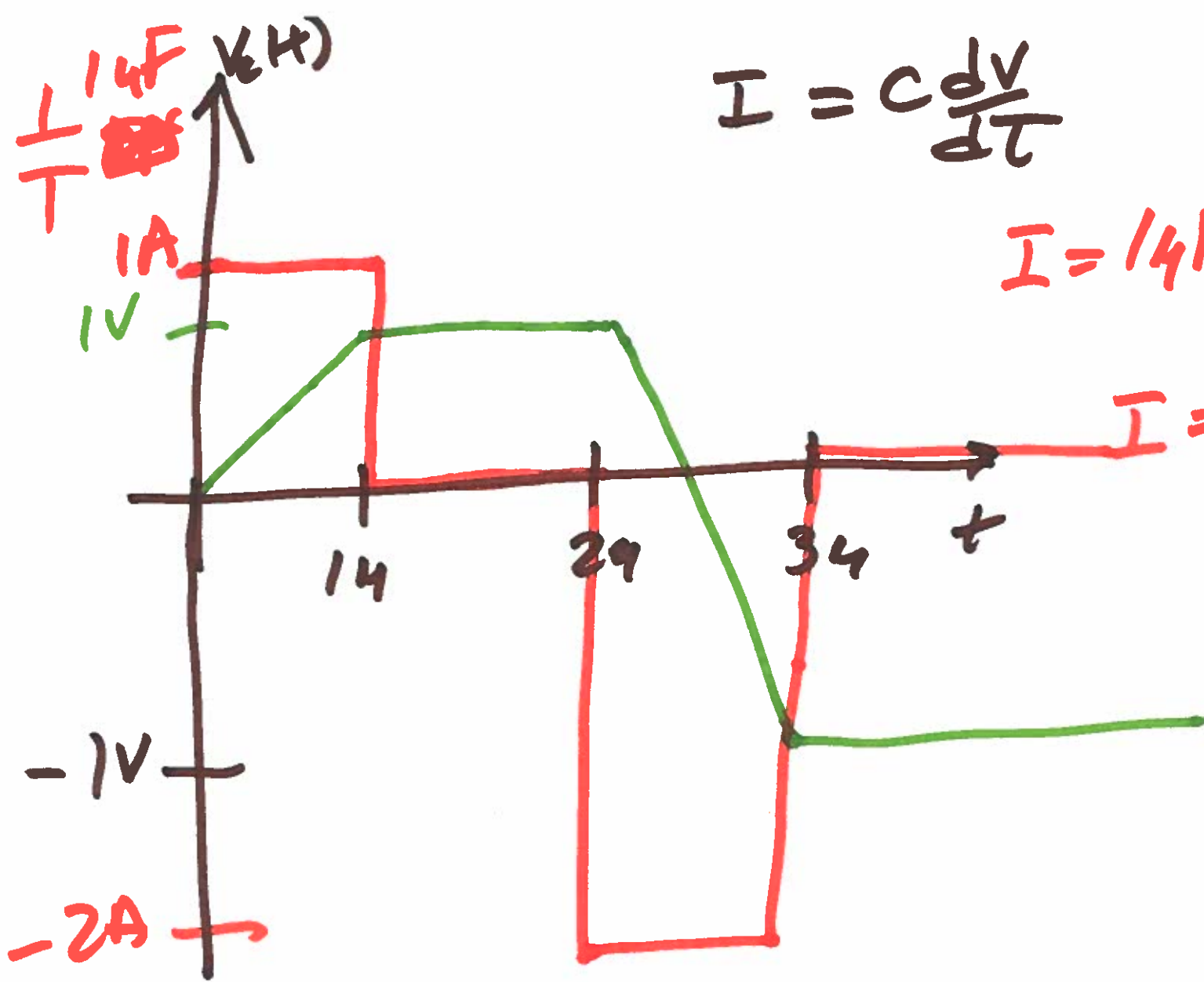


6)

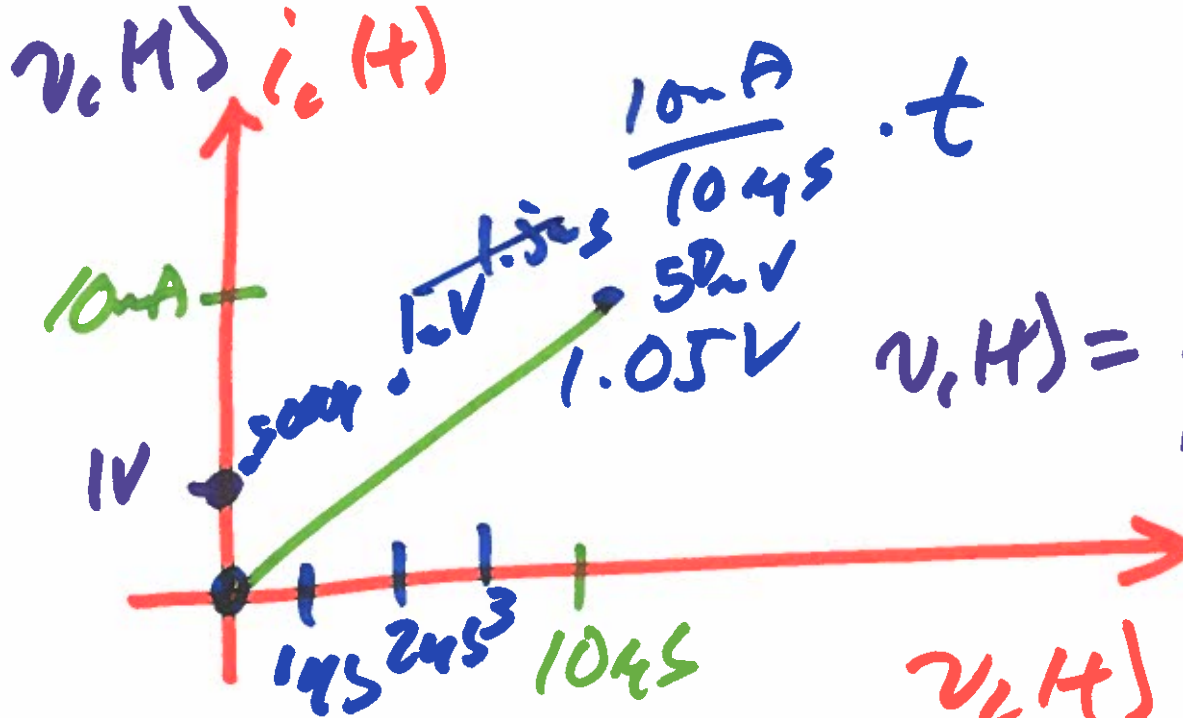

$$v_c(t) = \frac{1}{14F} \int_0^{1045} 10\mu A t dt + 1V$$

$$v_c(t) = \frac{10\mu A}{2 \cdot 10^{-6}} \cdot t \Big|_0^{1045} + 1$$

$$500 \cdot t^2$$

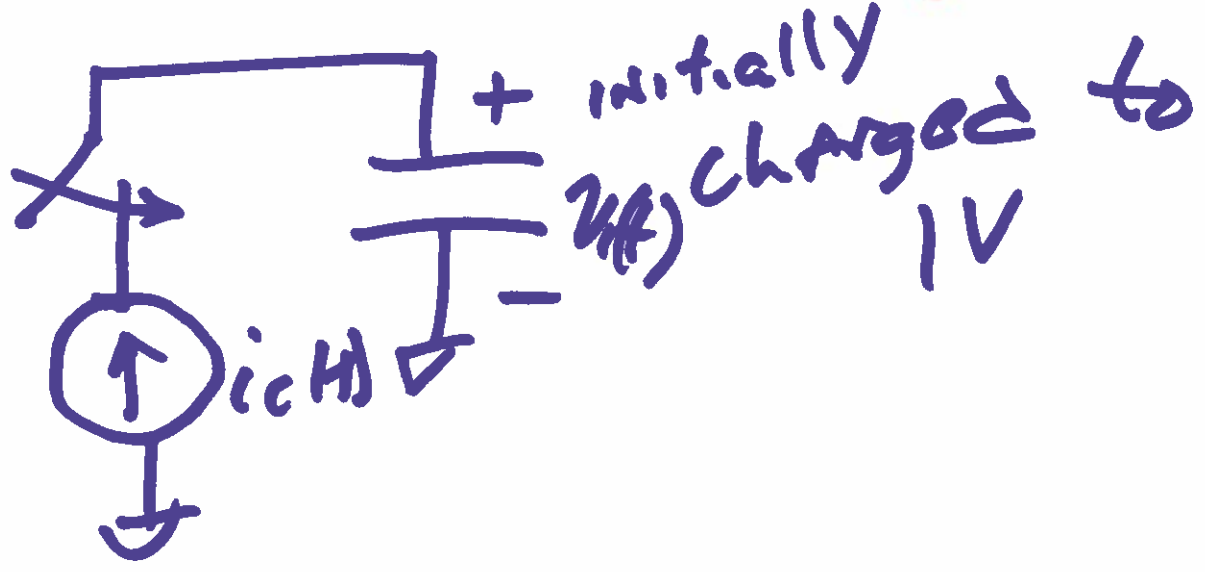

7)

$$i_c(t) = \frac{10 \mu\text{A} \cdot t}{10 \mu\text{s}} = \frac{10^{-3}}{10^{-6}} \cdot t = 10^3 t$$

$$v_c(t) = \frac{1}{1 \mu\text{F}} \int_0^{10 \mu\text{s}} 10^3 \cdot t \cdot dt + 1$$

$$= 10^6 \cdot 10^3 \cdot \frac{1}{2} t^2 + 1$$


$$v_c(t) = \frac{10^9}{2} \cdot t^2 + 1$$

$$t = 10 \mu\text{s} = \frac{10^9 \cdot 10^{-12}}{2} + 1$$

$$t = 10 \mu\text{s} = \frac{10^9 \cdot 10^{-12} \cdot 100}{2} + 1$$

500 μV  
50 mV



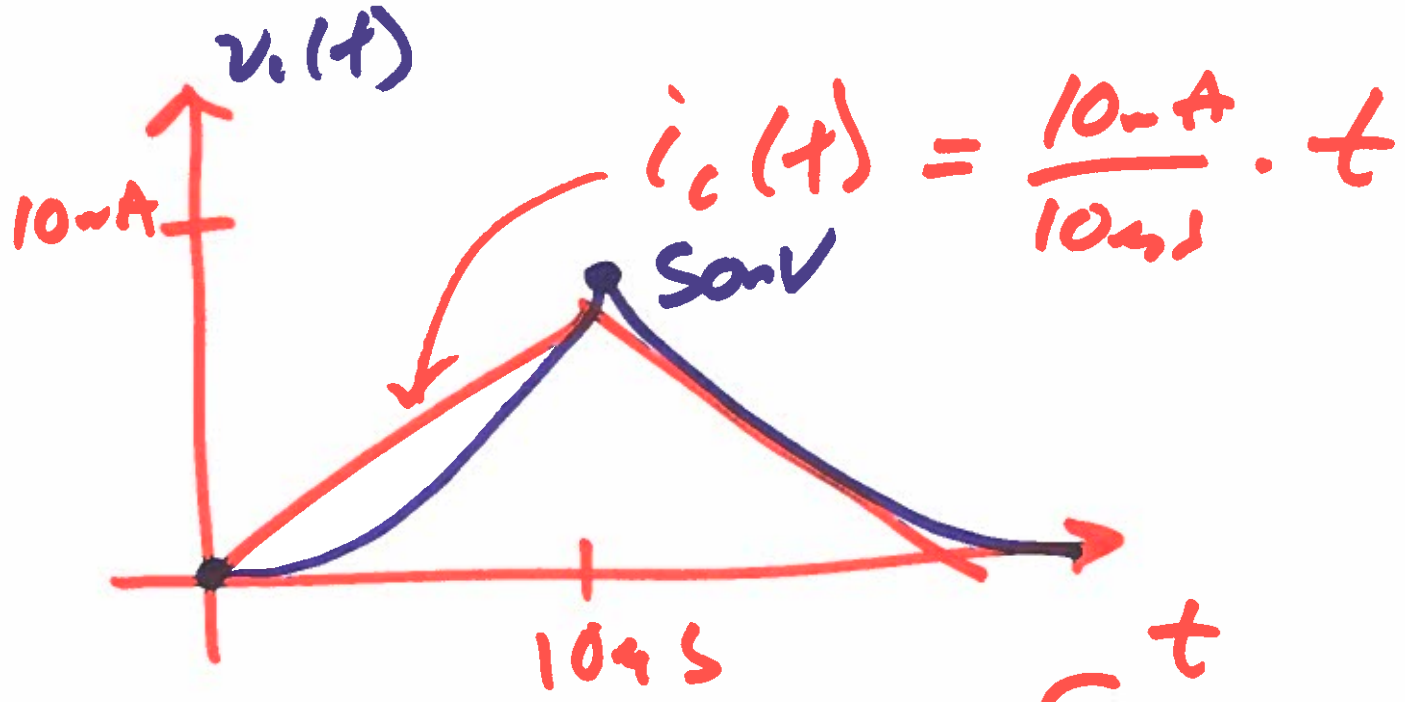

$$v_c(t) = \frac{1}{1\text{f}} \cdot \int_0^t \frac{10\text{mA}}{10\text{ns}} \cdot t \cdot dt$$

$$\frac{10^{-1}}{2} = \frac{0.1}{2} = 50\text{nV} = \frac{10 \cdot 10^{-3}}{10 \cdot 10^{-9} \cdot 10 \cdot 10^{-6}} \cdot \frac{1}{2} t^2$$

$$= \frac{10^9}{2} t^2$$

$t = 10\text{ns}$   
 $\frac{10^9 \cdot 10^{-9} \cdot 10^{-9}}{2}$

9)

