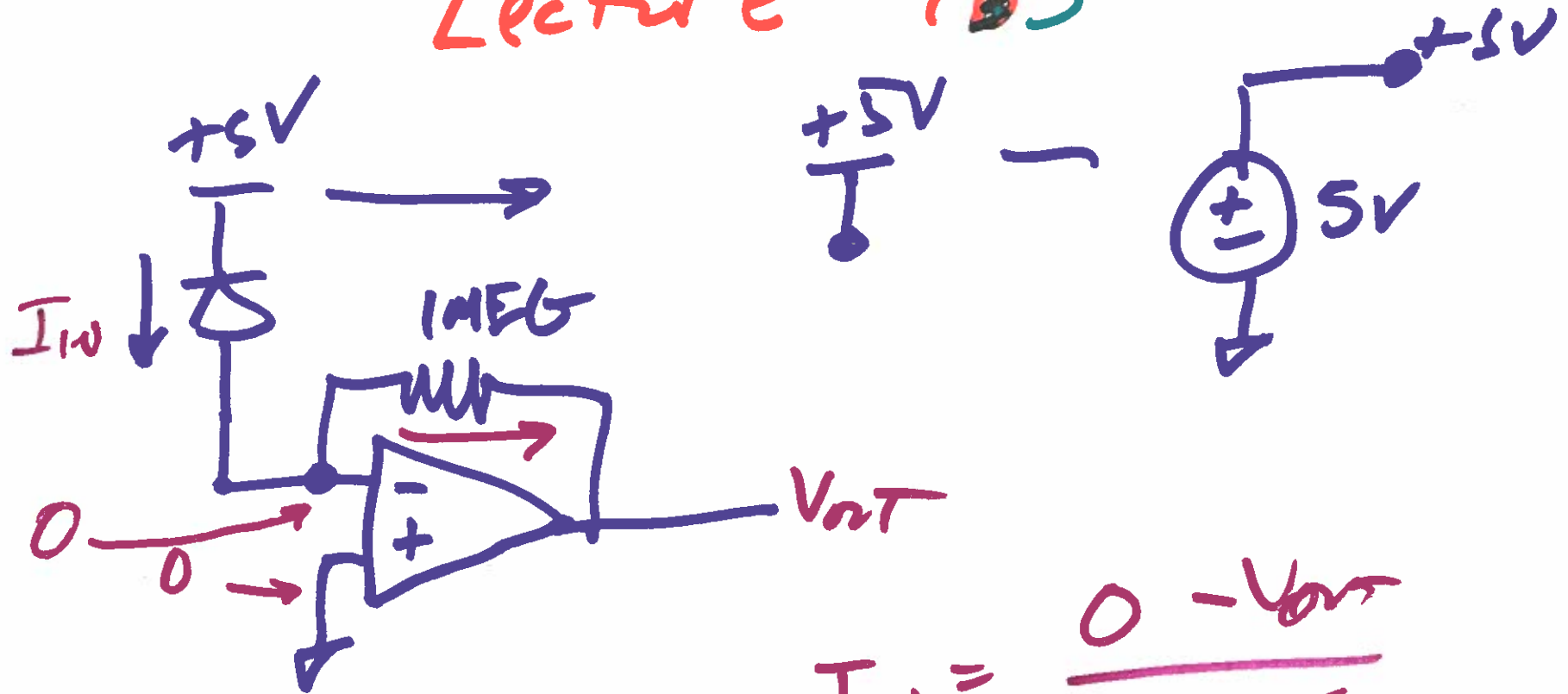


EE 220 Circuits I

OCT. 21, 2019


Lecture 15



$$I_{in} = \frac{0 - V_{out}}{1M\Omega}$$

$$V_{out} = -I_{in} \cdot 1M\Omega$$

1)

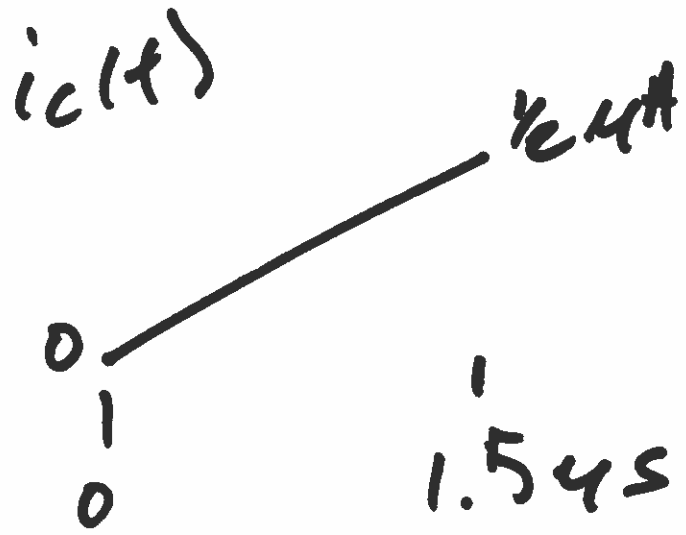

$$i_c(t) = \frac{0.54 \text{ A}}{1.54 \text{ s}} \cdot t$$

$$= \frac{1}{3} t$$

$$\frac{1}{10^9} = \frac{1}{10 \times 10^{12}} = \frac{1}{10^{11}} = 10^{-11}$$


$$v_c(t) = \frac{1}{C} \int_0^t i_c(t) \cdot dt$$

$$= 10^{-11} \int_0^t \frac{1}{3} t \cdot dt$$

$$= 10^{-11} \frac{1}{6} t^2$$

$100^6 = 10^{12}$
 $100 \cdot 10^9 = 10^{11}$
 $0.1 \cdot 10^{12} = 0.1 \text{ T}$



2)

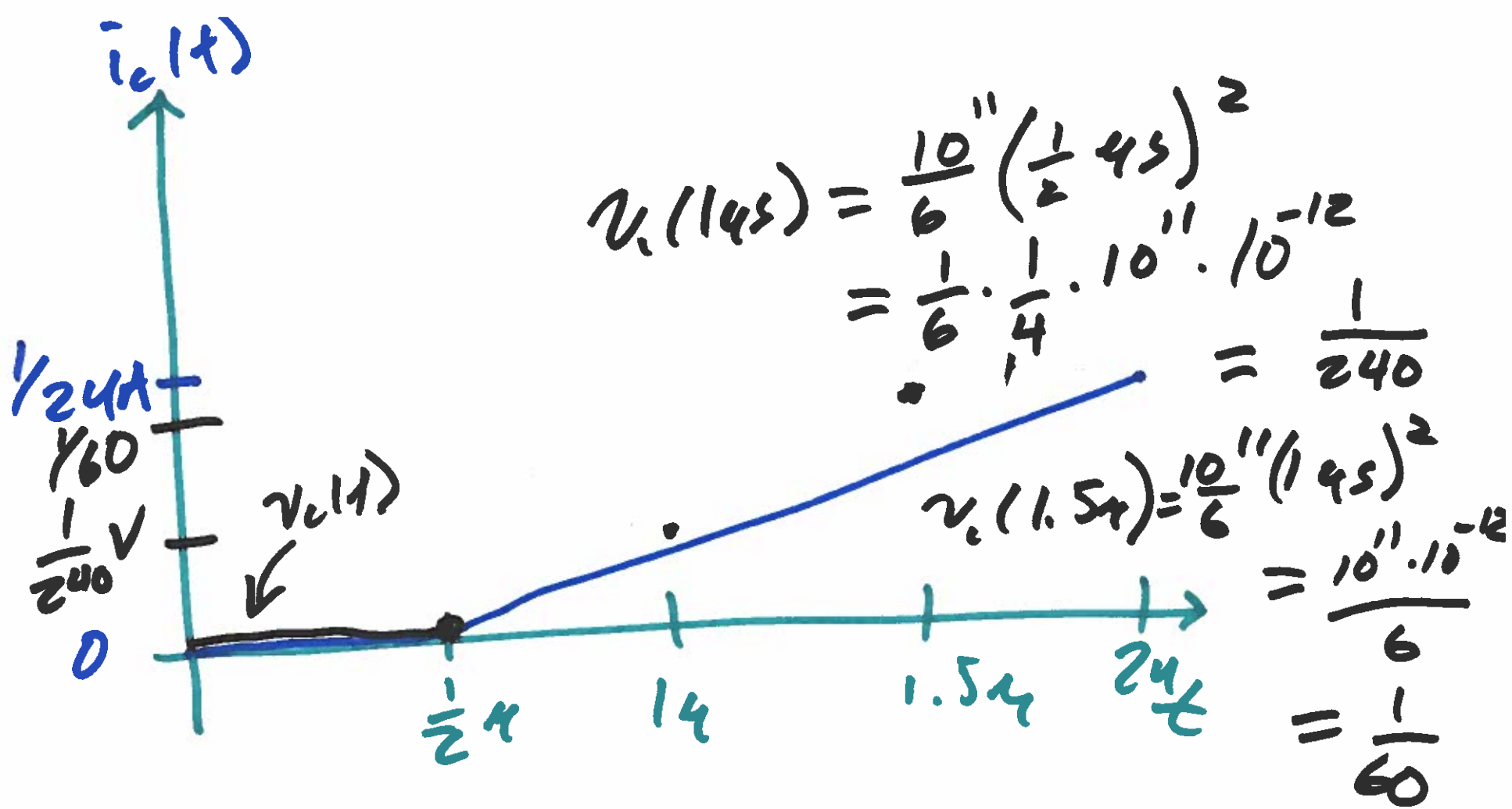


$$v_c(t) = \frac{10^{-11}}{6} t^2 \quad 0 < t < 1.54$$

$$v_c(t) = \frac{10^{-11}}{6} \left(t - \frac{1}{24}s\right)^2 \quad \frac{1}{24} \leq t \leq 2.04$$

3)

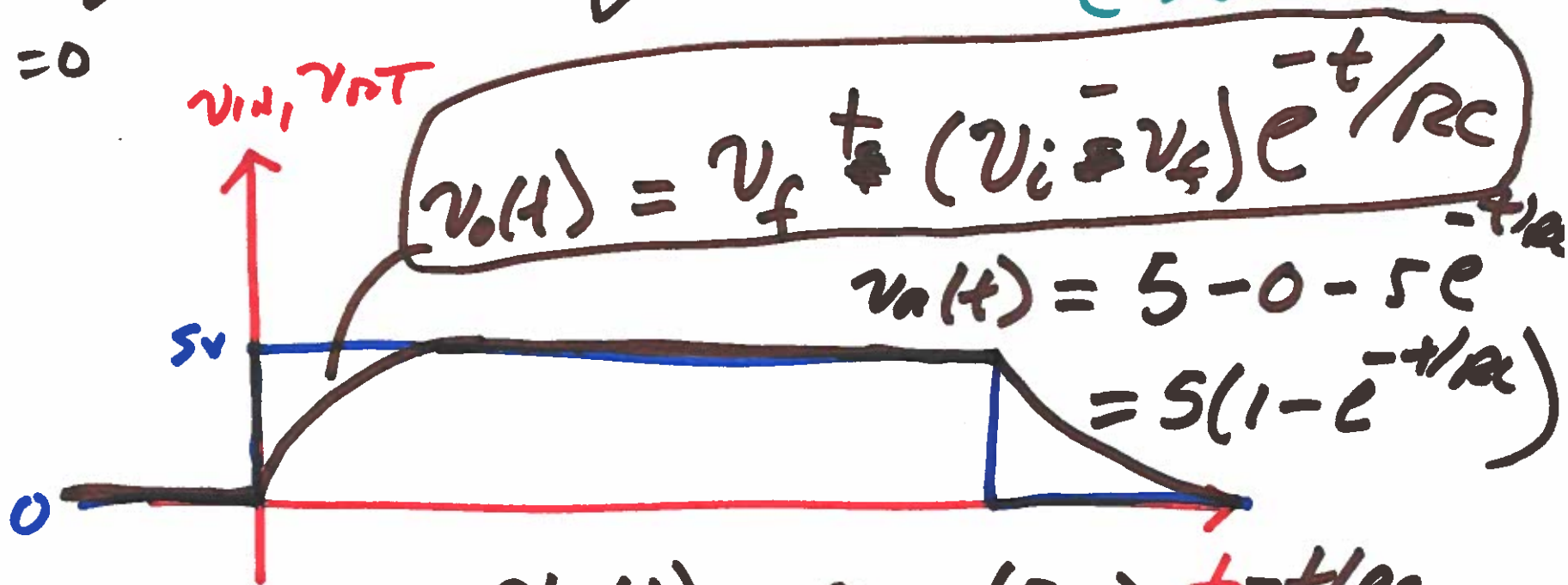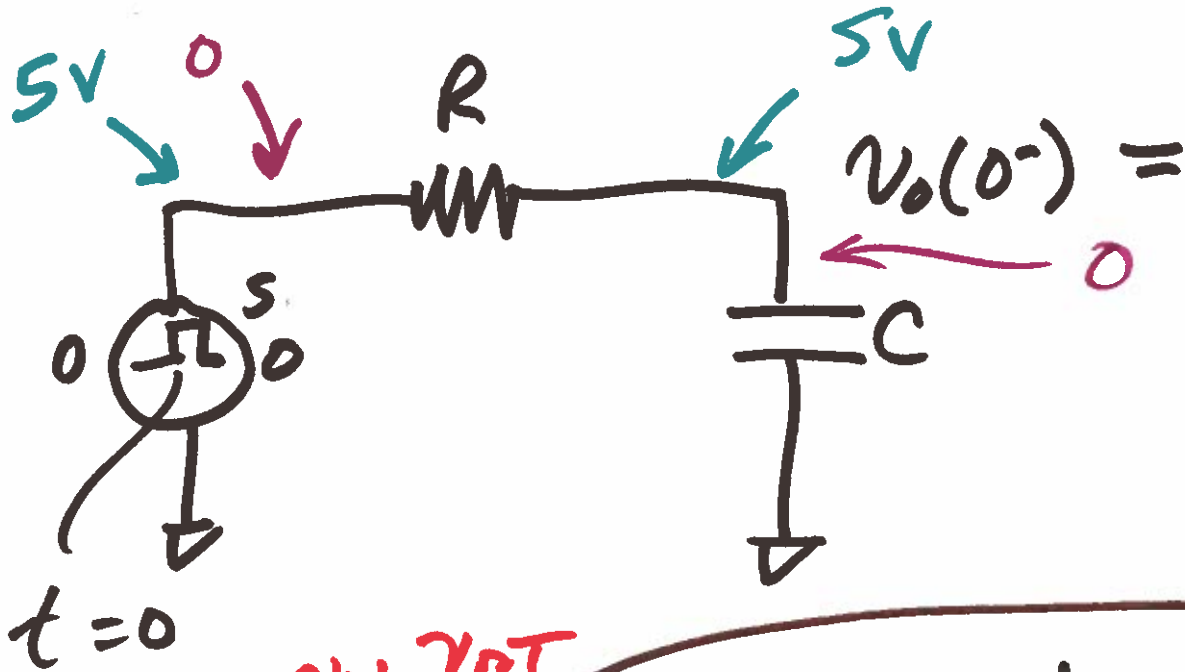
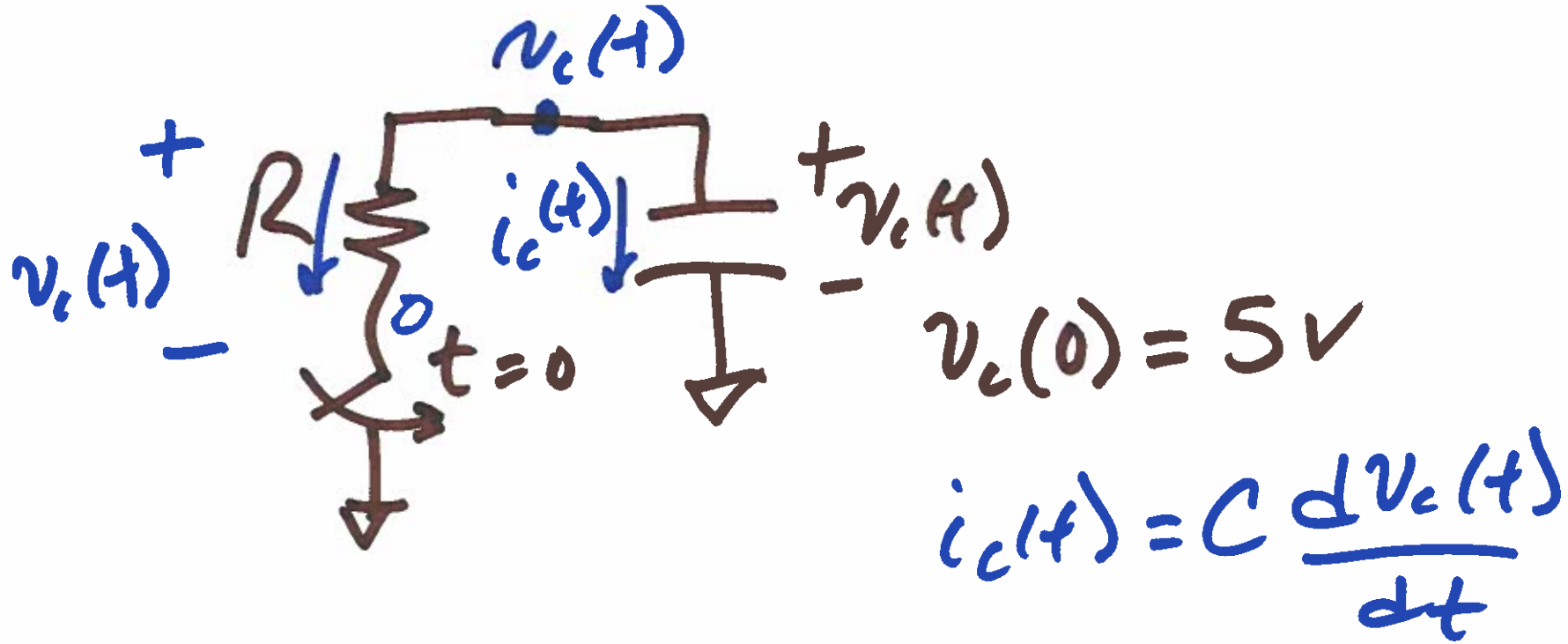
$$v_o(t) = 0 + (5 - 0)e^{-t/RC} = 5e^{-t/RC}$$



$$\frac{v_r(t)}{R} + C \frac{dv_c(t)}{dt} = 0$$

$$\frac{v_c(t)}{R} = -C \frac{dv_c(t)}{dt}$$

$$\int_0^t \frac{dt}{-RC} = \int_{V_c(0^-)}^{V_c(t)} \frac{dV_c(t)}{V_c(t)}$$

$$\frac{t}{-RC} = \ln x$$


$$-\frac{t}{RC} = \ln \frac{V_c(t)}{V_i}$$

$$V_c(t) = V_i e^{-t/RC}$$



b)

$\tau = RC = \text{time constant}$

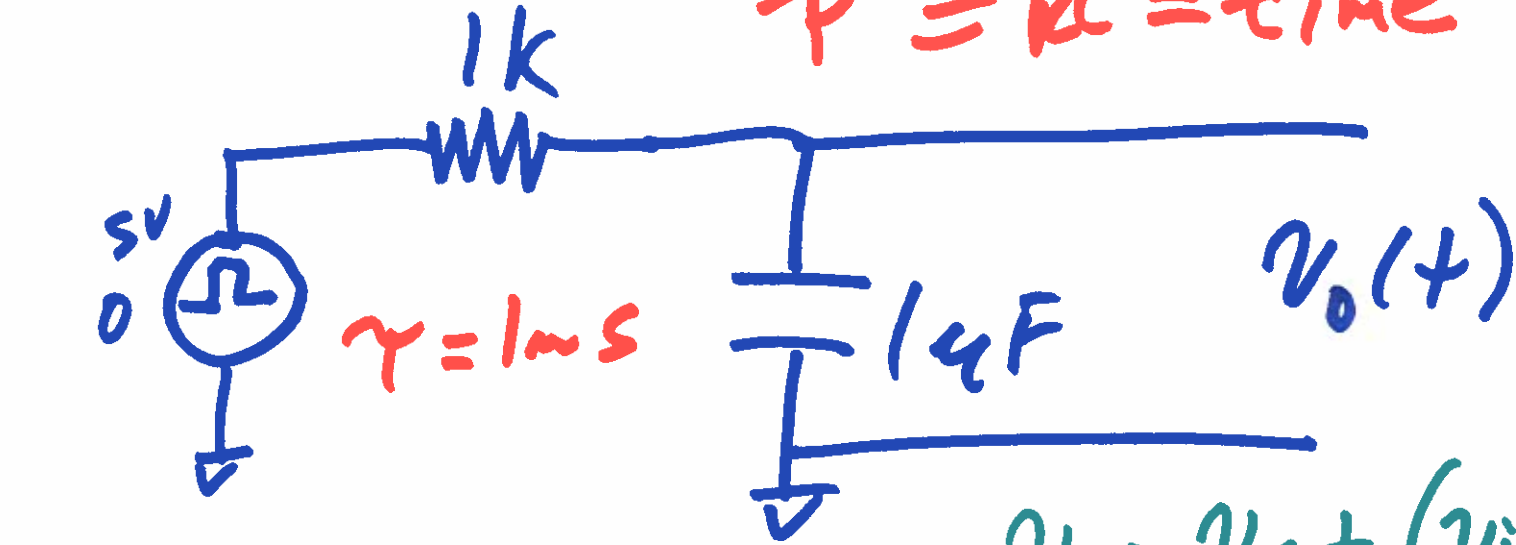

$$v_o = v_f + (v_i - v_f) e^{-t/\tau}$$

INPUT

$0 \rightarrow 5$

$$v_i = 0, v_f = 5V$$

$$v_o(t) = 5 + (0 - 5) e^{-t/1ms}$$

$$v_o(t) = 5(1 - e^{-t/1ms})$$


INPUT

$5 \rightarrow 0$

$$v_i = 5, v_f = 0$$

$$v_o(t) = 5e^{-t/1ms}$$

7)

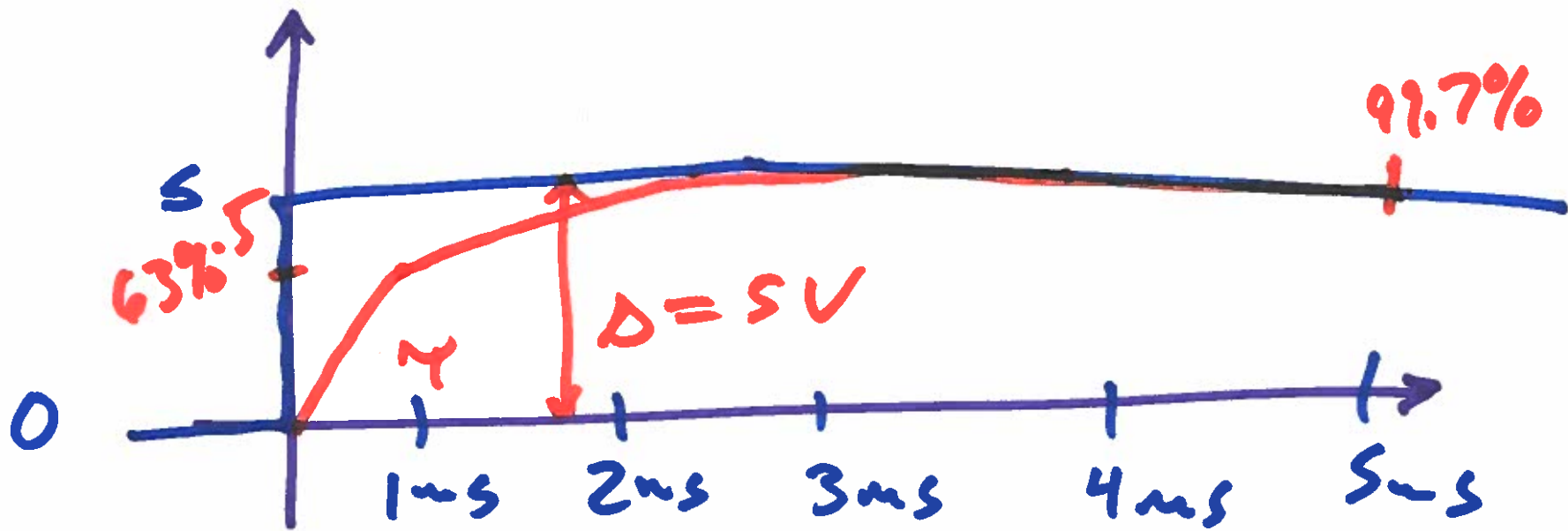

MEMORIZE

63% of transition
5V

1τ 5τ is settled

$$\frac{1}{e^5} \approx 0$$

$$t = 1 \mu s$$


$$v_o(t) = 5 \left(1 - \frac{1}{e} \right)$$

$$5(1 - .37)$$

$$5 \cdot 63\%$$

99.7%

8)

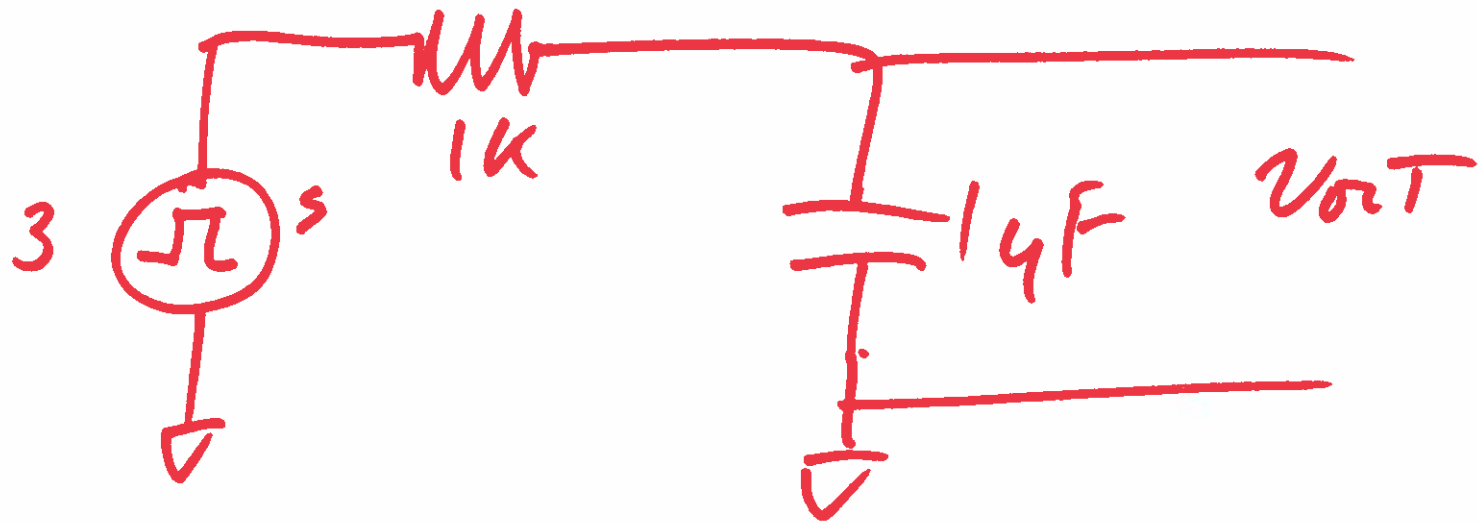

INPUT

$$3 \rightarrow 5$$

$$v_i = 3, v_f = 5$$

$$v_o(t) = 5 + (3 - 5)e^{-t/1\mu s}$$

$$5 - 3$$

$$v_i = 5$$

$$v_f = 3$$

$$v_o(t) = 3 + (5 - 3)e^{-t/1\mu s}$$

$$-t/1\mu s v_o(t) = 5 + (-2v)e^{-t/1\mu s}$$

