

# EE 220 Circuits 1

OCT. 30, 2019

## Lecture 18

$$V = L \cdot \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{V}{L}$$

$$v_L(t) = \frac{1V}{100\mu} \cdot t$$

$$i_L(t) = \frac{1}{400\mu} \int_0^{100\mu} \frac{1}{100\mu} t \cdot dt$$



$\Delta \frac{1}{2}$

$125 \cdot 10^8$

$$12.5 \cdot 10^6 \cdot t^2 = \frac{1}{4 \cdot 10^4 \cdot 10^{-12}} \frac{t^2}{2} \Big|_0^t$$

$$(t - 100\mu)^2$$

$$100\mu \leq t \leq 200\mu$$

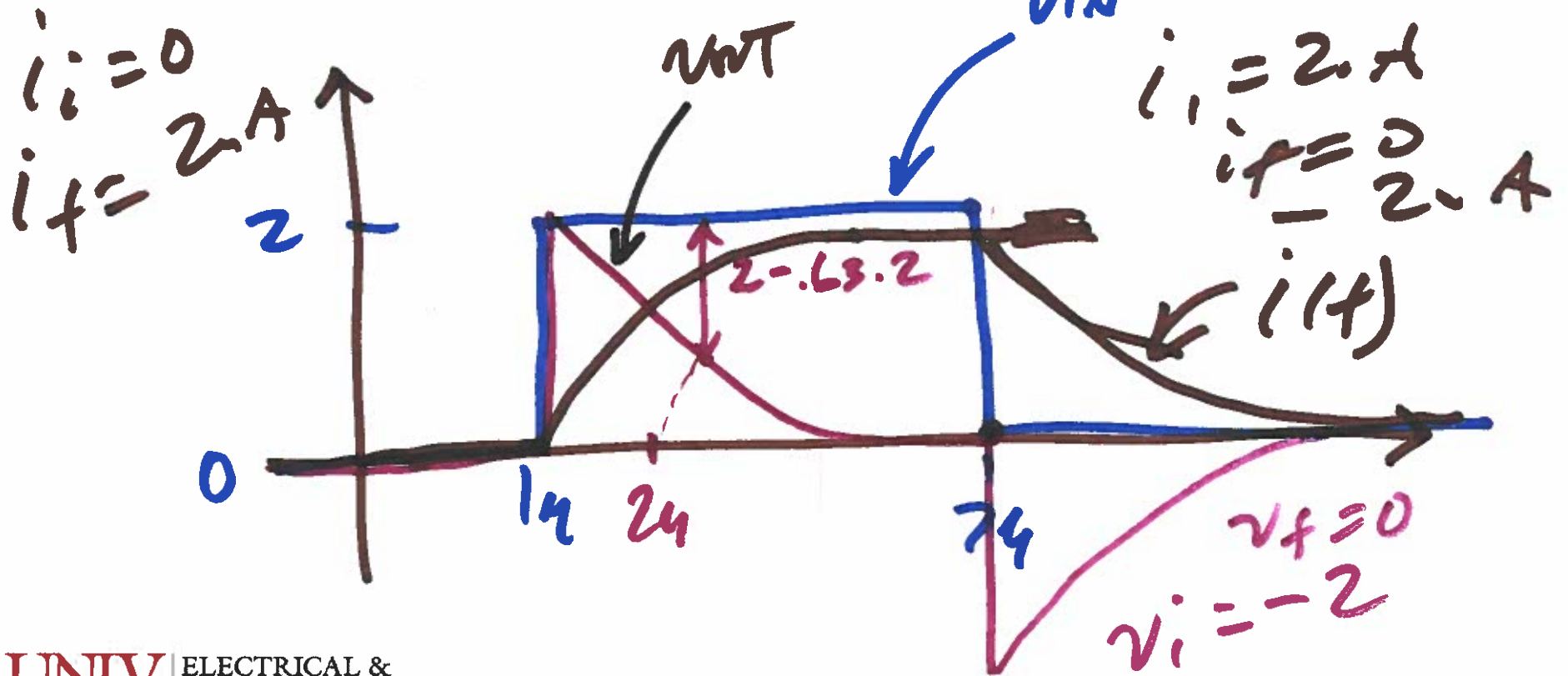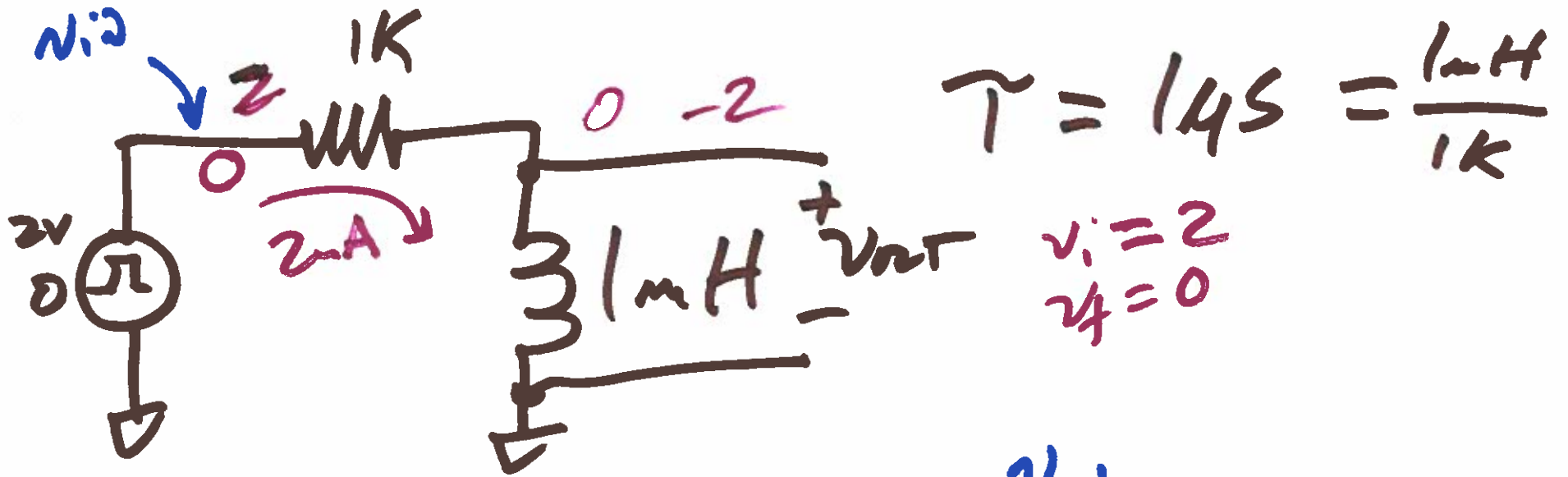


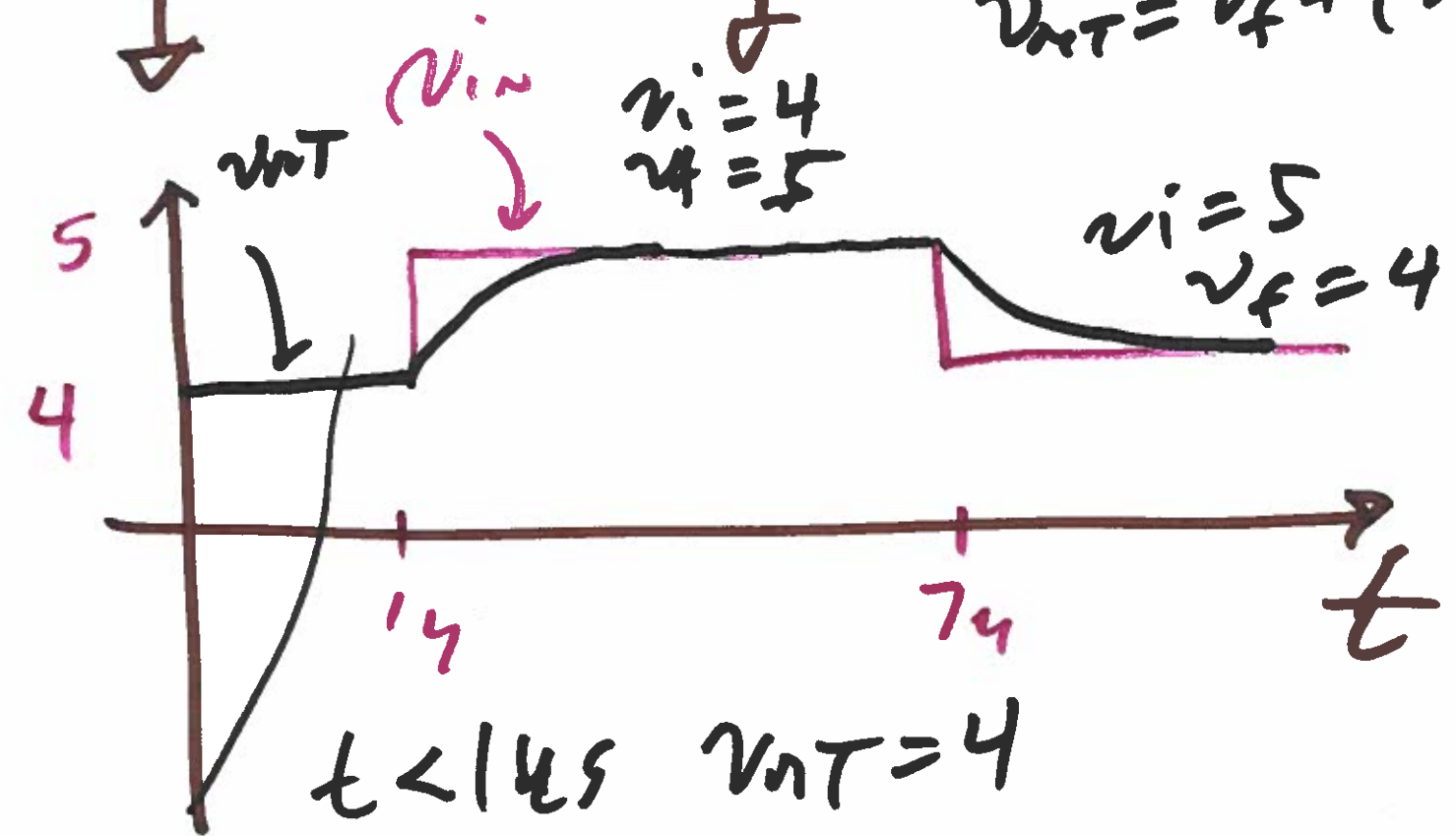2)


$$\tau = 1 \mu s$$



$$v_{out} = v_f + (v_i - v_f)e^{-t/\tau}$$



3)

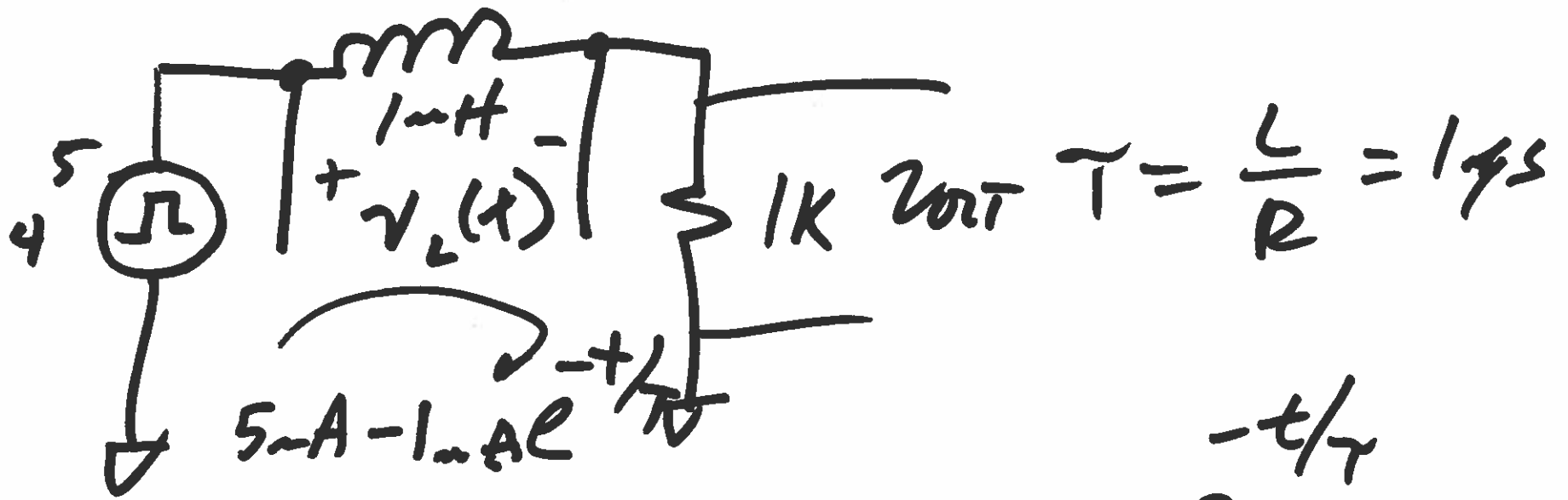

$$V_i = 1$$

$$V_f = 0$$

$$i_i = 4mA$$

$$i_f = 5mA$$

$$v_L(t) = 1 \cdot e^{-t/T}$$


$$i(t) = 5mA + (4mA - 5mA) e^{-t/T}$$

$$= 5mA - 1mA e^{-t/T}$$


$$v_{AT}(t) = 5 - e^{-t/T}$$

$$v_L = 5 - (5 - e^{-t/T})$$


4)

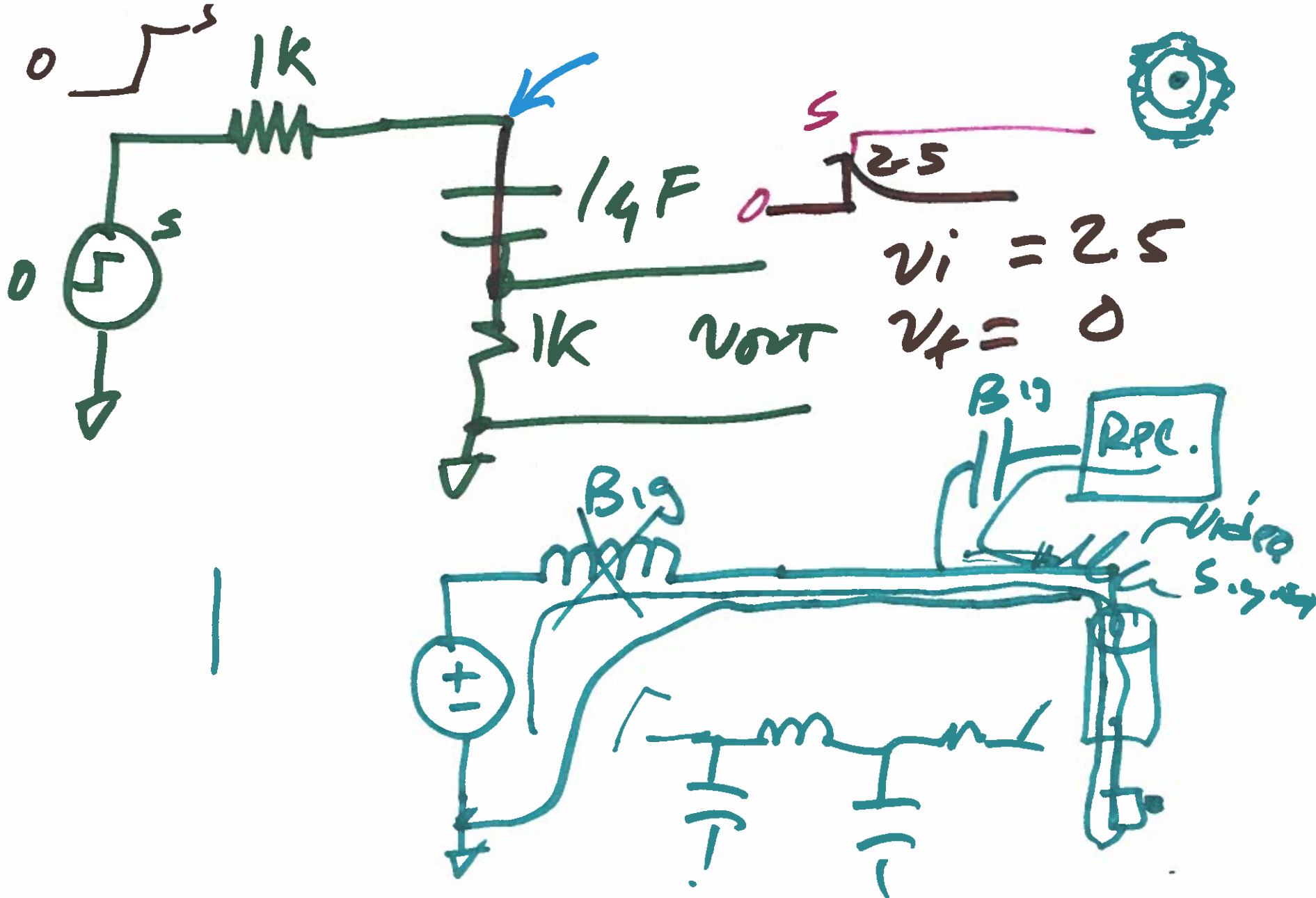

5)


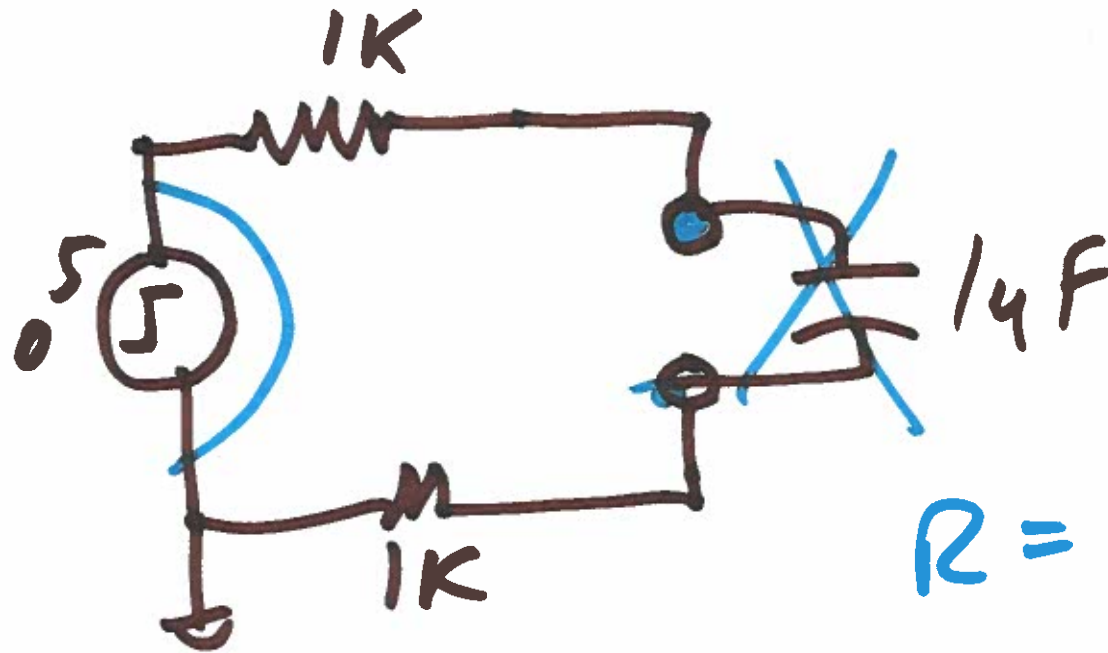


$R = 2k$

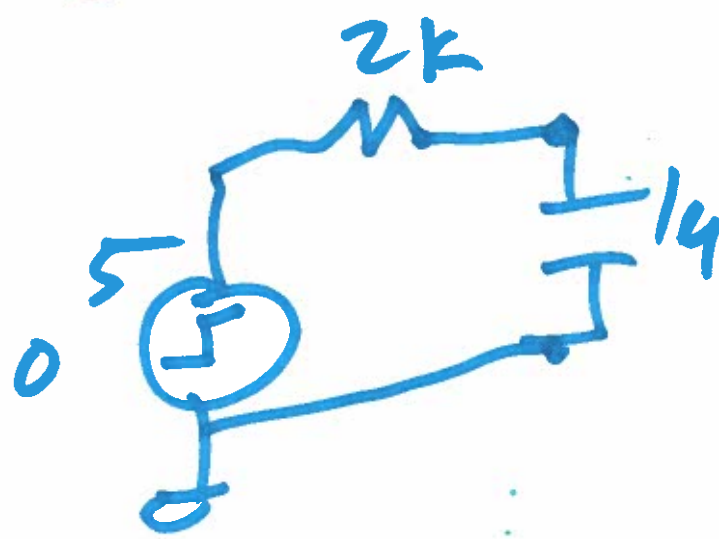


$\tau = 2k \cdot 14F$

b)

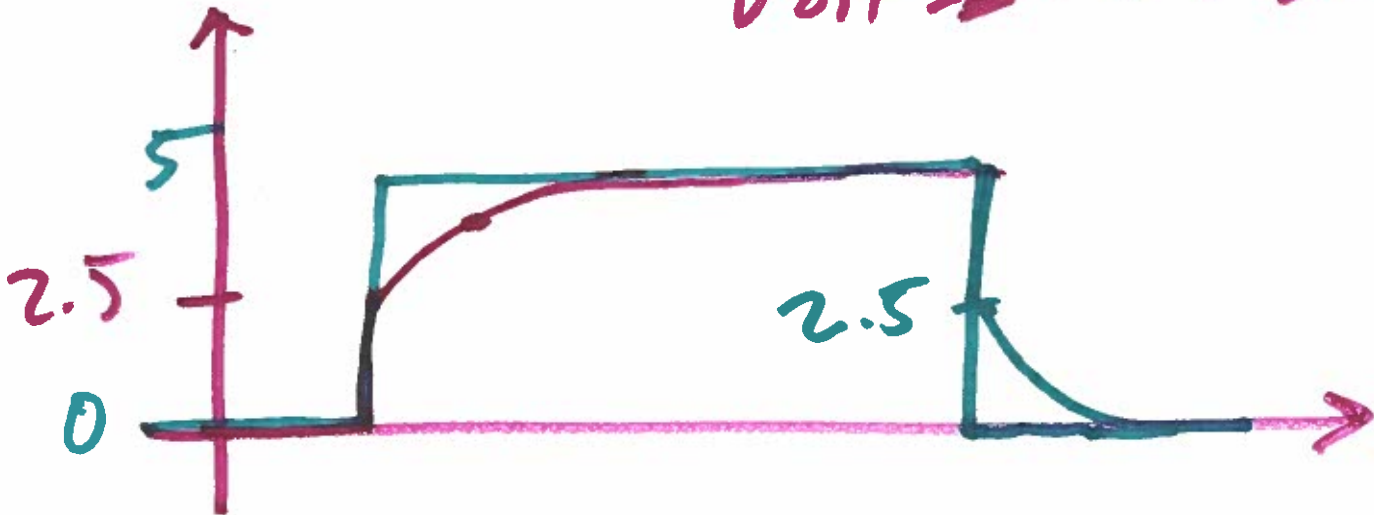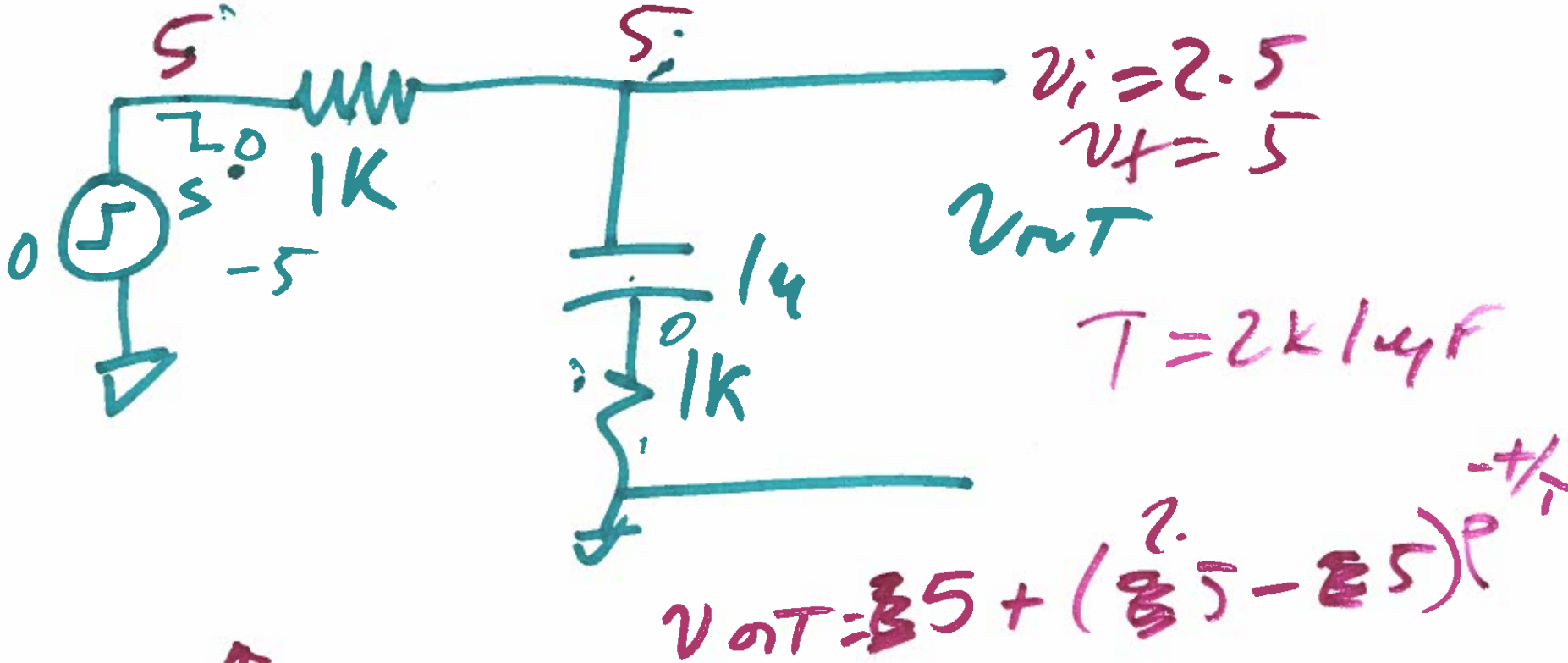

# AC COUPLING

AC → OUTPUT  
 $\tau = 1\mu s$

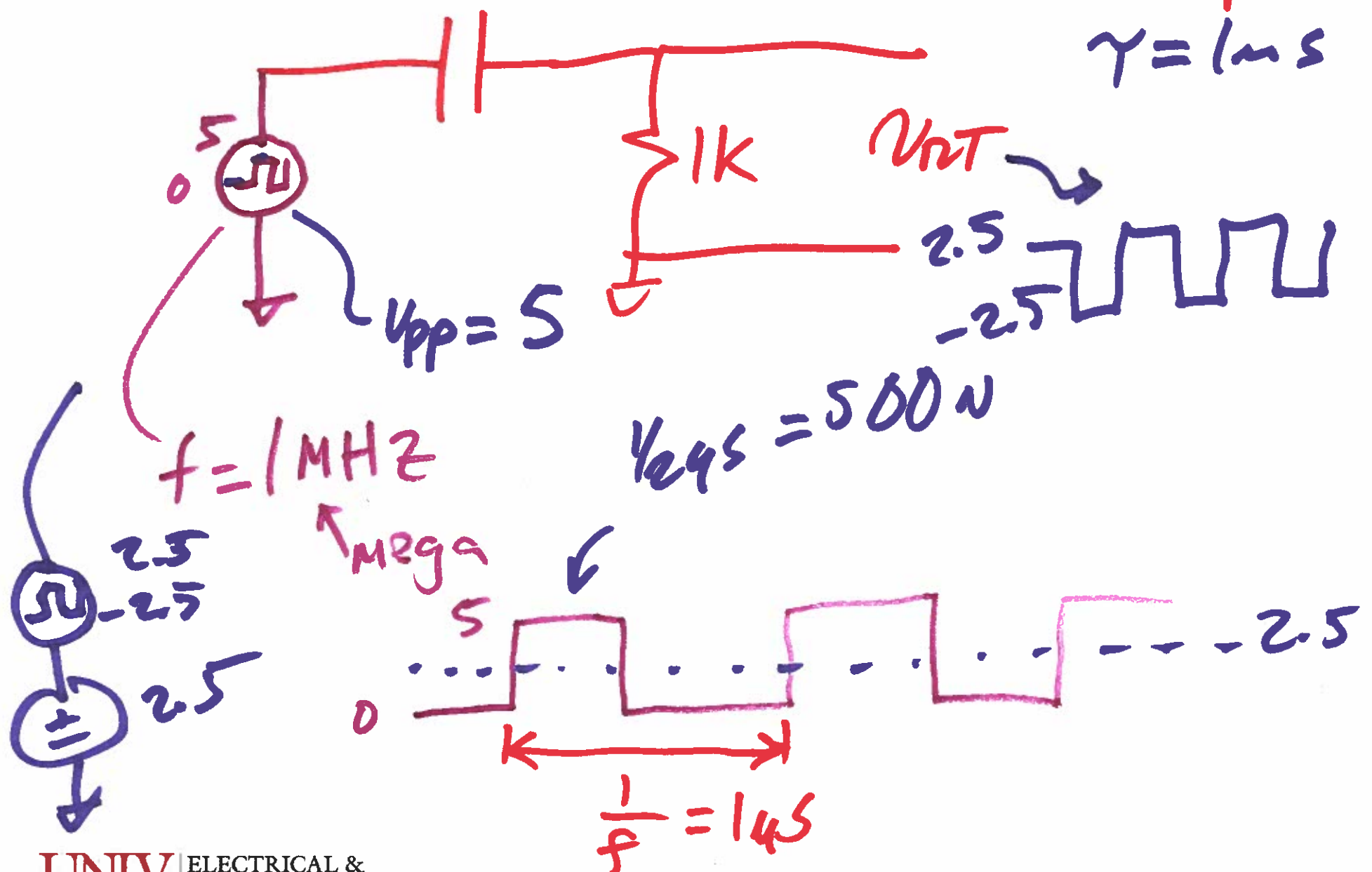

9)