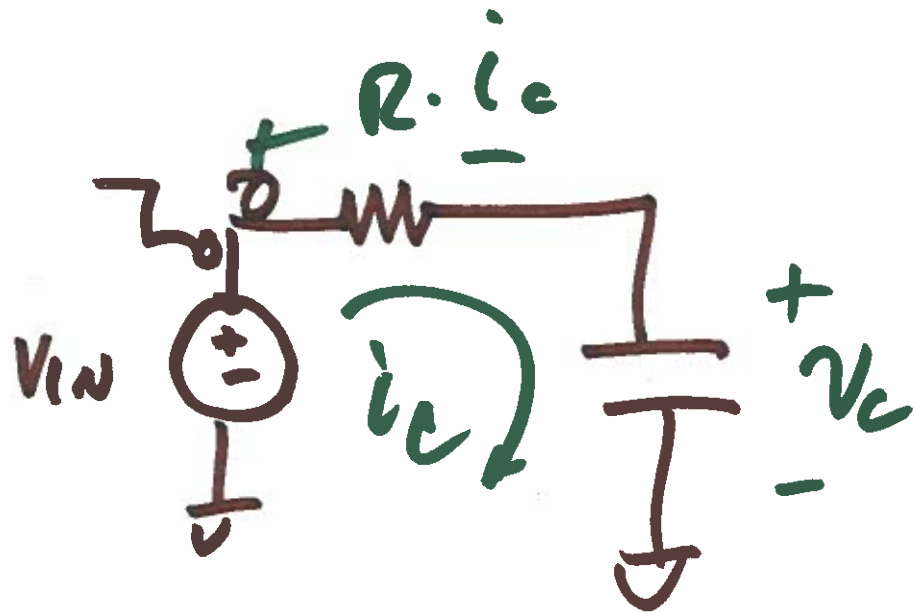


# EE 220 circuits 1

NOV. 4, 2019


## Lecture 19




$$V_{in} = i_c \cdot R + V_c$$

$$V_{in} = RC \cdot \frac{dV_c}{dt} + V_c$$

$$i_c = C \frac{dV_c}{dt}$$

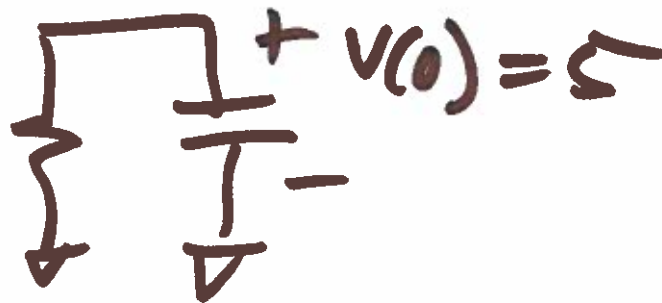

1)

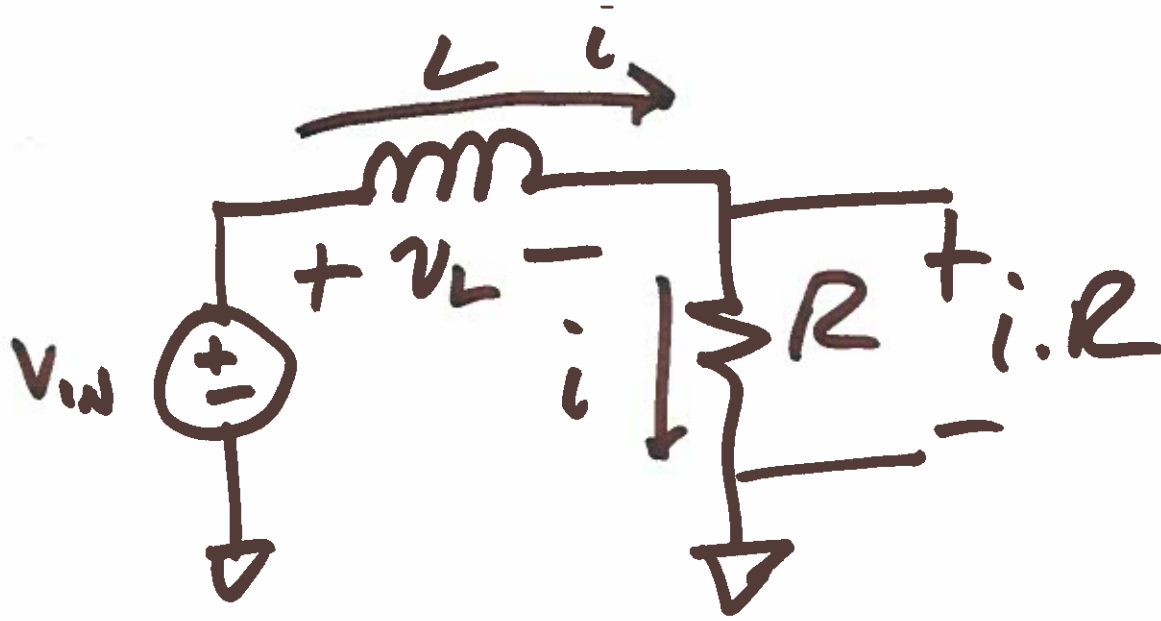


$$V_L = L \cdot \frac{di}{dt}$$

$$V_{in} = V_L + i \cdot R$$

$$V_{in} = L \cdot \frac{di}{dt} + i \cdot R$$
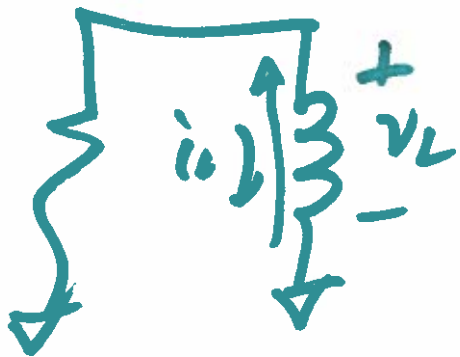
$$\frac{V_{in}}{R} = \frac{L}{R} \frac{di}{dt} + i$$




2)

Resistors


dissipating

NORTON'S

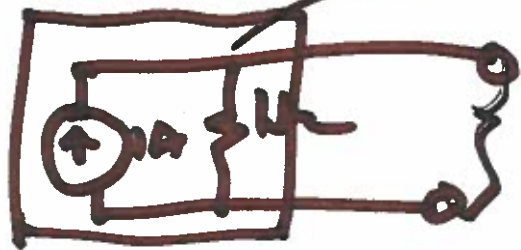

$$P = I^2 \cdot R = VI$$

$$= \frac{V^2}{R}$$

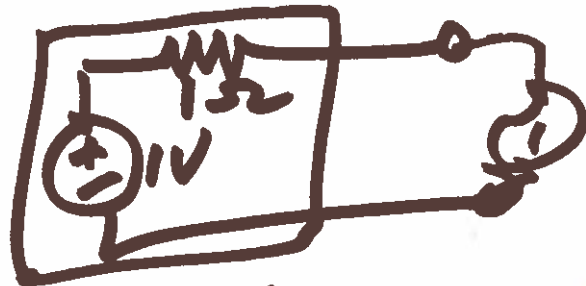

Thevenin

Inductors &  
Capacitors  
Store  
energy

$$E = \int_{t_1}^{t_2} v_L(t) \cdot i(t) dt$$

$$v_L(t) = L \cdot \frac{di(t)}{dt}$$

3)

$$dt = L \cdot \frac{di(t)}{v_L(t)}$$

$$E = \int_{i(t_1)}^{i(t_2)} v_L(t) \cdot i(t) \cdot L \cdot \frac{di(t)}{v_L(t)}$$

$$= L \int_0^I i \cdot di = \frac{1}{2} L \cdot I \Big|_0^I$$

$$E = \frac{1}{2} L I^2$$

$I = \text{Change in current}$

$$\downarrow \frac{1}{T} \int v_c(t) dt$$


$$C \cancel{V} = Q$$

$$E = \int_0^Q v_c(t) \cdot dq$$

$$= \int_0^Q \frac{q(t)}{C} \cdot dq = \frac{1}{2} \frac{Q^2}{C}$$

$$E = \frac{1}{2} C V^2$$

s)

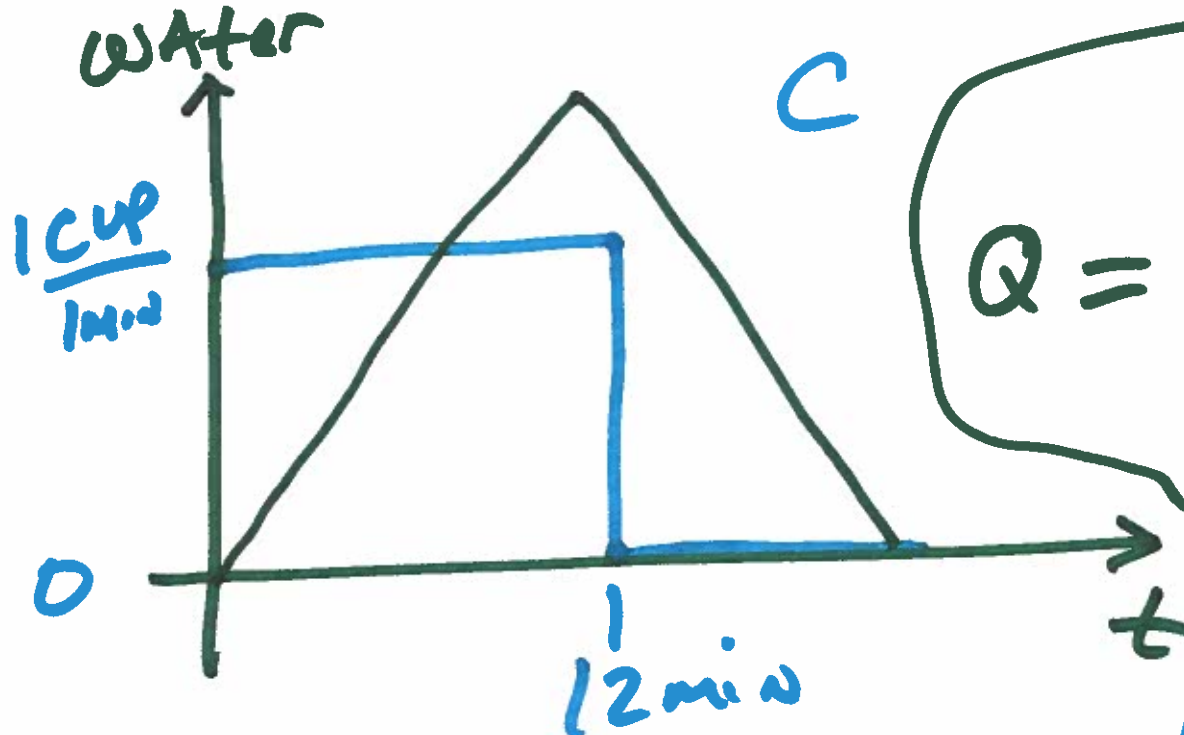


$$Q = \int_{t_1}^{t_2} i(t) \cdot dt$$


AMOUNT OF WATER =  $\int_0^{12 \text{ min}} \frac{1 \text{ cup}}{\text{min}} \cdot dt$

$$= \frac{1 \text{ cup}}{\text{min}} \cdot 12 \text{ min}$$

$$= 12 \text{ cups}$$

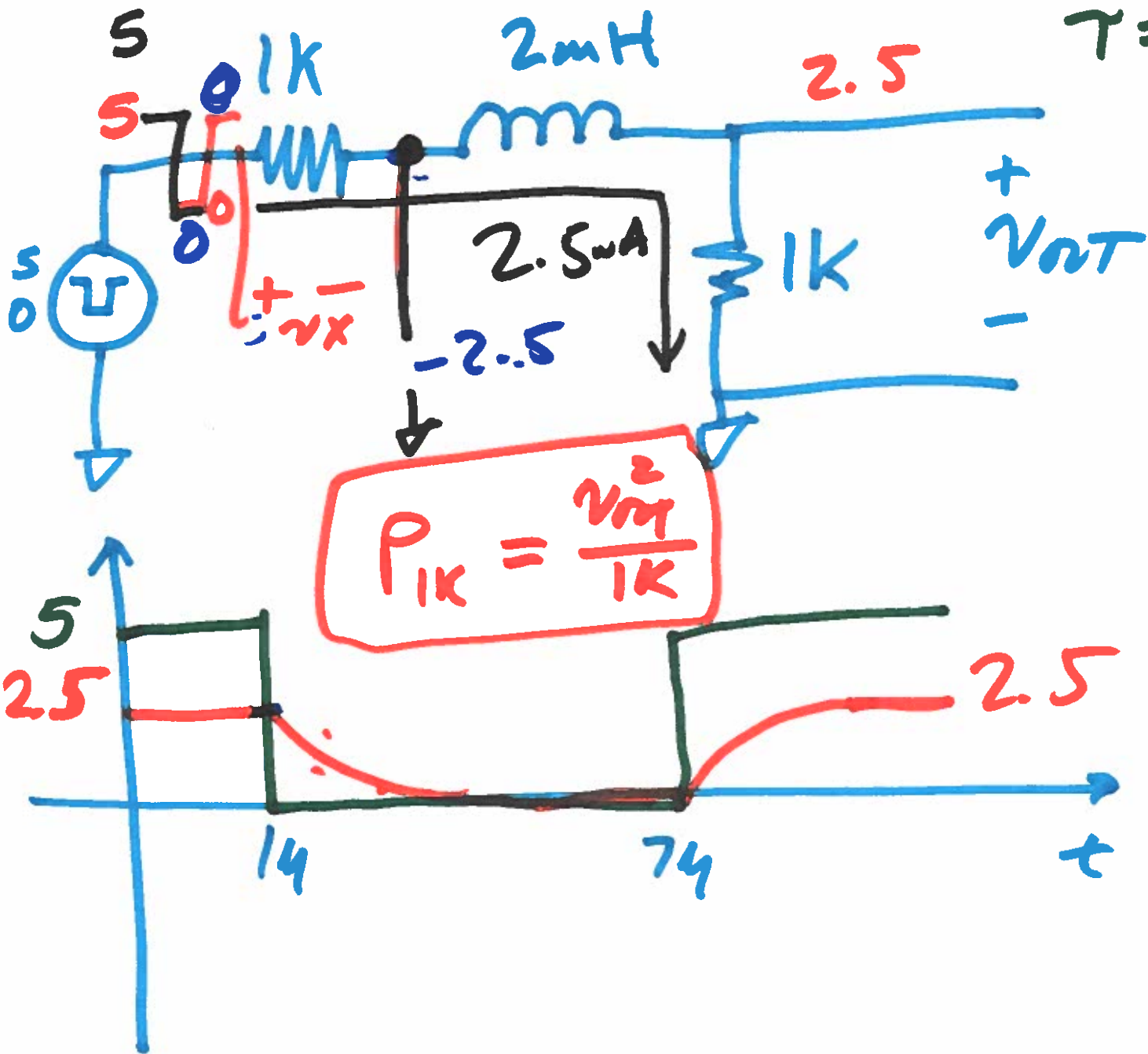


7)

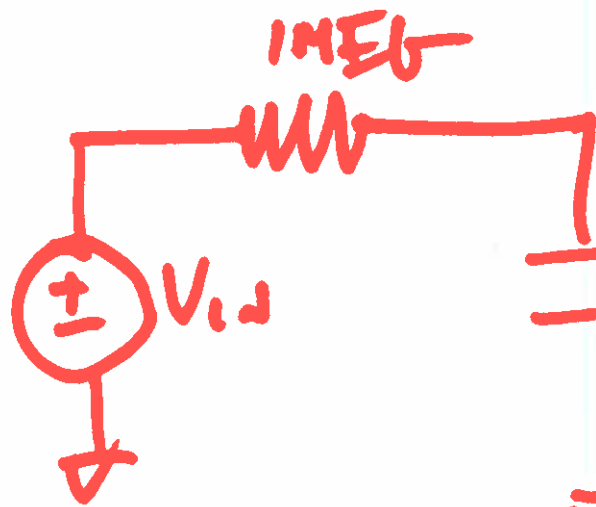

$$T = RC$$

$$= 10^6 \cdot 10 \cdot 10^{-12}$$


$$= 10 \text{ ns}$$

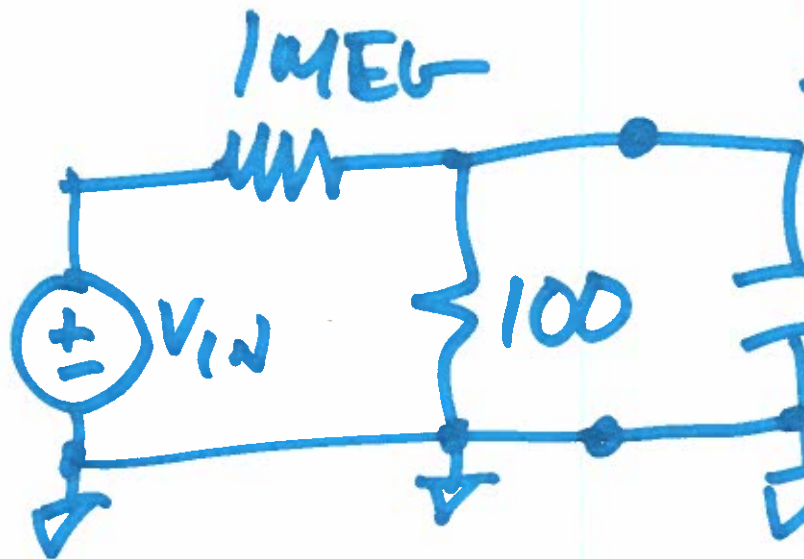



$$T = 100 \cdot 10 \cdot 10^{-12}$$

$$= \underline{\underline{1 \text{ ns}}}$$

$$T = (1 \text{MEG} + 100) C$$

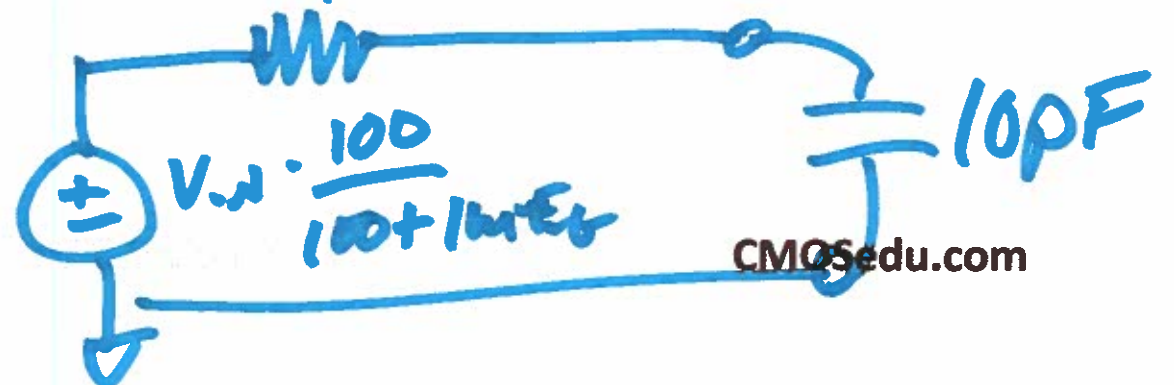



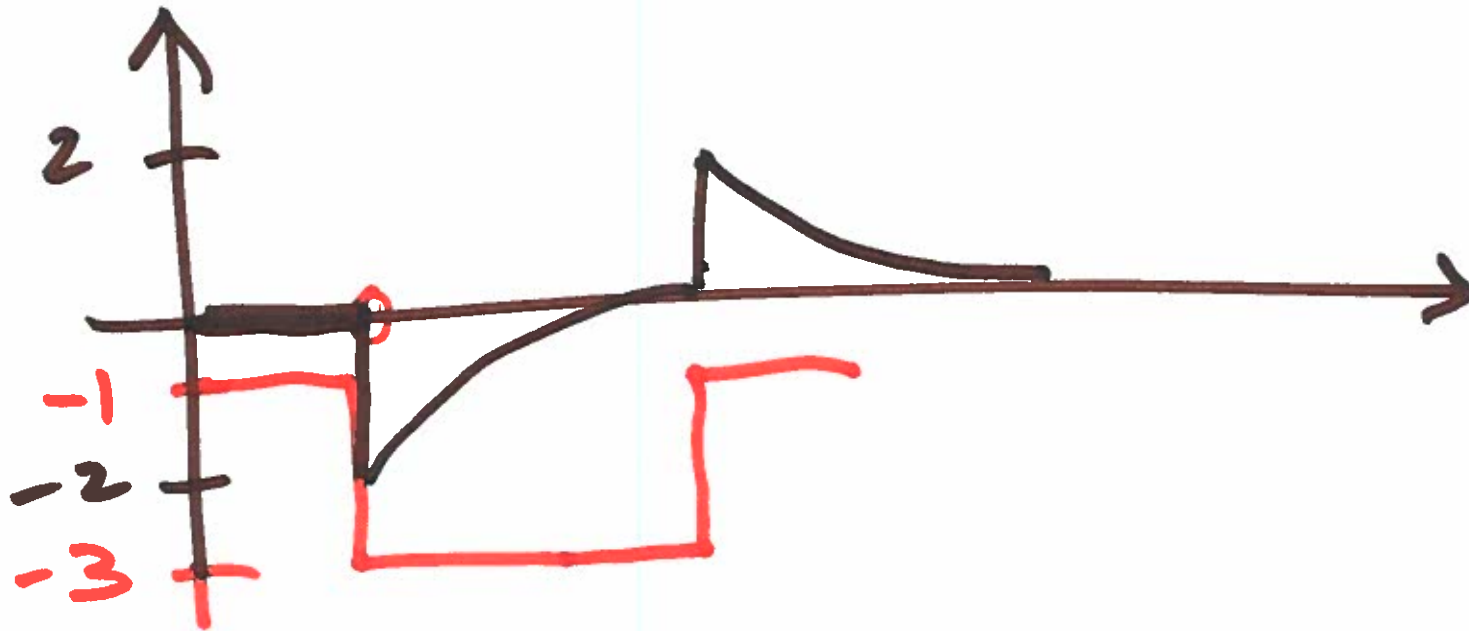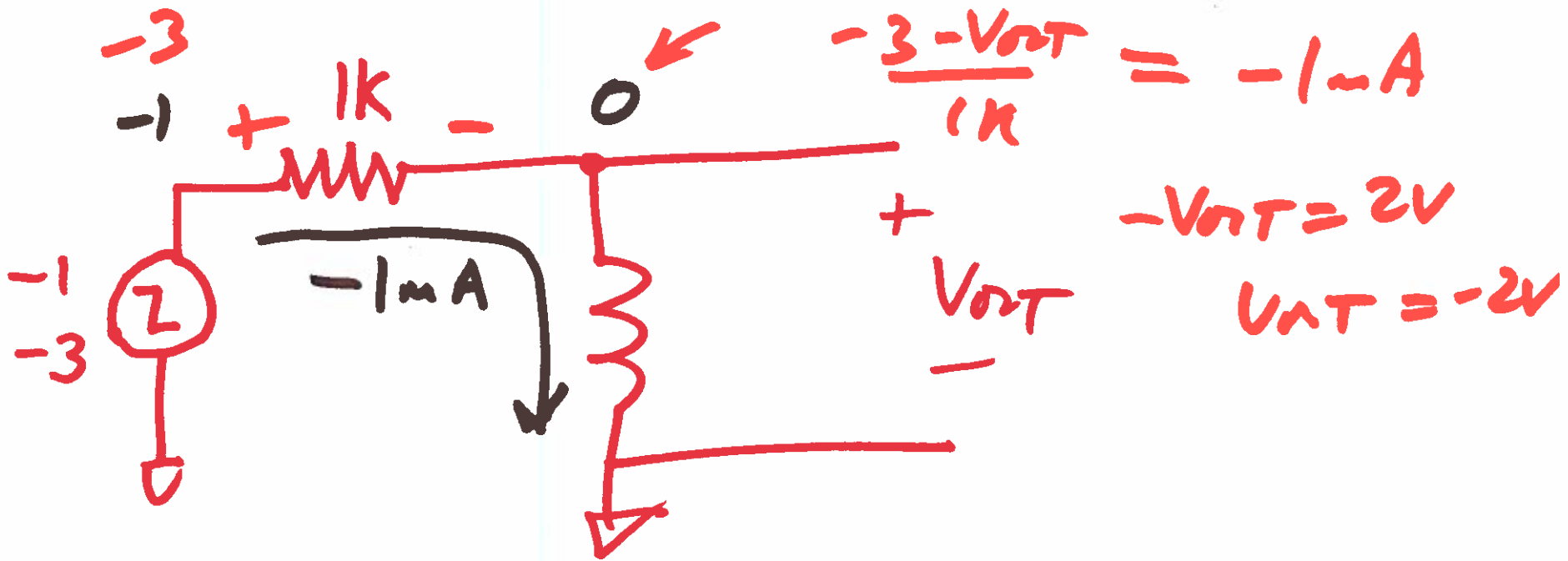

a)