
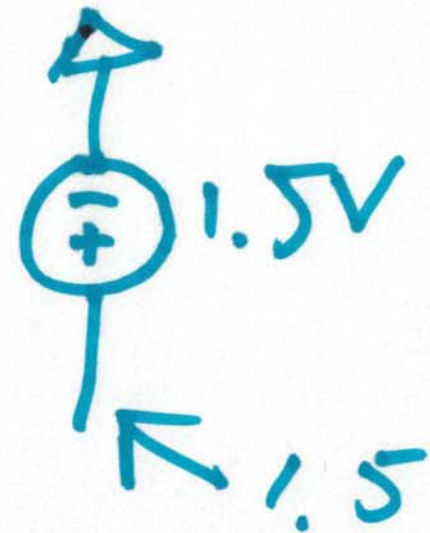


EE 220



Circuits I


August 26, 2019

Lecture 1

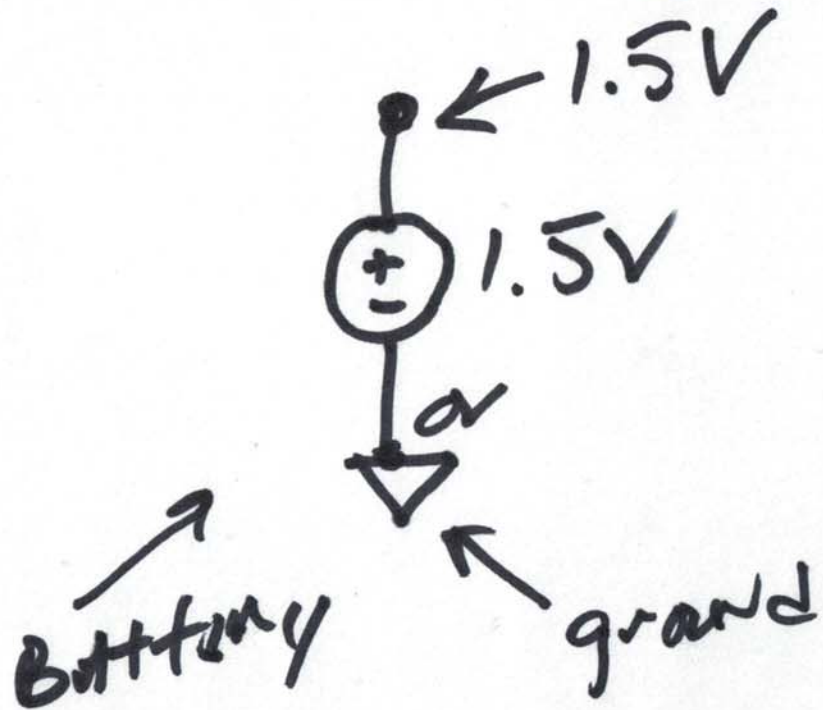


1)

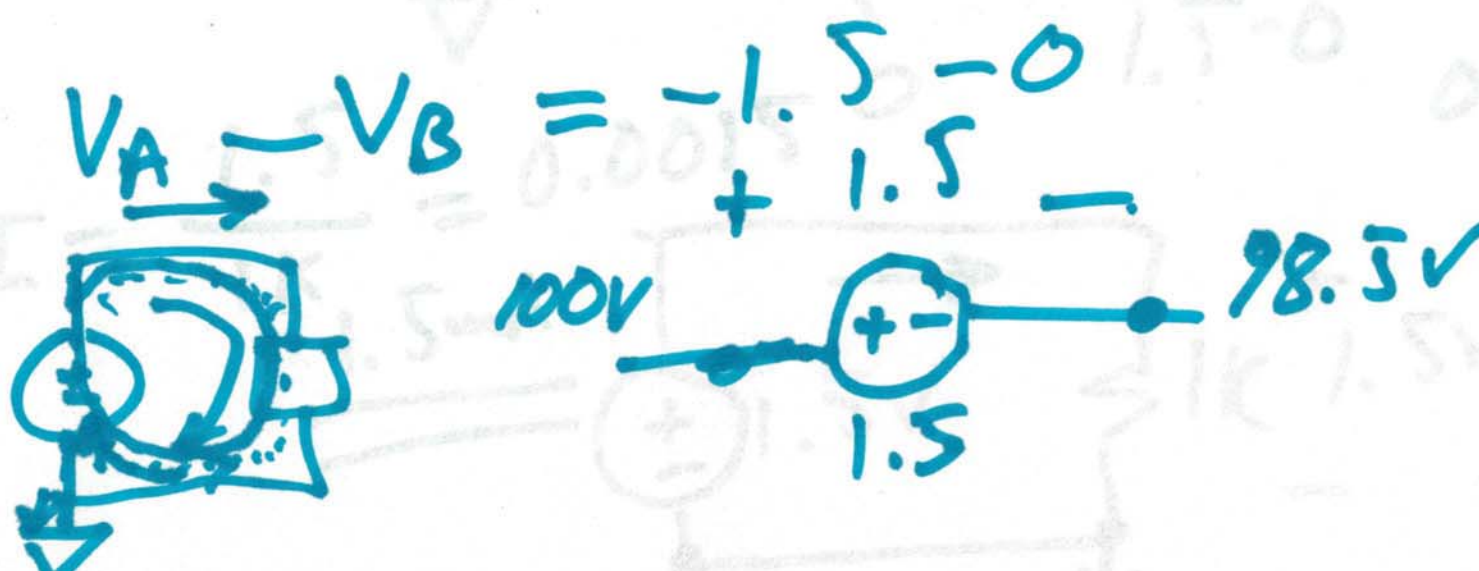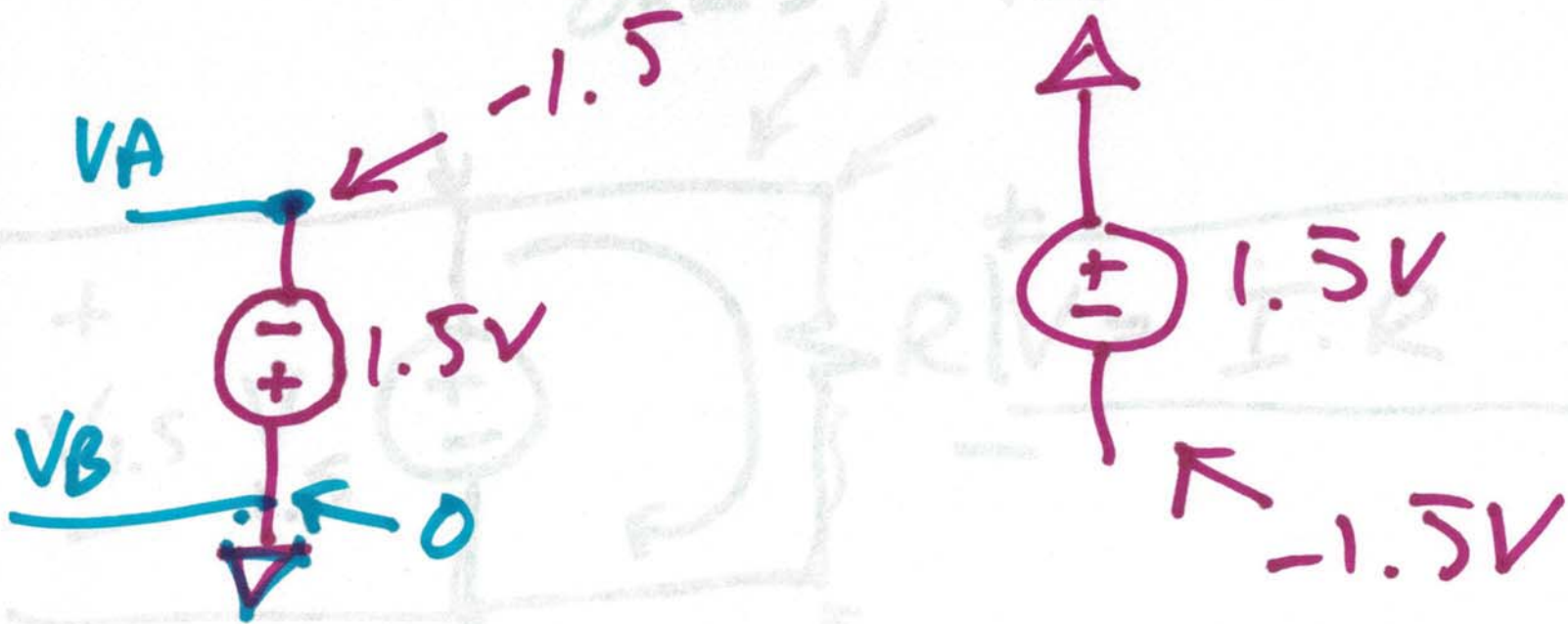

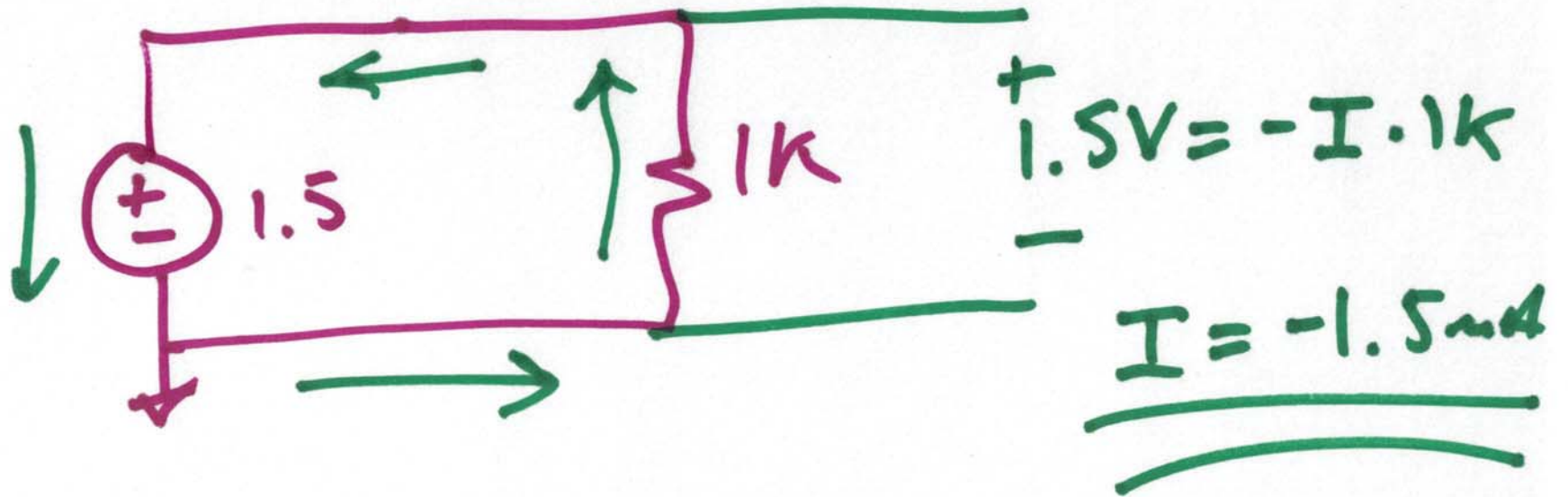

$$I \downarrow \begin{matrix} + \\ \downarrow \\ - \end{matrix} V = I \cdot R$$
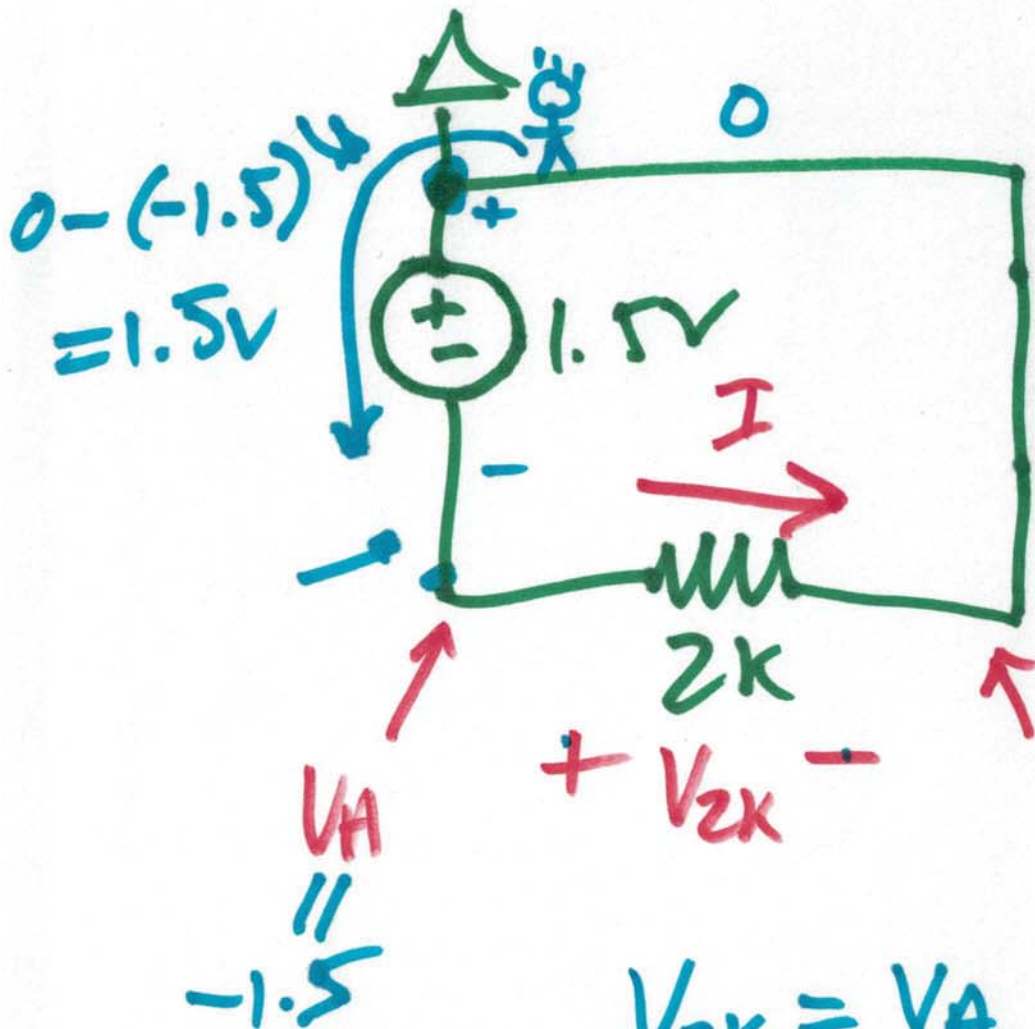
$$I \uparrow \begin{matrix} + \\ \downarrow \\ - \end{matrix} V = (-I) \cdot R$$




$I \downarrow \uparrow \begin{matrix} + \\ - \end{matrix} V = I \cdot R$   
 $\uparrow \downarrow \begin{matrix} + \\ - \end{matrix} V = (-I) \cdot R$   
 Ohm's

$V_{2k} = V_A - V_B = V_A = -1.5V$

$I = \frac{V_{2k}}{R} = \frac{-1.5V}{2k} = -750 \mu A = -\frac{3}{4} \mu A$

5)

# Voltage divider

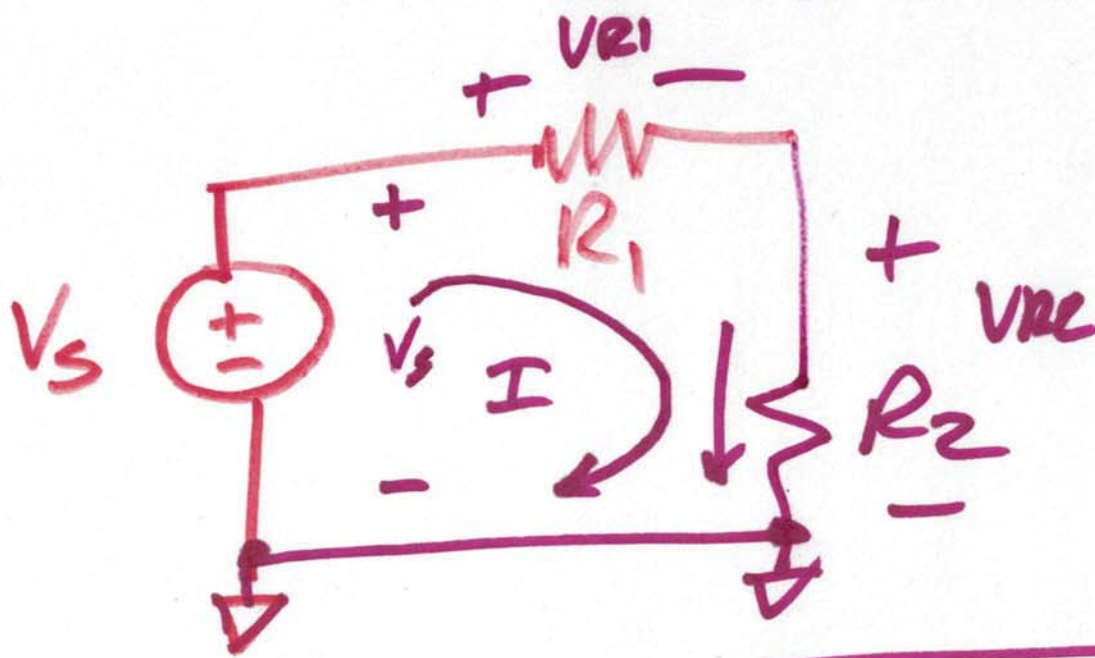

$$I = \frac{V_s}{R_1 + R_2}$$

$$V_{R1} = I \cdot R_1$$


$$V_{R2} = I \cdot R_2$$

$$I \downarrow \begin{matrix} + \\ | \\ - \end{matrix} V = I \cdot R$$

$$I \downarrow \begin{matrix} - \\ | \\ + \end{matrix} V = (-I) \cdot R$$

$$V_{R2} = V_s \cdot \frac{R_2}{R_1 + R_2}$$
$$V_{R1} = V_s \cdot \frac{R_1}{R_1 + R_2}$$

b)

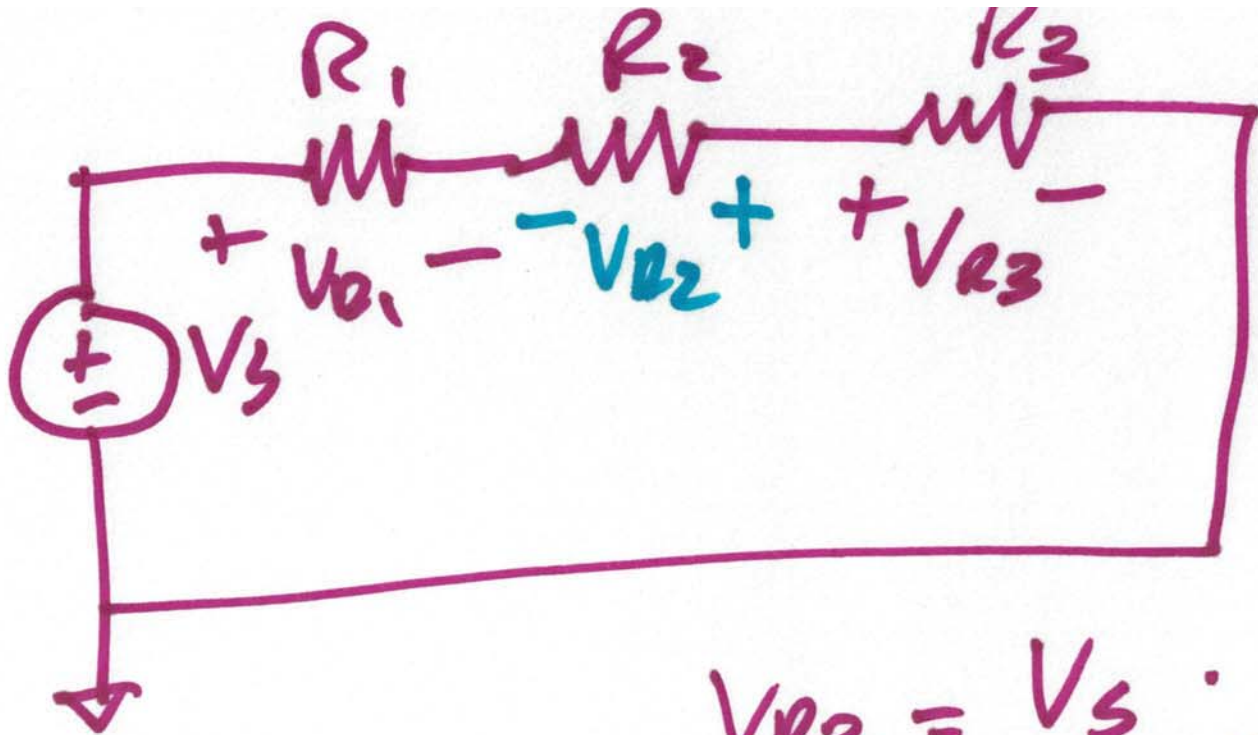


$$V_{R3} = V_s \cdot \frac{R_3}{R_1 + R_2 + R_3}$$

$$V_{R2} = \frac{-V_s \cdot R_2}{R_1 + R_2 + R_3}$$

$$V_{R1} = V_s \cdot \frac{R_1}{R_1 + R_2 + R_3}$$


1)

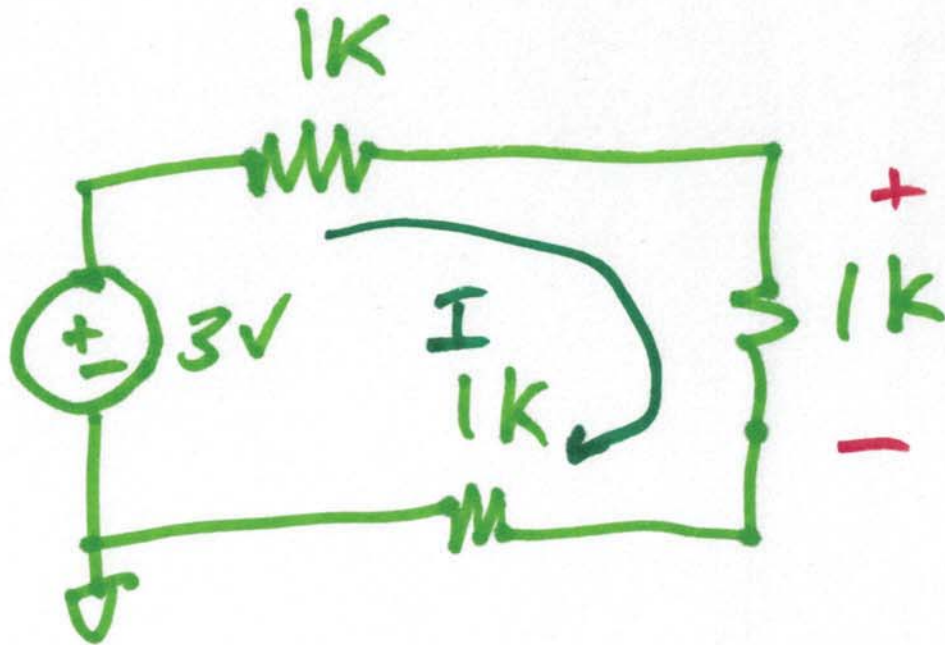

$$I = \frac{3V}{3k} = 1\mu A$$

$$= 3 \cdot \frac{1k}{1k + 1k + 1k} = \frac{3k}{3k} = \underline{\underline{1V}}$$


8)

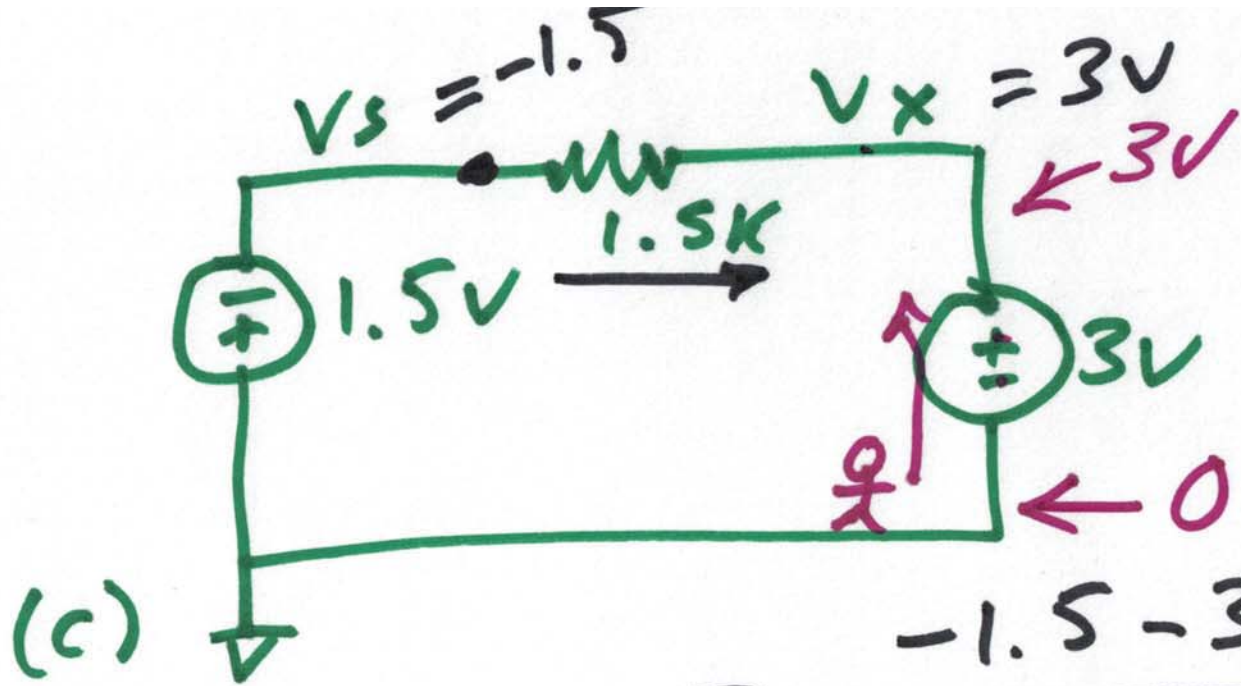

$$V = I \cdot R \quad I = \frac{-1.5 - 3}{1.5k} = \frac{-4.5}{1.5k} = -3\mu A$$

9)



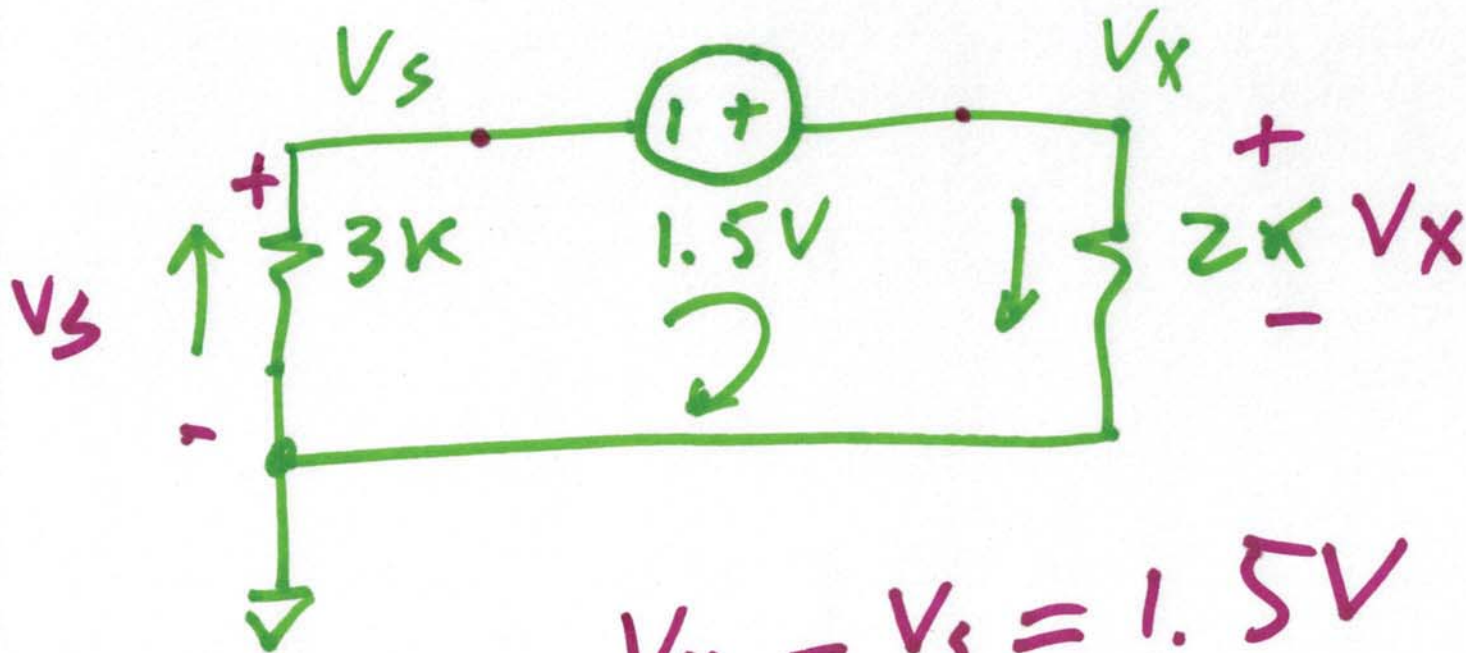

$$V_x - V_s = 1.5V$$

$$V_s = -I \cdot 3k$$

$$V_x = I \cdot 2k$$

$$I \cdot 2k + I \cdot 3k = 1.5V$$

$$I = \frac{1.5}{5k} = 0.3mA = 300\mu A$$