
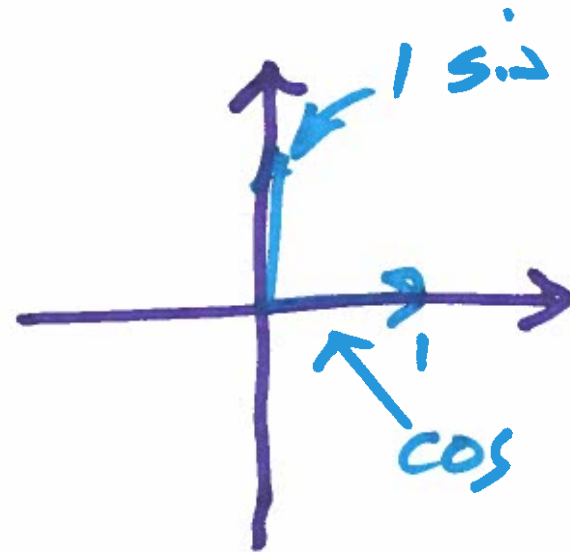


EE 220 circuits 1

Nov. 18, 2019


Lecture 22

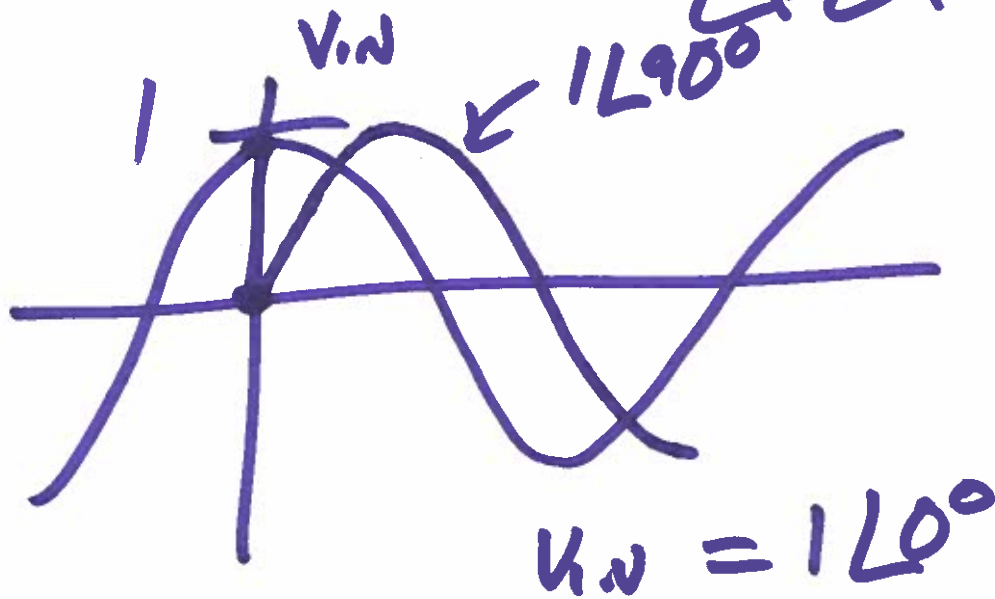

11

$$i_c(t) = C \cdot \frac{d v_c(t)}{dt} = C \cdot \underline{2\pi f} \cdot V_p \sin(\omega t)$$

$$\sin(2\pi f t)$$

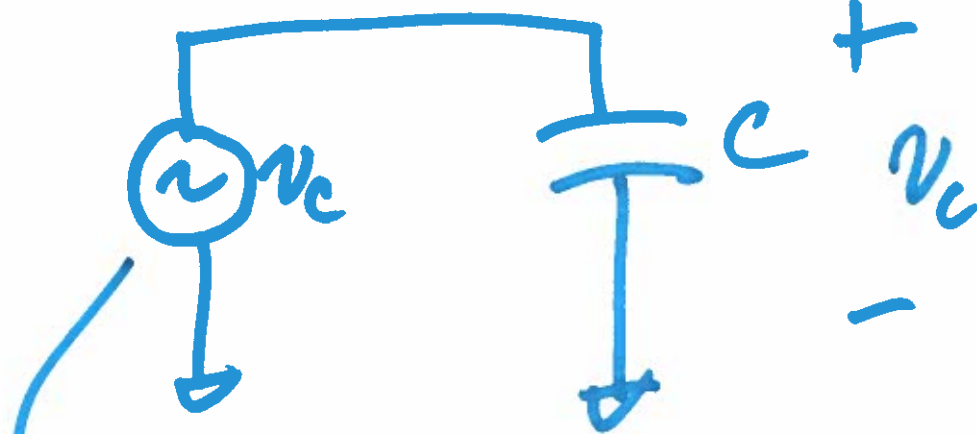

$$V_p \cdot \cos(2\pi f \cdot t)$$

$$V_p \angle 0^\circ$$

$$i_c(t) = 2\pi f \cdot C \cdot -V_p \sin(\omega t)$$

$$\omega = 2\pi f$$

← omega

$$i_c = \omega C \cdot -V_p \sin(\omega t)$$

2)

$$\frac{i_c}{\omega C} = -V_p \sin(2\pi f \cdot t)$$

$$= -V_p \overset{\cos}{\cancel{\sin}}(2\pi f \cdot t + 90^\circ)$$

$$\frac{i_c}{\omega C} = -V_p \cos(2\pi f \cdot t + 90^\circ)$$

$$\frac{1}{j} \cdot \frac{j}{j} = -j = V_p \angle -90^\circ$$


$$V_p \angle 0^\circ = \frac{i_c}{\omega C} \angle -90^\circ = i_c \cdot \frac{1}{j\omega C}$$

impedance of a CAP


$$Z_C = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90$$

impedance of an inductor

$$Z_L = j\omega L$$

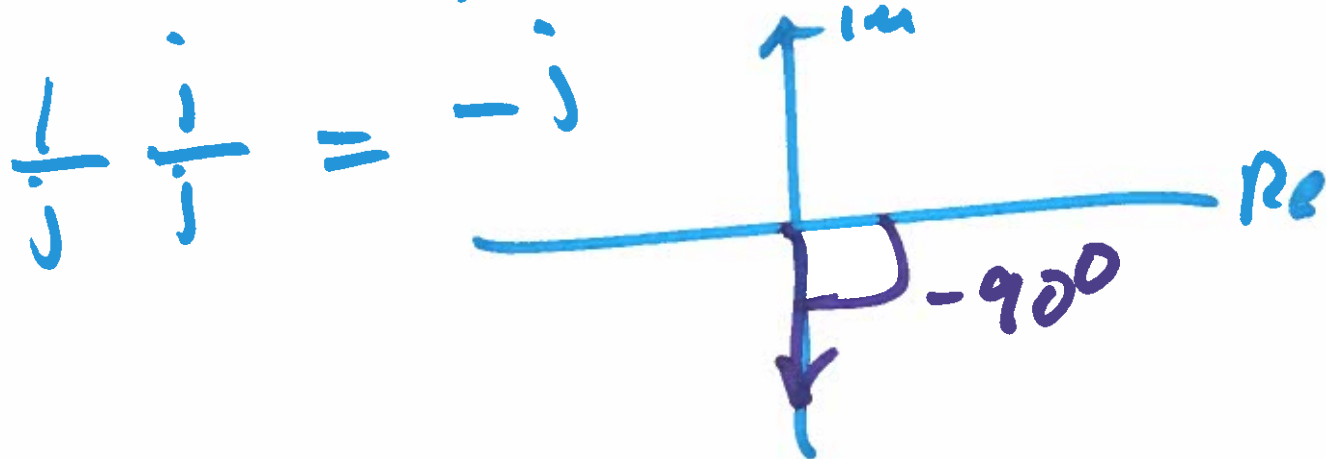

$$i_c = C \cdot \frac{dv_c}{dt}$$

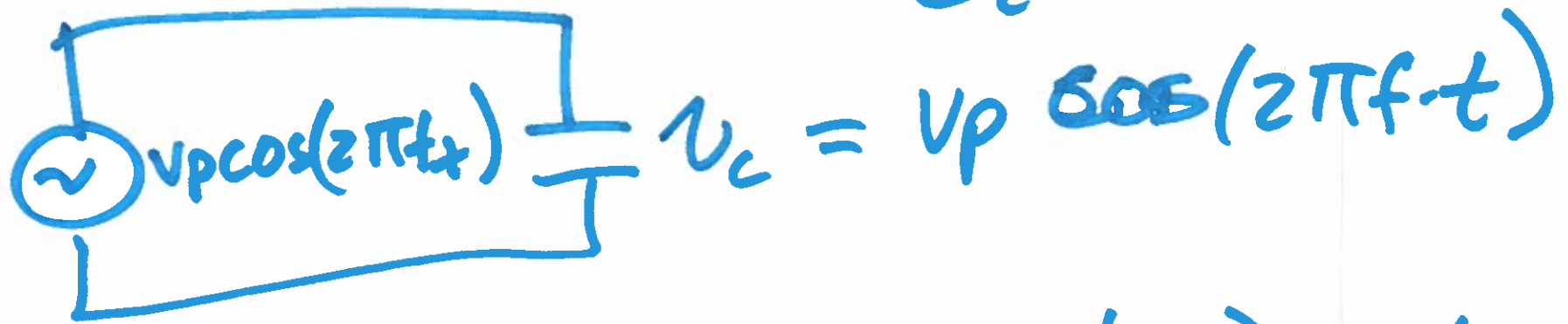

$$i_c = C \cdot 2\pi f \cdot (-V_p) \sin(2\pi ft)$$

$$= C \cdot \omega \cdot -V_p \cdot \cos(2\pi ft + 90)$$

odd
 $-f(x) = f(-x)$


even
 $f(x) = f(-x)$

$$\text{Phase shift } \begin{matrix} \uparrow \\ \ominus \\ \downarrow \end{matrix} \quad i_c = C \cdot \omega \cdot V_p \angle 90 \cdot 1 \angle 180$$

$$\frac{1}{-j} = \frac{1}{j} A \angle \theta_1 \cdot B \angle \theta_2 = AB \angle \theta_1 + \theta_2$$

$$V_p \angle 0 = i_c \angle 0 \cdot \frac{1}{j\omega C}$$

5)

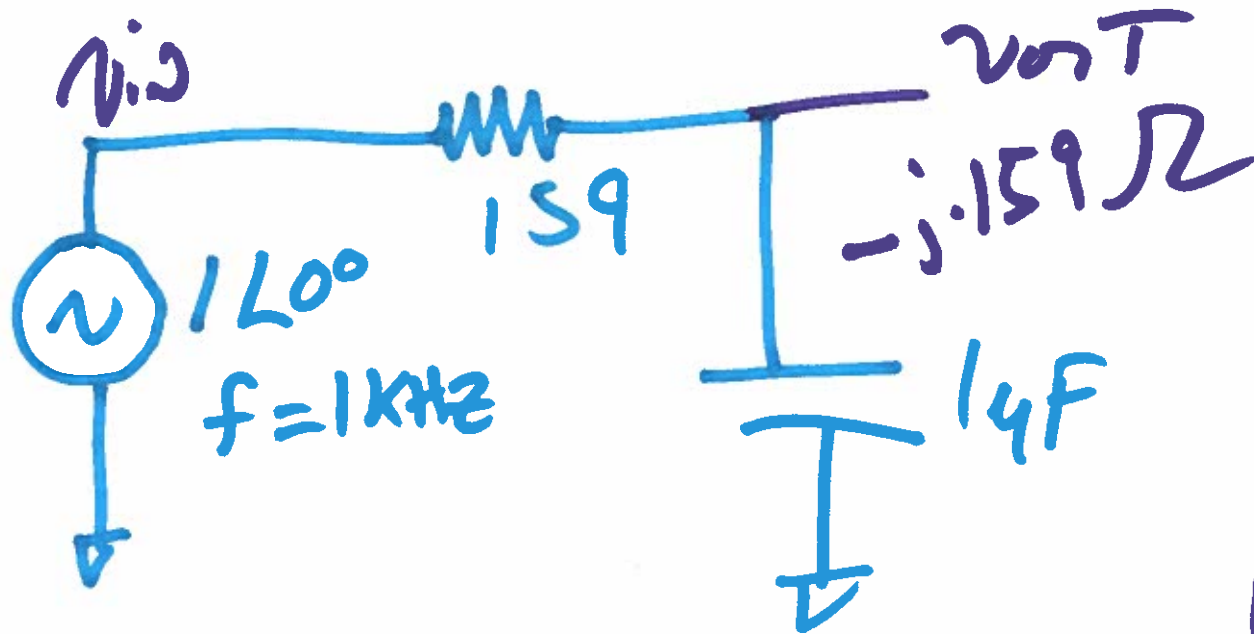

$$Z_C = \frac{1}{j \cdot 2\pi \cdot 10^3 \cdot 10^{-6}} = \frac{1}{j} = -j159$$


Reactance impedance

$$v_{OUT} = v_{in} \cdot \frac{-j159}{-j159 + 159}$$

$$V_{out} = 1 \angle 0^\circ \cdot \frac{0 + j(-159)}{159 + j(-159)}$$

$$\tan^{-1} \frac{-159}{0}$$

$$= -\tan^{-1} \infty = -90^\circ$$

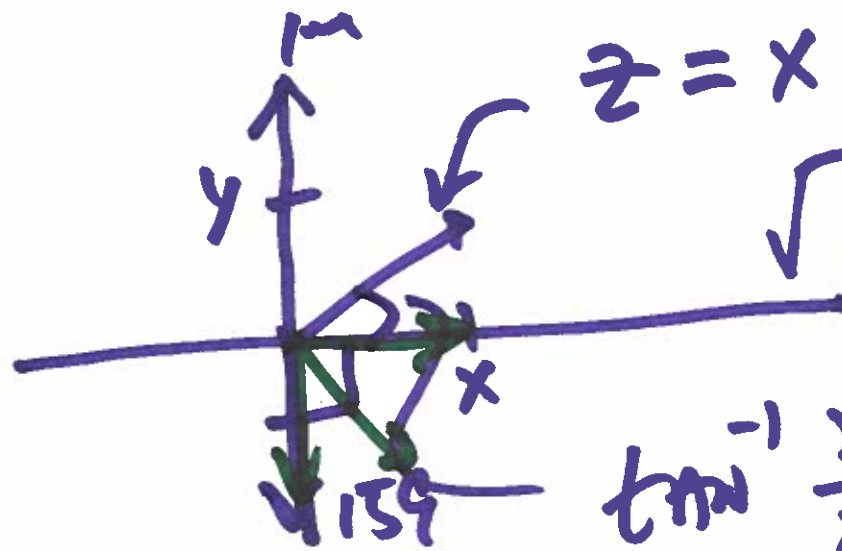

$$z = x + jy$$

$$\sqrt{x^2 + y^2} = M$$

$$\tan^{-1} \frac{y}{x} = \theta$$

$$M \angle \theta$$

$$V_{out} = \frac{1 \angle 0^\circ \cdot 159 \angle -90^\circ}{\sqrt{2} \cdot 159 \angle -45^\circ}$$

$$224.85$$

$$\sqrt{(159)^2 + (159)^2}$$

$$\sqrt{2 \cdot (159)^2}$$

7)

$$\theta = \frac{t_d}{T} \cdot 360$$


$$\frac{A \angle \theta_1 \cdot B \angle \theta_2}{C \angle \theta_3} = \frac{AB}{C} \angle \theta_1 + \theta_2 - \theta_3$$


$$45 = \frac{t_d}{1\text{ms}} \cdot 360 \quad V_{out} = 0.707 \angle -45^\circ$$

$$\frac{1}{8} \cdot 1\text{ms} = t_d$$

$$V_{out} = 0.707 \cos(2\pi \cdot 10^3 \cdot t - 45^\circ)$$

$$t_d = 125 \mu\text{s}$$

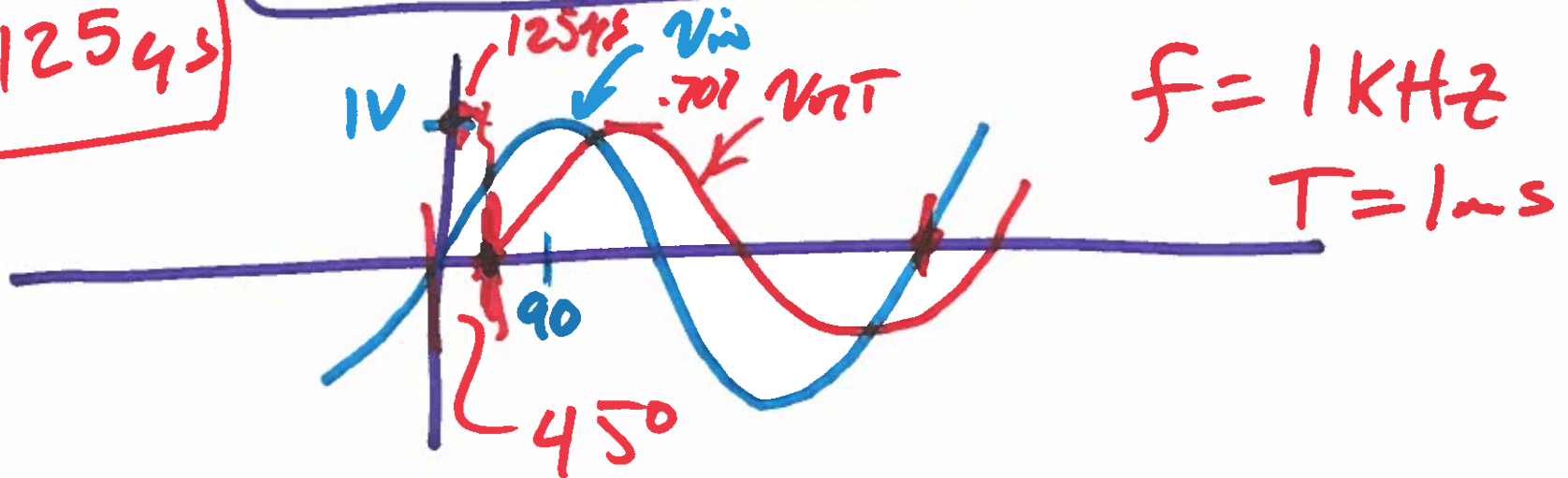

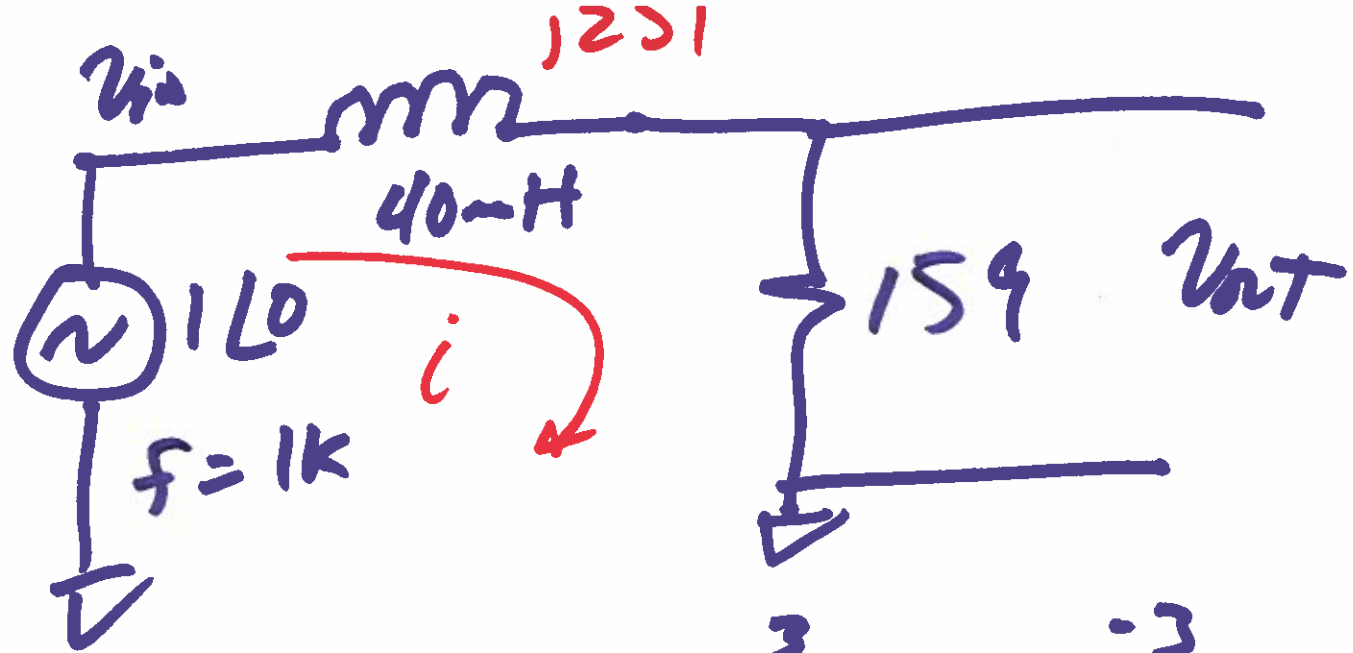

$$Z_L = j\omega L = j \cdot 2\pi \cdot 10^3 \cdot 40 \cdot 10^{-3}$$

$$= j \cdot 251$$

$$i = \frac{120}{159 + j \cdot 251} = \frac{120}{\sqrt{(159)^2 + (251)^2}} \angle \tan^{-1} \frac{251}{159}$$

9)


$$V_{nT} = 1\angle 0 \cdot \frac{159 + j0}{159 + j251} = 159 \cdot \angle$$

$$= \frac{1\angle 0 \cdot 159 \angle 0}{297 \angle 57.6^\circ} = .535 \angle -57.6^\circ$$

$$\sqrt{(159)^2 + (251)^2}$$

$$\tan^{-1} \frac{251}{159} =$$
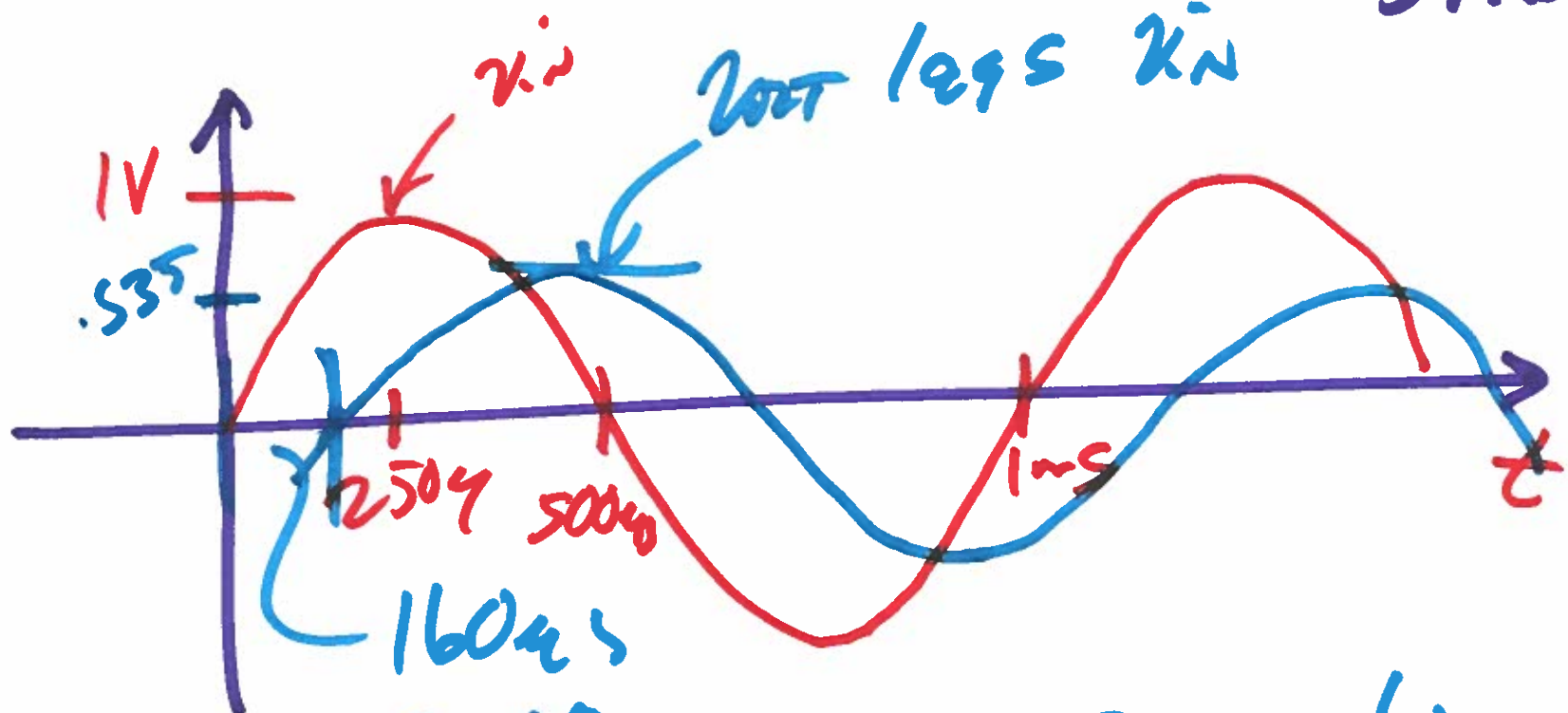
$$V_{out}(t) = 535 \text{ mV} \cdot \sin(2\pi \cdot 10^3 \cdot t - 57.6^\circ)$$



$$= 57.6^\circ \theta = 57.6 = 360 \cdot \frac{t_d}{1 \text{ ms}}$$

$$t_d = 160 \text{ ns}$$