




$$V_{Rms} = \sqrt{\frac{V_P^2}{2T} \int_0^T (1 - \cos 4\pi f \cdot t) dt}$$

$-j = \frac{1}{j} \cdot j$   
 $\rightarrow -j$

$$\sqrt{4} \cdot \sqrt{1} = \sqrt{\frac{V_P^2}{2T} \int_0^T dt - \int_0^T \cos 4\pi f t dt}$$

$j \cdot 1 = -j$   
 $\frac{1}{j} = -j$

$$V_{Rms} = \frac{V_P}{\sqrt{2}}$$



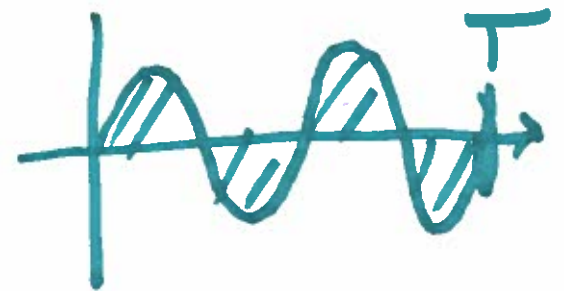


2)


120V Rms

$$V_{Rms} = \frac{V_p}{\sqrt{2}}$$
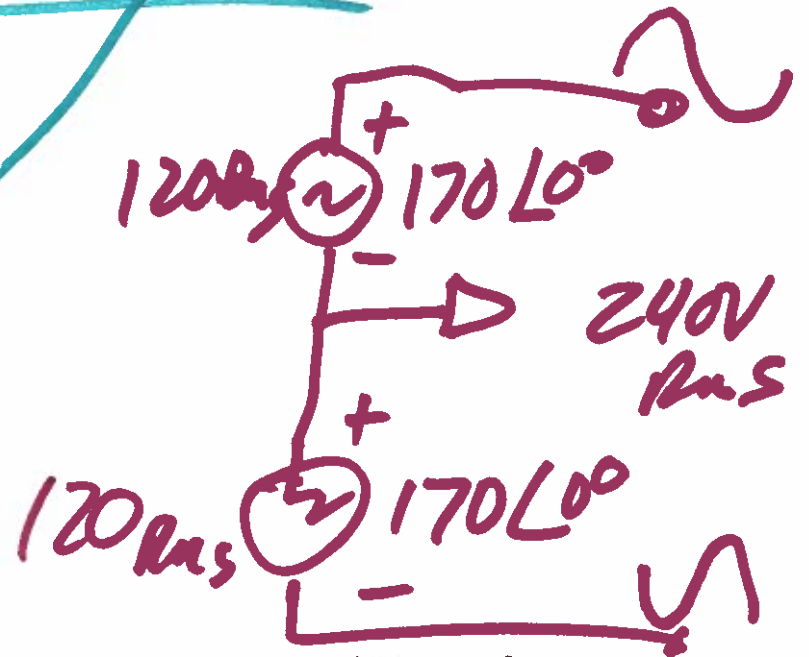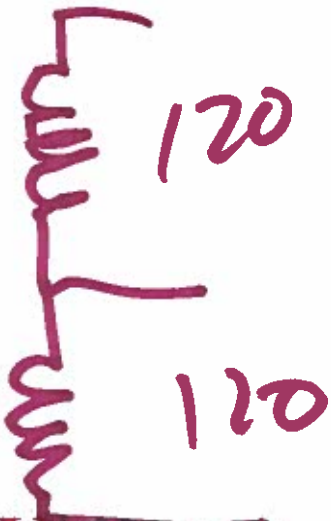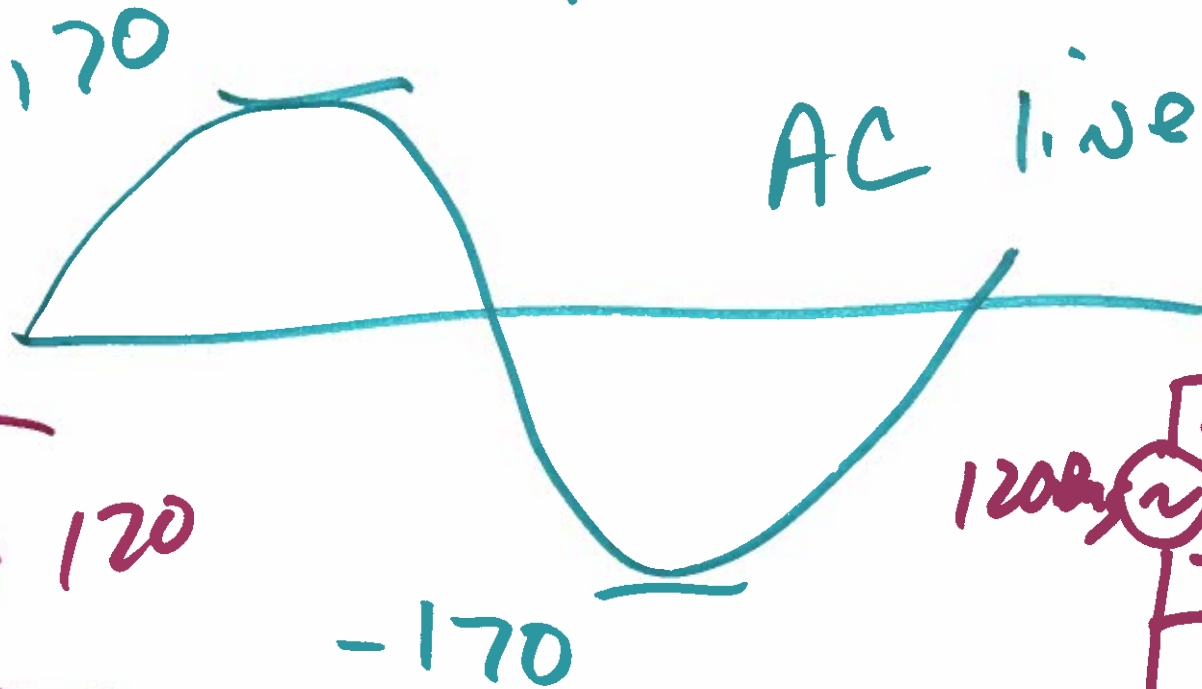
$$V_p = 120 \cdot \sqrt{2} = 169.2 \approx 170V$$



3)

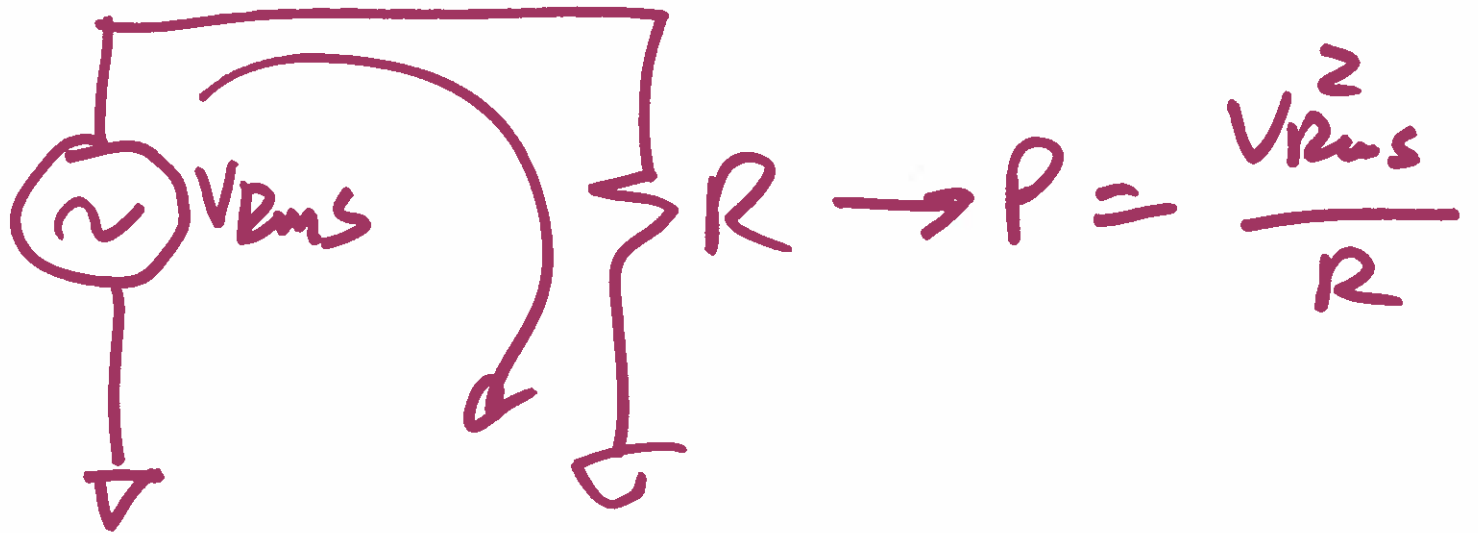

$$I_{rms} = \frac{V_{rms}}{R} = 1 \mu A$$

$$i(t) = 1 \mu A \cdot \sqrt{2} \cdot \cos(2\pi f \cdot t)$$

$$V_{Rms} \stackrel{\lim}{T \rightarrow \infty} = \sqrt{\frac{1}{T} \int_0^T v_{oc}^2 \cdot dt}$$



$$= \sqrt{\frac{1}{T} v_{oc}^2 T}$$

$$V_{Rms} = v_{oc} = \frac{v_p}{\sqrt{2}}$$

$$v(t) \cdot i(t)$$


$$I_{Rms} \cdot V_{Rms} = \frac{v_{rms}^2}{R}$$

5)

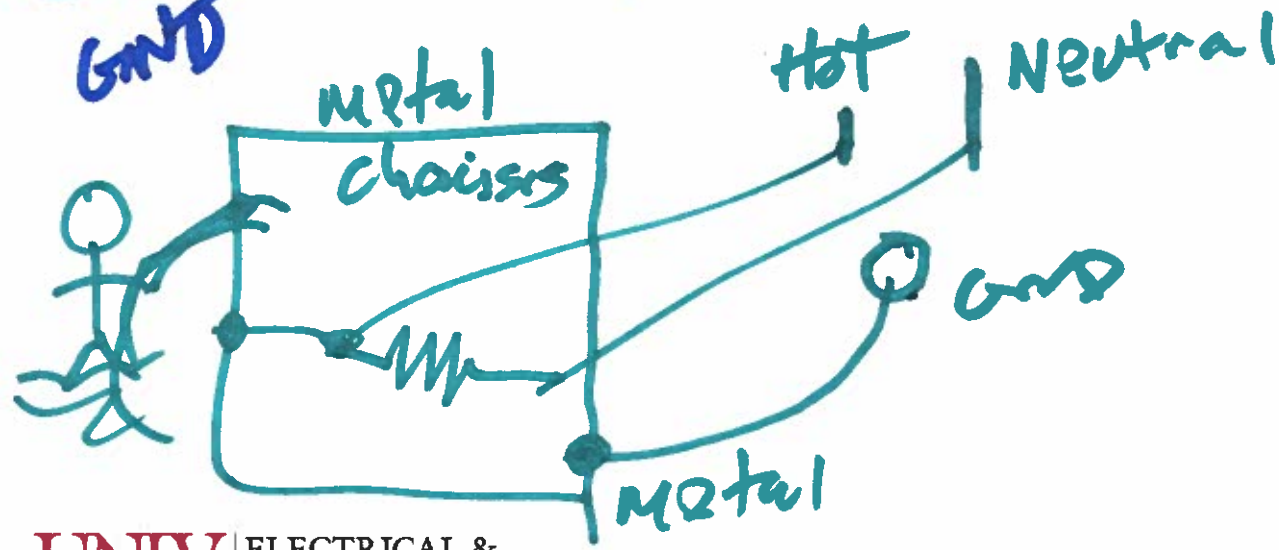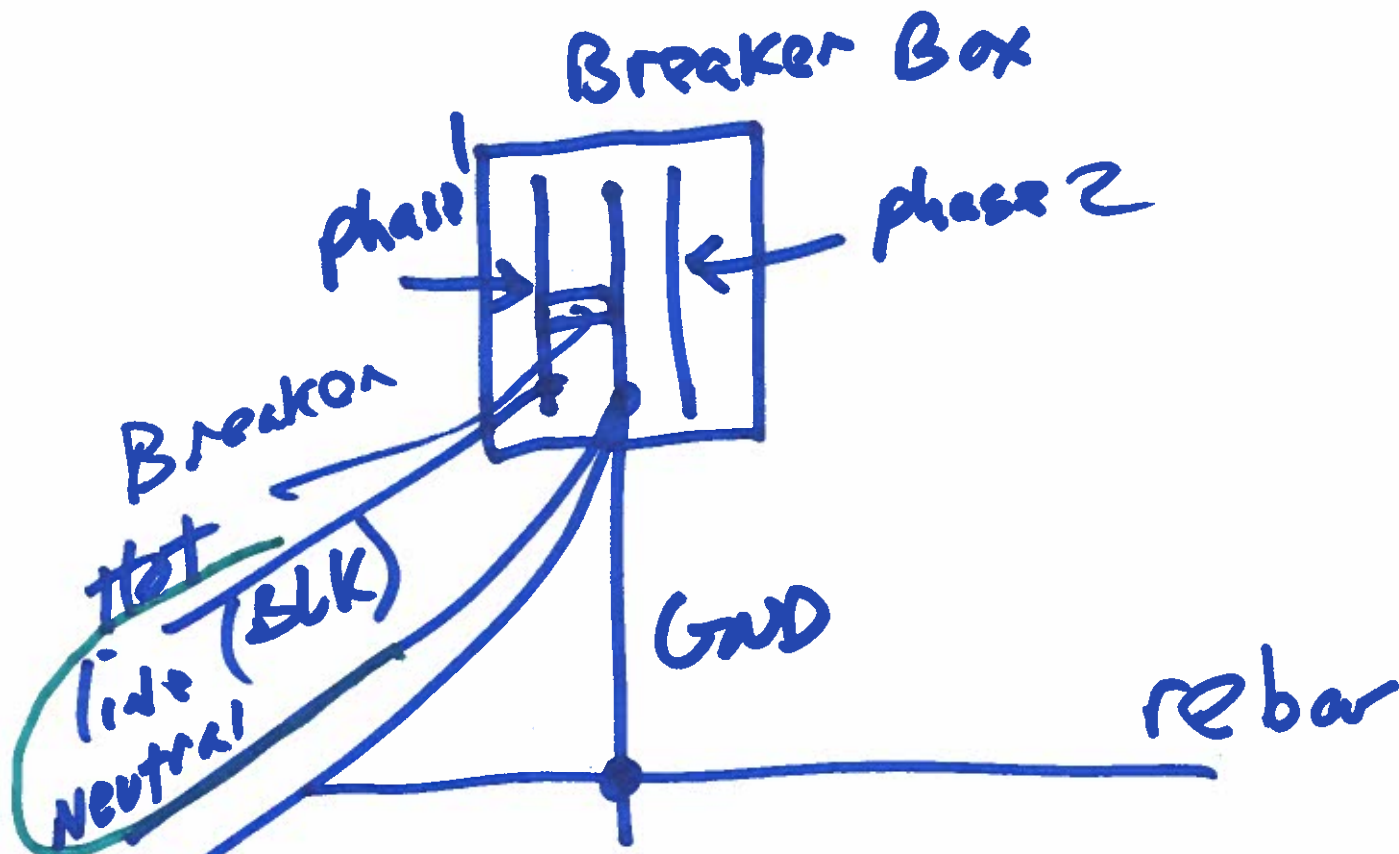

6)



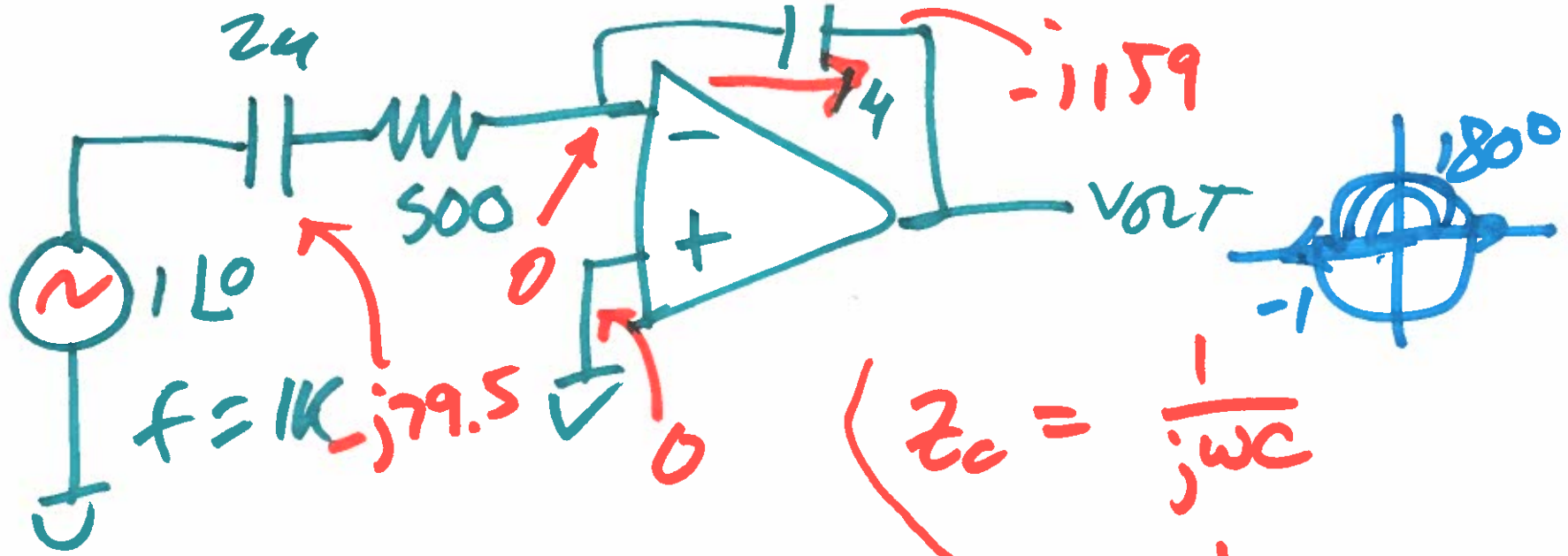

$$\frac{100}{500 + j(-79.5)} = \frac{0 - V_{out}}{j(-159)} = \frac{1}{j \cdot 2\pi \cdot 10^3 \cdot 10^{-6}} = -j159$$

$$\frac{100}{506.3 \angle -9^\circ} = \frac{V_{out} \angle 180^\circ}{159 \angle 270^\circ} \quad -1 \Rightarrow 1 \angle 180^\circ$$



$$D \angle \theta_4 \cdot \frac{A \angle \theta_1}{B \angle \theta_2} = \frac{C \angle \theta_3}{D \angle \theta_4} \cdot D \angle \theta_4$$

$$= \frac{C \angle \theta_3 + \theta_4 - \theta_4}{\cancel{\emptyset}}$$

$$\frac{1.159}{506}$$


$$= C \angle \theta_3$$

$$V_{out} = \frac{1 \angle 0 \cdot 1.159 \angle 270^\circ}{506.3 \angle -9^\circ \cdot 1 \angle 180^\circ} = \frac{\angle (270 - (-9))}{-180}$$

$$V_{out} = 0.314 \angle 99^\circ$$

$$v_{in} = 1 \cdot \sin(2\pi \cdot 10^3 \cdot t)$$
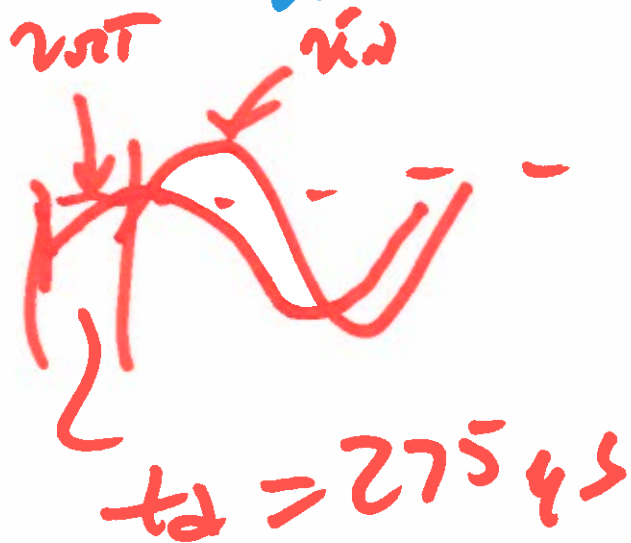
$$v_{out} = 314 \text{ mV} \cdot \sin(2\pi \cdot 10^3 \cdot t + 99)$$



$$\theta = \frac{t_d}{T} \cdot 360$$

$$\frac{99}{360} \cdot 1 \mu\text{s} = t_d$$

$$t_d = 275 \text{ ns}$$