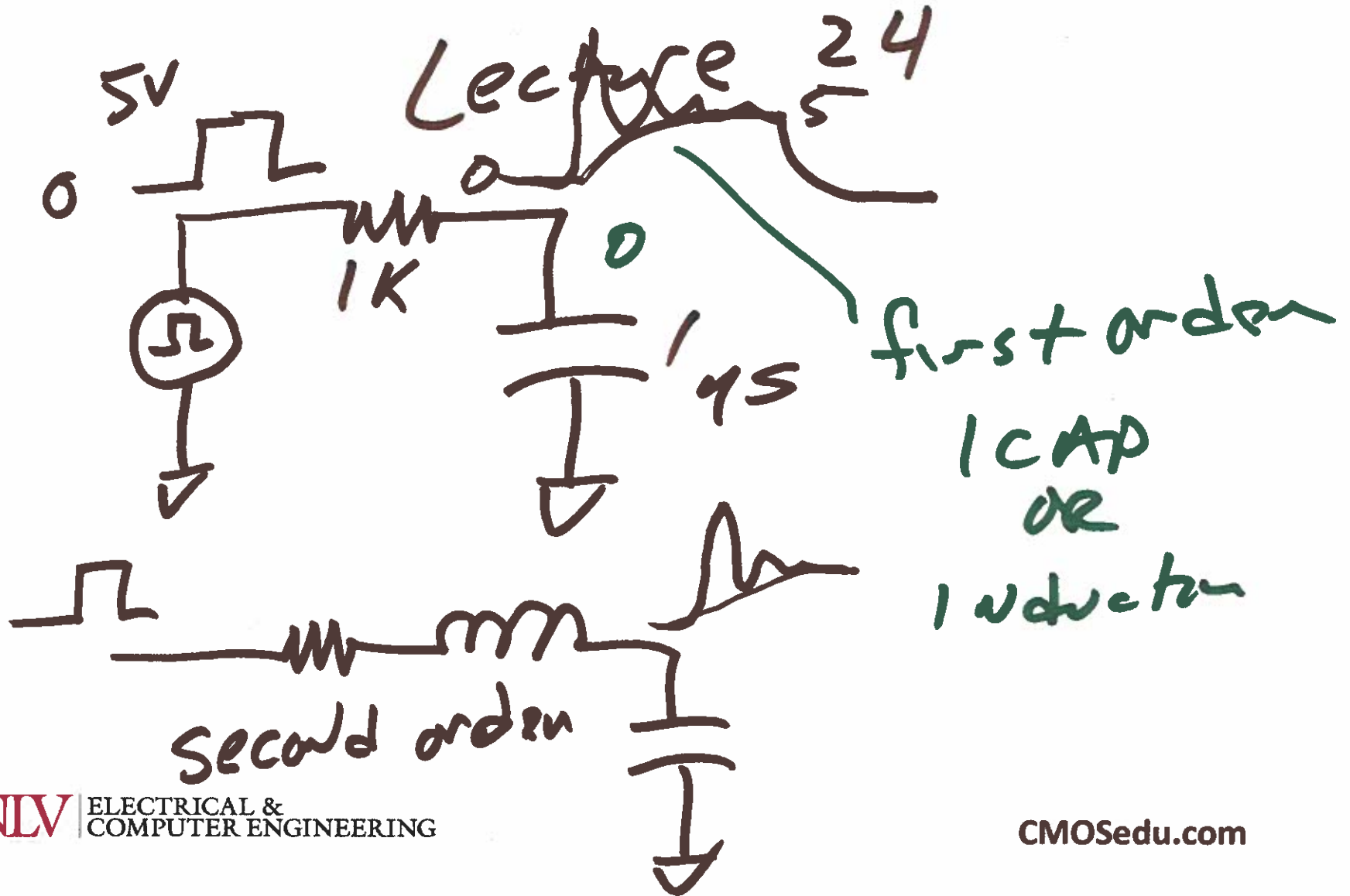



EE 220 Circuits I

Nov. 25, 2019

Lecture 24



1)

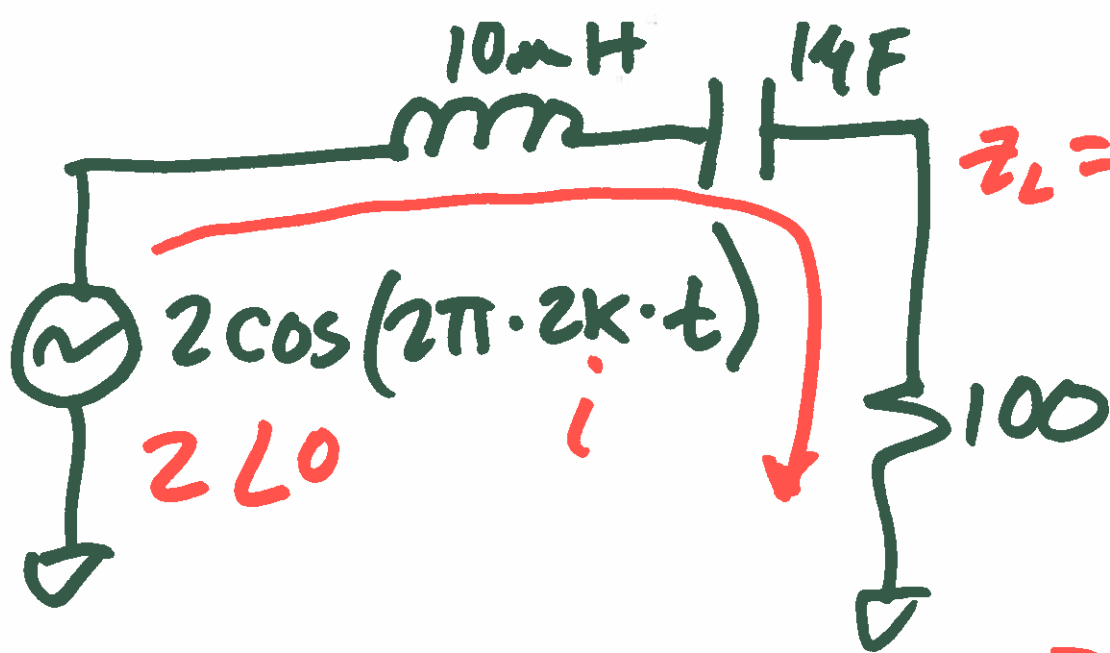

$$\begin{aligned}
 z_L &= j \cdot 2\pi \cdot 0.010 \cdot 2 \cdot 10^3 \\
 &= j \cdot 2\pi \cdot 10 \cdot 2 \\
 &= 40\pi j \\
 &= j \cdot 125.6
 \end{aligned}$$

$$i = \frac{2 \angle 0}{100 + j(125.6 - 79.6)}$$

$$\begin{aligned}
 z_C &= \frac{1}{j \cdot 2\pi \cdot 2 \cdot 10^3 \cdot 10^{-6}} \\
 &= \frac{1}{j 4\pi \cdot 10^{-3}} \\
 &= -j 79.6
 \end{aligned}$$

$$|100 + j 46| = 110$$


$$\angle 100 + j 46 = \tan^{-1} \frac{46}{100} = 25^\circ (24.7^\circ)$$

2)

$$i = \frac{2 \angle 0}{110 \angle 25} = i = 18.2 \text{ mA} \angle -25^\circ$$

$$-25 = \frac{t_d}{500 \mu\text{s}} \cdot 360$$

$$t_d = 34.7 \mu\text{s}$$

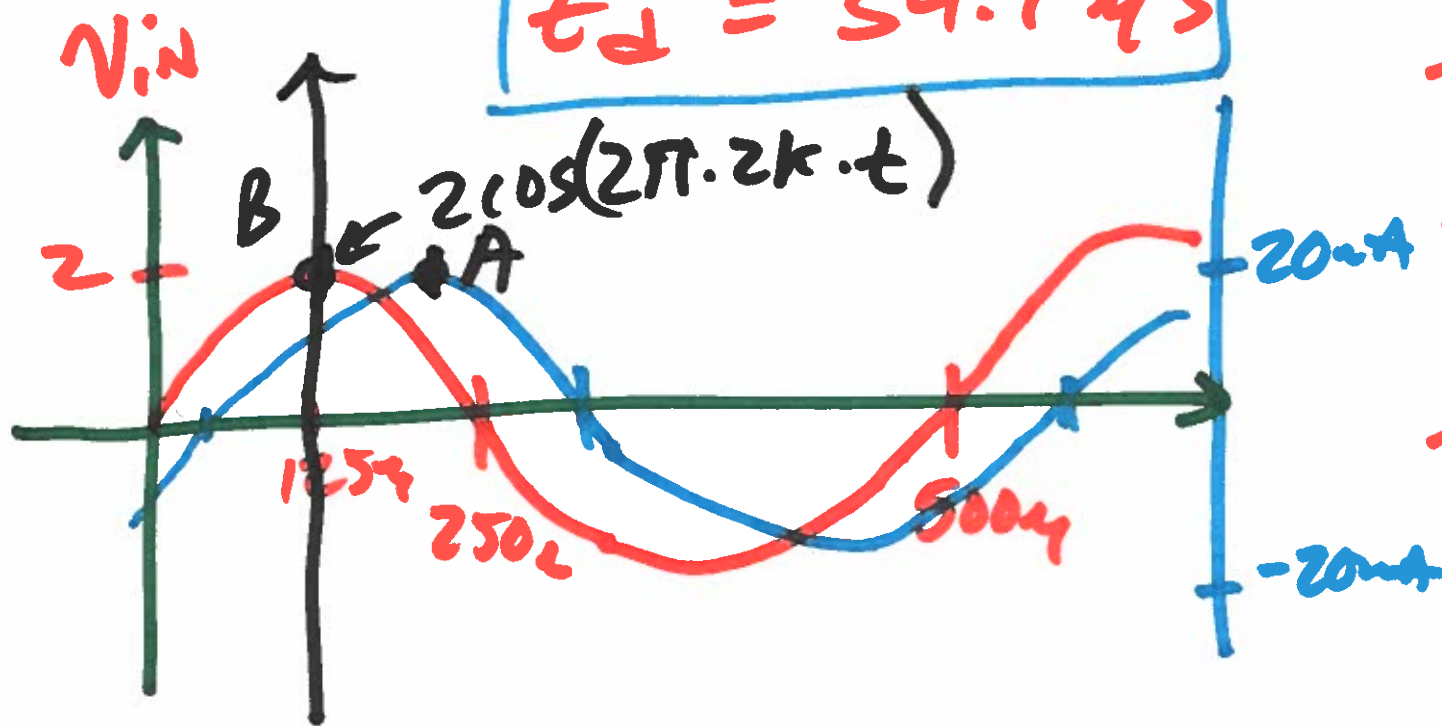

$$f = 1 \text{ K}, T = 1 \mu\text{s}$$


$$f = 2 \text{ K}, T = \frac{1}{2} \mu\text{s} = 500 \mu\text{s}$$

$$f = 1 \text{ MHz}, T = 1 \mu\text{s}, 2 \mu\text{s} =$$

$$i(t) = 18.2 \text{ mA} \sin(2\pi \cdot 10^3 \cdot 2t - 25)$$

$$i(t) = 18.2 \text{ mA} \cos(2\pi \cdot 2 \cdot 10^3 t - 25)$$

3)

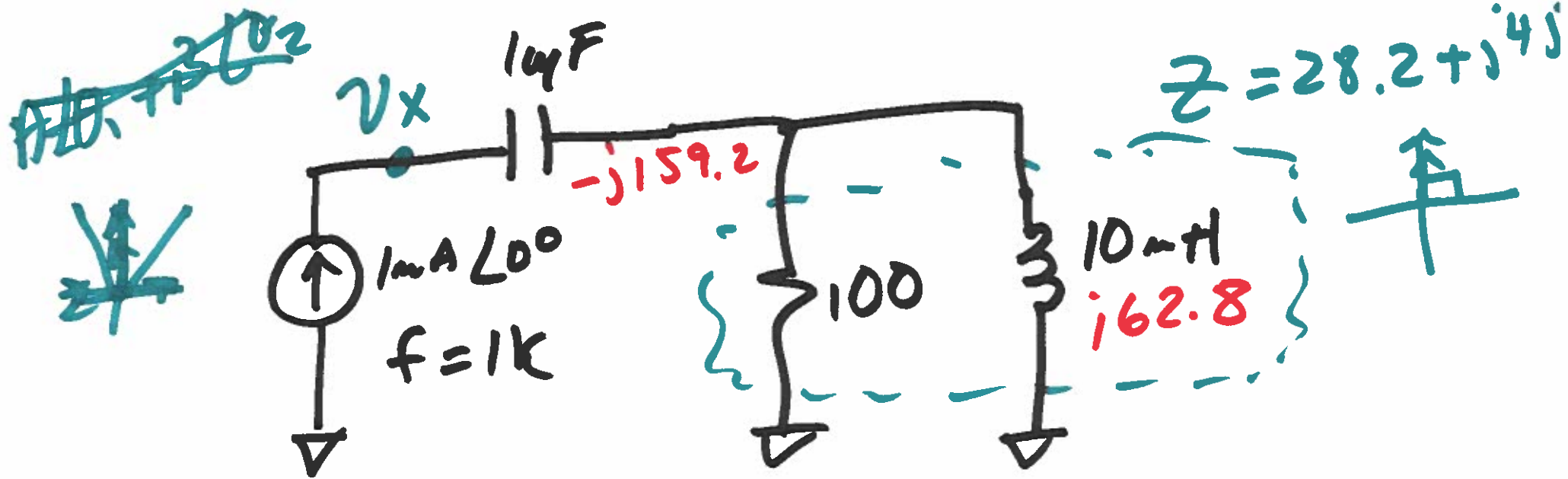

$$z = \frac{0 + 100 \cdot j62.8}{100 + j62.8} = \frac{6,280 \angle 90^\circ}{118 \angle 32^\circ}$$

$$28.2 + j45.1 = z = 53.2 \angle 58^\circ$$

$$R = X = 53.2 \cos(58^\circ)$$

$$Y = 45.1$$


$$X = 28.2$$

$$i_m = 53.2 \sin 58$$

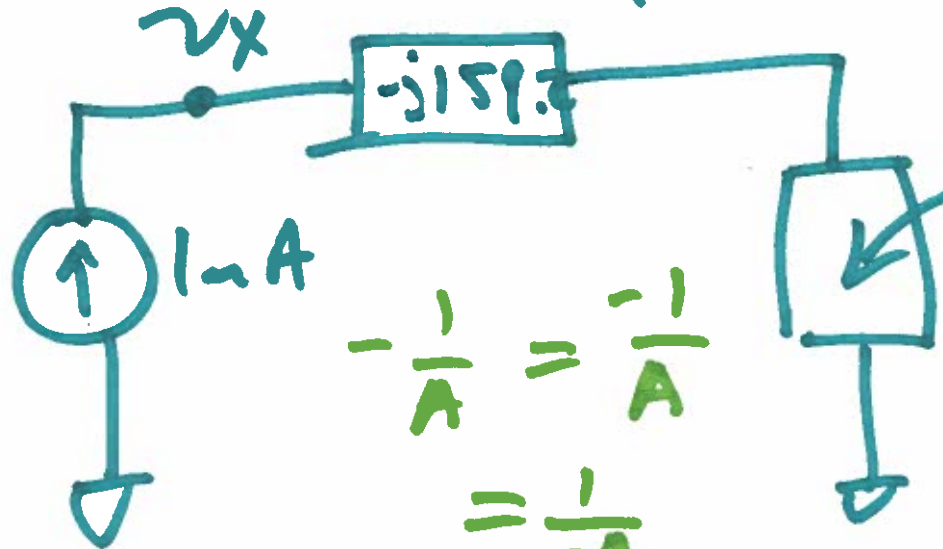4)

$$117.3 \mu V \angle -76^\circ$$

$$= V_x = 1 \mu A \cdot 20 \cdot \frac{(-j159 + 28.2 + j45.1)}{117.3 \angle -76^\circ}$$



$$28.2 + j45.1$$

$$-\frac{1}{A} = \frac{-1}{A} = \frac{1}{-A}$$


$$\frac{1}{1} = 1 = \frac{A}{A} = \frac{72}{72}$$

$$| 28.2 + j(45.1 - 159) |$$


$$-113.9$$

$$= 117.3$$
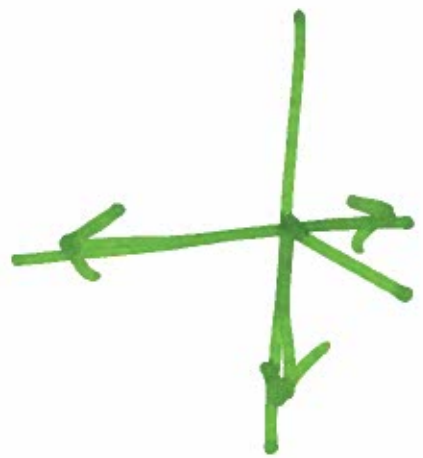
$$\angle \tan^{-1} \frac{-113.9}{28.2} = -76^\circ$$



5)

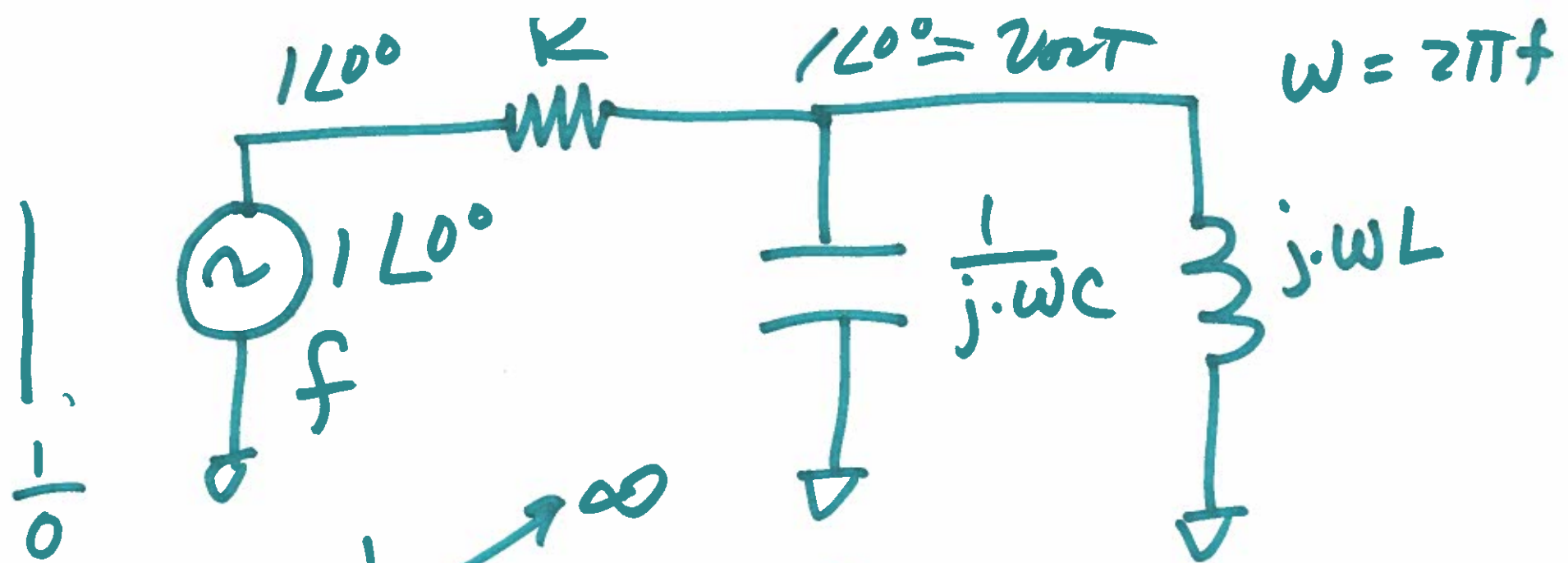

$j\omega L \cdot \frac{1}{j\omega C}$
 $\rightarrow \infty$

Resonance, $s = j\omega$

$j\omega L = \frac{L}{j\omega C}$

~~$j\omega L + \frac{1}{j\omega C}$~~

~~$j\omega L + \frac{1}{j\omega C}$~~
 $\frac{L}{C}$
 $\rightarrow 0$

$\omega^2 = \frac{1}{LC}$

$f = \frac{1}{2\pi\sqrt{LC}}$

b)