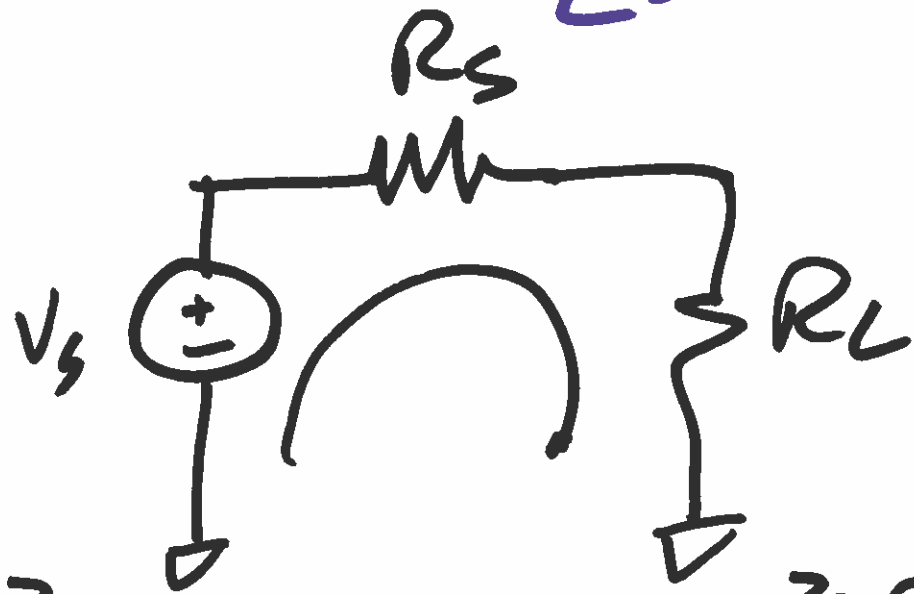


EE220 Circuits 1

Dec. 4, 2019

Lecture 27



$$I = \frac{V_s}{R_s + R_L}$$

$$P_L = I^2 R_L$$


$$\frac{V_s^2}{R_s^2 R_L^{-1} + 2R_s + R_L} = \frac{V_s^2 R_L}{R_s^2 + 2R_s R_L + R_L^2} = \frac{V_s^2 \cdot R_L}{(R_s + R_L)^2}$$

$$\frac{d}{dR_L} (R_S^2 R_L^{-1} + 2R_S + R_L) = 0$$

$$(-1) \cdot R_S^2 R_L^{-2} + 0 + 1 = 0$$

$$\frac{R_S^2}{R_L^2} = 1$$

$$R_S = R_L$$

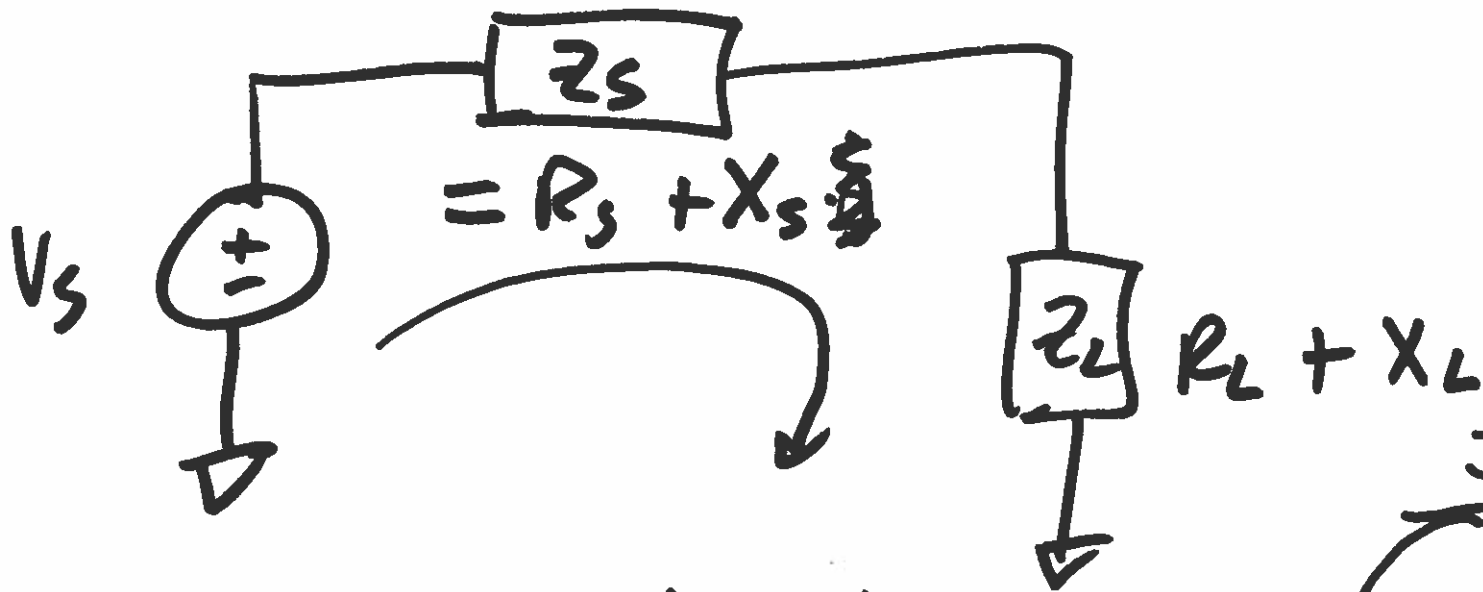

$$|I| = \frac{|V_s|}{|Z_s + Z_L|}$$

$$I_P = |I|$$

$$I_{\text{rms}} = \frac{I_P}{\sqrt{2}} = \frac{|I|}{\sqrt{2}}$$

$$P_L = I_{\text{rms}}^2 \cdot R_L = \frac{1}{2} \cdot \frac{|V_s|^2}{|Z_s + Z_L|^2} \cdot R_L$$

$$= \frac{1}{2} \frac{|V_s|^2 \cdot R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

$$P_L = \frac{1}{2} \frac{V_s^2 \cdot R_L}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

$a + jb$

$a - jb$

$$X_s = -X_L$$

X_s is the complex conjugate of X_L

$$X_L = 500 + j50$$

$$X_s = 500 - j50$$

MAX power transfer

$$\frac{a-jb}{a^2+b^2} = \frac{1}{a+jb} \cdot \frac{a-jb}{a-jb}$$

$$x + jy$$

$$\sqrt{x^2 + y^2} = | |$$


$$\frac{a}{a^2+b^2} + j \frac{-b}{a^2+b^2} = \sqrt{\left(\frac{a}{a^2+b^2}\right)^2 + \left(\frac{-b}{a^2+b^2}\right)^2}$$

$$\tan^{-1} \frac{y}{x} \quad \angle$$

$$\angle \tan^{-1} \frac{-b/a^2+b^2}{a/a^2+b^2} = \tan^{-1} \frac{-b}{a}$$

$$= -\tan^{-1} \frac{b}{a}$$

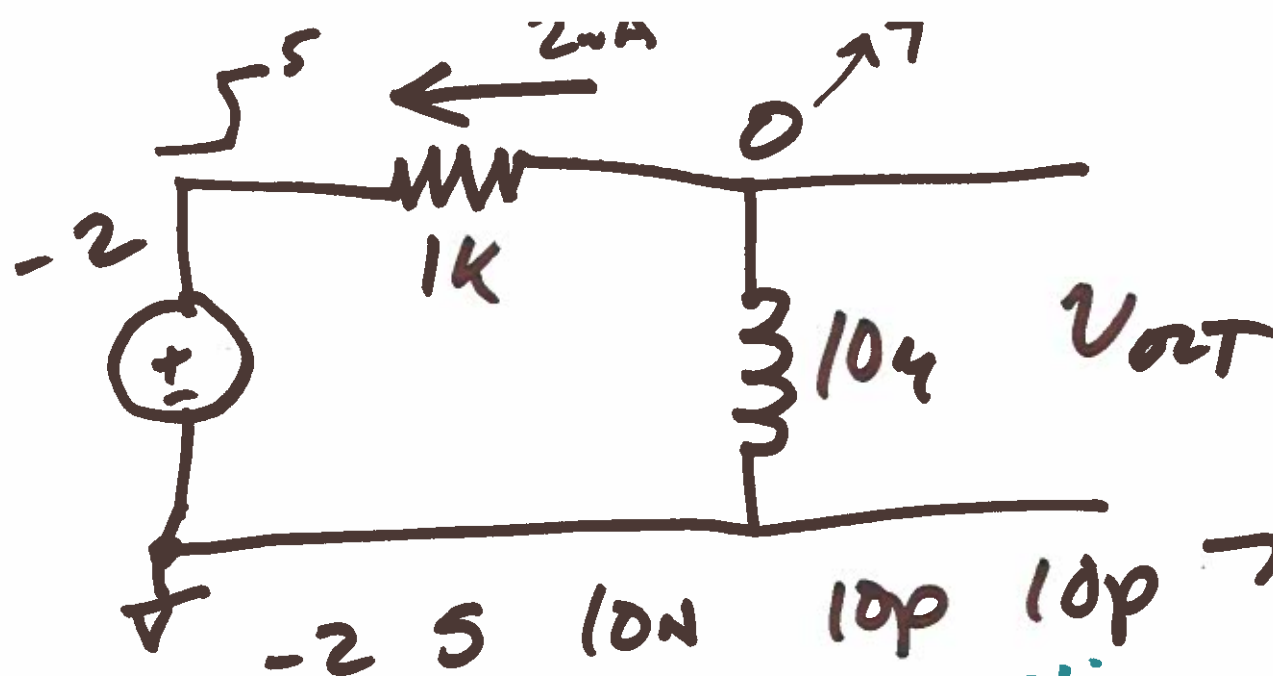
5) $\sqrt{\frac{a^2+b^2}{(a^2+b^2)^2}} = \frac{1}{\sqrt{a^2+b^2}}$ © 2015 edu.com





$$\tau = \frac{104}{1k} = 104ns$$

$$\frac{21}{10} \sim$$

-2 5 $10n$ $10p$ $10p$ $70n$

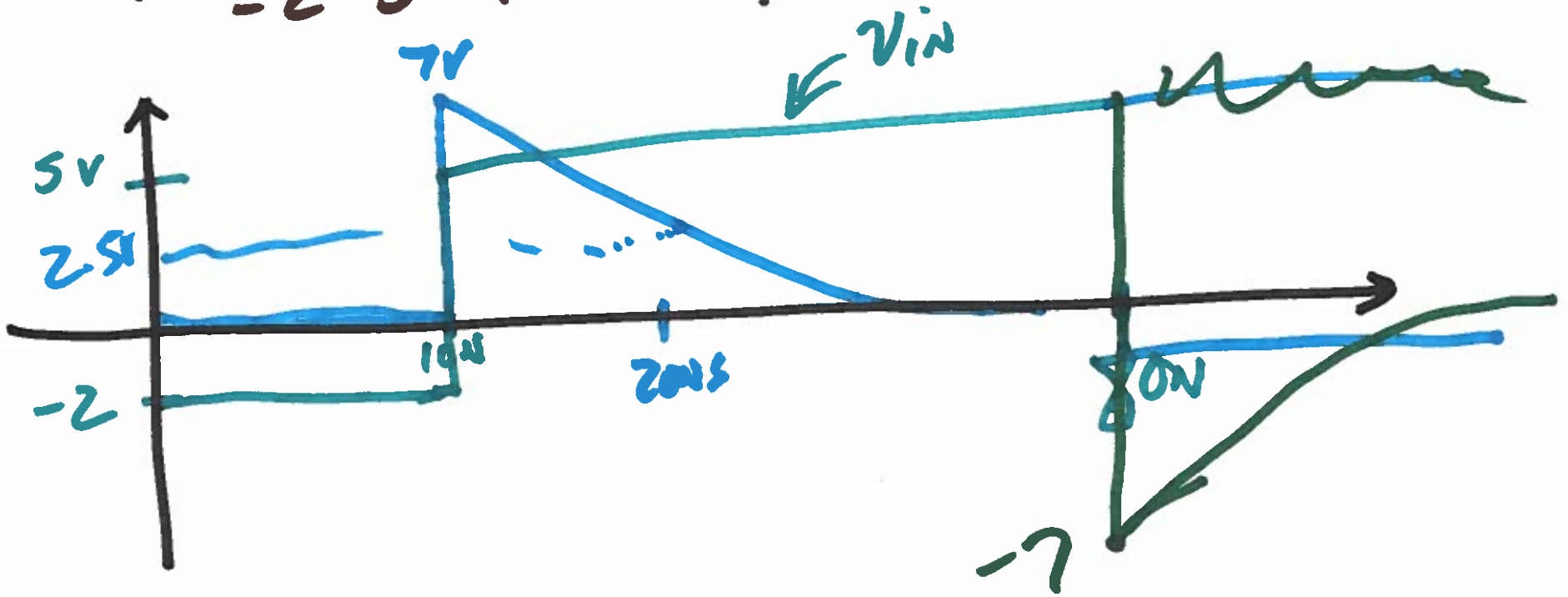

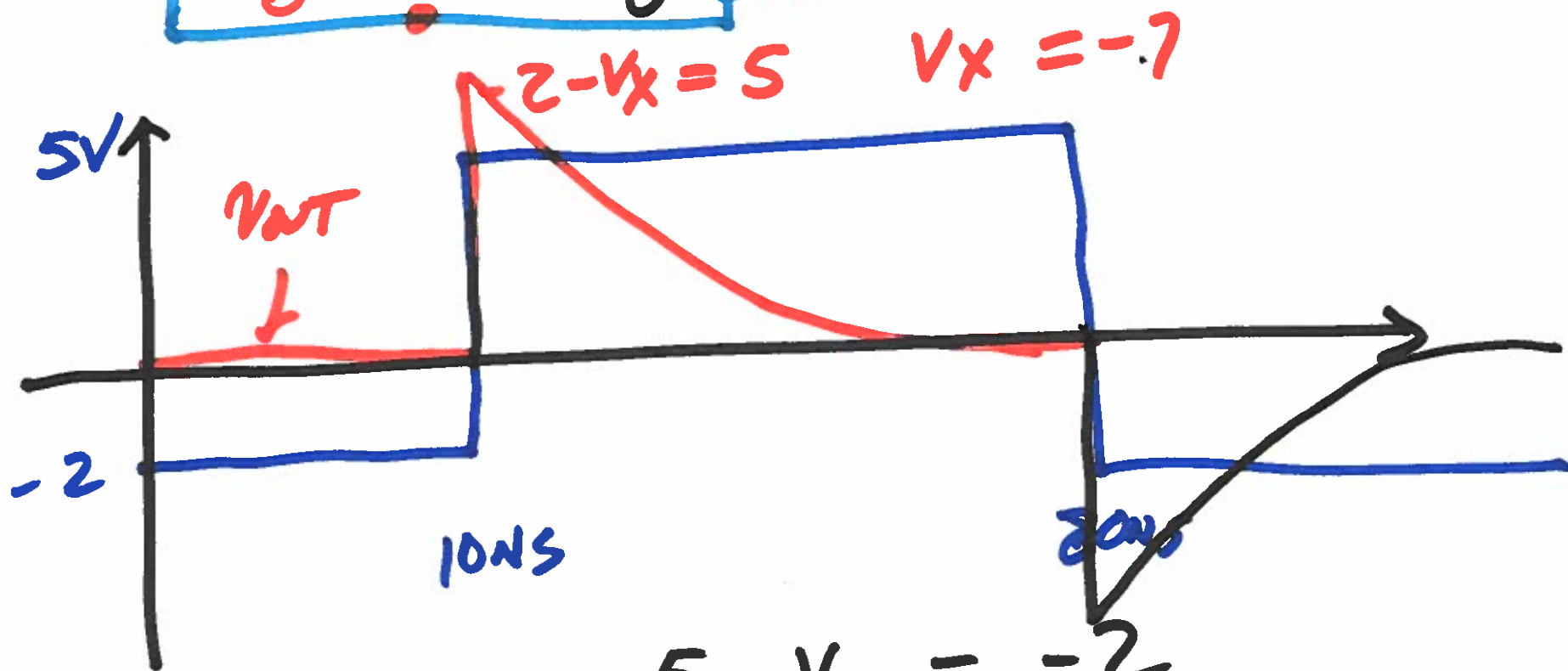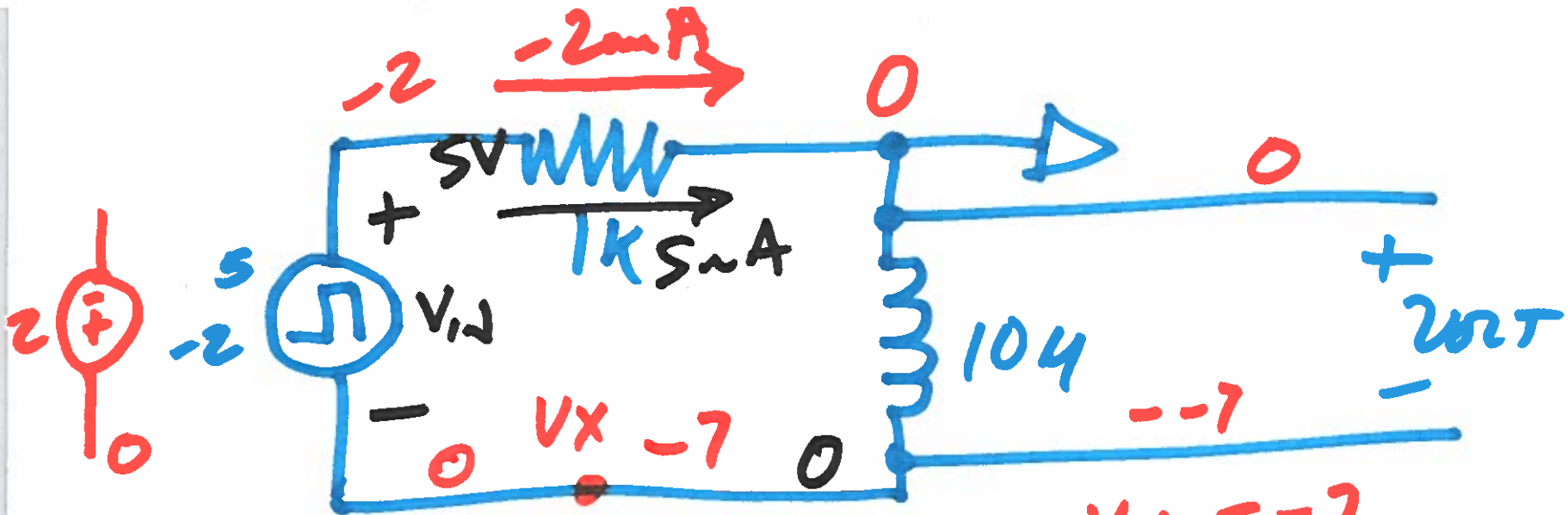

$2 - V_x = 5 \quad V_x = -7$

$5 - V_x = -2$

$V_x = 7$