


EE 220 circuits 1

August 28, 2019

Lecture 2

$$I \downarrow \begin{matrix} + \\ \downarrow \\ R \\ - \end{matrix} \quad V = I \cdot R$$

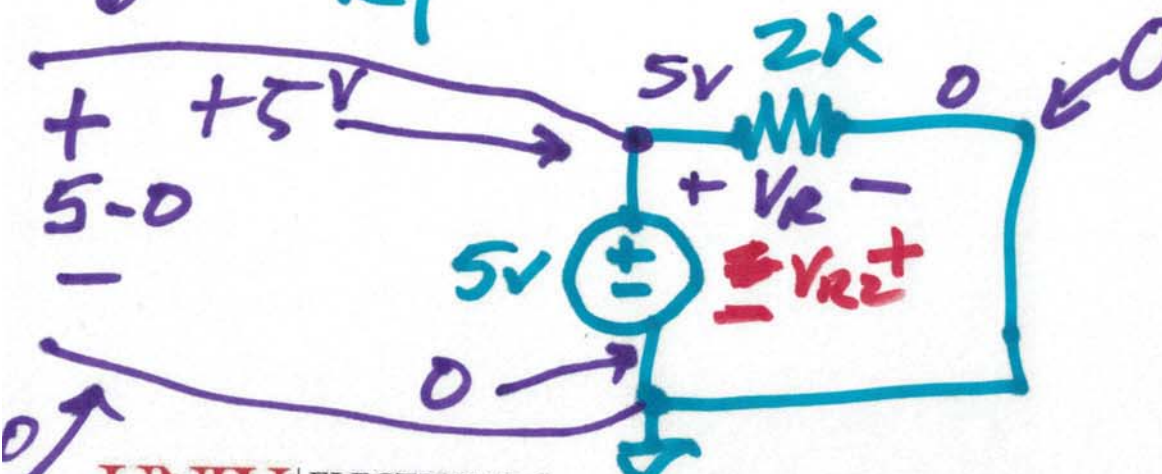
$$I \downarrow \begin{matrix} - \\ \downarrow \\ + \end{matrix} \quad V = -I \cdot R$$



$$5 - 0 = V_R = 5$$



$$V_{R2} = 0 - 5 = -5$$

1)

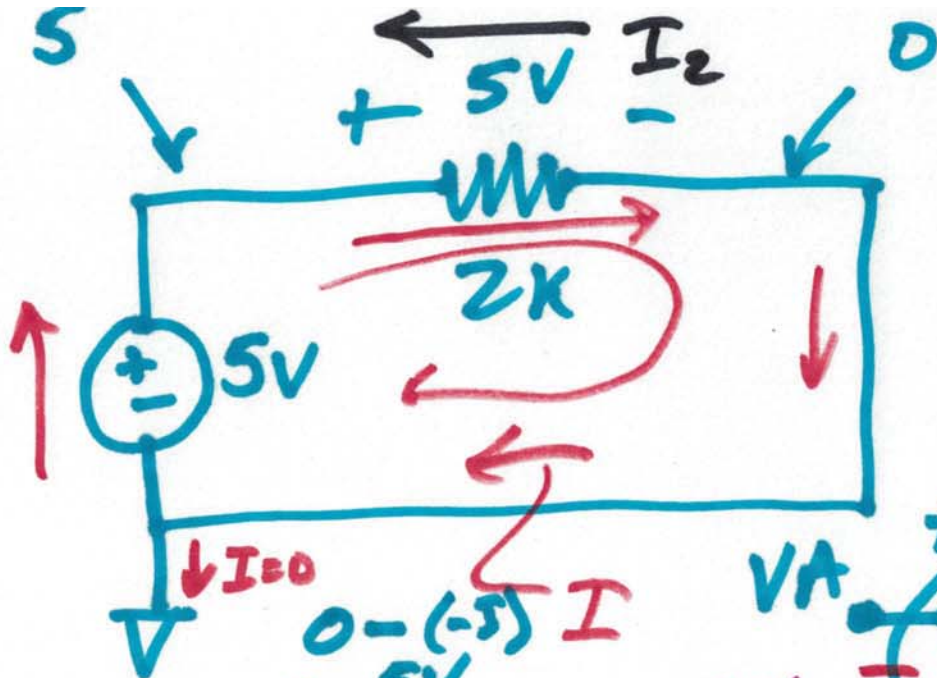

$$I = \frac{5}{2k} = 2.5 \mu A$$


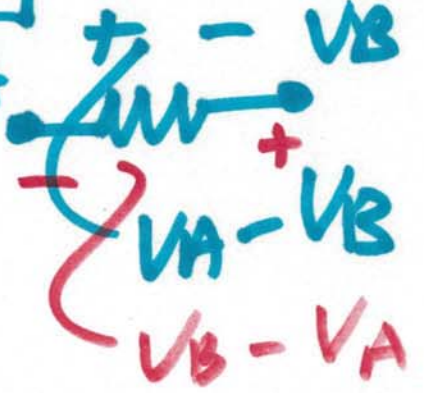
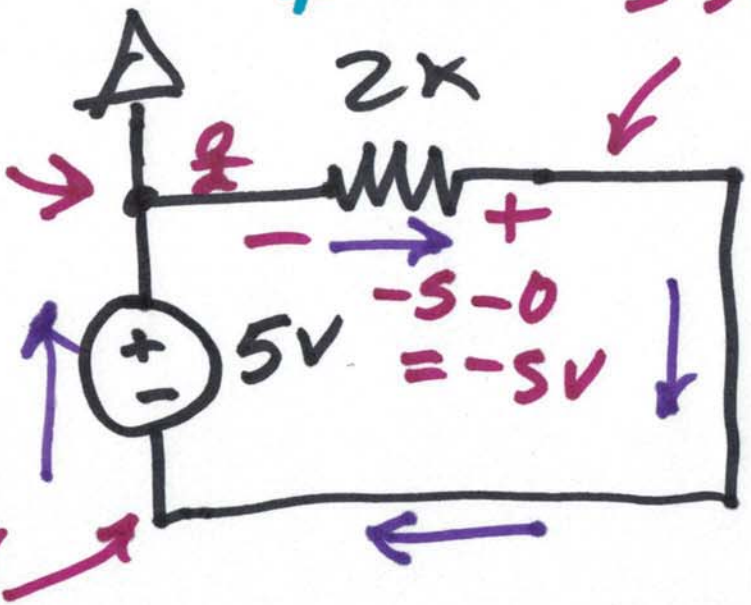
$$-I_2 = \frac{5}{2k} \Rightarrow I_2 = -I = -2.5 \mu A$$



$$V = -I \cdot R$$

$$-5 = -I \cdot 2k$$

$$I = 2.5 \mu A$$

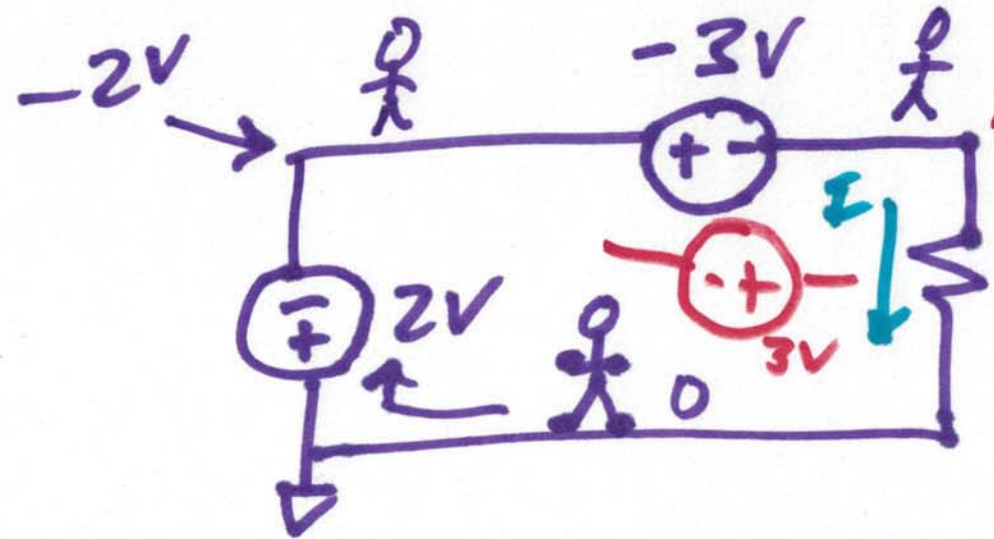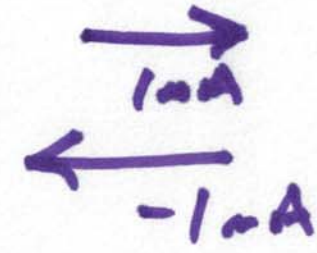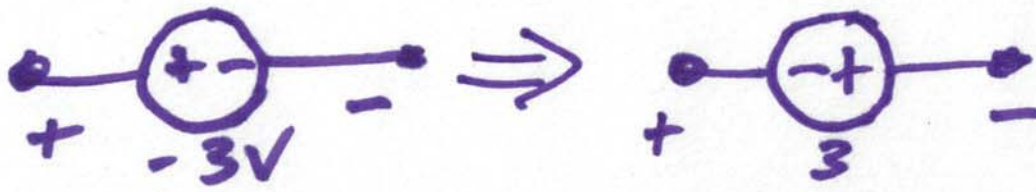


$+VR = I \cdot 1k$
 Kirchhoff's
 voltage
 law

$$-2V - (-3) - VR = 0$$


$$1 - I \cdot 1k = 0$$

$$I = \frac{1}{1k} = \underline{\underline{1mA}}$$
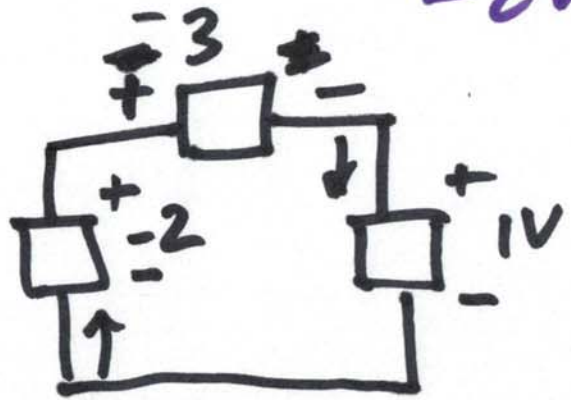
$$VR = I \cdot 1k = 1mA \cdot 1k = \underline{\underline{1V}}$$



b)

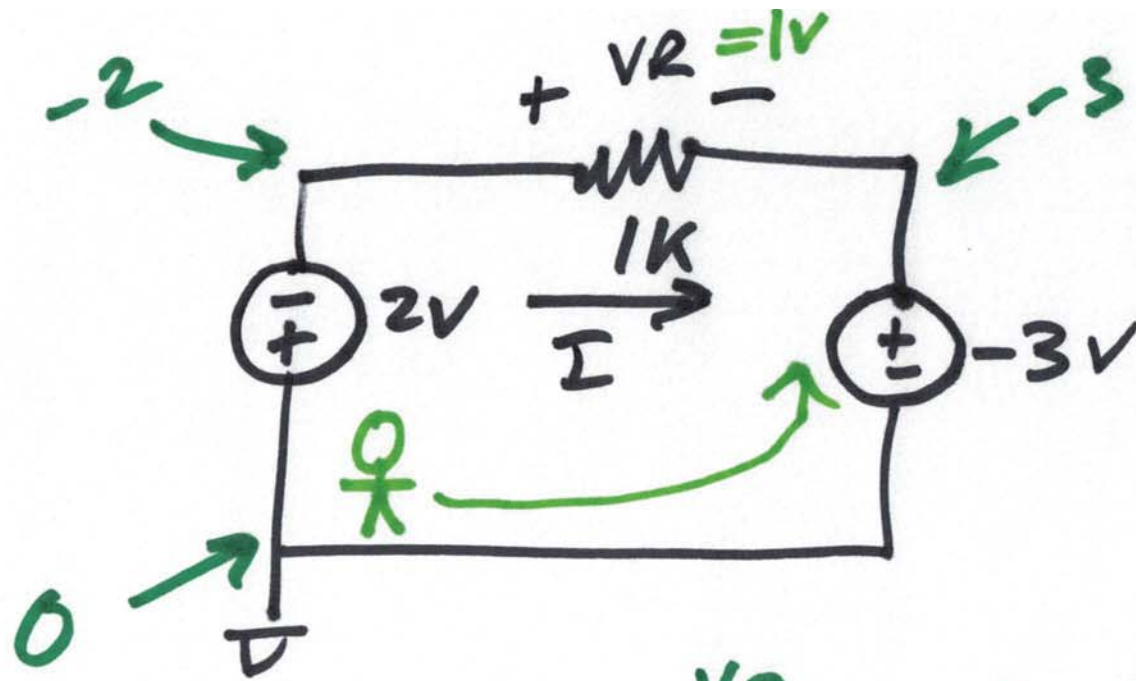


$$V_R = -2 - (-3) = 1V$$

$$I = \frac{V_R}{1k} = 1\mu A$$

$$+(-3) + 1 + 2 = 0$$

KVL

4)

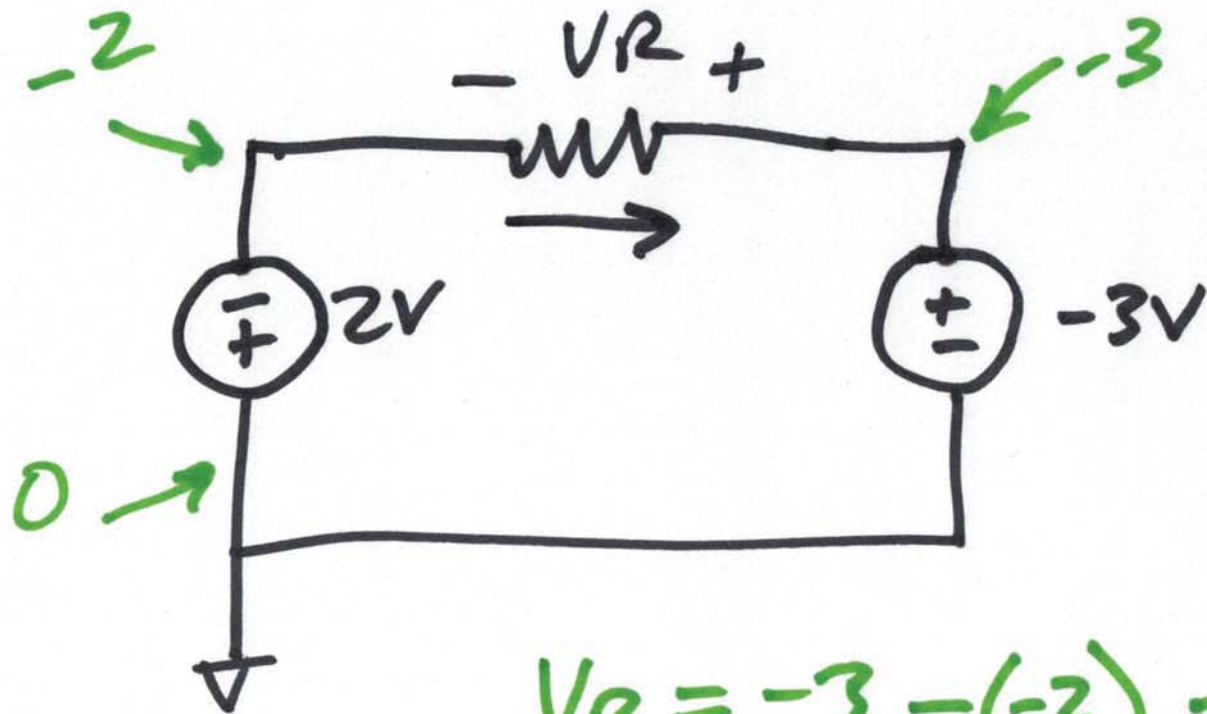



$$V_R = -3 - (-2) = \underline{\underline{-1V}}$$

$$V = -I \cdot R = -1V$$

$$-I = \frac{-1V}{1K}$$

$$I = 1mA$$

5)

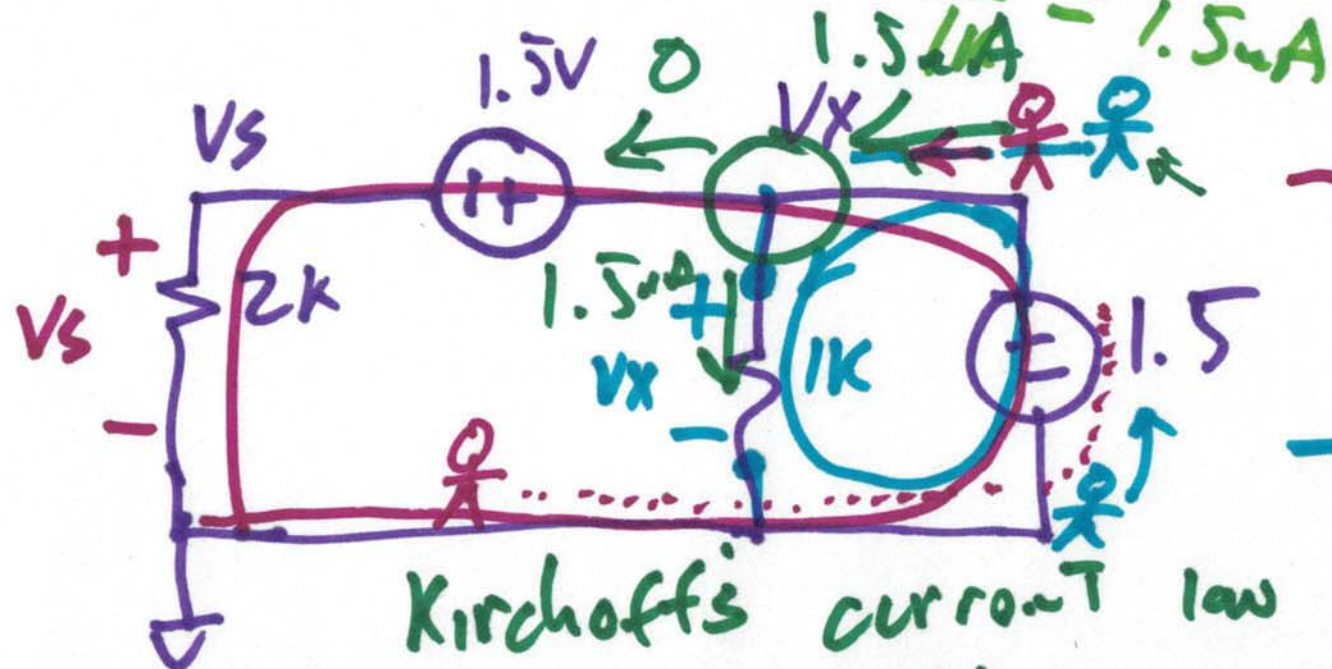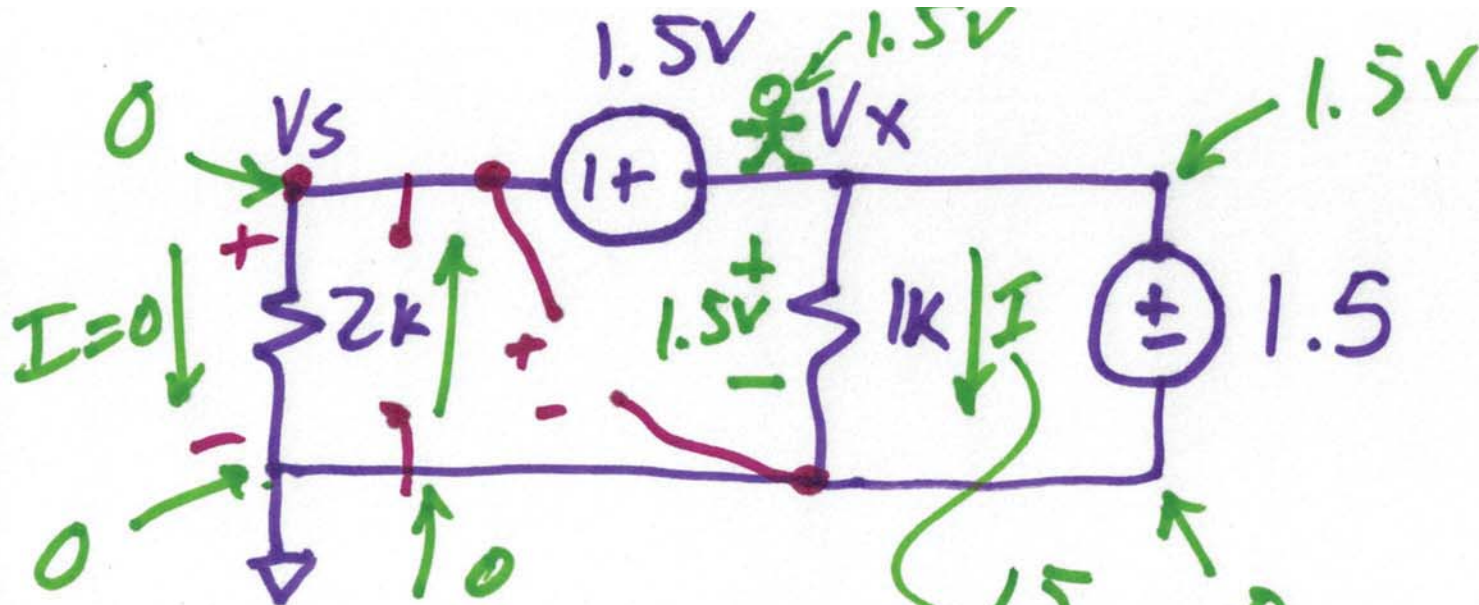

$$-1.5 - V_s + 1.5 = 0$$

$$V_s = 0$$

$$-V_x + 1.5 = 0$$

$$\underline{\underline{V_x = 1.5V}}$$


Kirchoff's current law

KCL

$$CURRENT_{IN} = CURRENT_{OUT}$$


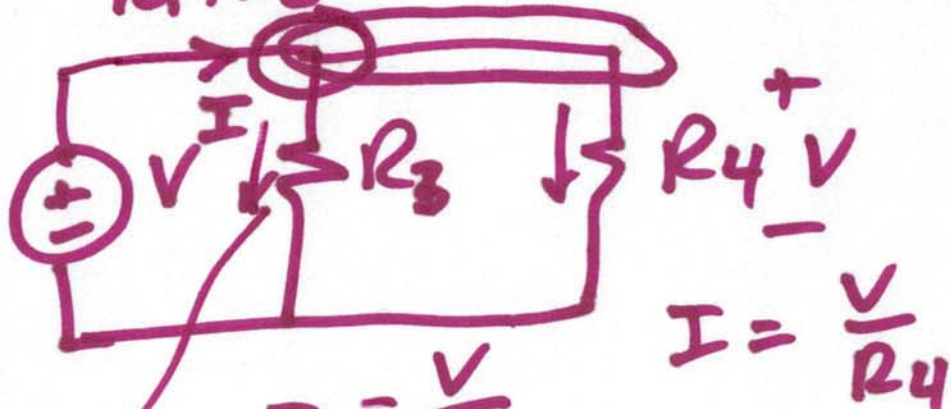
$$\frac{1}{20} + \frac{1}{10} = \frac{1}{T}$$




$$I = \frac{V}{R_4}$$

$$\frac{10}{20 \cdot 10} + \frac{20}{20 \cdot 10} = \frac{10 + 20}{20 \cdot 10}$$

$$T = \frac{20 \cdot 10}{20 + 10} = \frac{200}{30}$$

$$T = \frac{20}{3} \text{ hours}$$

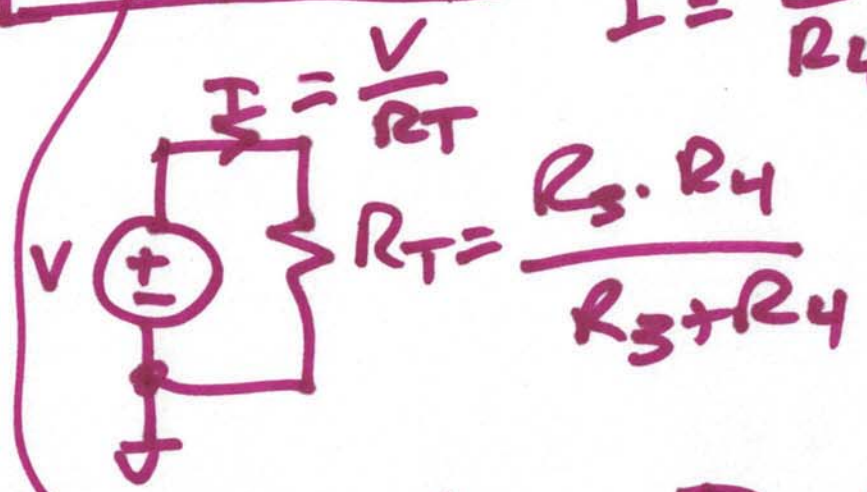


$$I_{R3} = \frac{V}{R_3}$$

$$I = I_{R3} + I_{R4}$$



$$I = \frac{V}{R_3} + \frac{V}{R_4} = \frac{V}{R_T}$$

CMOSedu.com

7)

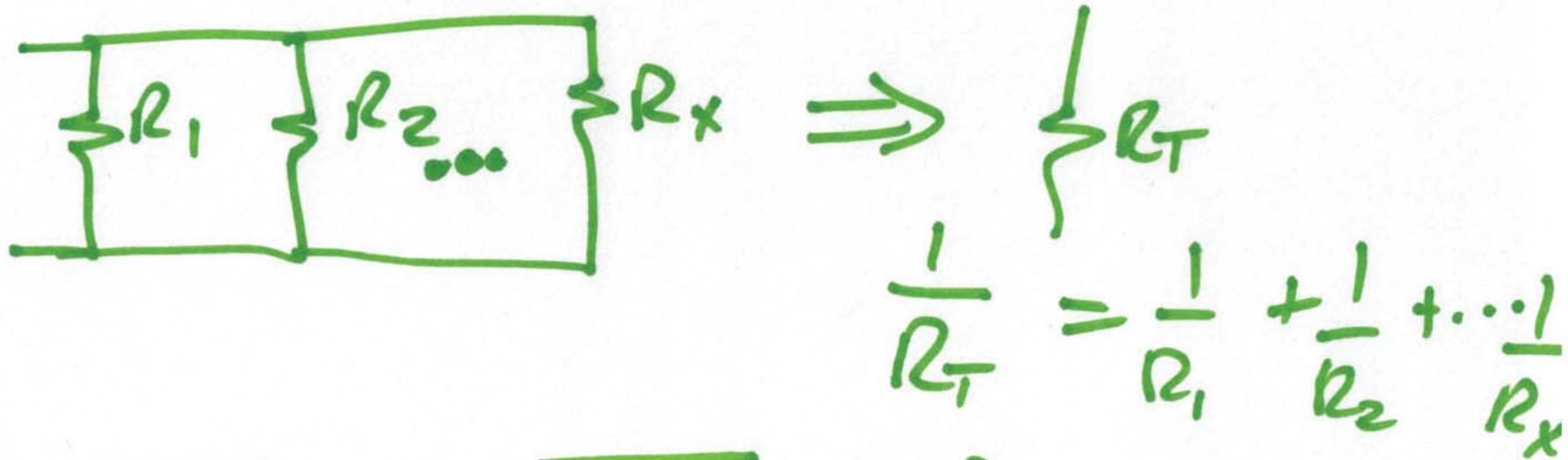


3)

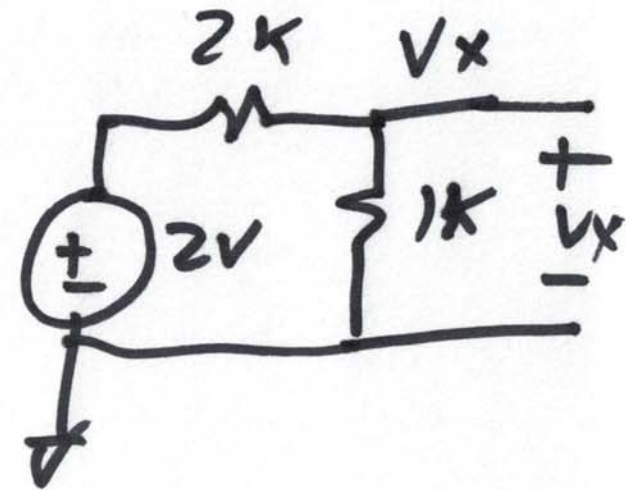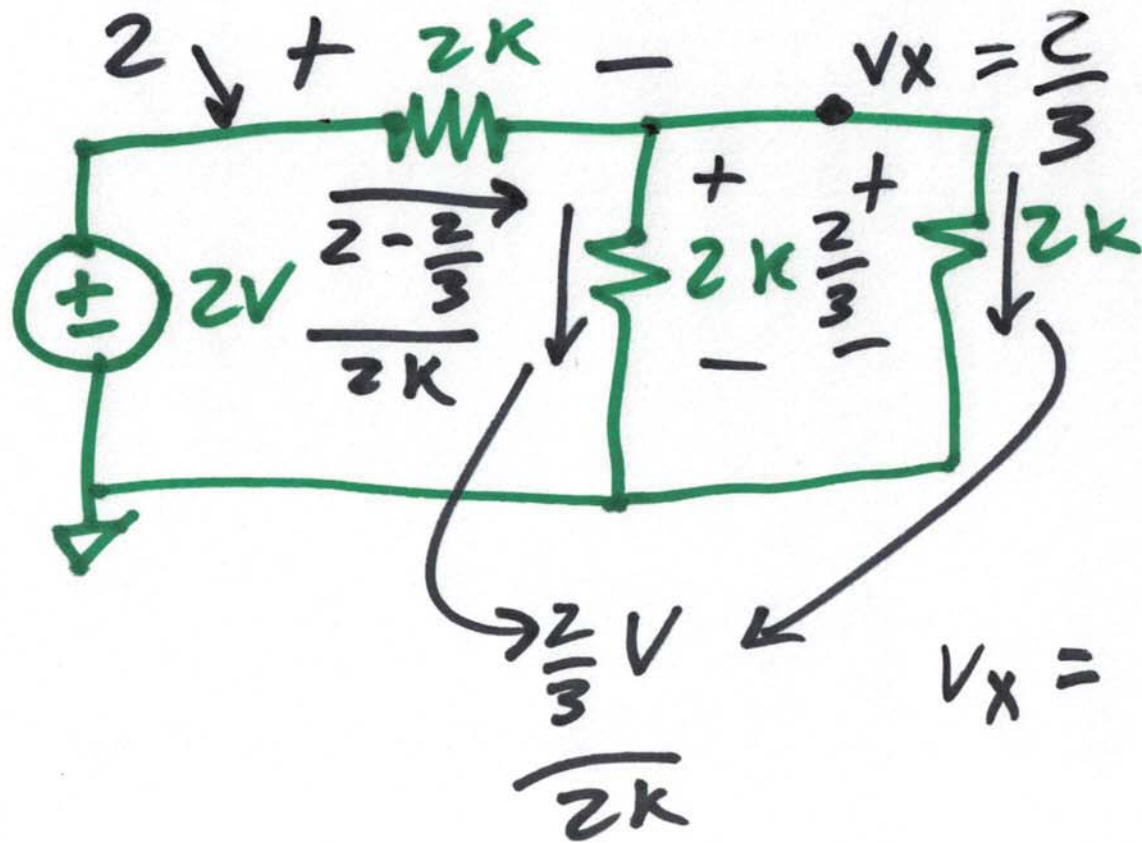

$$V_x = 2 \cdot \frac{1k}{1k + 2k} = \frac{2}{3} V$$

7)

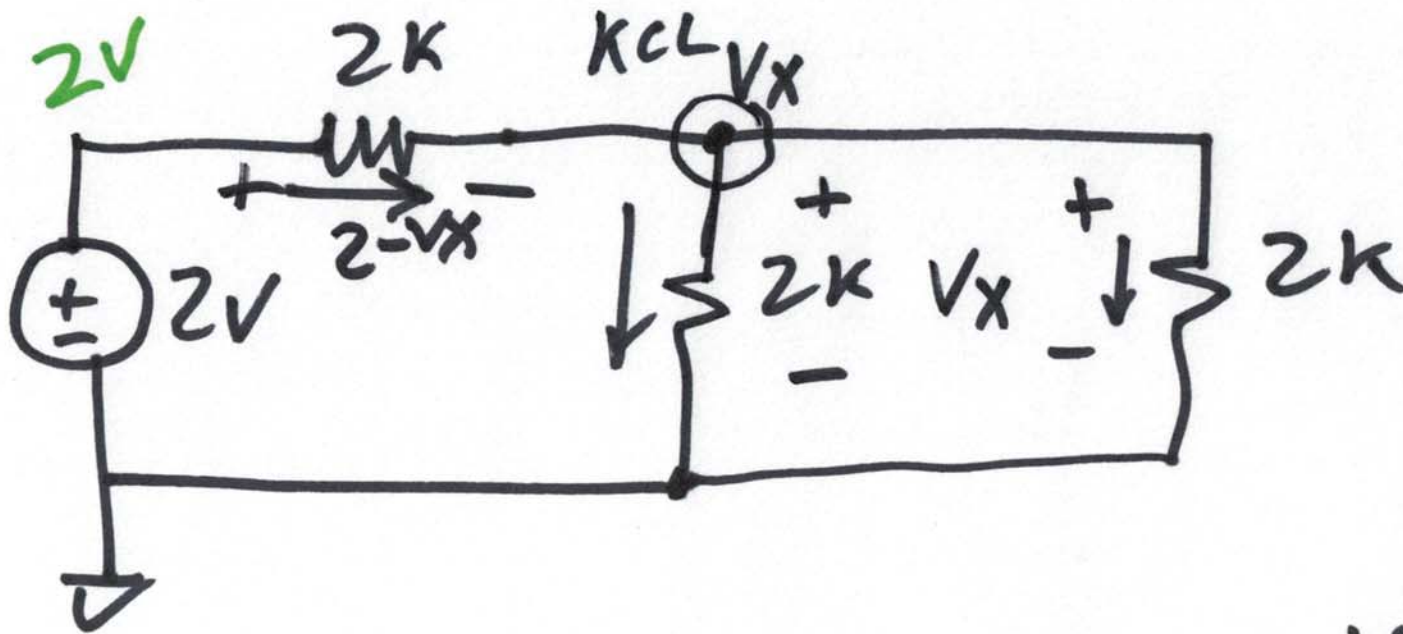

$$\frac{2 - V_x}{2k} = \frac{V_x}{2k} + \frac{V_x}{2k}$$

$$2 = 3 \cdot V_x$$

$$V_x = \frac{2}{3} V$$