
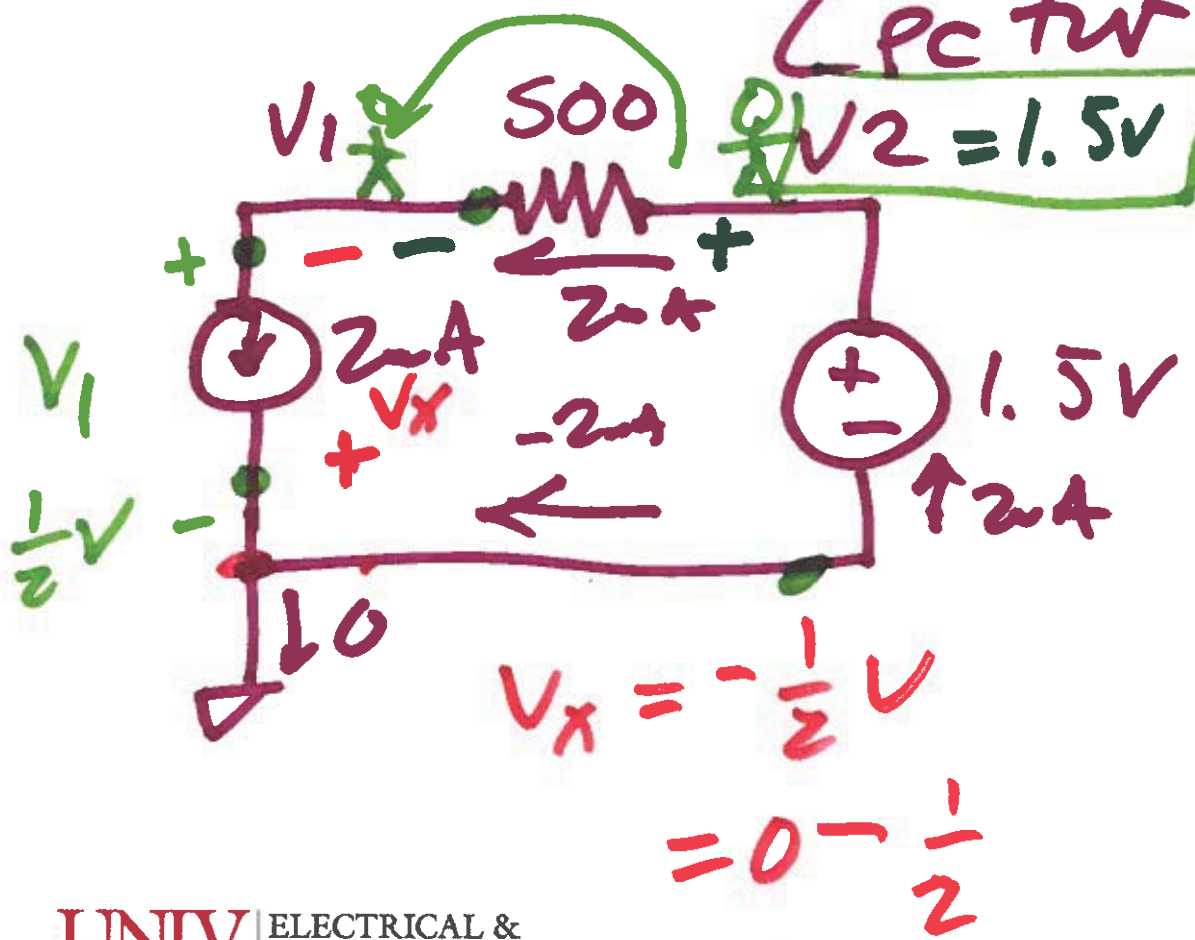


EE 220 circuits I

Sept. 4, 2019

Lecture 3

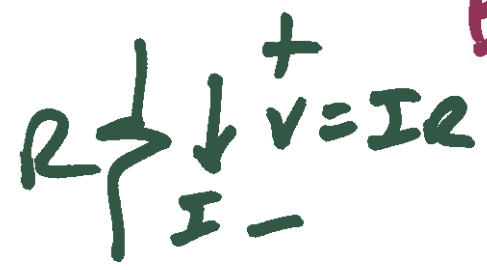


$$V_2 - V_1 = 2A \cdot 500 = 10V$$

$$V_1 = V_2 - 1 = 1.5 - 1$$

$$V_1 = 500\mu V = \frac{1}{2}V$$

1)

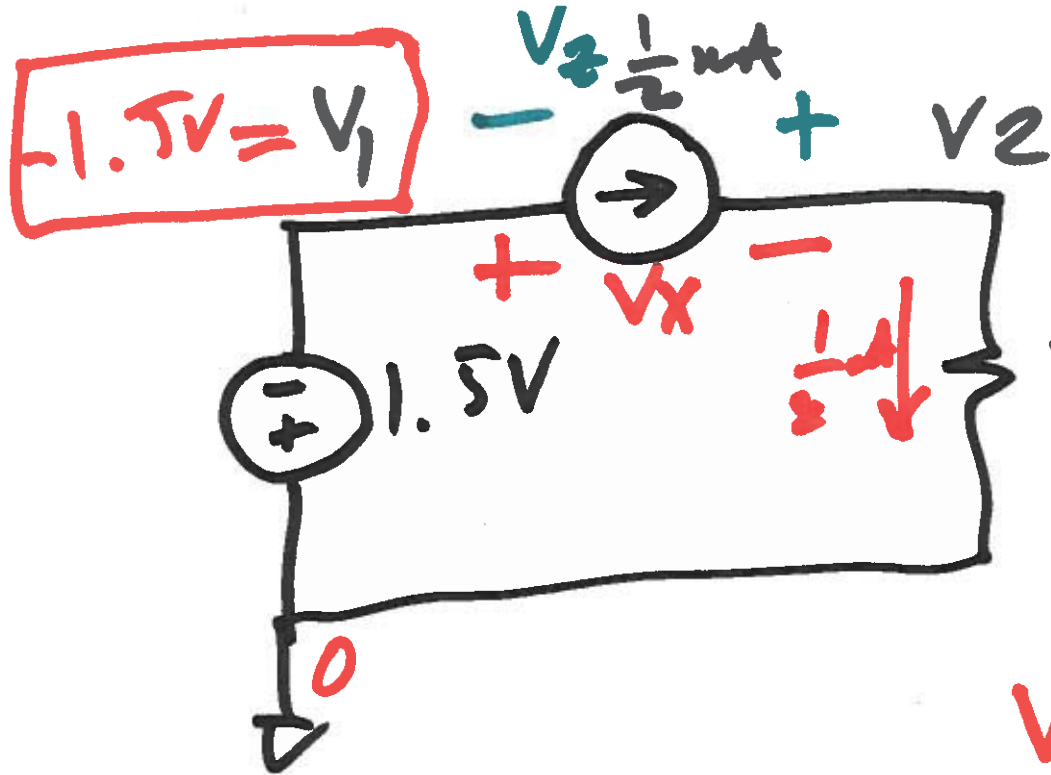

$$V_2 = \frac{1}{2} \mu A \cdot 5k = 2.5V$$


$$V_x = -1.5 - 2.5 = V_1 - V_2$$

$$V_x = -4.0V$$

$$V_z = V_2 - V_1 = 2.5 - (-1.5V)$$

$$V_z = 4V$$

2)

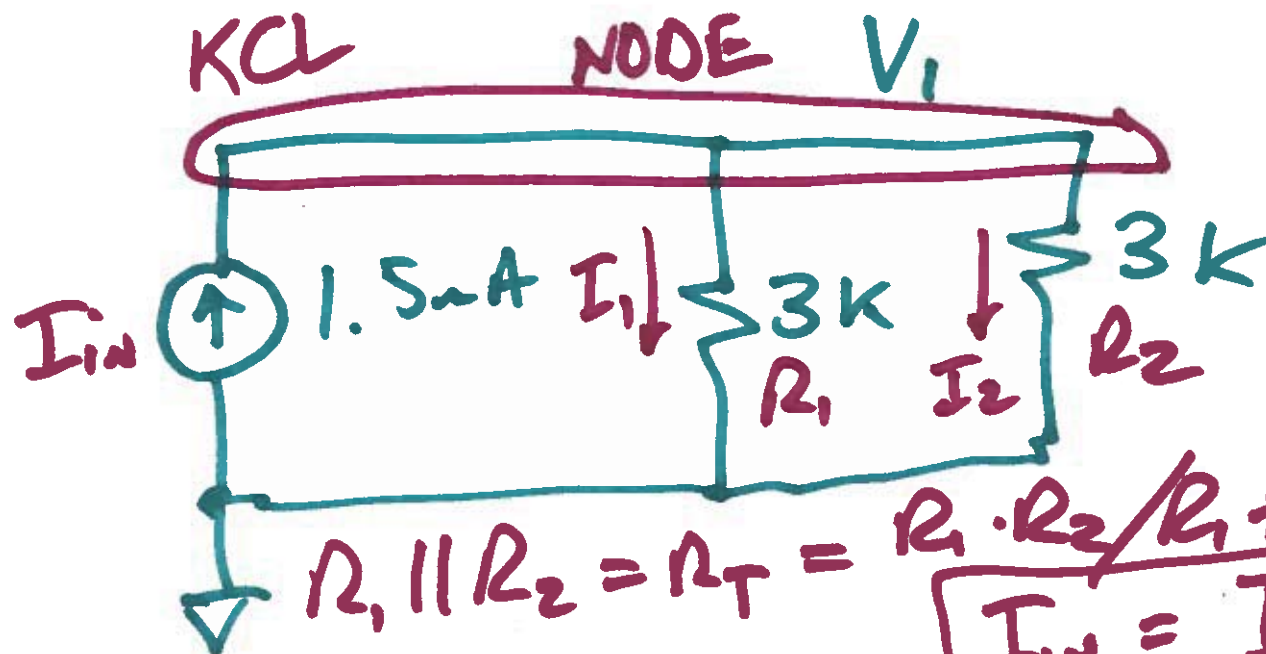

$$I_1 = \frac{V_1}{R_1}$$


$$I_2 = \frac{V_1}{R_2}$$

$$R_1 \parallel R_2 = R_T = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$I_{out} = I_1 + I_2$$
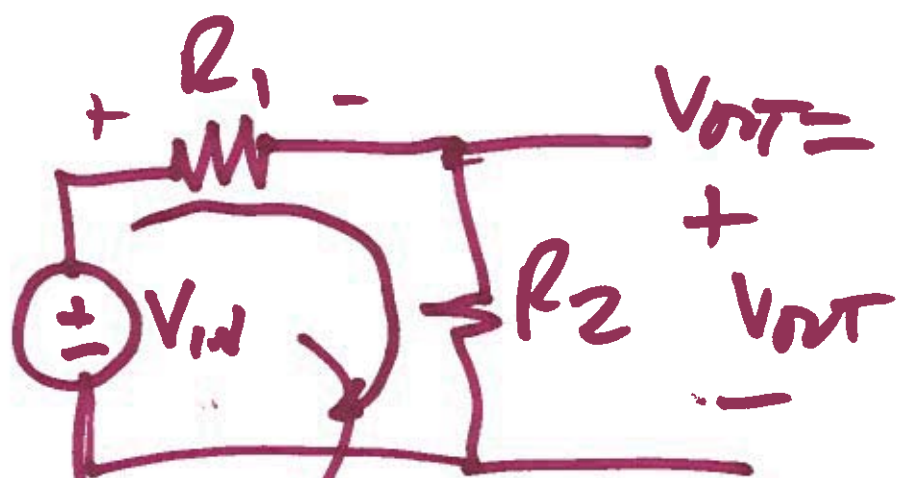
$$I_{out} = \frac{V_1}{R_1} + \frac{V_1}{R_2}$$




$$V_{out} = \frac{V_{in} \cdot R_2}{R_1 + R_2}$$

voltage divider

$$I_{out} = \frac{V_1}{R_1 \parallel R_2}$$

3)

$$V_{in} / (R_1 + R_2)$$

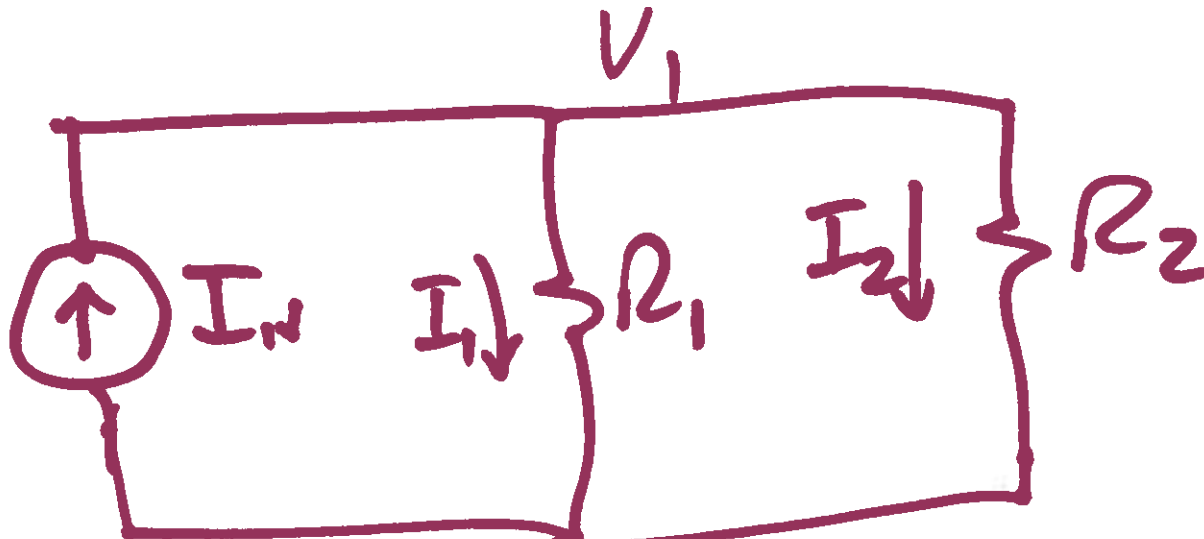

$$I_{IN} = \frac{V_1}{R_1 \parallel R_2}$$

$$= \frac{V_1}{\frac{R_1 R_2}{R_1 + R_2}}$$

$$I_2 = \frac{R_1}{R_1 + R_2} \cdot I_{IN}$$

$$I_1 = \frac{V_1}{R_1}$$

$$I_1 = \frac{R_2}{R_1 + R_2} \cdot I_{IN}$$


$$V_1 = I_{IN} \cdot \frac{R_1 R_2}{R_1 + R_2}$$

$$V_1 = I_{IN} \cdot \frac{R_1 R_2}{R_1 + R_2}$$

dividing equation

current

4)

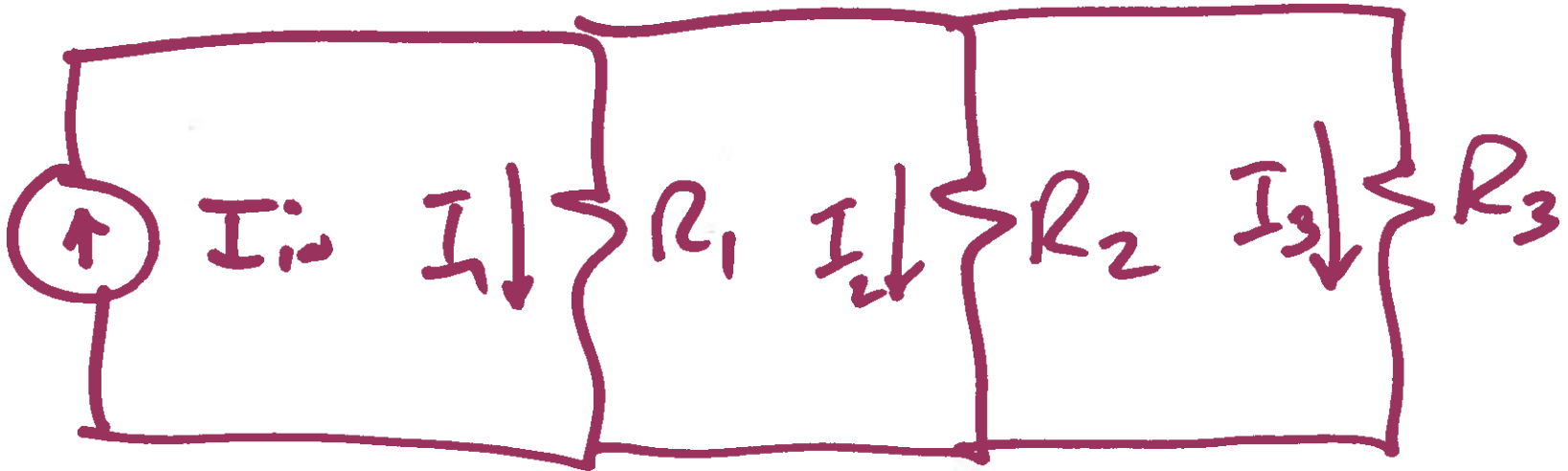


$$I_3 = I_{in} \cdot \frac{R_1 \parallel R_2}{R_1 + R_2 + R_3}$$

$$R_1 \parallel R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$\frac{A}{BC} = \frac{B \cdot (A+0)}{X}$$


$$X = \frac{BC \cdot B(A+0)}{A}$$

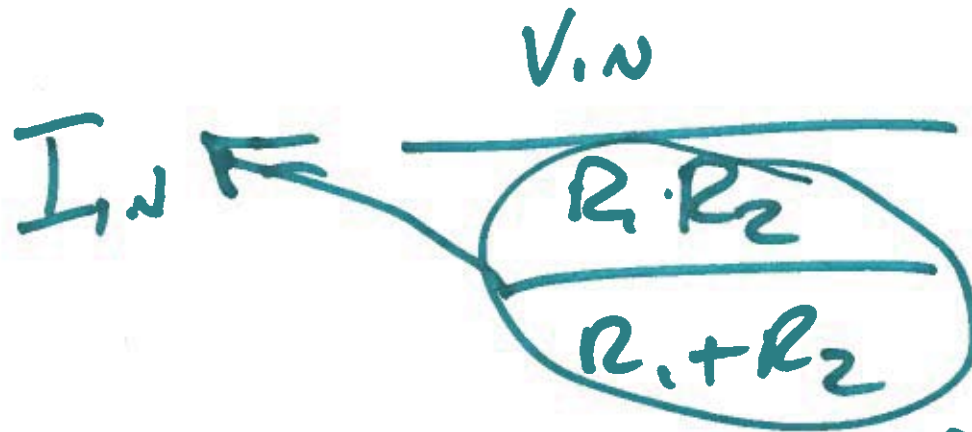

$$V_{in} = I_{in} \cdot \frac{R_1 \cdot R_2}{R_1 + R_2}$$

b)

1.5 mA


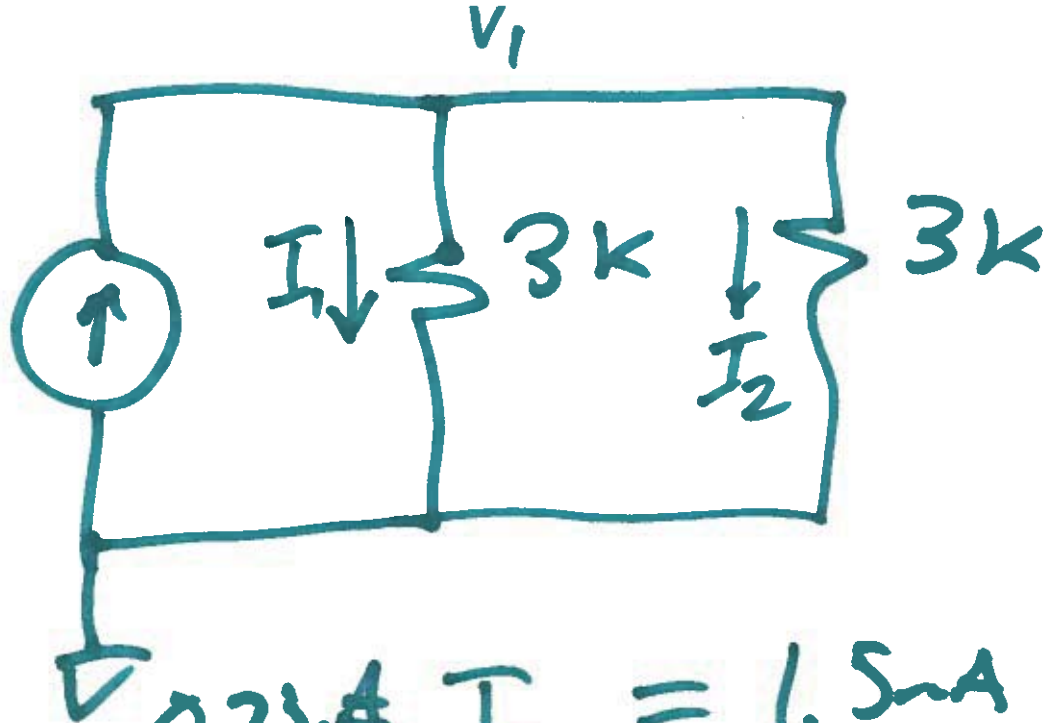


$$0.75 \text{ mA} = I_1 = 1.5 \text{ mA}$$

$$\frac{3 \text{ k}}{3 \text{ k} + 3 \text{ k}}$$


$$0.75 \text{ mA} = I_2 = 1.5 \text{ mA} \cdot \frac{3 \text{ k}}{3 \text{ k} + 3 \text{ k}}$$

7)

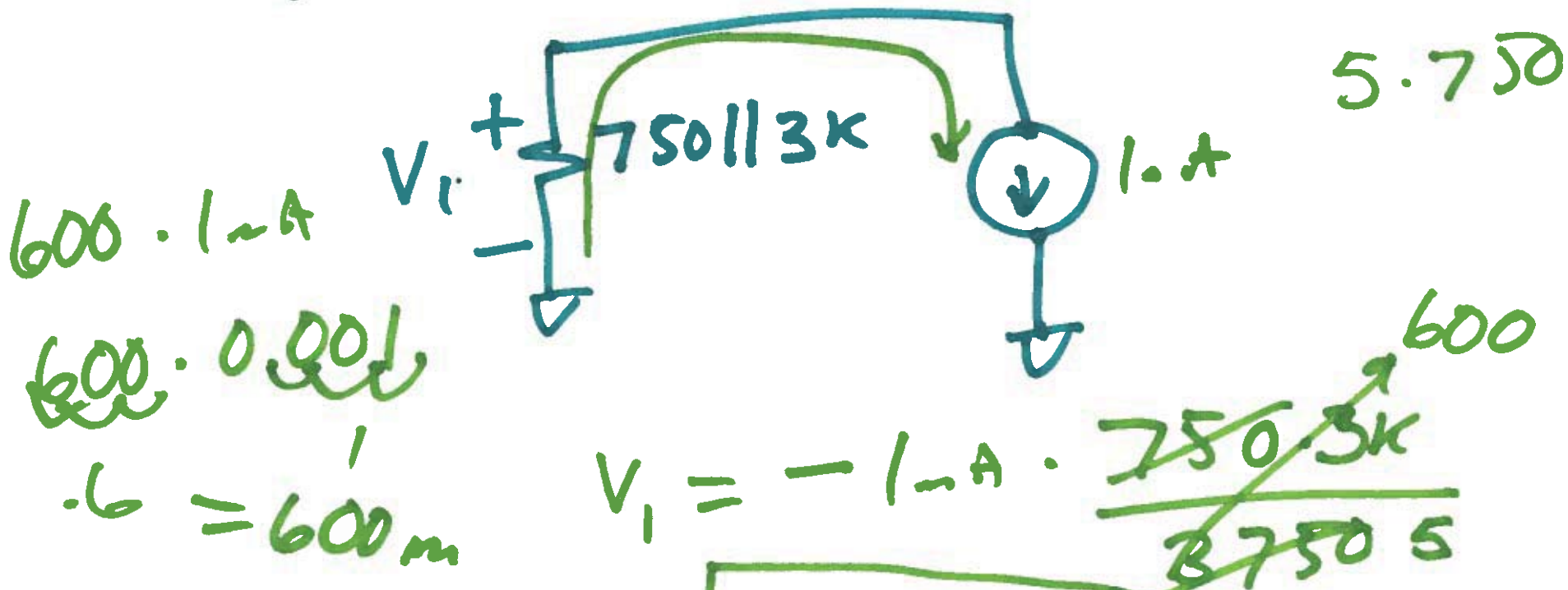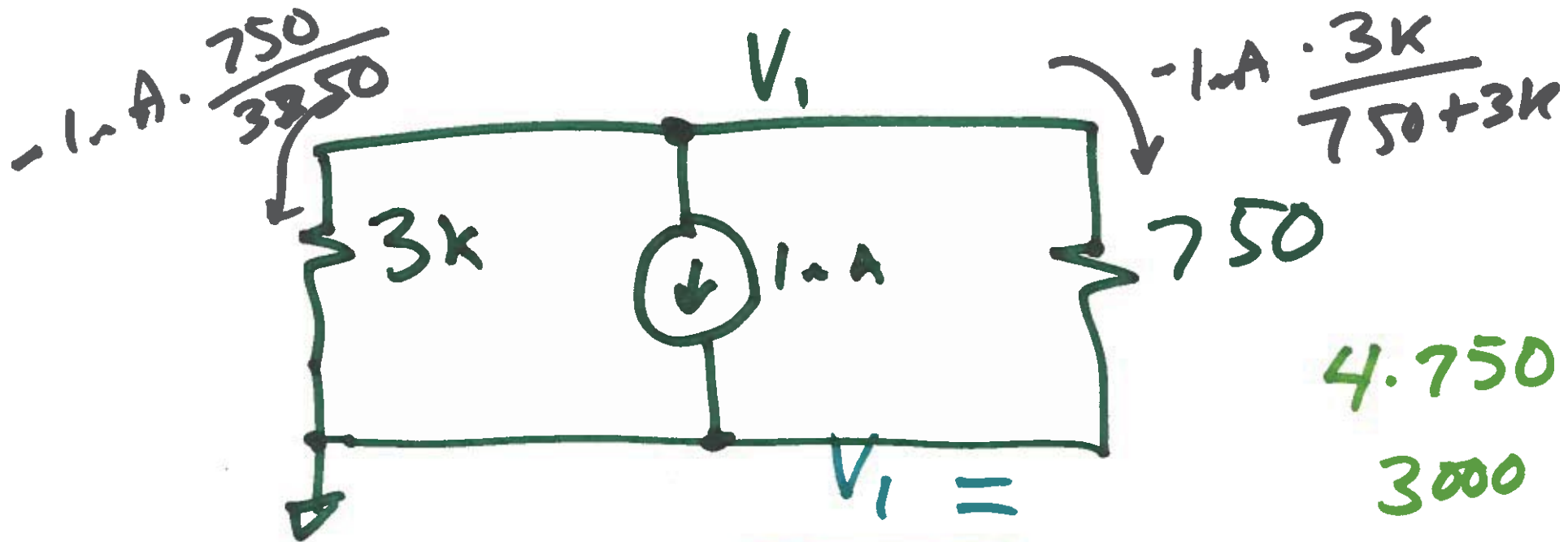


$$V_1 = -600\mu\text{V}$$



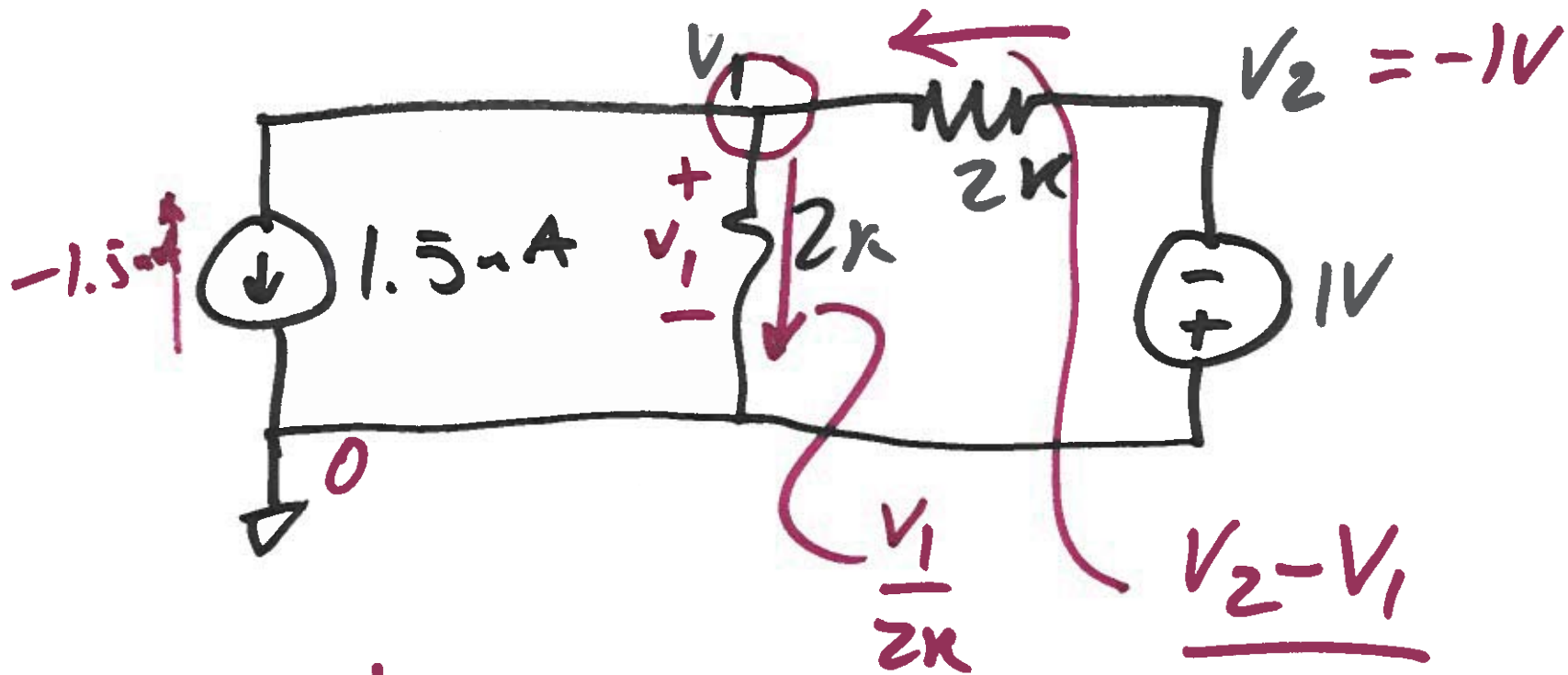

$$\frac{-1}{2k} = \frac{V_1}{2k} + \frac{V_2 - V_1}{2k} + 1.5 \text{ mA}$$

9)

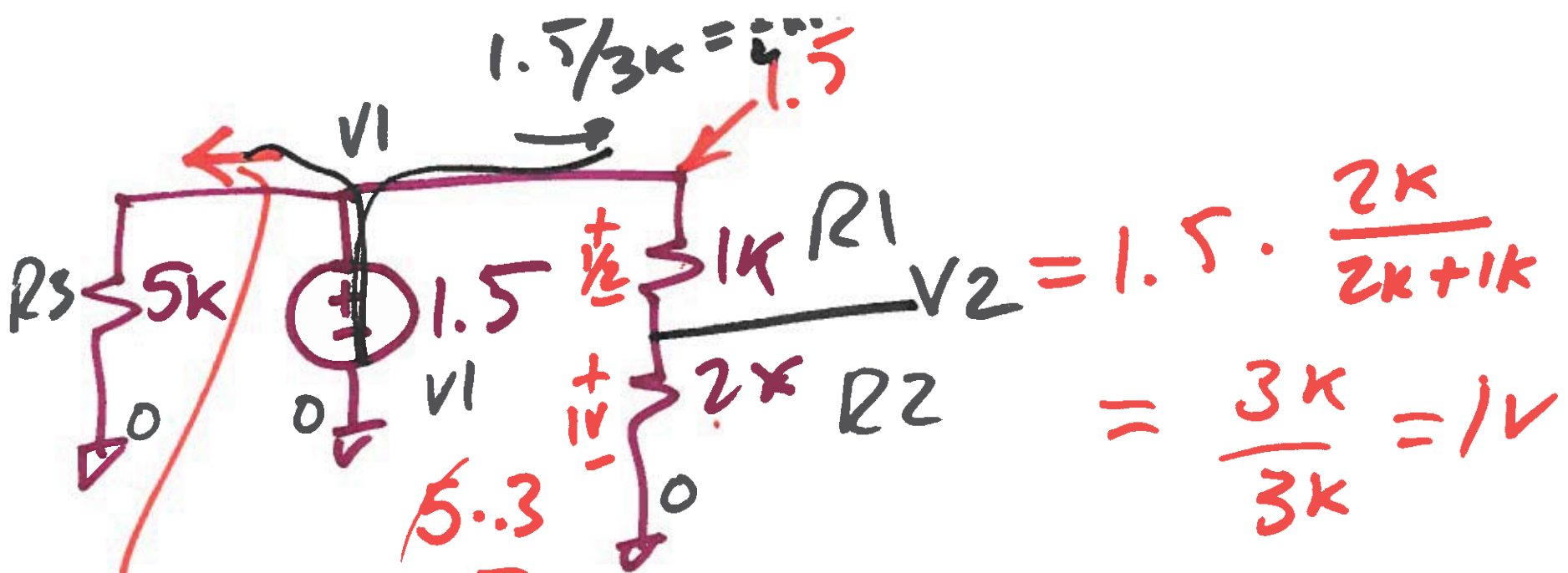


$V_1 = \frac{1.5V}{5k}$
 $= 0.3mA$

MY netlist

V1	V1	0	DC	1.5V
R3	V1	0	5k	
R1	V1	V2	1k	
R2	V2	0	2k	

end

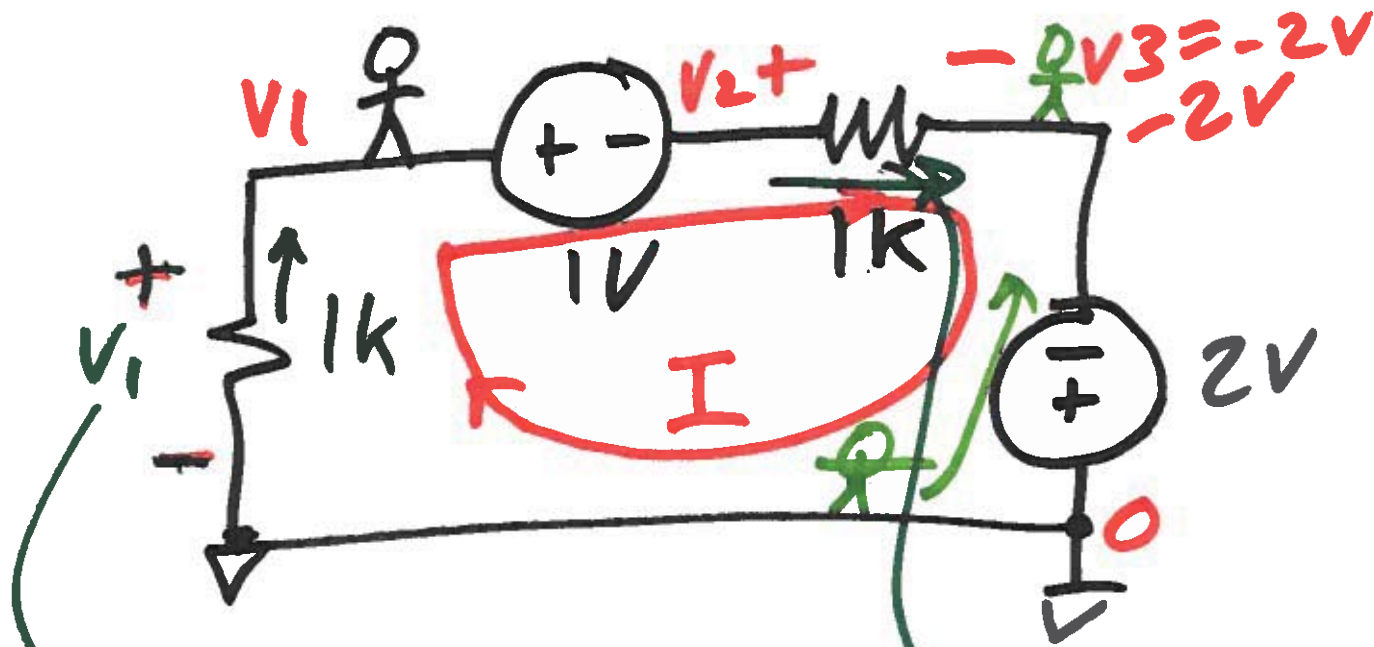

$$-I \cdot 1k = V_1$$

$$I \cdot 1k = V_2 - (-2)$$

$$V_2 + 2$$

$$-2 + I \cdot 1k + 1V - (-I \cdot 1k) = 0$$

$$-V_1$$

ii)