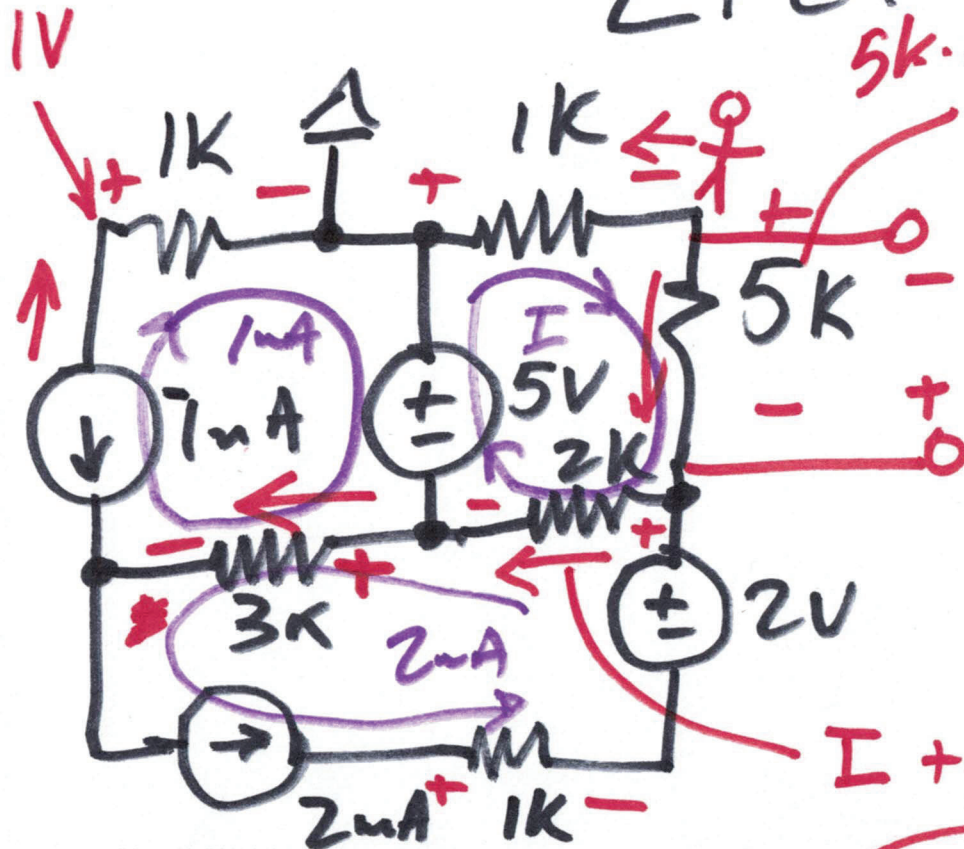


EE 220 Circuits 2

Sept. 28, 2020

Lecture $= \frac{10}{5k \cdot 125\mu A} = 1.625V$




- 1) label currents
- 2) Label + and -
- 3) go running (KVL)

$$1k \cdot I - 5 + 2k(I + 2mA) + 5k \cdot I = 0$$

$$I + 2mA \quad I(8k) = 1$$

$$I = 125\mu A$$


1)

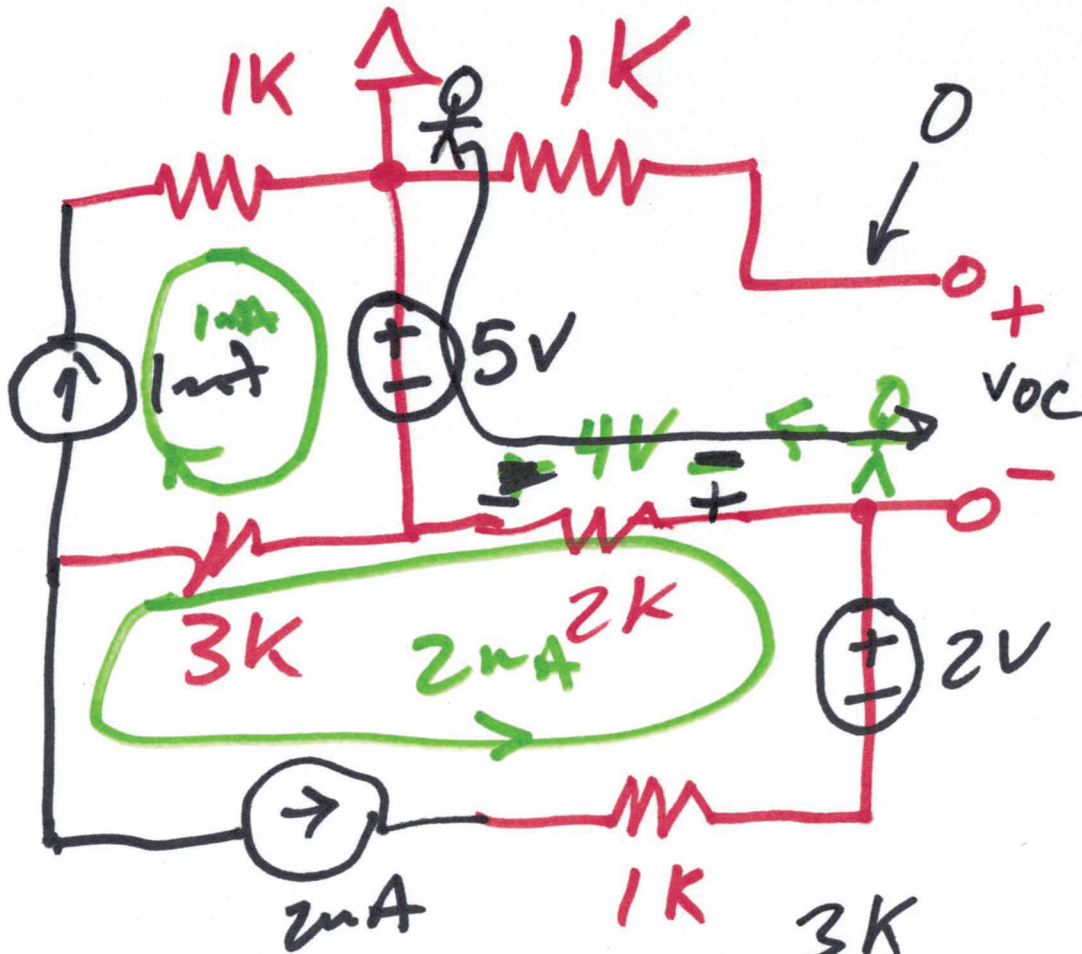

$$R_{TH} = 3k$$

$$V_{OC} = -5 + 4$$

$$V_{TH} = -1 = V_{OC}$$

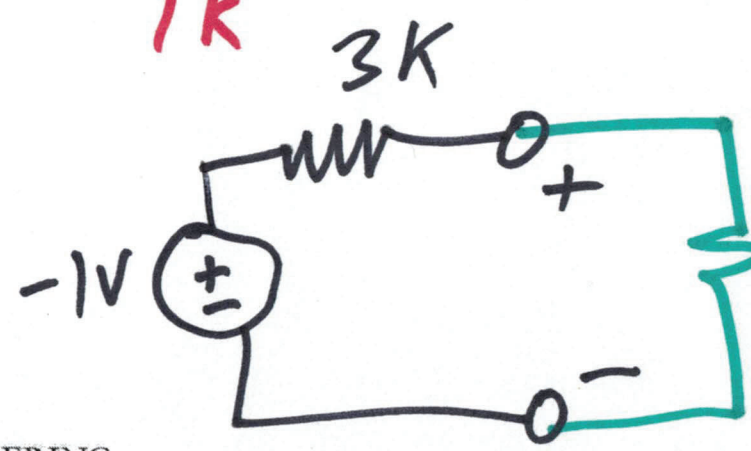


$$= -1 \frac{5}{3+5}$$

$$= -\frac{5}{8}$$

$$= -.625V$$

2)

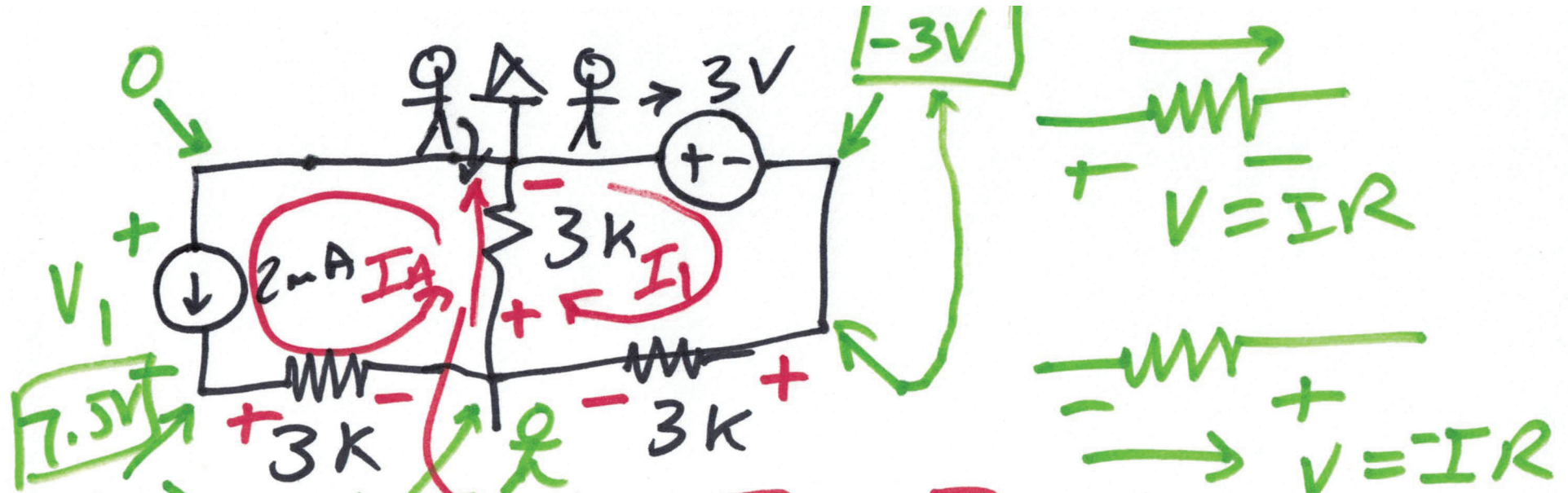

$I_3 = I_A + I_1$
 $I_A = 2\text{mA}$

$$-3 - 3kI_1 - 3kI_A - 3kI_1 = 0$$

$$3kI_A + 3kI_1 + 3kI_A + V_1 = 0 \quad \left[\begin{array}{l} I_1 = -1.5\text{mA} \\ I_1 = -9\text{mA} \end{array} \right]$$



$$-3 - 6kI_1 - 6V = 0, \quad I_1 = \frac{1}{6}\text{mA}$$

$$6 + 6 + 3kI_1 + V_1 = 0$$

$$12 + (-4.5V) + V_1 = 0$$

$$V_1 = -7.5V$$

3)

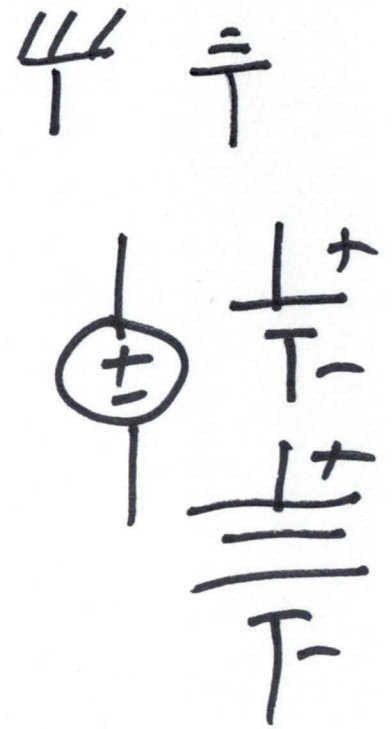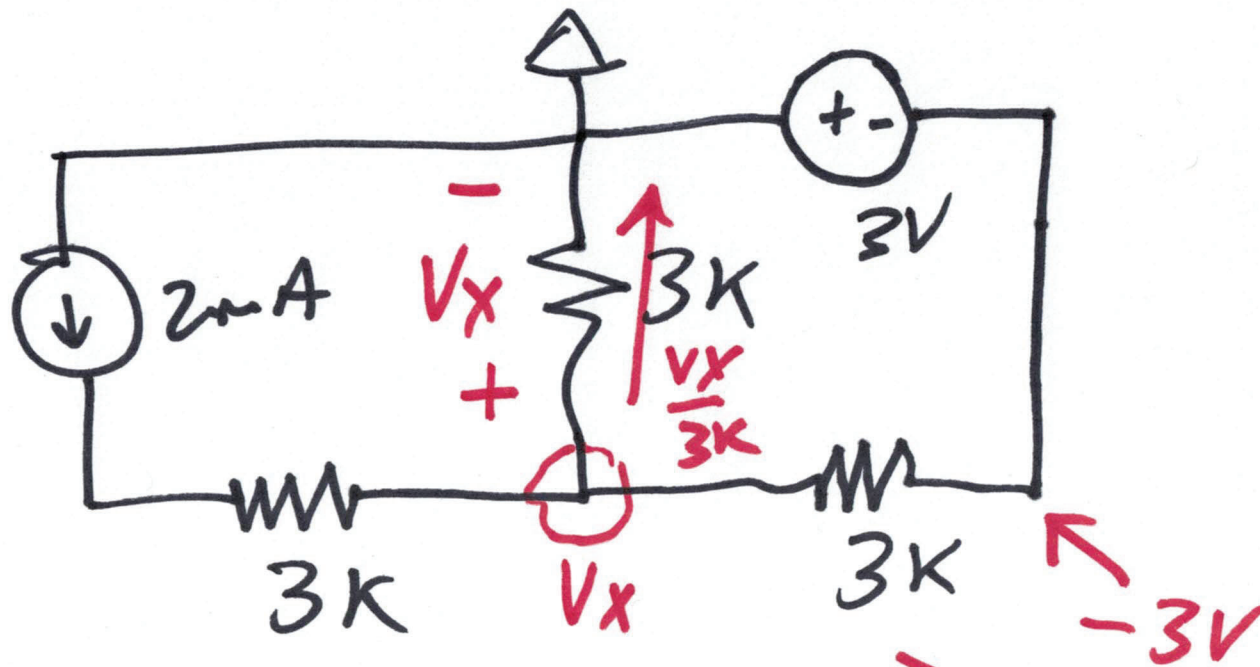


$$\frac{V_x - (-3)}{3k}$$

$$2mA = \frac{V_x}{3k} + \frac{V_x + 3}{3k}$$

$$\boxed{V_x = 1.5V}$$

$$6 = 2V_x + 3$$

4)

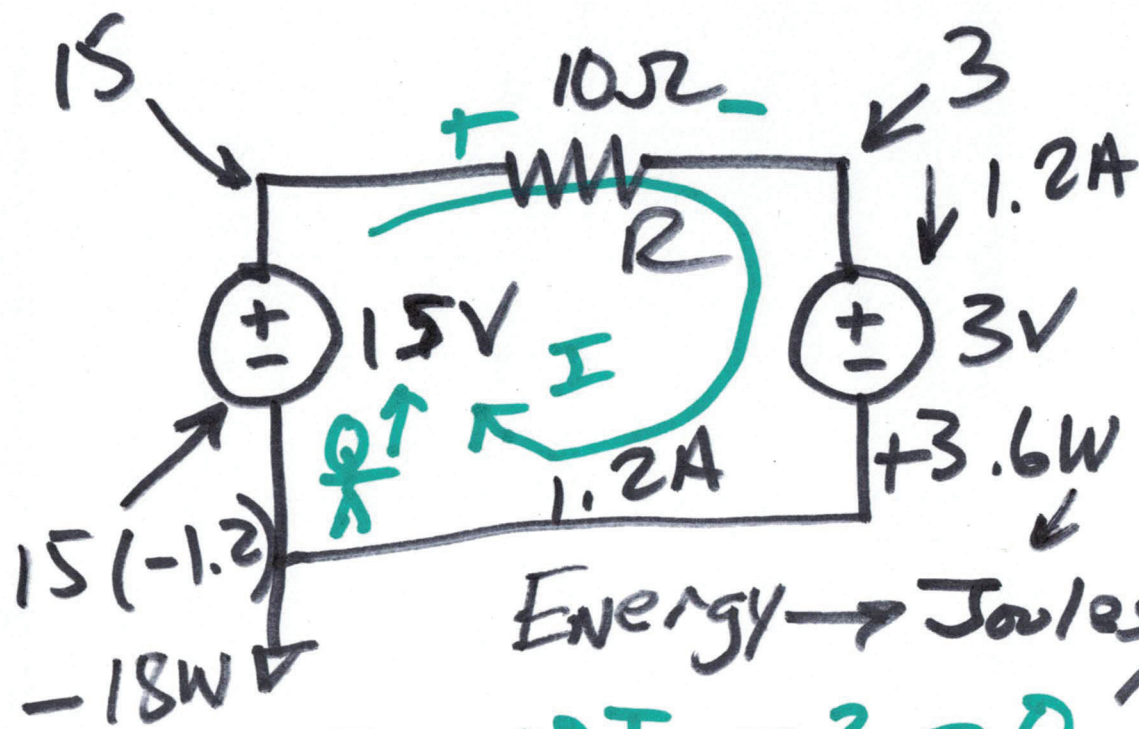

Det. power dis. By R




$$P = V \cdot I$$

$$= \frac{V^2}{R} = I^2 R$$


$$P = \frac{12^2}{10} = 14.4W$$

$$+15 - 10I - 3 = 0$$

$$I = 1.2A$$

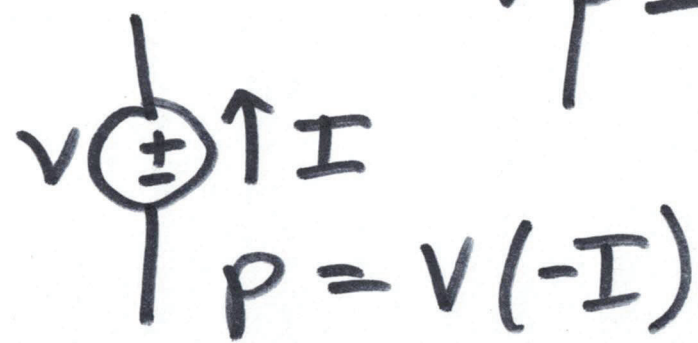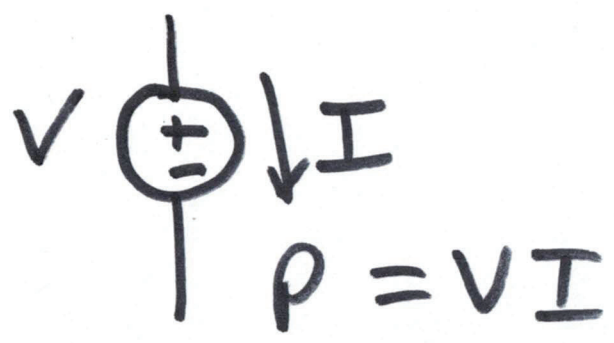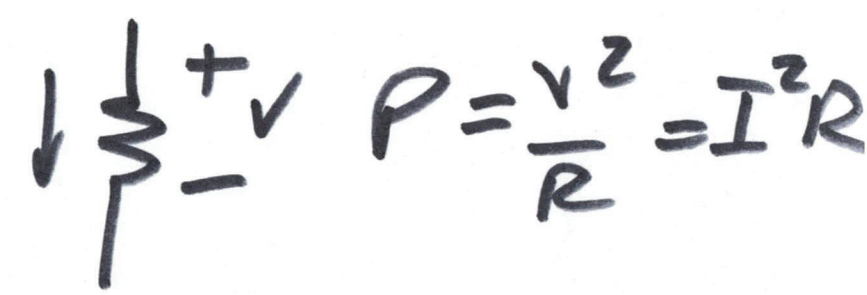

5)

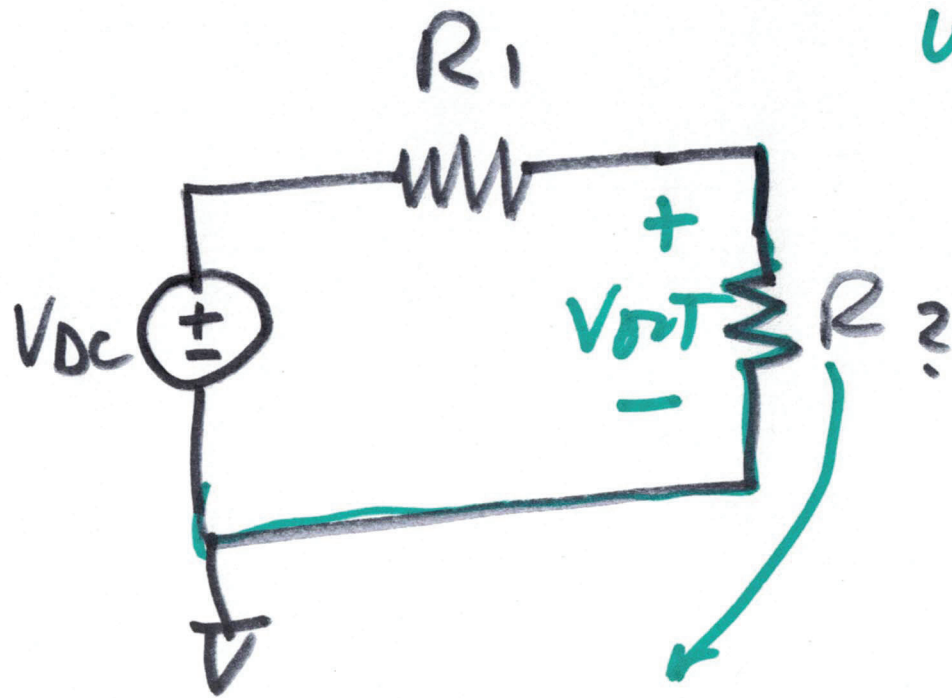

What \$R\$ results
in MAX power
dis. in \$R\$

$$P = \frac{V_{OUT}^2}{R}$$

$$P = \left(\frac{V_{DC}}{R_1} \right)^2 \cdot R$$

$$V_{OUT} = \frac{R}{R + R_1} \cdot V_{DC} = R (R + R_1)^{-1} \cdot V_{DC}$$

$$P_{MAX} \rightarrow \frac{R^2 (R + R_1)^{-2} \cdot V_{DC}^2}{R} = \frac{V_{OUT}^2}{R}$$

$$\frac{dP}{dR} = 0$$

6)

$$\frac{d}{dR} R (R+R_1)^{-2} = 0$$

$$\frac{dx^{-2}}{dx} = -2x^{-3}$$

$$\cancel{(R+R_1)^{-2}} + (-2)R(R+R_1)^{-3} = 0$$

A.B
 ~~$\frac{1}{5x}$~~
 $y(D+c)$

$$1 + \frac{-2R}{R+R_1} = 0$$

$$1 \pm \frac{2R}{R+R_1}$$

$$R+R_1 = 2R \rightarrow \text{MAX POWER}$$

$$\boxed{R_1 = R}$$

7)