
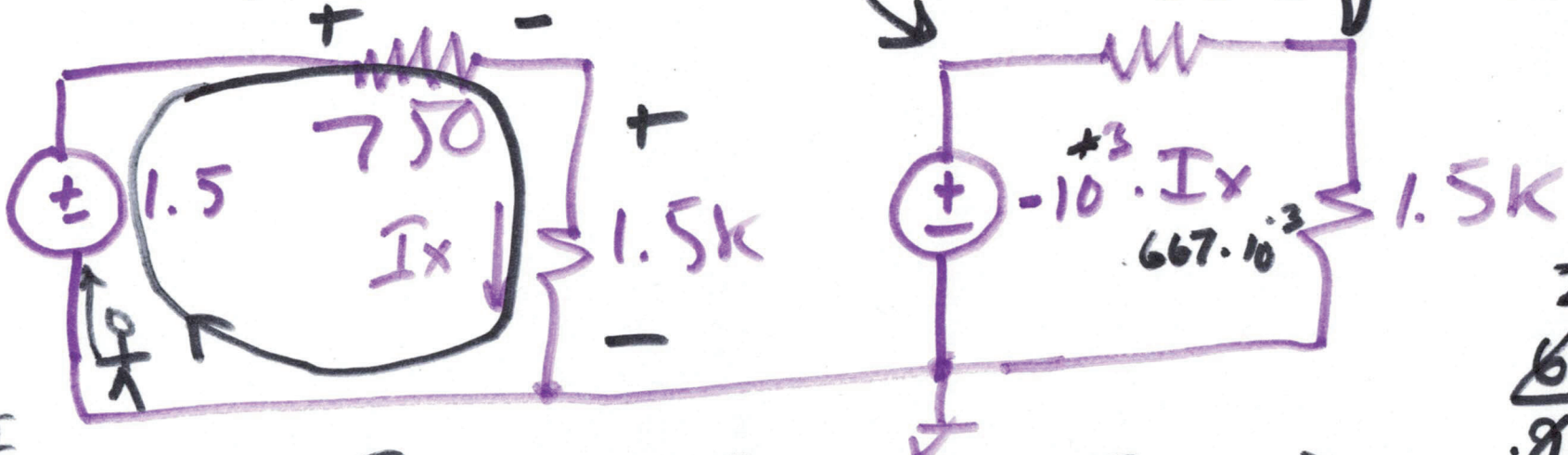



# EE 220 Circuits 1

Sept. 20, 2020

Lecture 11

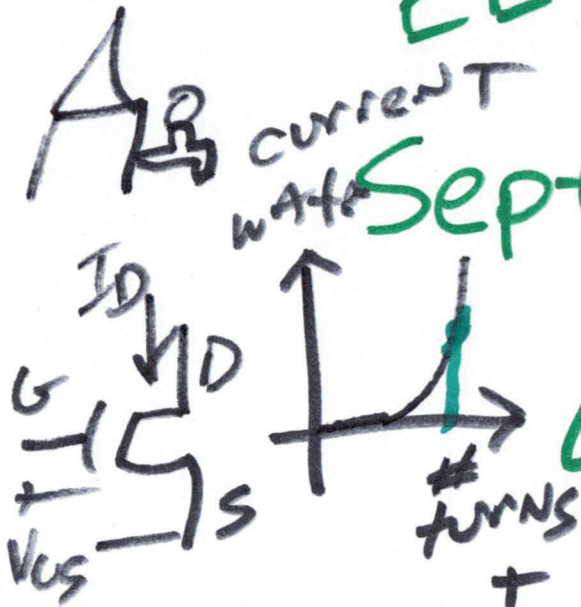



$$\frac{1.5k}{750 + 1.5k} = -0.444V$$

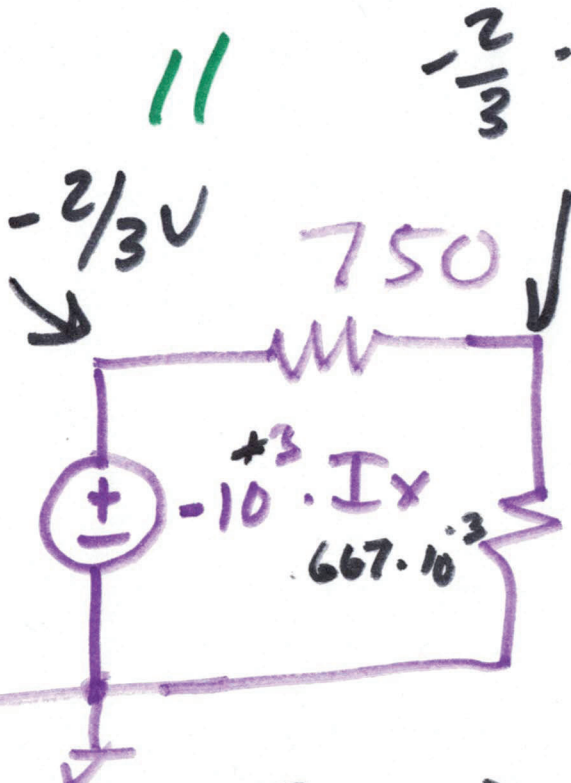

$I = \frac{V}{R}$


$$1.5 - 750 \cdot I_x - 1.5k I_x = 0$$

$$I_x = \frac{1.5}{2.25k} = 0.667mA$$

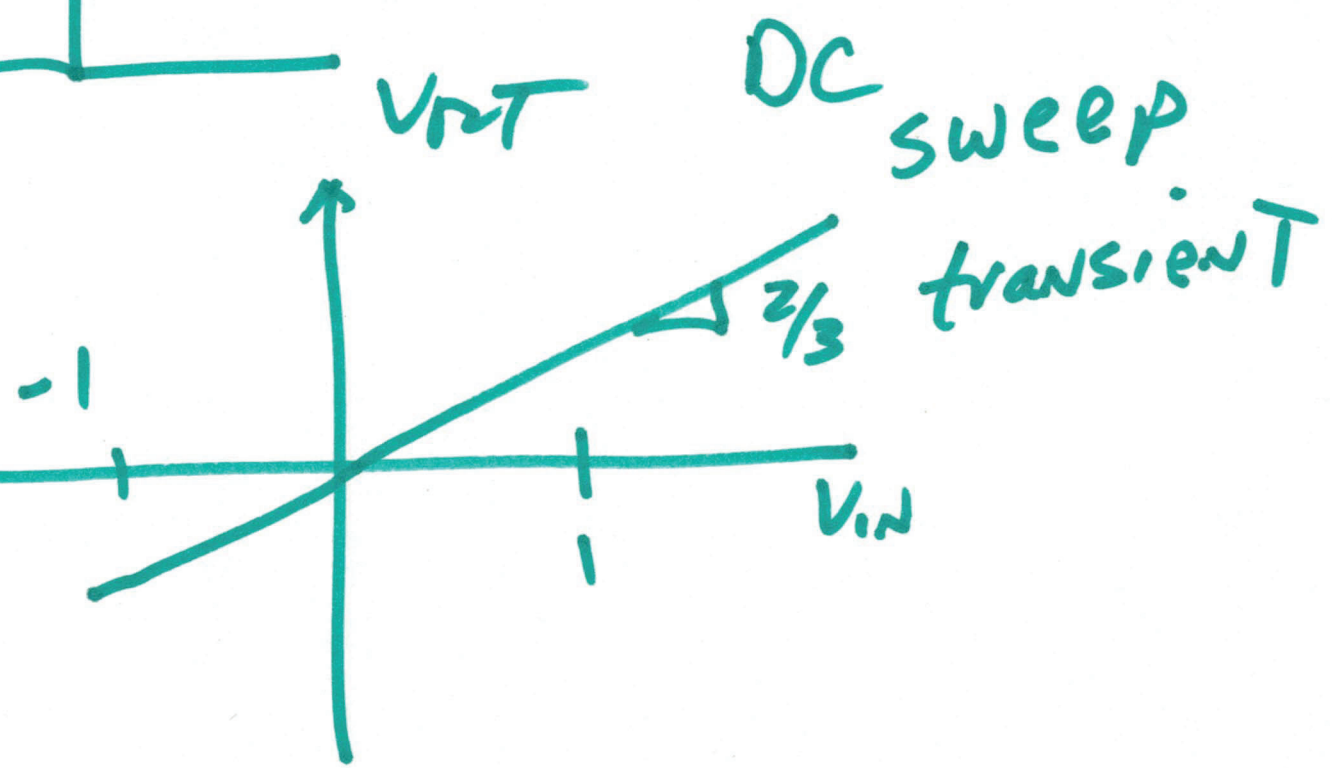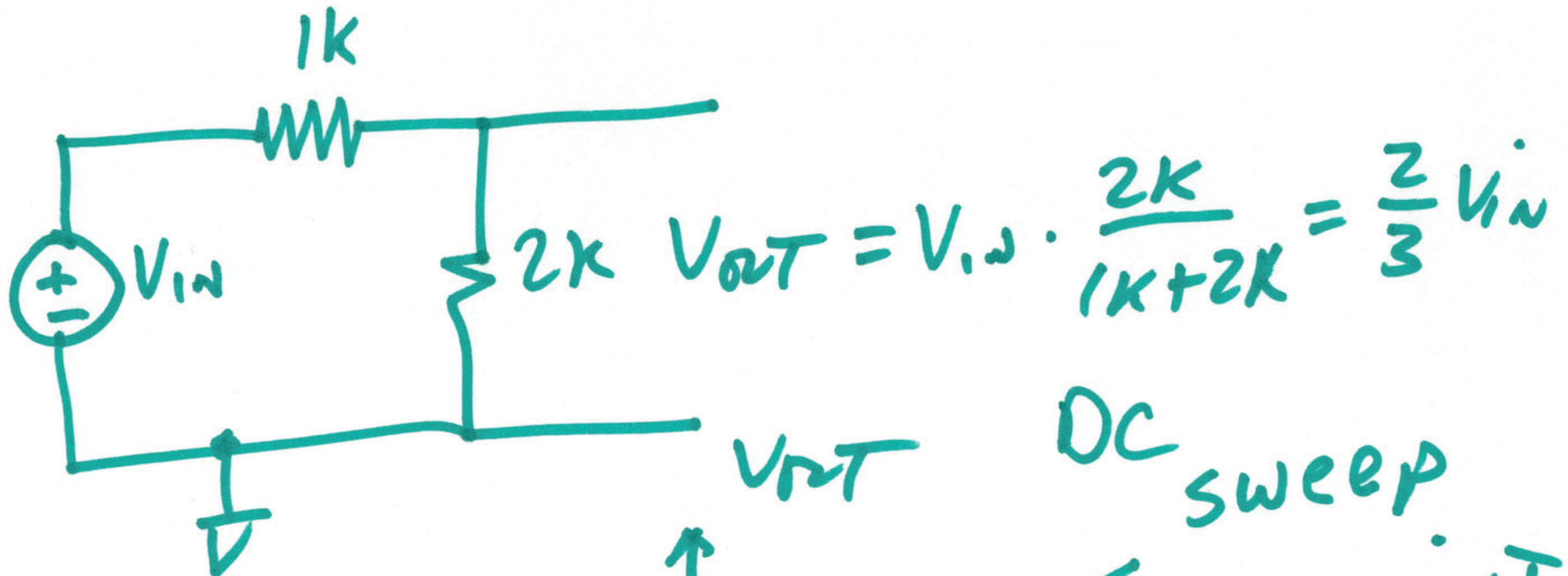

2)

# OP-AMPS


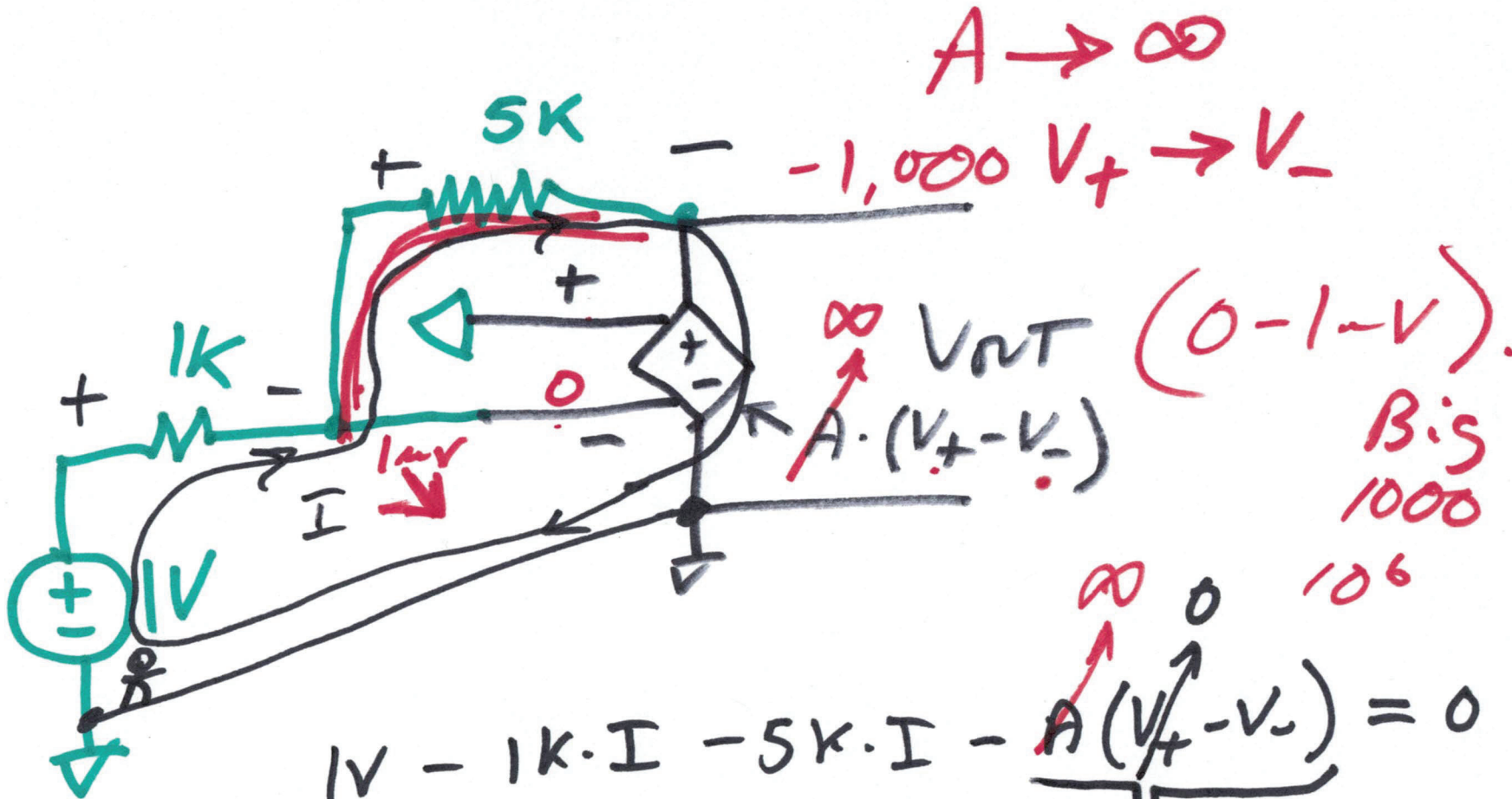


$$1V - 1K \cdot I - 5K \cdot I - \underbrace{A(V_+ - V_-)}_{V_{out}} = 0$$

$$1 - A \cdot V_{out} = I \cdot 6K$$


3)

non-inverting OP-Amp

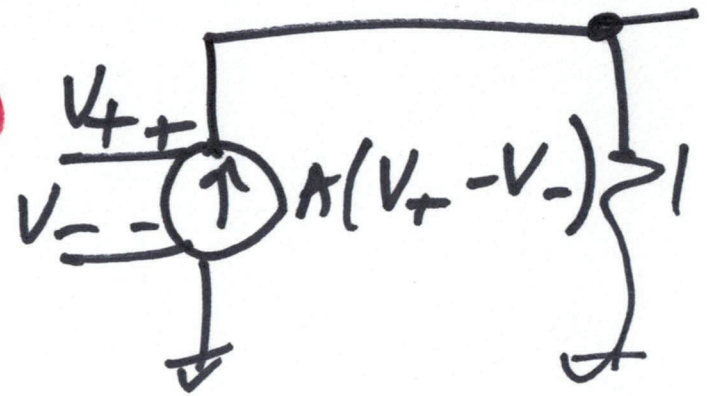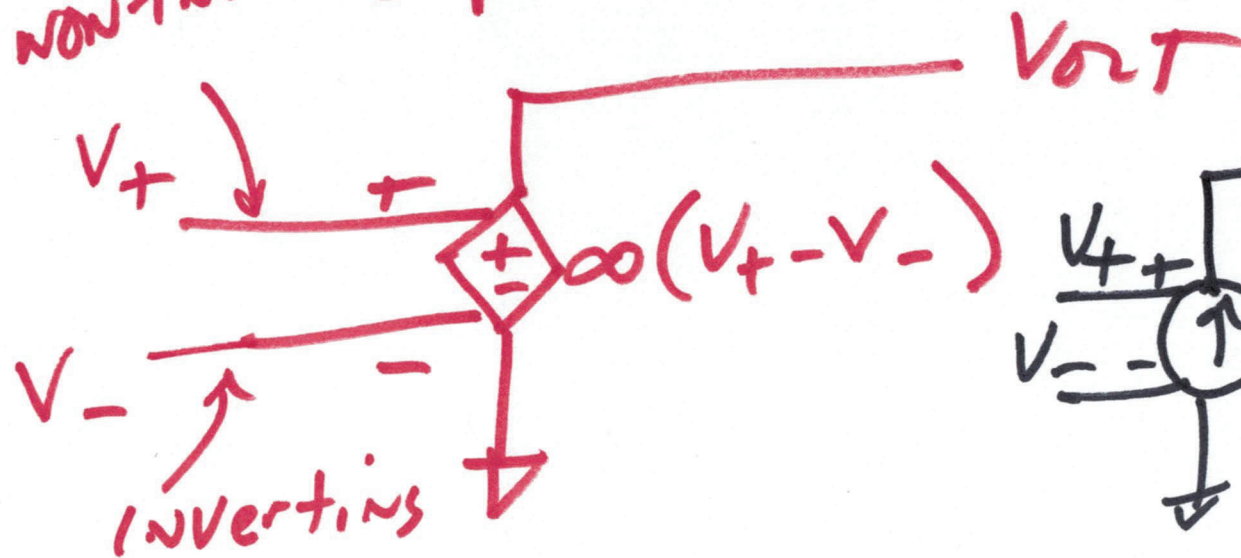

4)

# Inverting op-amp

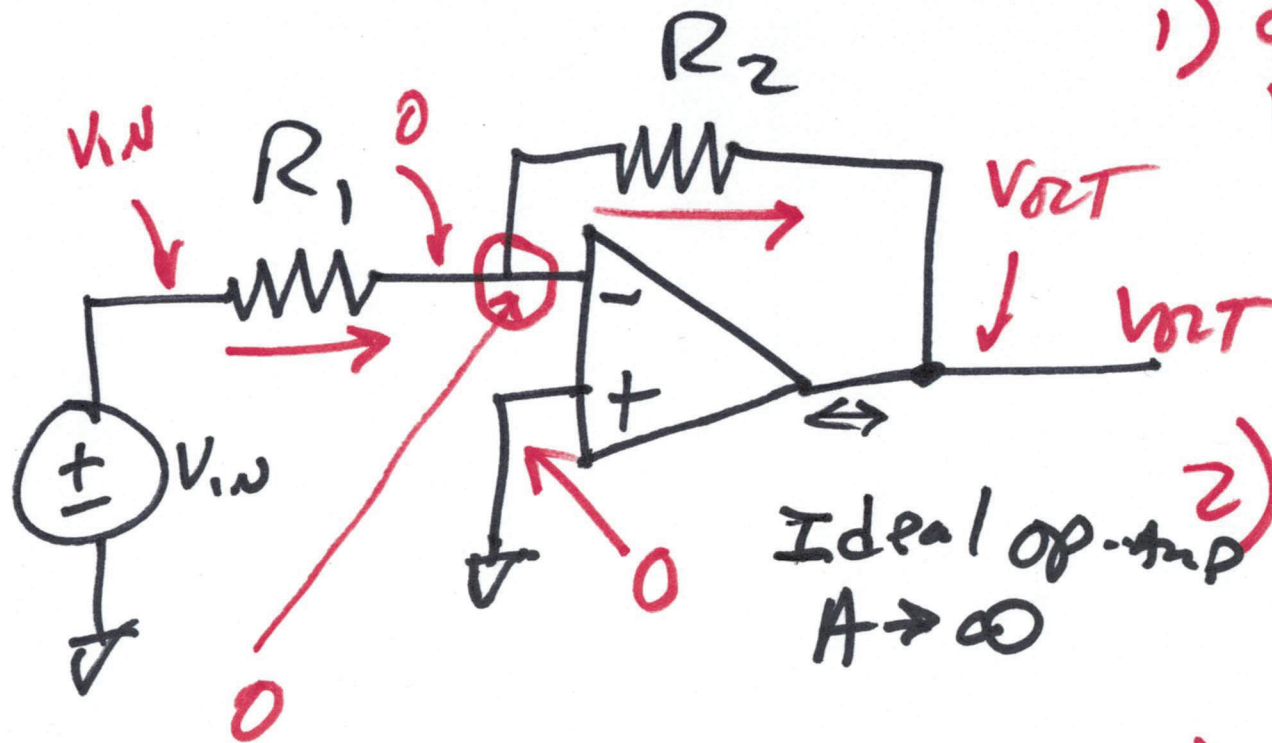


1) determine  $V_+$  (voltage on non-inverting input)

2) set  $V_-$  to  $V_+$

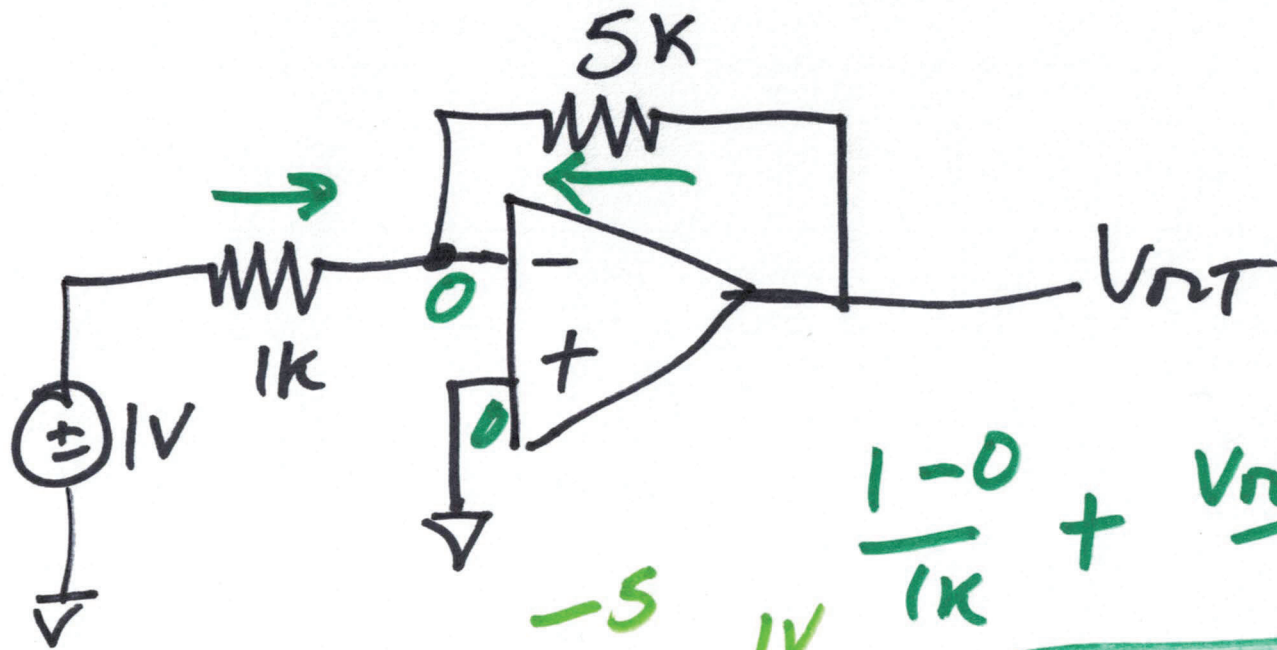3) KCL AT inverting (-) input

$$\frac{V_{IN} - 0}{R_1} = \frac{0 - V_{OUT}}{R_2}$$


$$\frac{V_{OUT}}{V_{IN}} = -\frac{R_2}{R_1}$$



$$\frac{1-0}{1k} + \frac{V_{out}-0}{5k}$$


$$V_{out} = -5V$$
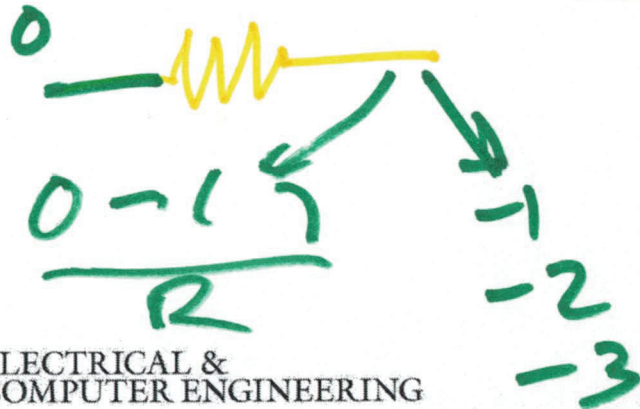
$$V_{out} = \left( -\frac{R_2}{R_1} \right) \cdot V_{in}$$



6)


# NON-INVERTING OP-AMP

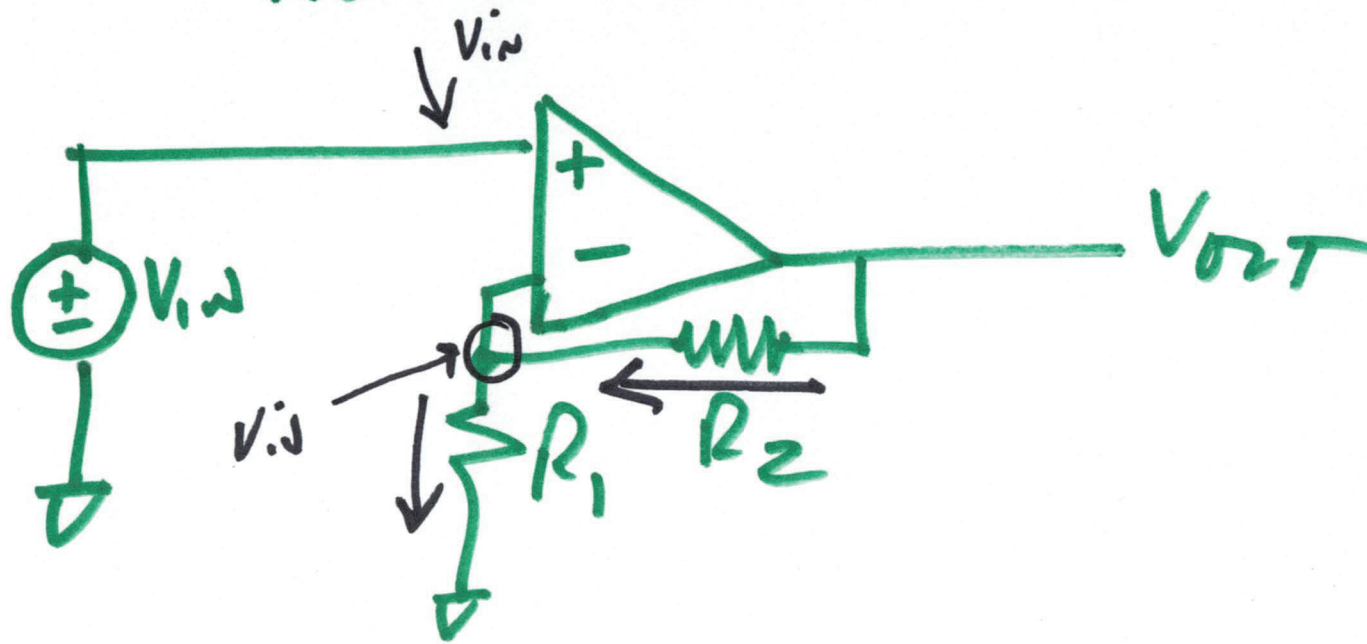

$$\frac{V_{IN}}{R_1} = \frac{V_{OUT} - V_{IN}}{R_2} \rightarrow V_{IN} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_{OUT}}{R_2}$$
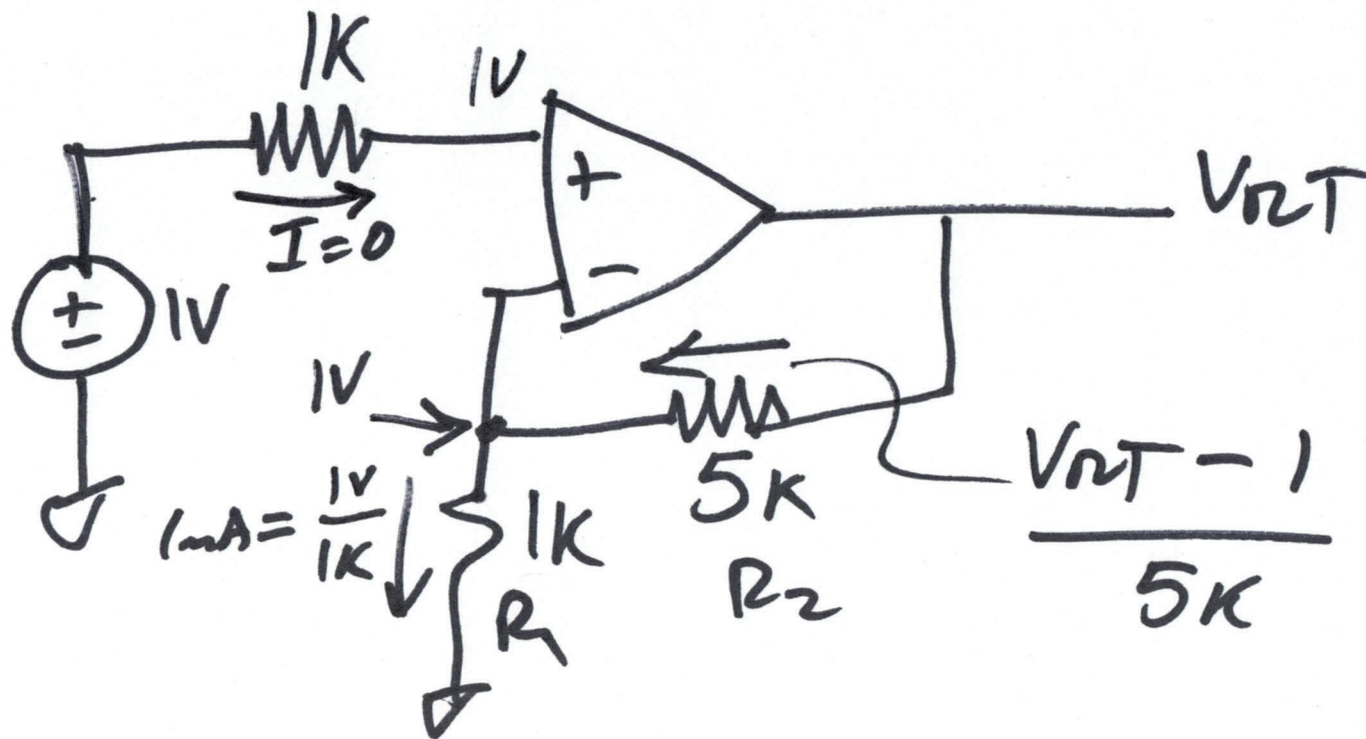
$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_2}{R_1} = \frac{R_1 + R_2}{R_1}$$





$$\frac{1}{1k} = \frac{V_{out} - 1}{5k} \rightarrow S = V_{out} - 1$$

$$1 + \frac{R_2}{R_1}$$

$$V_{out} = 6$$

8)