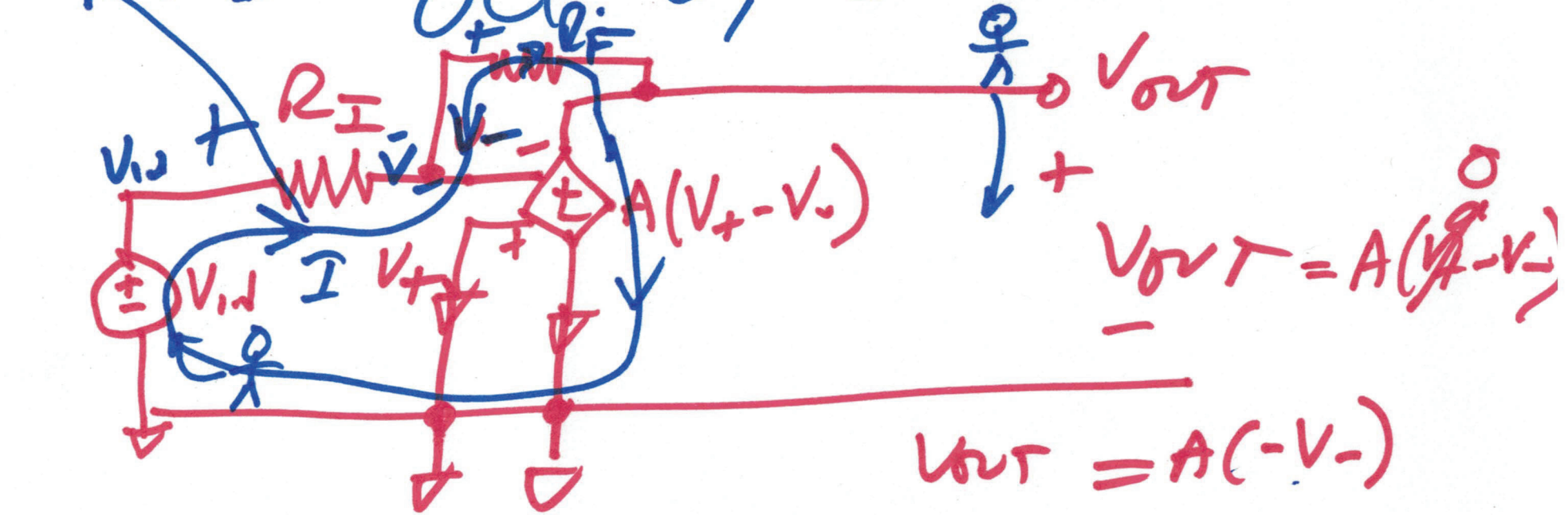


EE 220 circuits 1

Lecture 12

Oct 5, 2020



$$V_{in} - I R_I - I \cdot R_f - V_{out} = 0$$

1)

u

$$V_{IN} - IR_I - I \cdot R_F - V_{OUT} = 0$$

$$I = \frac{V_{IN} - V_-}{R_I}$$

$$V_{IN} - (V_{IN} - V_-) - \frac{R_F}{R_I}(V_{IN} - V_-) - V_{OUT} = 0$$

$$V_- = -\frac{V_{OUT}}{A}$$

$$V_{IN} - V_{IN} - \frac{V_{OUT}}{A} - \frac{R_F}{R_I} \frac{V_{IN}}{A} - \frac{R_F}{R_I} \frac{V_{OUT}}{A} - V_{OUT} = 0$$


$A \rightarrow \infty$

$$-\frac{R_F}{R_I} V_{IN} = V_{OUT}$$

$$\frac{V_{OUT}}{V_{IN}} = -\frac{R_F}{R_I}$$

CMOSedu.com

2)

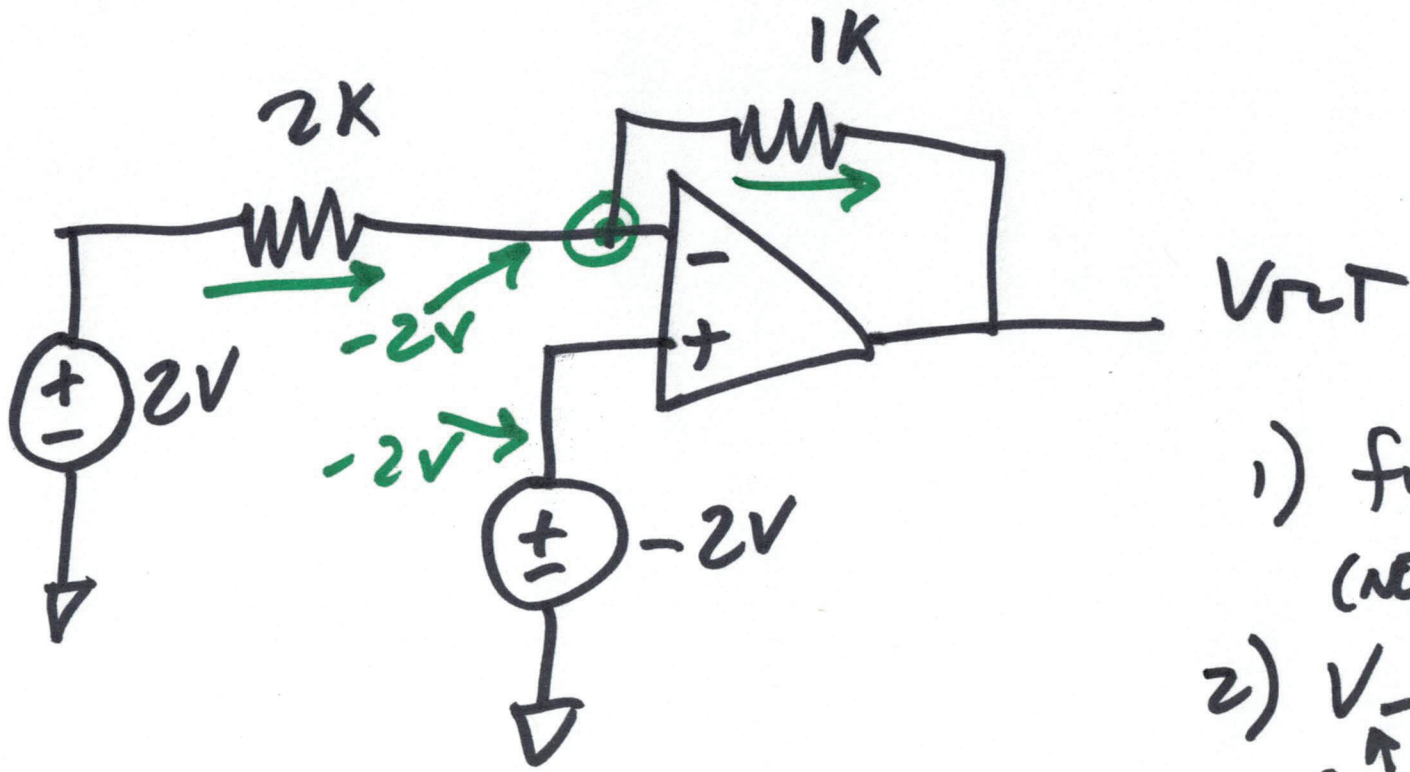

V_{out}

- 1) find V_+ (NON-INVERTING)
- 2) $V_- = V_+$ (INVERTING)
- 3) KCL @ V_-


$$\frac{2 - (-2)}{2k} = \frac{-2 - V_{out}}{1k}$$

$$4 = -4 - 2V_{out}$$

$$V_{out} = -\frac{8}{4} V$$

3)

INVERTING R_F

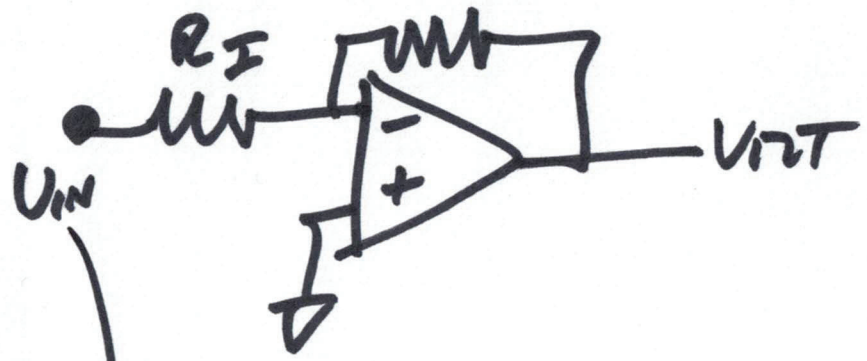


$$V_{OUT} = -V_{IN} \cdot \frac{R_F}{R_I}$$



VDD →
VCC




NON-INVERTING

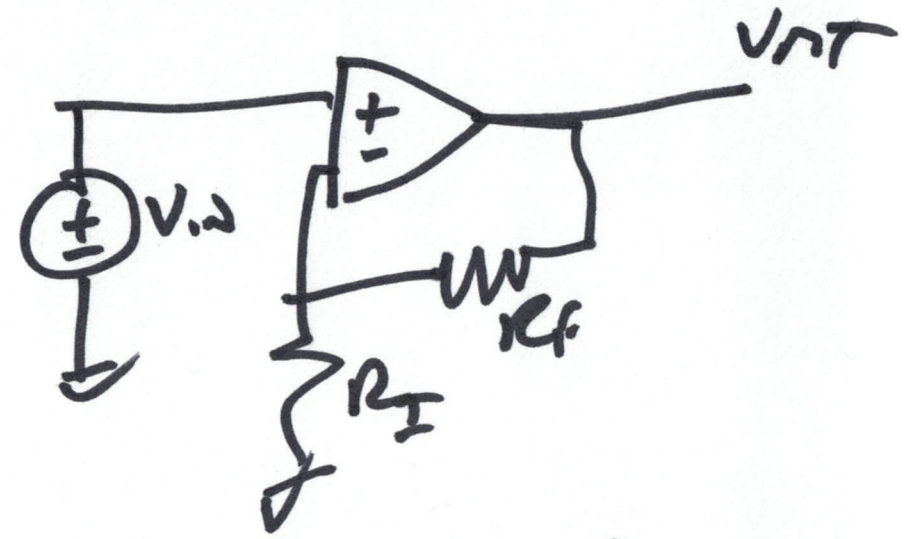

$$\frac{V_{OUT}}{V_{IN}} = \frac{R_F}{R_I} + 1$$

$$= \frac{R_F + R_I}{R_I}$$

4)

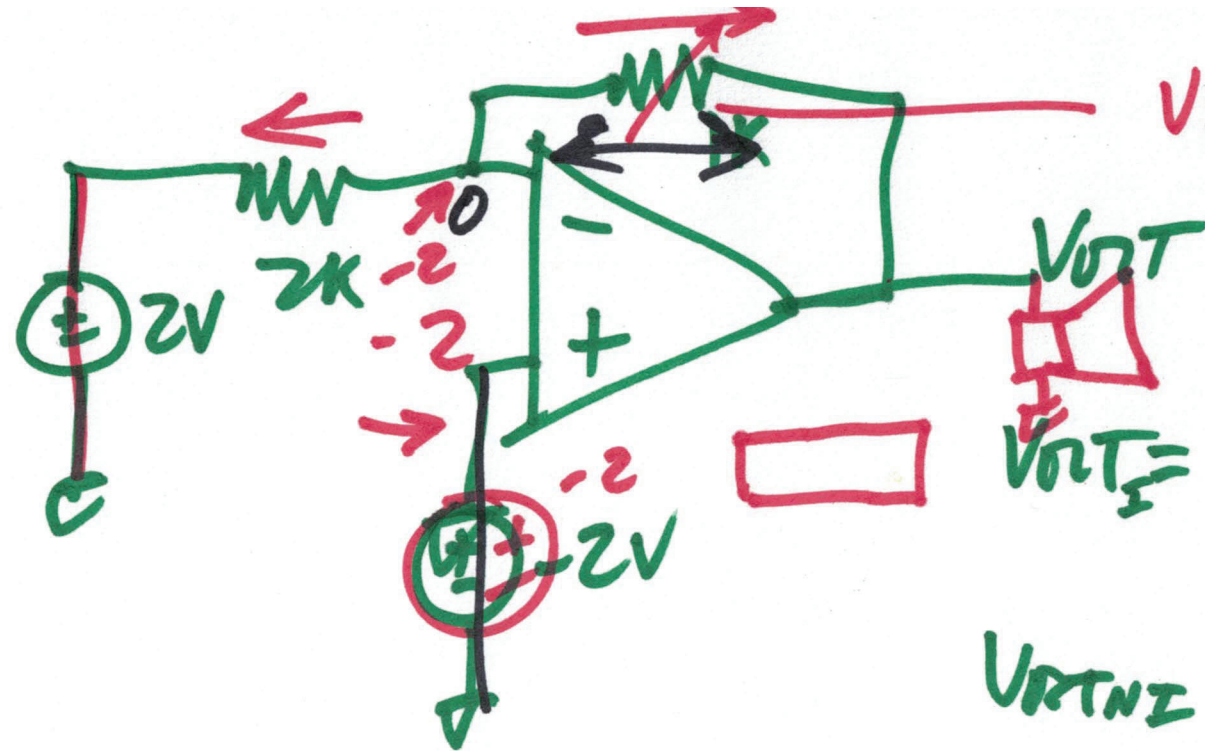

VARIABLE
RESISTOR
is called
a potentiometer

$$-2 \cdot \frac{1k}{2k} = \underline{\underline{-1V}}$$

$$V_{OUT} = -2 \cdot \left(1 + \frac{1k}{2k}\right)$$

$$= \underline{\underline{-3V}}$$


$$V_{OUT} = -1 + -3$$

$$= \underline{\underline{-4}}$$

$$\frac{2-0}{2k} = \frac{0 - V_{OUT}}{1k}$$

$$\frac{-2-0}{2k} + \frac{0 - V_{OUT}}{1k}$$

5)

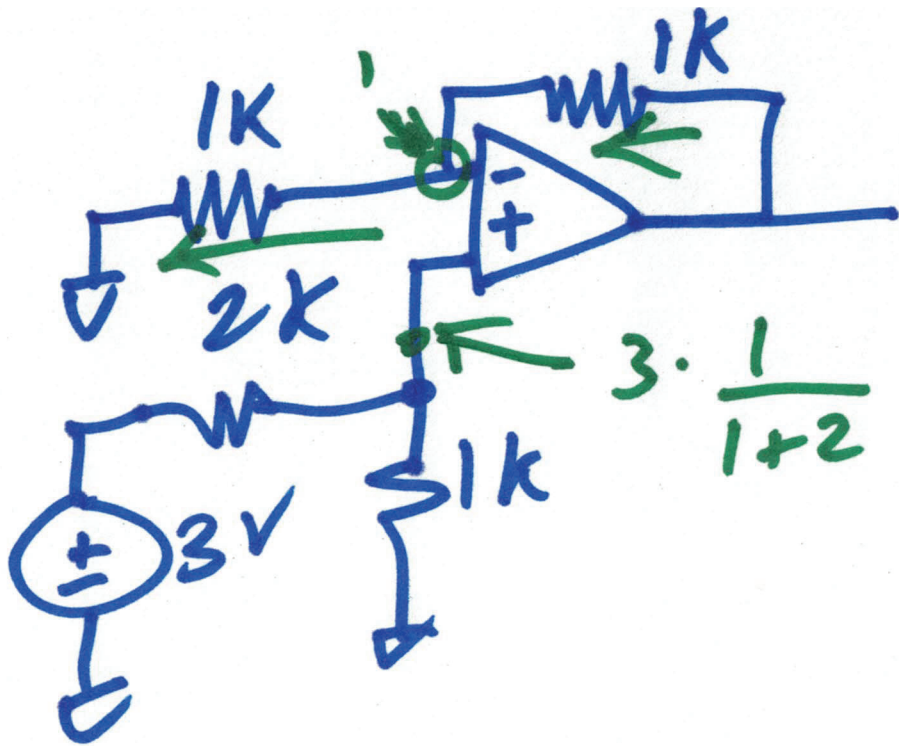

$$V_{out} \left(1 + \frac{1k}{1k}\right) = 2V$$

1) find V_+

$$3 \cdot \frac{1}{1+2} = 1V \quad 2) V_+ = V_-$$

Ideal op-amp

$$A_{OL} \rightarrow \infty$$

$$\frac{1-0}{1k} = \frac{V_{out} - 1}{1k}$$

$$V_{out} = 2V$$

b)


-64 (micro)
 -3 milli
 3 k
 6 MEB
 9 Giga

NAME: _____


Closed book and notes.


Show your work for credit and put a box around your answers.

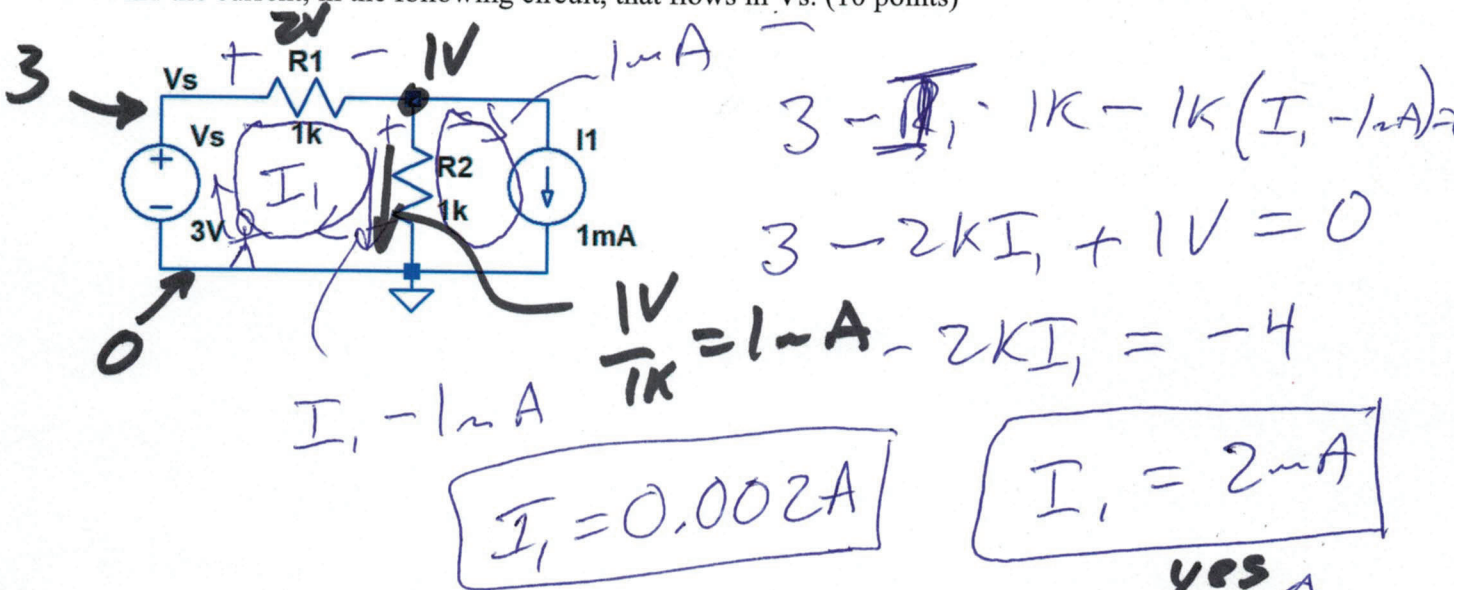1. Find the current, in the following circuit, that flows in V_s . (10 points)



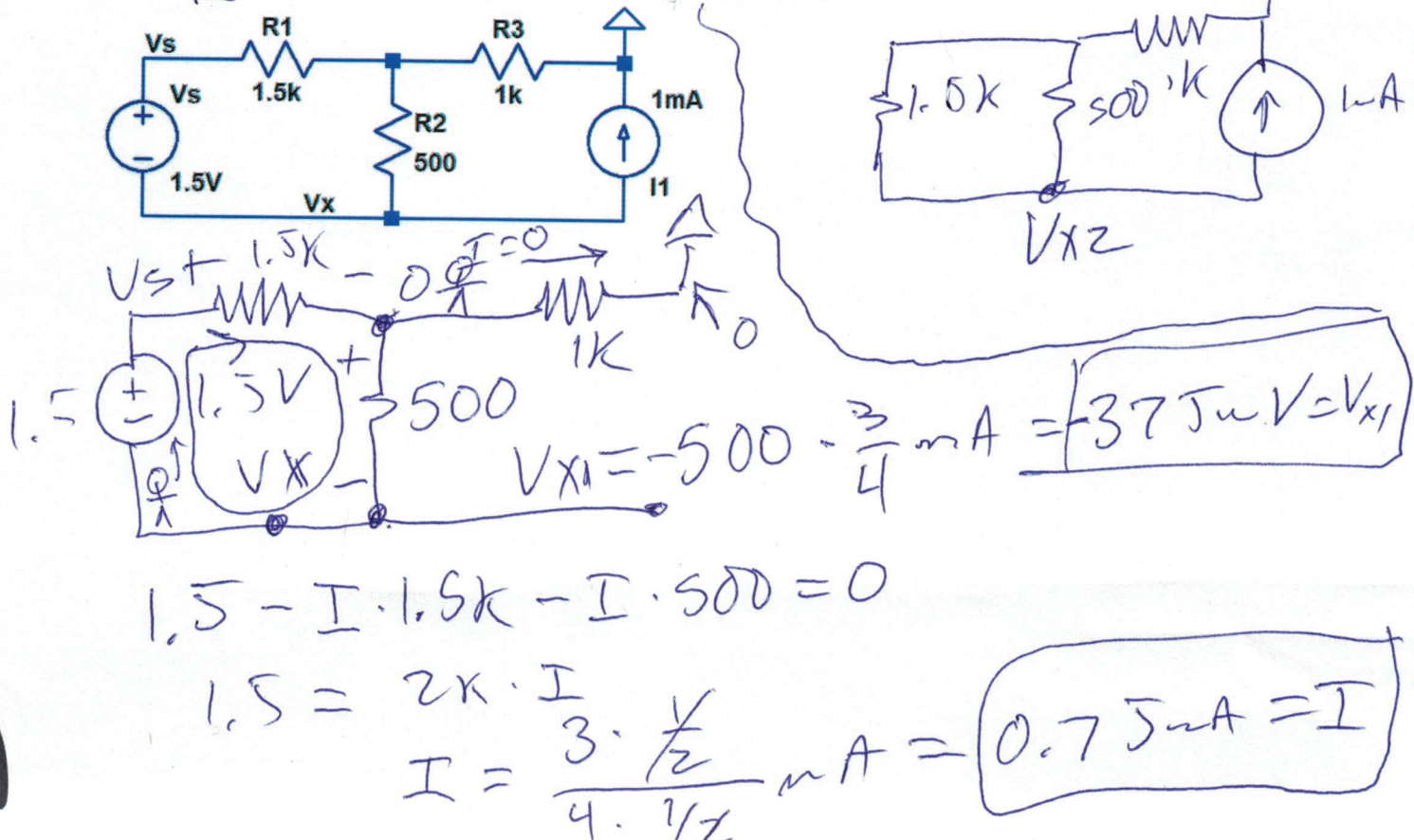2. Find V_x in the following circuit using superposition. (10 points)



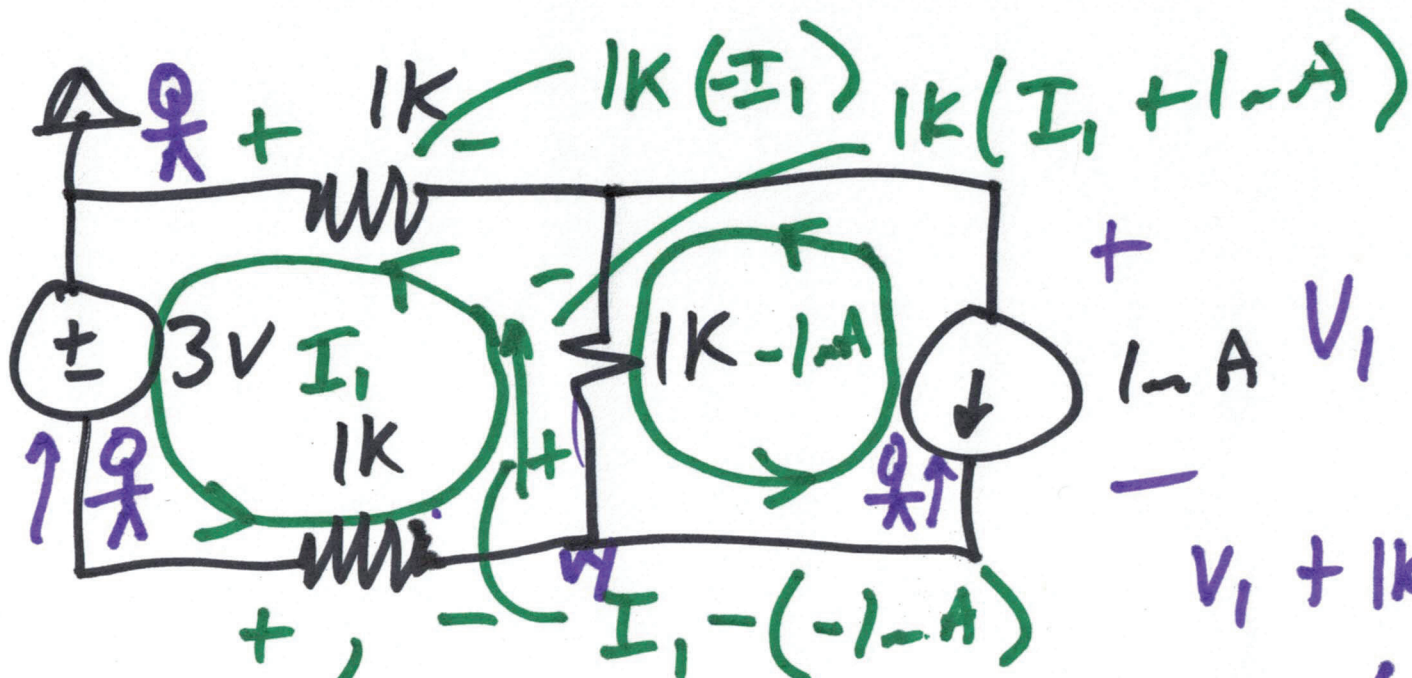

$$+ \quad 1mA \quad V_1$$

$$- \quad$$

$$V_1 + 1k(I_1 + 1mA) = 0$$

$$I_1 \cdot 1k = I_1 + 1mA$$

$$3 - (1k(-I_1)) + 1k(I_1 + 1mA)$$

$V_y = ?$


$$-3 - I_1 \cdot 1k$$

$$V = -IR$$


$$+ I_1 \cdot 1k = 0$$

$$V = IR$$

8)

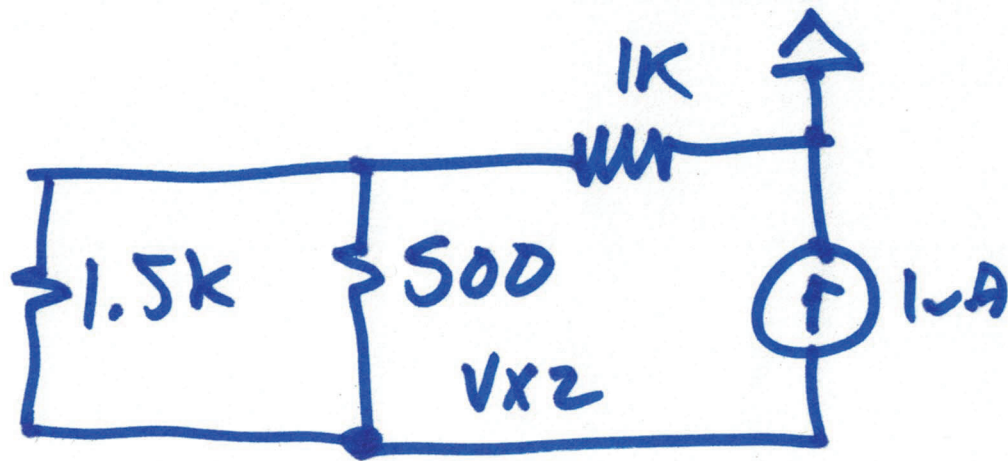
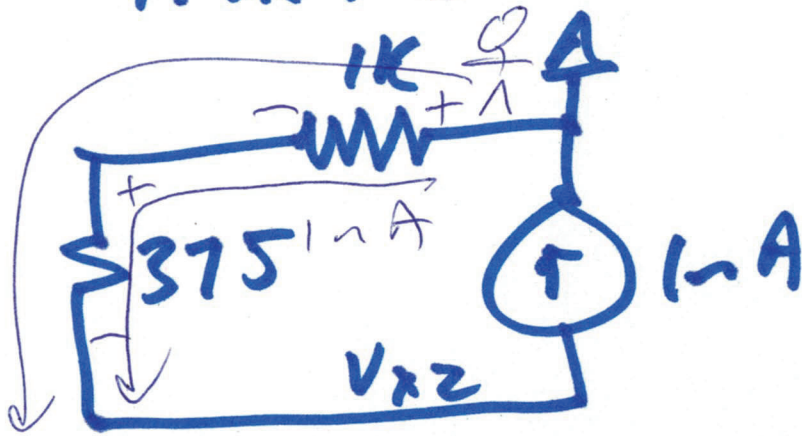
$$\frac{1.5k \cdot 500}{1.5k + 500} = \frac{1,500 \cdot 500}{2000} = 375\Omega$$



$$V_{x2} = -1k(1mA) - 1mA \cdot 375$$

$$= -1V - .375V$$

$$V_{x2} = -1.375$$

$$V_x = V_{x1} + V_{x2} = .375 - 1.375$$

$$= -1.0V$$

a)