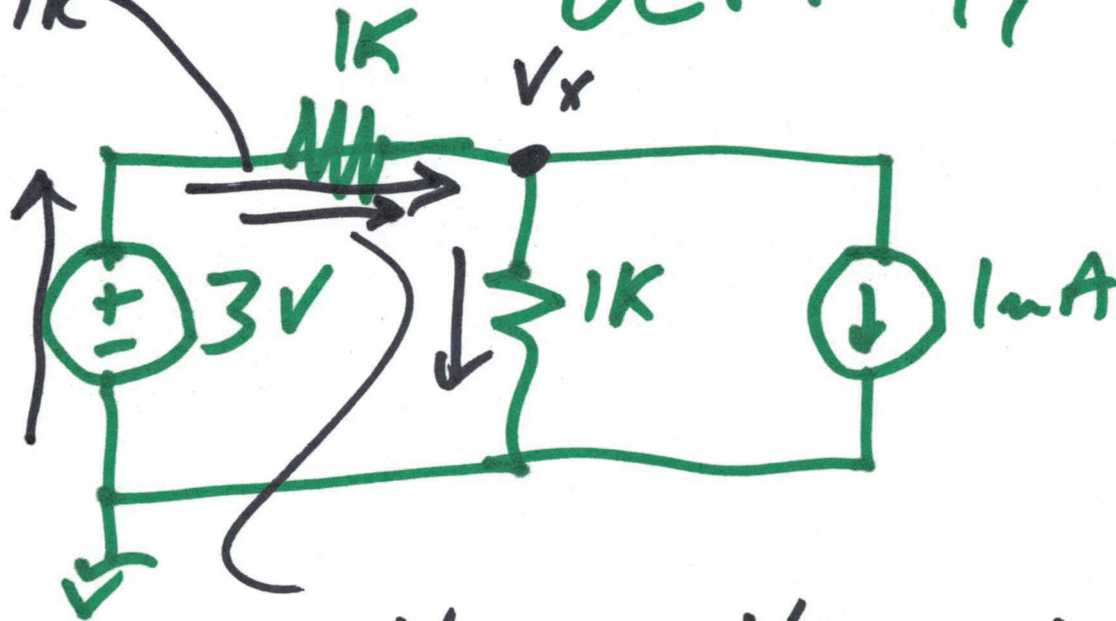


EE 270 circuits 1

Lecture 13

OCT. 7, 2020


$$\frac{3-1}{1K} = 2\mu A$$



$$\frac{3-V_x}{1K} = \frac{V_x}{1K} + 1\mu A$$

$$3 - V_x = V_x + 1$$

$$V_x = 1$$

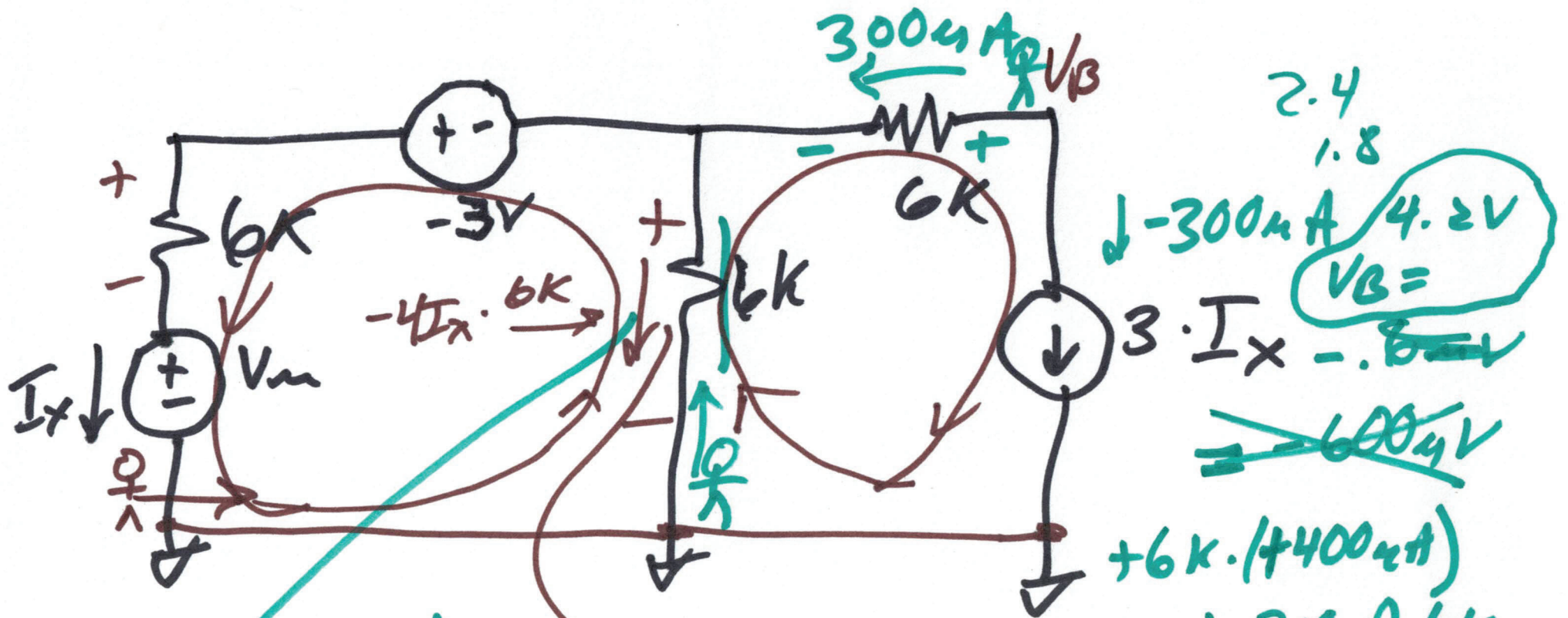

2.4
1.8
 $\downarrow -300\mu A$ $4.2V$
 $V_B =$
 ~~$3 \cdot I_x = 0.8$~~
 ~~$= 600\mu V$~~

$+400\mu A$

$$-I_x - 3I_x = -4I_x$$

$$+6k \cdot (+400\mu A) + 300\mu A \cdot 6k = V_B$$

$$+(-4I_x \cdot 6k) + (-3V) - 6kI_x = 0$$


$$-5I_x \cdot 6k = 3V$$

$$-5I_x = \frac{1}{2} \mu A = 500\mu A$$

$$I_x = +100\mu A$$

2)

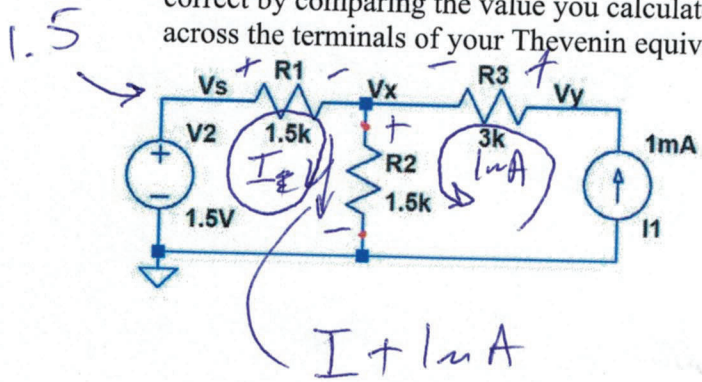3. Find the voltage V_x in the circuit seen below. Then find the Thevenin equivalent circuit, with R_2 removed, at the terminals marked by dots. Show that your Thevenin circuit is correct by comparing the value you calculated for V_x to the one you get when you put R_2 across the terminals of your Thevenin equivalent. (20 points)



$$1.5 - 1.5k \cdot I - 1.5k(I + 1mA) = 0$$

$$1.5 - 3kI - 1.5V = 0$$


$$I = 0$$

$$V_x = 1.5V$$


$$R_{TH} = 1.5k$$

$$V_{OC} = 1.5 + 1.5$$

$$V_{OC} = V_{TH} = 3V$$

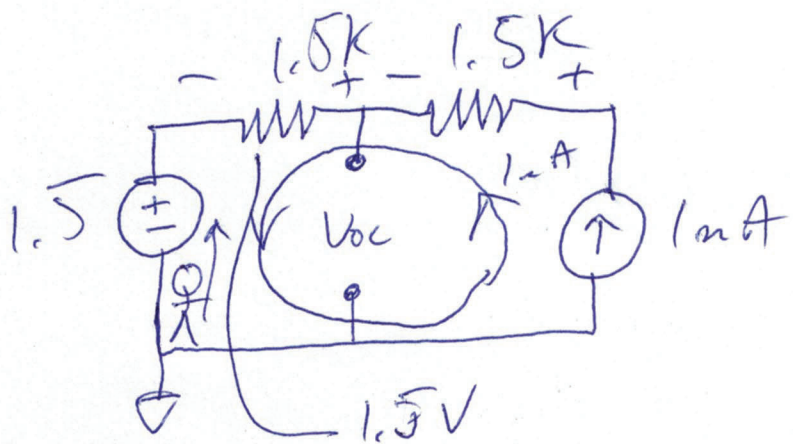

Thevenin

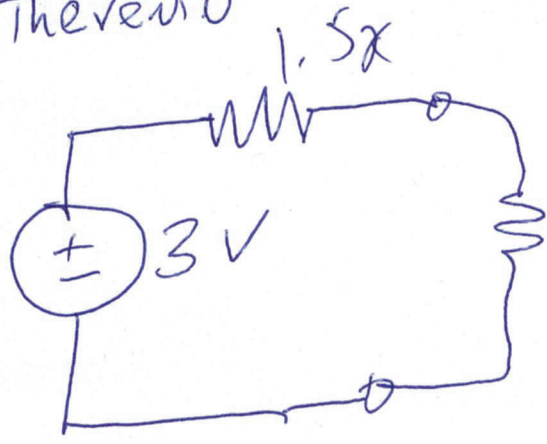


$$V_x = \frac{1.5k \cdot 3}{1.5k + 1.5k}$$

$$V_x = 1.5V$$

QED

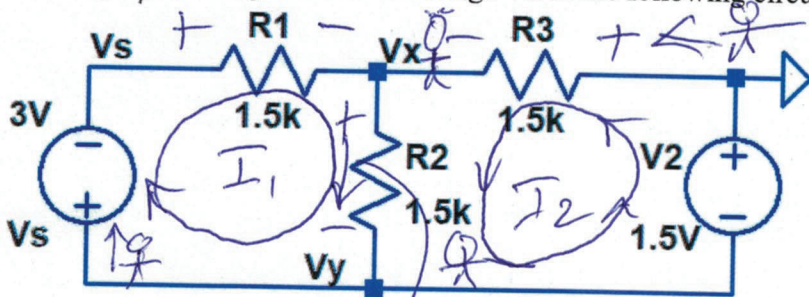4. Using mesh analysis find the voltage V_x in the following circuit. (20 points)



$$V_x = -I_2 \cdot 1.5k$$

$$= -\frac{4}{3} \mu A \cdot 1.5k$$

$$V_x = -2V$$

$$+ 1.5k(I_1 + I_2) + (3) + 1.5k \cdot I_1 = 0$$

$$+ 1.5k(I_1 + I_2) - (1.5) + 1.5kI_2 = 0$$

$$3kI_1 + 1.5kI_2 + 3 = 0$$

$$1.5kI_1 + 3kI_2 - 1.5 = 0$$

$$I_1 + \frac{1}{2}I_2 + 1 \mu A = 0$$

$$I_1 =$$

$$I_1 = -\frac{1}{2}I_2 - 1 \mu A = -\frac{1}{3} \mu A$$


$$1.5k\left(-\frac{1}{2}I_2 - 1 \mu A\right) + \frac{1.5k}{3k}I_2 - 1.5 = 0$$

$$-750I_2 - 1.5V + 3kI_2 - 1.5 = 0$$

$$I_2 = \frac{4}{3} \mu A \quad 2.25kI_2 = 3$$

4)

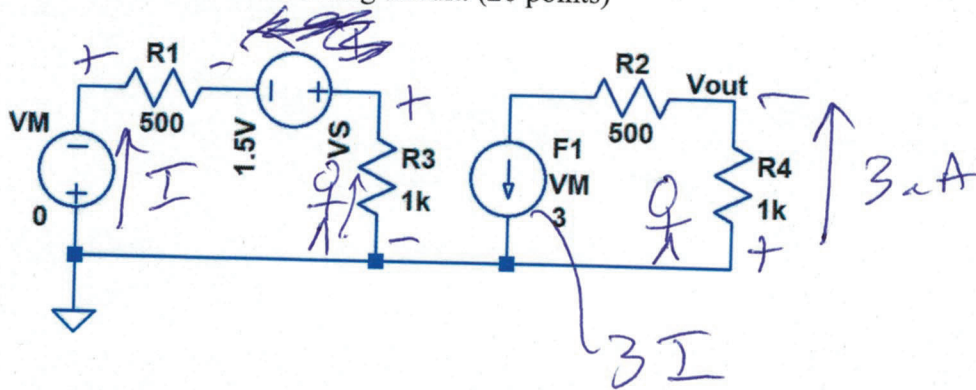5. Find V_{out} in the following circuit. (20 points)



$$1kI - 1.5 + 500 \cdot I = 0$$

$$1.5k \cdot I = 1.5$$


$$I = 1 \mu A$$

$$V_{out} = -3 \mu A \cdot 1k$$

$$V_{out} = -3V$$

S)

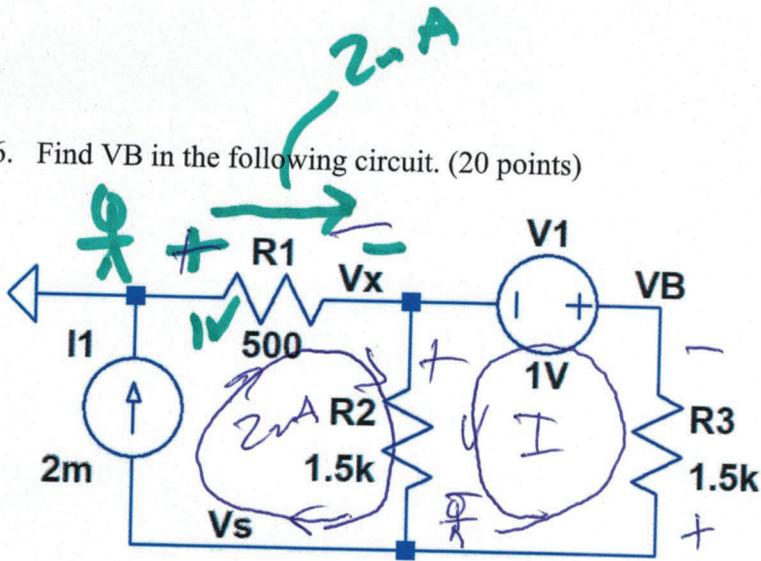6. Find V_B in the following circuit. (20 points)



$$-1.5kI - 1V - 1.5k(2mA + I) = 0$$


$$-3kI - 4 = 0$$

$$I = -1\frac{1}{3}mA$$

$$V_B = -1 + 1 = 0$$

$$\boxed{V_B = 0}$$

b)

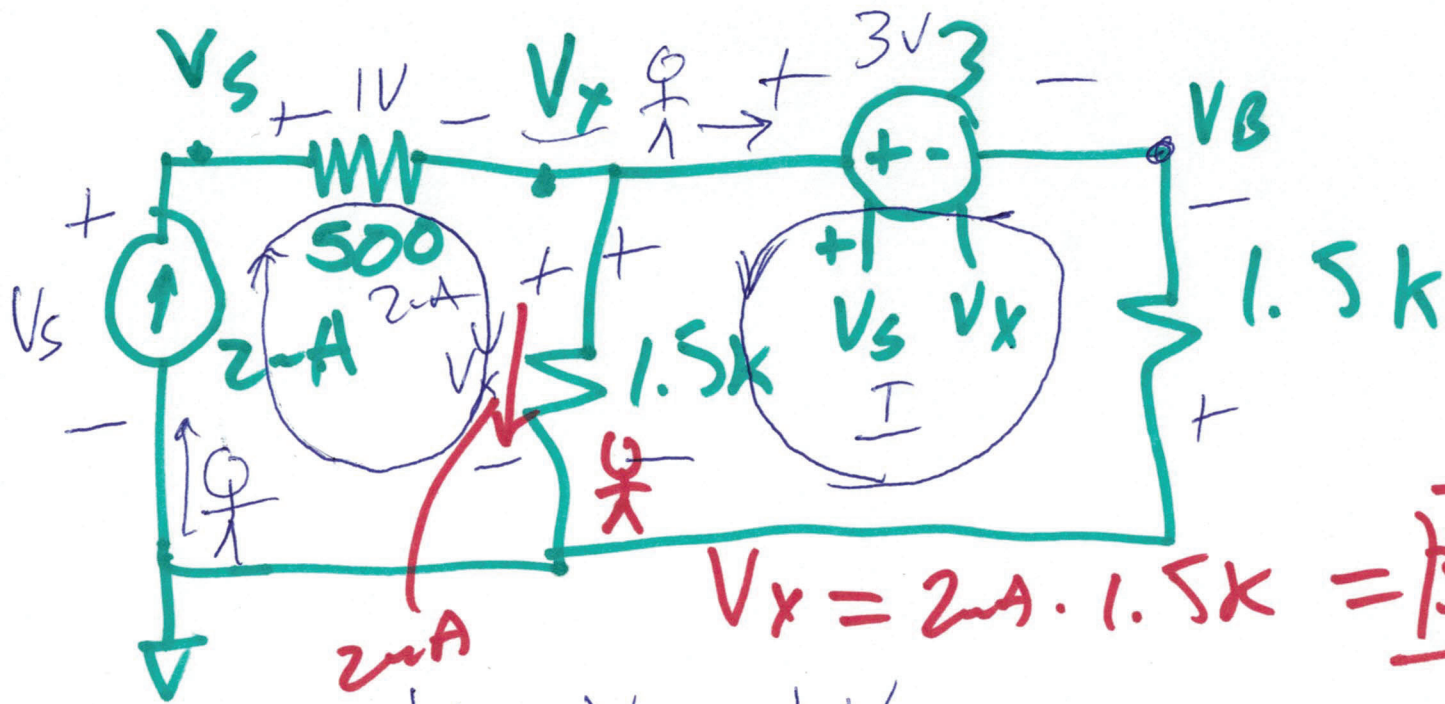

$$V_s = V_x = 1V$$

$$-3(V_s - V_x) + 1.5k \cdot I + 1.5k(2mA + I) = 0$$


$$V_s - 500 \cdot 2mA - V_x = 0$$

$$V_s - V_x = 1V$$

$$-3 + 3 + 3k \cdot I = 0$$

$$I = 0$$

1)

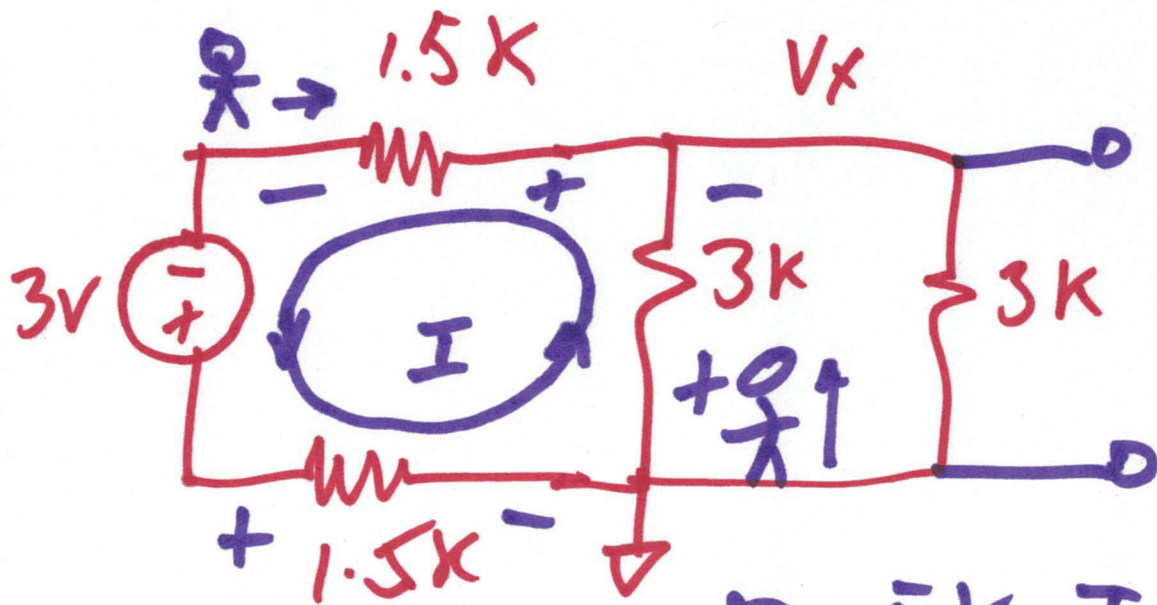

$$-1.5k \cdot \frac{2}{3} \text{ mA} = V_x$$

$$V_x = -1V$$

$$R_{TH} = 1k\Omega$$


$$1.5k \cdot I + 1.5k \cdot I + 1.5kI - 3 = 0$$

$$4.5k \cdot I = 3$$

$$I = \frac{3}{3 \cdot 1.5k} = \frac{1}{3} \text{ mA}$$

$$I = \frac{2}{3} \text{ mA}$$

ϵ & R_x

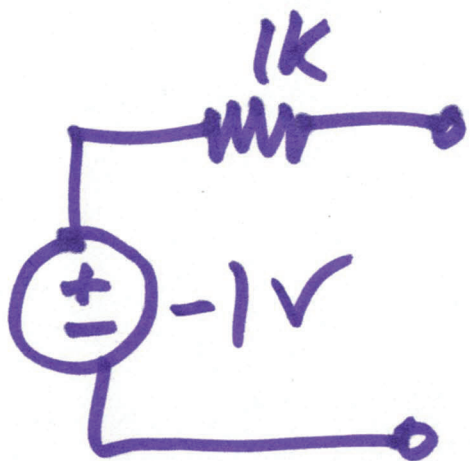

3)