

EE 220 Circuits I

October 26, 2020



Lecture 17

$$I = C \frac{dv_c}{dt}$$



$$V_c(t) = V_{init} + \frac{1}{C} \int_{t_s}^t i(t) \cdot dt$$

$$v_c(t) = -1 + t/100$$

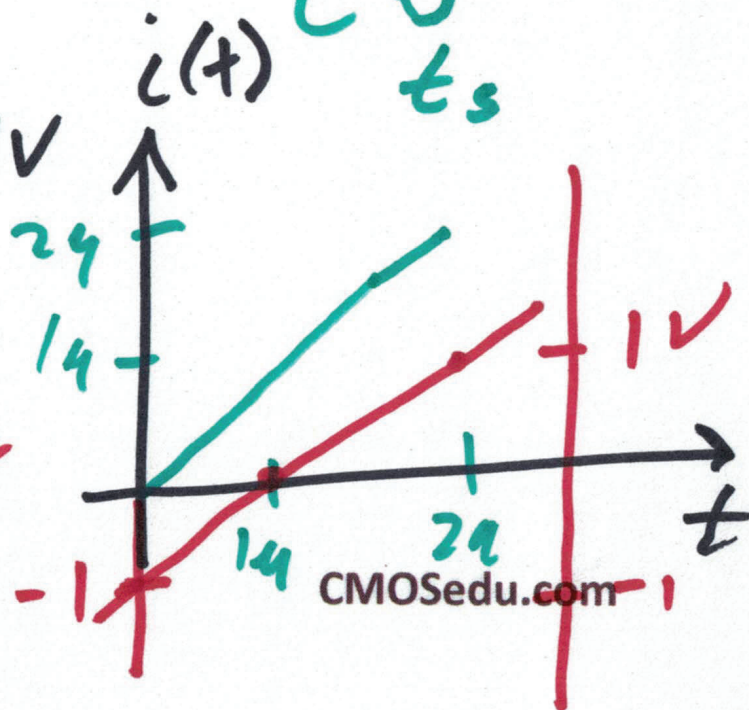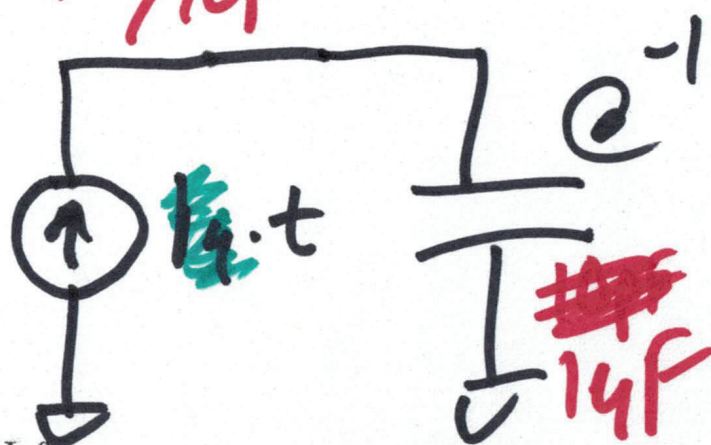


$$v_c(t) = -1 + \frac{1}{14F} \int_0^t t \, dt$$
$$= -1 + \frac{1}{14F} \frac{t^2}{2}$$

wrong!!

do it again
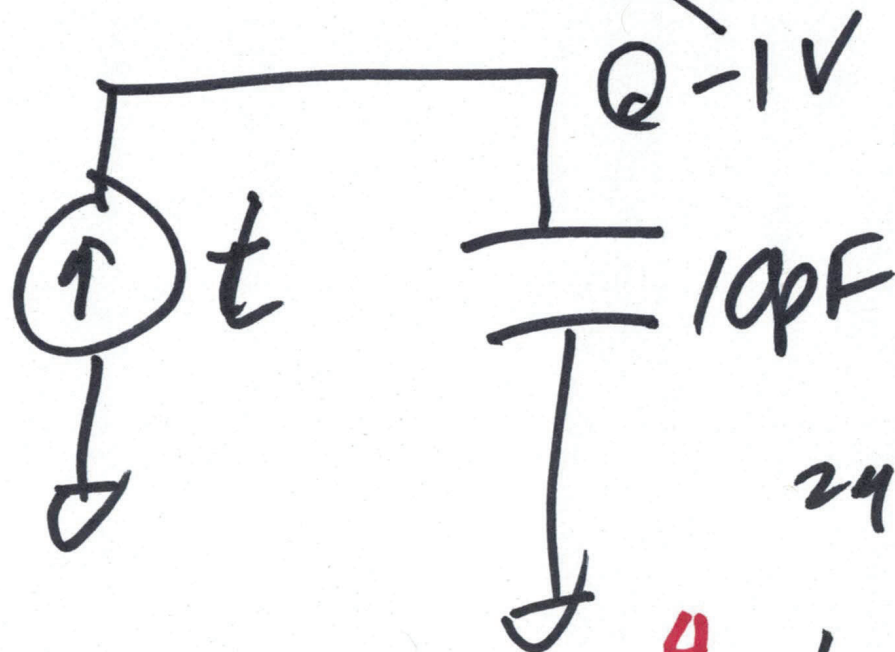
$$v_c(t) = -1 + \frac{1}{10\text{pF}} \int_0^t t \cdot dt$$



$$v_c(t) = -1 + \frac{1}{2} \cdot \frac{1}{10\text{p}} \cdot t^2$$


$$= -1 + \frac{1}{20} \cdot \frac{(10^{-6})^2}{10 \cdot 10^{-12}}$$

$$= -1 + \frac{1}{20} \cdot \frac{10^{-12}}{10^{-11}}$$

$$= -1 + \frac{1}{20} \cdot 10$$

$$= -1 + 0.5$$

$$= -0.5$$

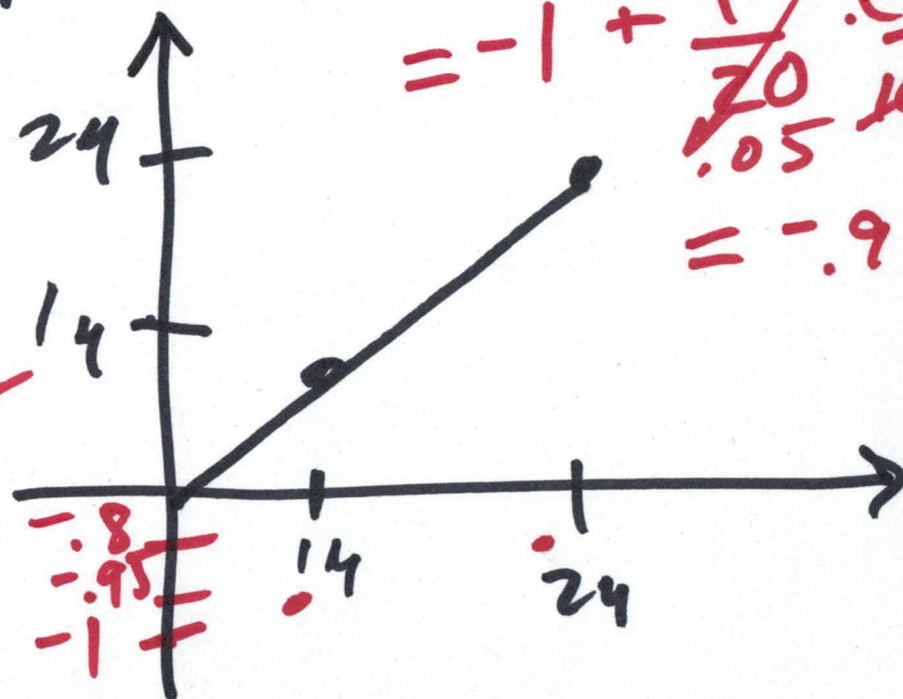


$$t = 20\text{s}$$

$$v_c(t) = -1 + \frac{1}{20} \cdot \frac{(10^{-6})^2}{10 \cdot 10^{-12}}$$

$$= -1 + \frac{1}{5}$$


5)

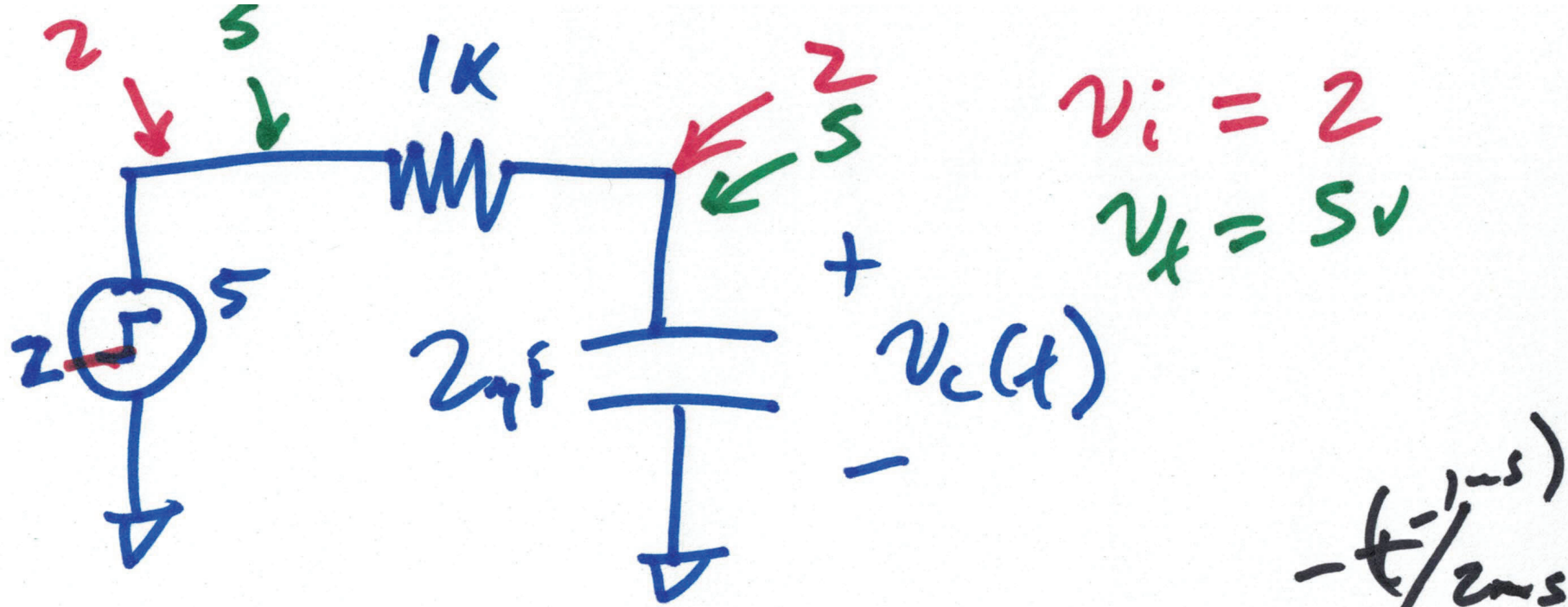

$$v_c(t) = 5 + (2 - 5)e^{-t/2ms}$$


$$t \geq 1ms$$

4)

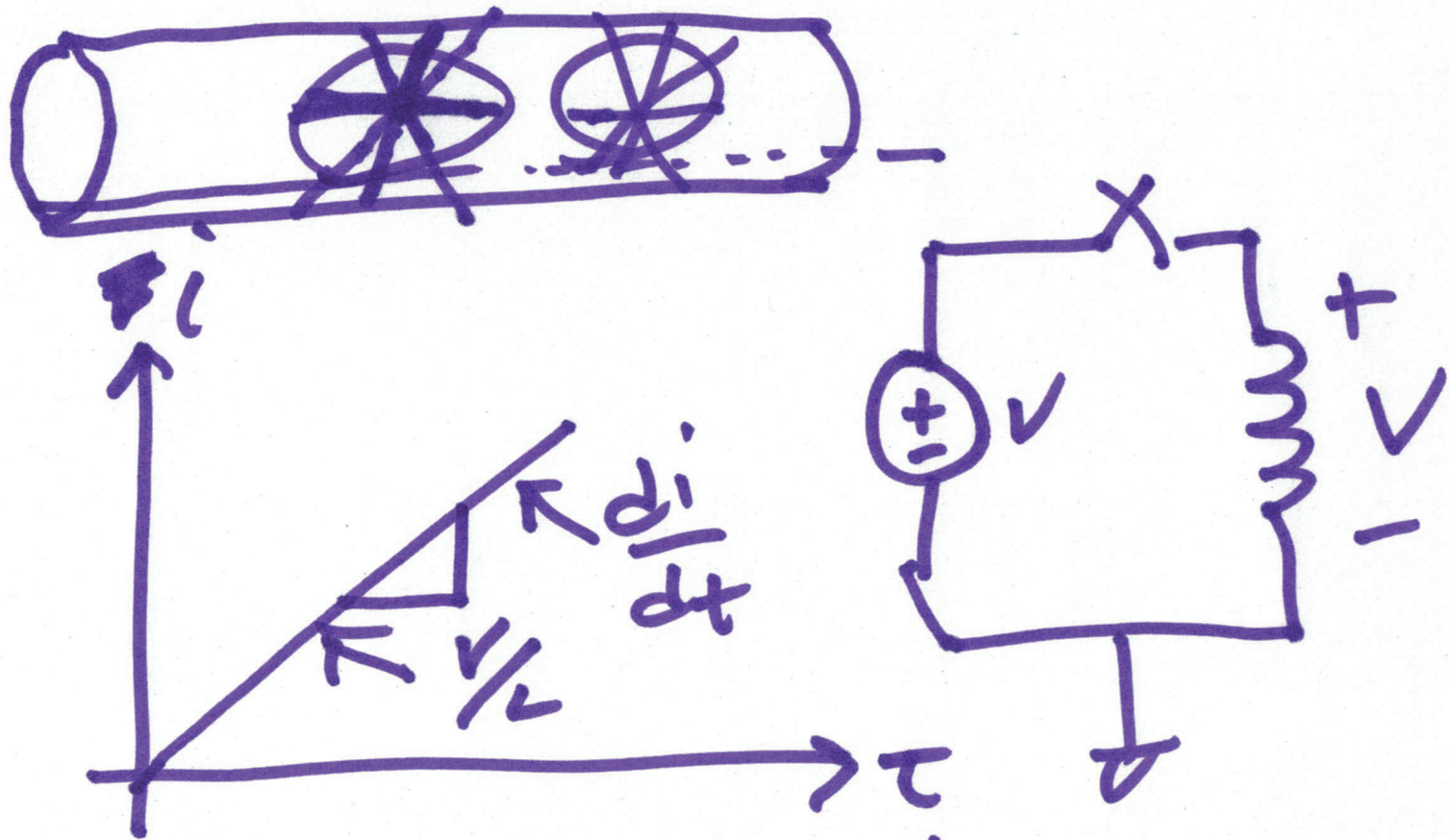

$$V = L \cdot \frac{di}{dt}$$
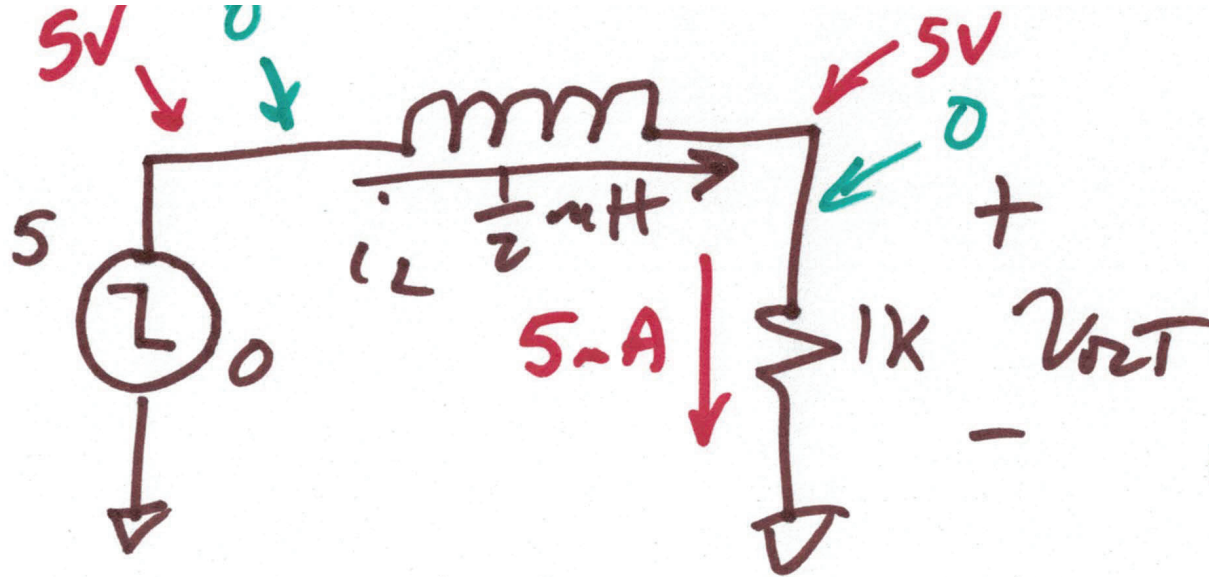
$$i_L(t) = i_i + \frac{1}{L} \int_0^t V_L(t) \cdot dt$$





$$i_i = 5 \mu\text{A}$$

$$i_f = 0$$

$$\tau = \frac{L}{R} = \frac{\frac{1}{2} \cdot 10^{-3}}{10^3} = 500 \text{ ns}$$
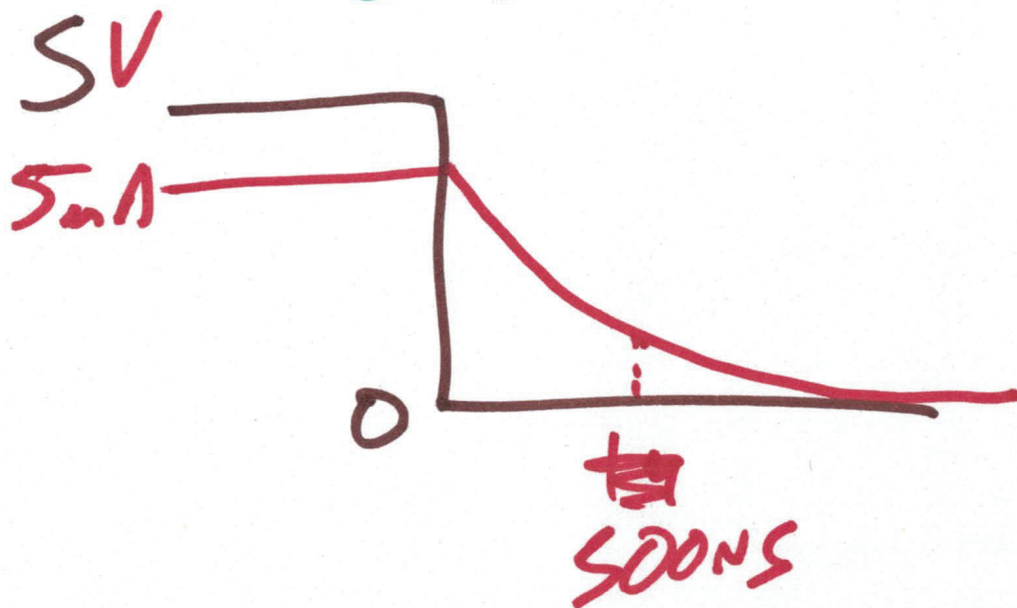
$$i_L(t) = 0 + (5 \mu\text{A} - 0)e^{-t/500 \text{ ns}}$$



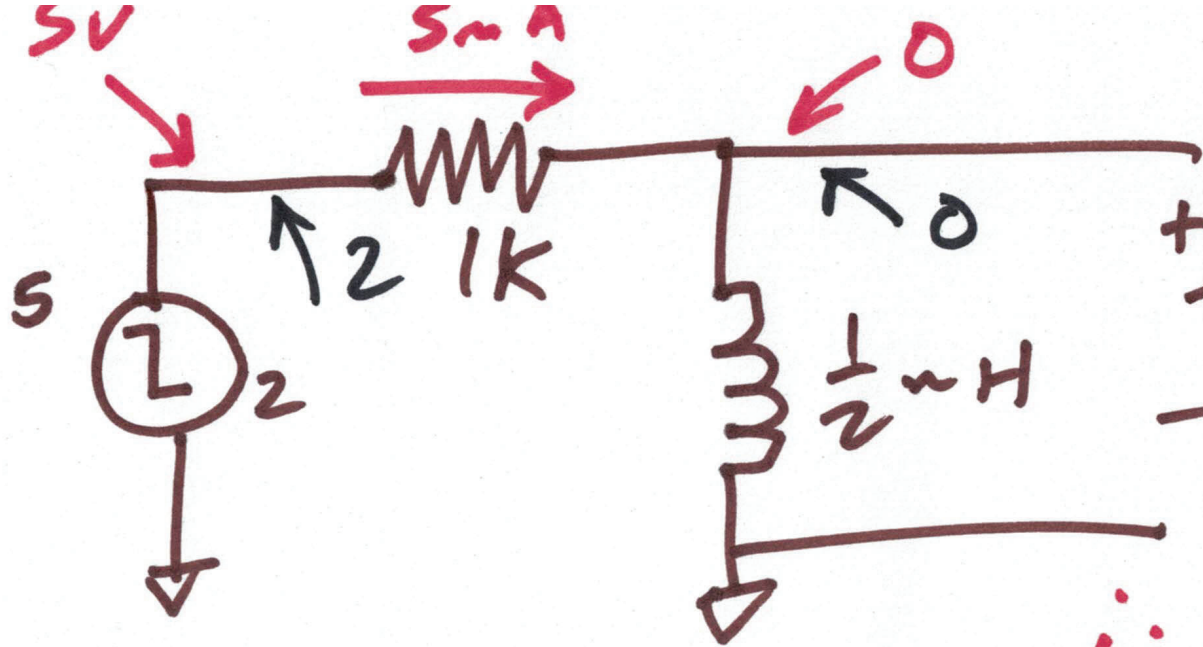

$$\frac{1}{2} \frac{10^{-3}}{10^3} = \frac{1}{2} 10^{-6}$$


$$\frac{1}{2} \frac{10^{-3}}{10^3} = 500 \mu\text{s}$$

$$i_i = 5 \text{ mA}$$

$$i_f = 2 \text{ mA}$$

$$i_L = 2 \text{ mA} + (5 \text{ mA} - 2 \text{ mA}) e^{-t/500 \mu\text{s}}$$
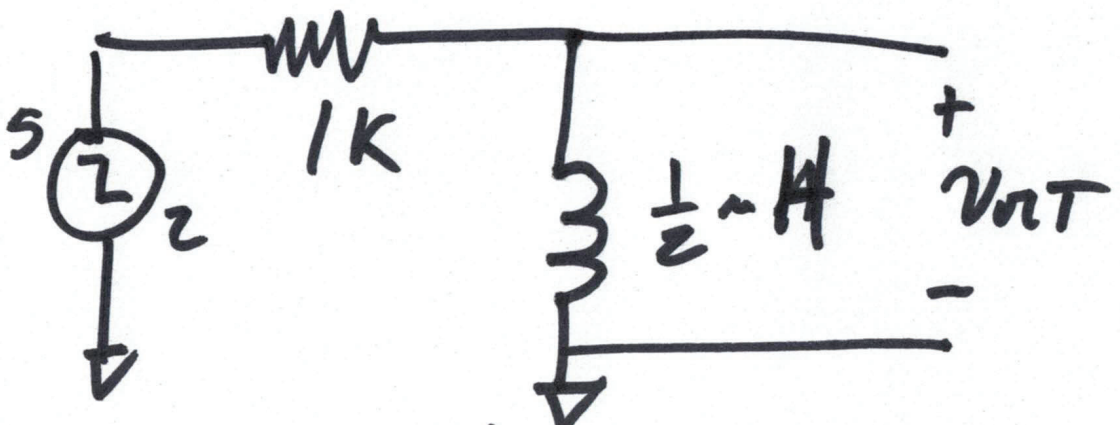
$$2 \text{ mA} + 3 \text{ mA} e^{-t/500 \mu\text{s}}$$



$$i_L = 2 - A + 3 - A e^{-t/500\mu\text{s}}$$

$$v_L = L \frac{di_L}{dt}$$

$$\frac{dAe^{-x \cdot b}}{dx} = A \frac{de^{-x \cdot b}}{dx}$$


$$v_L = \frac{1}{2} \cdot 10^{-3} \text{ H} \cdot \bullet$$

$$= A \cdot e^{-x \cdot b} \cdot \frac{d(-x \cdot b)}{dx} \quad 3 - A \cdot \left(\frac{-1}{500\mu\text{s}} \right) e^{-t/500\mu\text{s}}$$

$$= A(-b) e^{-x \cdot b} \quad -\frac{3}{2} \cdot \frac{10^{-6}}{\frac{1}{2} \cdot 10^{-6}} e^{-t/500\mu\text{s}}$$

$$v_L = -3 e^{-t/500\mu\text{s}}$$

8)

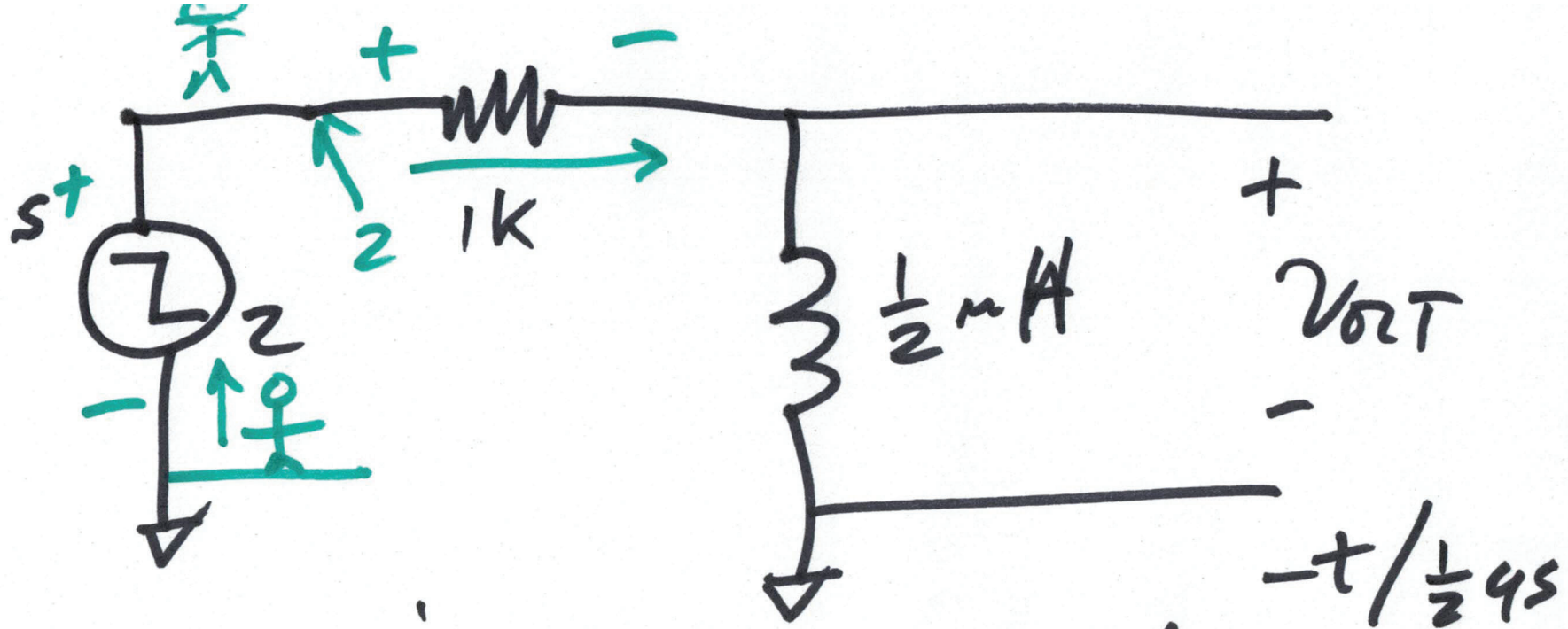


$$i_L = 2\text{mA} + 3\text{mA}e^{-t/1/2 4s}$$

$$2 - 1\text{k} \cdot i_L = 2\text{V}$$

$$2 - 2\text{V} - 3\text{V}e^{-t/1/2 4s} = 2\text{V}$$

$$2\text{V} = -3e^{-t/1/2 4s}$$

8)

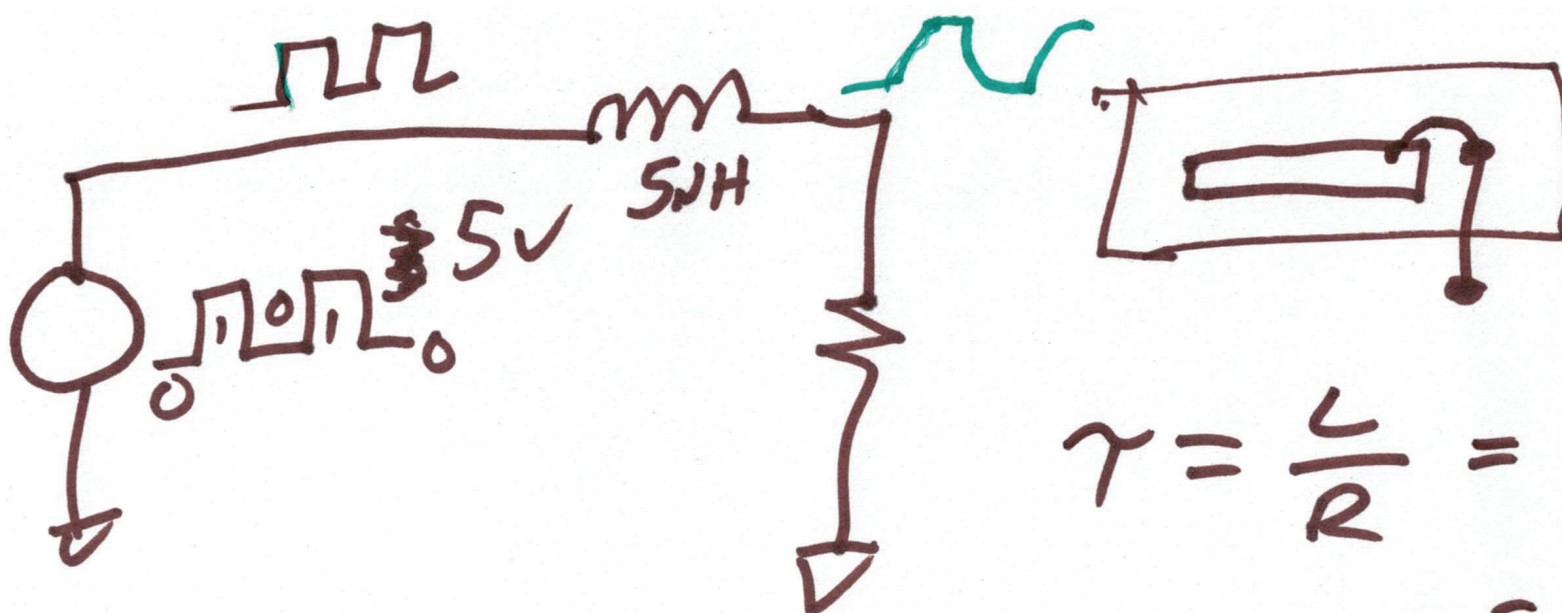

$$\tau = \frac{L}{R} = \frac{5nH}{1k} = 5ps$$