

EE 220

Circuits 1


Nov. 2, 2020

Lecture 19

first-order circuits
have one inductor or
one capacitor




Second-order circuit

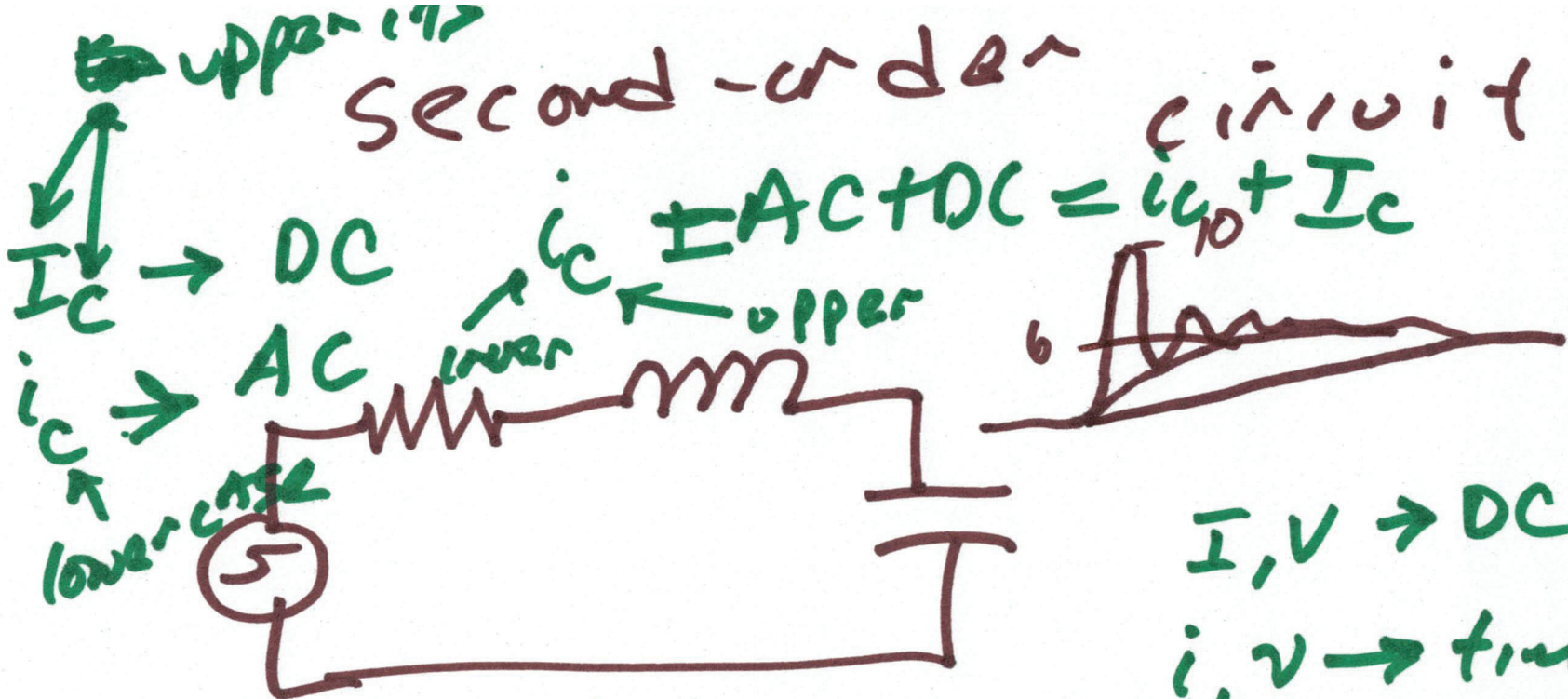


$I, V \rightarrow DC$
 $i, v \rightarrow$ time varying

$I \downarrow \uparrow \begin{matrix} + \\ v \\ - \end{matrix}$
 $R = \frac{V}{I}$
 Ohms

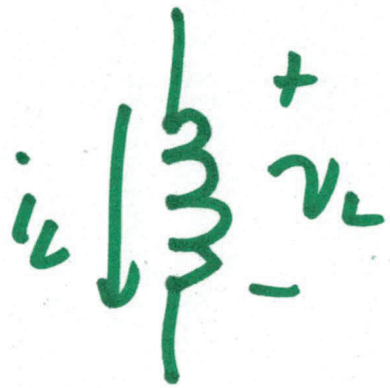
$I \downarrow \uparrow \begin{matrix} + \\ v \\ - \end{matrix}$
 $\frac{I}{V} = \left(\frac{1}{R} \right)$ conductance
 siemens



$$v_L = L \cdot \frac{di_L}{dt}$$

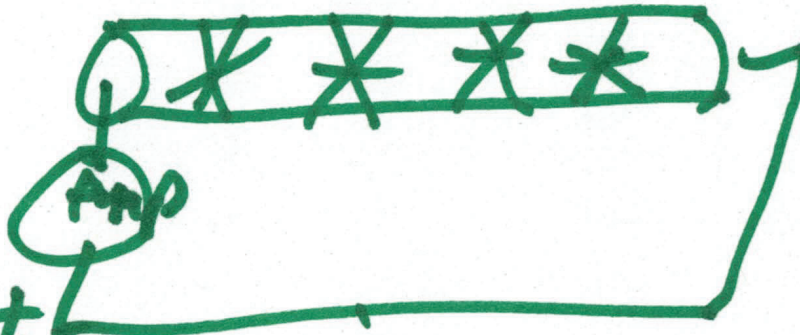
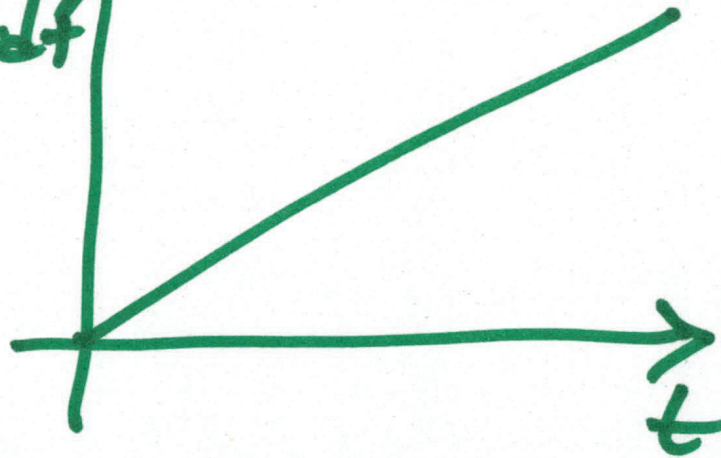
$$i_L = i_{init} + \frac{1}{L} \int_{t_{init}}^t v_L(t) dt$$



3)

Energy in an inductor

$$v_L(t) = L \cdot \frac{di_L(t)}{dt}$$

$$E = \int_{t_1}^{t_2} v_L(t) \cdot i_L(t) dt$$

$$\rightarrow dt = \frac{L \cdot di(t)}{v_L(t)}$$


$$E = \int_{t_1}^{t_2} v_L(t) \cdot L \cdot \frac{i_L(t) di_L(t)}{v_L(t)}$$

$$E = \int_{t_1}^{t_2} L \cdot i_L \cdot di_L = L \left. \frac{1}{2} i_L^2 \right|_{t_1}^{t_2}$$

$$t_2 \rightarrow t \quad t_1 \rightarrow 0$$

$$\underline{E = \frac{1}{2} L \cdot i^2}$$

CAPACITORS

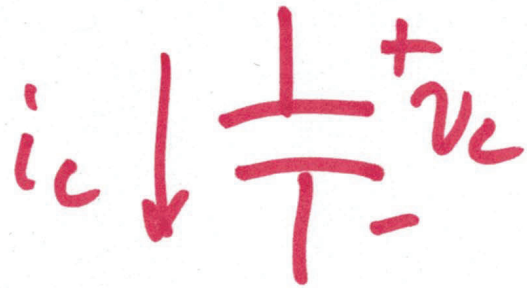


$$C \cdot V = Q$$


$$i_c = C \cdot \frac{dv_c}{dt}$$

$$v_c(t) = v_i + \frac{1}{C} \int_0^t i_c(t) \cdot dt$$

$u(t) \rightarrow$ ^{unit} step function

$$\mathcal{L}\{u(t)\} = \frac{1}{s}$$

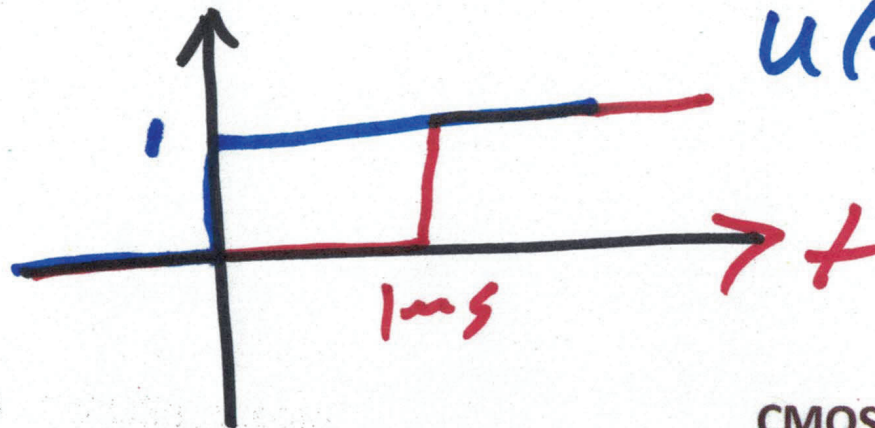

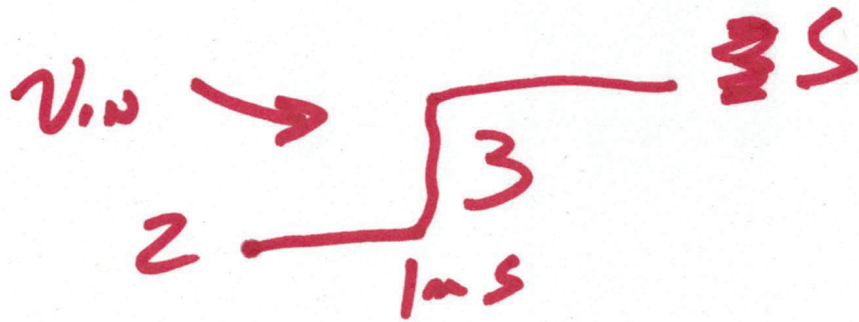

$$v_{in} = 2 + 3 \cdot v(t-1-s)$$

$$E = \int_0^t v_c(t) \cdot i_c(t) \cdot dt \rightarrow i_c(t) = \frac{dv_c(t)}{dt}$$

$$dt = C \cdot \frac{dv_c(t)}{i_c(t)}$$

$$E = \int_0^t v_c(t) \cdot \cancel{i_c(t)} \cdot C \cdot \frac{dv_c(t)}{\cancel{i_c(t)}}$$


$$E = \frac{1}{2} C V_c^2$$

$$E = \int_0^Q v_c(t) \cdot dt = \frac{1}{2} v_c \cdot t \Big|_0^Q$$

$$= \frac{1}{2} v_c \cdot Q$$

$$CV = Q \rightarrow Q = CV$$

$$E = \frac{1}{2} CV^2$$

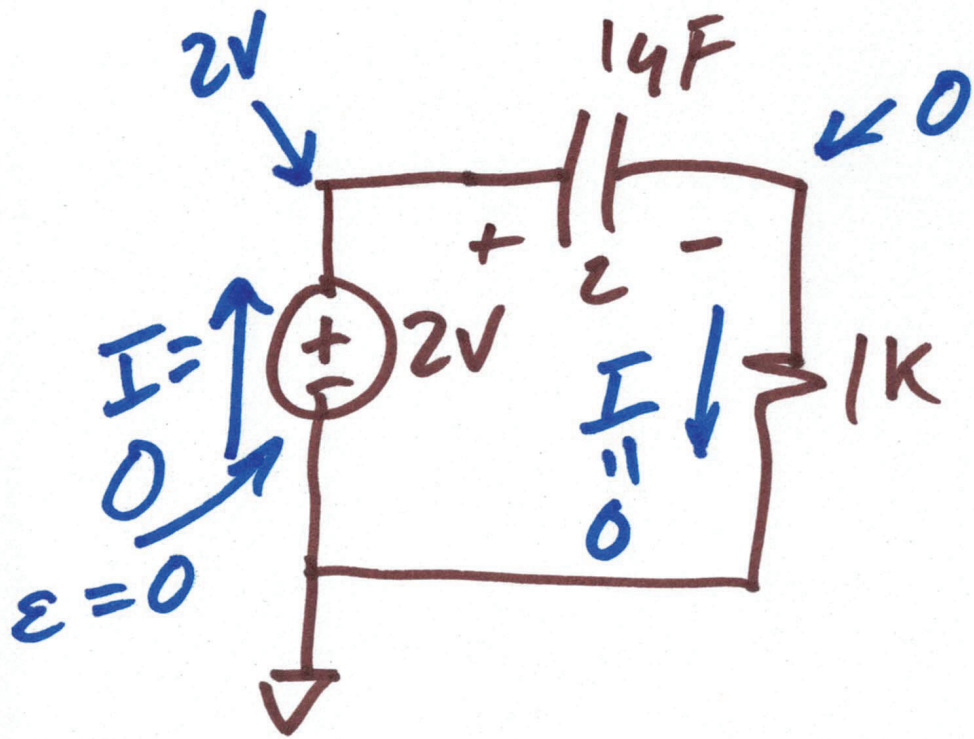


$$\rightarrow P_R = I \cdot V = \frac{V^2}{R} = I^2 \cdot R$$

$$P_R = 0$$

$$\epsilon = \frac{1}{2} 10^{-6} \cdot 2^2$$

$$\epsilon = 2 \mu\text{J}$$

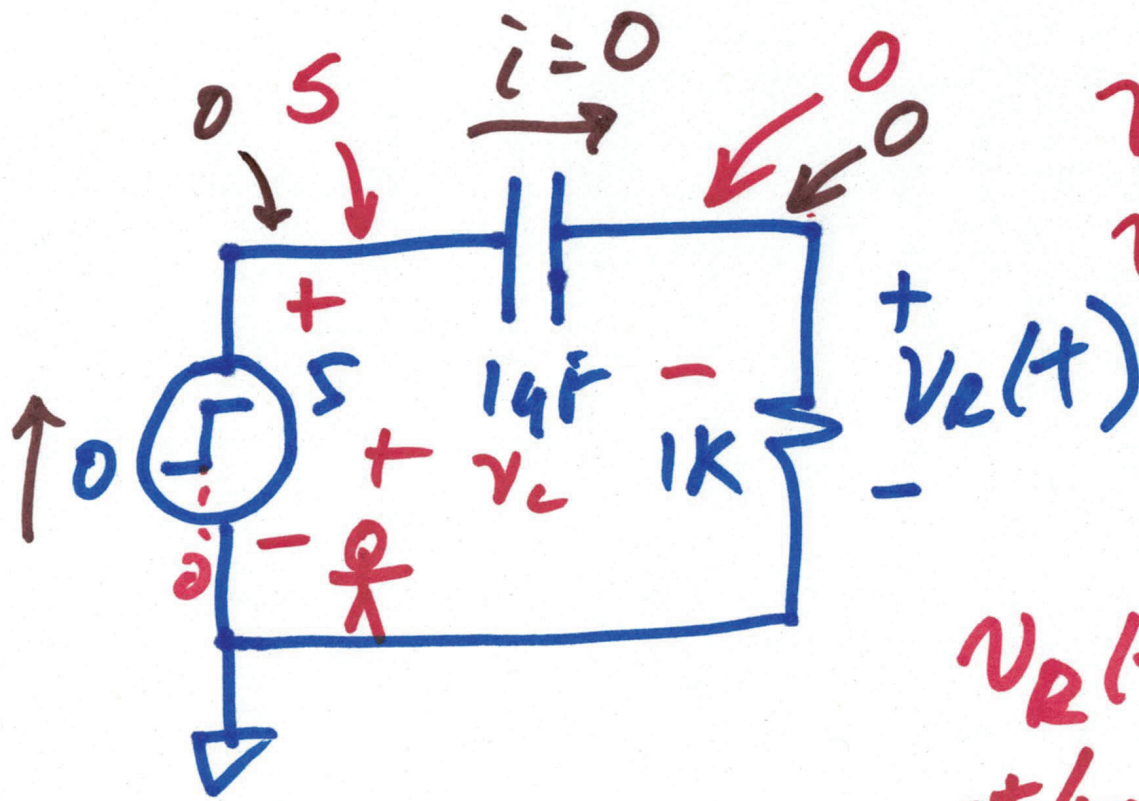

$$v_i = 0$$

$$v_f = 5 - 0 = 5$$


$$v_R(t) = 0$$

$$-t/1\mu s \quad t \leq 0$$

$$v_c(t) = 5 + (0 - 5)e^{-t/1\mu s}$$


$$v_R(t) = 5 - v_c(t) = 5e^{-t/1\mu s}$$

$$v_c(t) = 5(1 - e^{-t/1\mu s})$$

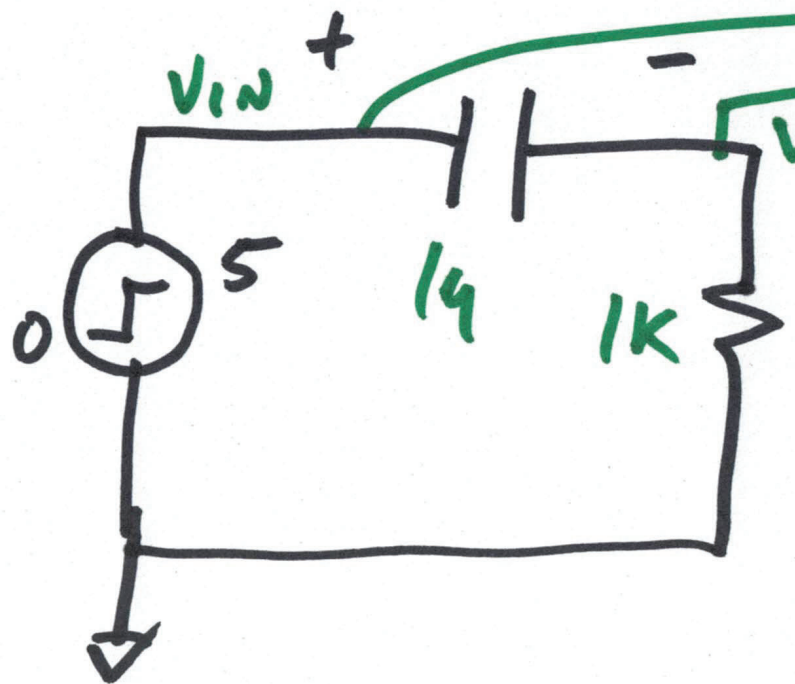

$$v_R(t) = 5e^{-t/1\mu s}$$

$$v_c = v_{in} - v_R$$

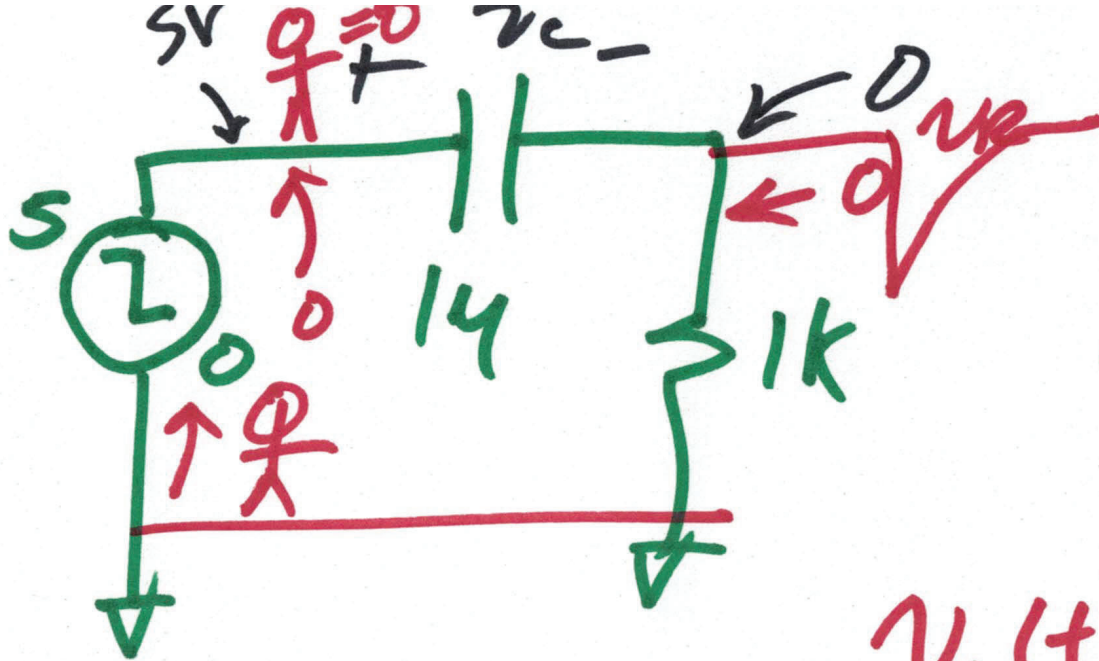


$$v_i = 5$$

$$v_f = 0 \quad -t/1ms$$

$$v_c(t) = 5e^{-t/1ms}$$

$$-v_c(t) = v_R(t) = -5e^{-t/1ms}$$

12)

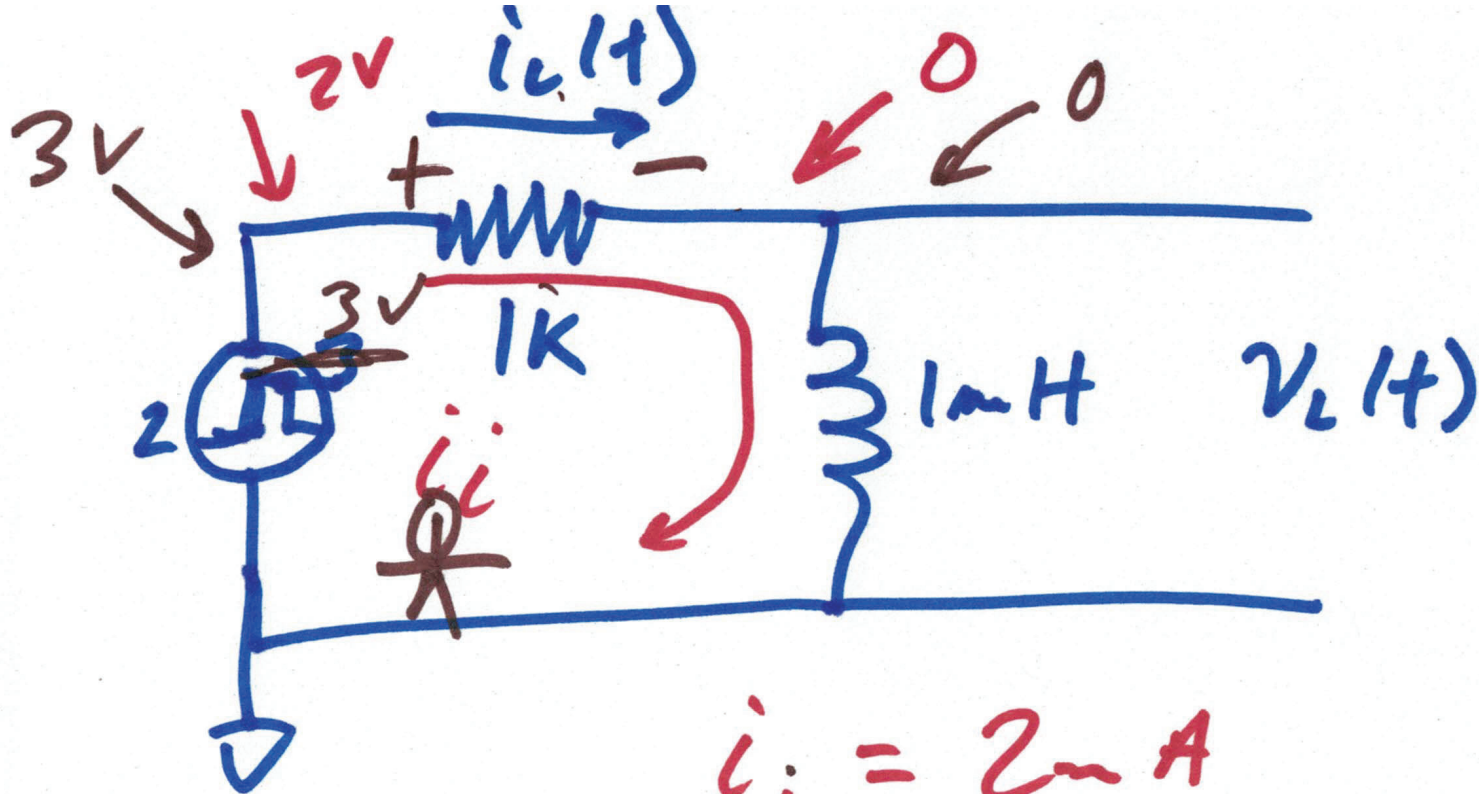

$$\frac{L}{R} = 14s$$

$$i_i = 2mA$$

$$i_f = 3mA$$

$$i_L(t) = 3mA + (2mA - 3mA)e^{-t/14s}$$

$$v_L(t) = 3 - i_L \cdot 1k = 3 - 1k(3mA - 1mAe^{-t/14s})$$