

EE 220


Circuits 1

Nov. 4,

2020

Lecture

20

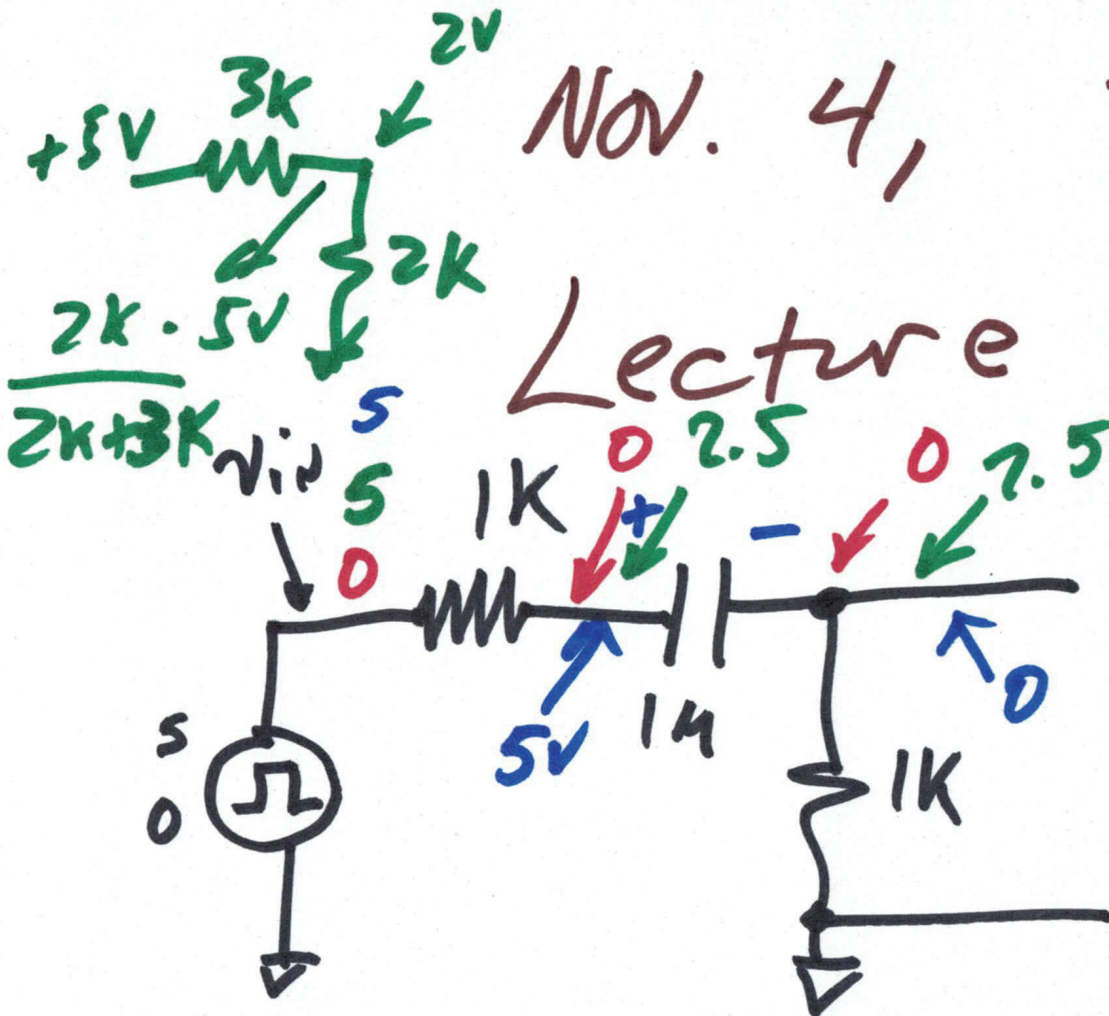

$$v_{i|bs} = 0$$

$$v_{i|as} = 0$$

$$v_f = 5V$$


$$v_c(t) = 5 - 5e^{-t/2ms}$$

$$v_c(t) = 5(1 - e^{-t/2\mu s})$$

$$i_c = C \frac{dv_c(t)}{dt}$$

$$\frac{d}{dt} \left(\frac{-t}{2RC} \right)$$

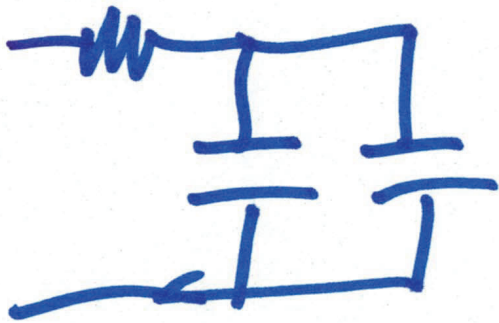
$$i_c = C \left(\frac{d}{dt} (5 - 5e^{-t/2RC}) \right)$$




$$= C \left(0 - 5e^{-t/2RC} \cdot \left(\frac{-1}{2RC} \right) \right)$$

$$i_c = 2.5 \mu A e^{-t/2\mu s}$$
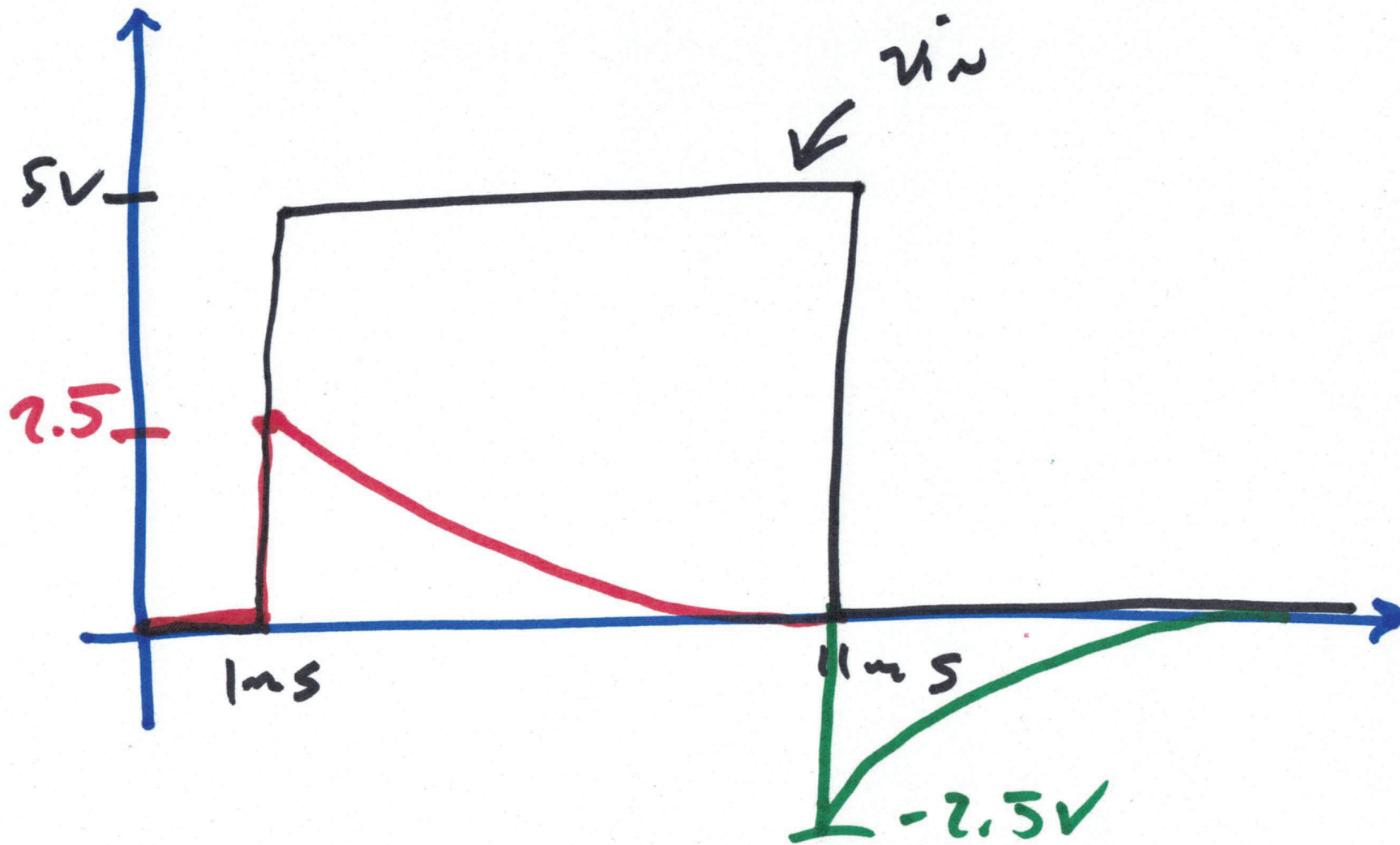
$$v_R = 1k \cdot i_c = 2.5 e^{-t/2\mu s}$$




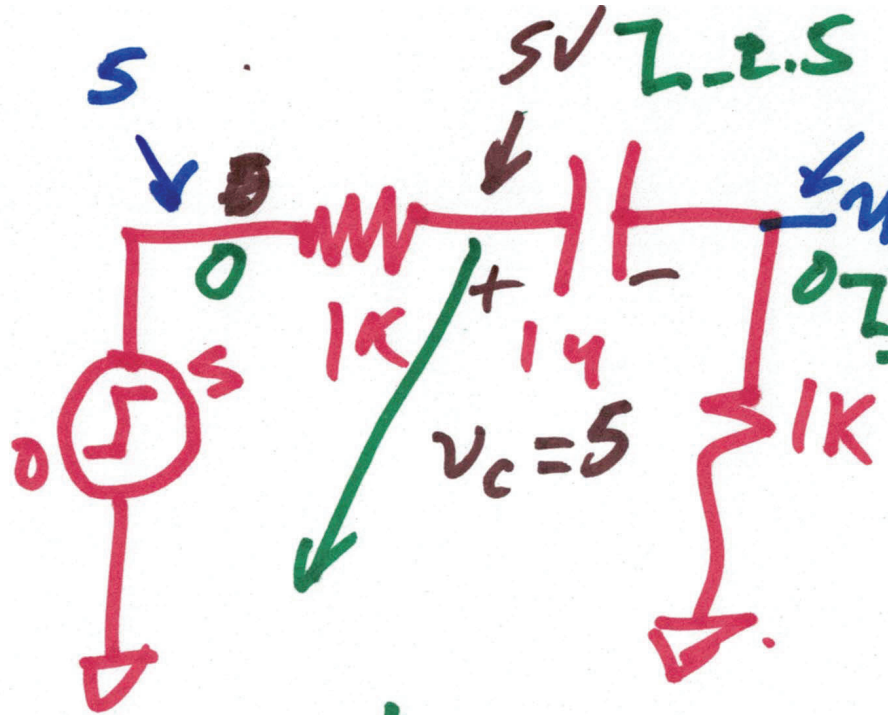

$v_i = 2.5V$
 $v_f = 0$
 $v_i = -2.5, v_f = 0$
 $v_e = v_f + (v_i - v_f)e^{-t/\tau}$


$\tau = 2RC = 2\mu s$

$v_e(t) = 2.5 e^{-t/2\mu s}$

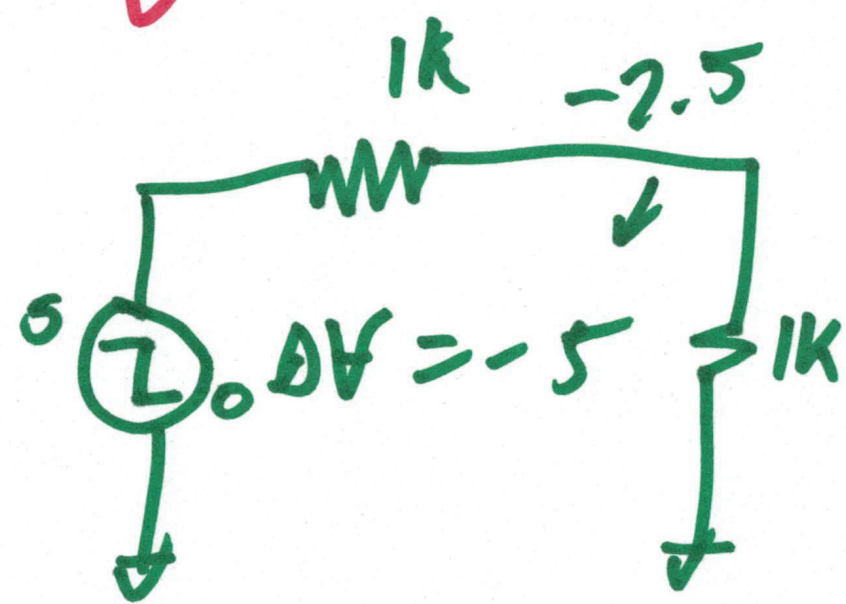


$t \geq 1\mu s$
 $v_r(t) = -2.5 e^{-\frac{-(t-1\mu s)}{2\mu s}}$
 $t \geq 1\mu s$

4)

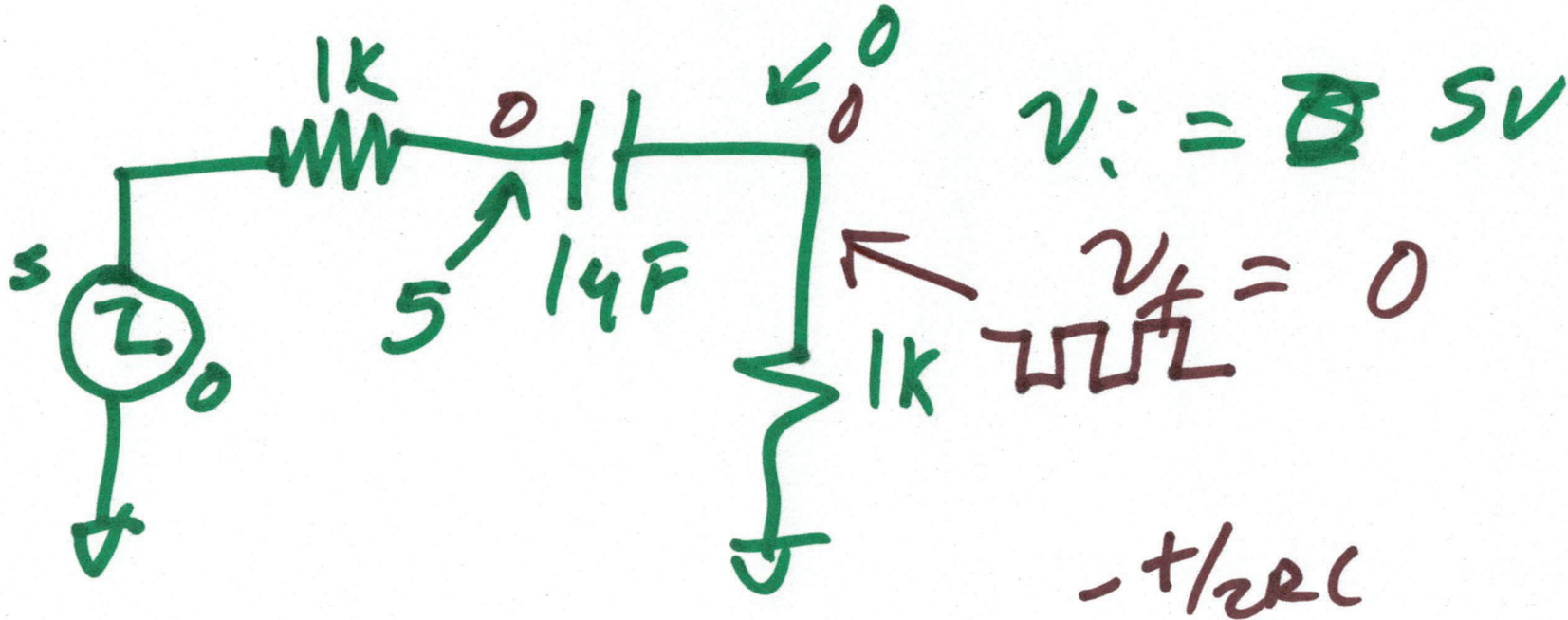


$$v_c(t) = 5e^{-t/2RC}$$

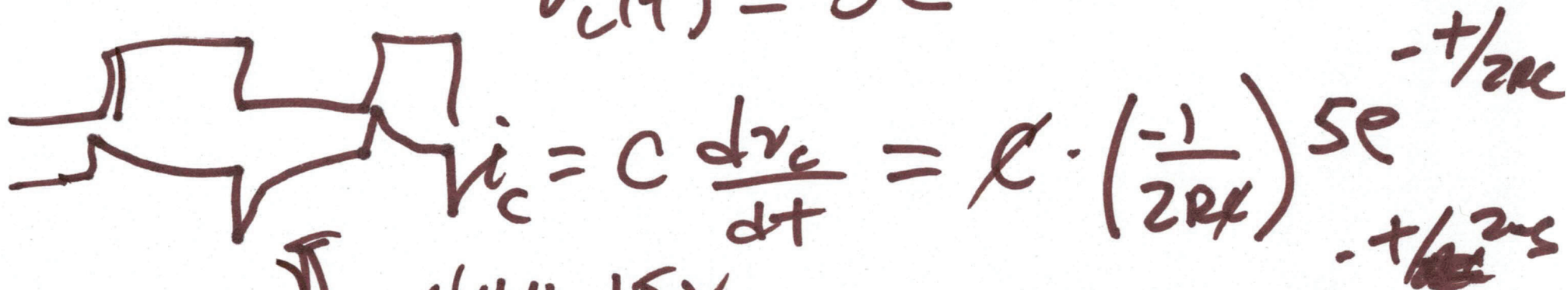

$$i_c = -2.5 \mu A e^{-t/2RC}$$

$$v_r(t) = -2.5e^{-t/2RC}$$

5)

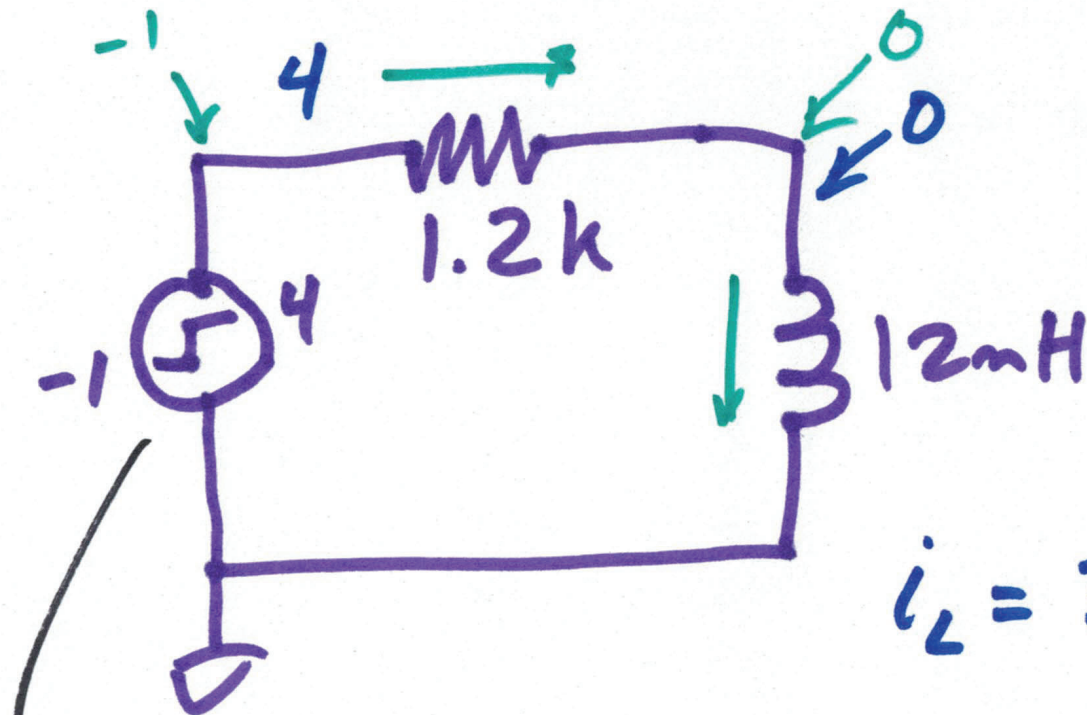


$$i_i = \frac{-1 - 0}{1.2k} = -.83 \mu A$$

$$i_f = \frac{4 - 0}{1.2k} = 3.33 \mu A$$

$$i_L = 3.33 \mu A + (-.83 \mu A) \rightarrow 3.33 \mu A$$

$$e^{-t/10 \mu s}$$

(-14 14 10V 10V 70μ)

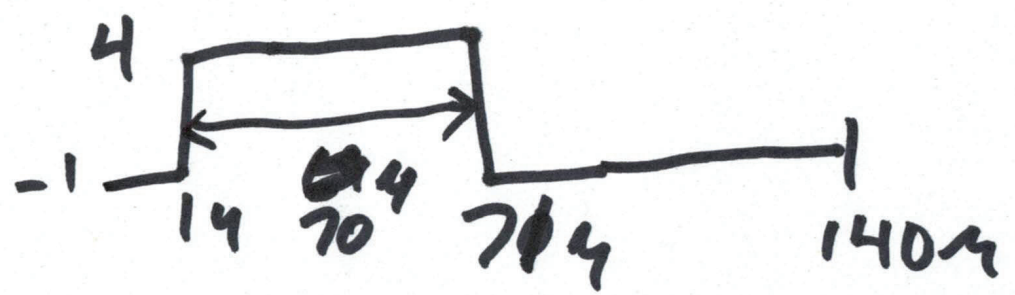

$$v_L = L \cdot \frac{di_L}{dt}$$

6)


$$i_L(t) = 3.33 \text{ mA} - 4.16 \text{ mA} e^{-t/10 \mu\text{s}}$$

$$v_L(t) = L \frac{di_L(t)}{dt} =$$

$$\overset{12 \mu\text{H}}{\uparrow} (-4.16 \text{ mA}) \cdot \left(-\frac{1}{10 \mu\text{s}}\right) e^{-t/10 \mu\text{s}}$$


$$v_L(t) = \frac{12 \cdot 4.16}{10} e^{-t/10 \mu\text{s}}$$
$$= 5 e^{-t/10 \mu\text{s}}$$

Integrators

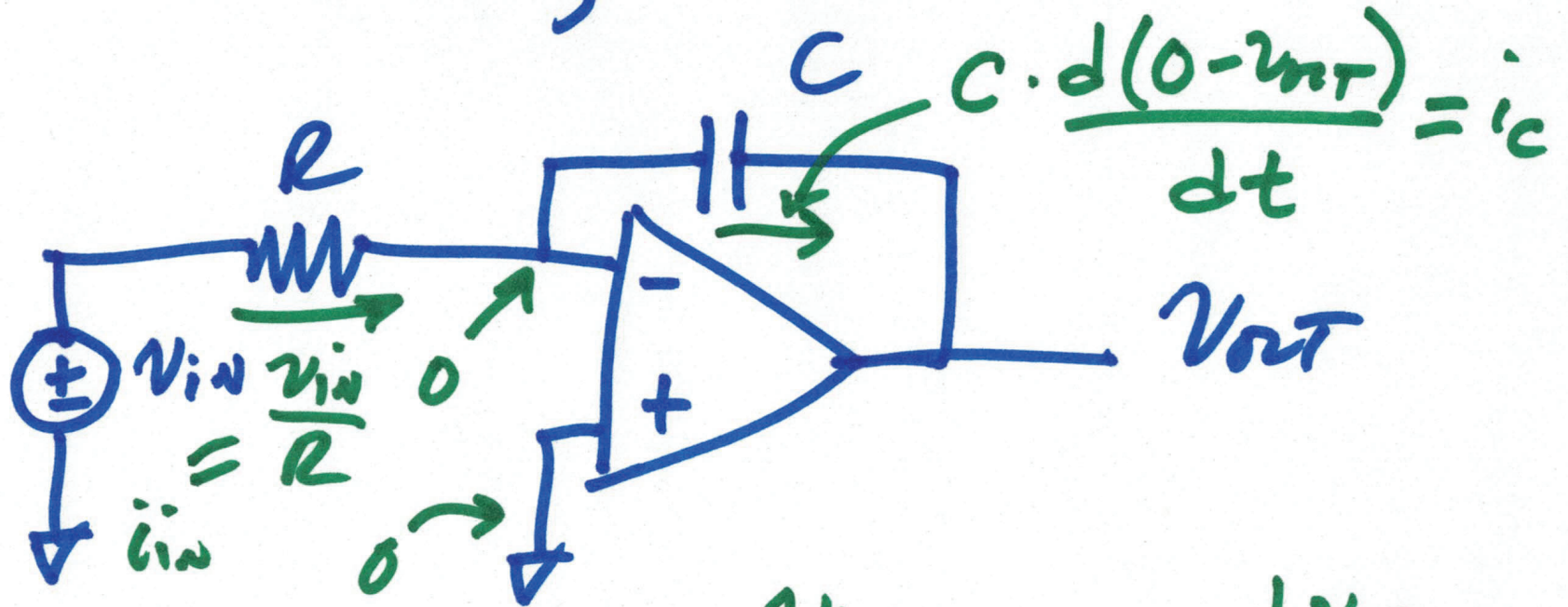

$$\frac{v_{in}}{R} = -C \cdot \frac{d v_{out}}{dt}$$
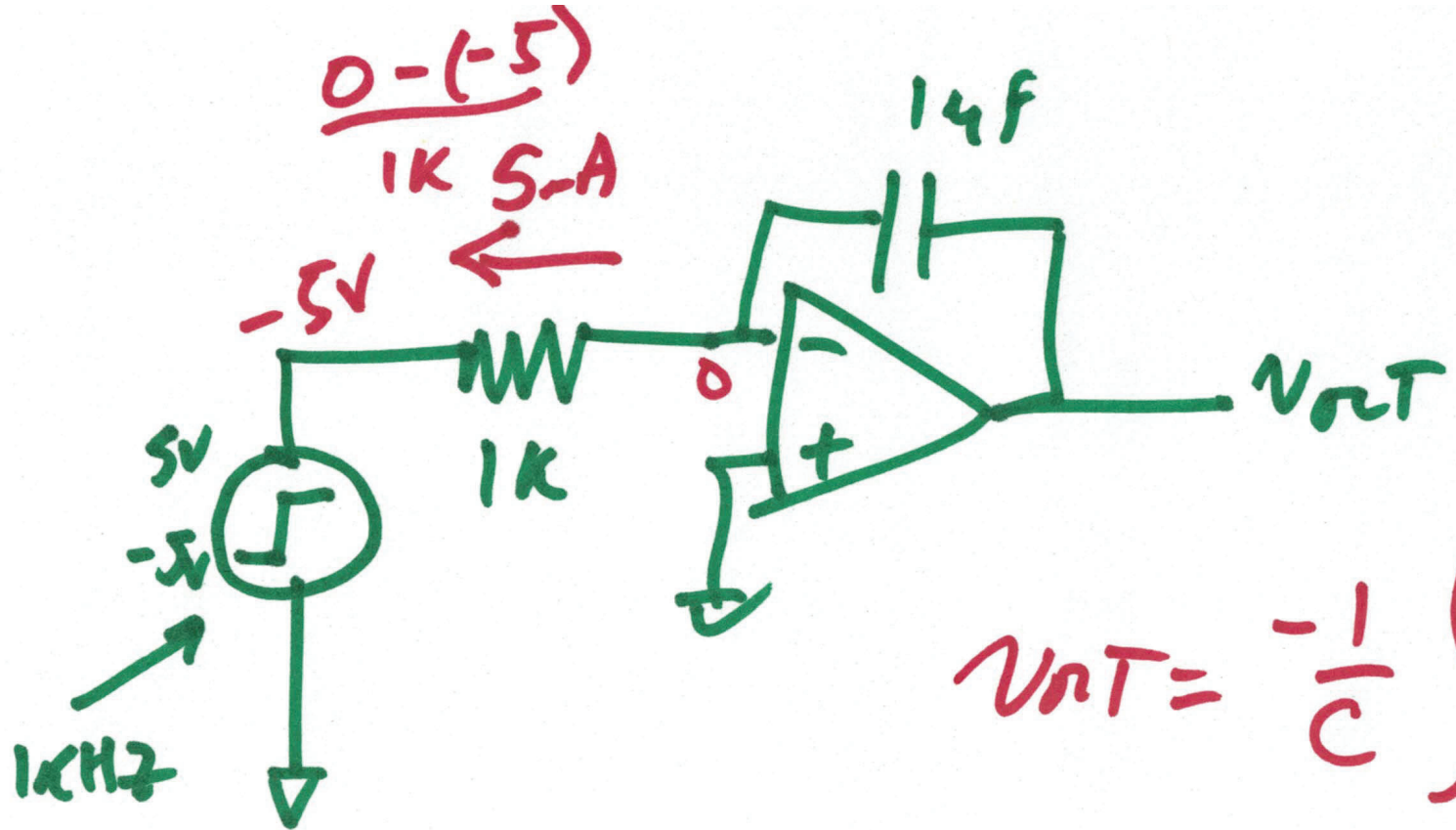
$$-\frac{1}{C} \int_0^t i_{in} dt = \int_0^t -\frac{1}{C} \cdot \frac{v_{in}}{R} \cdot dt = \int d v_{out} = v_{out}$$



$$V_{out} = -\frac{1}{C} \int_0^t 5\mu A \cdot dt$$

$$= -\frac{5\mu A}{14F} \cdot t$$

$$V_{out} = -\frac{5V}{ms} \cdot t$$

