

EE 220 circuits 1

Lecture 22

NOV. 16, 2020


micron = 10^{-6} meters

ITIC


DRAW

$CV = Q$
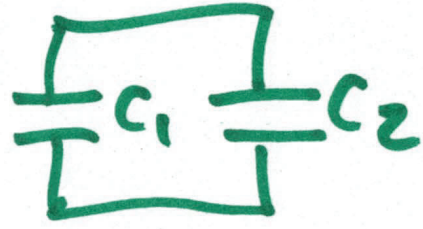
$$V_f = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$



$$\frac{1}{C_1 + C_2}$$

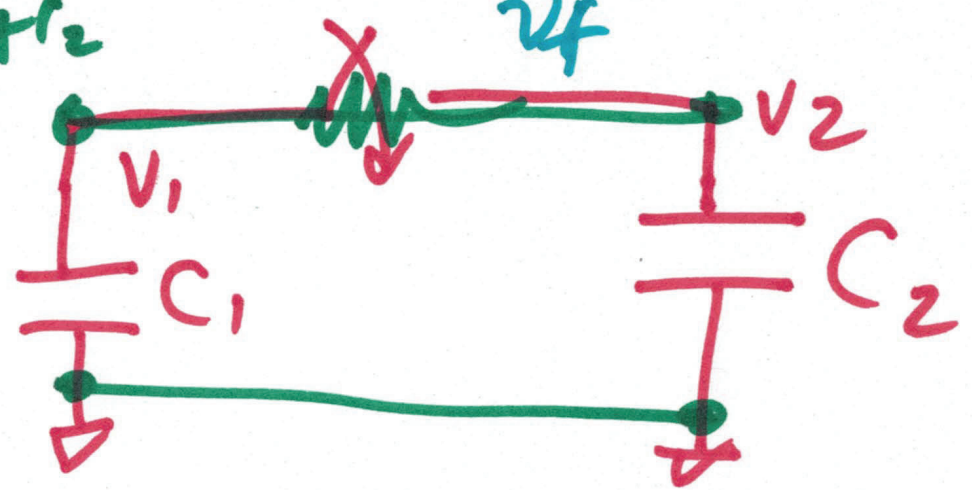


- a = 10^{-18}
- f = 10^{-15}
- p = 10^{-12}
- n = 10^{-9}
- μ = 10^{-6}

$Q_1 = C_1 V_1$

$Q_2 = C_2 V_2$
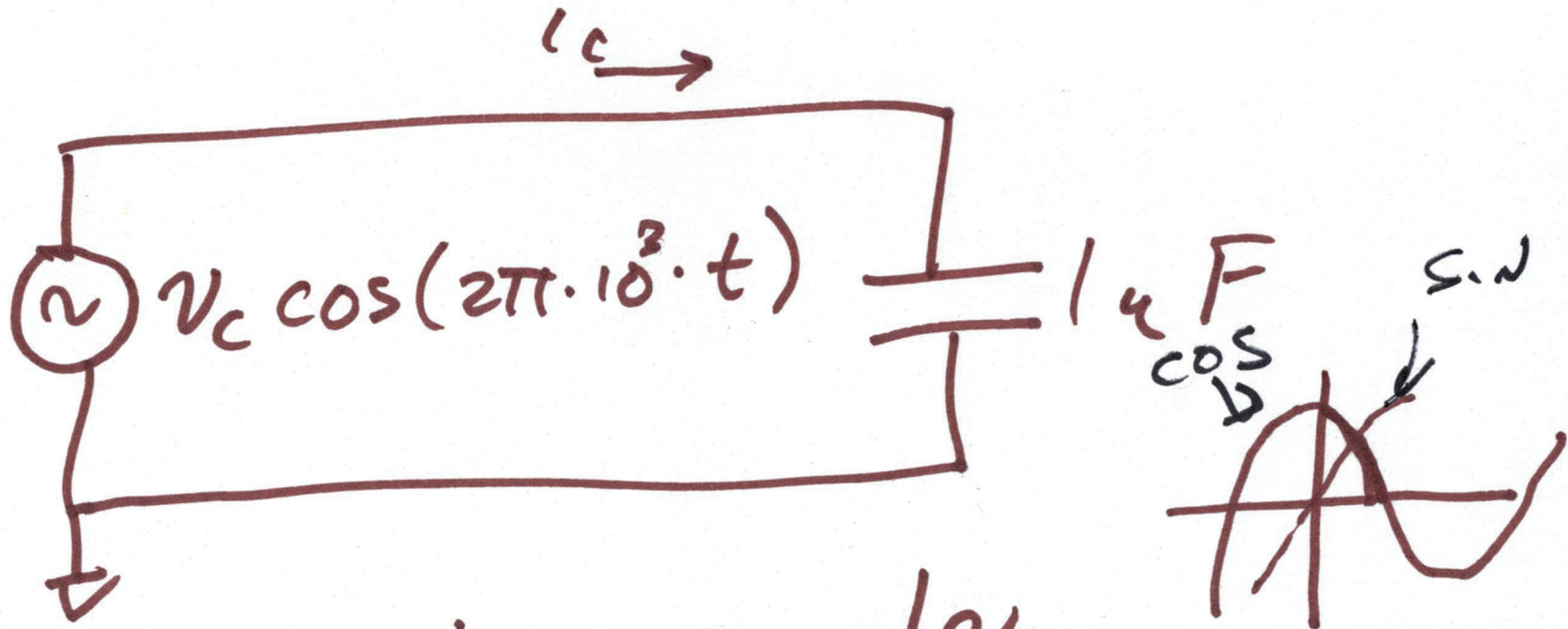
$$Q_1 + Q_2 = Q_f = (C_1 + C_2) \cdot V_f = C_1 V_1 + C_2 V_2$$



$$i_c = C \cdot \frac{dv_c}{dt}$$

$$= 10^{-6} \cdot \frac{d(\cos 2\pi \cdot 10^3 \cdot t)}{dt}$$

$$= -10^{-6} \cdot 2\pi \cdot 10^3 \cdot \sin(2\pi \cdot 10^3 \cdot t) = -10^{-6} \cdot (\sin 2\pi \cdot 10^3 \cdot t) \cdot$$

$$\frac{d 2\pi \cdot 10^3 \cdot t}{dt}$$

$$v_i(t) = V_c \cos(2\pi \cdot 1\text{kHz} \cdot t)$$

$$i_d(t) = -2\pi \cdot 10^{-3} \text{ S} \cdot \sin(2\pi \cdot 10^3 \cdot t)$$

$$i_{d,r} = -2\pi \cdot 10^{-3} \cdot \cos(2\pi \cdot 10^3 \cdot t + 90)$$


← earlier
later →
+ phase
- phase

$$\frac{i_c(t)}{2\pi f \cdot C} = \frac{i_c}{\omega C}$$

$$i_c(t) = \frac{2\pi \cdot 10^{-3}}{2\pi f \cdot C} \cos(2\pi \cdot 10^3 \cdot t + 270^\circ)$$

$$= 2\pi \cdot 10^{-3} \cos(2\pi \cdot 10^3 \cdot t - 90)$$

$$\omega = 2\pi f$$

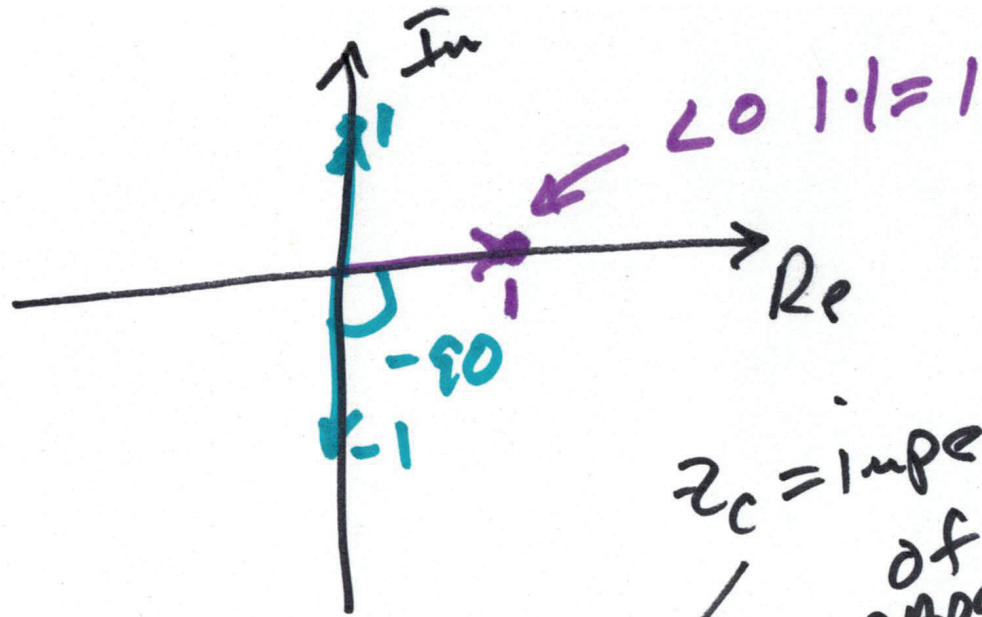

$$1 + j0 \rightarrow \sqrt{1^2 + 0^2} = 1$$

$$\angle = \tan^{-1} \frac{0}{1} = 0$$

$Z_C = \text{impedance of capacitor}$

$$0 + j \cdot 1 \rightarrow \sqrt{0^2 + 1^2} = 1$$

$$\angle = \tan^{-1} \frac{1}{0} = 90^\circ$$

$$V_C = I_C \cdot \frac{1}{j\omega C}$$



$$\frac{1}{j} \cdot \frac{j}{j} = \frac{j}{-1}$$

$$= -j \rightarrow$$


$$0 - j = 0 + j(-1)$$

$$|1| = 1$$
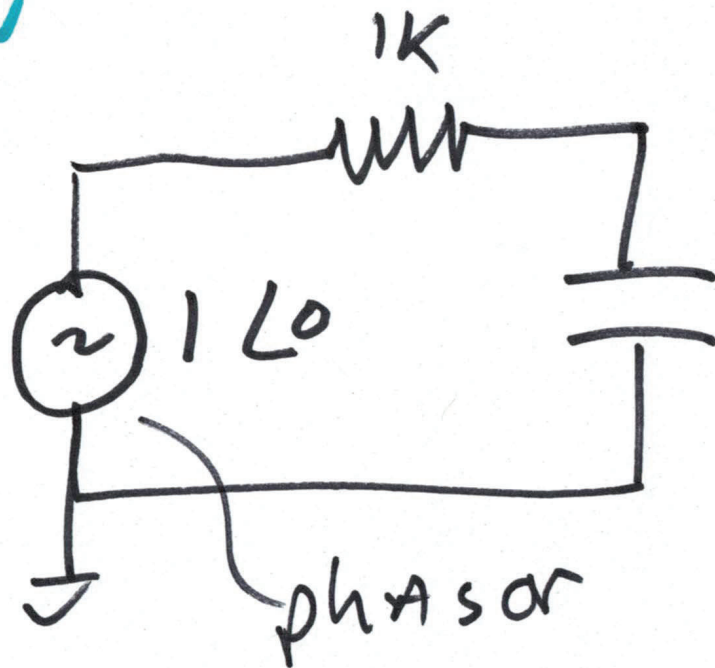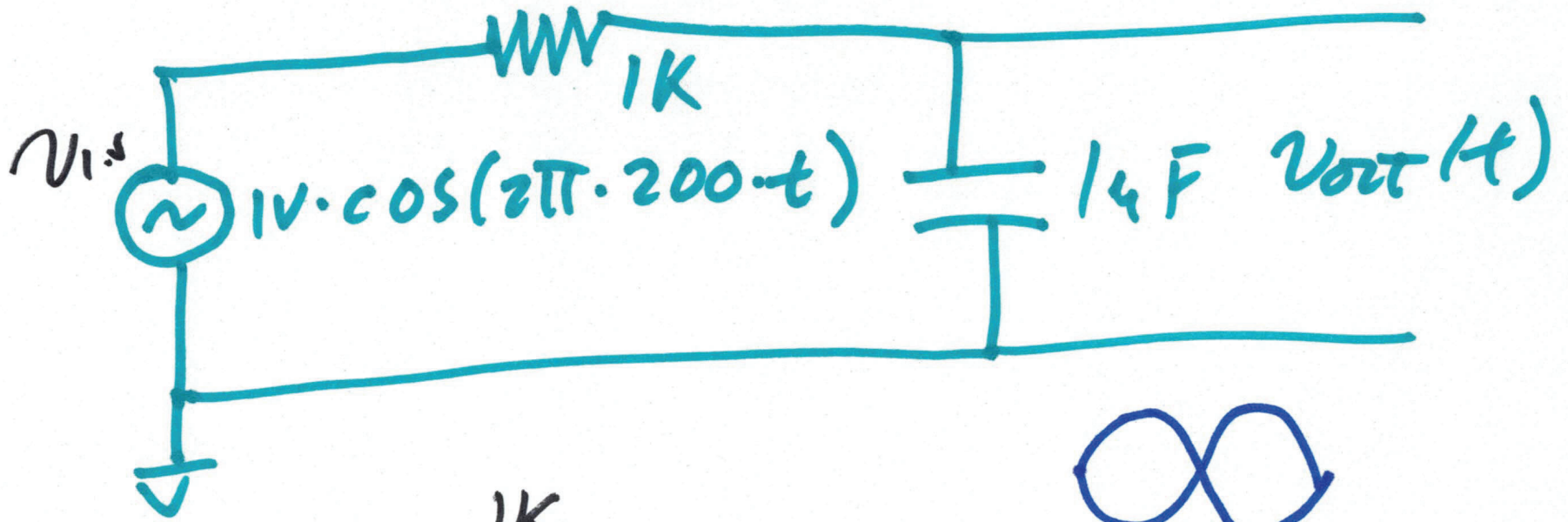
$$\angle = \tan^{-1} \frac{-1}{0} = -90^\circ$$


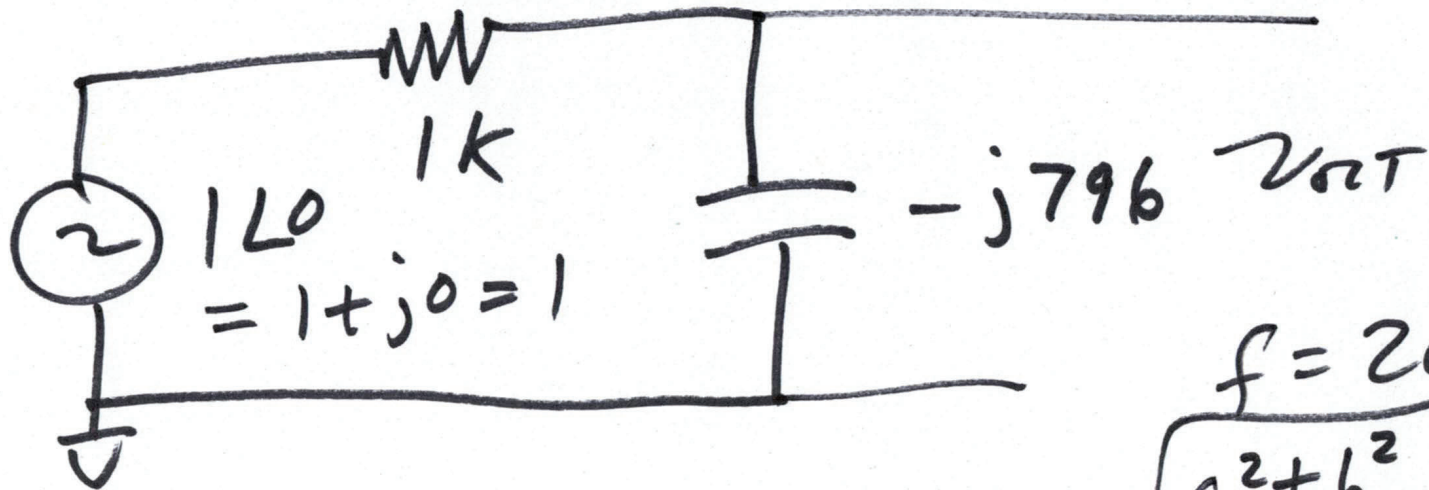
$$\begin{aligned}
 & \frac{1}{j \cdot 2\pi \cdot 200 \cdot 10^{-6}} \\
 &= \frac{-j}{1.256 \cdot 10^{-3}} \\
 &= -j796
 \end{aligned}$$



$$V_{out} = 1\angle 0 \cdot \frac{-j796}{1000 - j796}$$

$$f = 200$$

$$\frac{\sqrt{a^2 + b^2}}{\sqrt{c^2 + d^2}} \angle \tan^{-1} \frac{b}{a} - \frac{d}{c}$$

$$x + jy = \sqrt{x^2 + y^2} \angle \tan^{-1} \frac{y}{x}$$

$$a + jb + c + jd = a + c + j(b + d)$$

$$\frac{a + jb}{c + jd} = \frac{\sqrt{a^2 + b^2} \angle \tan^{-1} \frac{b}{a}}{\sqrt{c^2 + d^2} \angle \tan^{-1} \frac{d}{c}}$$

$$\begin{aligned}
 V_{out} &= (1 + j0) \cdot \frac{0 + j(-796)}{1000 + j(-796)} \quad \angle -90^\circ \\
 &= \sqrt{1^2 + 0^2} \cdot \frac{\sqrt{0^2 + (-796)^2} \angle \tan^{-1} \frac{-796}{0}}{\sqrt{1000^2 + (-796)^2} \cdot \tan^{-1} \frac{-796}{1000}}
 \end{aligned}$$

$$\begin{aligned}
 V_{out} &= \frac{796 \angle -90^\circ}{1,278 \angle -38.5^\circ} \\
 &= \frac{796}{1,278} \angle -90^\circ - (-38.5^\circ)
 \end{aligned}$$

$$V_{out} = .623 \angle -51.5^\circ$$

$$v_{out}(t) = 0.623 \cos(2\pi \cdot 200 \cdot t - 51.5^\circ)$$


$$v_{in} = 1 \cdot \cos(2\pi \cdot 200 \cdot t) \quad \sqrt{\frac{t_d}{T}}$$


$$\theta = \frac{t_d}{T} \cdot 360, \quad T = \frac{1}{f}$$

$$T = 5 \text{ms}$$

$$51.5 = 200 \cdot t_d \cdot 360$$

$$t_d = 0.715 \text{ms}$$

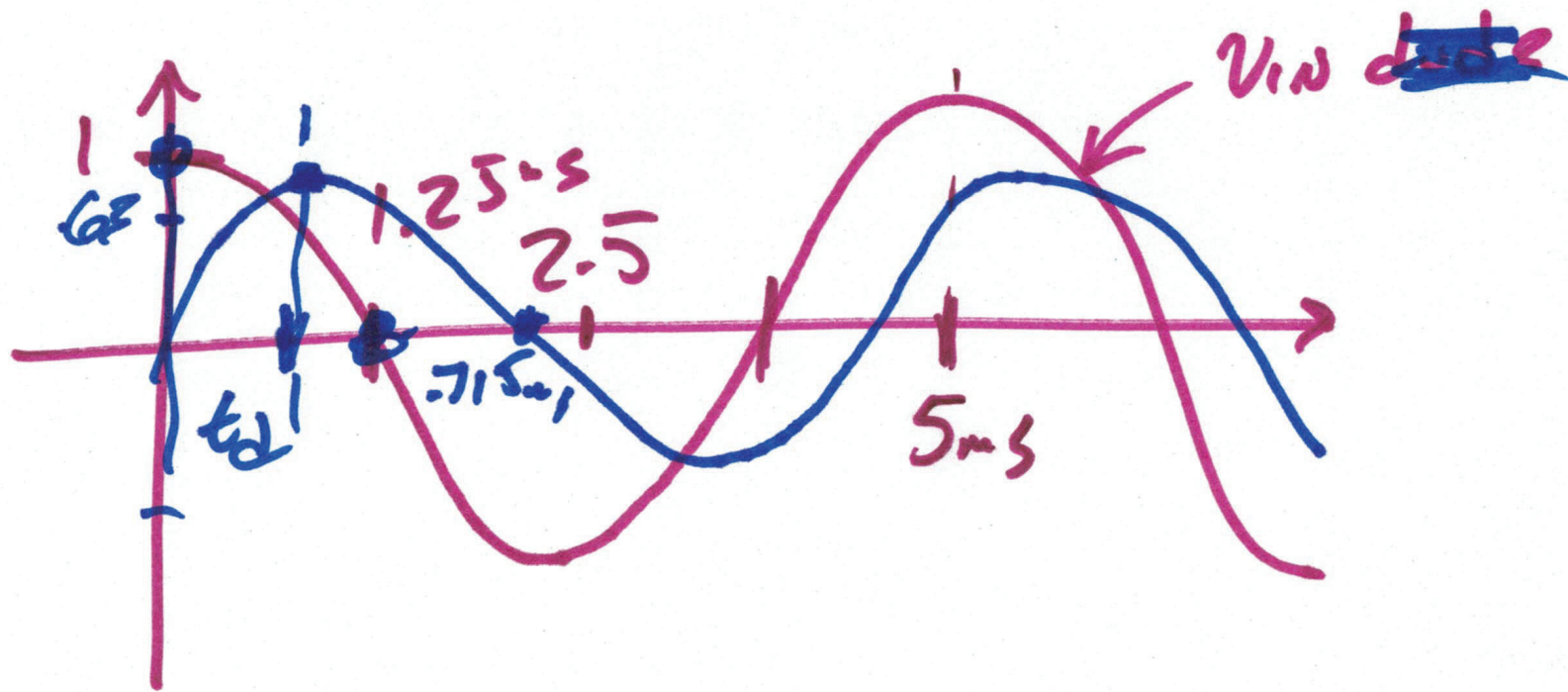


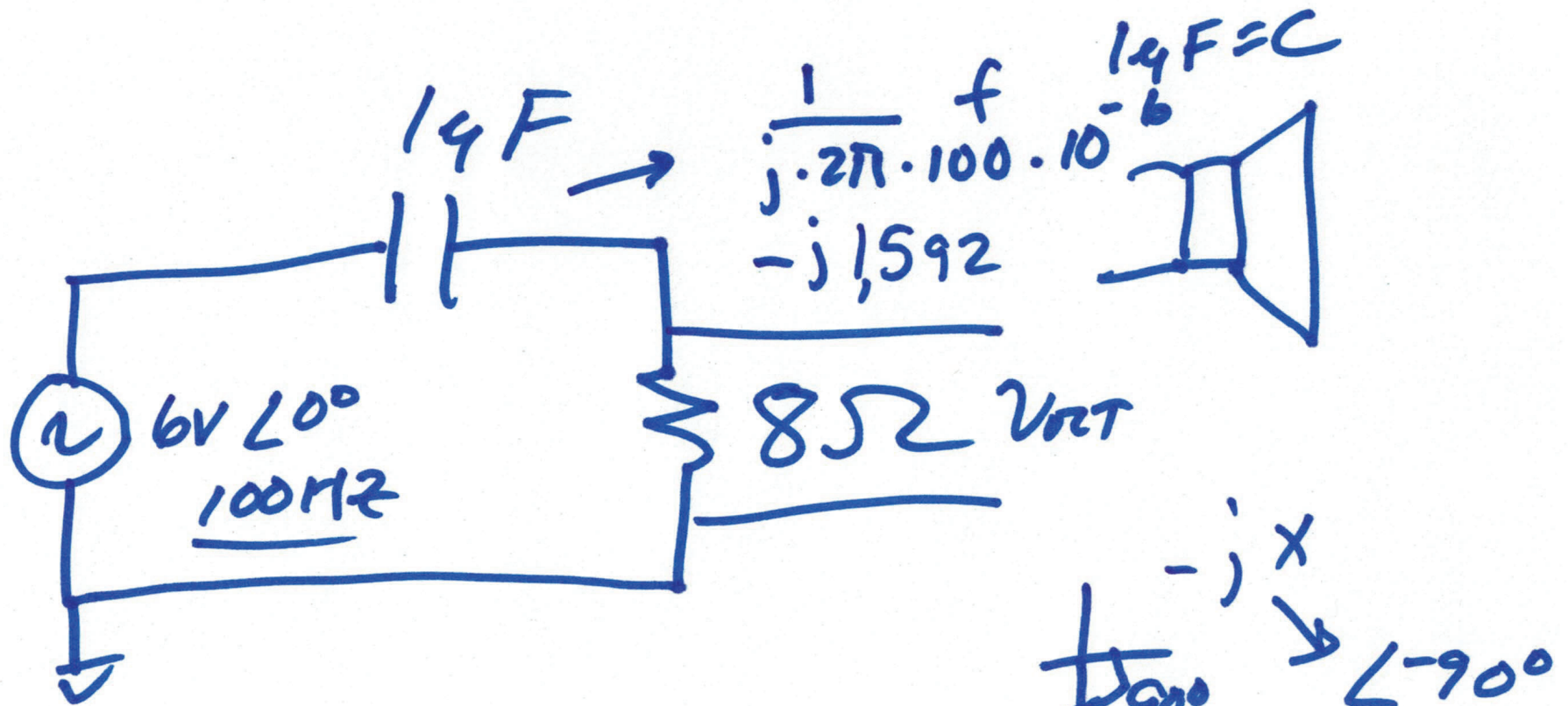

$$V_{th} = \frac{6 \angle 0^\circ}{6 + j0} \cdot \frac{8}{8 + j(-1.592)}$$

$$\approx 6 \cdot \frac{8 \angle 0^\circ}{1.592 \angle -90^\circ}$$

$$= 0.03V \angle 90^\circ$$

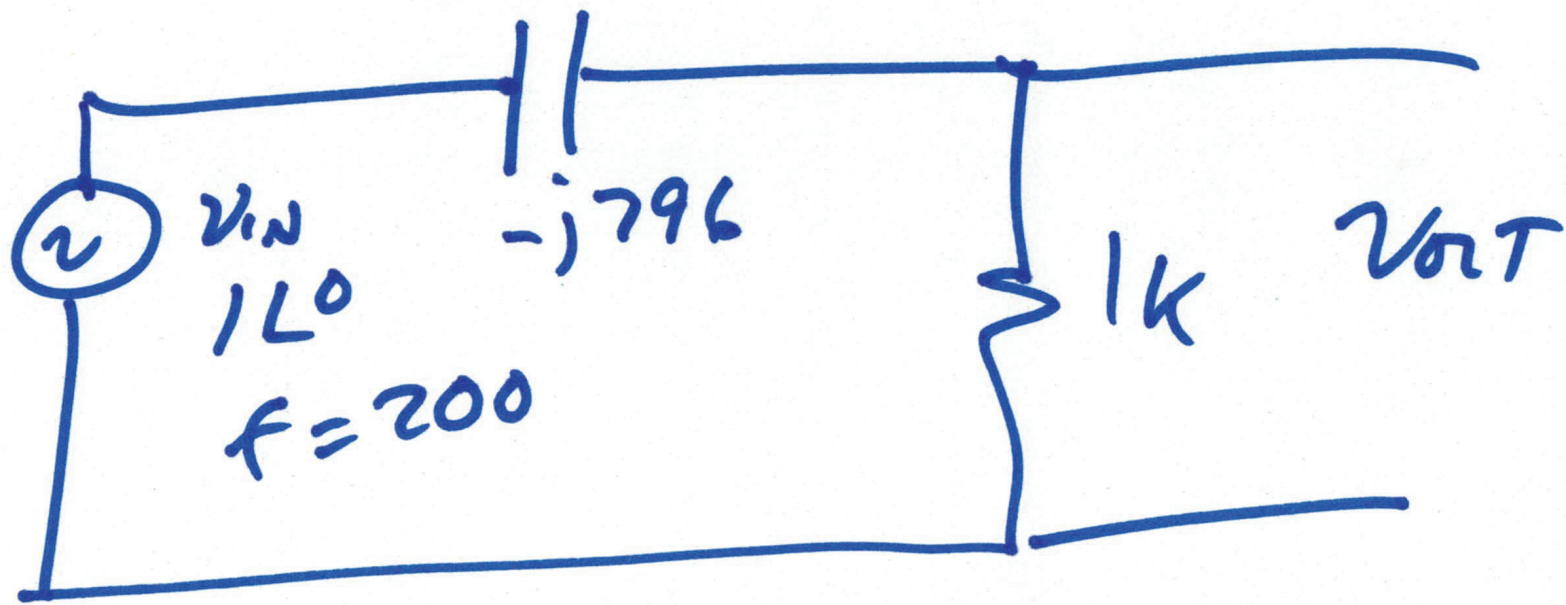

$$v_{out} = 1 \cdot \frac{1k}{1k + j(-796)}$$

$$v_{out} = .782 \cos(2\pi \cdot 200 \cdot t + 38.5^\circ)$$

$$38.5 = \frac{t_d}{5\mu s} \cdot 360$$

$$t_d = .53\mu s$$

$$= .782 \angle 38.5^\circ$$