
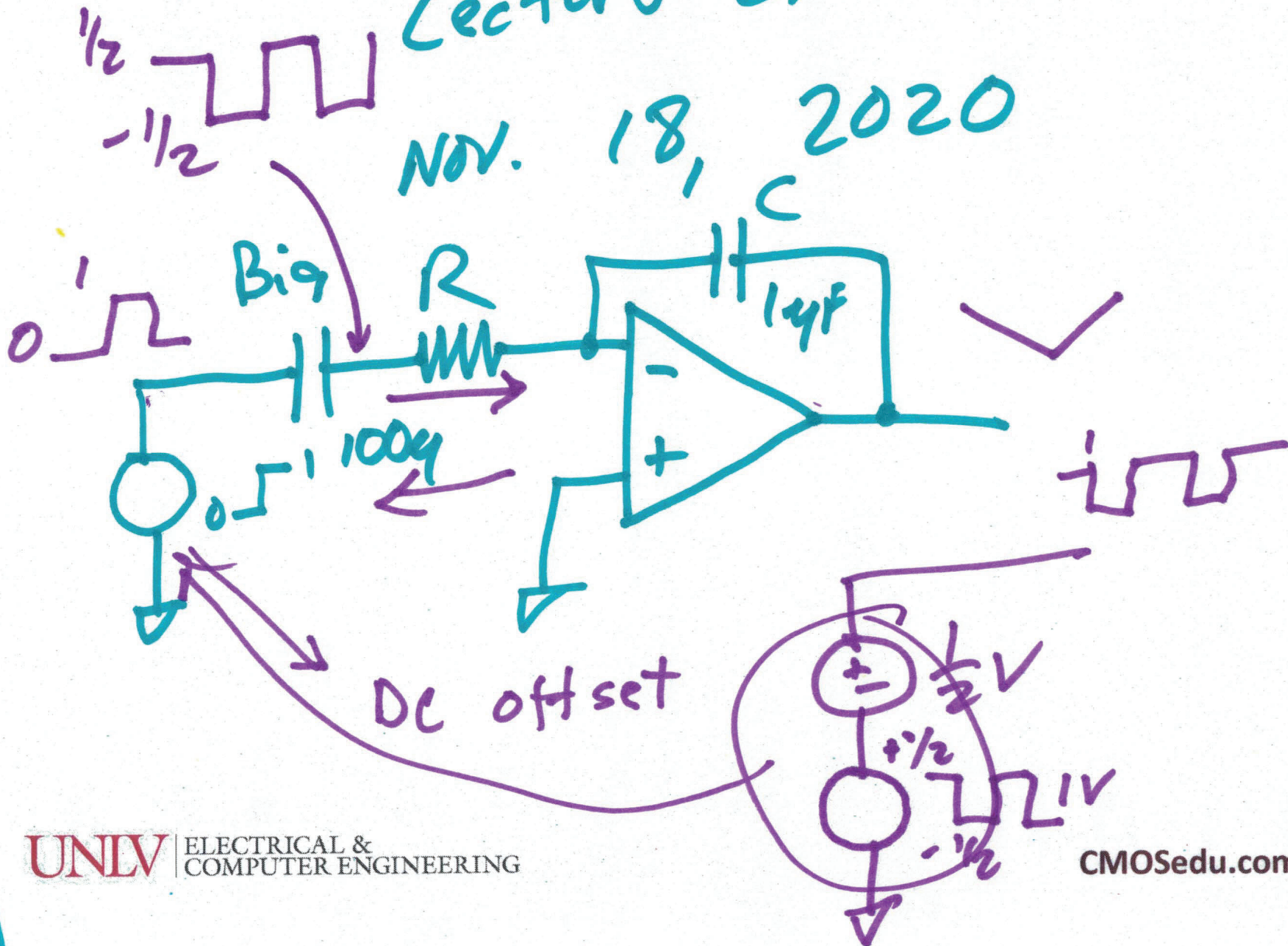


EE 220 circuits 1

Lecture 23

Nov. 18, 2020

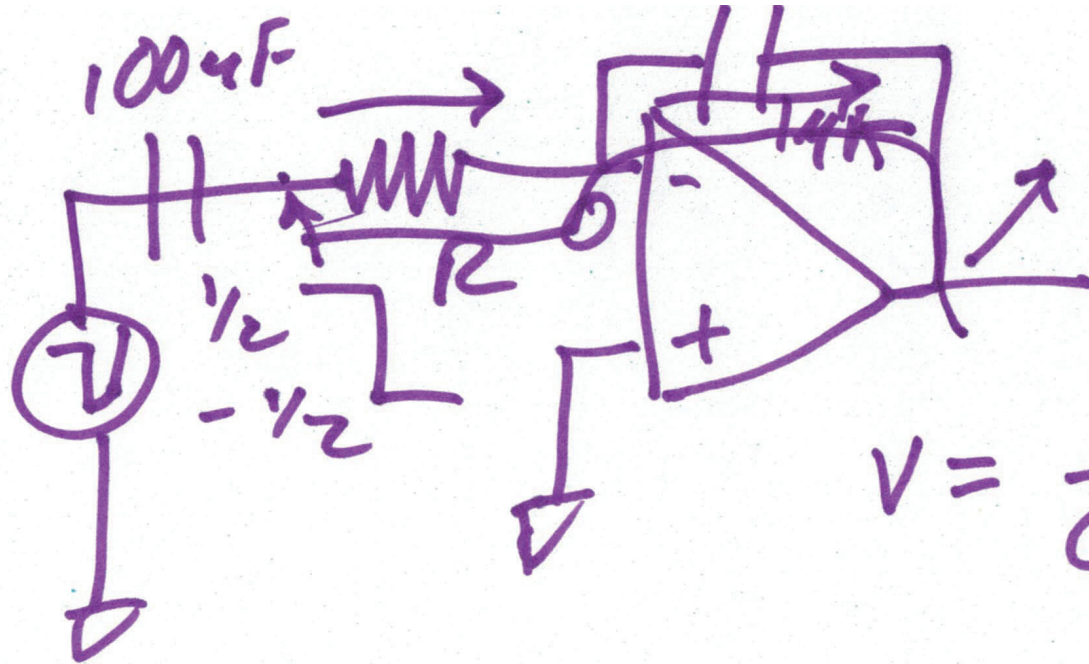




$$10\text{KHz} = \frac{1}{T}$$

$$T = 100\mu\text{s}$$

$$V = \frac{1}{C} \int_0^t i \cdot dt$$

$$i = \frac{1/2}{R}$$

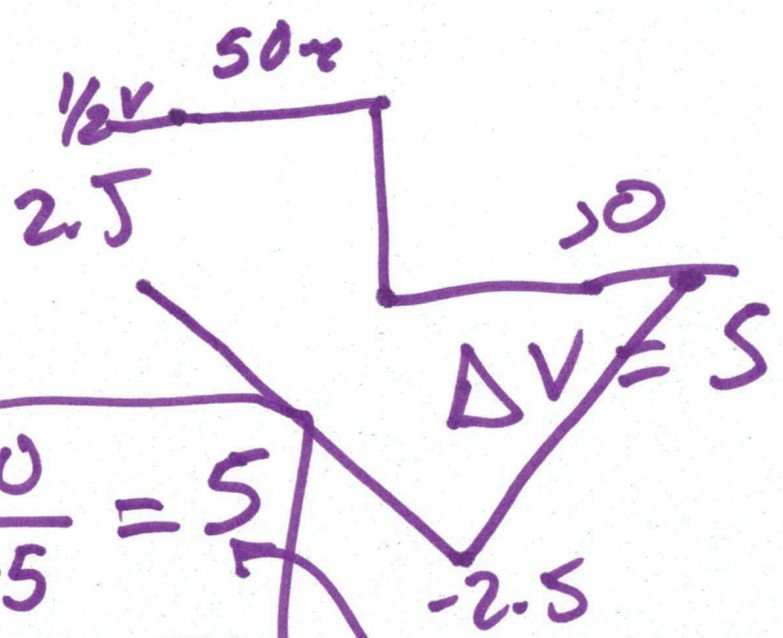


$$R = \frac{50}{2.5} = 20$$

$$5 = \frac{1}{10^{-6}} \int_0^{50\text{ns}} \frac{1}{R} \cdot dt$$

$$5 = \frac{1}{2 \cdot 10^{-6}} \cdot \frac{1}{R} (50\text{ns} - 0)$$

2)

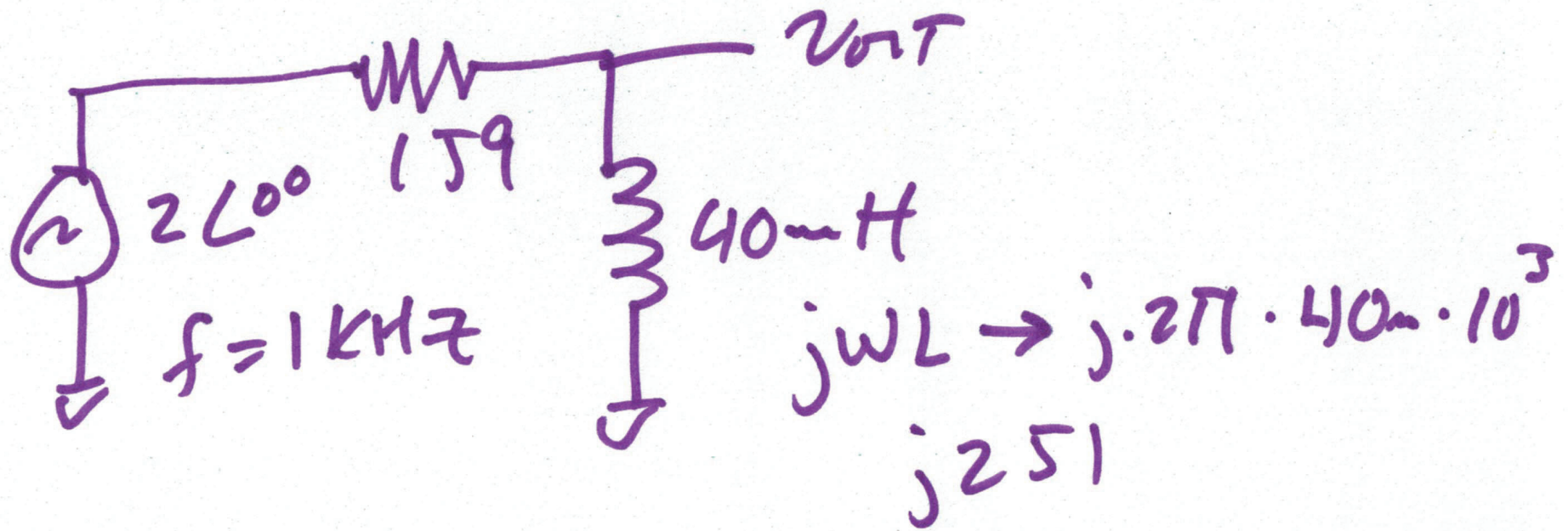

$$V_{out} = 2 \cdot \frac{0 + j251}{159 + j251}$$

$$V_{out} = \frac{0 + j \cdot 502}{159 + j251}$$

$$v_{out} = \frac{502 \angle 90^\circ}{297 \angle 57.6^\circ}$$


$$v_{out} = 1.69 \angle 32.4^\circ$$

$$v_{in} = 2 \sin(2\pi \cdot 10^3 \cdot t)$$

$$v_{out} = 1.69 \sin(2\pi \cdot 10^3 \cdot t + 32.4^\circ)$$




$$32.4 = \frac{t_d \cdot 360}{1 \mu s} \rightarrow t_d = 90 \text{ ns}$$

4)

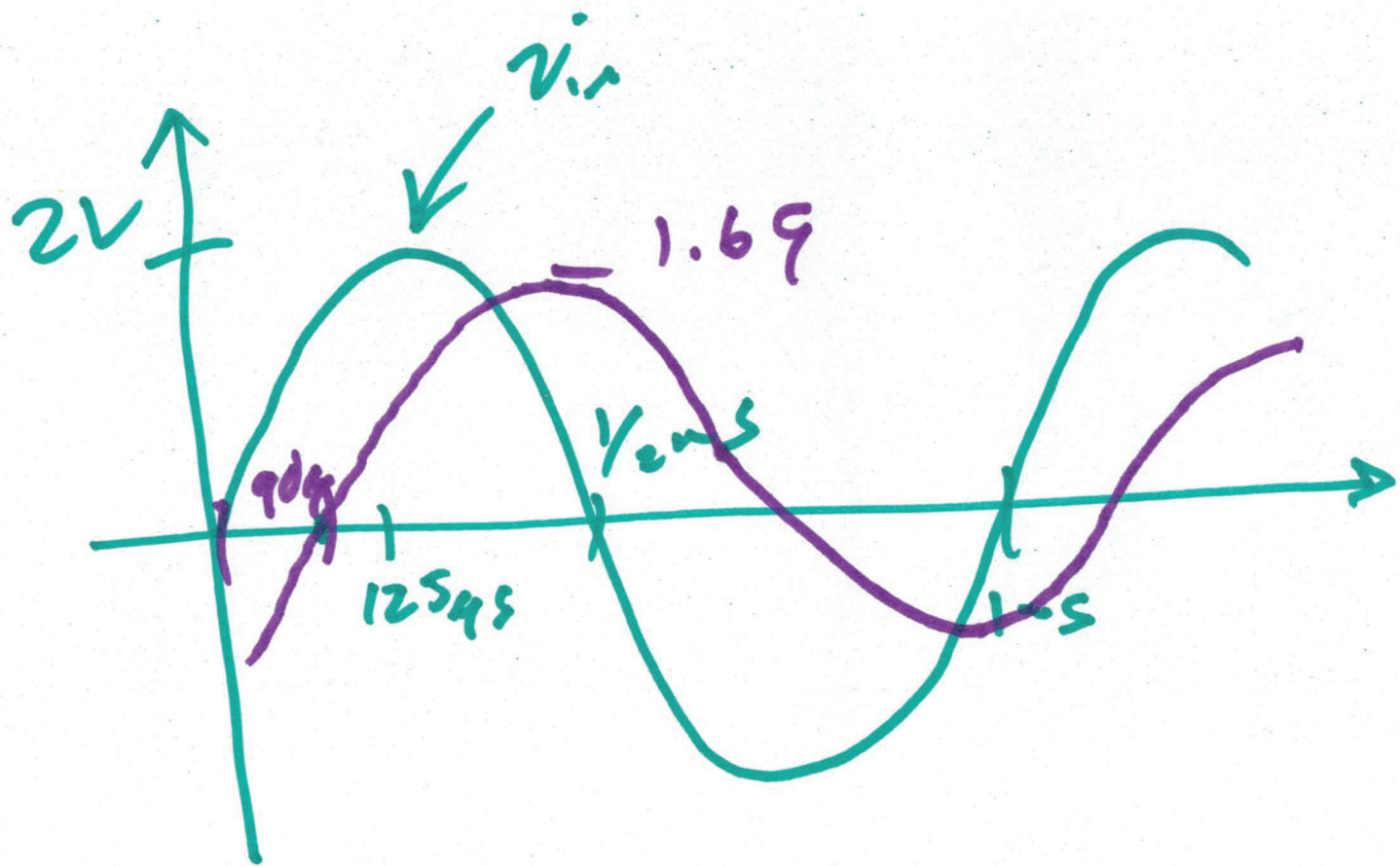

120V


Rms
value
of
square
wave

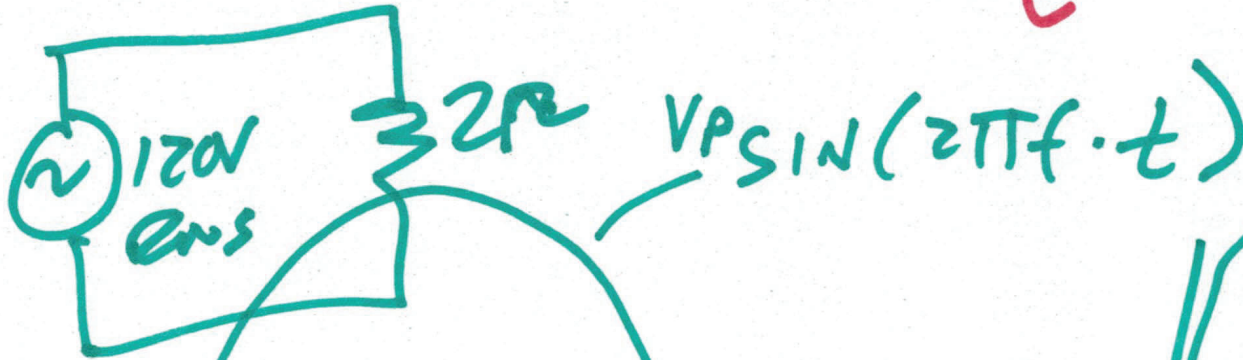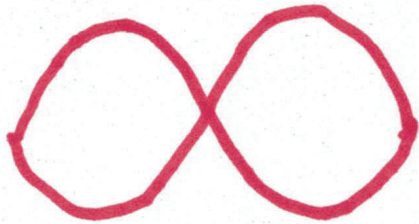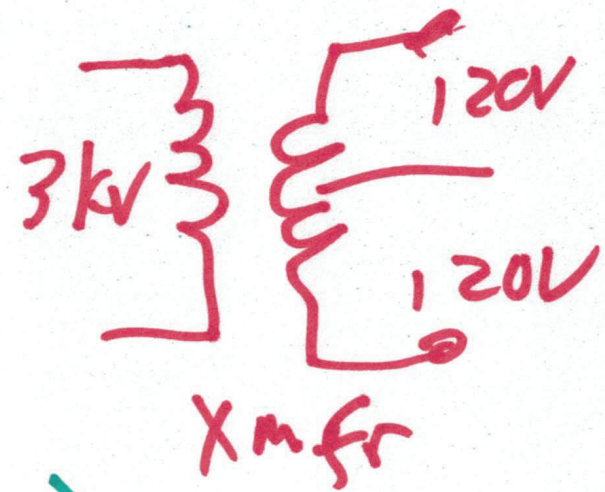

$$\frac{1}{T} \int_0^T V_p^2 \cdot \sin^2(2\pi f t) \cdot dt$$

b)
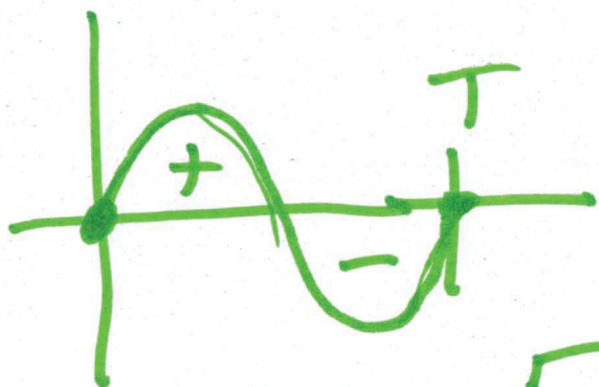
$$V_{Rms} = \sqrt{\frac{1}{T} \int_0^T V_p^2 \sin^2(2\pi f t) dt}$$



$$\sin^2 x = \frac{1 - \cos 2x}{2}$$

$$f = \frac{1}{T}$$

$$= \sqrt{\frac{V_p^2}{2T} \int_0^T (1 - \cos 2 \cdot 2\pi f t) dt}$$

$$V_{Rms} = \sqrt{\frac{V_p^2}{2} \cdot \frac{1}{T} \left(T + \frac{\sin(2\pi f \cdot T)}{2\pi f} \right)}$$


1)

$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

$$120V = \frac{V_p}{\sqrt{2}} \quad V_p \approx 170V$$
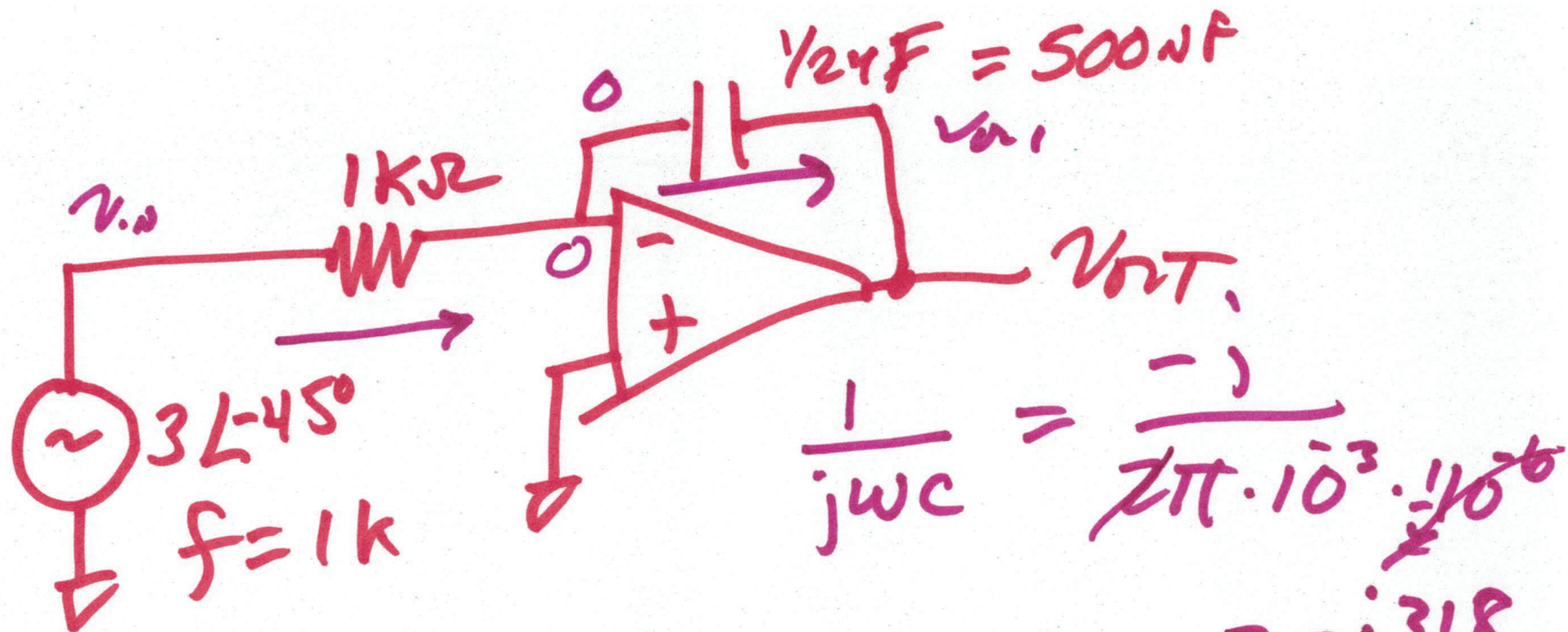
$$v_{wall}(t) = 170 \cdot \sin(2\pi \cdot 60 \cdot t)$$





$$\frac{1}{j\omega C} = \frac{-j}{2\pi \cdot 10^3 \cdot 5 \cdot 10^{-7}} = -j318$$

$$v_{in} = 3 \sin(2\pi \cdot 1 \text{ kHz} \cdot t - 45^\circ)$$

$$\frac{3 \angle -45^\circ}{1 \text{ k}} = 3 \text{ mA} \angle -45^\circ = \frac{0 - 2.121j}{j\omega C}$$

$$\frac{1}{j} = \frac{1}{\sqrt{-1}} \cdot \frac{\sqrt{-1}}{\sqrt{-1}} = \frac{j}{-1} = -j$$


9)

$$3 \mu\text{A} \angle -45^\circ = \frac{-2\sqrt{\pi}}{-j318} = \frac{2\sqrt{\pi}}{318 \angle 90^\circ}$$

$$V_{out} = 318 \angle 90^\circ \cdot 3 \mu\text{A} \angle -45^\circ$$
$$= .954 \angle 45^\circ$$

$$V_{out} = .954 \sin(2\pi \cdot 10^3 t + 45^\circ)$$

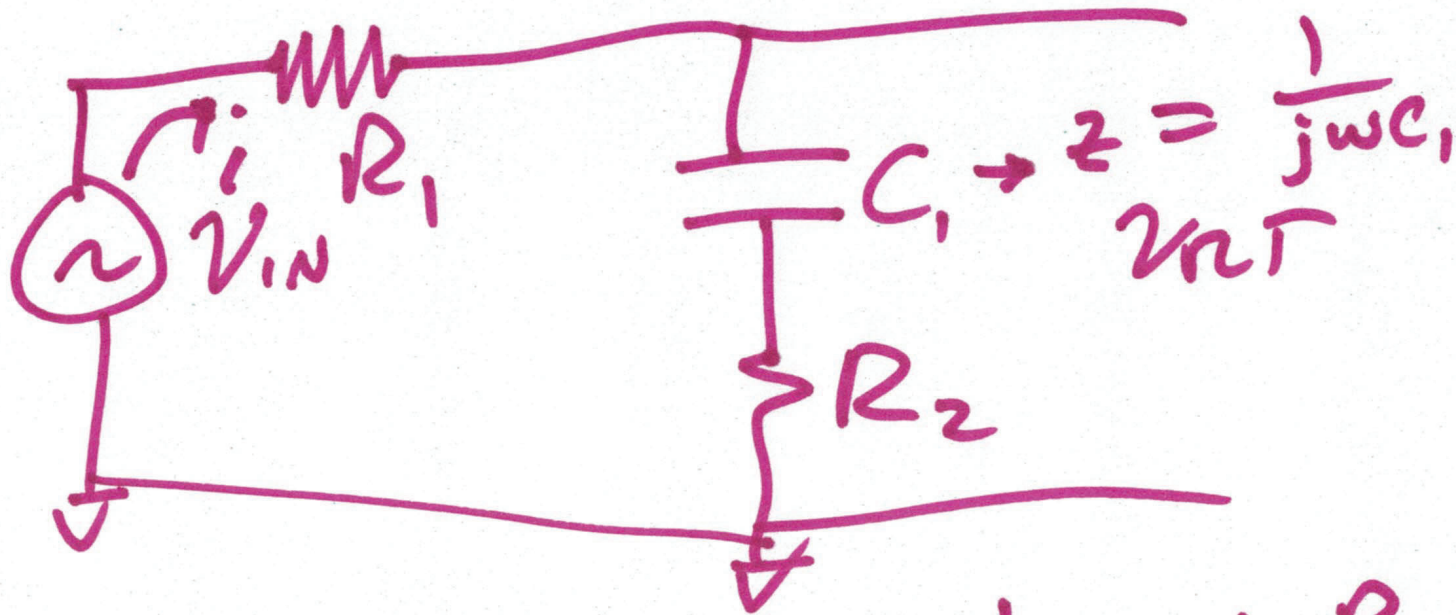
$$45 = \frac{t_d}{1 \mu\text{s}} \cdot 360 \rightarrow t_d = 125 \mu\text{s}$$



$$v_{out} = v_{in} \cdot \frac{\frac{1}{j\omega C_1} + R_2}{\frac{1}{j\omega C_1} + R_2 + R_1}$$

$$i_{in} = \frac{v_{in}}{R_1 + R_2 + \frac{1}{j\omega C_1}}$$

11)

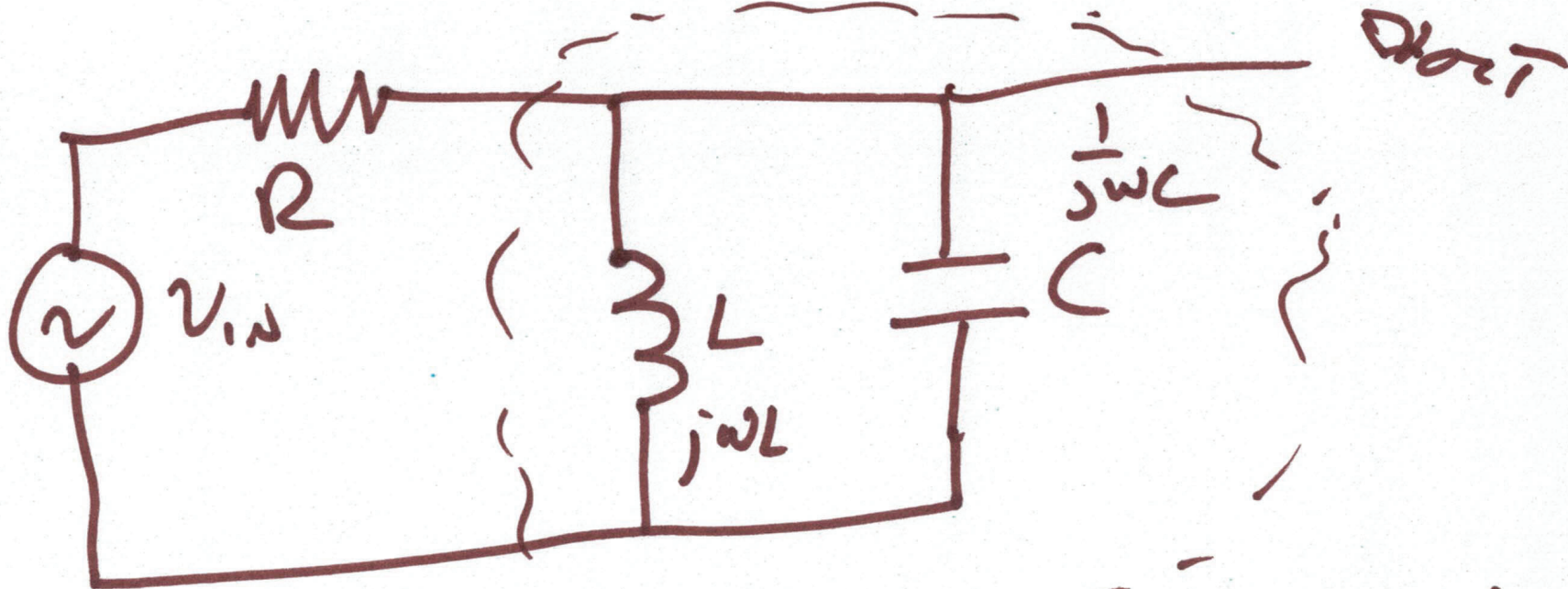

$$v_T = v_{in} \cdot \frac{z_{eq}}{R + z_{eq}}$$

$$z_{eq} = \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}}$$

$$\frac{j\omega L}{-\omega^2 LC + 1}$$

$$= \frac{j\omega L}{j\omega L \cdot j\omega C + 1}$$