

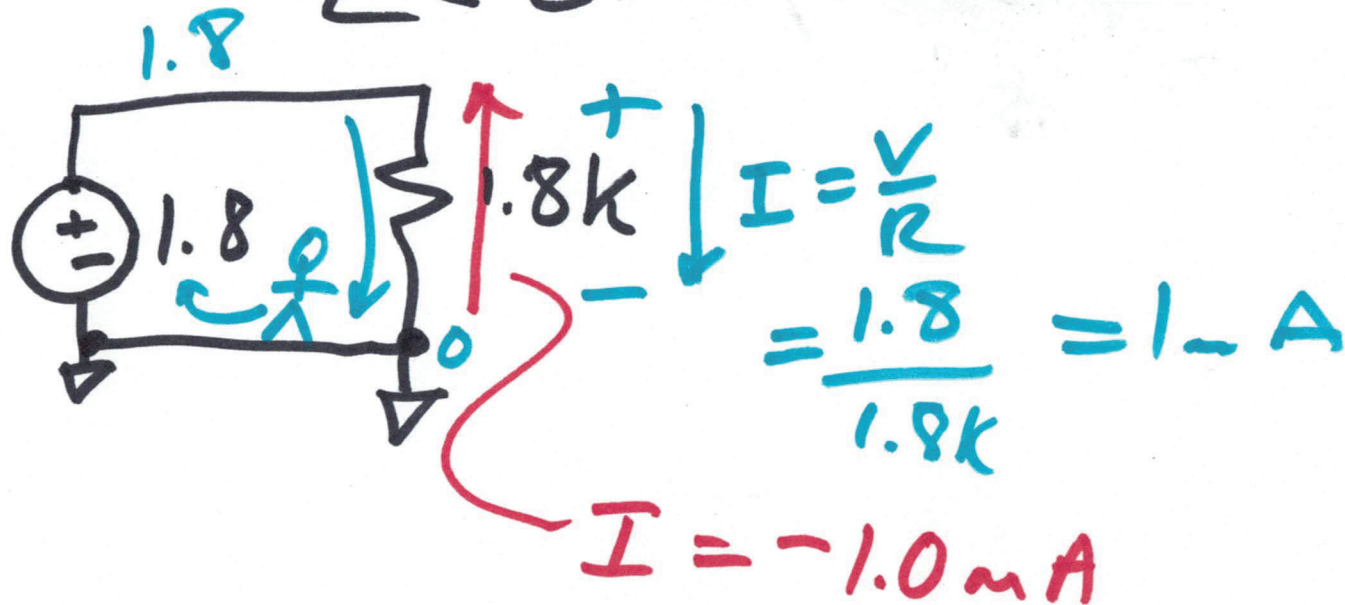



EE 220 circuits 1

August 26, 2020


Lecture 2

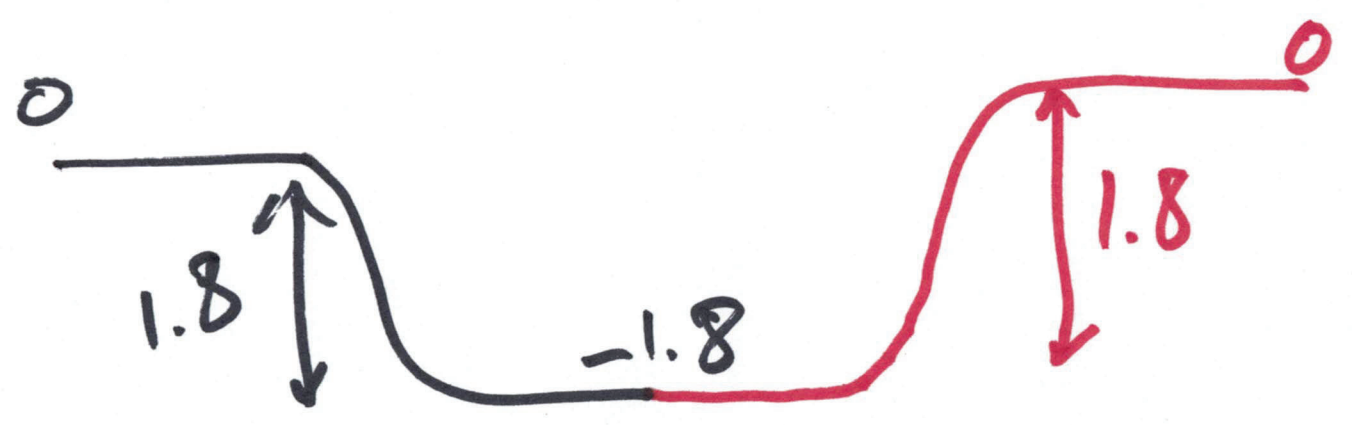

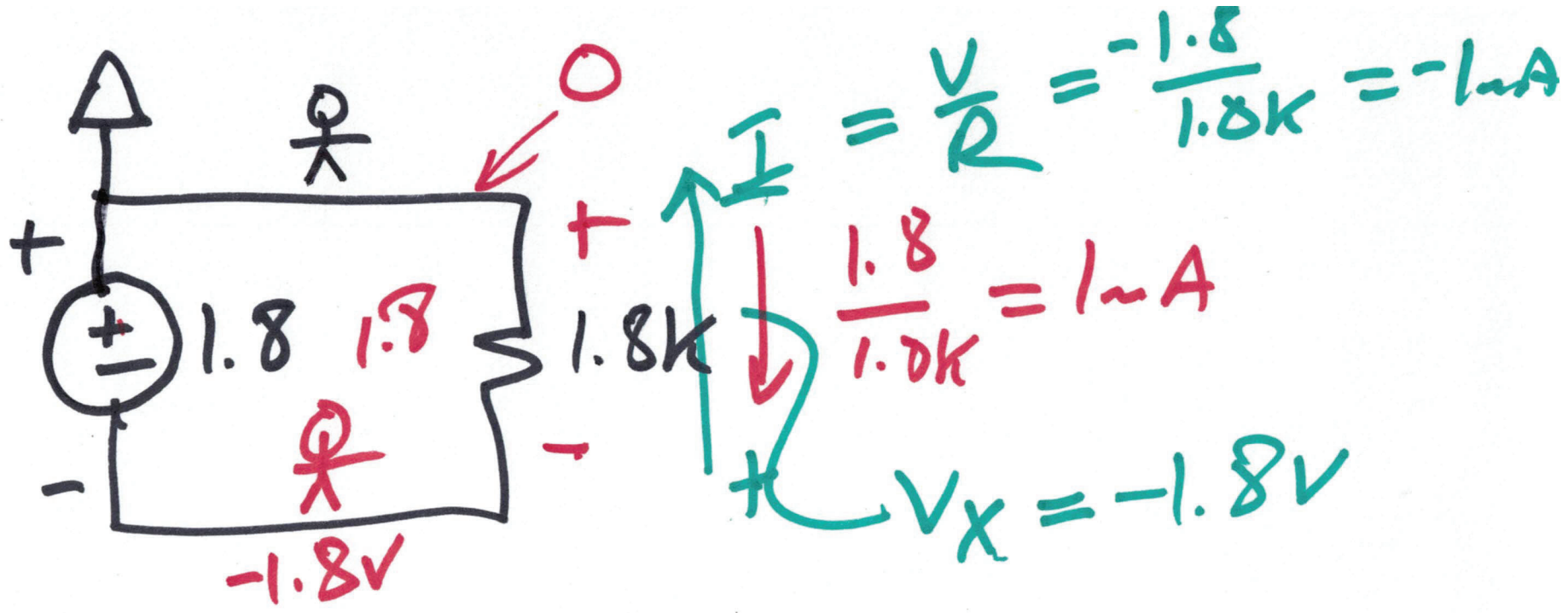

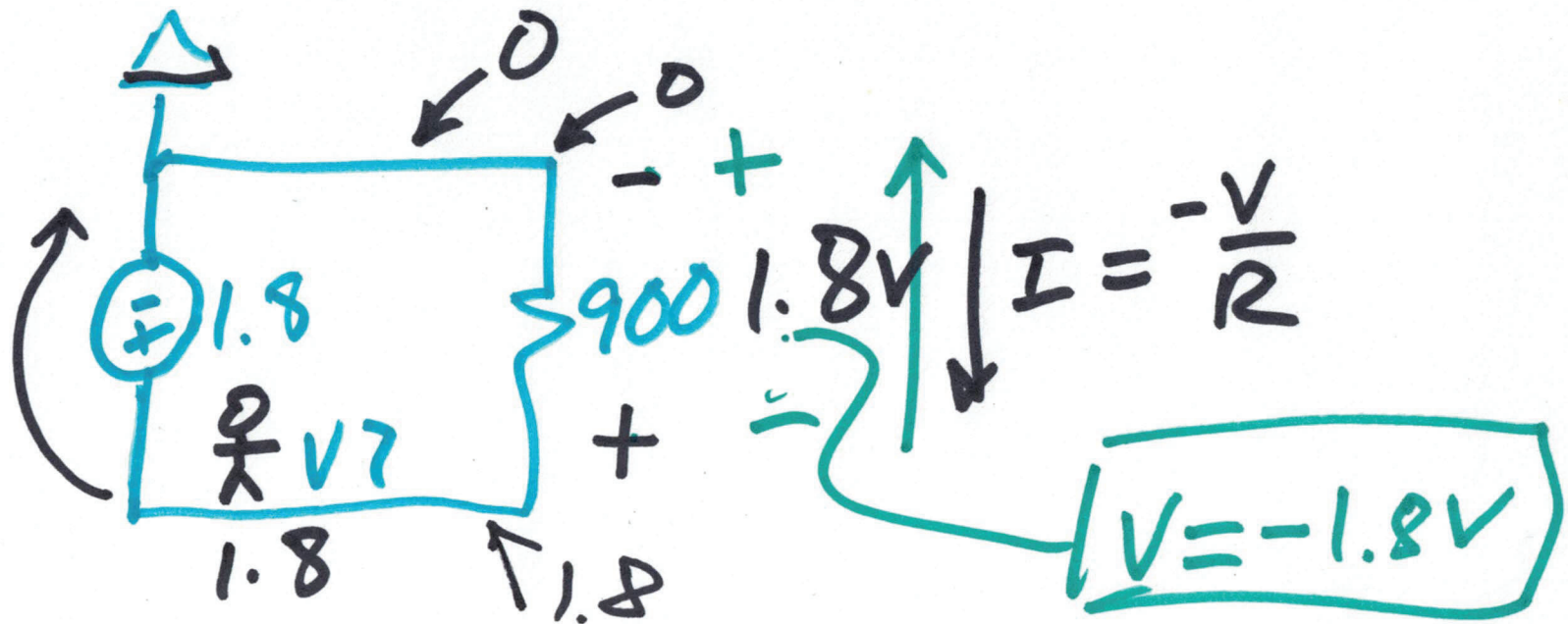

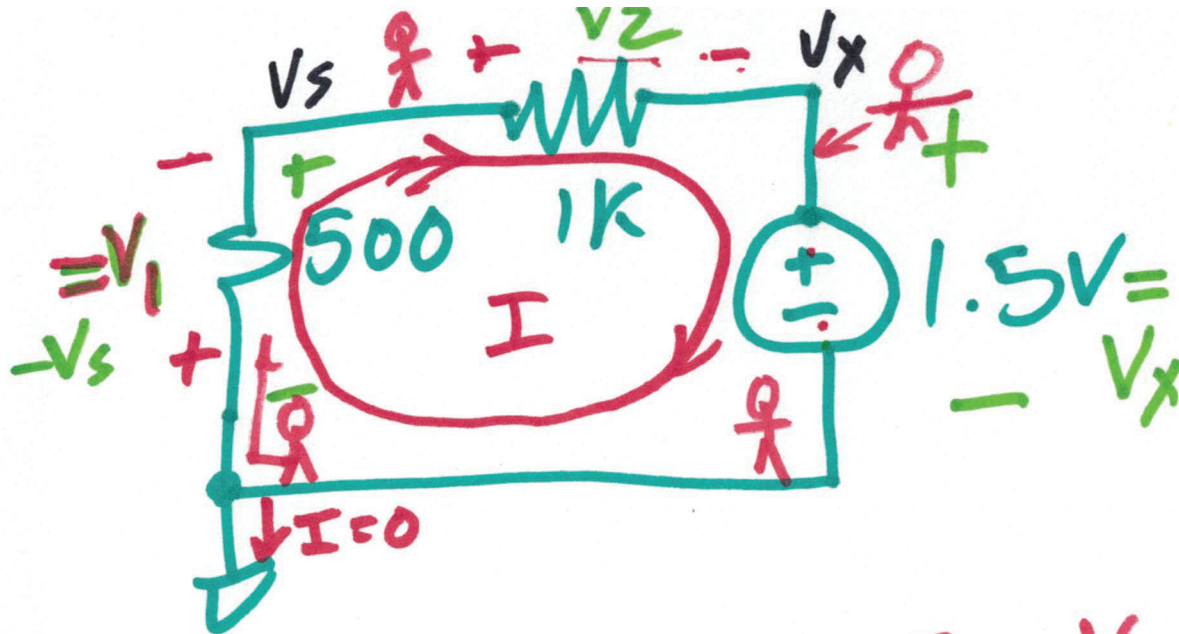
$$\begin{aligned}
 \downarrow \begin{matrix} + \\ - \end{matrix} V = IR & \quad \uparrow \begin{matrix} - \\ + \end{matrix} V = IR & \quad I = \frac{V}{R} = 2\mu A \\
 \downarrow \begin{matrix} - \\ + \end{matrix} V = -I \cdot R & & \quad \frac{1.8}{900} = 2\mu A
 \end{aligned}$$



$$\begin{aligned}
 +V &= IR \\
 \overline{V_1} &= I \cdot 500 \\
 V_2 &= I \cdot 1K \quad (OL)
 \end{aligned}$$
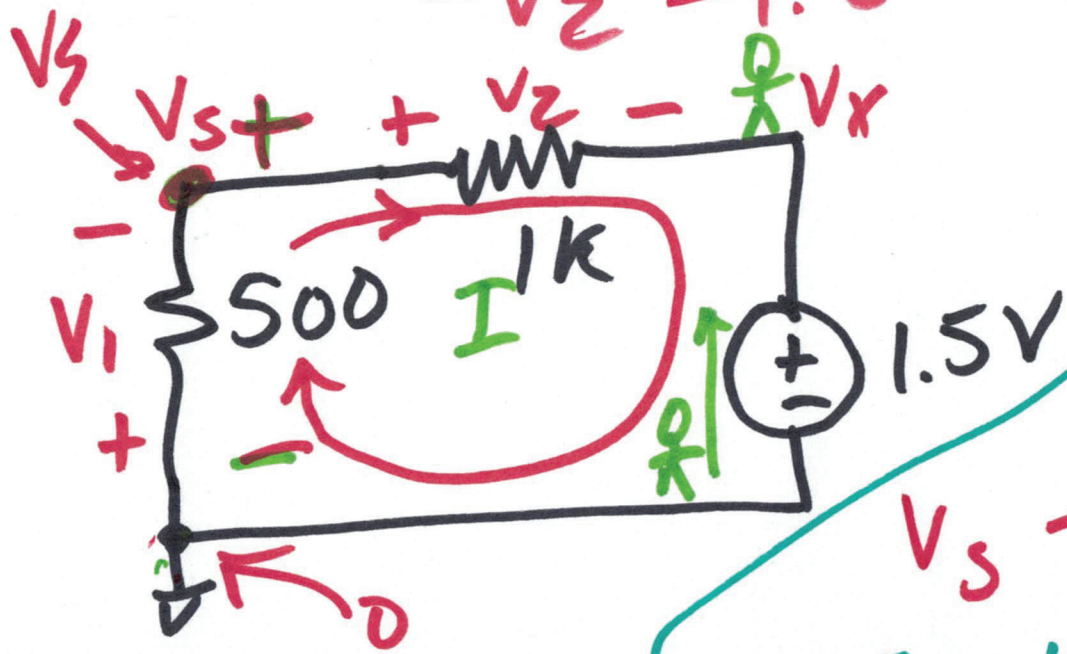
$$-V_2 - 1.5 - V_1 = 0 \quad (\text{KVL})$$




$$1.5 + \underbrace{I \cdot 1K}_{V_2} + \underbrace{I \cdot 500}_{V_1 = -V_S} = 0$$

$$V_S - 0 = 0 - V_1 = 0 - (-V_S)$$


$$1.5 + 1.5K \cdot I = 0$$

$$I = \frac{-1.5}{1.5K} = \boxed{-1\mu A = I}$$

4)

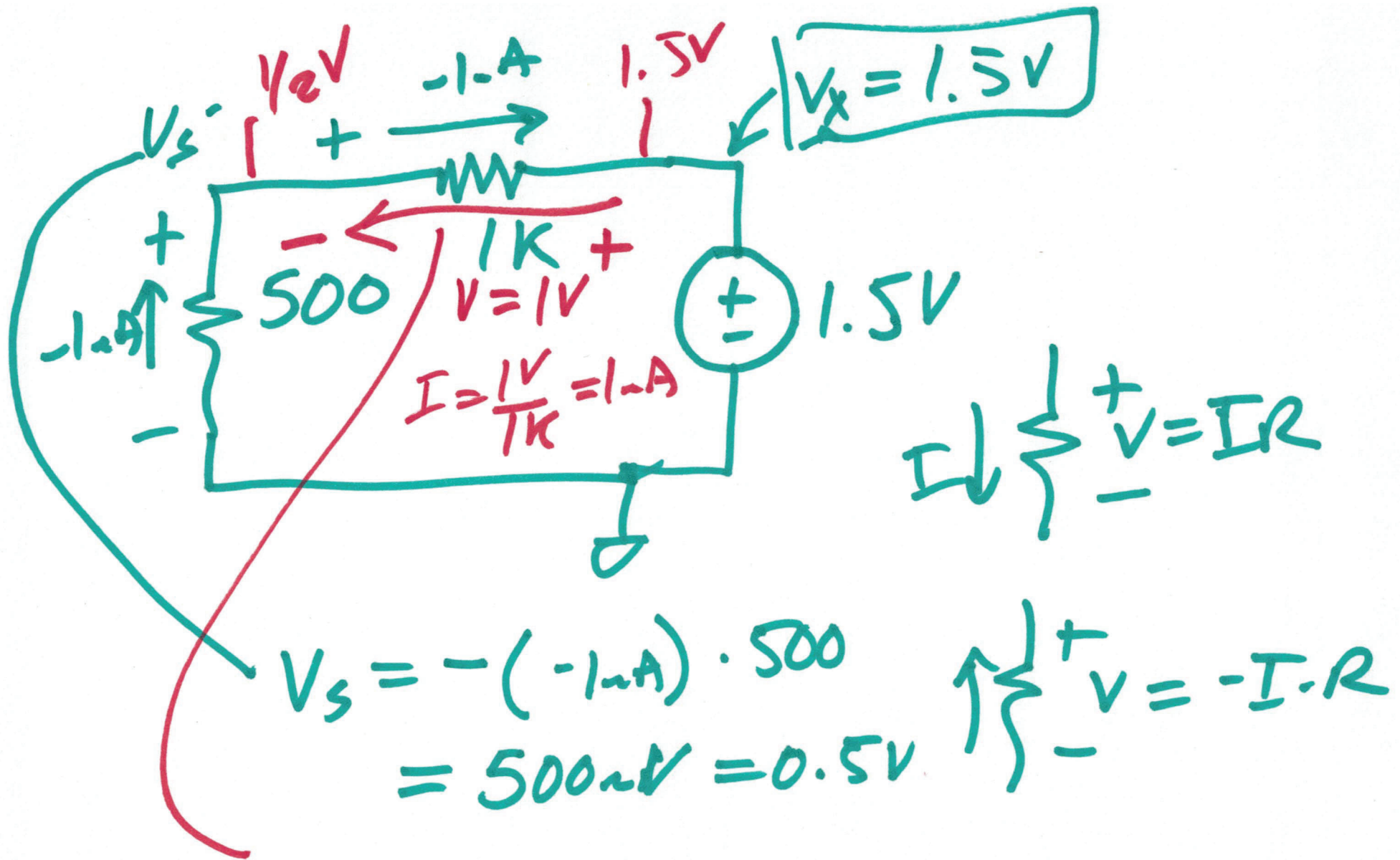

5)

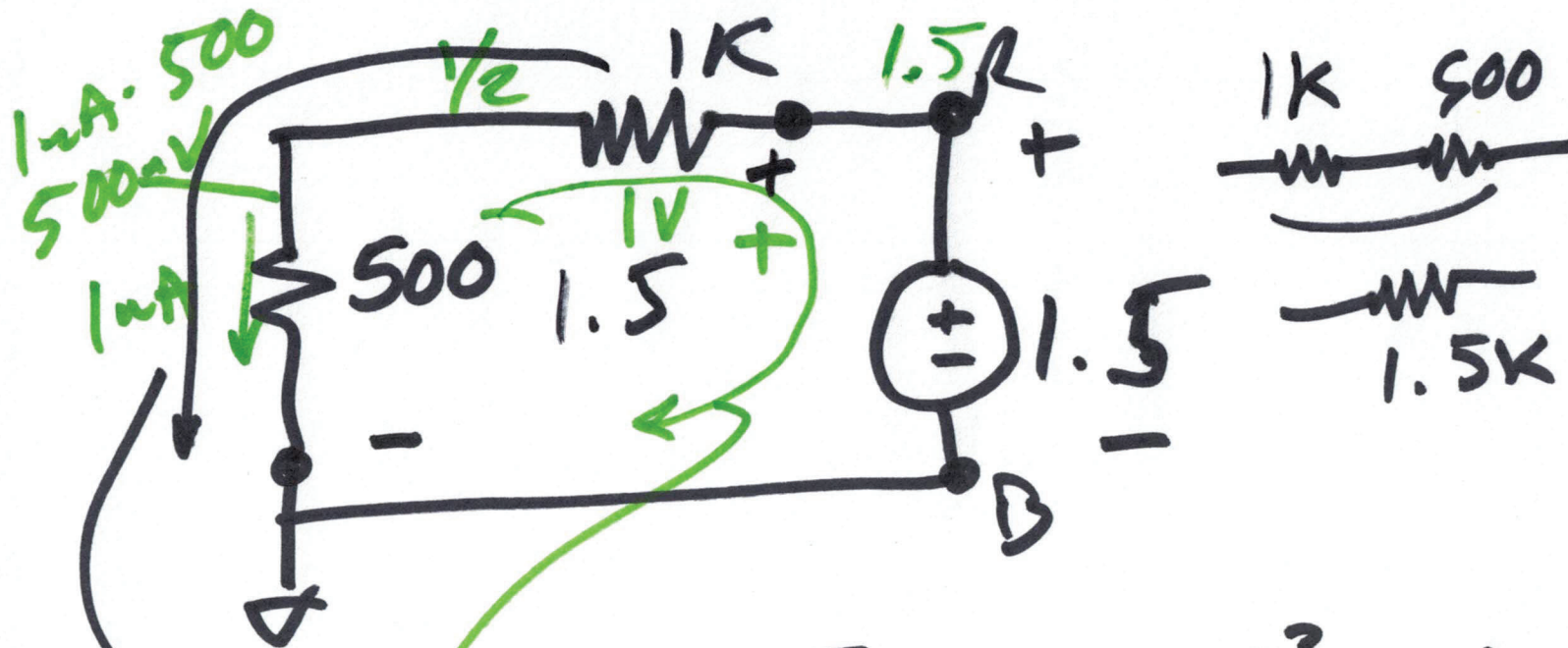


$$I = \frac{1.5}{1.5\text{k}} = 1 \cdot 10^{-3} = 1\mu\text{A}$$

$$I = -1\mu\text{A}$$

6)

Voltage dividers

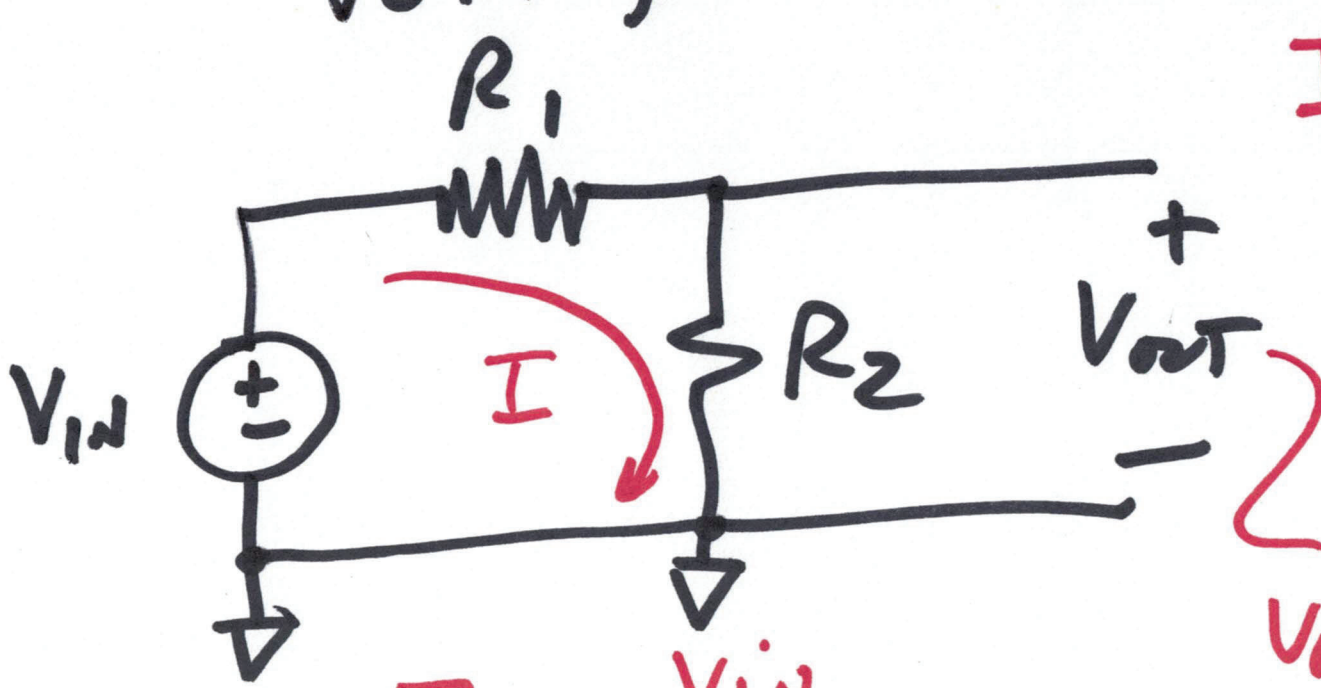

$$I = \frac{V}{R}$$

$$V = IR$$

$$V_{OUT} = I \cdot R_2$$


$$I = \frac{V_{IN}}{R_1 + R_2}$$

Attenuation

Voltage divider equation

$$V_{OUT} = V_{IN} \cdot \frac{R_2}{R_1 + R_2}$$


1)

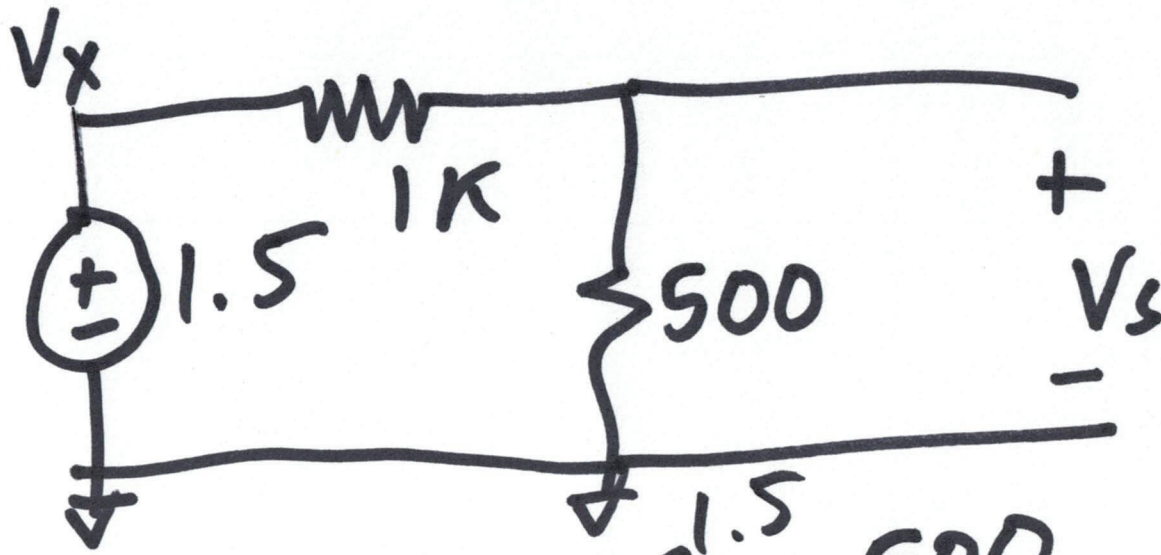

$$V_s = V_x \cdot \frac{500}{500 + 1K} = 1.5 \cdot \frac{1}{3}$$

$$V_s = 500mV$$

voltage divider II

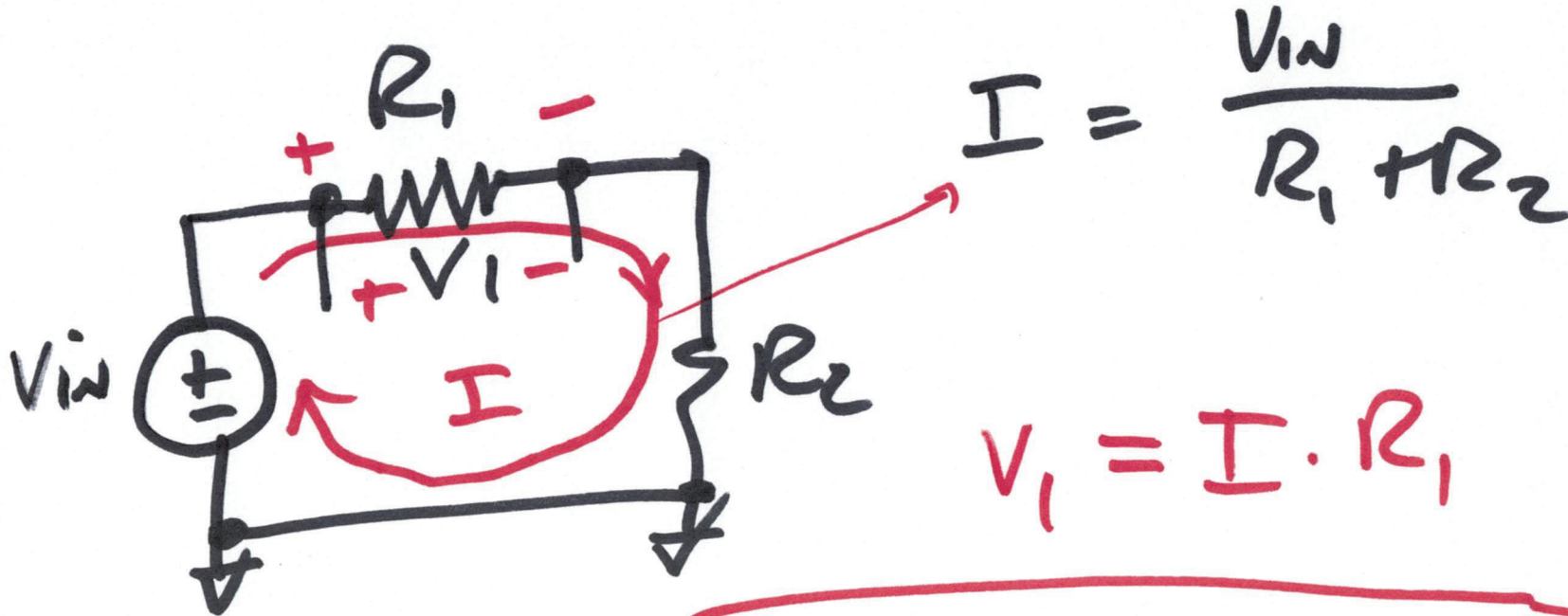

$$V_1 = I \cdot R_1$$


$$V_1 = V_{in} \cdot \frac{R_1}{R_1 + R_2}$$

9)


CURRENT SOURCE

KCL

CURRENT IN =
CURRENT OUT

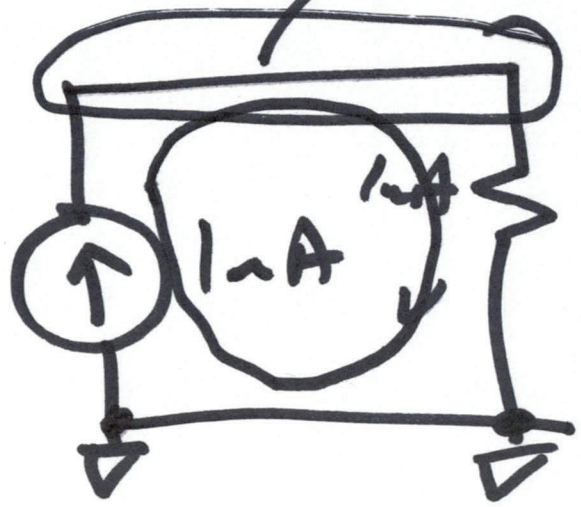


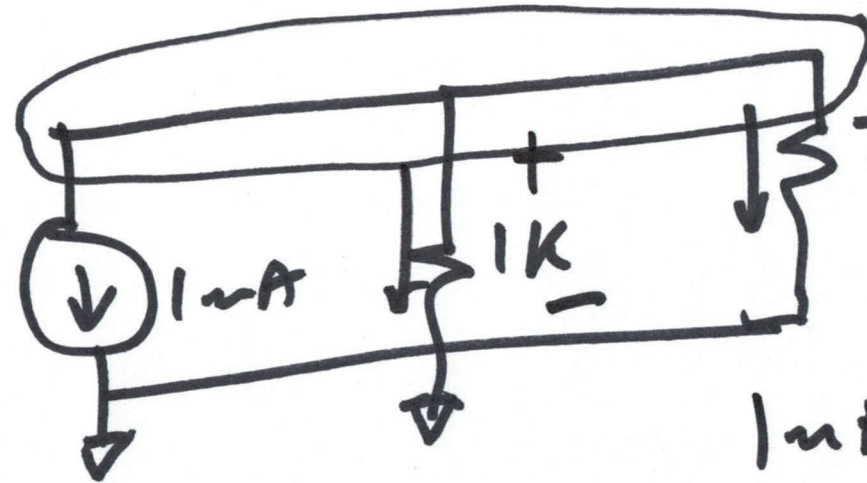$1k \downarrow 1mA$
 $V = 1V = 1k \cdot 1mA$



$1mA + \frac{V_1}{1k} + \frac{V_1}{2k} = 0$

10)

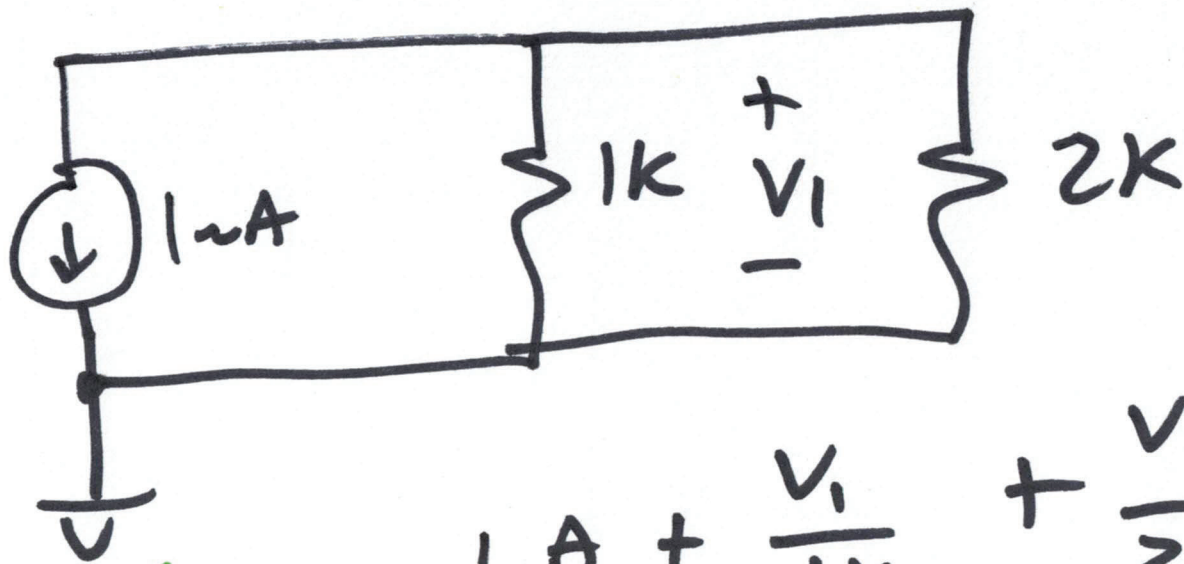

$$R = \frac{1k \cdot 2k}{1k + 2k} = 666$$

$$1\mu A + \frac{V_1}{1k} + \frac{V_1}{2k} = 0$$


$$V_1 = 1\mu A \cdot \frac{1k \cdot 2k}{1k + 2k}$$

$$= 666 \mu V$$

devil's voltage

20 hours




10 hours

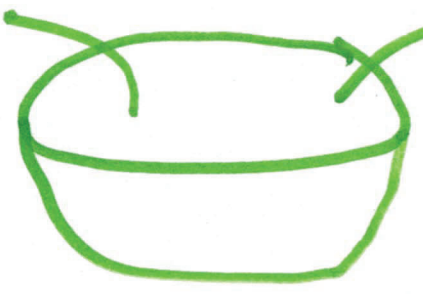

$$\frac{1}{R} = \frac{1}{20} + \frac{1}{10} + \frac{1}{10 \cdot 20}$$

$$R = \frac{10 \cdot 20}{10 + 20}$$

11)

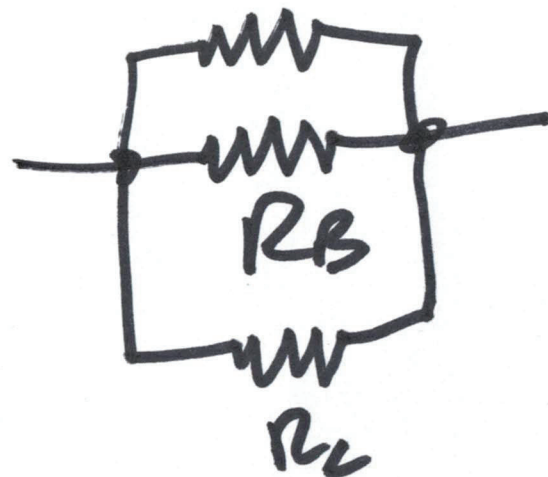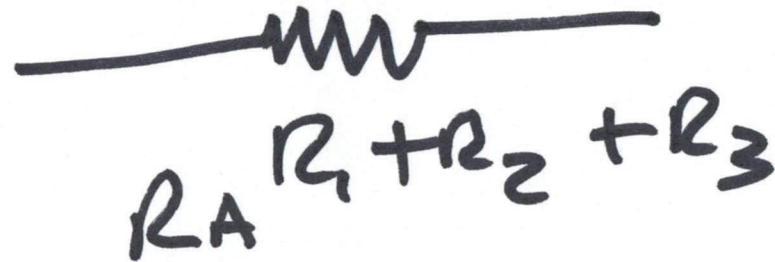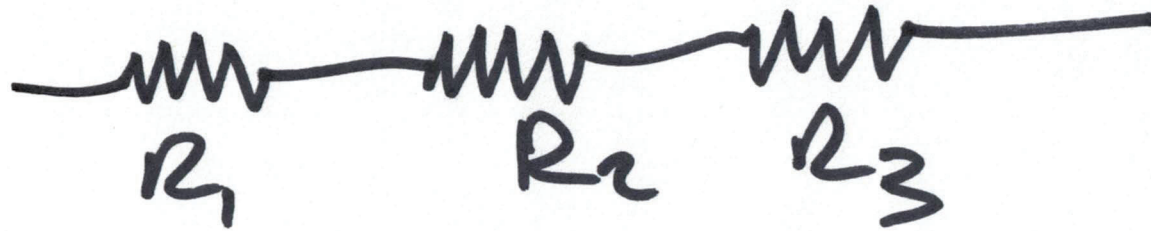

$$\frac{1}{R_T} = \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C}$$

A circuit diagram showing a single resistor, labeled R_T , connected in series. This resistor represents the equivalent resistance of the three resistors in parallel.

12)