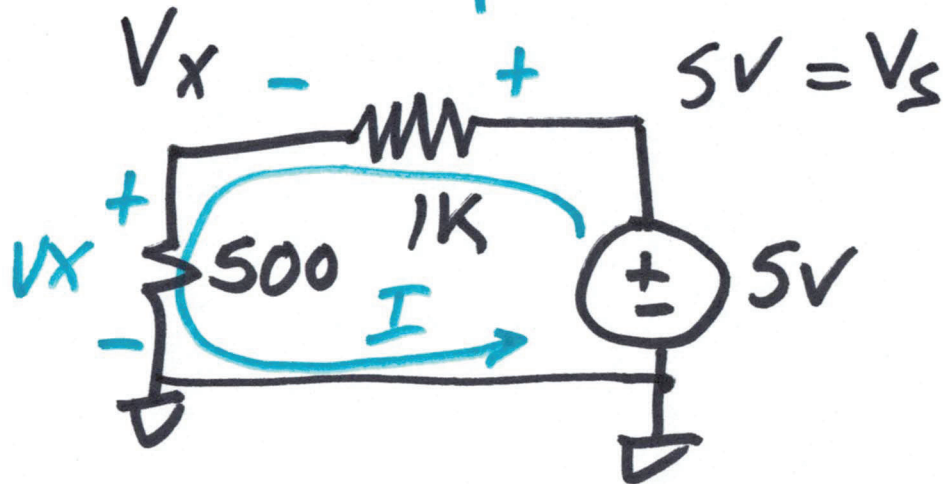


EE 220 circuits I

Lecture 4

Sept. 2, 2020




$$V_x = 5 \cdot \frac{500}{1K + 500}$$

$$V_x = \frac{5}{3} = 1.667V$$

$$I = \frac{5}{1.5K} = \frac{5}{\frac{3}{2}K} = \frac{10}{3} \mu A = 3.33 \mu A$$

$$V_x = 3.33 \mu A \cdot 500 = 3.33 \mu A \cdot \frac{1}{2}K$$

$$V_x = 1.667V$$

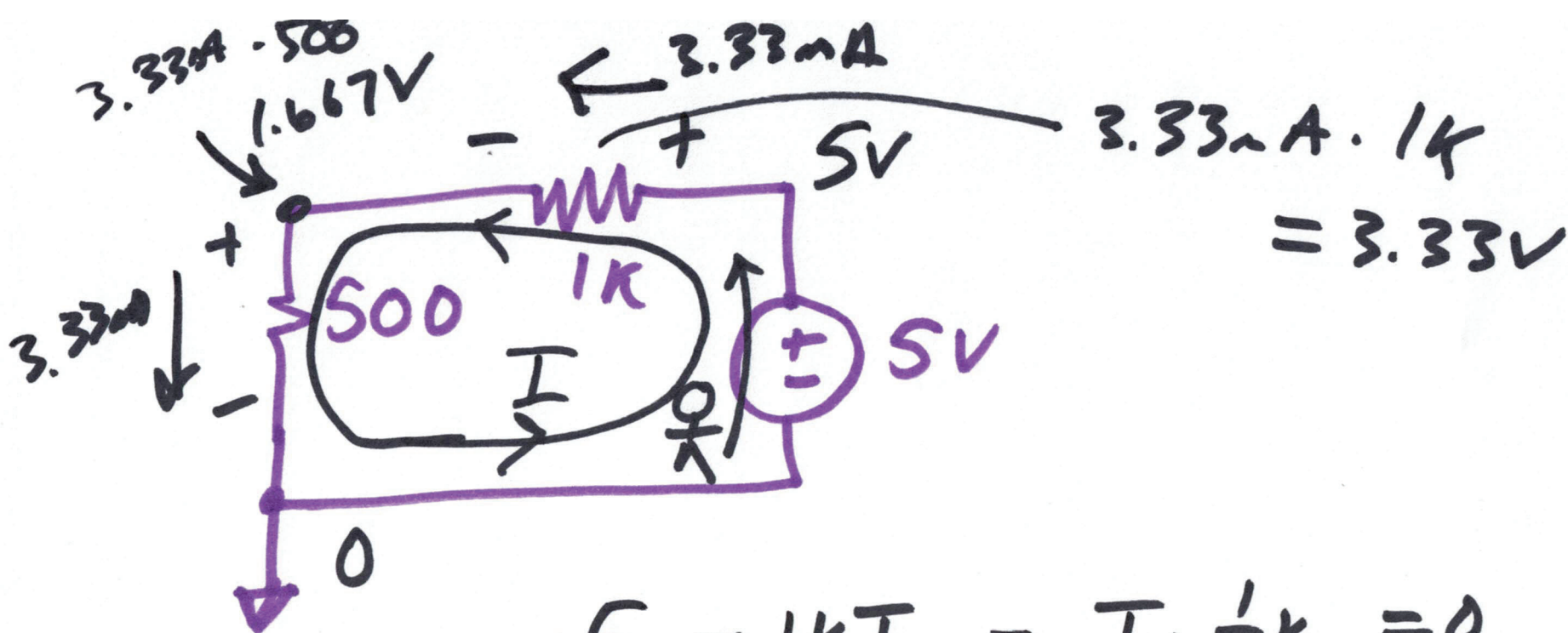


$$5 - 1\text{k}I - I \cdot \frac{1}{2}\text{k} = 0$$

$$5 = 1.5\text{k} \cdot I$$

$$I = 3.33\text{mA}$$

2)

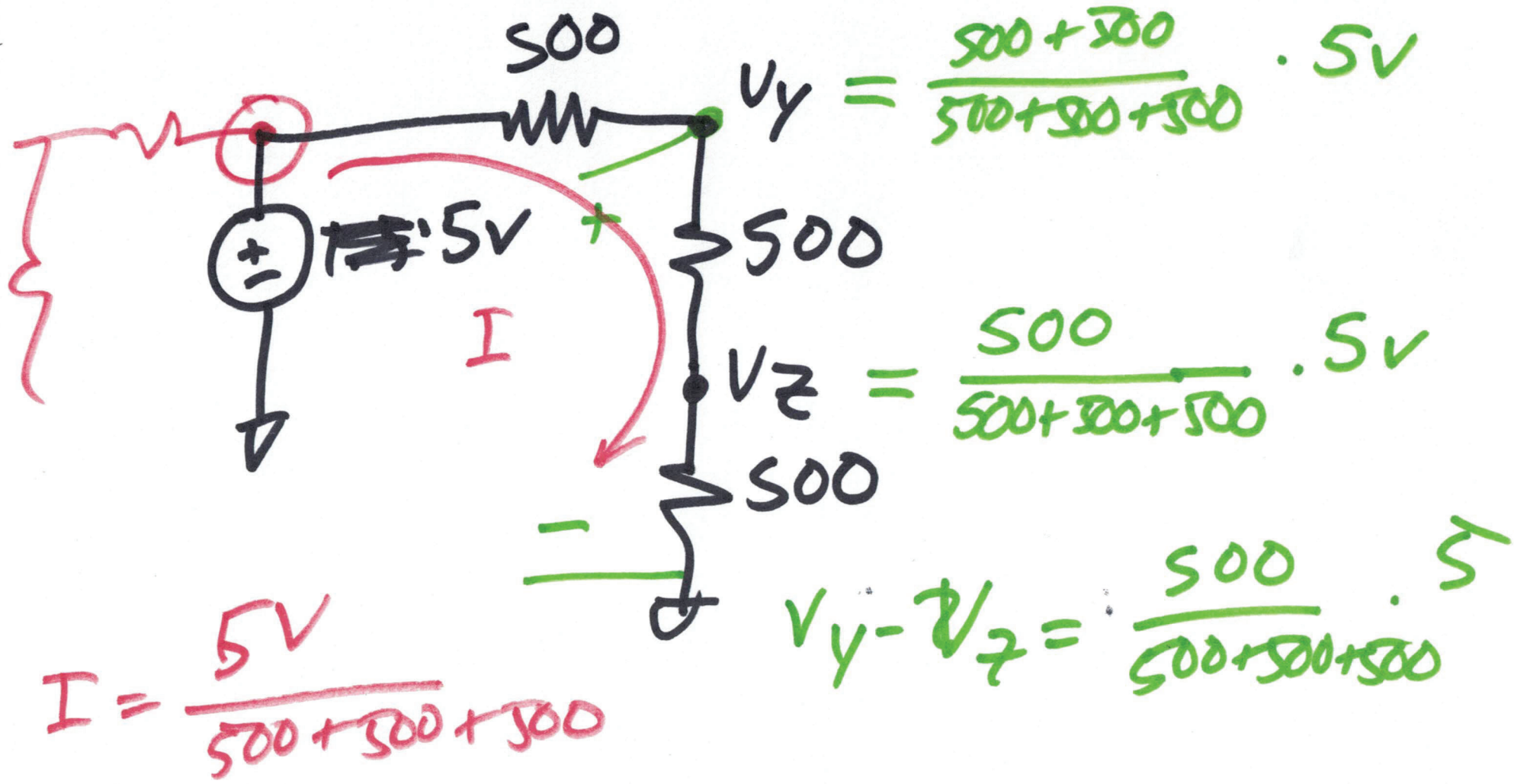


$$I = \frac{5V}{500 + 500 + 500}$$

$$= 3.33 \text{ mA}$$

$$V_z = 3.33 \text{ mA} \cdot 500 = I \cdot 500$$

$$V_y = 3.33 \text{ mA} \cdot (500 + 500)$$


3)

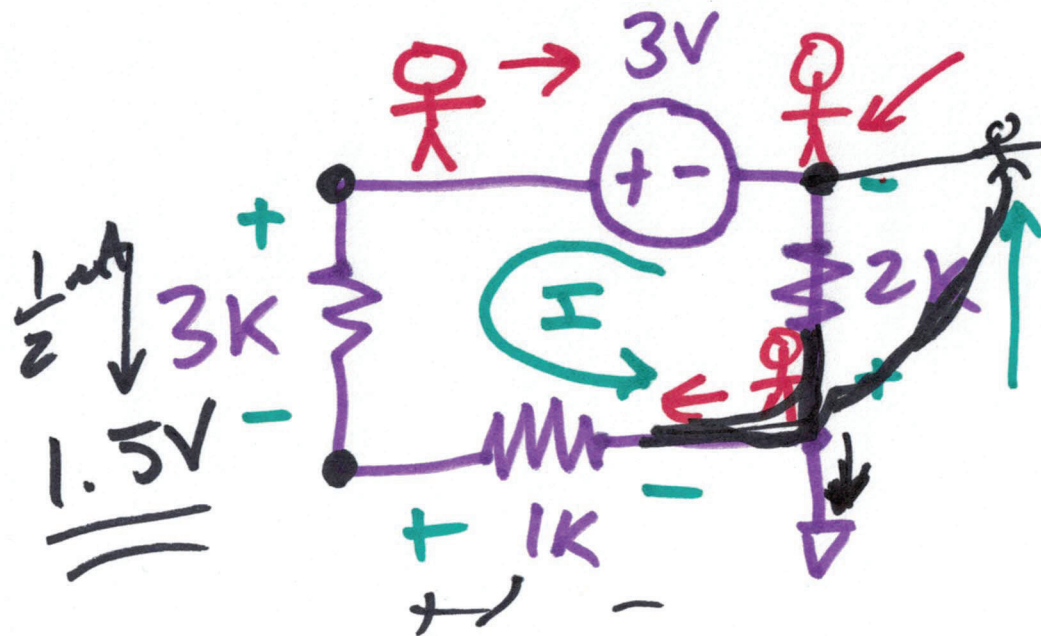

$$-2k \cdot \frac{1}{2} \mu A + 1V = 0$$


$$-3 + 2k \cdot I + 1k \cdot I + 3kI = 0$$

$$I = \frac{3}{6k} = \frac{1}{2} \mu A$$

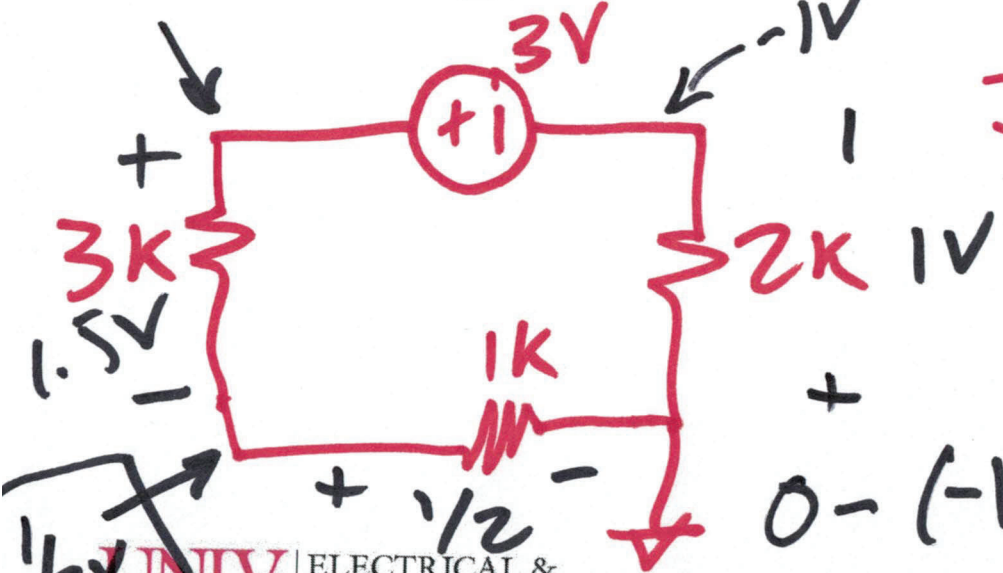

$$0 - (-1V) = 1V$$

4)

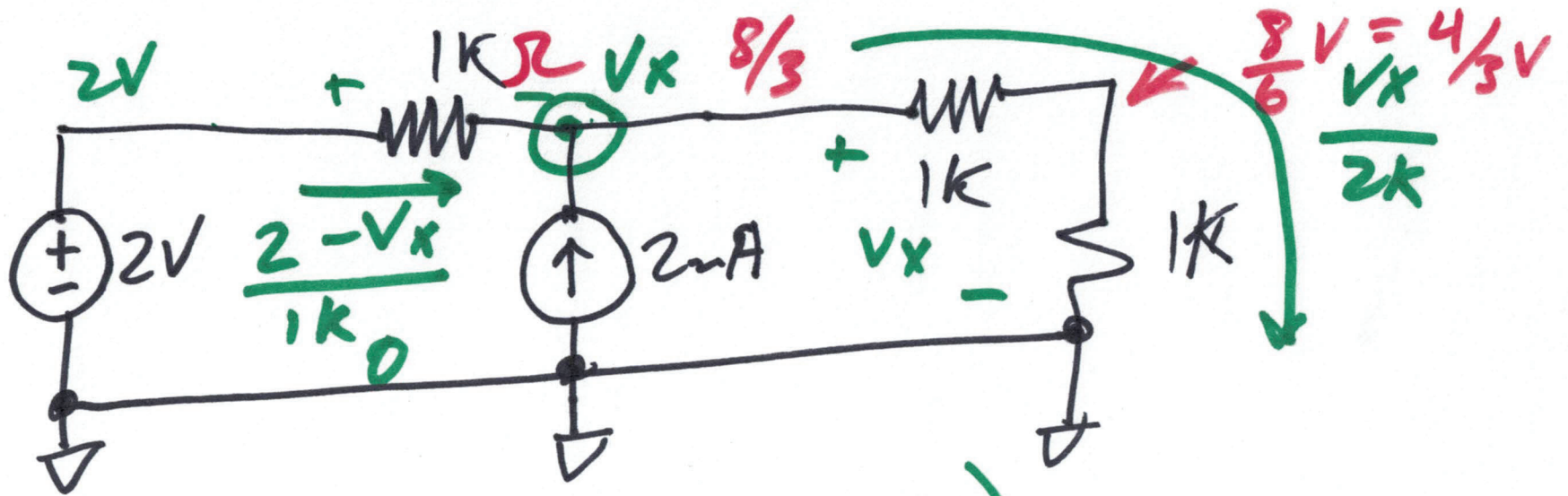

$$2k \left(2mA + \frac{2 - V_x}{1k} - \frac{V_x}{2k} \right) = 0 \cdot 2k$$


$$4V + 4V - 2V_x - V_x = 0$$

$$3V_x = 8$$

$$V_x = \frac{8}{3} V$$

5)


Superposition

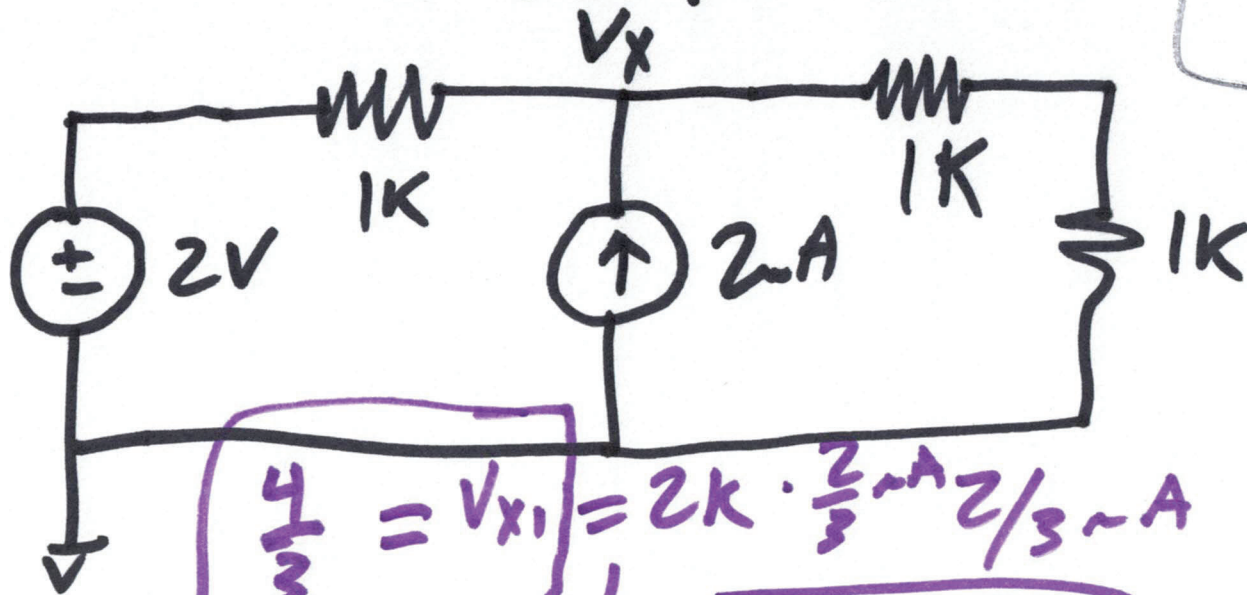

Replace current with open
 Replace voltage source with short


$$\frac{4}{3} = V_{x1} = 2k \cdot \frac{2mA}{3} = \frac{2}{3}mA$$

①

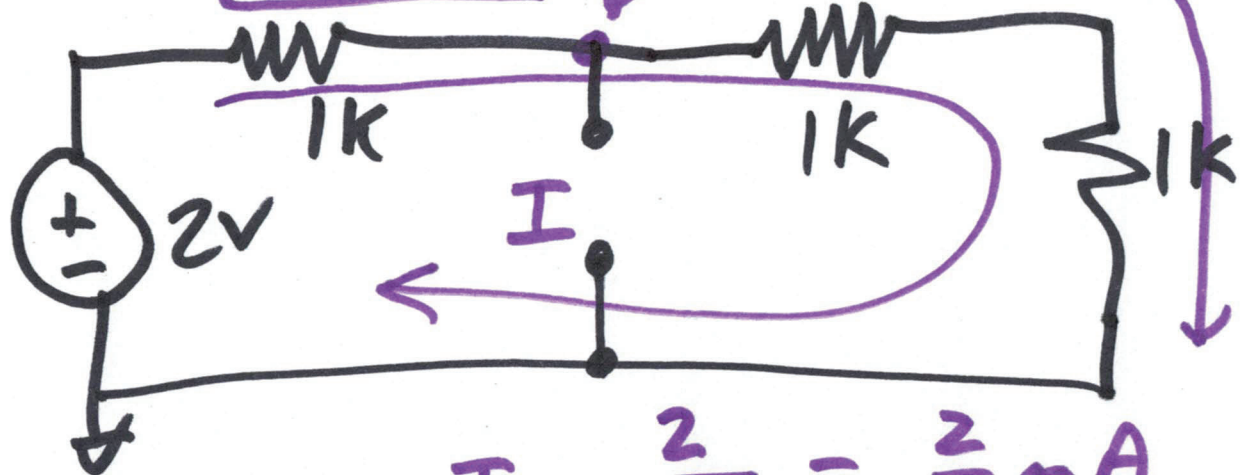


$$I = \frac{2}{3k} = \frac{2}{3}mA$$

o)

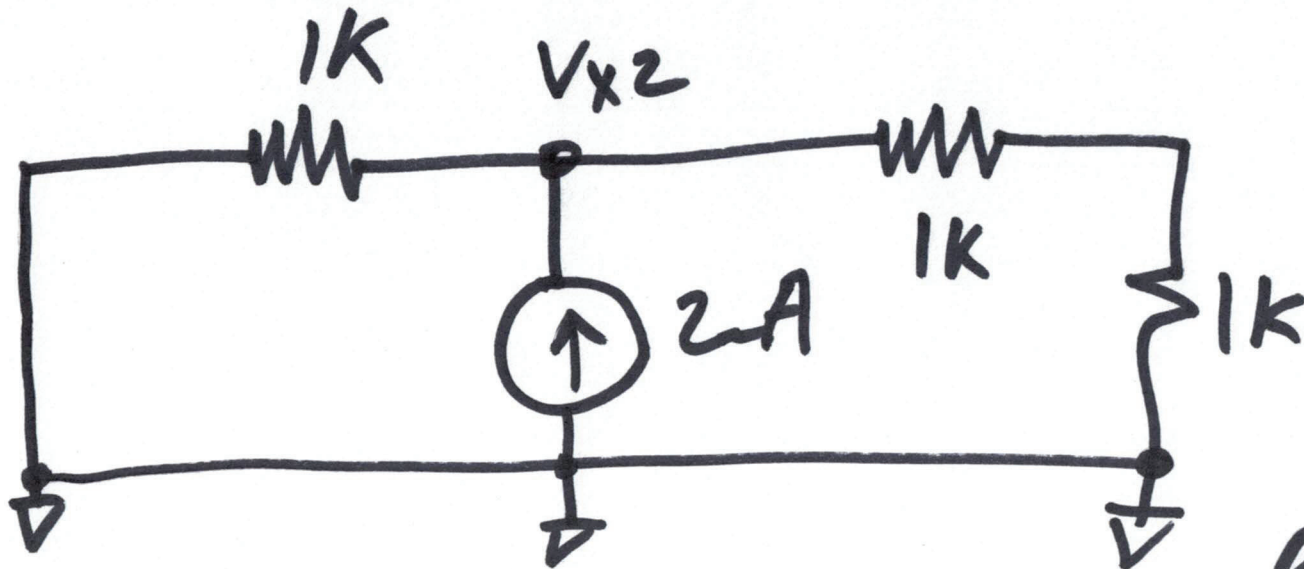


$$1k // 2k$$
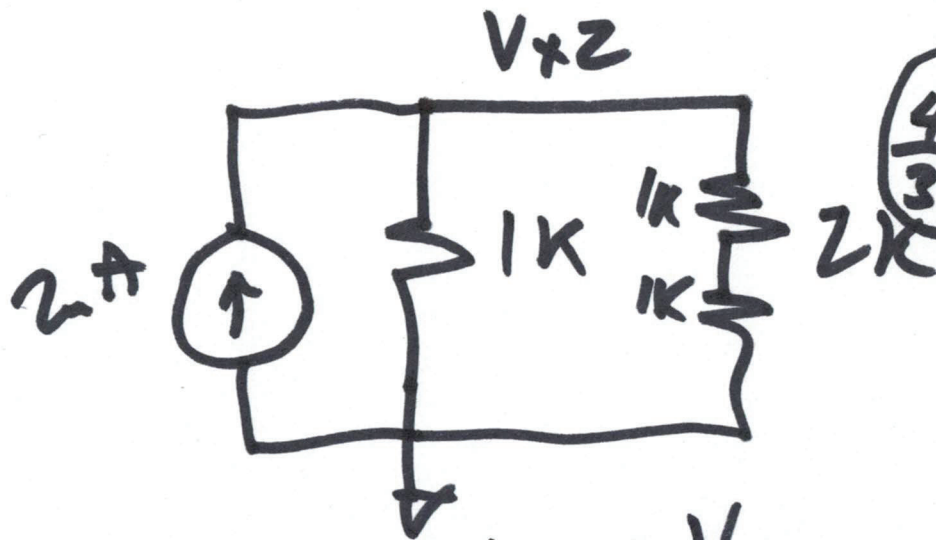
$$R_{eq} = \frac{1k \cdot 2k}{1k + 2k} = 666\Omega = \frac{2}{3}k$$



$$\frac{4}{3}V = V_{x2}$$


$$V_x = V_{x1} + V_{x2}$$

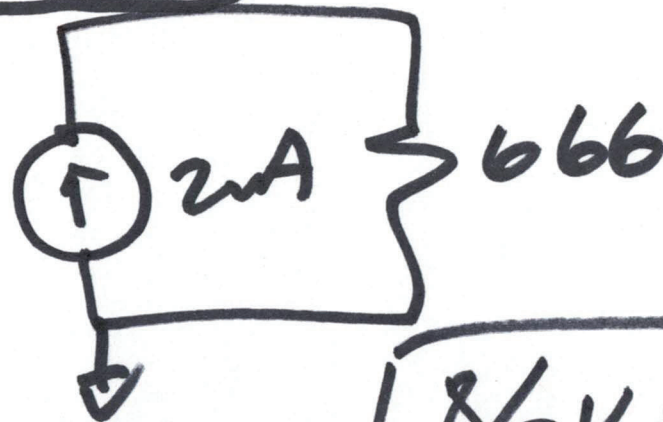

$$= \frac{4}{3}V + \frac{4}{3}V =$$

$$\frac{8}{3}V = V_x$$

7)

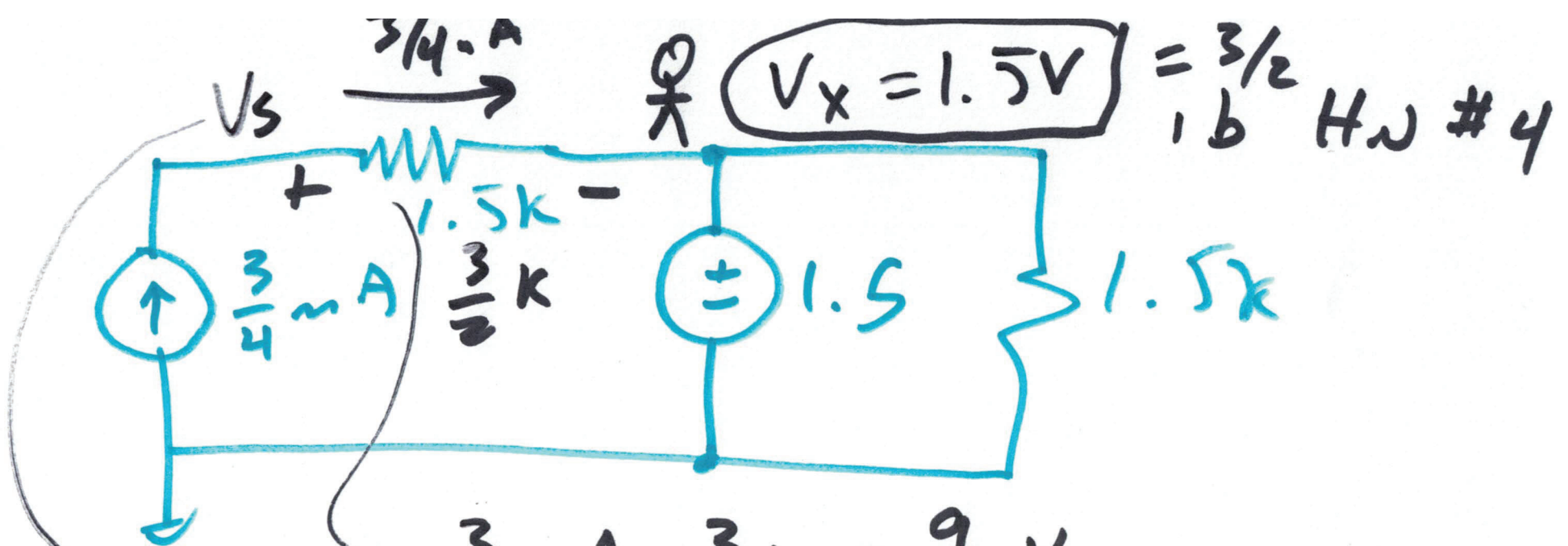


$$\frac{3}{4} \text{ mA} \cdot \frac{3}{2} \text{ k} = \frac{9}{8} \text{ V}$$

$$\rightarrow V_s = 1.5 + \frac{9}{8} = \frac{3}{2} + \frac{9}{8} = \frac{12}{8} + \frac{9}{8}$$

$$V_s = \frac{21}{8} \text{ V}$$

8)

2b Hw #4

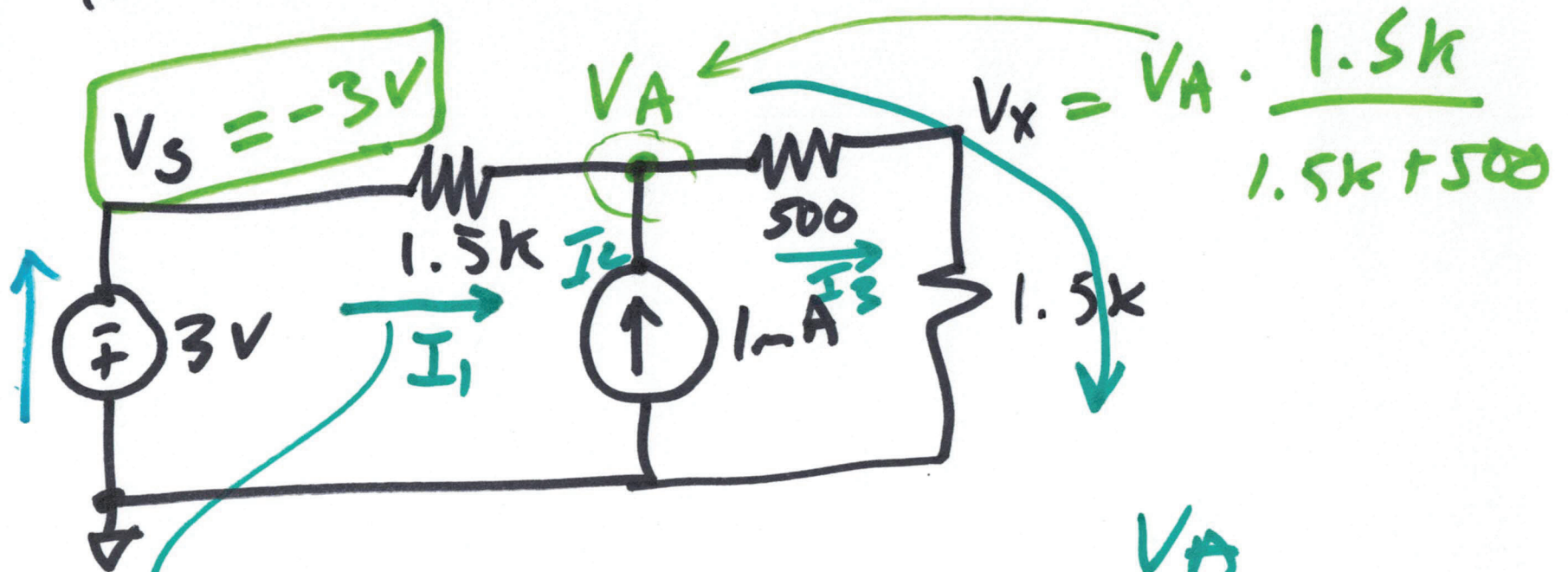

$$V_x = V_A \cdot \frac{1.5k}{1.5k + 500}$$

$$\frac{-3 - V_A}{1.5k} + 1mA = \frac{V_A}{500 + 1.5k}$$

$$I_1 + I_2 = I_3$$