
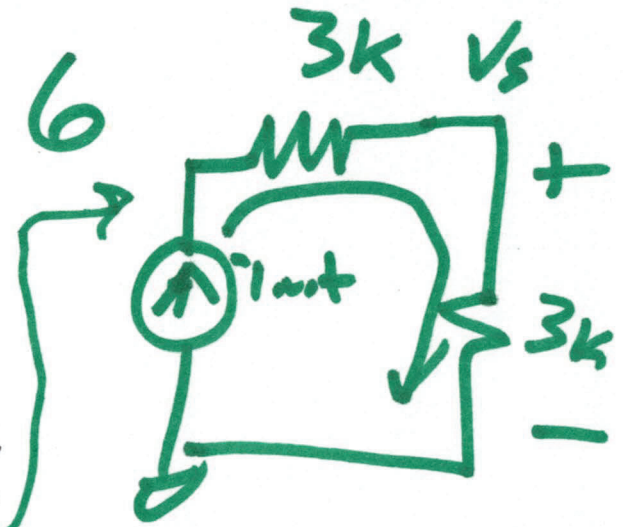
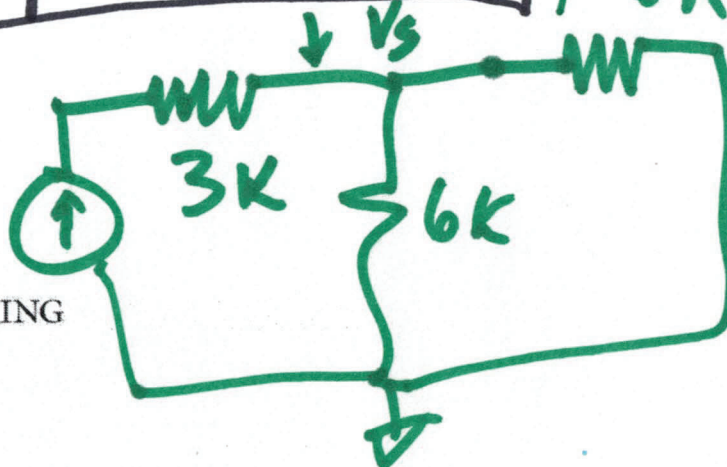


EE 220

Circuits 1

Sept. 14, 2020

Lecture 6

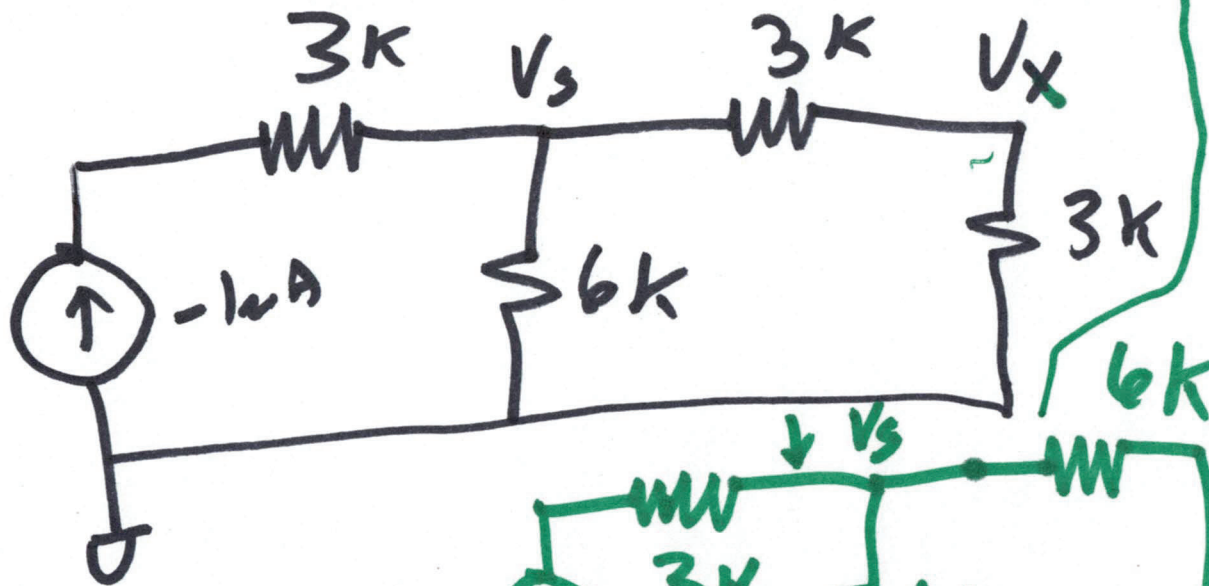

$$V_s = (-1\mu\text{A})3\text{k}$$


$$V_s = -3\text{V}$$

1)

Closed book and notes.


Show your work for credit and **place a box around each of your answers.**

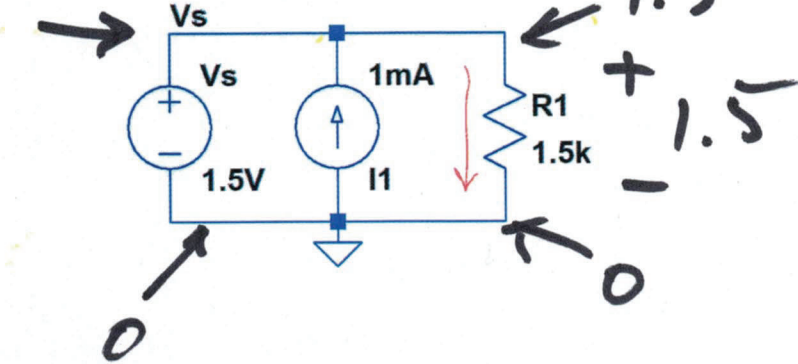1. Determine the current through R1 in the direction indicated. Again, show your work for credit. (2 points)



$$I = \frac{1.5V}{1.5k} = 1mA$$

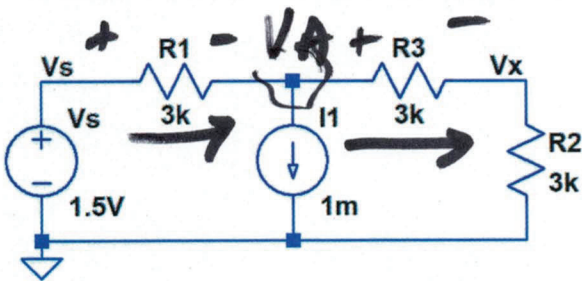2. Find  $V_x$  in the following circuit. (5 points)




$$\frac{1.5 - V_A}{3k} = 1mA + \frac{V_A}{6k}$$

$$3 - 2V_A = 6 + V_A$$

$$-3 = 3V_A$$

$$V_A = -1V$$

2)

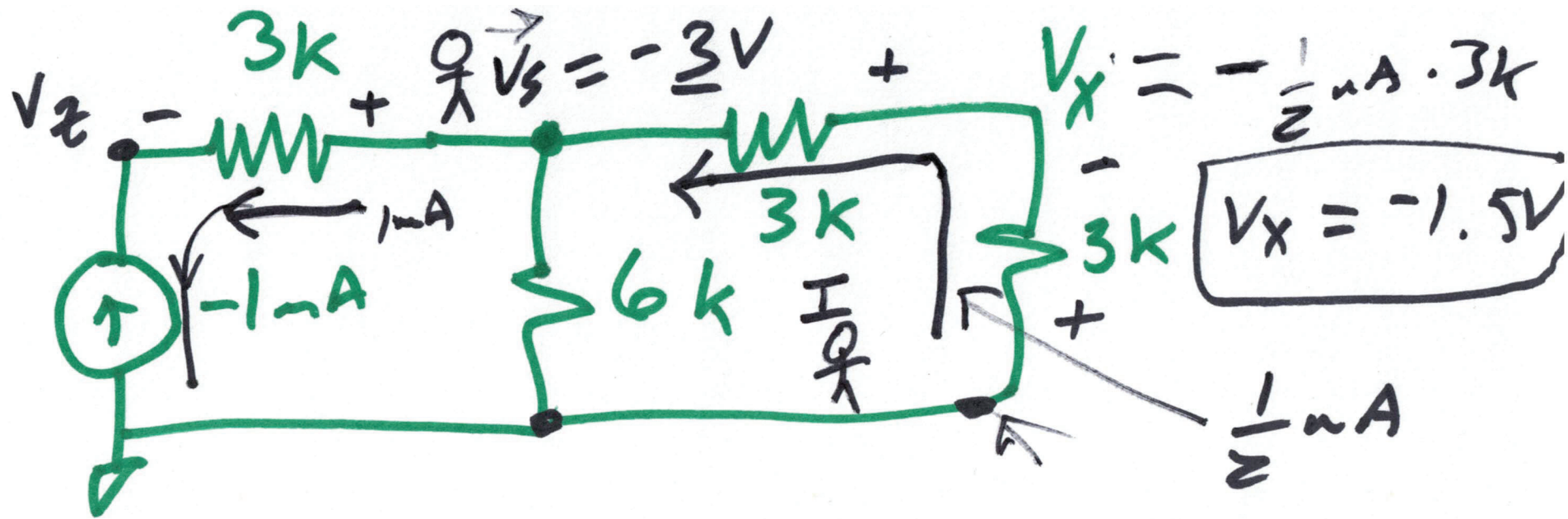

$$-3V - 3k \cdot 1\mu A = \boxed{V_z = -6V}$$


$$-3V + 3k \cdot I + 3k \cdot I = 0$$

$$6kI = 3$$

$$I = \frac{1}{2}\mu A$$

3)



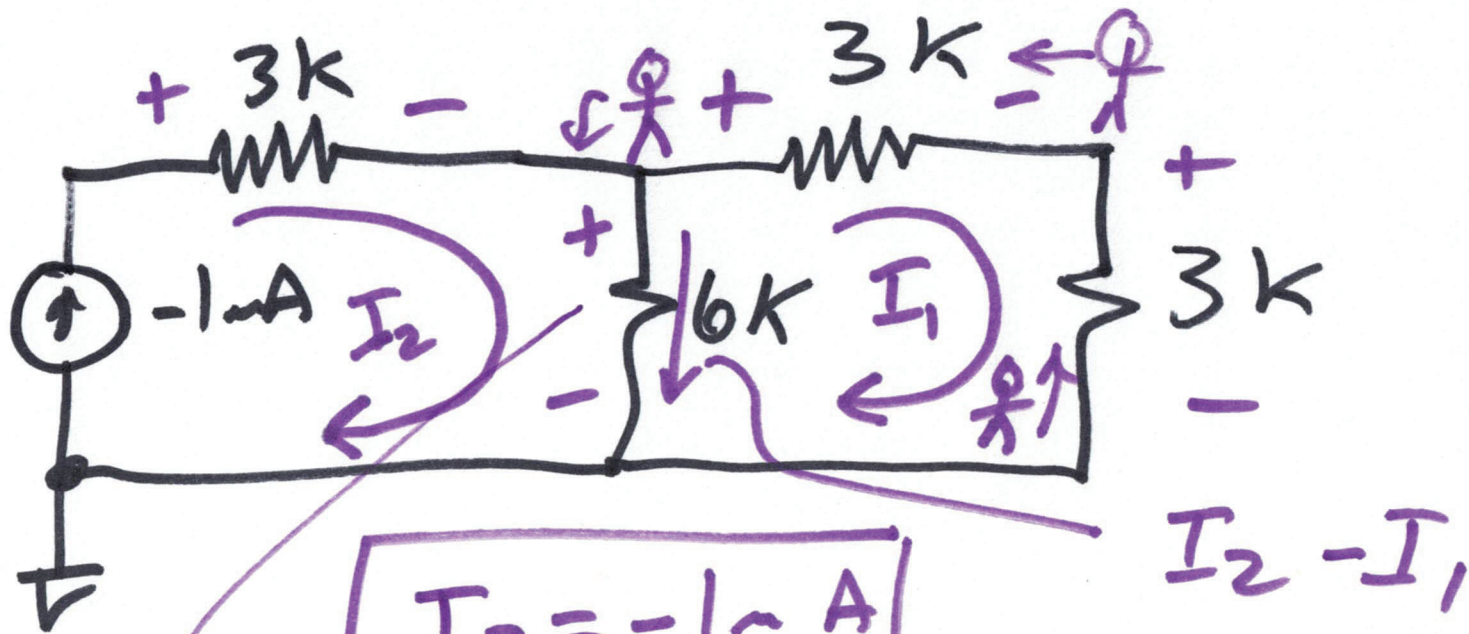

$$I_2 = -1 \mu A$$

$$6k \cdot (I_2 - I_1)$$


$$I_1 = -\frac{1}{2} \mu A$$

$$-6k(I_2 - I_1) + 3k \cdot I_1 + 3k \cdot I_1 = 0$$

$$6V + 6kI_1 + 3kI_1 + 3kI_1 = 0$$

$$6 = -12kI_1$$

4)

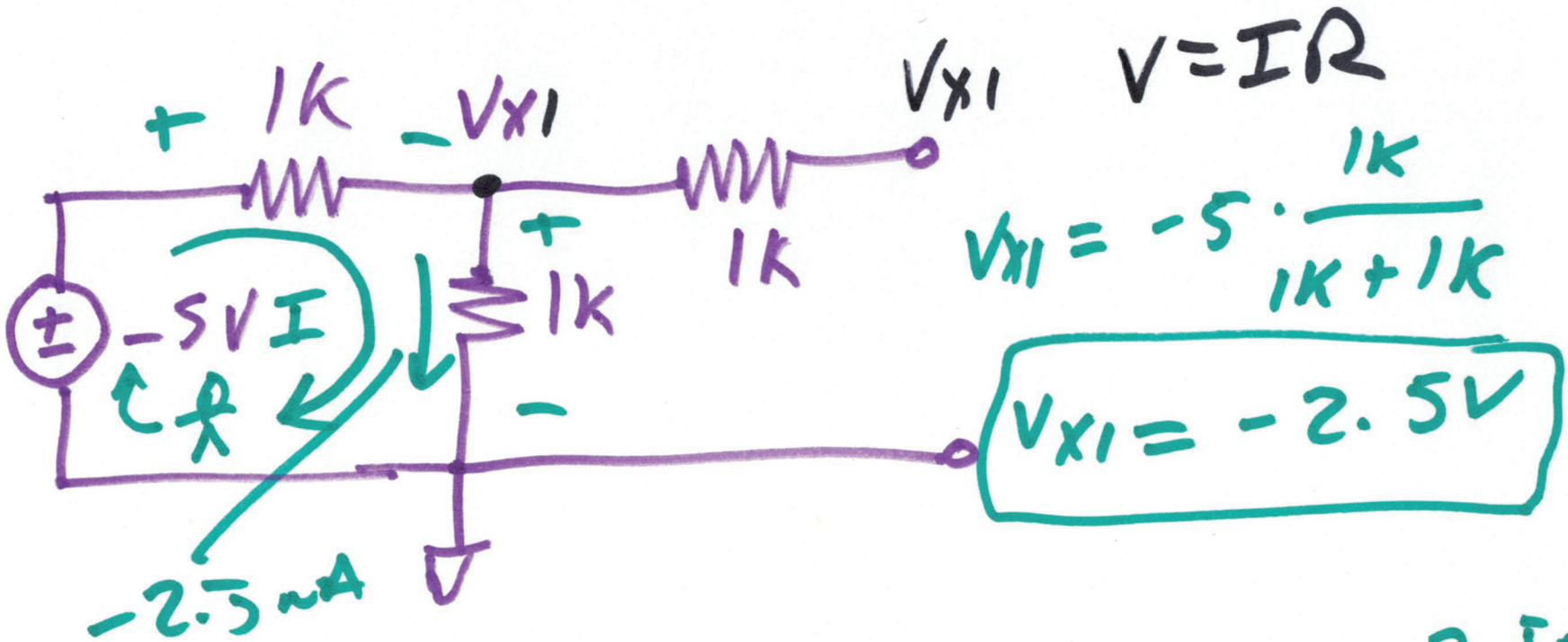


$$-5 - 1k \cdot I - 1k \cdot I = 0, I = -2.5 \mu A$$

$$V_{X1} = -2.5 \mu A \cdot 1k$$

$$V_{X1} = -2.5V$$

5)

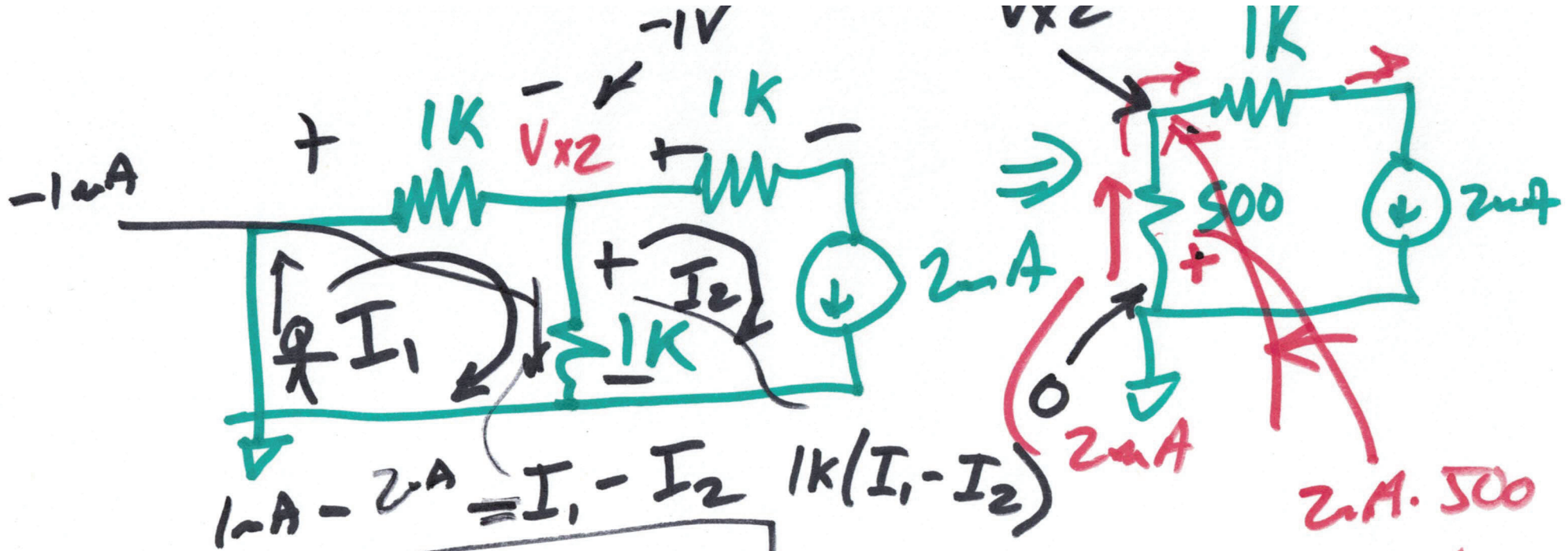

$$1\mu A - 2\mu A = I_1 - I_2 \quad 1K(I_1 - I_2)$$

$$I_2 = 2\mu A$$

$$I \uparrow \downarrow \frac{V}{R} = IR$$

$$2\mu A \cdot 500 = 1V$$

$$I_1 \cdot 2K = 2V \quad I_1 = 1\mu A$$

$$-1K I_1 - 1K(I_1 - I_2) = 0$$

$$0 - V_{x2} = 1V$$

$$-1KI_1 - 1KI_1 + 2\mu A = 0$$

$$V_{x2} = -1V$$

$$V_x = V_{x1} + V_{x2}$$

$$-3.5V = -2.5 + -1$$


6)



Ohm's Law, Kirchhoff's voltage law (KVL)


Kirchhoff's current law (KCL)

super node

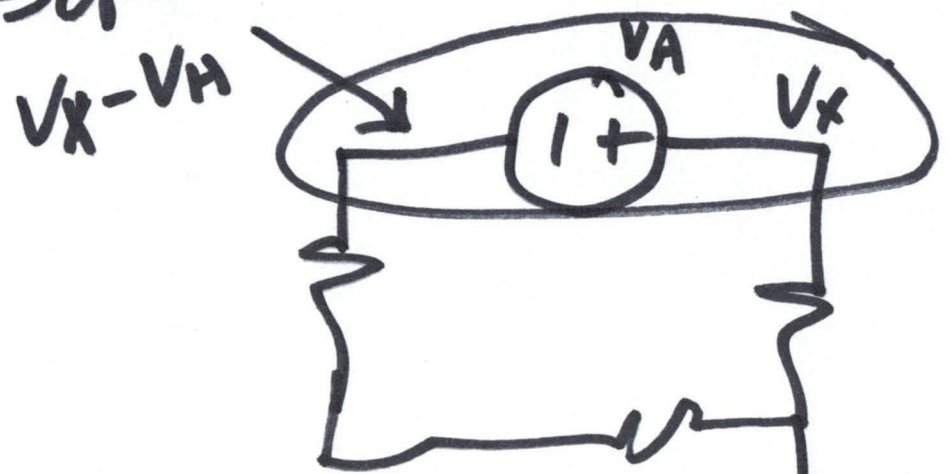



super mesh

super mesh

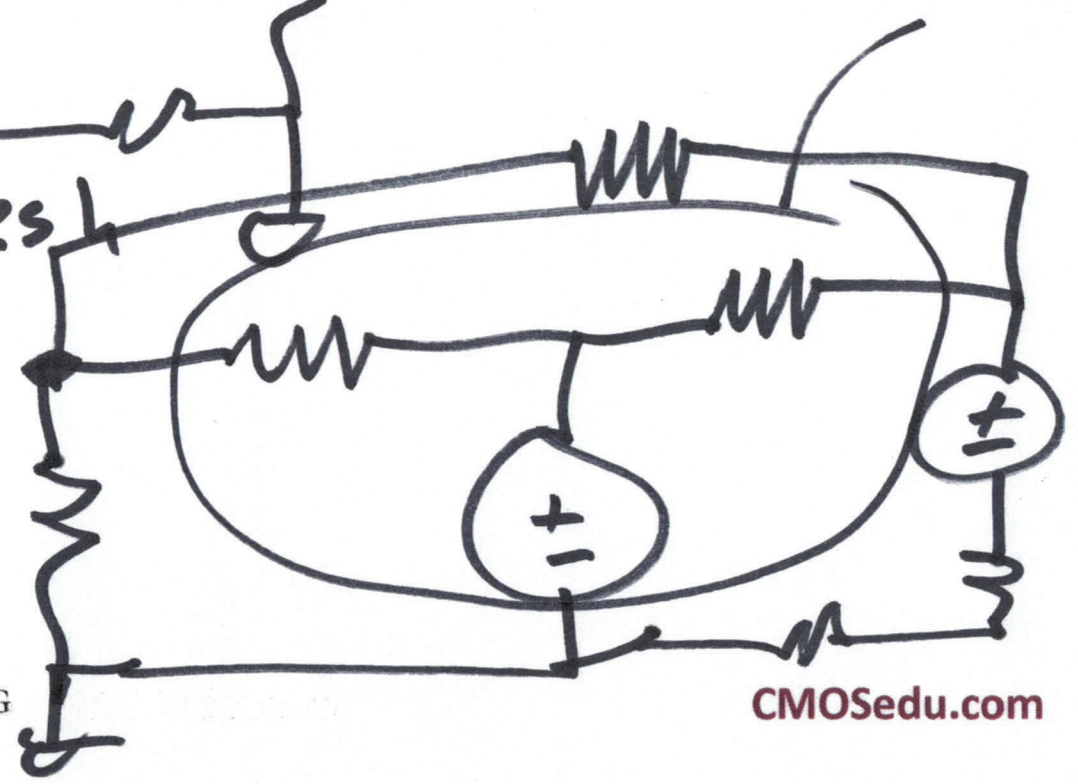


1)

# THEVENIN EQUIVALENT

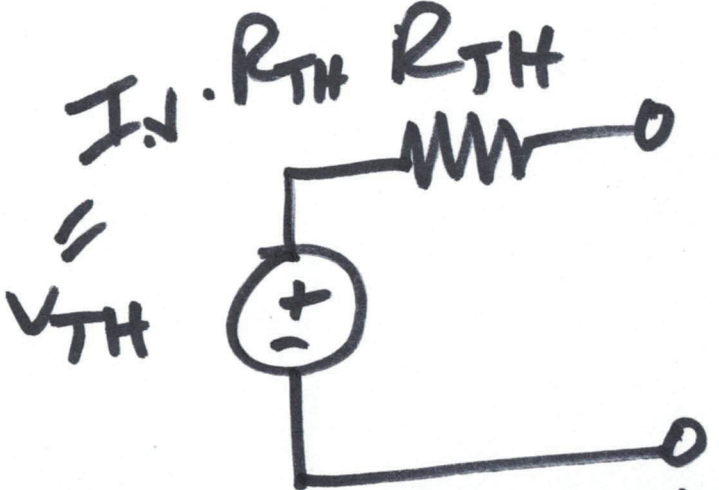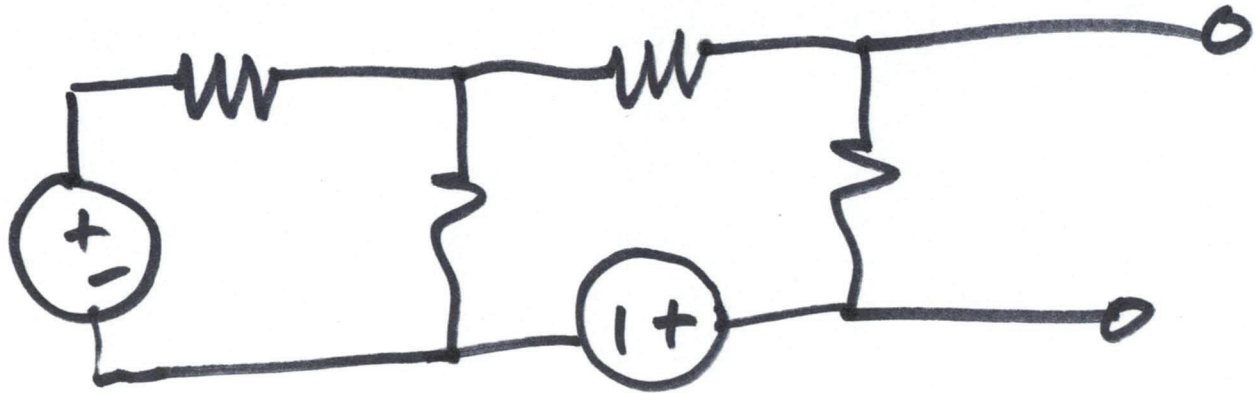



THEVENIN EQUIVALENT

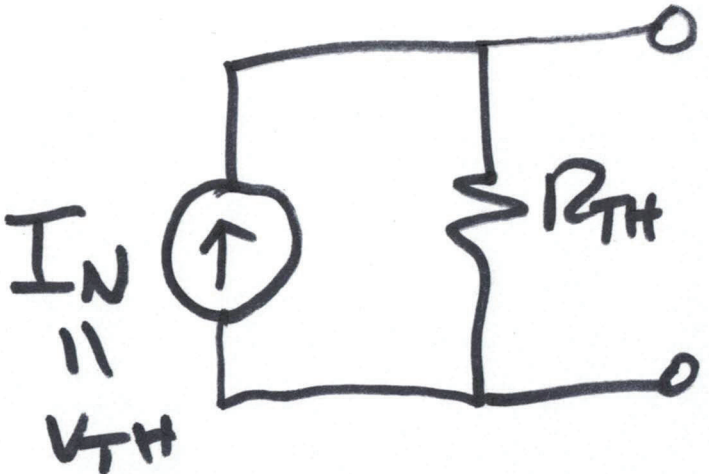


8)



3(a)

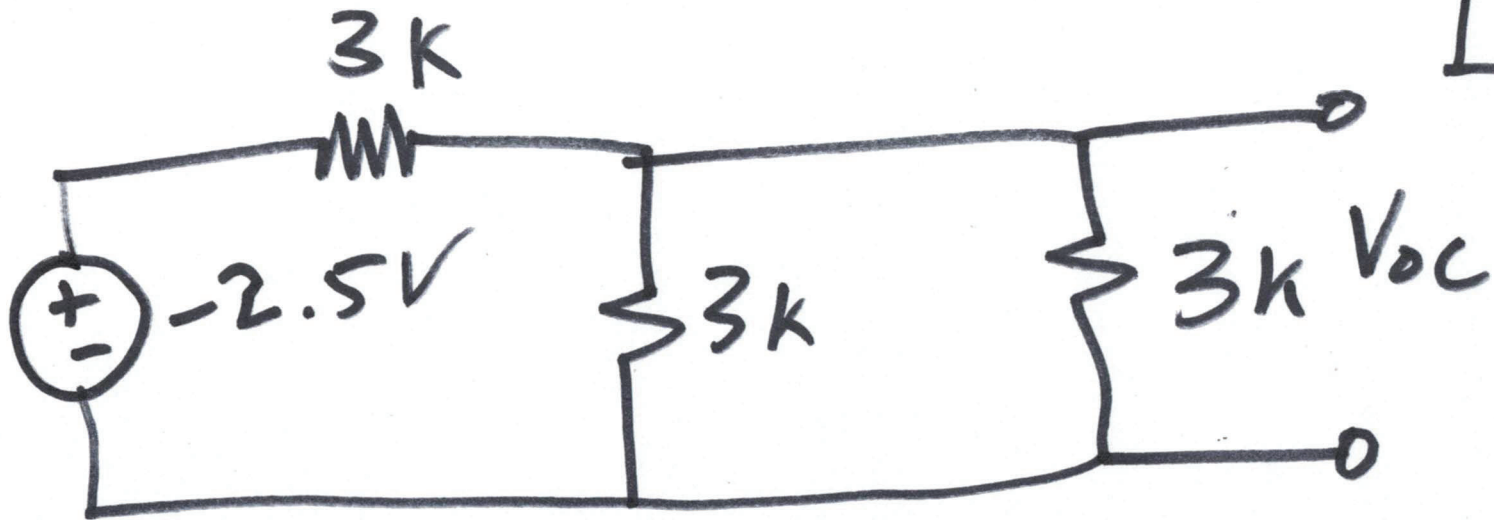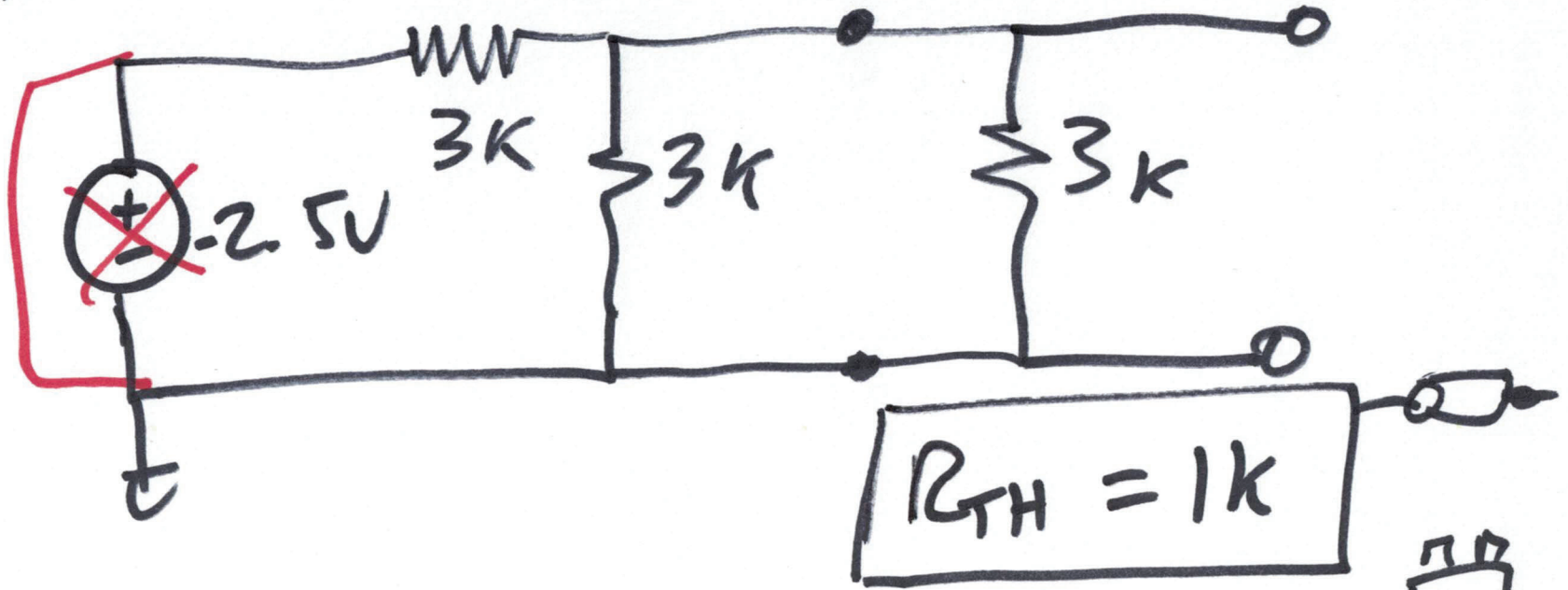

9)

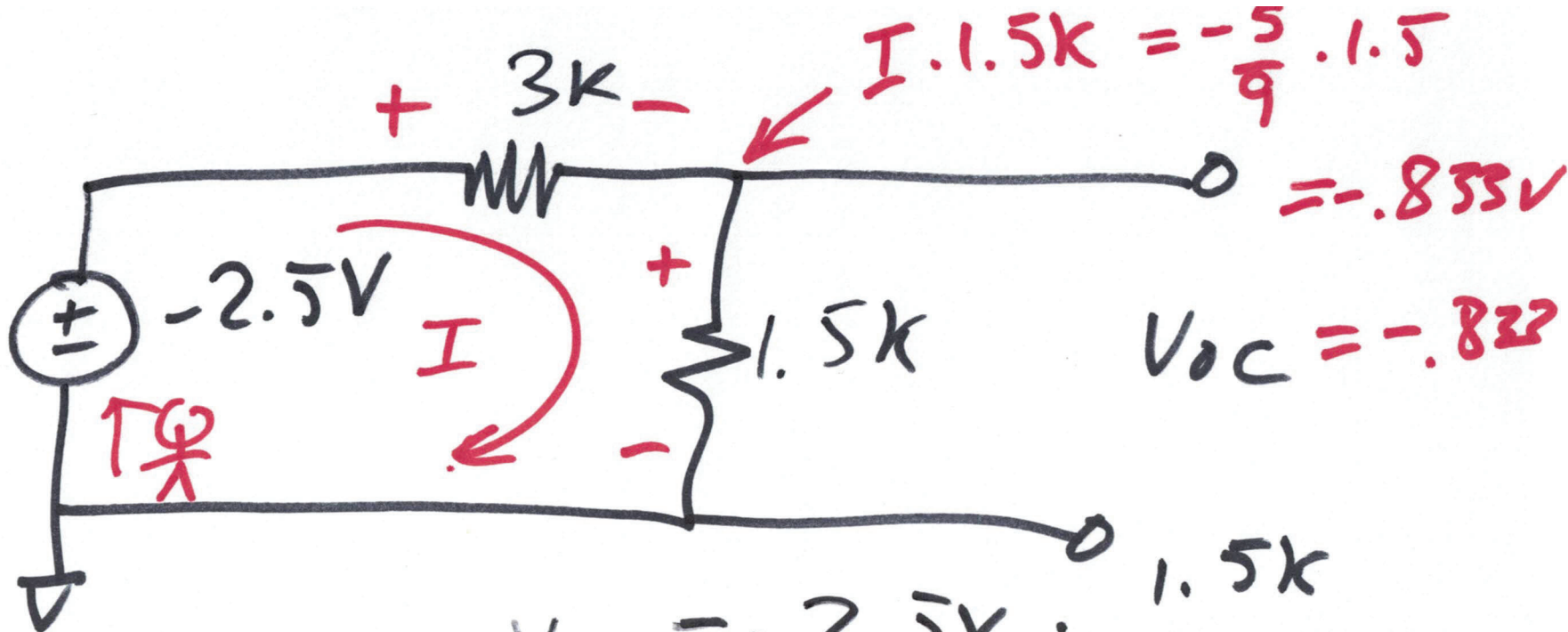

$$V_{oc} = -0.833$$

$$V_{oc} = -2.5V \cdot \frac{1.5k}{1.5k + 3k}$$

$$-2.5V - I \cdot 3k - I \cdot 1.5k = 0$$

$$= -2.5 \cdot \frac{3}{3+6} = -2.5 \cdot \frac{3}{9} = -\frac{1}{3}$$

$$-2.5 = I \cdot 4.5k$$

$$I = \frac{2.5}{4.5} = \frac{5}{9} \text{ mA}$$

$$V_{oc} = \frac{-2.5}{3} = -0.833V$$

10)

