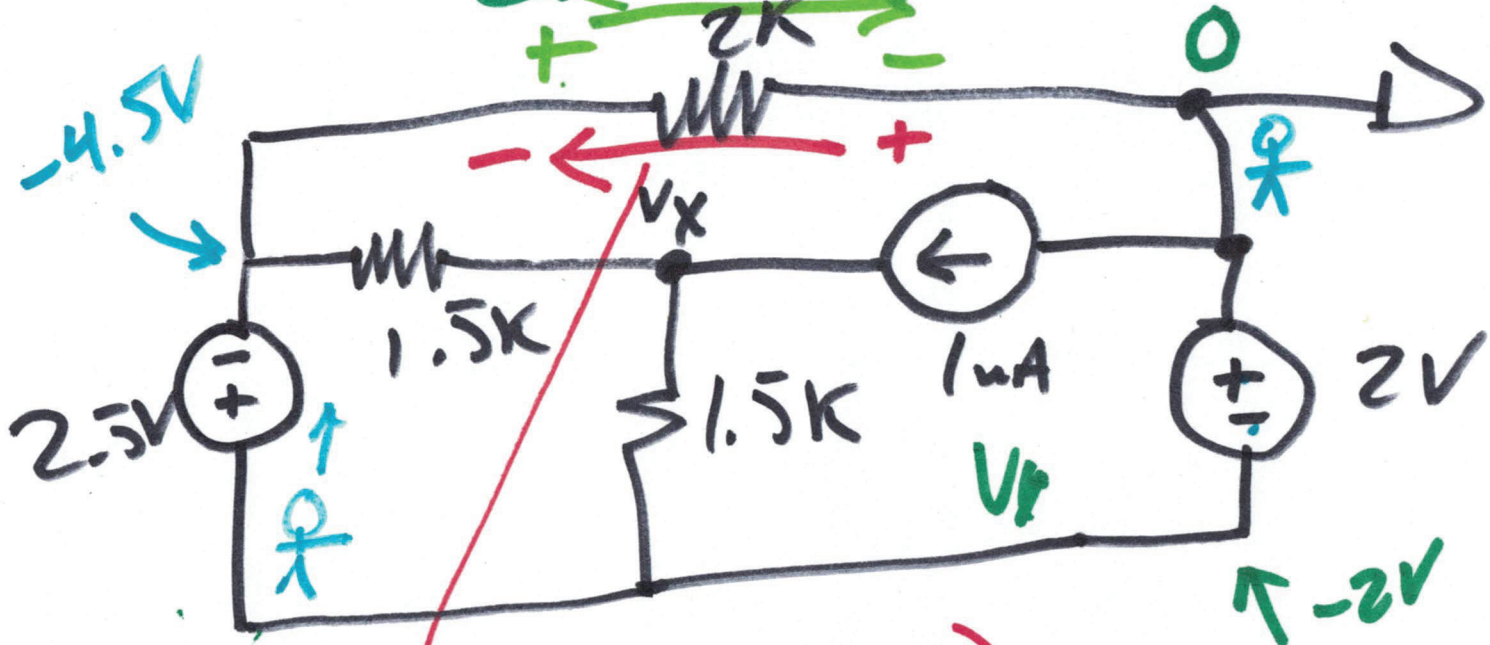


EE 220 Circuits 1
 Sept. 23, 2020

$$= \frac{-4.5 - 0}{2k} = -2.25 \mu A$$


Lecture 9,
 2k

$$V = IR$$



$$\frac{0 - (-4.5)}{2k} = +2.25 \mu A$$

1)

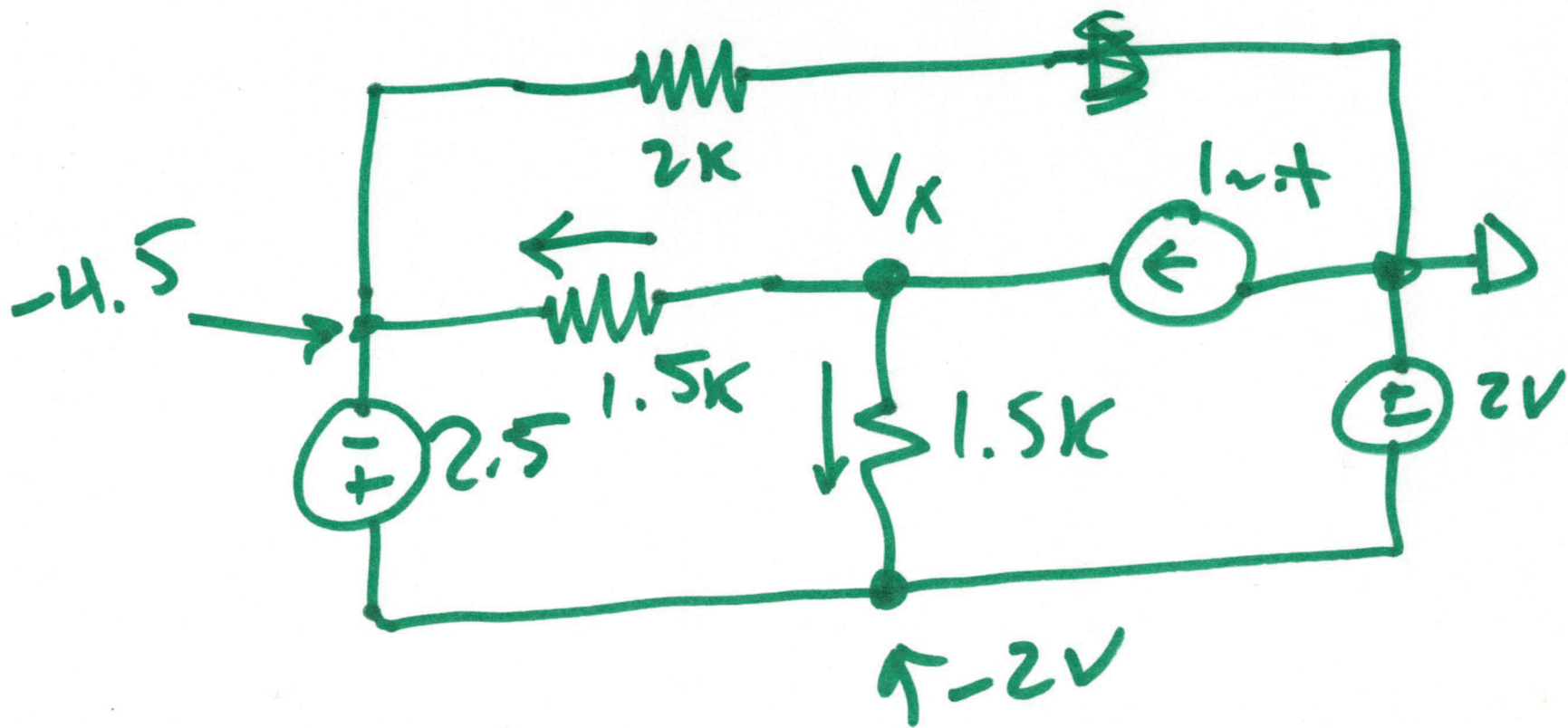


$$\frac{V_x - (-4.5)}{1.5k} + \frac{V_x - (-2)}{1.5k} = 1mA$$

$$V_x + 4.5 + V_x + 2 = 1.5$$


$$2V_x + 6.5 = 1.5$$

$$2V_x = -5V, \quad V_x = -2.5V$$


2)

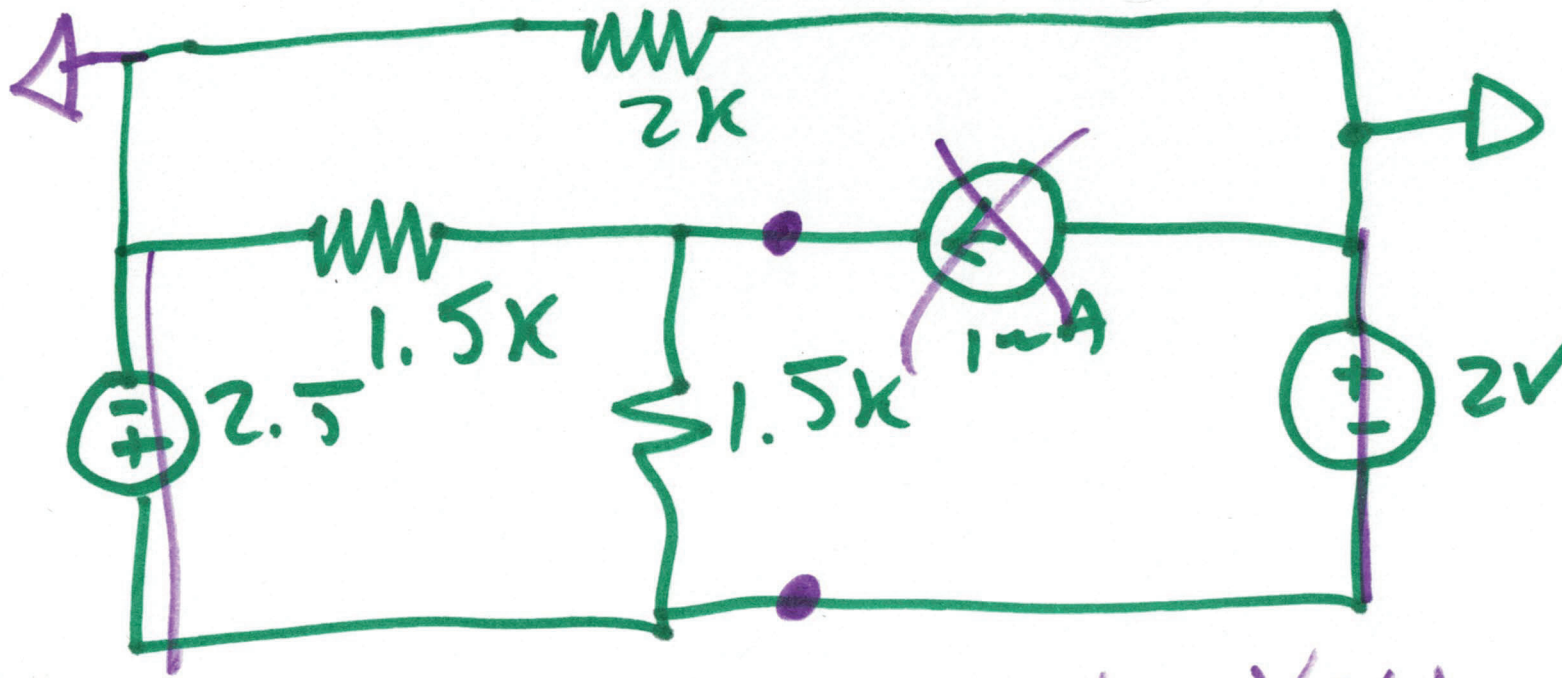

$$V_{oc} = V_x = -2.5V = V_{THN}$$

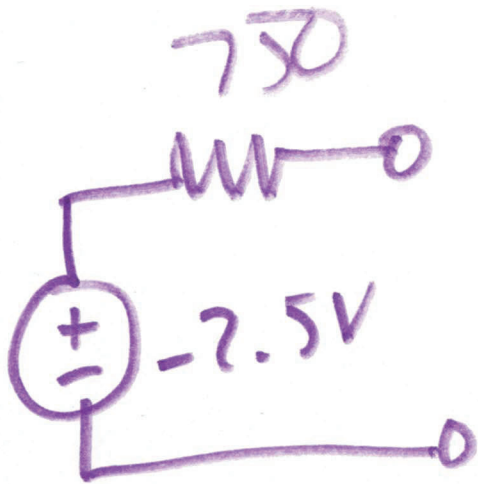
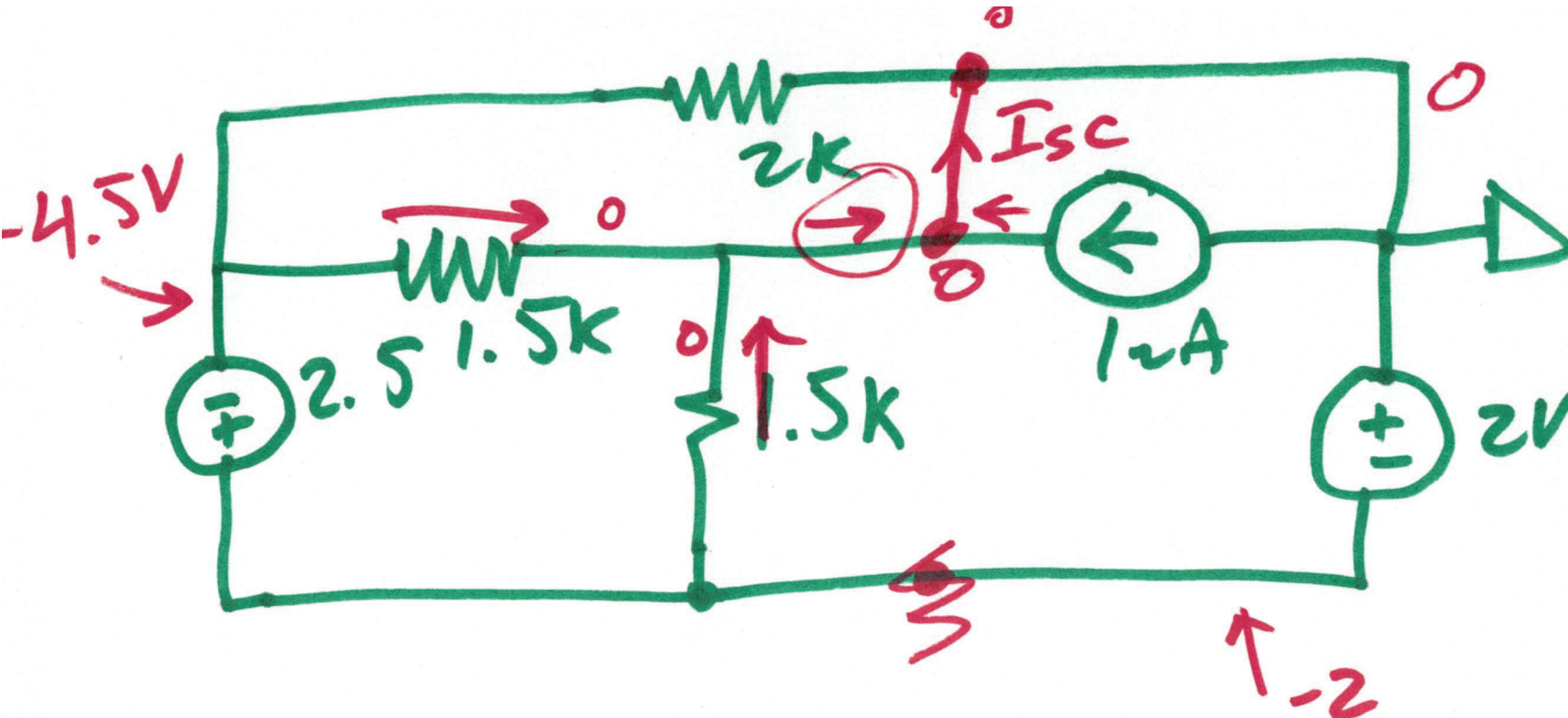
$$R_{THN} = \underbrace{1.5k \parallel 1.5k}_{750}$$



$$\frac{2}{3} = \frac{4}{3}$$

$$\frac{-4.5 - 0}{1.5k} + \frac{-2 - 0}{1.5k} + 1mA = I_{sc}$$

$$-3mA + -1.33mA + 1mA = I_{sc}$$

$$I_{sc} = -3.33mA$$




41

$$V_{oc} = -2.5V$$



$$I_{sc} = -3.33mA$$

$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{2.5}{3.33mA}$$


$$= 750\Omega$$

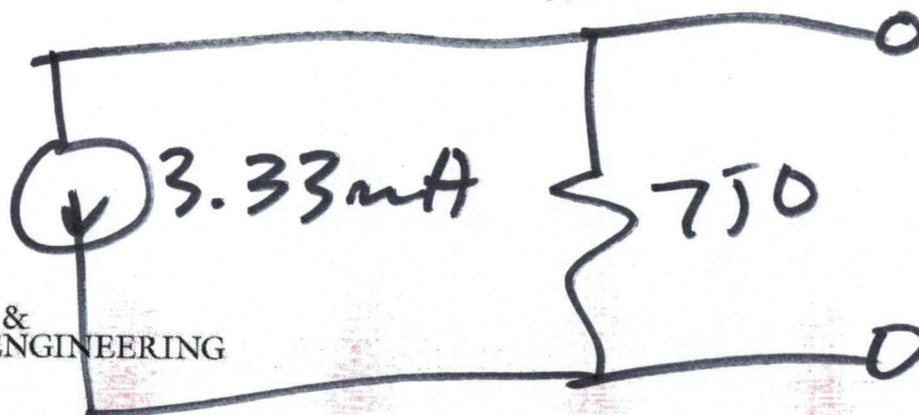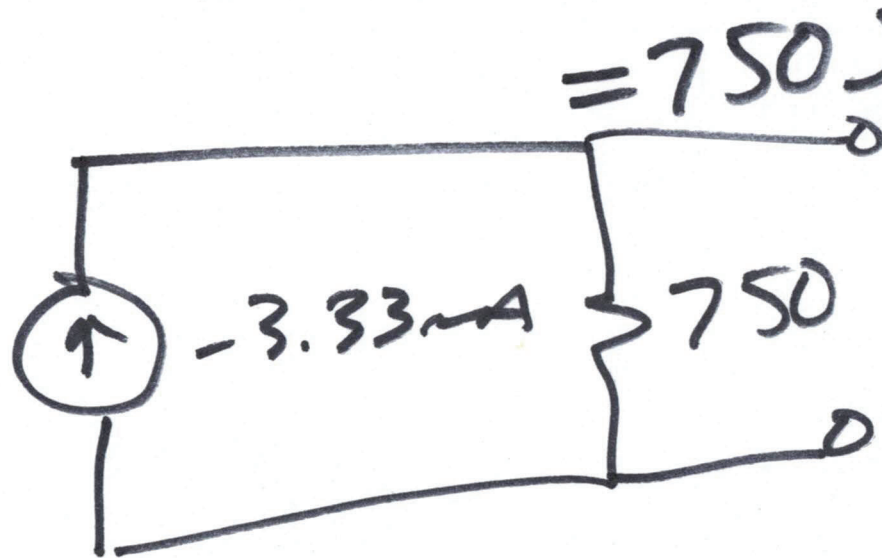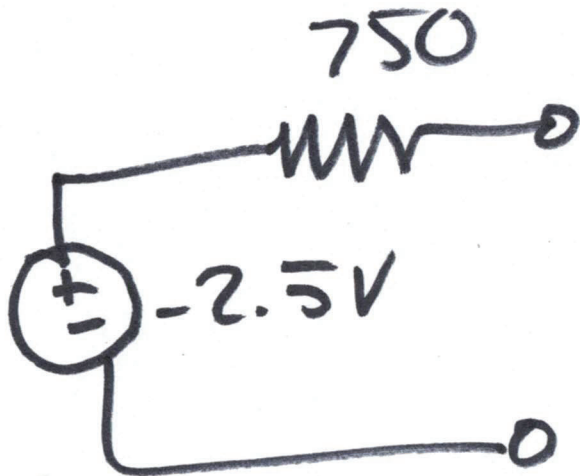

Power = Voltage · current

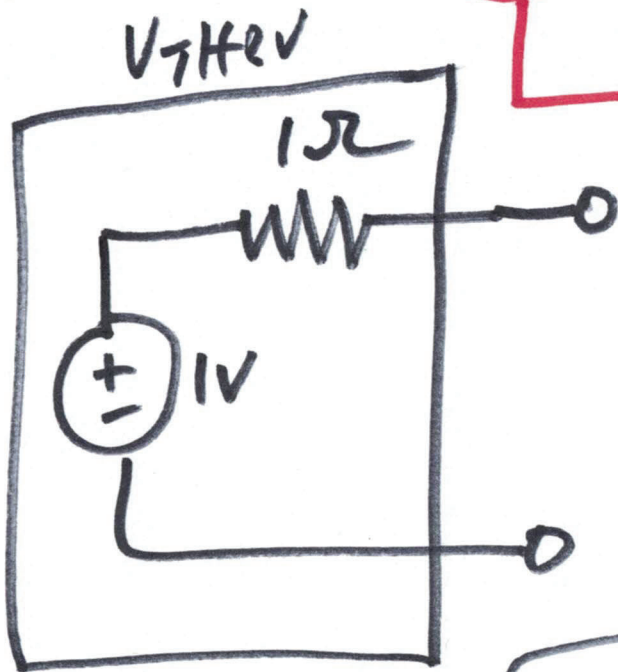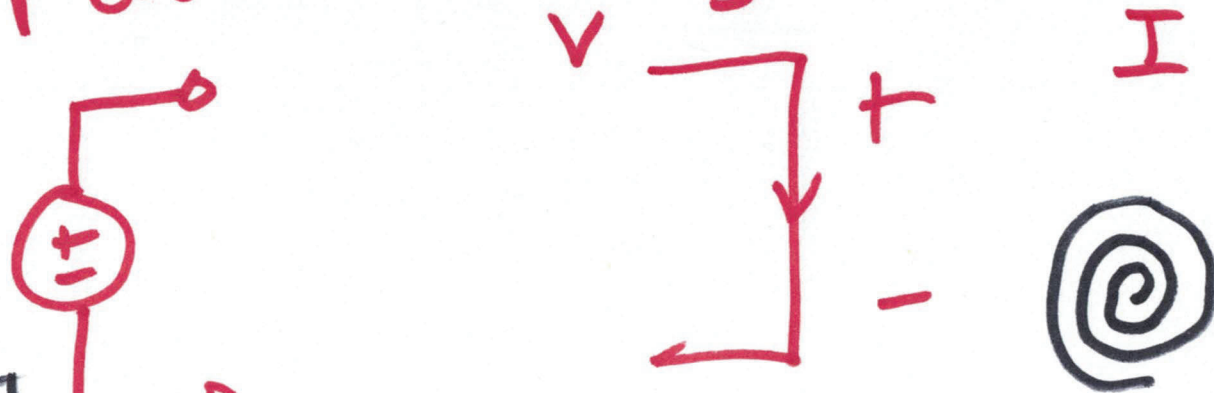

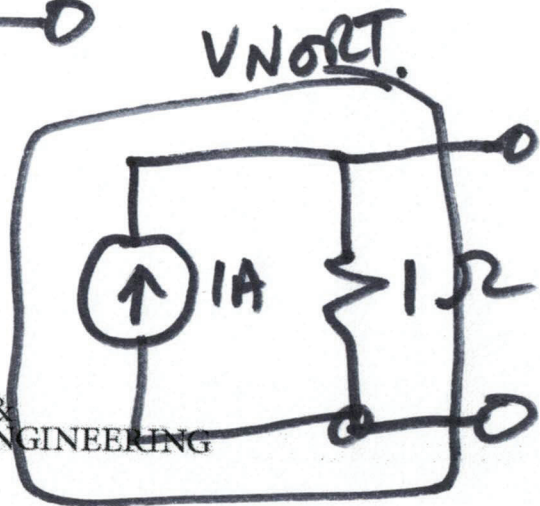
$$R = \frac{V}{I} \rightarrow I = \frac{V}{R}$$



$$P = VI = I^2R = \frac{V^2}{R}$$

b)

$$2kI_3 + 2.5 + 2 = 0$$

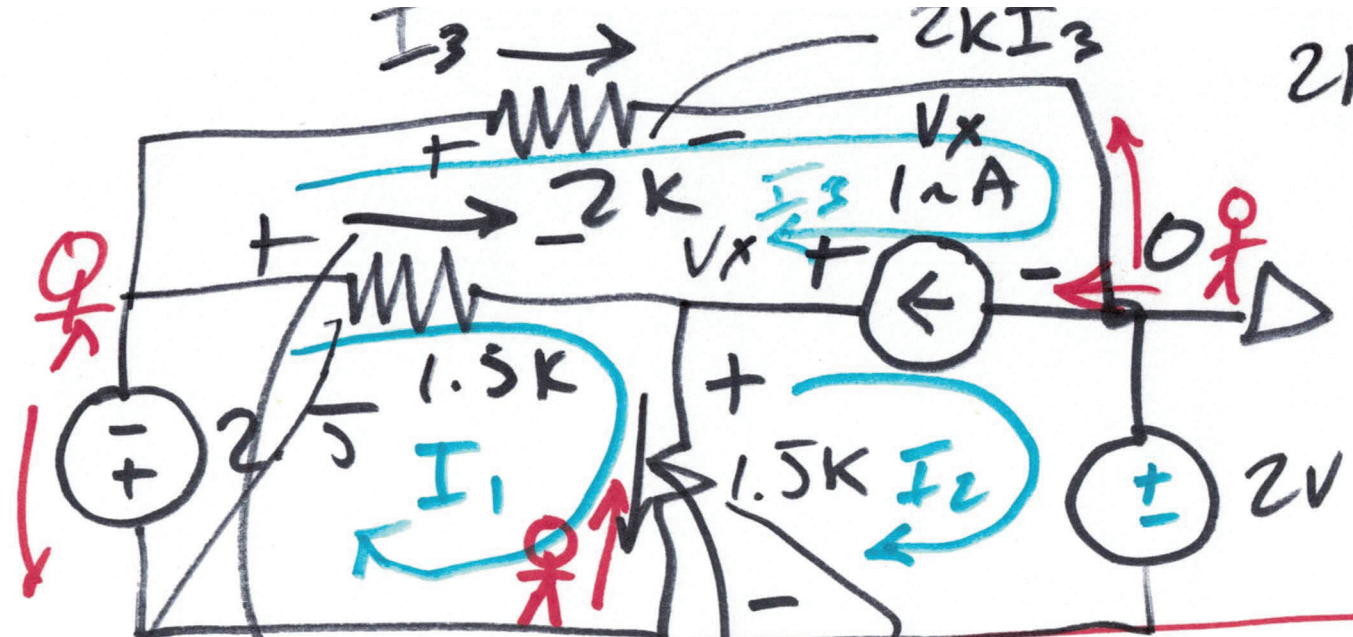

$$1mA = I_3 - I_2$$


$$1.5k(I_1 - I_3) \quad 1.5k(I_1 - I_2) \quad 1.5k(I_1 - I_2)$$

$$2kI_3 - 1.5k(I_1 - I_3) - V_x = 0$$

$$V_x - 1.5k(I_1 - I_2) + 2 = 0$$

1) $1.5k(I_1 - I_2) + 1.5k(I_1 - I_3) + 2.5 = 0$

2b

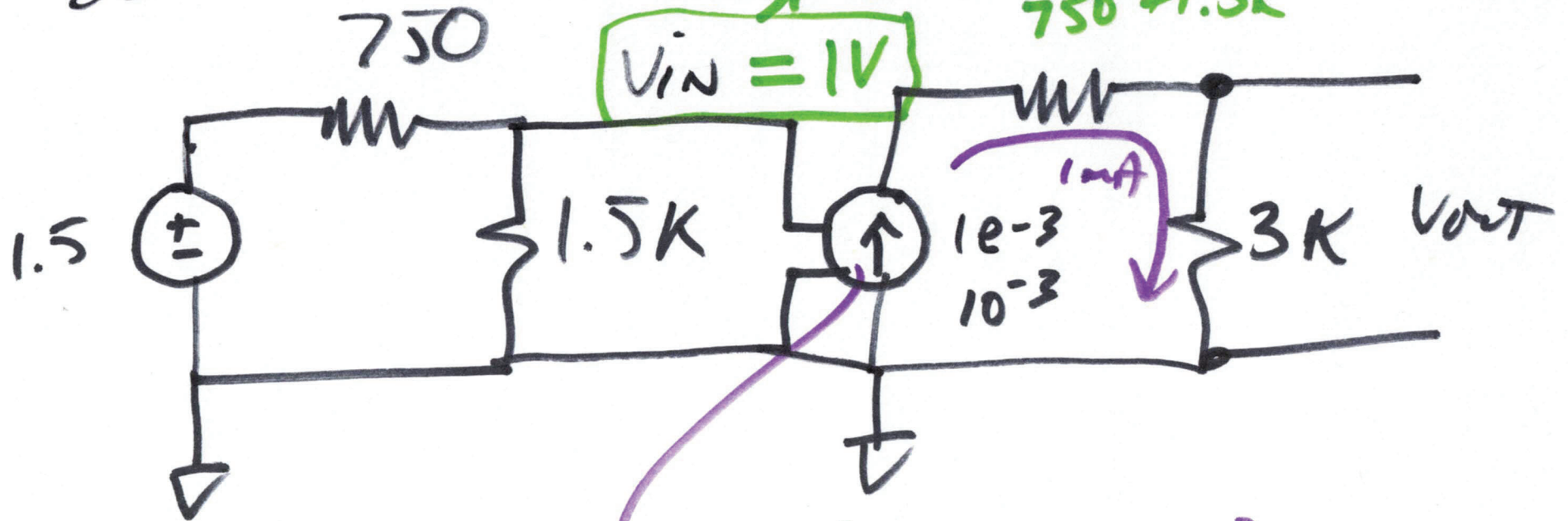


$$1.5 \cdot \frac{1.5K}{750 + 1.5K} = 1.5 \cdot \frac{2}{3}$$

$V_{IN} = 1V$


$$10^{-3} \cdot V_{IN} = 10^{-3} \cdot 1 = 1\mu A$$

$$V_{OUT} = 1\mu A \cdot 3K = 3V$$

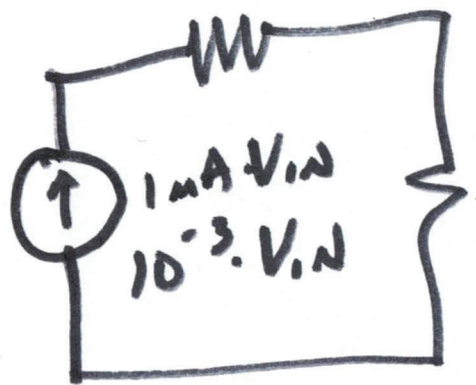

8)

2d

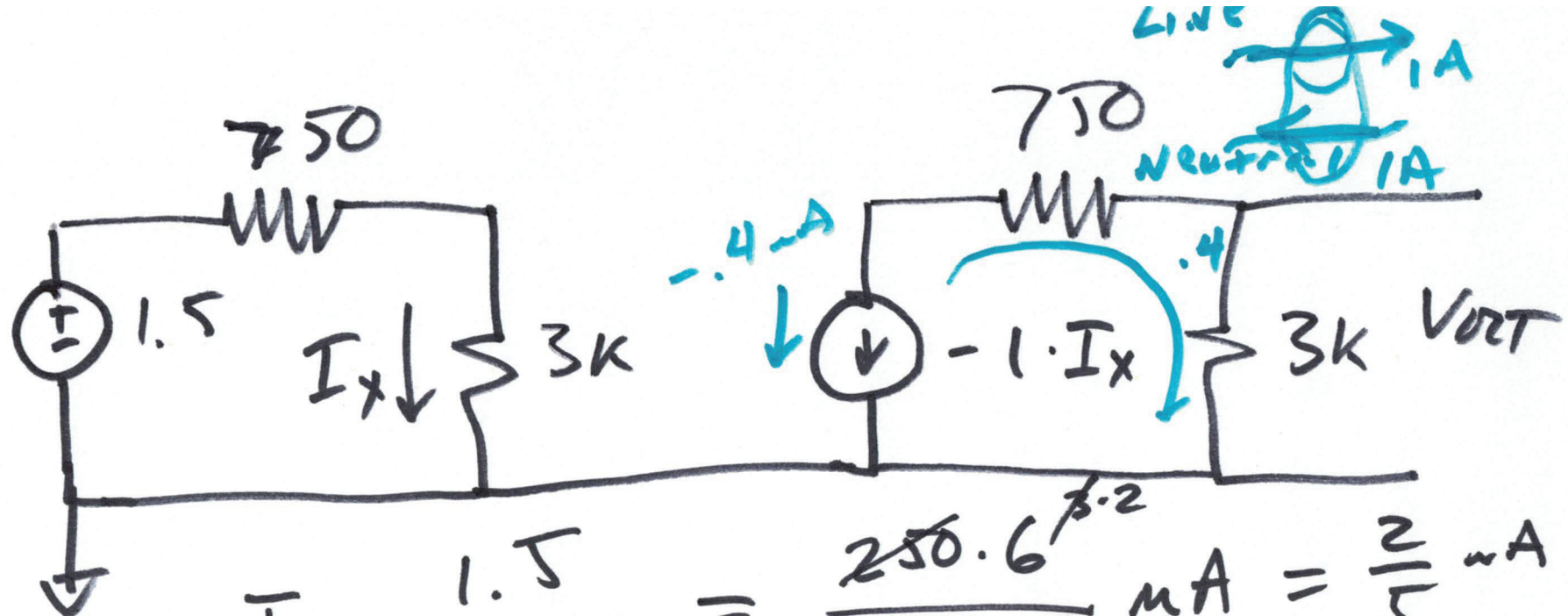

$$I_x = \frac{1.5}{3.75k} = \frac{250 \cdot 6^{0.2}}{250 \cdot 15^{0.5}} \mu A = \frac{2}{5} \mu A$$

$$I_x = 0.4 \mu A$$

$$\frac{250 \cdot 4}{1000} + \frac{250 \cdot 2}{500} = 1.5k$$

$$V_{out} = 3k \cdot \frac{2}{5} \mu A = \frac{6}{5} V = 1.2V$$

a)