
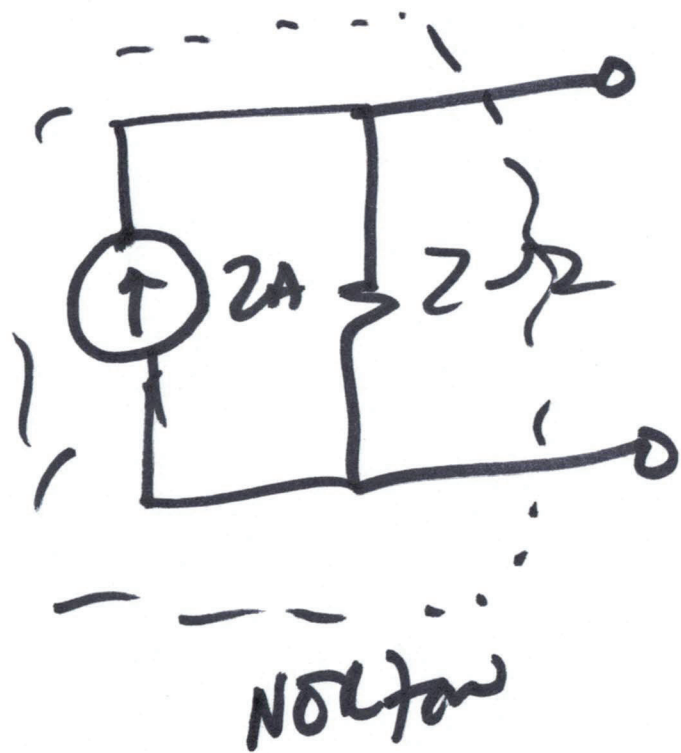


EE 220 Circuits 1

Sept. 27, 2021

Lecture 10

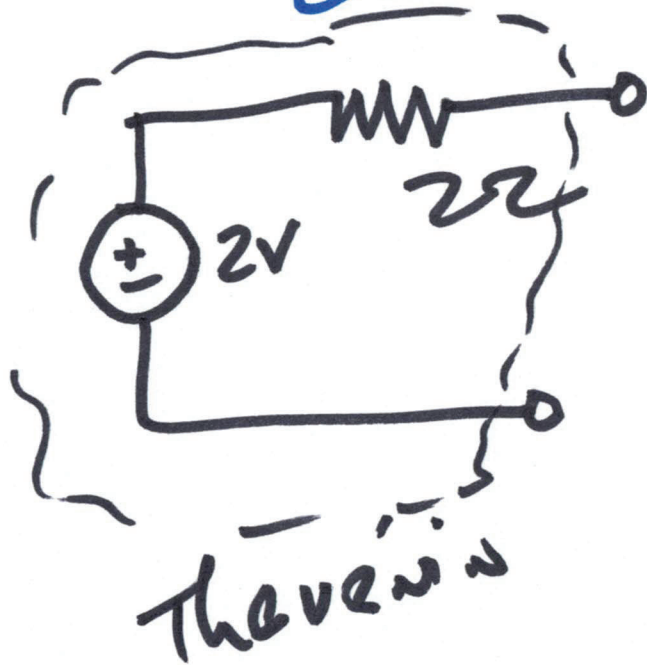

DC POWER

$$V = IR$$


$$I = \frac{V}{R}$$

$$\frac{V_{OC}^2}{R} = P_{OC} = I_{DC} \cdot V_{DC} = I_{DC}^2 \cdot R$$

$$P = 1mA \cdot 1V = 1mW$$


$$P = (10^{-3})^2 \cdot 1K = 1mW$$

$$P = \frac{(1)^2}{1K} = 1mW$$

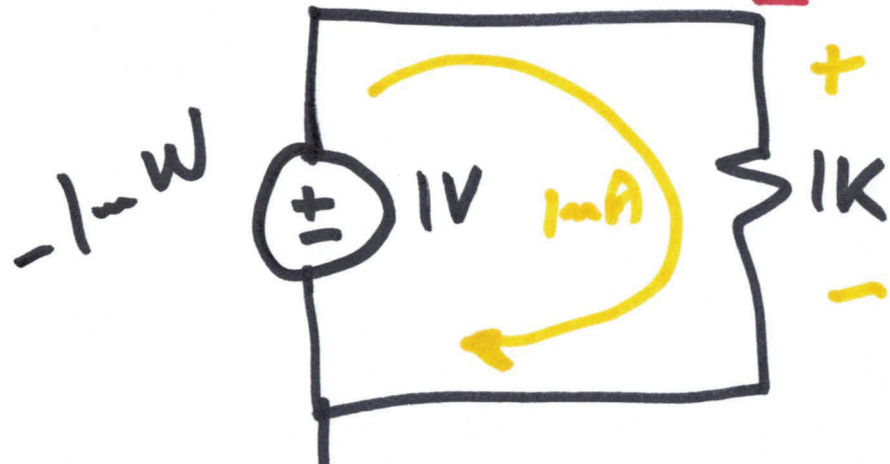

neg resistance
 source of power

MAXIMUM POWER TRANSFER

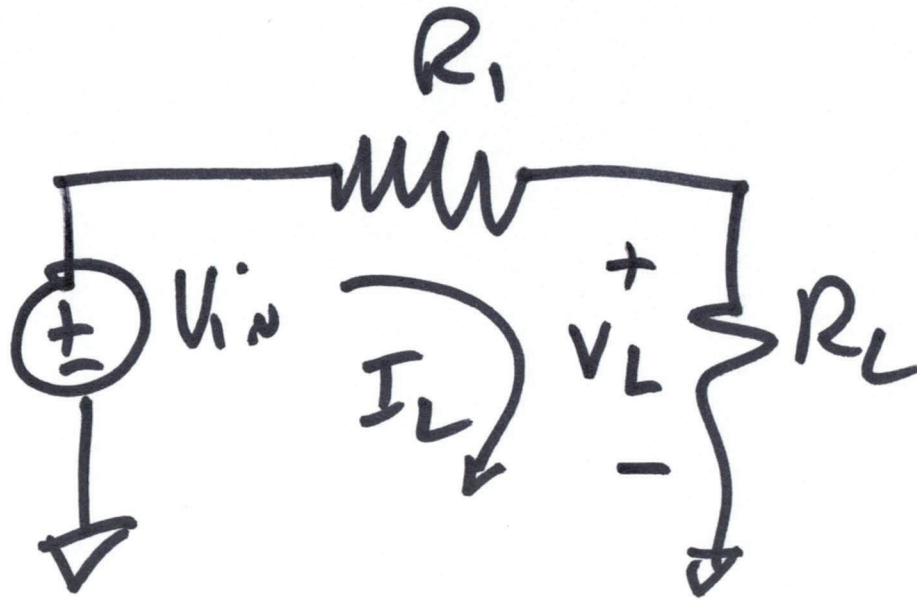

$R_L = ?$
for maximum
power transfer

$$P_L = V_L \cdot I_L = \frac{V_{in} \cdot R_L}{R_L + R_1} \cdot \frac{V_{in}}{R_1 + R_L}$$

$$P_L = V_{in}^2 \cdot R_L (R_L + R_1)^{-2}$$



MAX power transfer

$$0 = \frac{d}{da} a \cdot (a+b) \frac{dP_L}{dR_L} = 0 = \frac{d}{dR_L} \left(\frac{V_{oc}}{R_L} \cdot R_L (R_L + R_i)^{-2} \right)$$

$$\frac{d}{dR_L} (R_L + R_i)^{-2} R_L = 0$$


$$0 = \left[(R_L + R_i)^{-2} + R_L (-2) (R_L + R_i)^{-3} \frac{d(R_L + R_i)}{dR_L} \right]$$

$$0 = 1 + (-2) R_L (R_L + R_i)^{-1}$$

$$\frac{2R_L}{R_L + R_1} = 1$$

$$2R_L = R_L + R_1$$

$$R_L = R_1$$

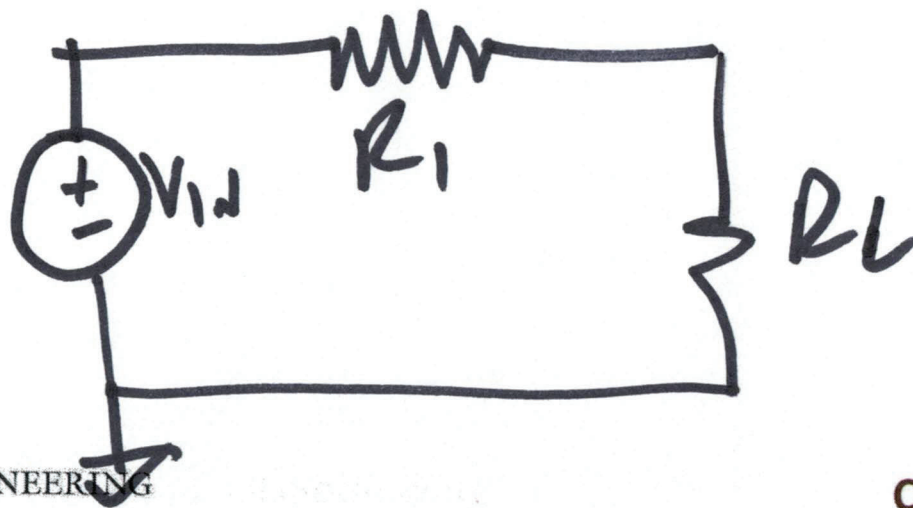

5)

$$\text{Power} = \text{Watts}$$

$$\text{WATTS} = \frac{\text{Joules}}{\text{s}}$$

1sRC

650

$$\text{Energy} = \text{Joules}$$



$$\mathcal{E} = \int_0^t P_{DC} \cdot dt$$

$$\mathcal{E} = \int_0^1 1 \mu\text{W} \cdot dt = 1 \mu\text{W} \cdot (t_1 - t_0)$$

$$= 1 \mu\text{J}$$

CMOSedu.com

NV ENERGY

\$15/kw.hr

$1,000W \cdot 3,600s$
1,000,000 J

60W INCANDESCENT bulb


2,000 hrs

$$\frac{\$15}{kw.hr} \cdot 60W \cdot 2,000hrs =$$

$$= \$18.00$$

\$2.50

→ 7W

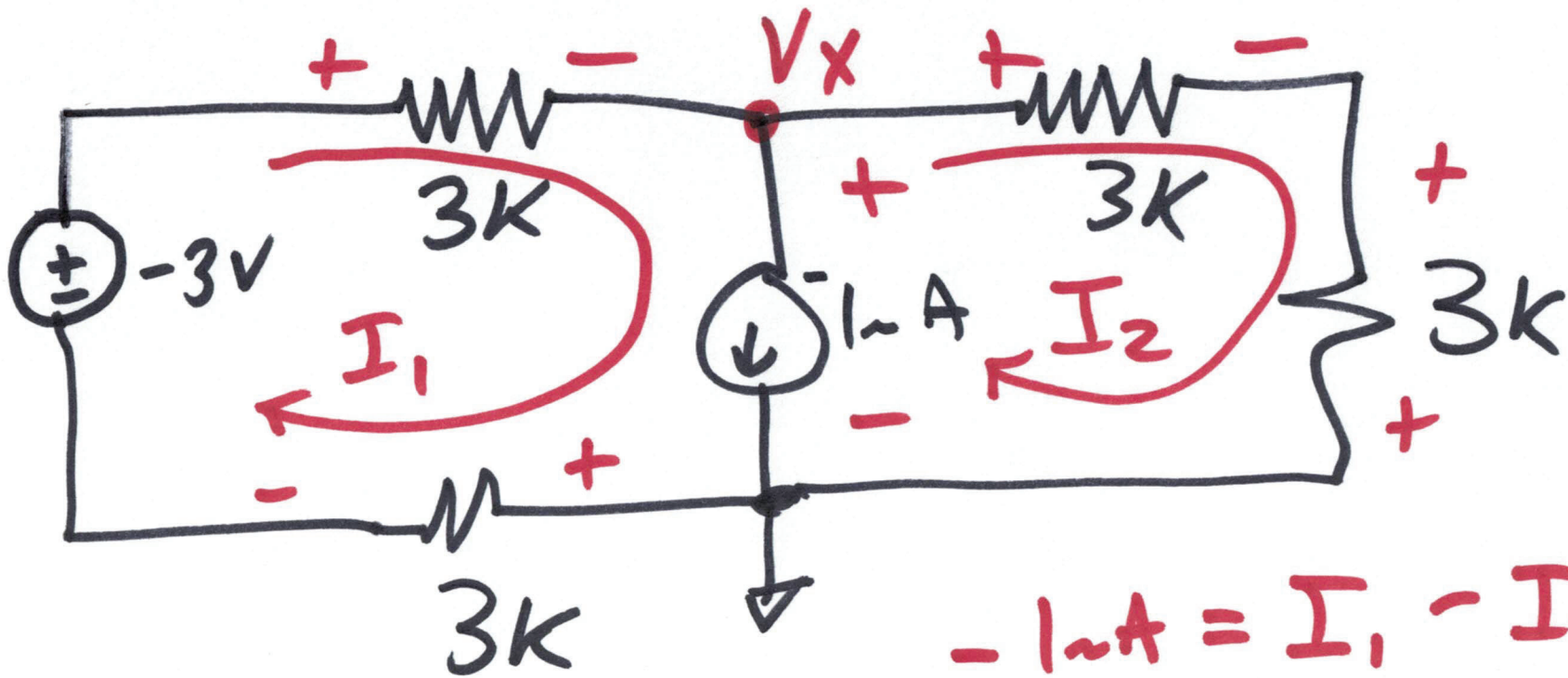

$$-1\text{mA} = I_1 - I_2$$

$$-3\text{k}I_1 + (-3\text{V}) - 3\text{k}I_1 - V_x = 0$$

$$I_1 = \frac{V_x}{6\text{k}} - 1\text{mA}$$

$$\frac{V_x}{6\text{k}} = I_2$$

8)

$$-6k \left(\frac{V_x}{6k} - 1\mu A \right) - 3 - V_x = 0$$


$$-V_x + 6V - 3 - V_x = 0$$

$$2V_x = 3V$$

$$V_x = 1.5V$$

$$\frac{1.5V - 0}{6k} = 250\mu A$$

3... $75\mu A$
 $2.25\mu W$

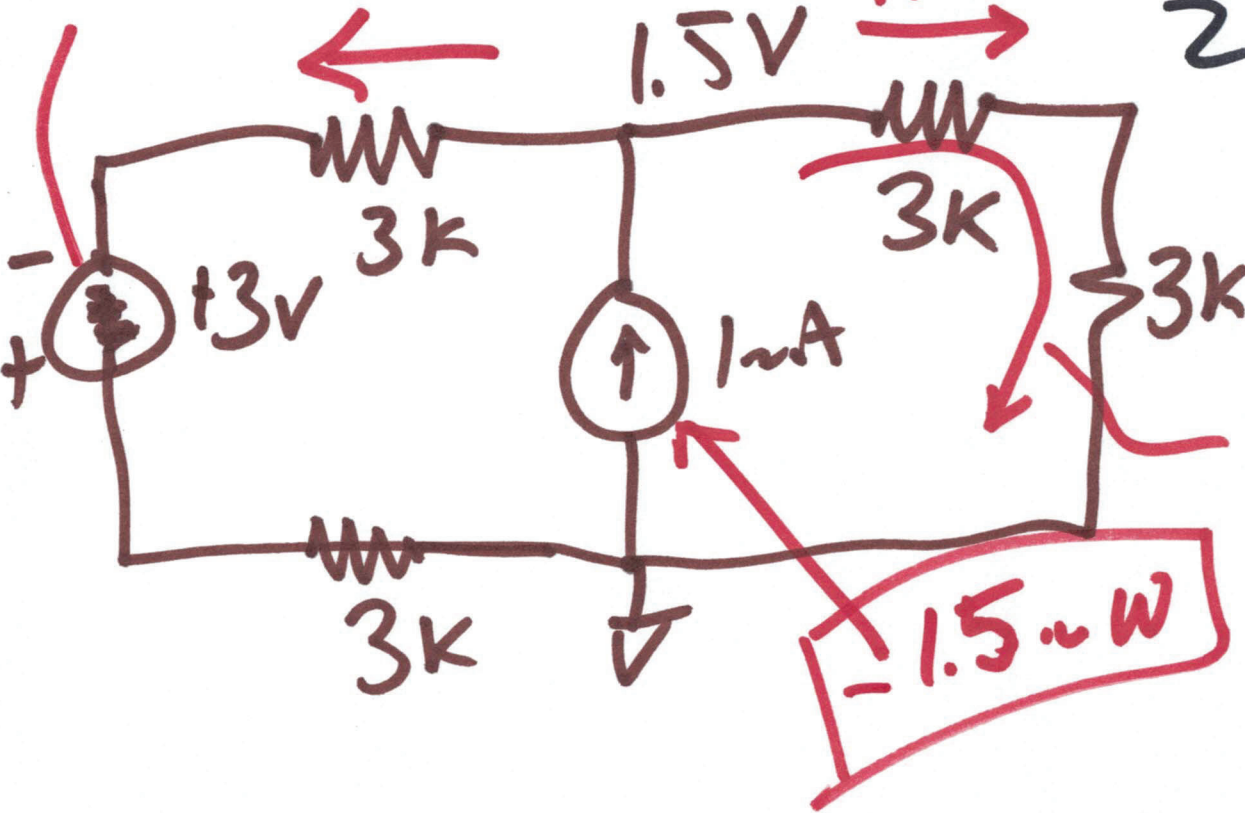

9)

$$P_T = 2.25 + 1.5 = 3.75 \text{ mW}$$

$$3k \left(\frac{3}{4} \text{ mA} \right)^2 + 3k \left(\frac{3}{4} \text{ mA} \right)^2 + 3k \left(\frac{1}{4} \text{ mA} \right)^2 + 3k \left(\frac{1}{4} \text{ mA} \right)^2$$

$$3k \left(\frac{9}{16} + \frac{9}{16} + \frac{1}{16} + \frac{1}{16} \right)$$

$$3k \left(\frac{20}{16} \right) = \frac{60}{16} \text{ mW}$$

$$= \underline{\underline{3.75 \text{ mW}}}$$