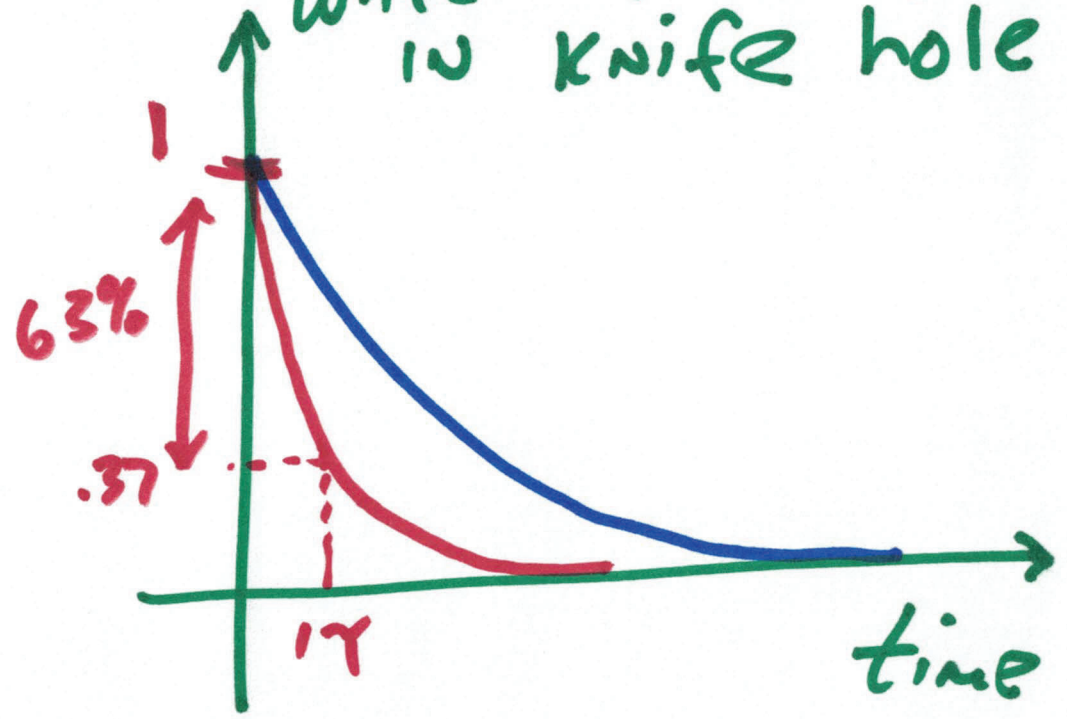



EE 270 circuits 1

OCT. 18, 2021

Lecture 15  
water flowing  
in knife hole



11

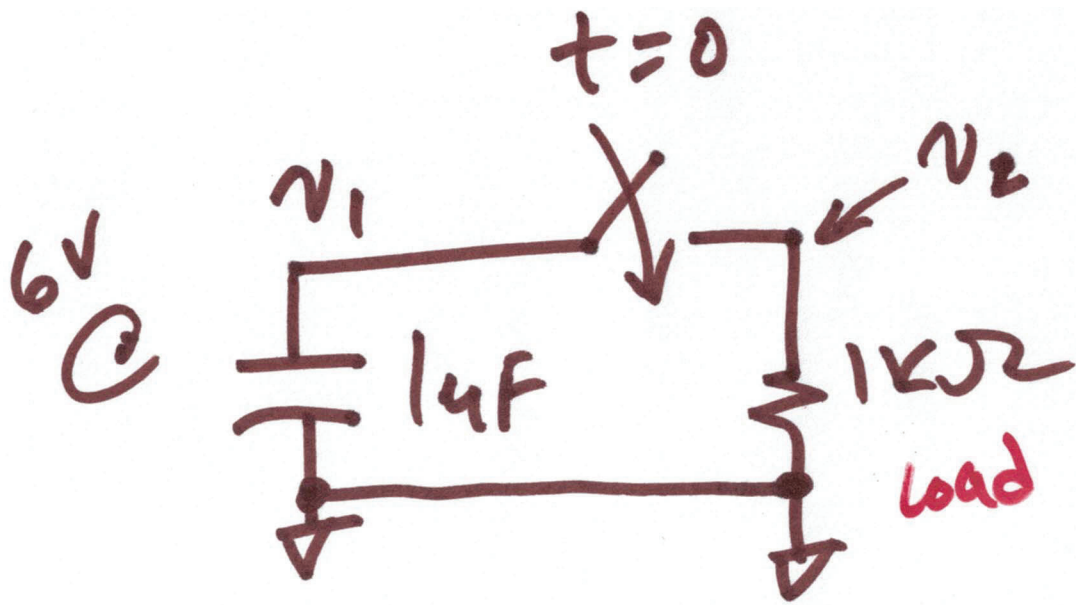

Before switch closes

$$v_2 = 0$$

$$v_1 = 6V$$

$$CV = Q$$

$$1\mu F \cdot 6V = 6\mu C$$

Farad

coulombs

After switch closes

$$v_1 = v_2$$

$$-t/RC \cdot V_f = 0$$

$$v_1 = v_2$$

$$T = RC \text{ (seconds)}$$


$$v_2(t) = v_1(t) = V_f + (v_i - V_f)e^{-t/RC}$$

$$v_i(t) = 6e^{-t/RC}$$

2)

$$v(t) = v_f + (v_i - v_f) e^{-t/RC}$$

$$t = 2\text{ms}$$

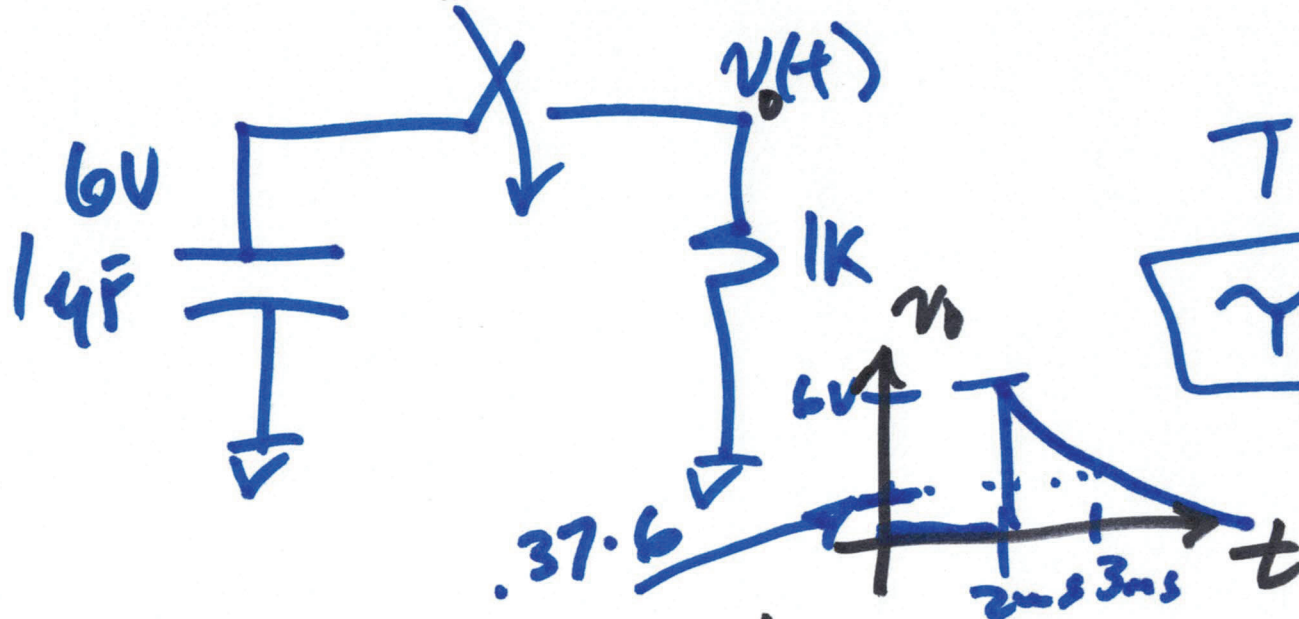

$$T = 1K \cdot 14$$

$$\tau = 1\text{ms}$$


$$v_0(t) = 0 \quad t \leq 2\text{ms}$$

$$v_0(t) = 6 e^{-\frac{(t-2\text{ms})}{1\text{ms}}} \quad t \geq 2\text{ms}$$

$$\frac{-(t-2\text{ms})}{1\text{ms}}$$

RC

3)

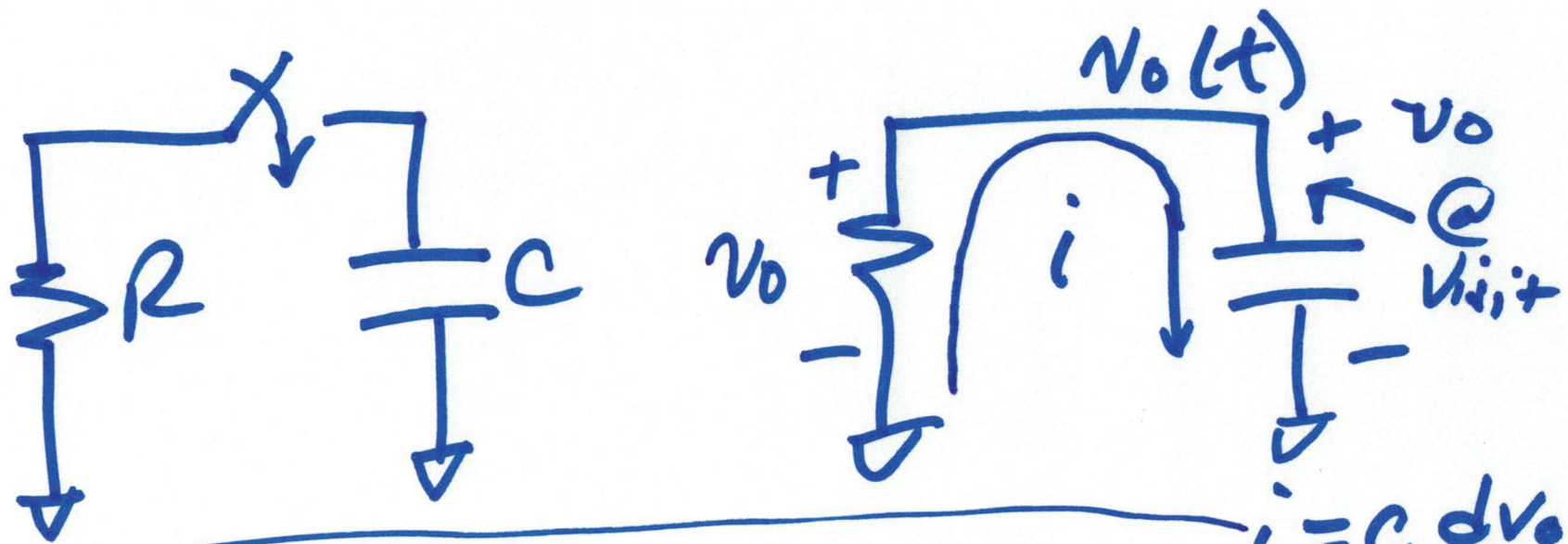

BOUNDARY CONDITIONS

$$v_0(0) = V_{init}$$

$$v_0(\infty) = 0$$

$$v_0(t) = -i \cdot R$$

$$v_0(t) = -RC \frac{dv_0(t)}{dt}$$

$$\int_0^t \frac{dt}{-RC} = \int_{V_{init}}^{v_0} \frac{dv_0}{v_0}$$

$$-\frac{t}{RC} = \ln x \Big|_{V_{init}}^{v_0}$$

4)


$$-\frac{t}{RC} = \ln V_0(t) - \ln V_{init}$$

$$e^{-\frac{t}{RC}} = \ln \frac{V_0(t)}{V_{init}}$$

$$e^{-t/RC} = \frac{V_0(t)}{V_{init}}$$

$$V_0(t) = V_{init} e^{-t/RC}$$

5)

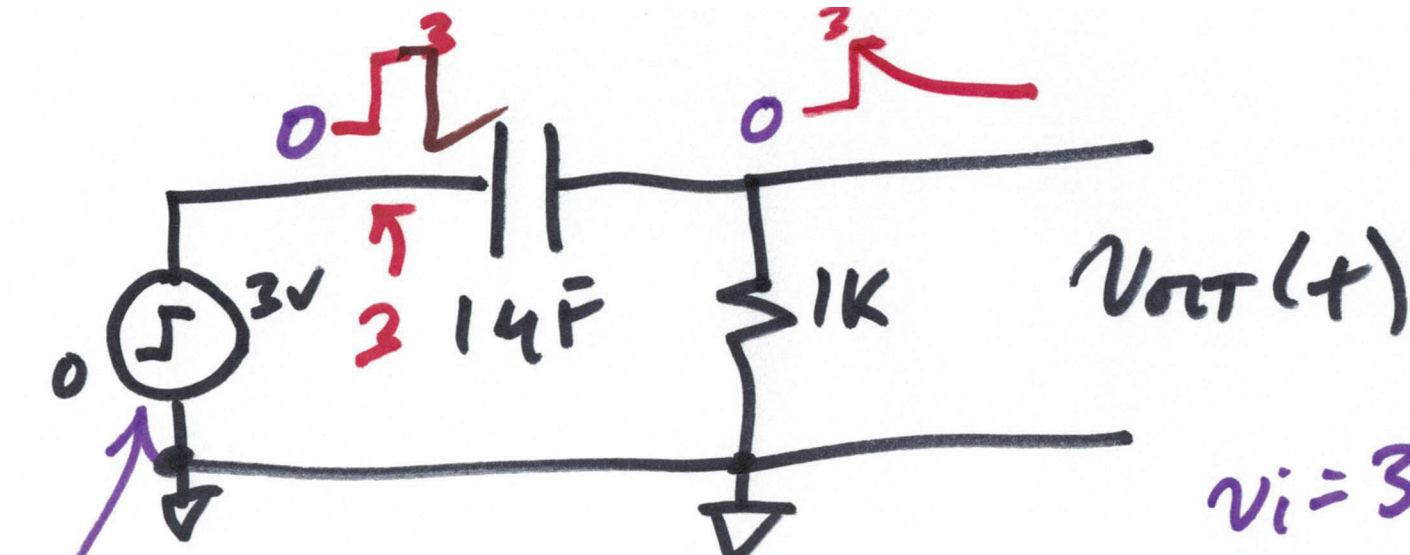


pulse from  
0 to 3

$$v_i = 3V$$

$$v_f = 0$$

$$v = v_f + (v_i - v_f)e^{-t/RC}$$

$$= 3e^{-t/RC}$$

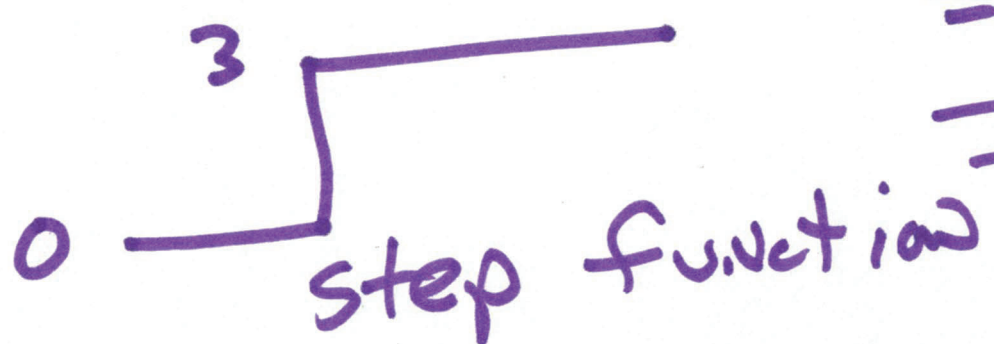

6)

