


EE 221 Circuits 1

OCT. 29, 2021

Lecture 17

$$i = \frac{1}{L} \int v \cdot dt$$

$$v = L \cdot \frac{di}{dt}$$

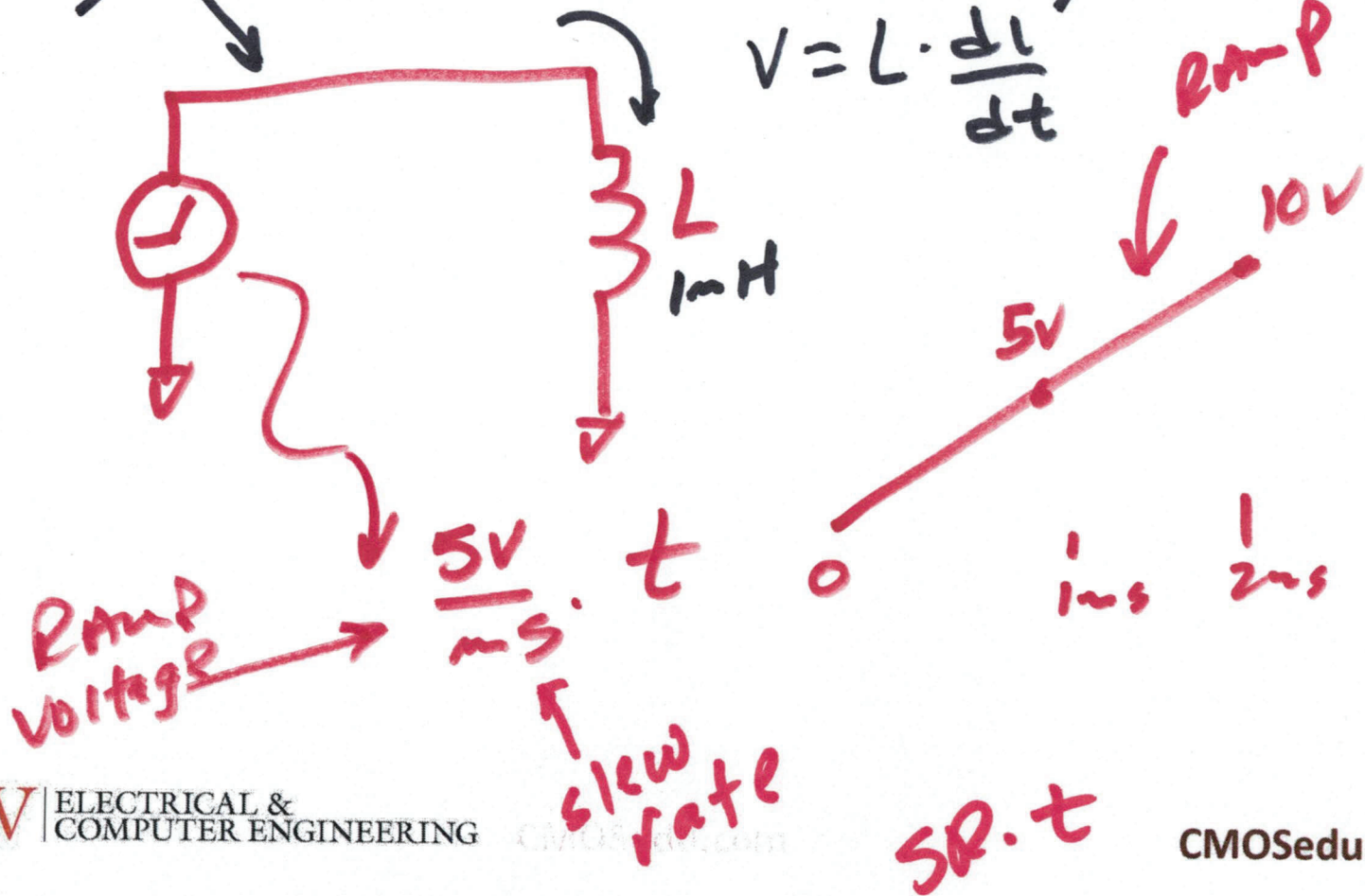

$$i = \frac{1}{L} \int v(t) \cdot dt$$


$$i = \frac{1}{1\mu\text{H}} \int_0^{t \swarrow \text{SR}} \frac{5\text{V}}{\text{ms}} \cdot dt = \frac{1}{1\mu\text{H}} \cdot \frac{5}{1\text{ms}} \cdot \frac{t^2}{2} \Big|_0^t$$

10^{-3} 10^{-3}

\leftarrow start of simulation

$$i(t) = \frac{2.5\text{A}}{(10^{-3}\text{s})^2} \cdot t^2$$

2)

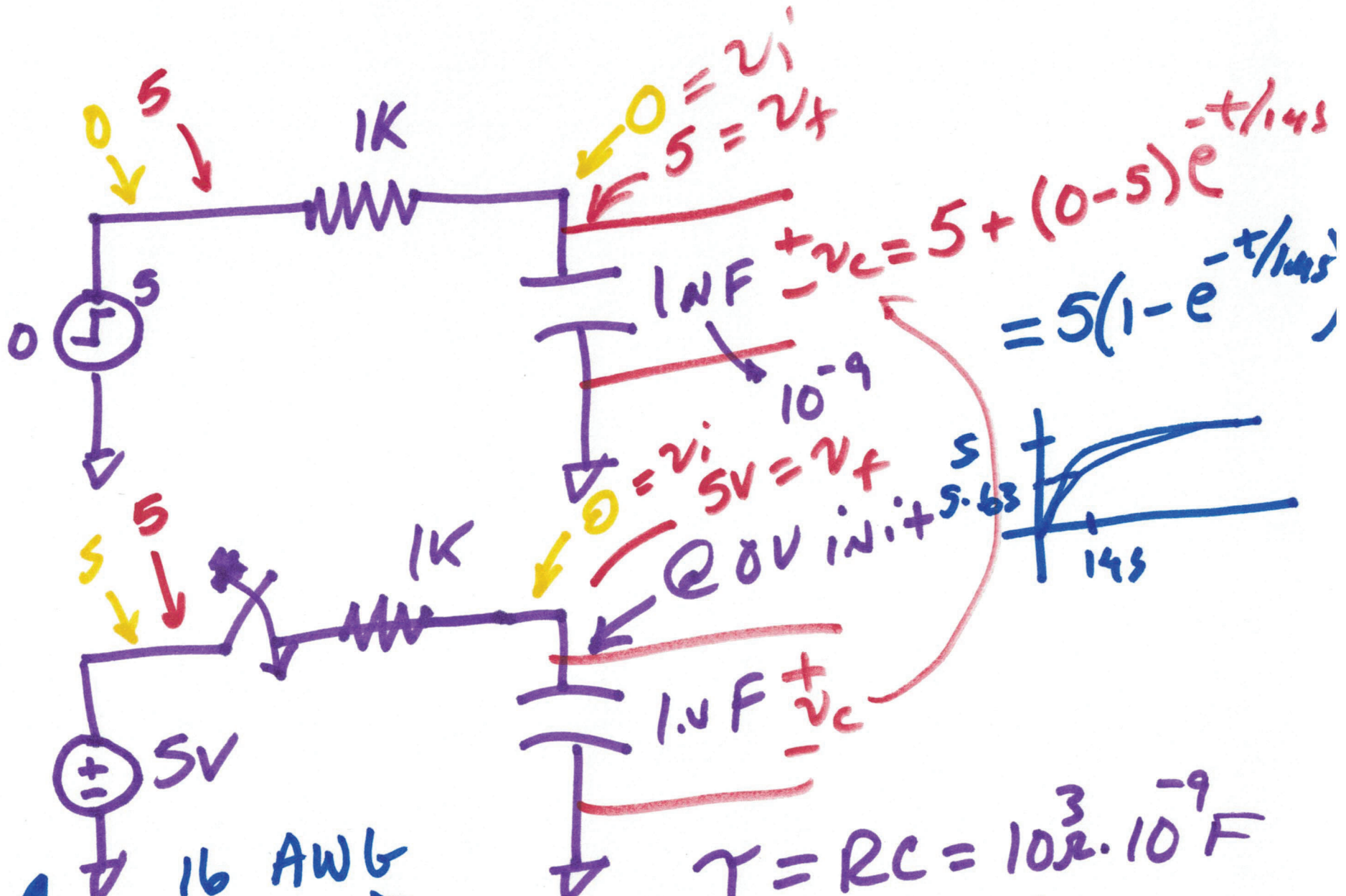


16 AWG

AMERICAN
wire
gauge


3)

$$v_c(t) = 5 \left(1 - e^{-\frac{(t-1\mu s)}{1\mu s}} \right) \quad t \geq 1\mu s$$

$$v_c(t) = 0 \quad t \leq 1\mu s$$

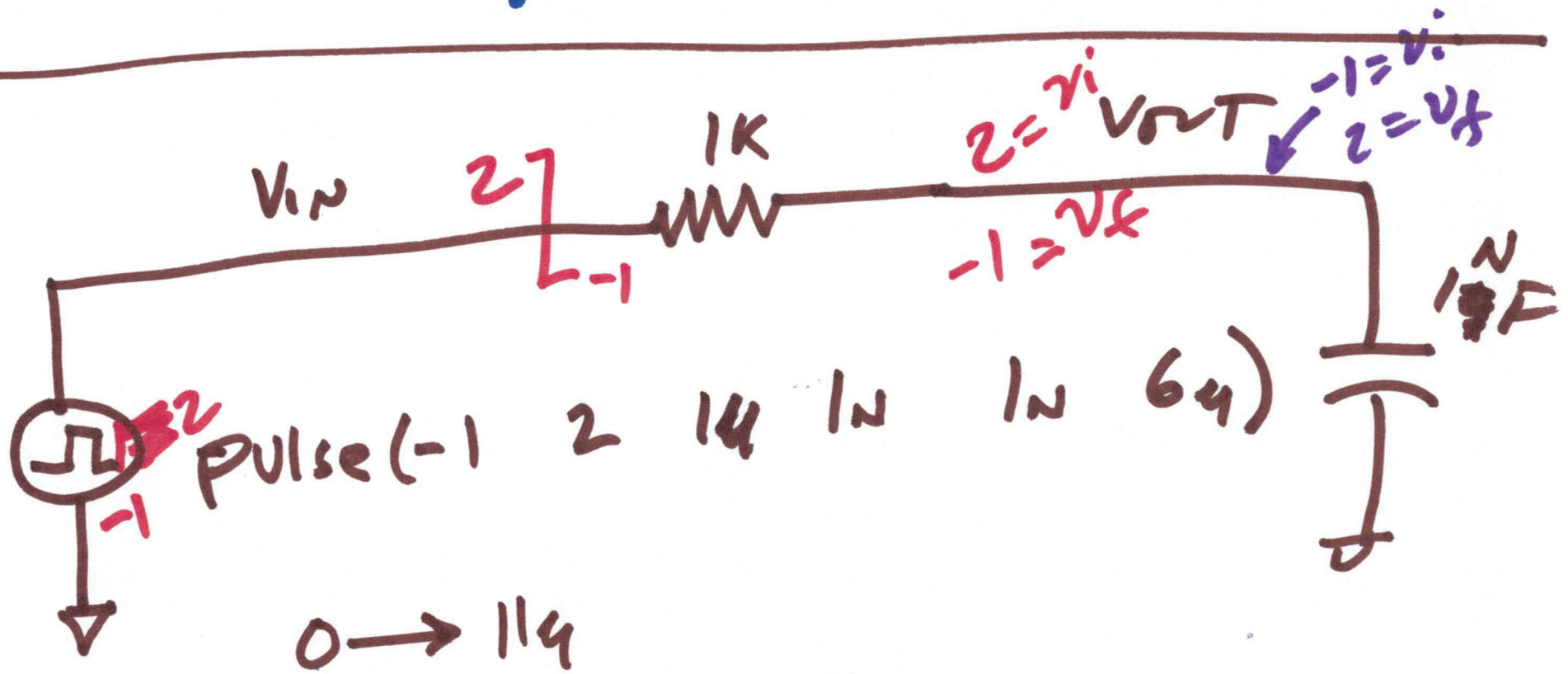

4)

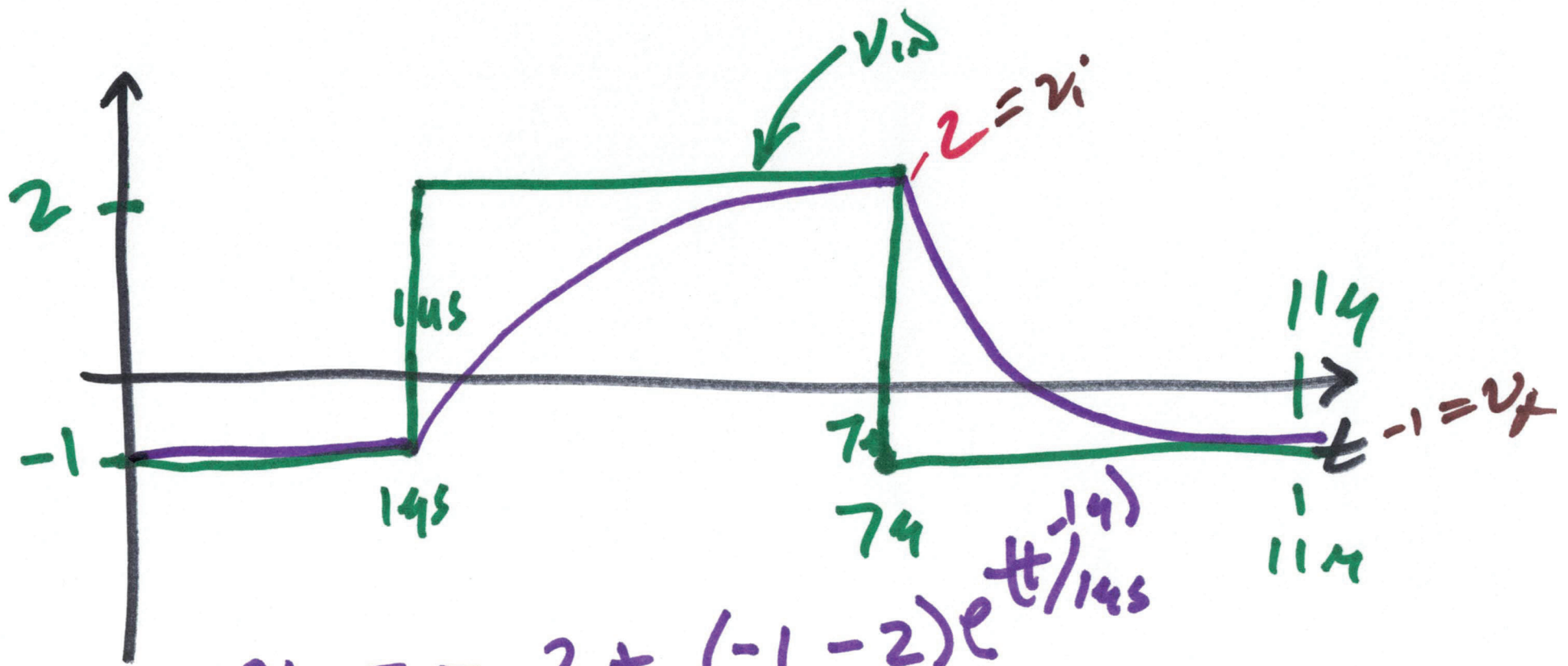

$$v_{out} = 2 + (-1 - 2)e^{t/145}$$


$$145 \leq t \leq 74$$

$$v_{out} = -1V \quad t \leq 145$$

$$v_{out} = -1 + (2 - (-1))e^{-t/114}$$

$$t \geq 74$$


5)

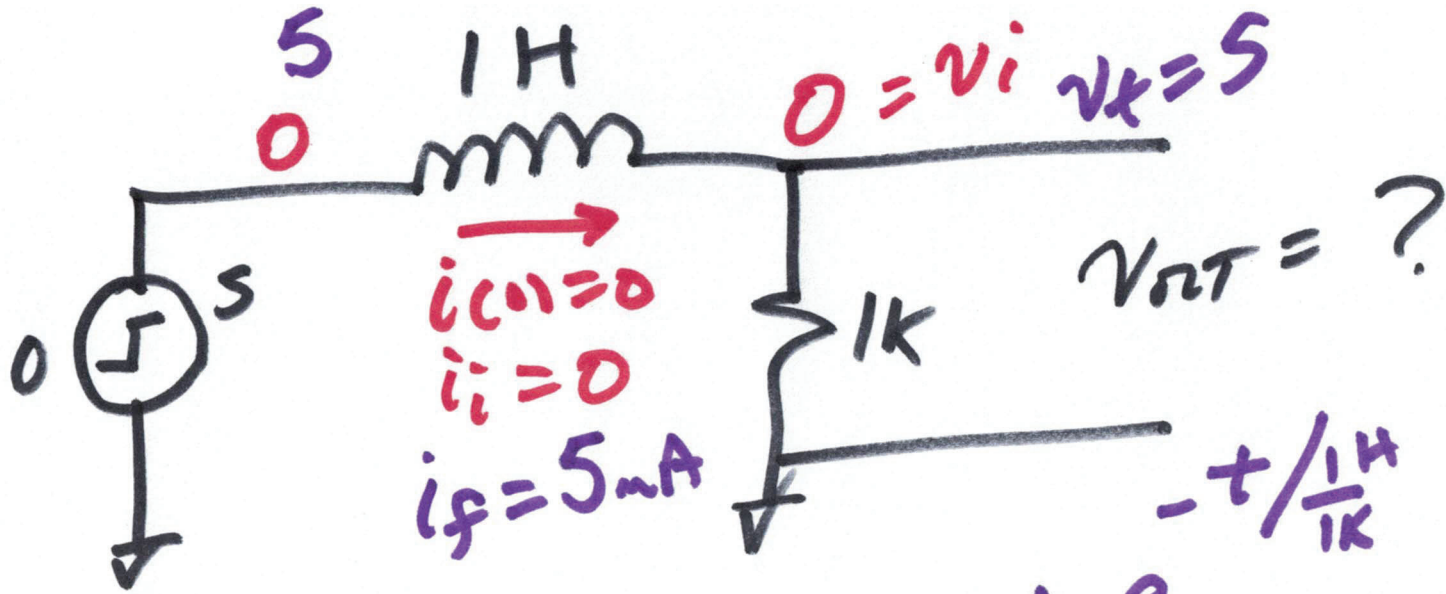

$$v_{out} = 5 + (0 - 5) e^{-t / \frac{1 \text{ H}}{1 \text{ k}}}$$

$$i = 5 \text{ mA} + (0 - 5 \text{ mA}) e^{-t / \frac{1 \text{ H}}{1 \text{ k}}}$$

6)

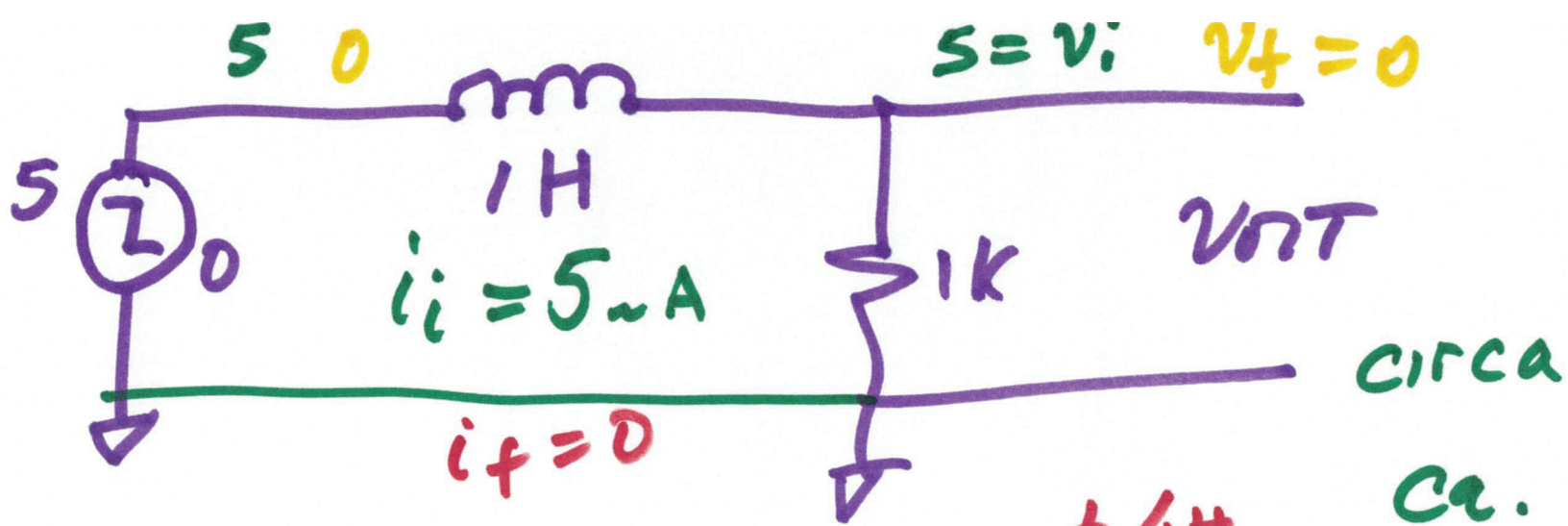


$$v_{OUT}(t) = 0 + (5 - 0)e^{-t / \frac{1 \text{ H}}{1 \text{ k}}} \text{ ca. } 1880$$

$$i(t) = 0 + (5 \text{ mA} - 0)e^{-t / \frac{1 \text{ H}}{1 \text{ k}}}$$

$$\tau_L = \frac{L}{R} \text{ (seconds)}$$

$$\tau_R = RC \text{ (seconds)}$$



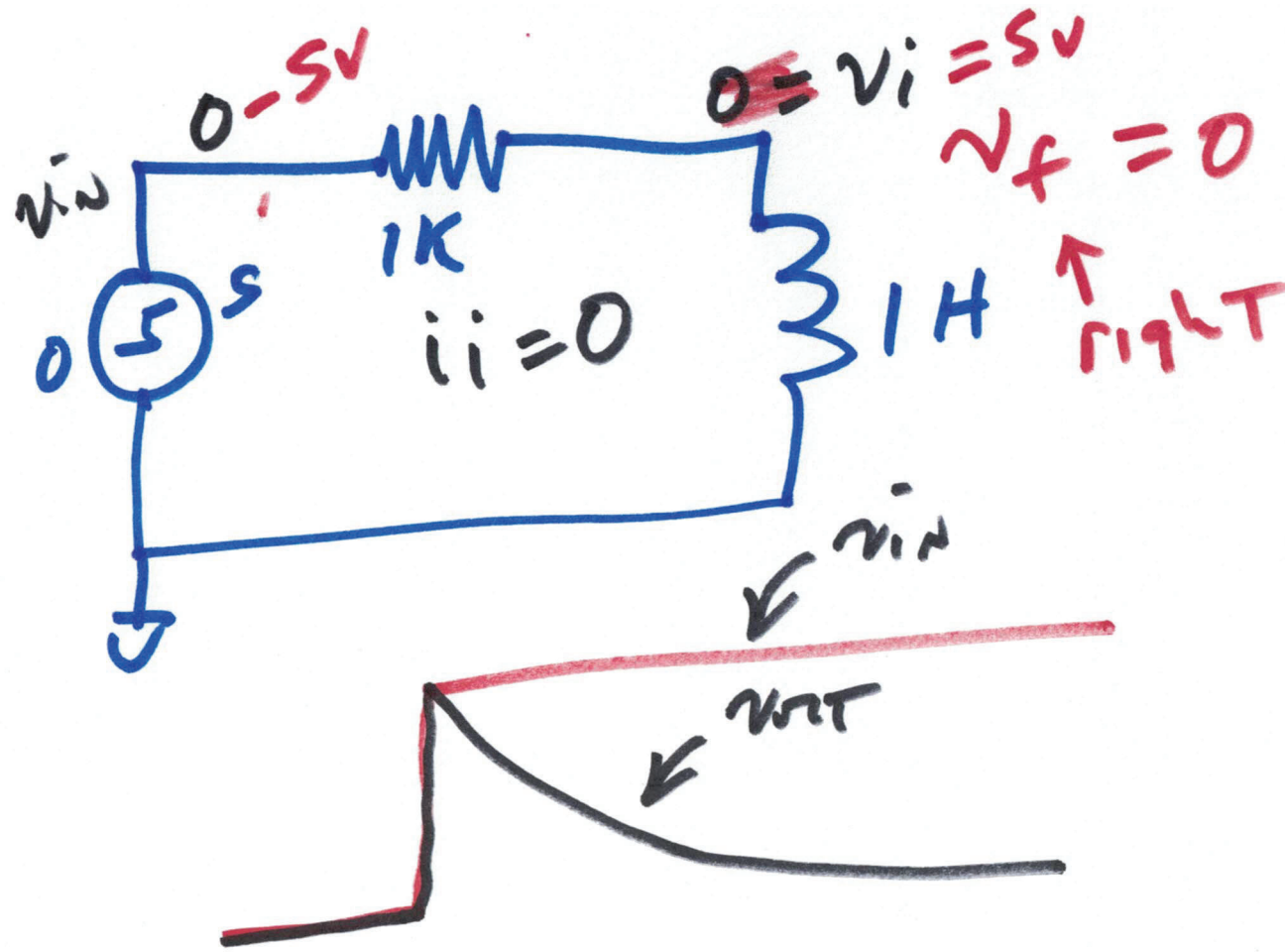

8)