


# EE 220 CIRCUITS 1

## Lecture 18

OCT. 27, 2021

$$v_i = 4V \times 0 = 0$$
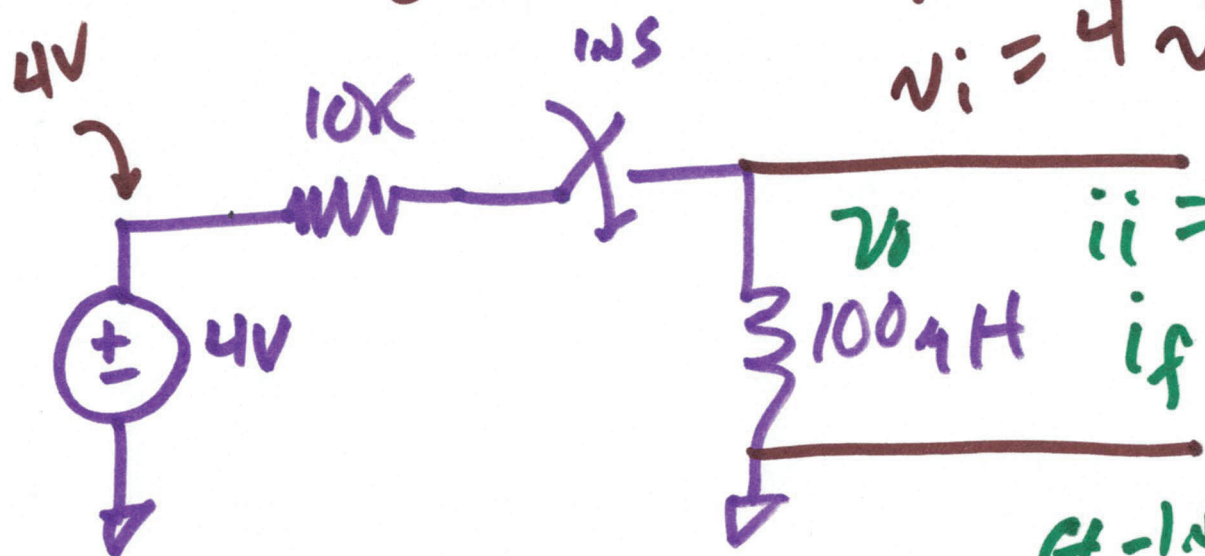
$$\frac{L}{R} = \frac{100 \times 10^{-6}}{10^4} = 10^2 \times 10^{-10} = 10 \text{ ns}$$



$$i_f = \frac{4}{10K} = 400 \mu A = 0.4 \text{ mA}$$


$$v_0 = 0 + (4 - 0) e^{-\frac{(t - 1 \text{ ns})}{10 \text{ ns}}}$$

$t \geq 1 \text{ ns}$


$$i = \frac{4 - v_0}{10K} = 0.4 \text{ mA} - 0.4 \text{ mA} e^{-\frac{(t - 1 \text{ ns})}{10 \text{ ns}}}$$

$$v_0 = 4 e^{-\frac{(t-1\text{ns})}{10\text{ns}}}$$
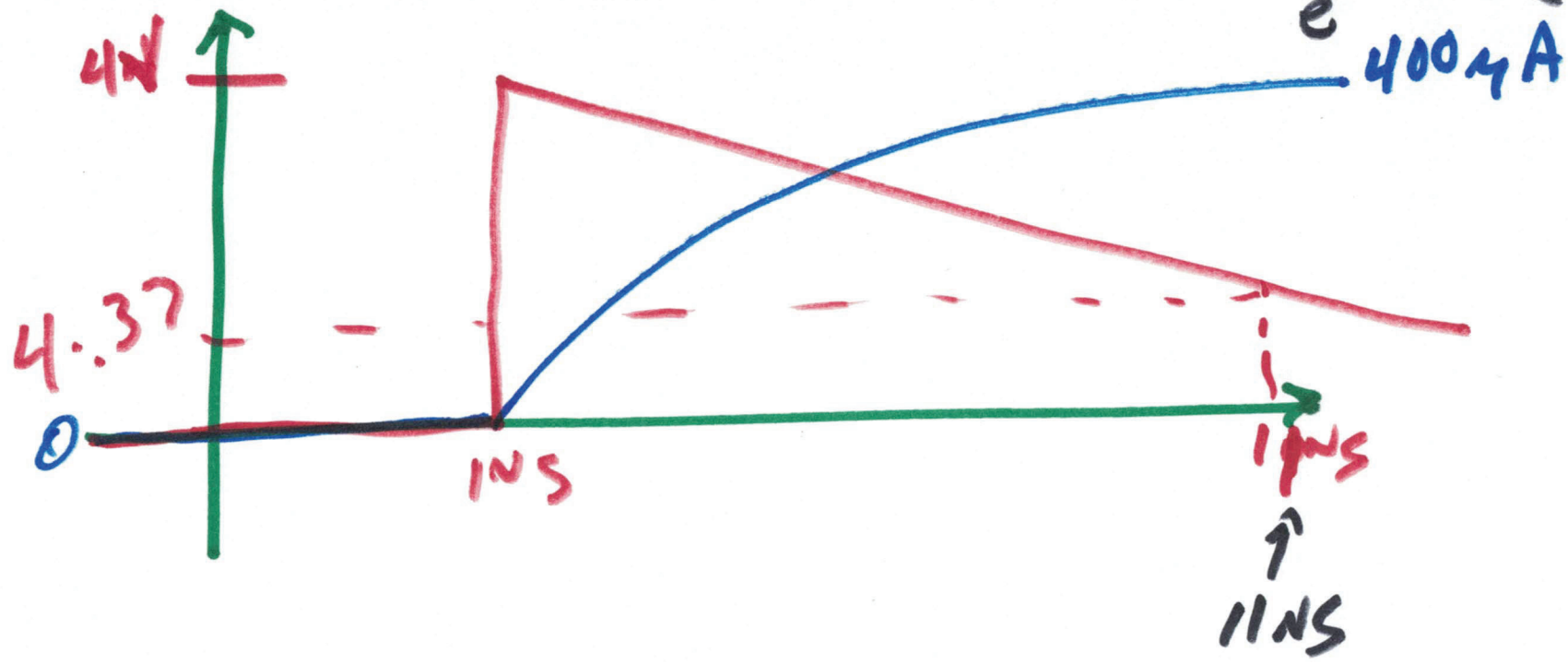
$$t = 11\text{ns} \rightarrow v = 4 e^{-\frac{10\text{ns}}{10\text{ns}}} = \frac{4}{e} = 4 \cdot (.37)$$



2)

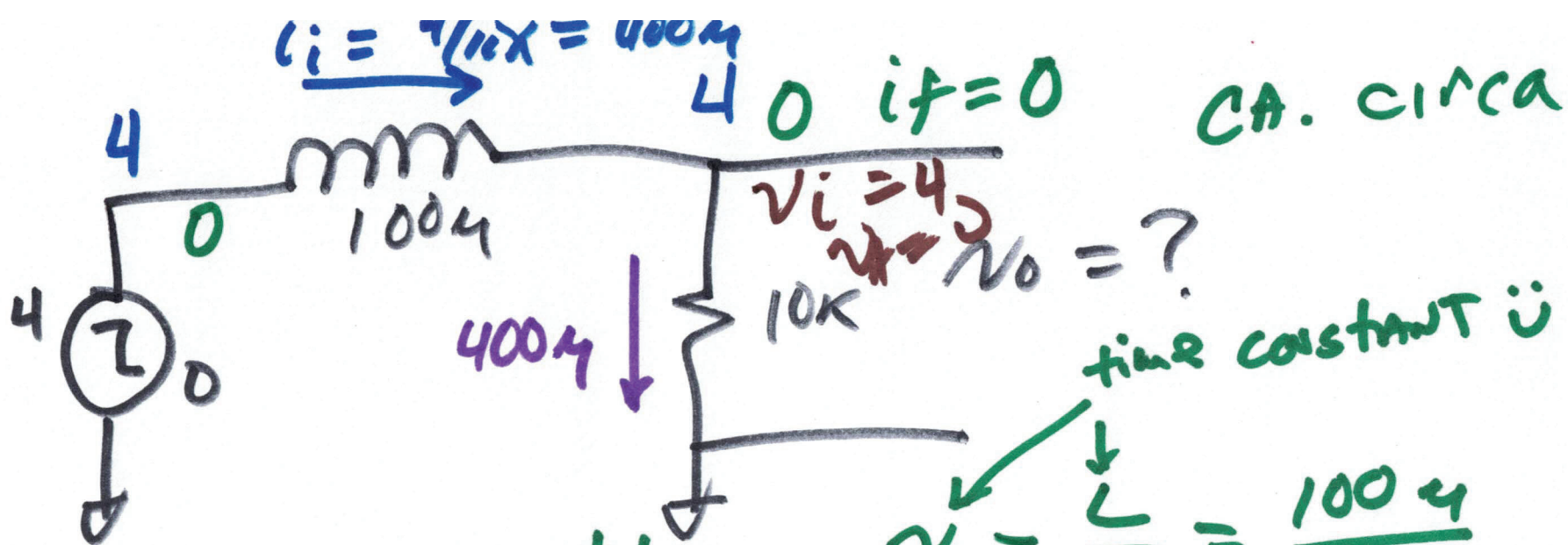

$$i = 400\mu A e^{-t/10ns}$$

$$v_o = i \cdot 10k = 4e^{-t/10ns}$$

$$\tau = \frac{L}{R} = \frac{100\mu}{10k}$$


$$= \frac{100}{10} \cdot \frac{10^{-6}}{10^3}$$

$$= 10 \cdot 10^{-9}$$

$$= 10ns$$


that is

3)

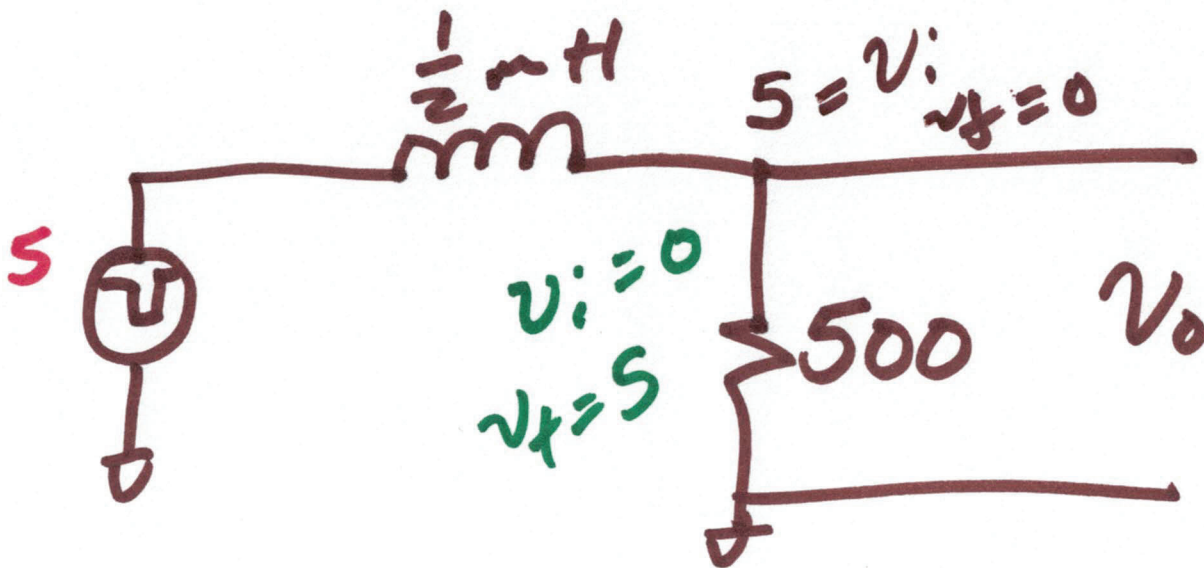


$$\tau = \frac{\frac{1}{2} \times 10^{-3}}{\frac{1}{2} \times 10^3}$$

$$\tau = 14 \text{ s}$$

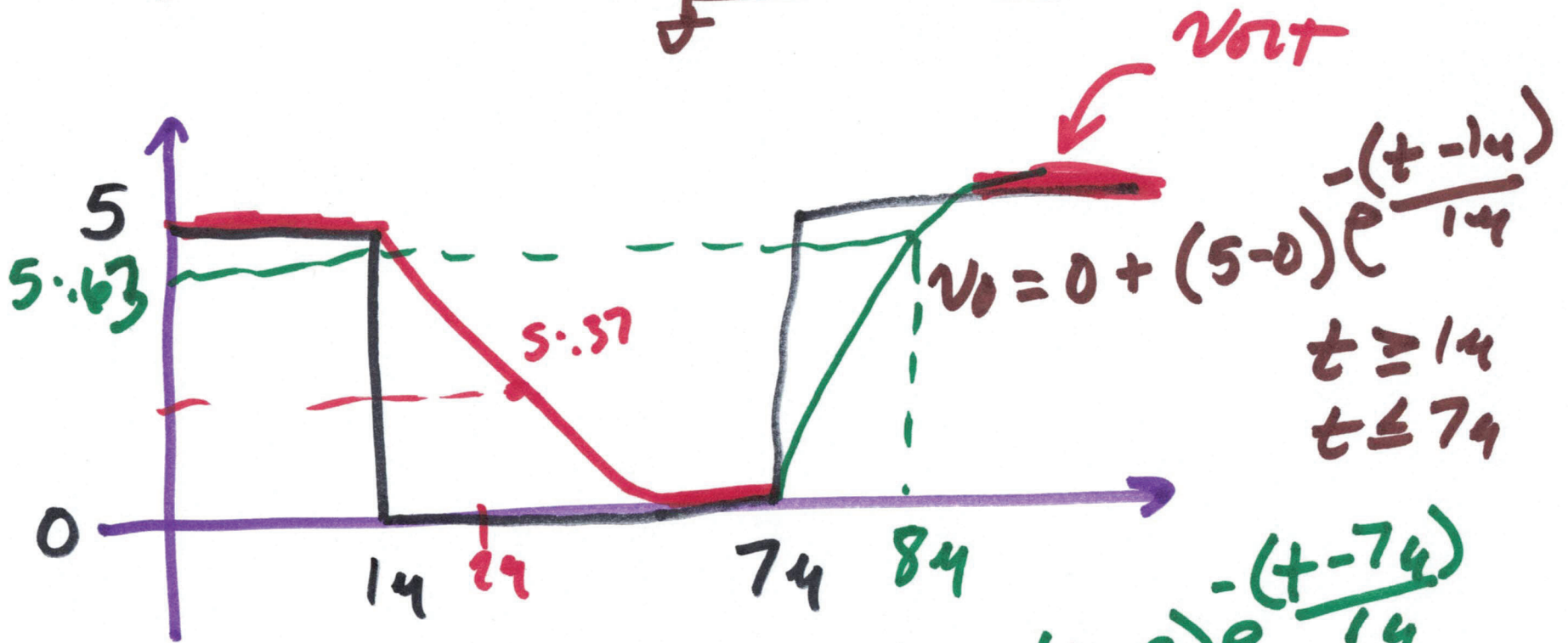

4)

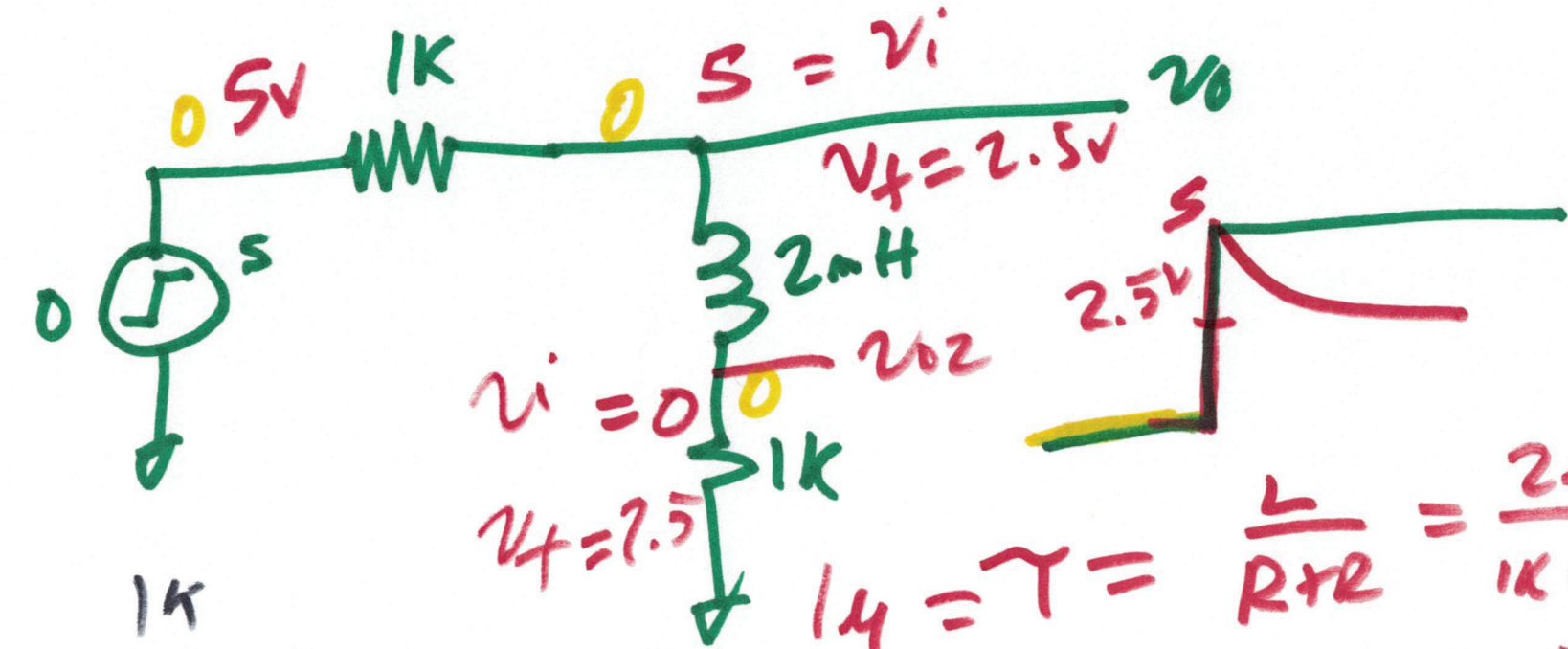


$v_i = 0$   
 $v_f = 2.5$


$$\tau = \frac{L}{R_{eq}} = \frac{2\text{mH}}{1\text{k} + 1\text{k}}$$

$$v_0 = 2.5 + (5 - 2.5)e^{-t/\tau}$$

$$v_{02} = 2.5 + (0 - 2.5)e^{-t/\tau}$$

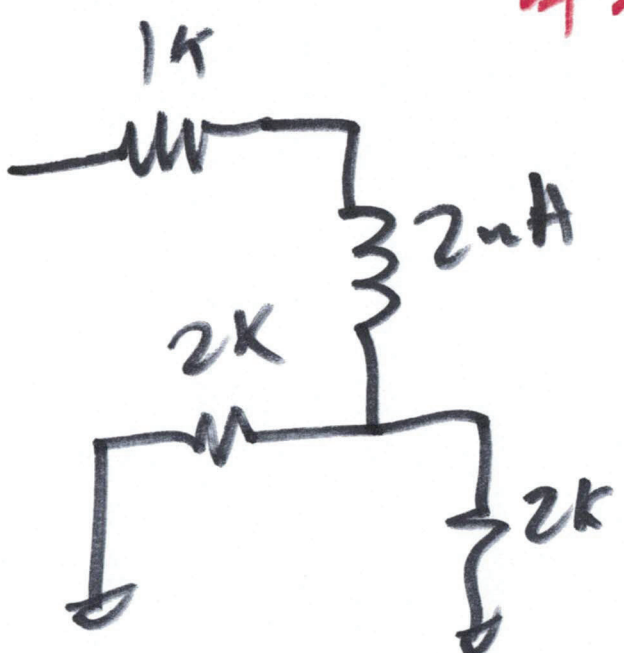


5)

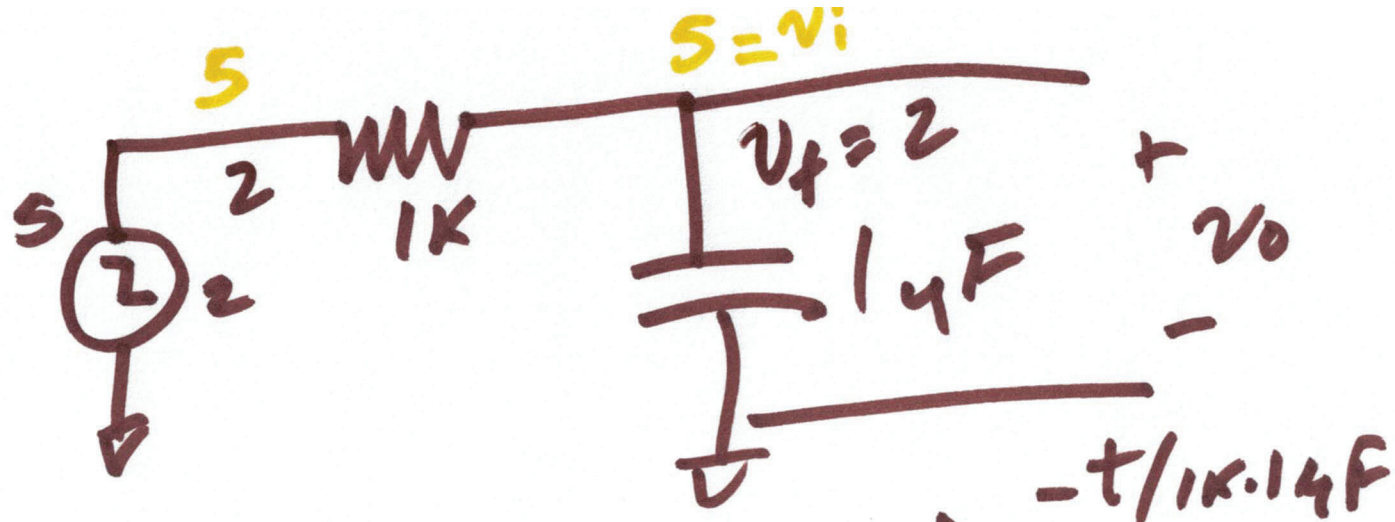

$$v_o = 2 + (s - 2)e^{-t / (1k \cdot 1\mu F)}$$

6)

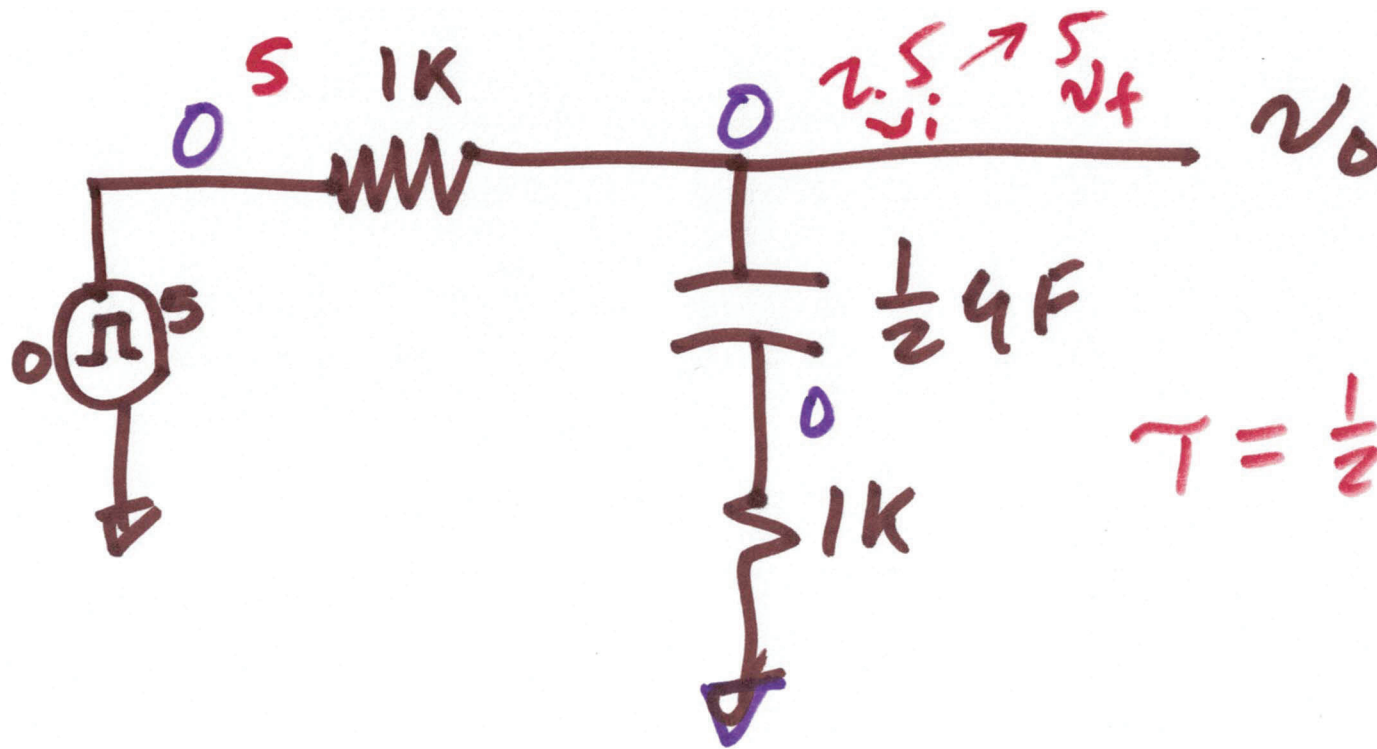

$$\tau = \frac{1}{24} (1k + 1k) = 1\mu s$$

$$v_o = 5 + (2.5 - 5)e^{-t/\tau}$$

1)