
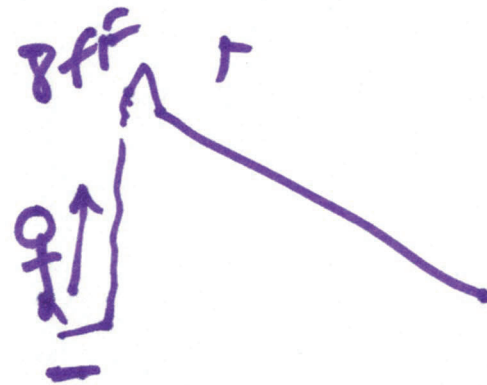





EE 220 Circuits I

Lecture 1


8/23/2021

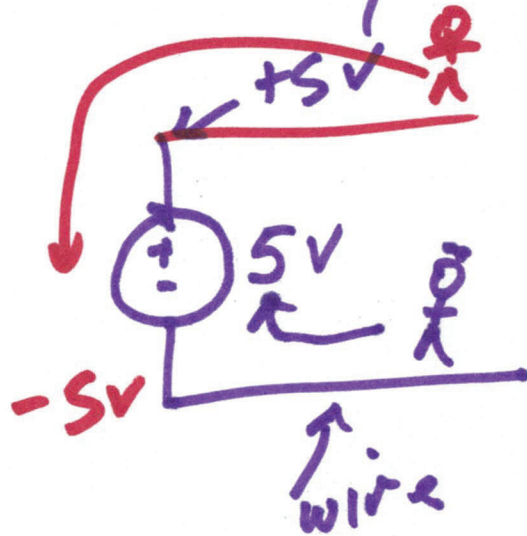


1)

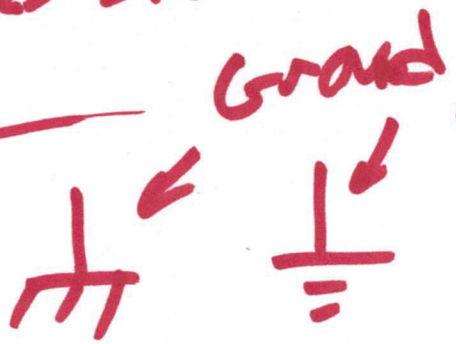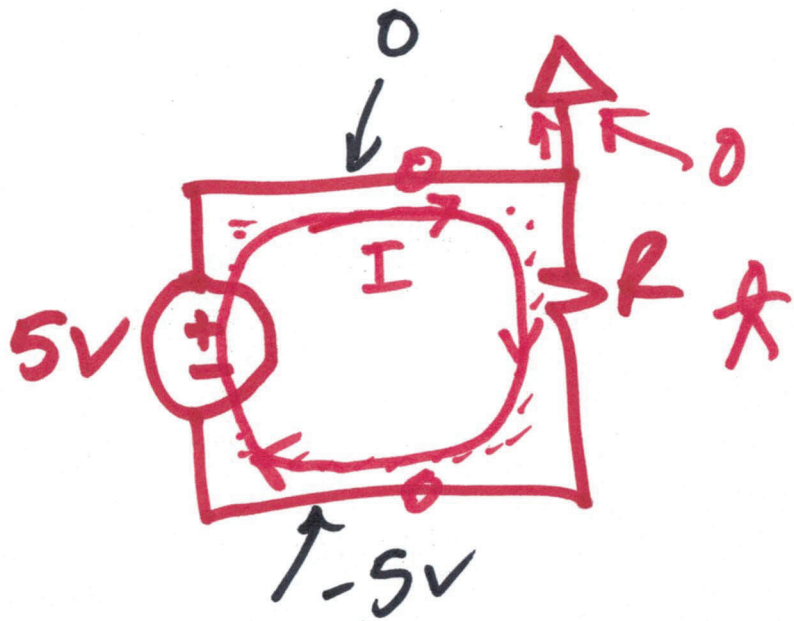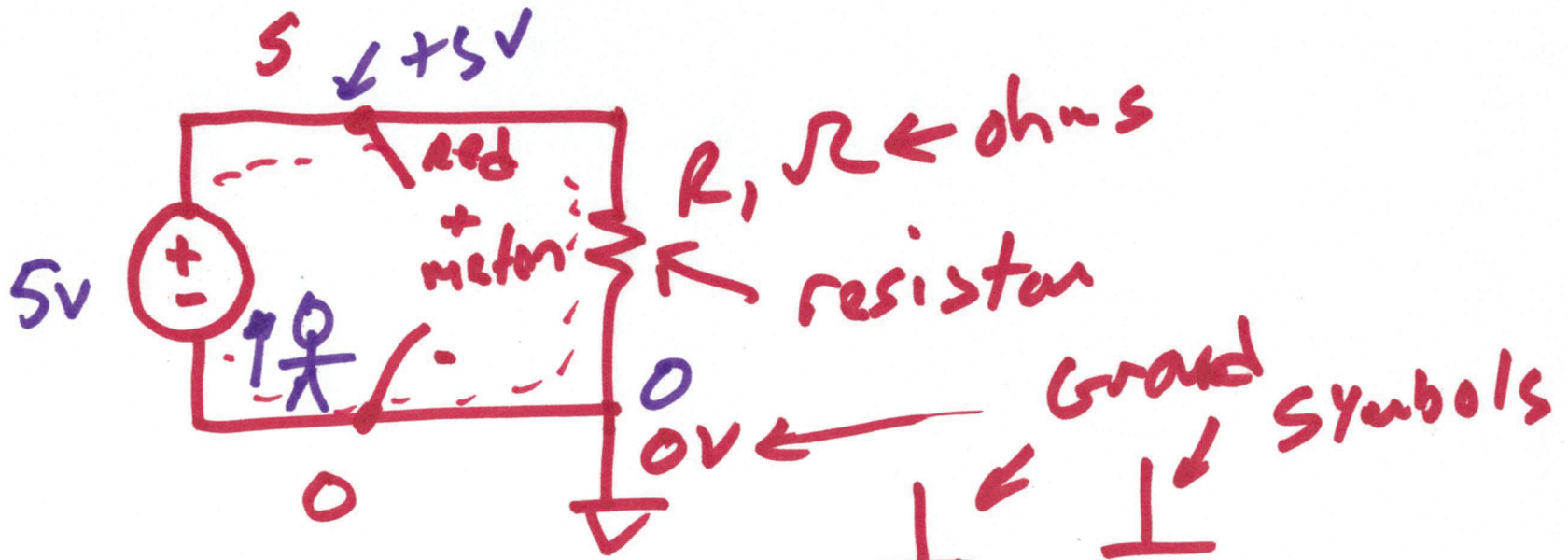

GFCI

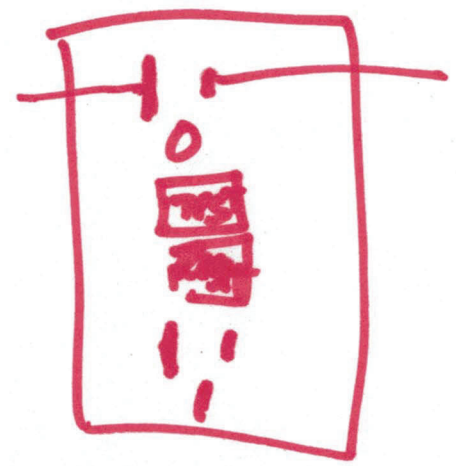


2)

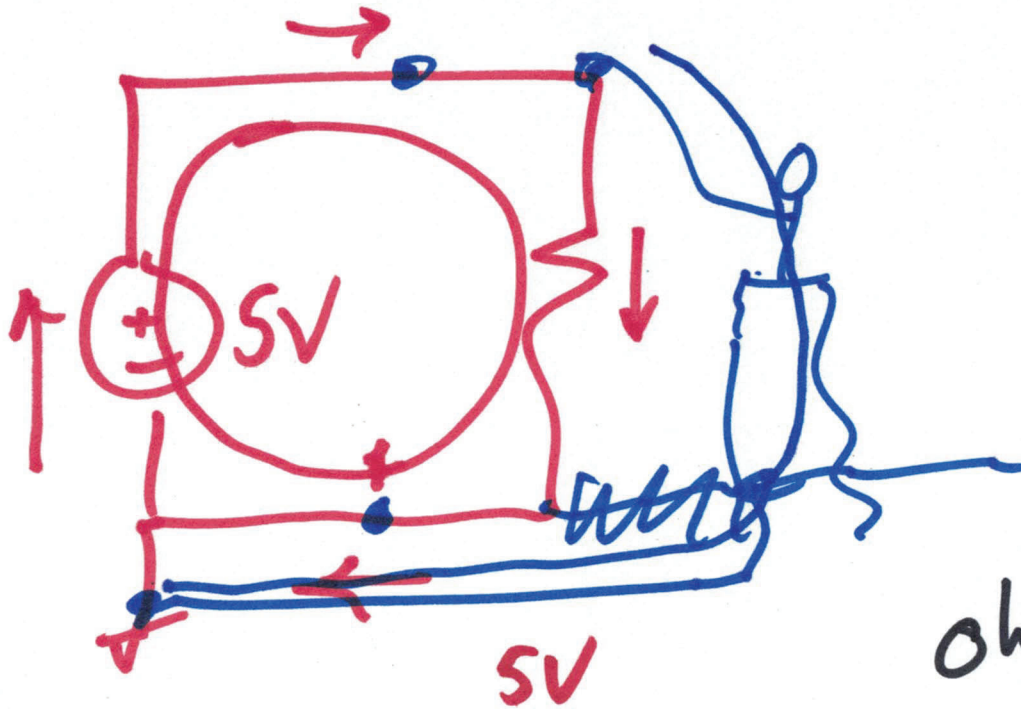

Ohm's Law

$$V = I \cdot R$$

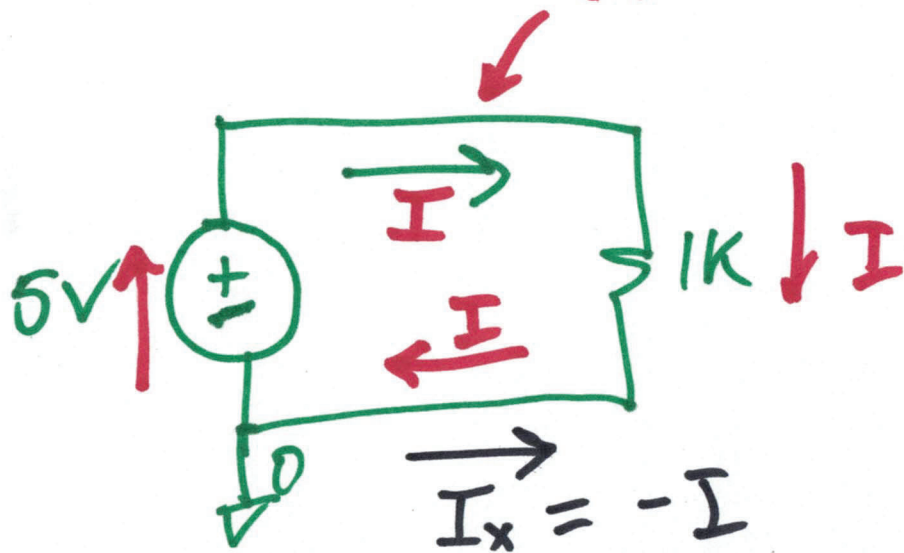


3)




H.W. #1 EE 220 Fall 2021

Show your work for credit and put a box around each of your answers!

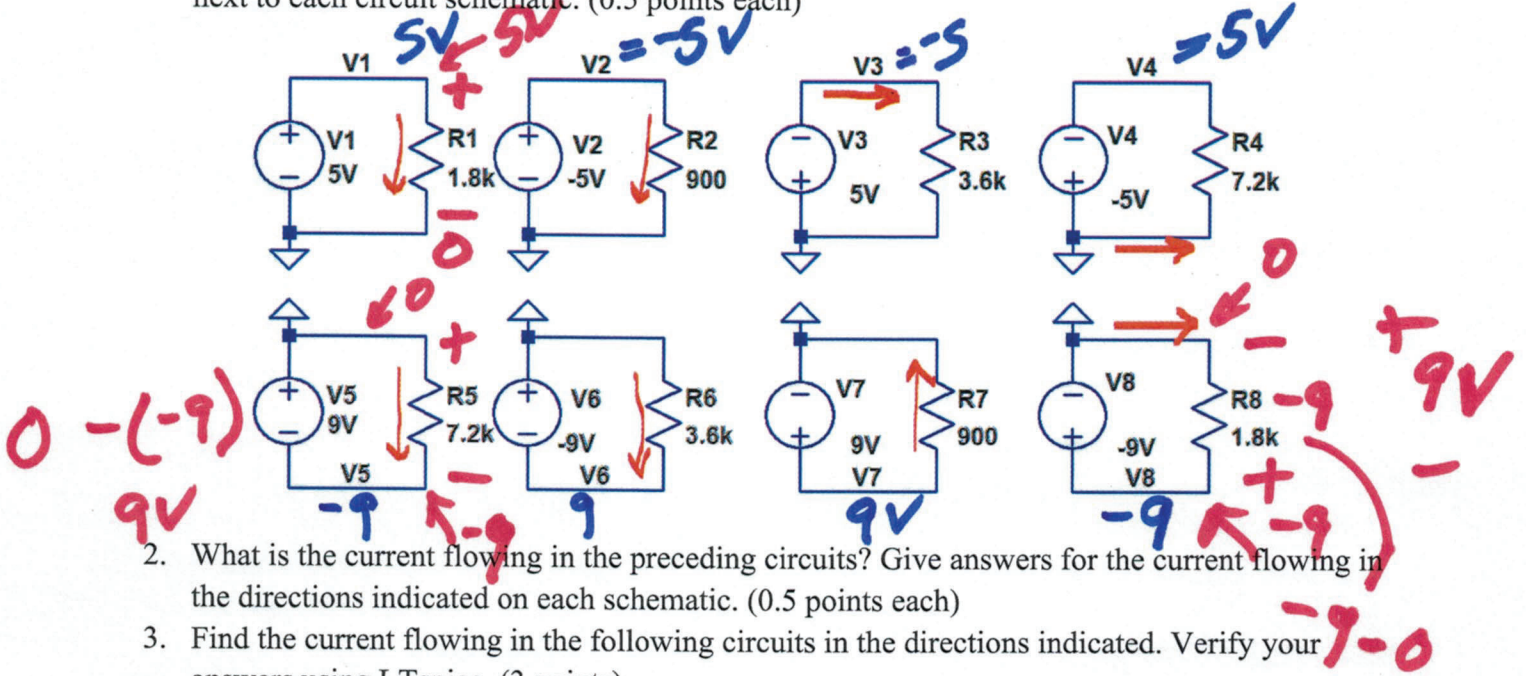
1. What are V_1 - V_8 , in each of the following circuits? It's okay to simply write your answer next to each circuit schematic. (0.5 points each)



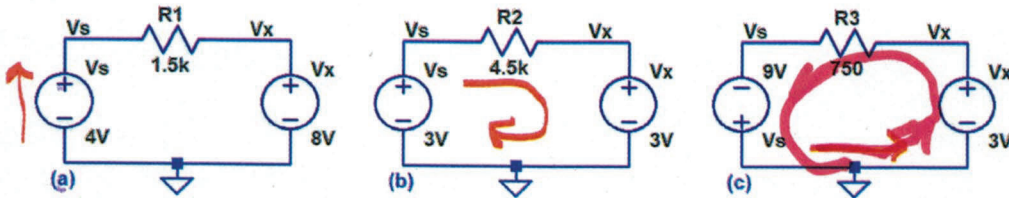
2. What is the current flowing in the preceding circuits? Give answers for the current flowing in the directions indicated on each schematic. (0.5 points each)
3. Find the current flowing in the following circuits in the directions indicated. Verify your answers using LTspice. (3 points)



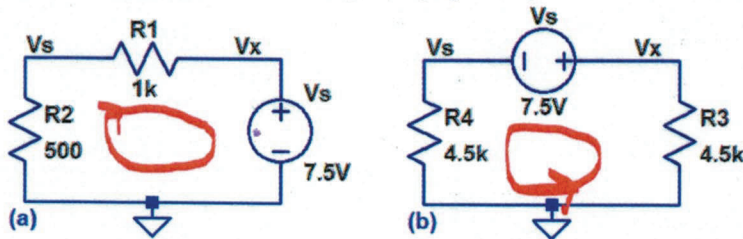
4. Find the voltages V_s , V_x , and the voltages across all resistors. Find the current flowing in each circuit. Verify your answers with LTspice. (4 points)



57

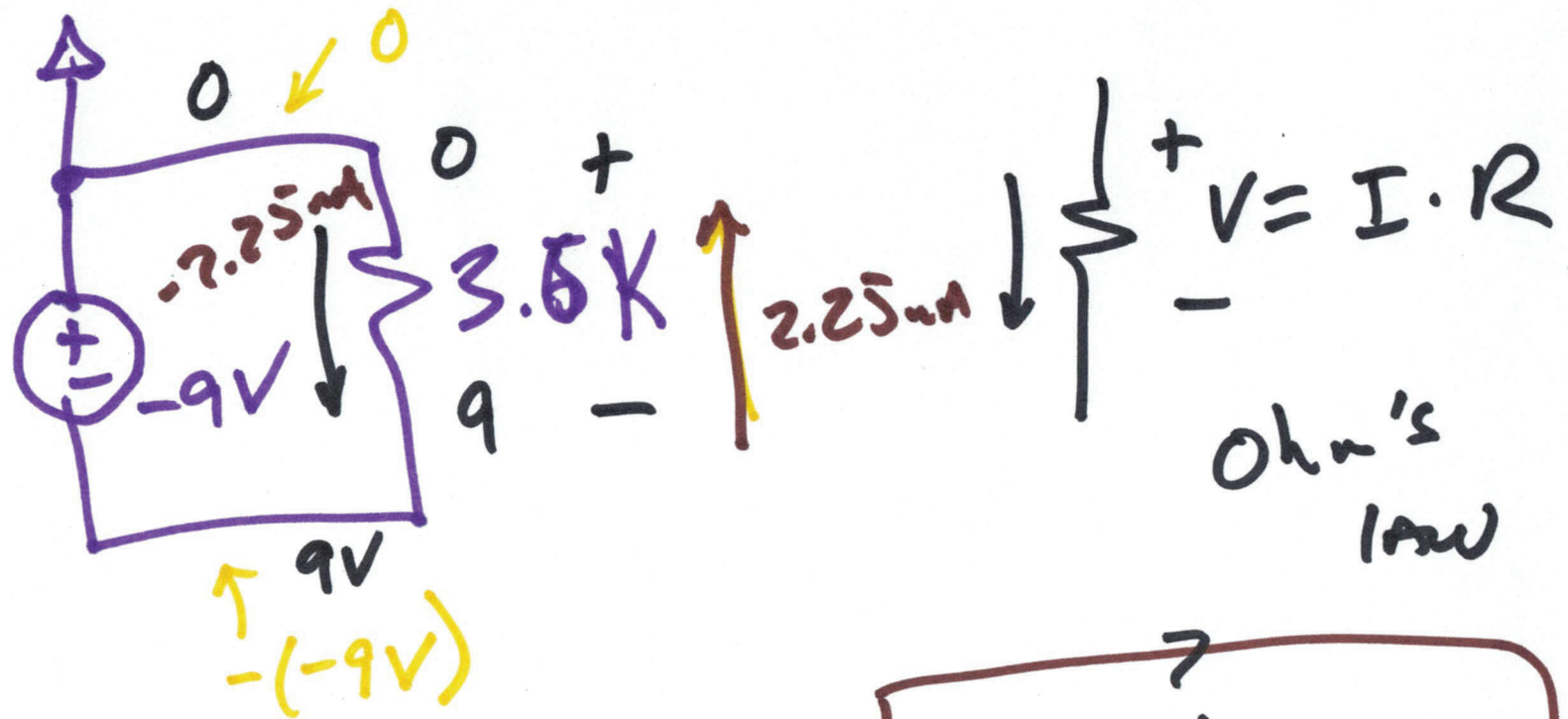

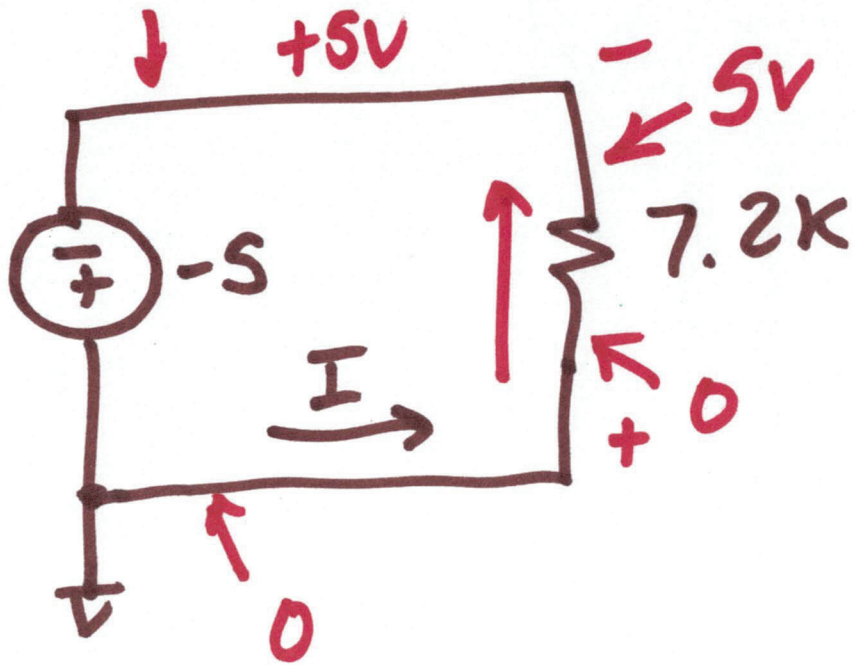
$$I = \frac{0 - 9}{3.6\text{k}} = \boxed{-2.25\text{mA} = I}$$



$$I \downarrow \begin{matrix} + \\ \downarrow \\ v = IR \\ - \end{matrix}$$

$$I = \frac{0 - 5}{7.2K}$$


$$I = -.69 \mu A$$

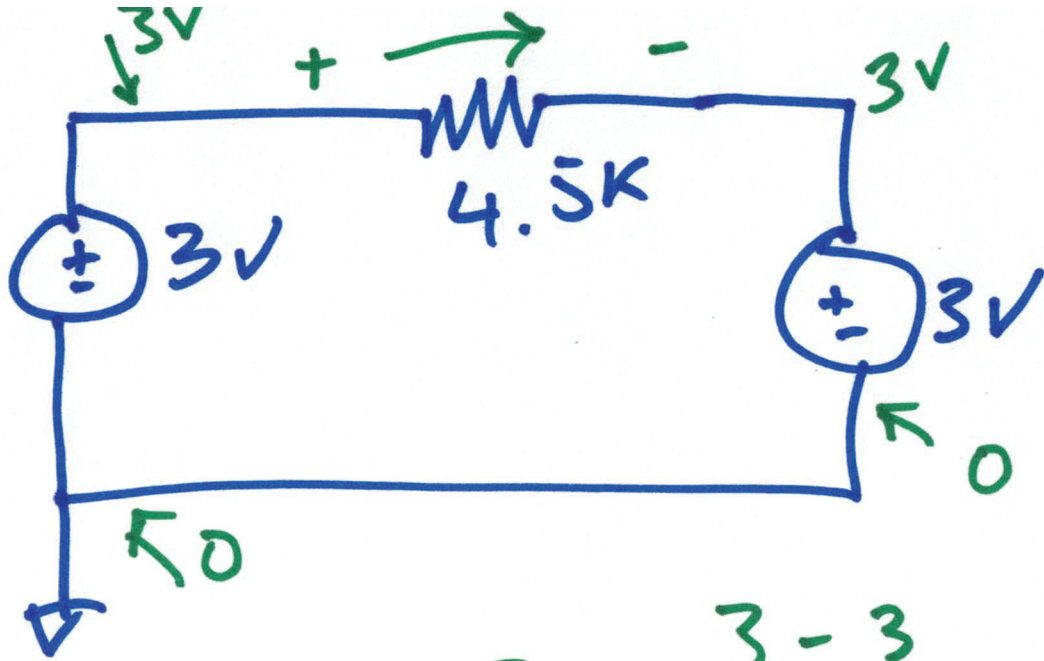

$$I \downarrow \int \downarrow \begin{matrix} + \\ v = IR \\ - \end{matrix}$$

$$I = \frac{3 - 3}{4.5K} = \boxed{0 = I}$$

8)

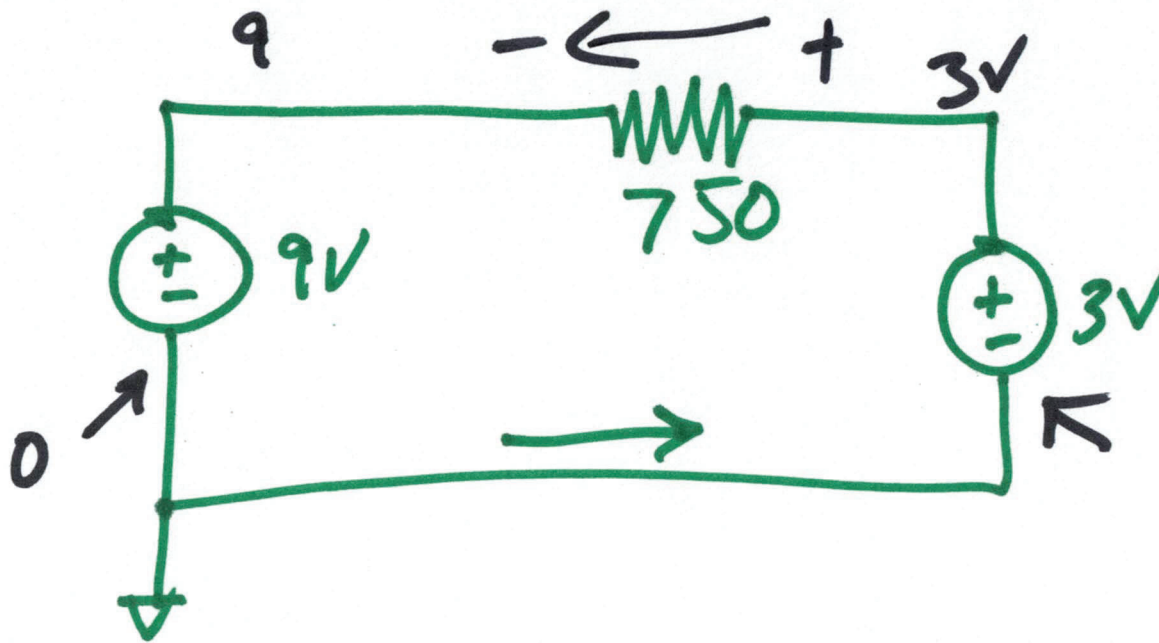


$$RI = V$$

$$V = (-I) \cdot R$$

$$I = \frac{3 - 9}{750}$$

7)

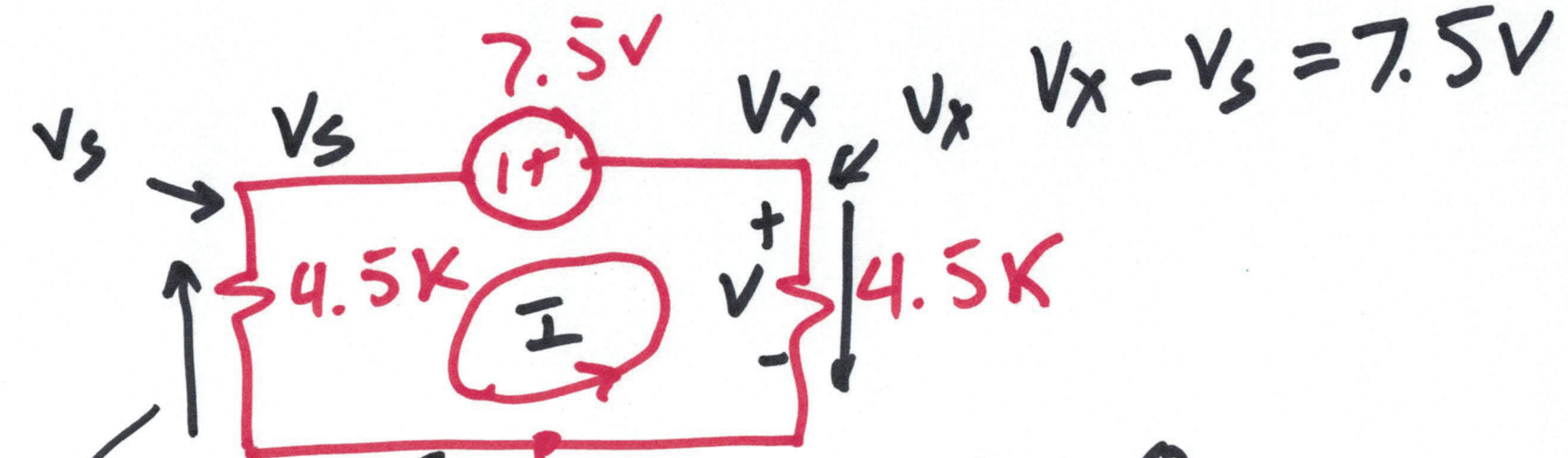

$$\frac{0 - V_s}{4.5K} = \frac{V_x - 0}{4.5K}$$

$$-V_s = V_x$$

$$V_x - V_s = 7.5V$$

10)