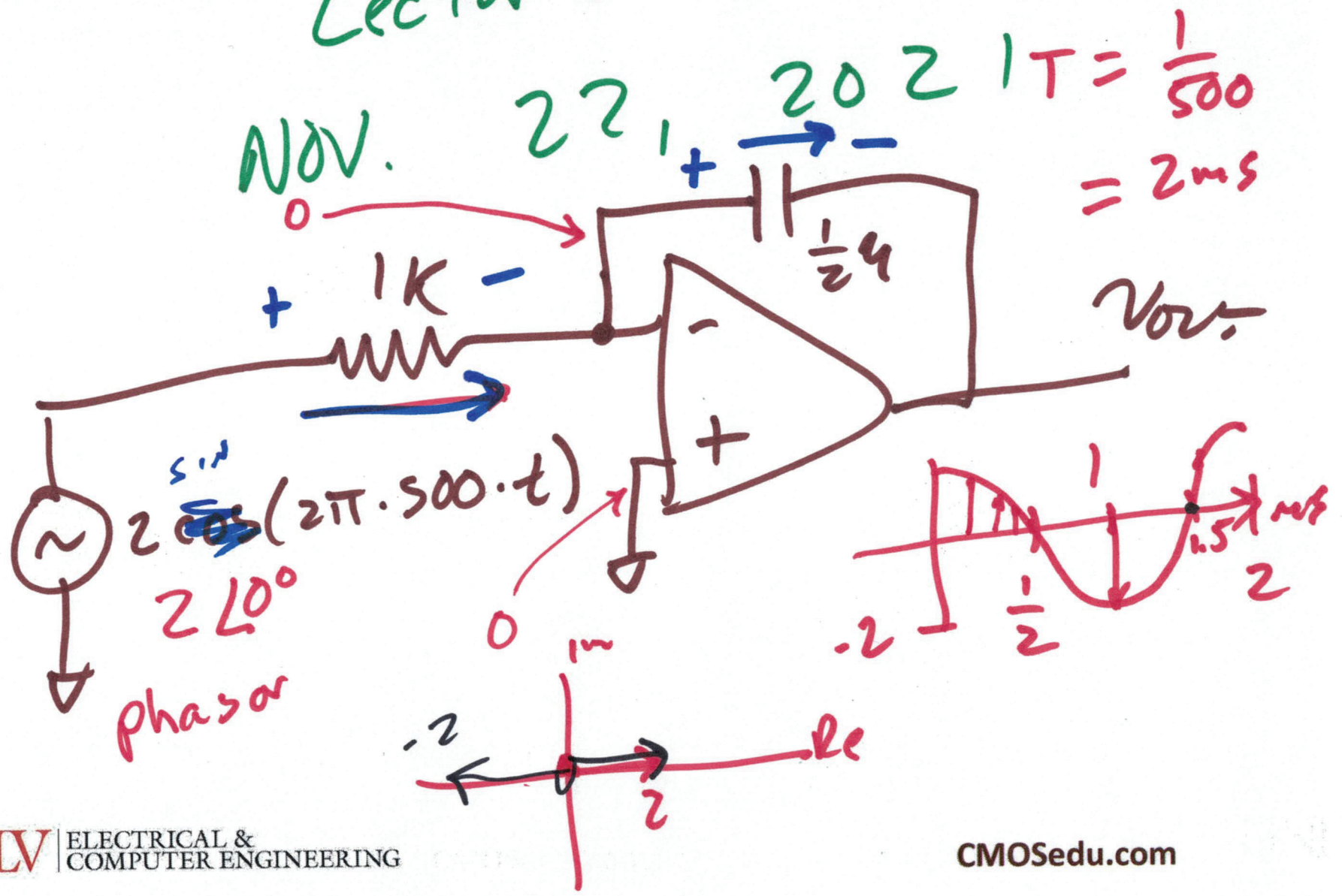


EE 220 circuits 1


Lecture 24



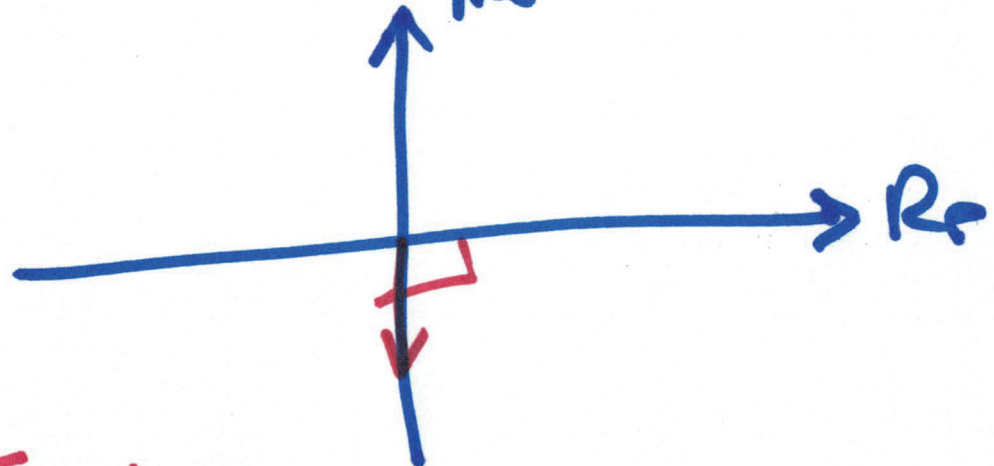
1)

$$\frac{2L^0 - 0}{1K} = \frac{0 - 202T}{\frac{1}{j \cdot 2\pi \cdot \frac{1}{2} \mu f}}$$

$$Z_{in} L^0 \quad \frac{1}{j\omega C} = -j \cdot \frac{1}{\omega C} = 637 \angle -90$$


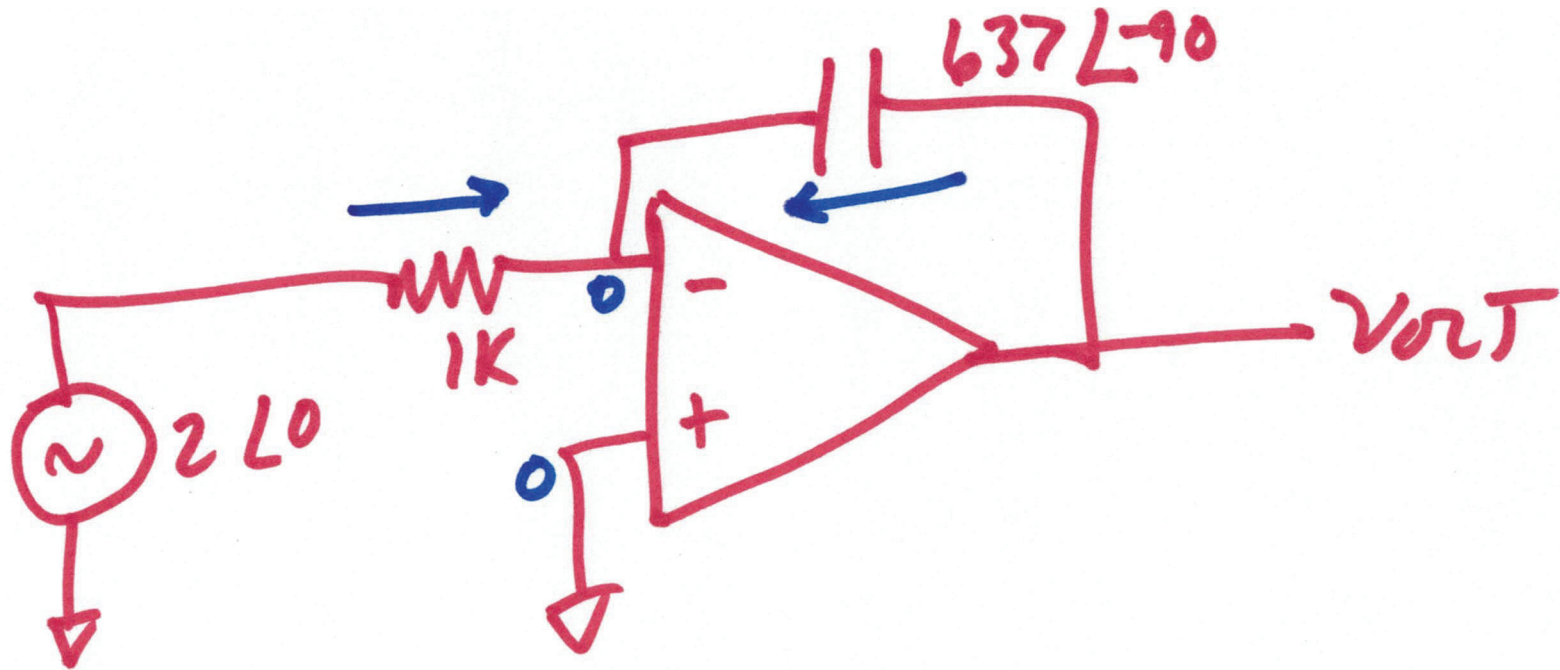
$$\frac{1}{2\pi \cdot 500 \cdot \frac{1}{2} \cdot \mu} = 637$$




$$\frac{2L0 - 0}{1K} + \frac{V_{out} - 0}{637L-90} = 0$$

$$2AL0 \cdot 637L-90 = V_{out}$$

$$V_{out} = 1.27L-90$$


$$v_{in} = 2 \cos = 2 \sin(2\pi \cdot 500 \cdot t)$$
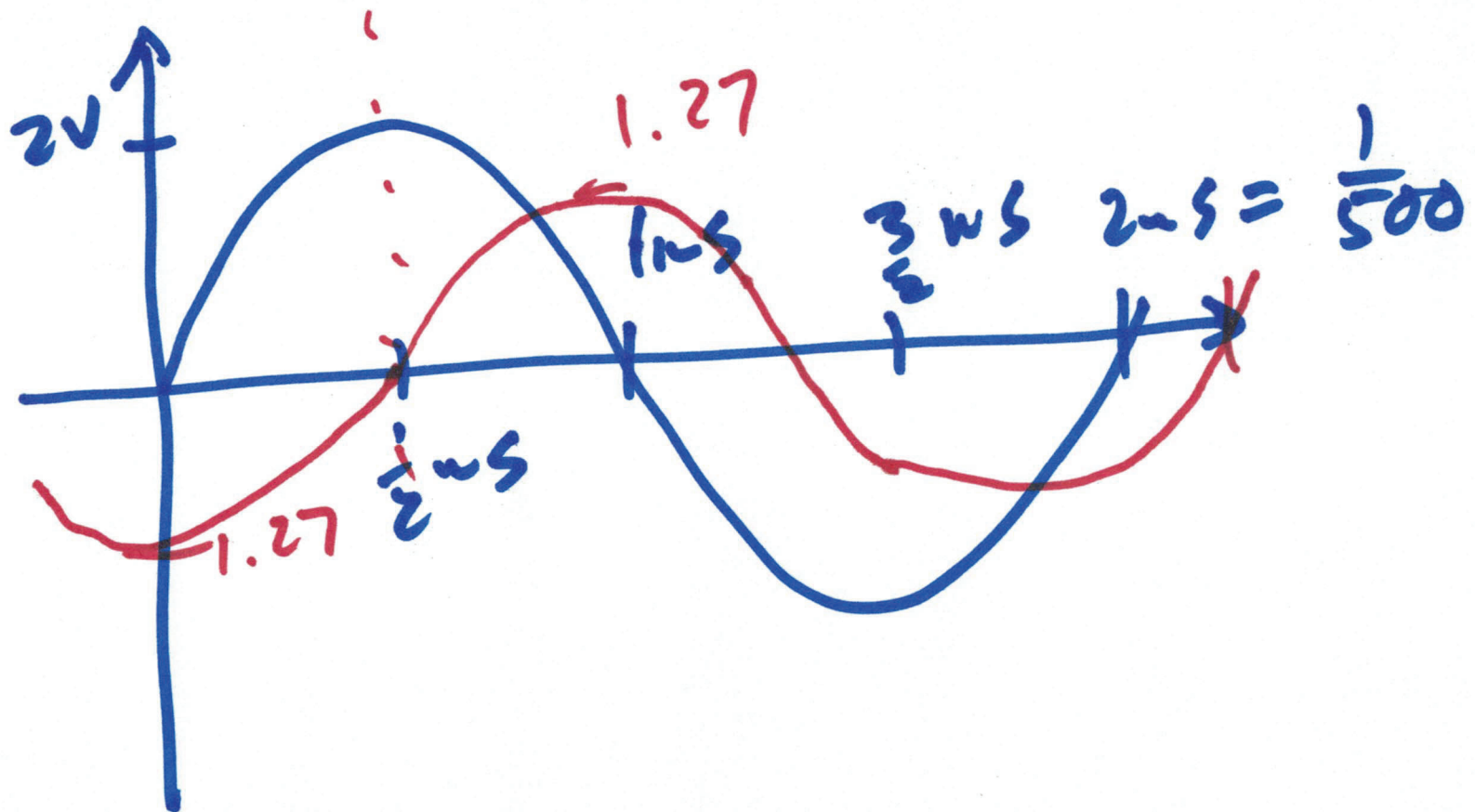
$$v_{out} = 1.27 \angle -90 = 1.27 \sin(2\pi \cdot 500 \cdot t - 90)$$




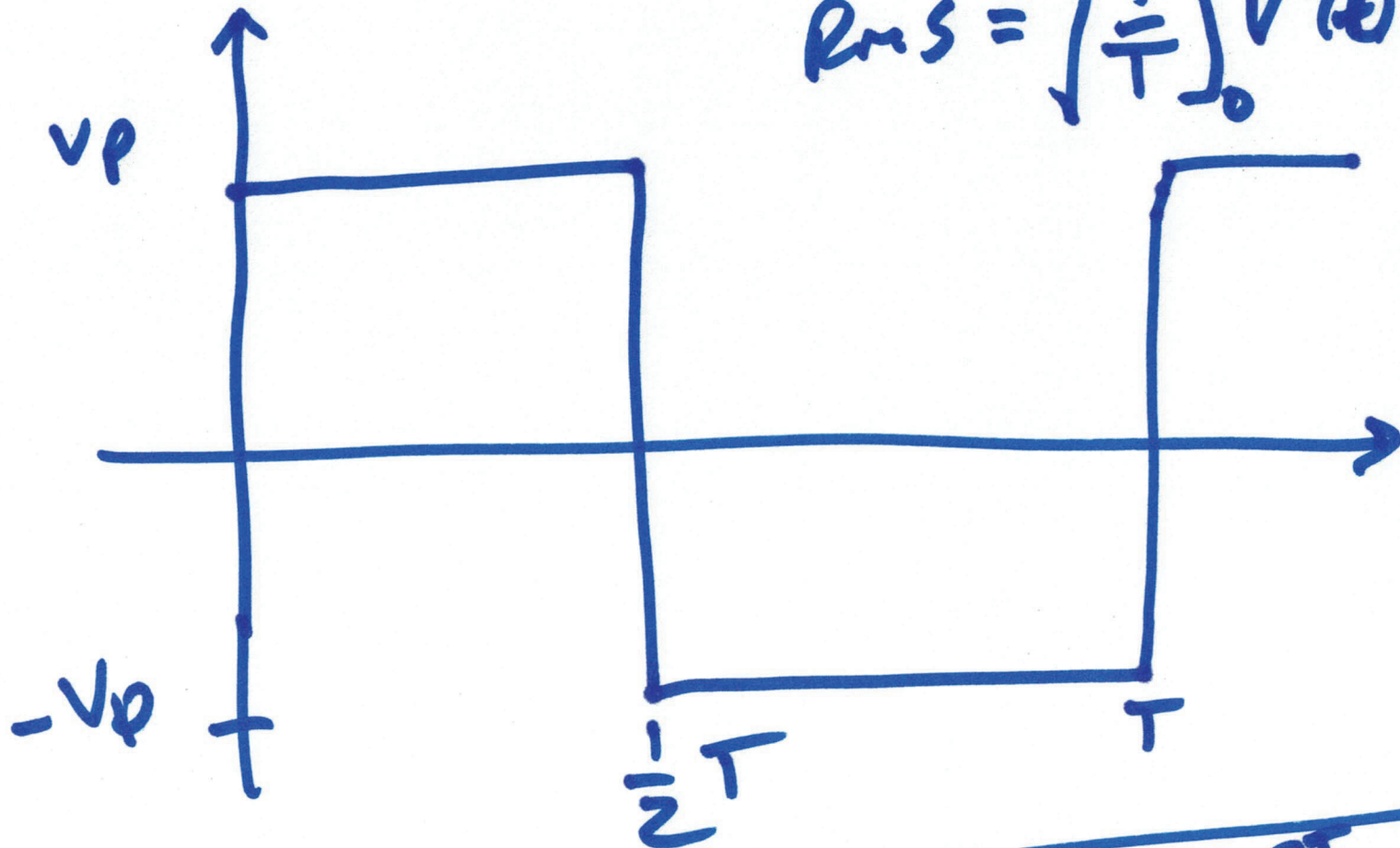4)

$$R_{ms} = \sqrt{\frac{1}{T} \int_0^T \dot{v}^2(t) \cdot dt}$$


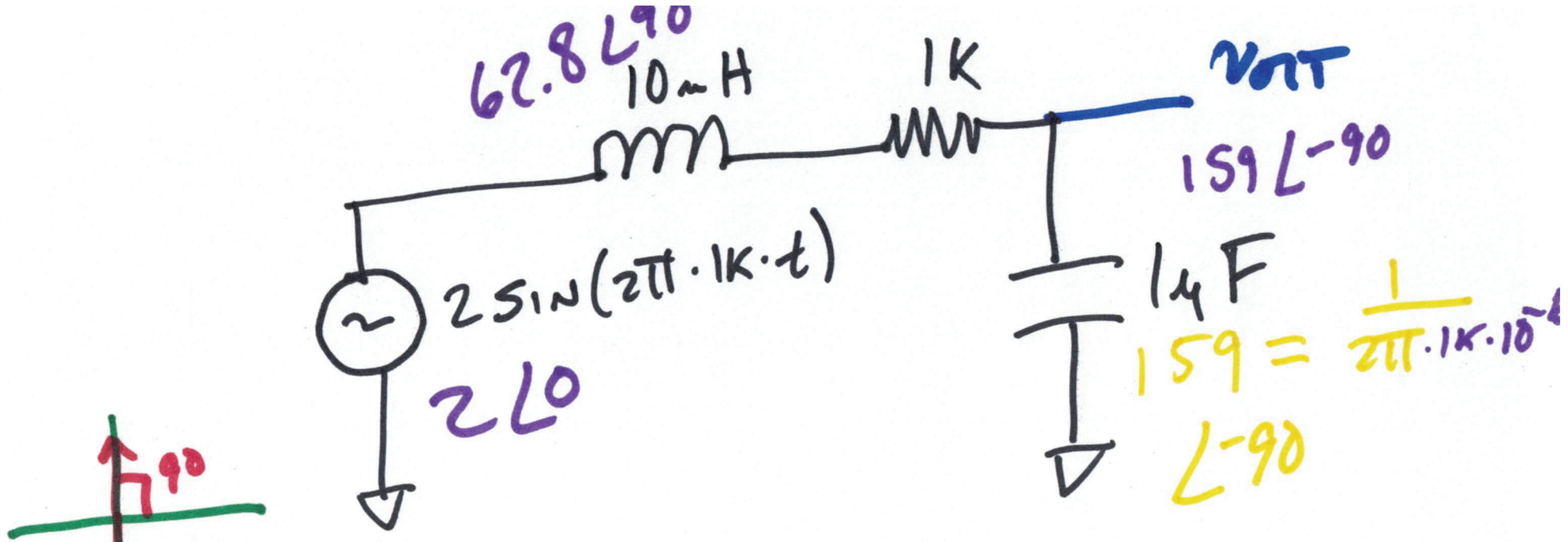
$$R_{ms} = \sqrt{\frac{1}{T} \left[\int_0^{1/2 T} v_p^2 \cdot dt + \int_{1/2 T}^T (-v_p)^2 \cdot dt \right]}$$



$$V_{out} = \frac{2\angle 0 \cdot 159\angle -90}{62.8\angle 90 + 1000 + 159\angle -90}$$


$$= \frac{2 \cdot 159 \cdot \cos 90 + j \cdot 2 \cdot 159 \cdot \sin 90}{62.8 \cdot \cos 90 + 1000 + 62.8 \cdot \sin 90 - 159j}$$

$$= \frac{0 + j \cdot 62.8}{1000 - 159j}$$

6)

$$V_{out} = \frac{318 \angle -90}{1000 + (-96.2j)}$$

$$318 \angle -90$$

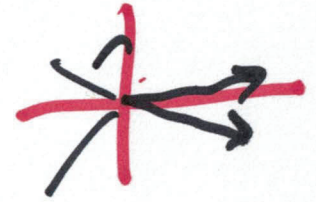

$$= \frac{1,004 \angle -5.5^\circ}{}$$

$$\frac{84.5}{360} \cdot 360 = t_d$$

$$t_d = .234 \text{ ms}$$

$$\tan^{-1} \frac{-96.2}{1000} = -5.5^\circ$$

$$V_{out} = 316 \text{ mV} \angle -84.5^\circ$$

$$\theta = \frac{t_d \cdot 360}{T} \rightarrow \text{ms}$$