

# EE 220 Circuits 1

12/1/2021

## Lecture 27

$$V_{IN} = 1 \cdot \sin(2\pi \cdot 10^3 \cdot t) \text{ Volts}$$

$$V_{OUT} = 313 \mu\text{Volts} \sin(2\pi \cdot 10^3 \cdot t + 99^\circ)$$

$$\theta = \frac{t_d}{T} \cdot 360 = t_d \cdot 360 \cdot f$$


$$t_d = 275 \mu\text{s}$$

$$f = \frac{1}{T}$$

$$\frac{99}{360} \cdot 10^3 = t_d$$


$$\frac{1}{j\omega C} = \frac{1}{\omega C} (-j) = \frac{1}{\omega C} \angle -90^\circ$$

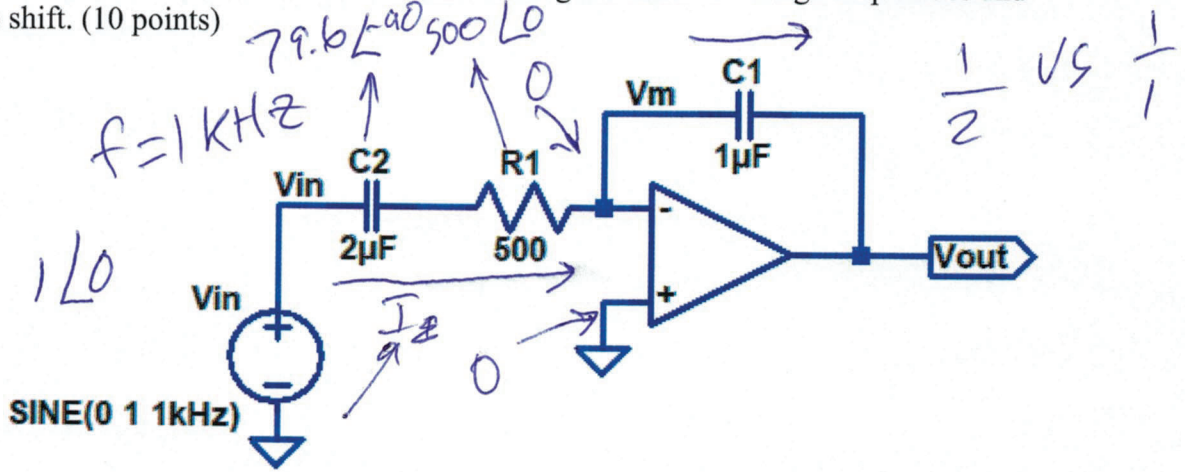9. Find the output voltage of the following circuit using phasor analysis and sketch it along with the input voltage in the time domain showing the relative voltage amplitudes and phase shift. (10 points)



$$\frac{1 \angle 0}{500 + j(-79.6)} = \frac{1 \angle 0}{79.6 \angle -90^\circ + 500 \angle 0} = \frac{1 \angle 0}{506 \angle -9^\circ}$$

$\tan^{-1} \frac{-79.6}{500}$

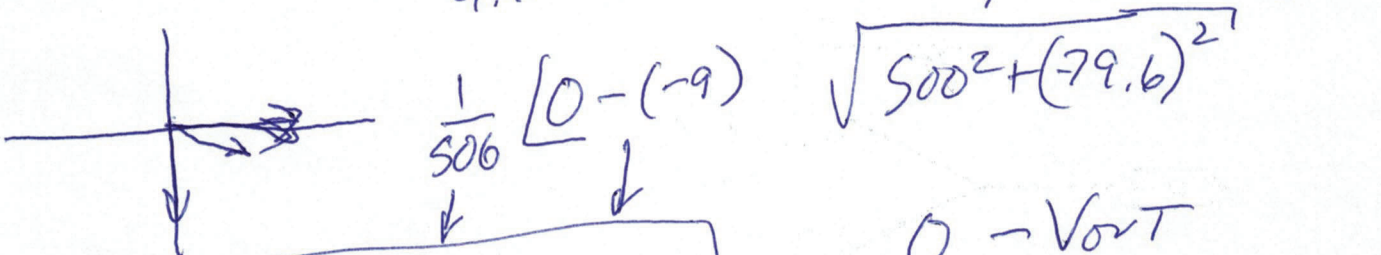

$$I = 1.97 \mu A \angle 9^\circ = \frac{0 - V_{out}}{159 \angle -90^\circ}$$


$$V_{out} \angle 180^\circ = -V_{out} = 1.97 \mu A \angle 9^\circ \cdot 159 \angle -90^\circ$$

$$V_{out} = 313 \text{ mV} \angle 180^\circ$$

$$V_{out} = 313 \text{ mV} \angle 99^\circ$$

$$9 + (-90) - (180) = -261^\circ = +99^\circ$$

v)

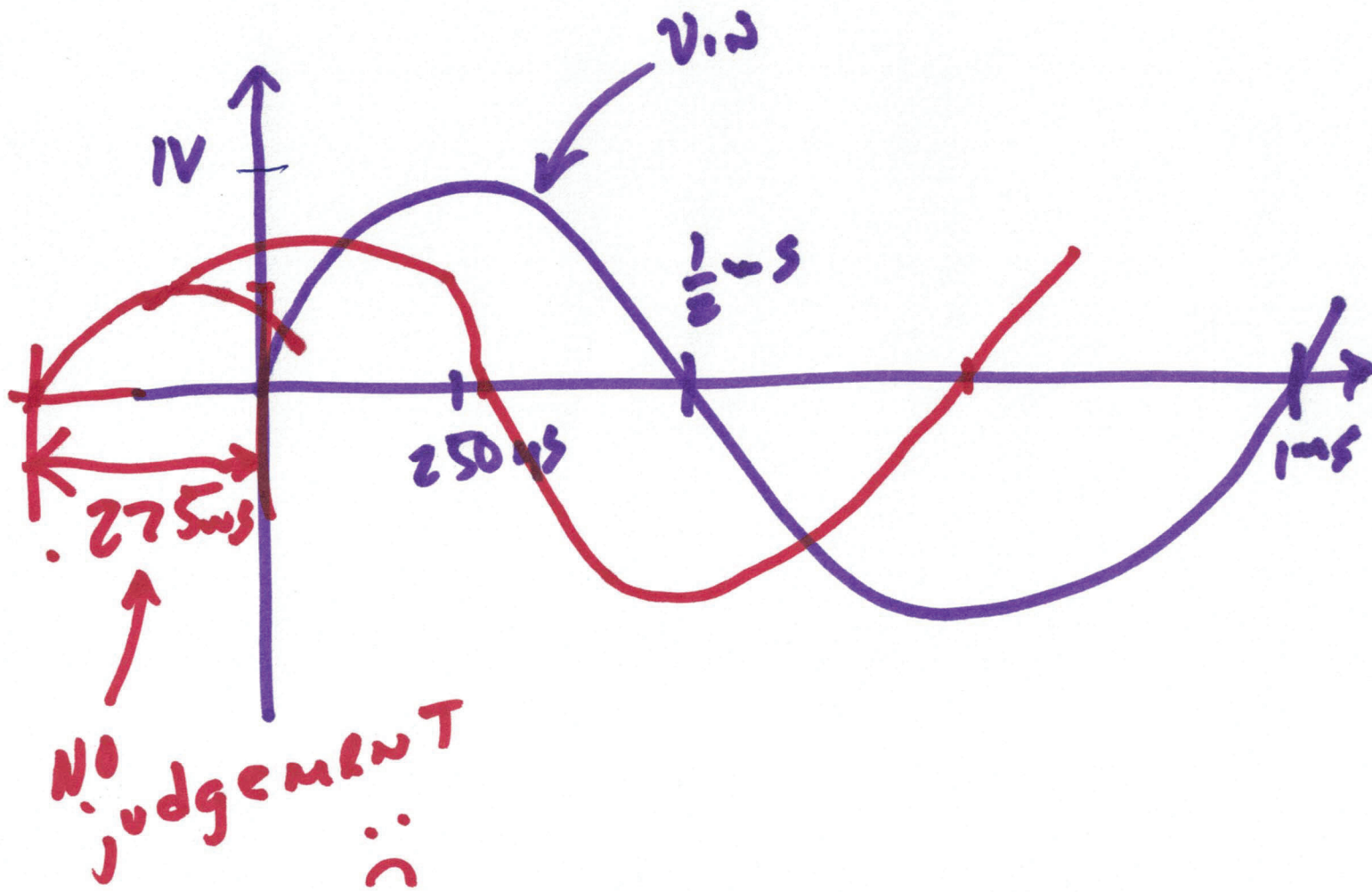


3)

Practice Final Exam – EE 220 Circuits I  
 University of Nevada, Las Vegas

NAME: \_\_\_\_\_

Closed book and notes.  
 Use the back of the sheet of paper when needed.

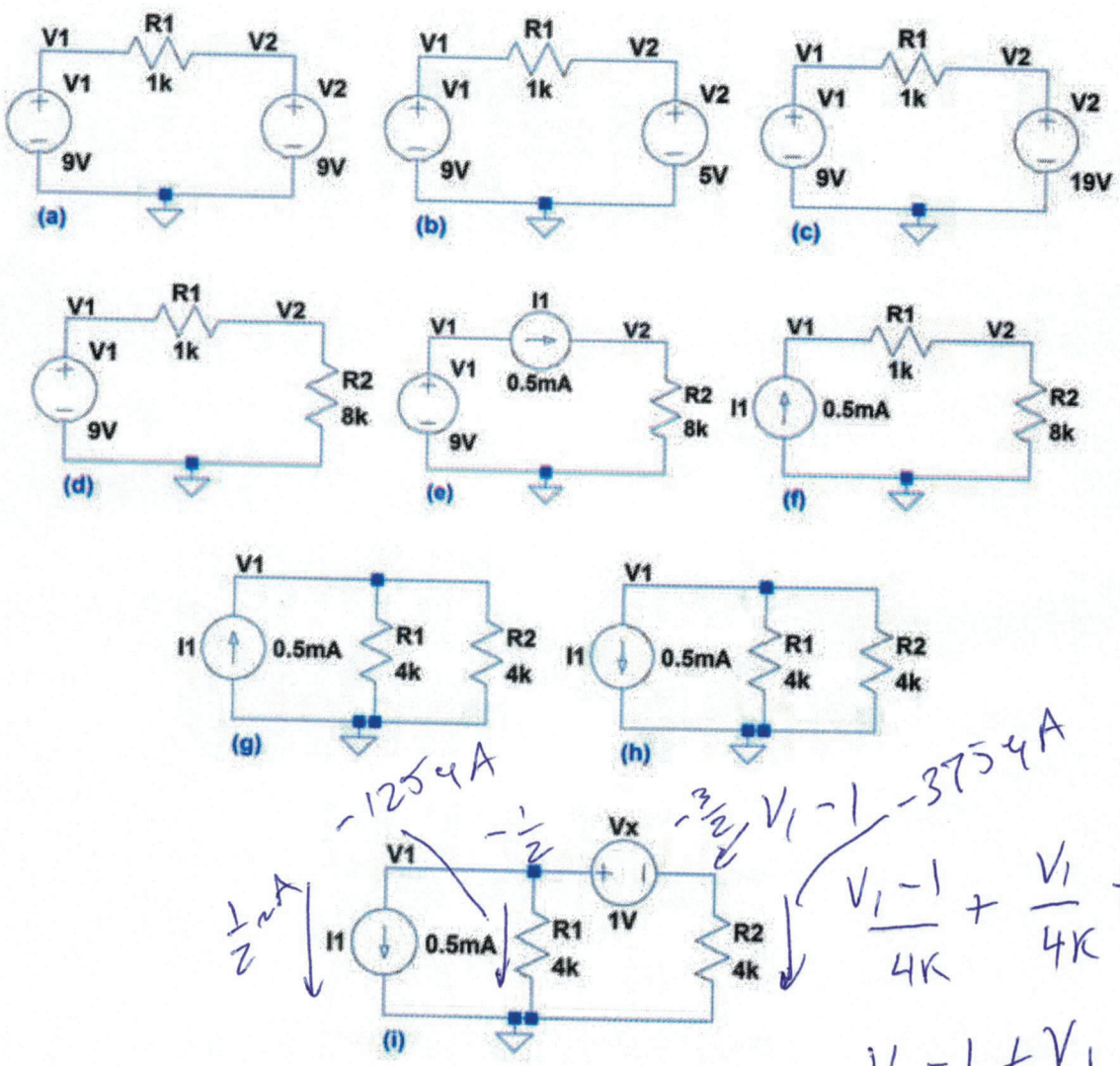- Find the currents and voltages in the following circuits. Clearly label the values on the schematics. No need to show your hand calculations, simply write the values. (10 points)




Handwritten notes and equations for circuit (i):


- $-125 \mu A$
- $-\frac{1}{2}$
- $\frac{1}{2} \mu A$
- $\frac{V_1 - 1}{4k} + \frac{V_1}{4k} + \frac{1}{2} \mu A = 0$
- $V_1 - 1 + V_1 + 2V = 0$
- $2V_1 = -1$
- $V_1 = -\frac{1}{2}$

4)

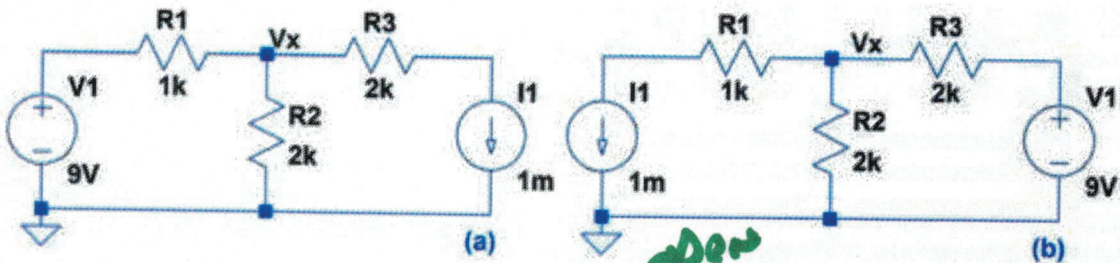2. Using superposition show how to find  $V_x$  in each of the following circuits. Show your work for credit. (10 points)



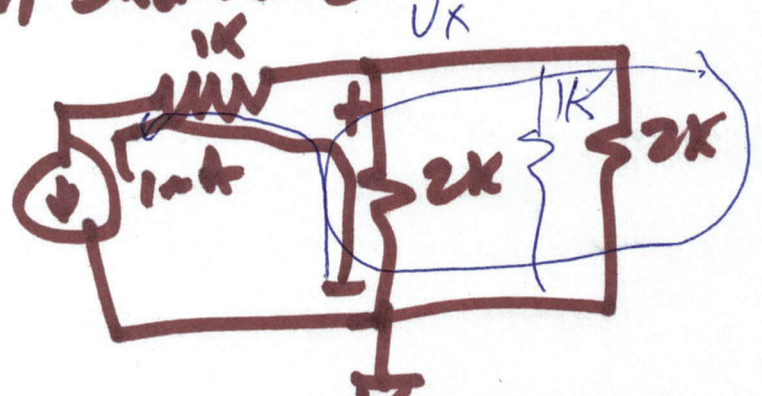$I_1$  open  
 $V_{x1} = 9 \cdot \frac{2k}{2k+2k} = 4.5V$   
 $V_1$  Shortened




$$V_{x2} = -1mA \cdot 1k = -1V$$

$$V_x = 4.5 - 1$$

$$V_x = 3.5V$$

5)

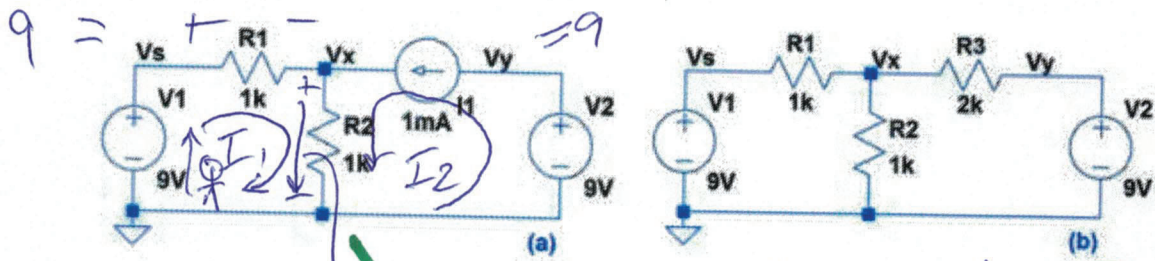3. Find the voltages and currents in each of the following circuits using mesh analysis. Show your work for credit. (10 points)



$$1k(I_1 + 1mA) \quad I_1 + I_2 = I_1 + 1mA \quad I_2 = 1mA$$

$$+9 - 1kI_1 - 1k(I_1 + 1mA) = 0$$

$$9 - 2kI_1 - 1V = 0$$



$$2kI_1 = 8$$

$$I_1 = 4mA$$

$$V_x = 1k \cdot 5mA = \underline{\underline{5V}}$$

6)

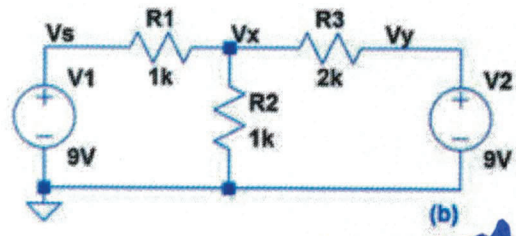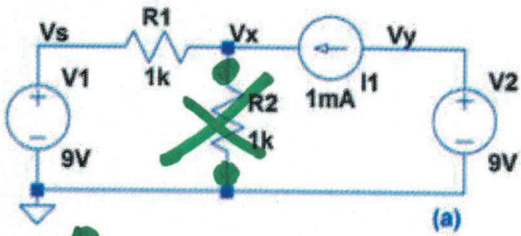
4. Find the Thevenin and Norton equivalent circuits between  $V_x$  and ground with  $R_2$  removed in the following circuits. Show your work for credit. (10 points)



$$R_{TH} = 1K$$

$$V_{OC} = V_{TH} = 10V$$

$$-1K + V_x$$

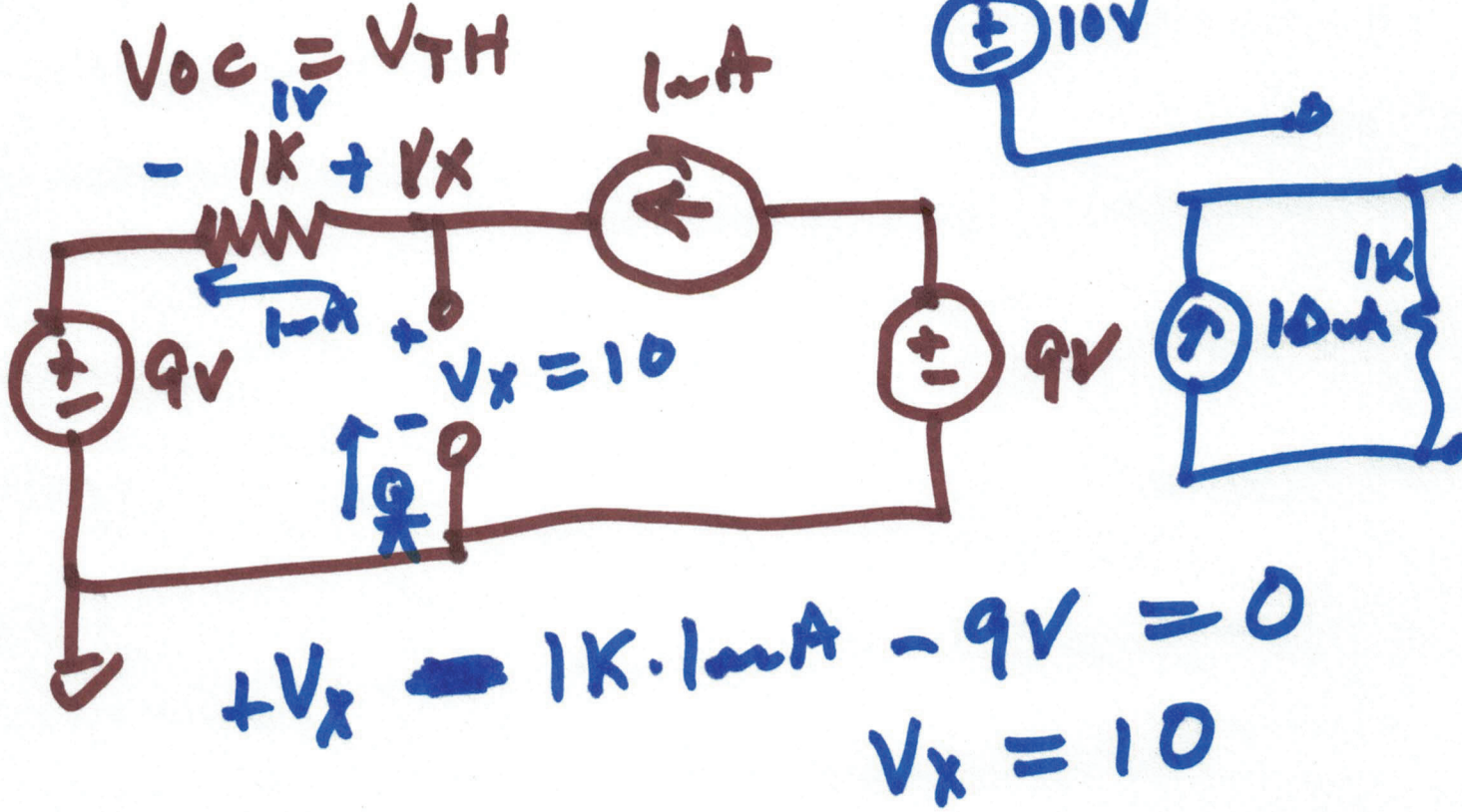


$$+V_x = 1K \cdot 1mA - 9V = 0$$

$$V_x = 10$$


7)

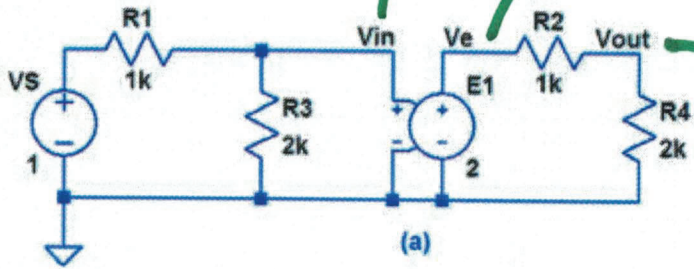5. Find  $V_{out}$  in each of the following circuits. Show your work for credit. (10 points)



$\frac{2}{3}V$   $\frac{4}{3}V$


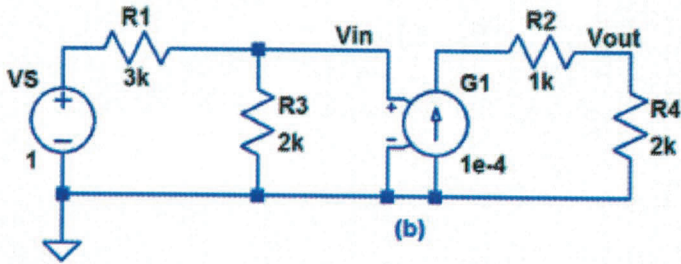
$$\frac{4}{3} \cdot \frac{2}{2+1} = \frac{8}{9}V$$



8)



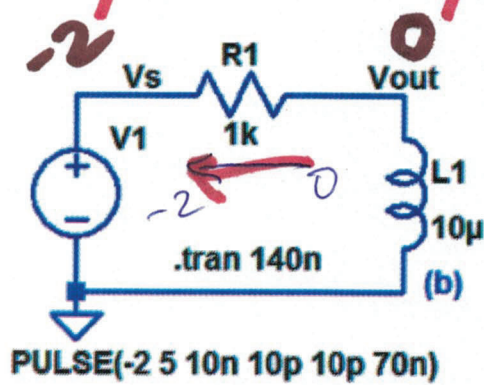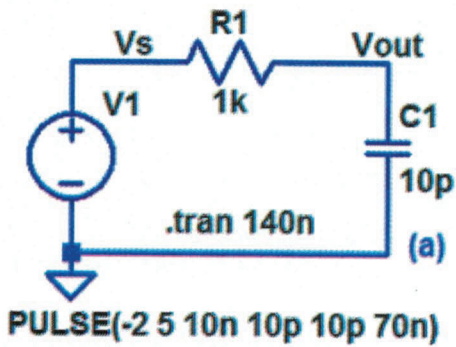6. Write the equations and sketch along with the input pulse (on the same plot), for each of the input pulse's transitions, for the output of each of the following circuits. (10 points)




$$\frac{7-5}{1k} = 2\mu A$$

$$\frac{0 - (-2)}{1k} = 2\mu A$$

$$N_i = 7$$

$$N_k = 0$$
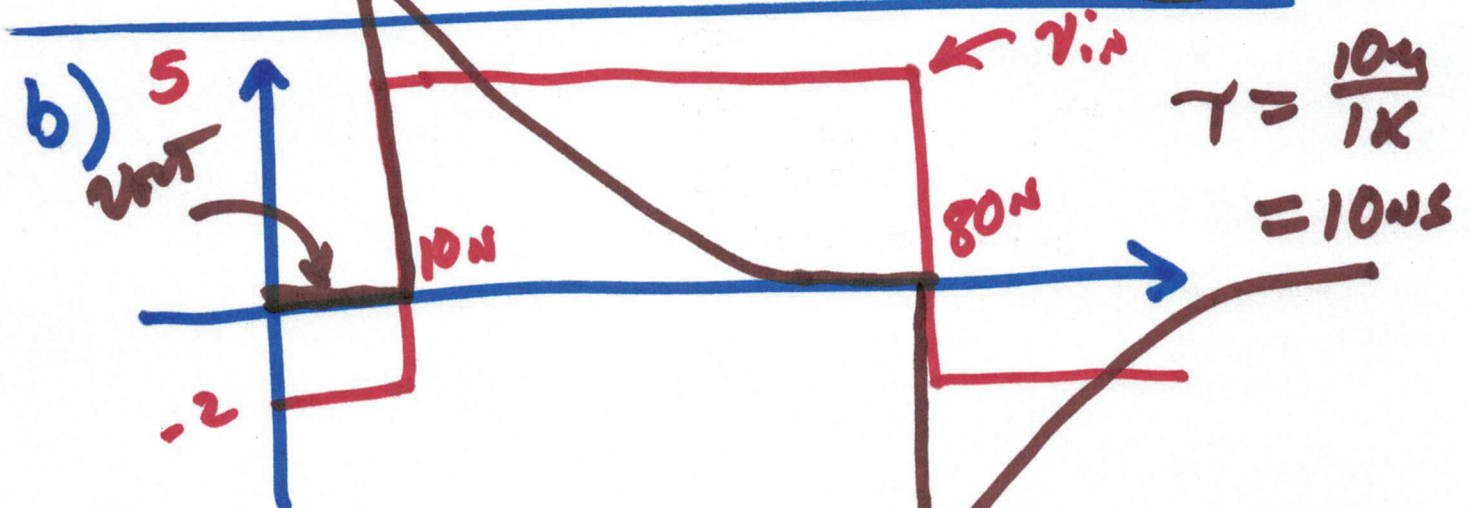
$$v_{out} = 0 + (7 - 0)e^{-\frac{(t-10n)}{10n}} \quad 10n \leq t \leq 80n$$



$$T = \frac{10\mu}{1k} = 10ns$$


$$v_i = -7$$

$$v_f = 0$$

$$v_{out} = -7e^{-\frac{(t-80n)}{10n}} \quad t \geq 80n$$

a)

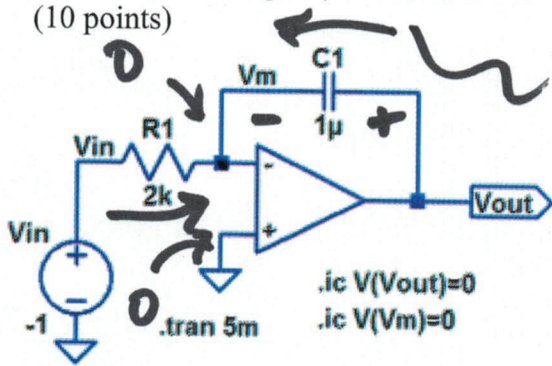7. Plot the output of the following circuit from a time 0 to 5 ms. Assume that the capacitor is initially discharged (both sides are at 0 V). Ensure you show how you calculate  $V_{out}$ . (10 points)




$$i_c = \frac{V_{in} - V_{out}}{R_1} = C \frac{dV_{out}}{dt}$$

$$2k \cdot 1\mu = 2m$$

$$\frac{V_{in}}{2k} + i_c = 0$$

$$\frac{V_{in}}{2k} + C \cdot \frac{dV_{out}}{dt} = 0$$
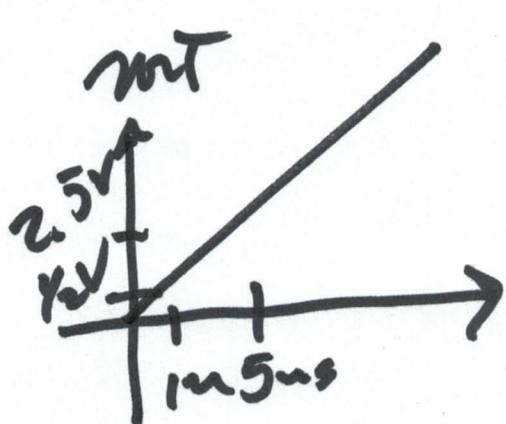
$$\frac{dV_{out}}{dt} = -\frac{V_{in}}{2m} t^{-1}$$



$$V_{out} = -\frac{1}{2m} \int_0^t V_{in} \cdot dt$$

$$V_{out} = \frac{1V}{2ms} \int_0^t \cdot dt$$

$$V_{out} = \frac{t}{2ms} V$$

10)