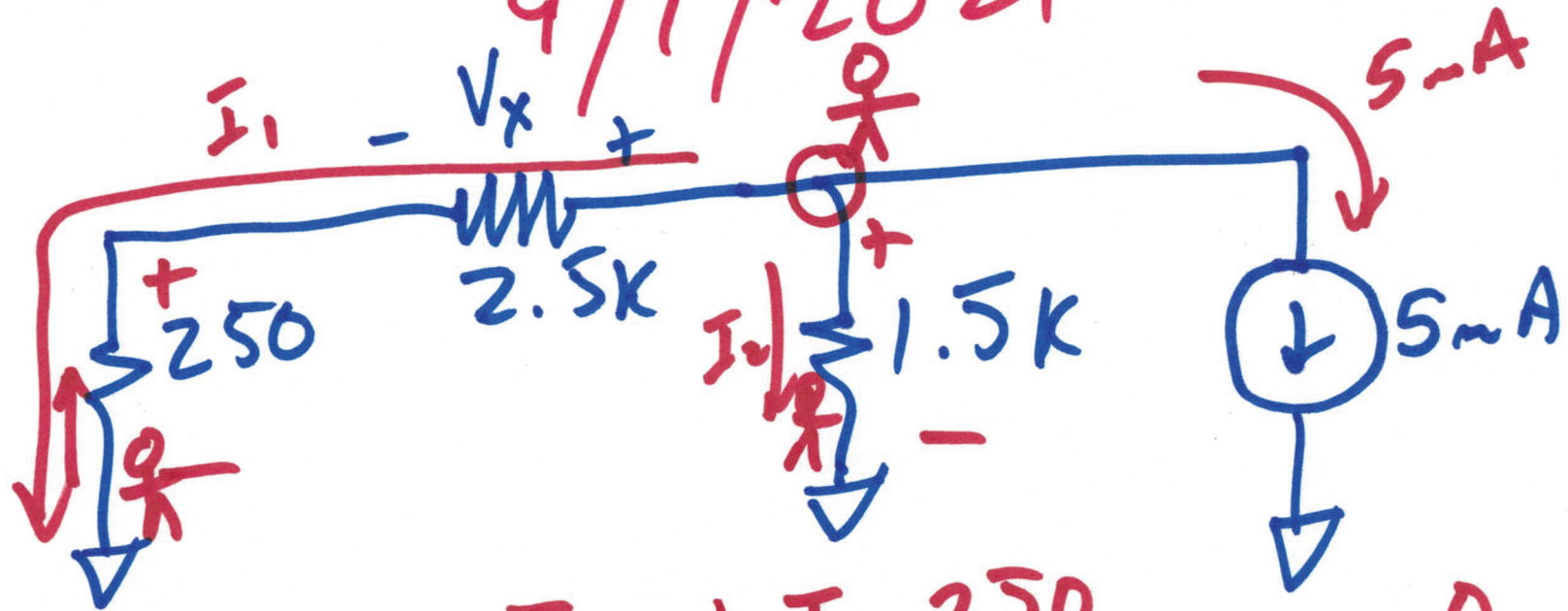


EE 220 Circuits I

Lecture 4

$$I \downarrow \begin{matrix} + \\ | \\ - \end{matrix} v = IR \quad \downarrow \begin{matrix} | \\ + \\ - \end{matrix} v = -I \cdot R$$

9/1/2021



$$\begin{aligned} \text{KVL} & -1.5k \cdot I_2 + I_1 \cdot 250 + \cancel{v_x} = 0 \\ \text{KCL} & I_1 + I_2 + 5mA = 0 \\ & I_1 = 2,500 \end{aligned}$$

1)

$$-1.5kI_2 + I_1 \cdot 250 + 2.5kI_1 = 0$$

$$I_1 + I_2 + 5\mu A = 0 \rightarrow I_1 = -I_2 - 5\mu A$$

$$-6I_2 + I_1 + 10I_1 = 0$$

$$-6I_2 + 11I_1 = 0$$

$$-6I_2 + 11I_2 - 55\mu A = 0$$

$$-17I_2 = 55\mu A$$

$$I_2 = \frac{-55\mu A}{17}$$


$$I_2 = 3.23\mu A$$

v)

$$I_1 + I_2 + 5 \mu A = 0$$

$$I_2 = -3.23 \mu A$$

$$I_1 = -1.77 \mu A$$

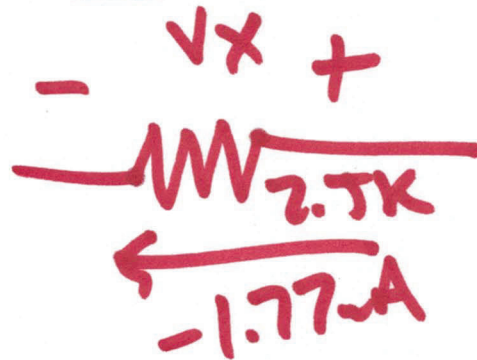


$$V_x = I \cdot 2.5K$$

$$V_x = -1.77 \mu A \cdot 2.5K$$

$$V_x = -4.425V$$

3)

Voltage Divider

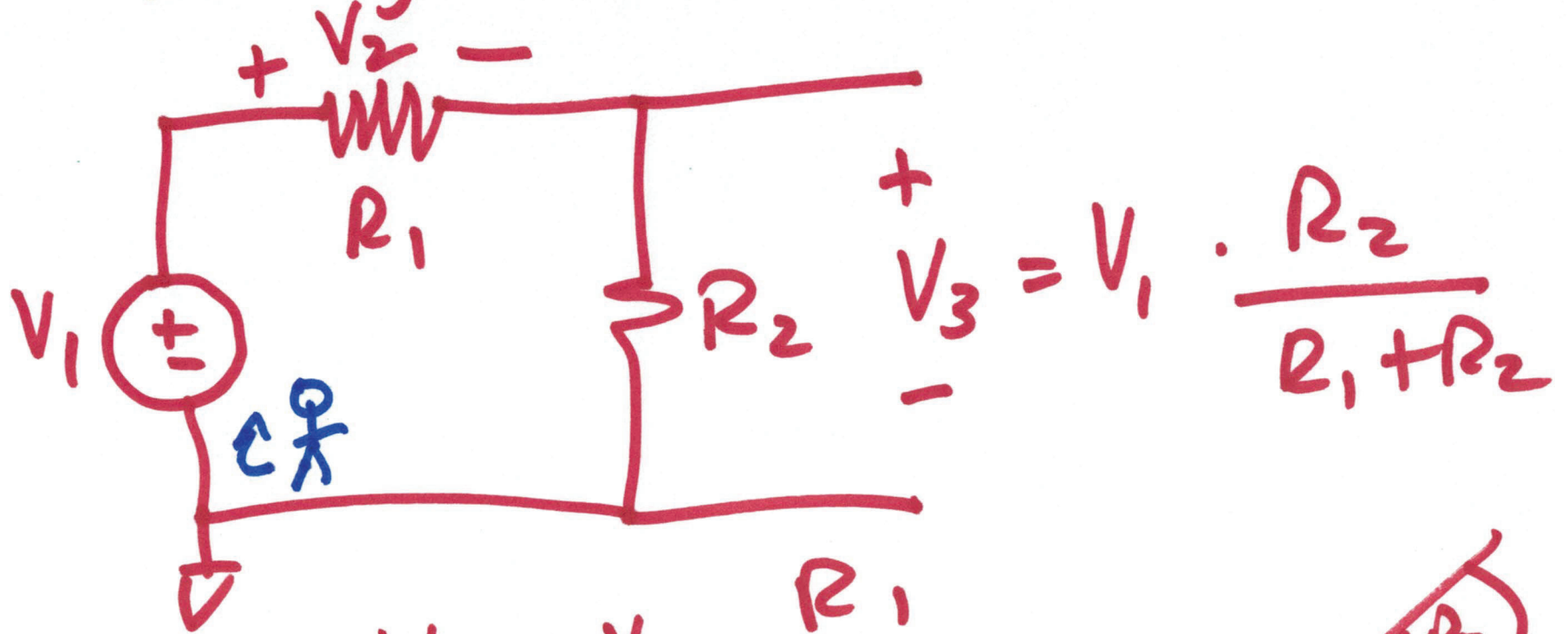

$$V_3 = V_1 \cdot \frac{R_2}{R_1 + R_2}$$

$$V_2 = V_1 \cdot \frac{R_1}{R_1 + R_2}$$

$$V_1 - V_2 - V_3 = 0$$


$$V_1 = V_2 + V_3$$

$$\frac{V_1 \cdot R_1}{R_1 + R_2}$$

$$+ \frac{V_1 \cdot R_2}{R_1 + R_2}$$

$$\frac{V_1 (R_1 + R_2)}{R_1 + R_2}$$

4)

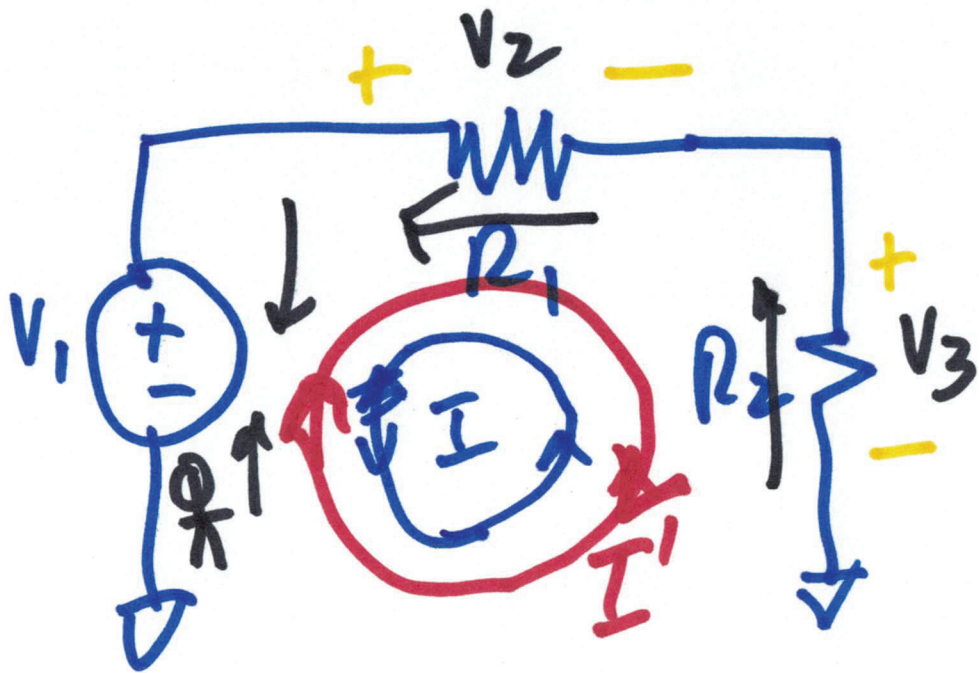

$$I \uparrow \downarrow \begin{matrix} + \\ - \end{matrix} \frac{V}{-} = -I \cdot R$$

$$I' = \frac{V_1}{R_1 + R_2}$$


$$V_1 = V_2 + V_3$$

$$V_1 - V_2 - V_3 = 0$$

$$V_1 - (-I \cdot R_1) - (-I \cdot R_2) = 0$$

$$I = -\frac{V_1}{R_1 + R_2}$$


5)

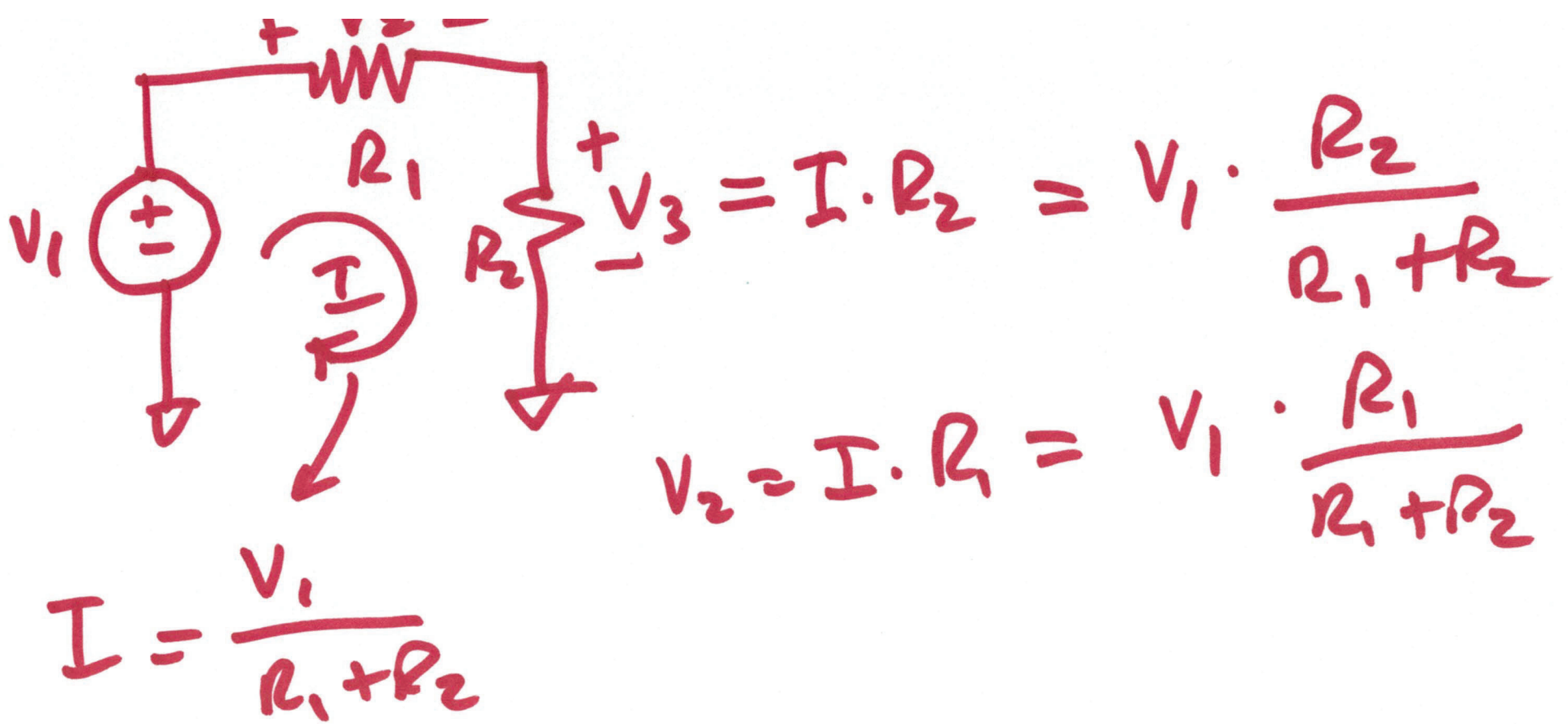

b)

CURRENT divider


$$I_1 = I_2 + I_3$$

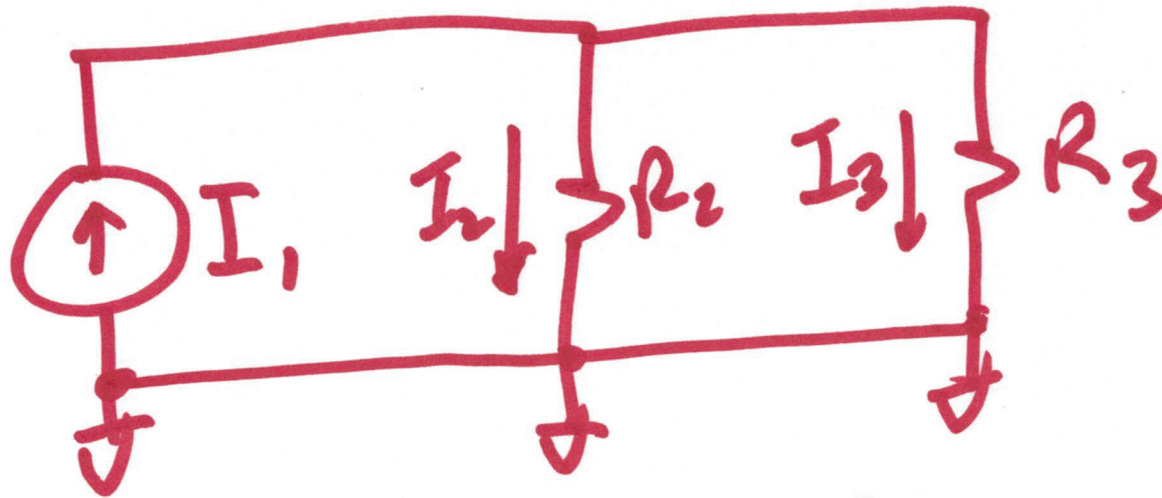

$$I_2 = I_1 \cdot \frac{R_3}{R_2 + R_3}$$
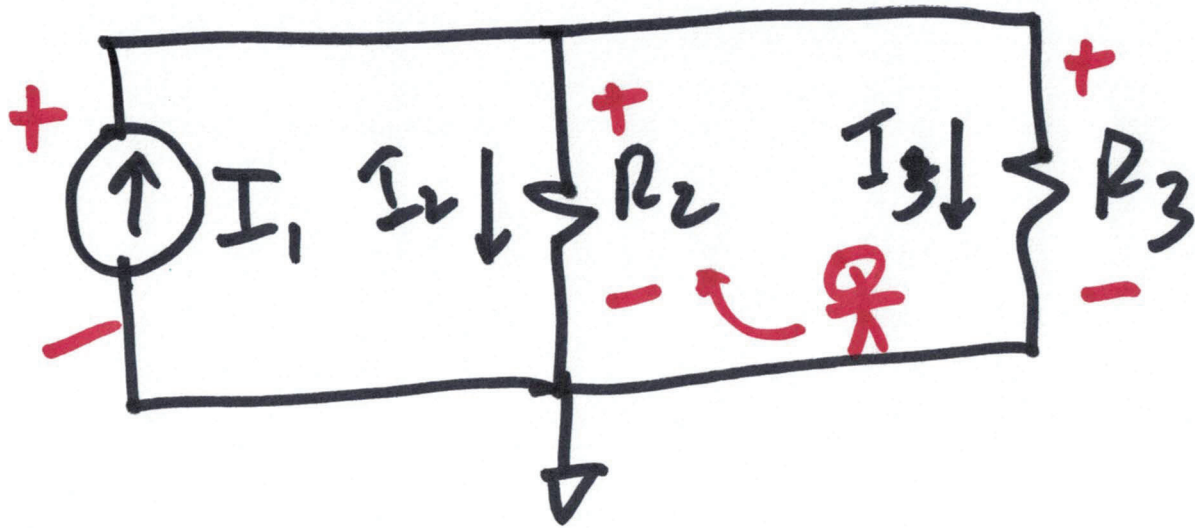
$$I_3 = I_1 \cdot \frac{R_2}{R_2 + R_3}$$





$$I_2 = I_1 \cdot \frac{R_3}{R_2 + R_3}$$

$$I_2 \cdot R_2 - I_3 \cdot R_3 = 0$$


$$I_1 = I_2 + I_3$$

$$I_3 = I_1 \cdot \frac{R_2}{R_2 + R_3}$$

$$I_2 = -I_3 + I_1$$

$$R_2(-I_3 + I_1) - I_3 \cdot R_3 = 0$$

$$I_1 \cdot R_2 = I_3(R_2 + R_3)$$

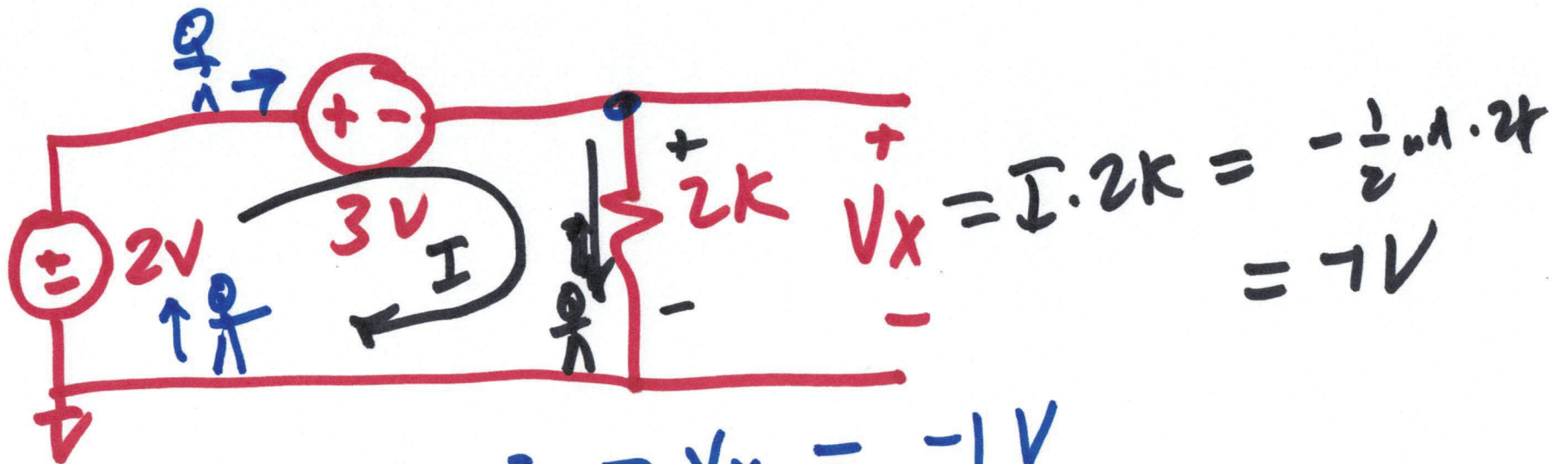

$$+2 - 3 = V_x = -1V$$


$$V_x + 3 - 2 = 0$$

$$+I \cdot 2k + 3 - 2 = 0$$

$$I \cdot 2k + 1 = 0$$

$$I = -\frac{1}{2k} = -\frac{1}{2} \mu A$$

a)

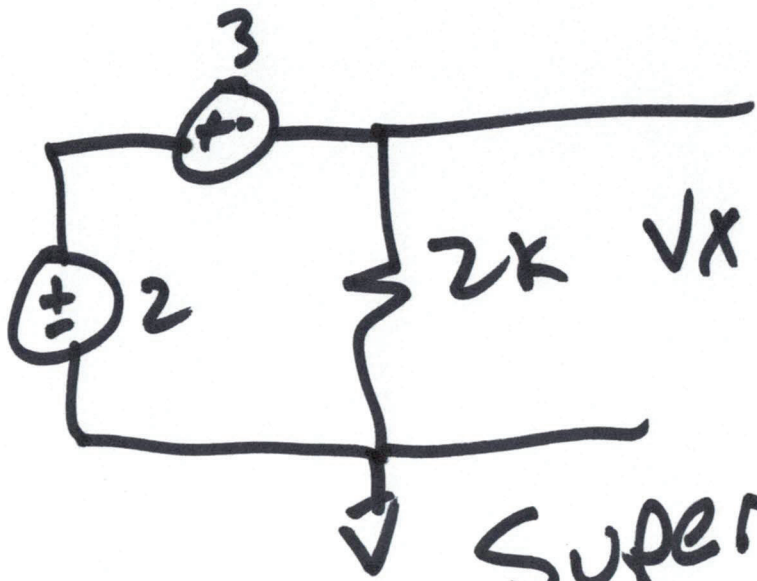


Super position

Look At one source at a



time

Voltage \rightarrow wire (short)


Current sources \rightarrow open

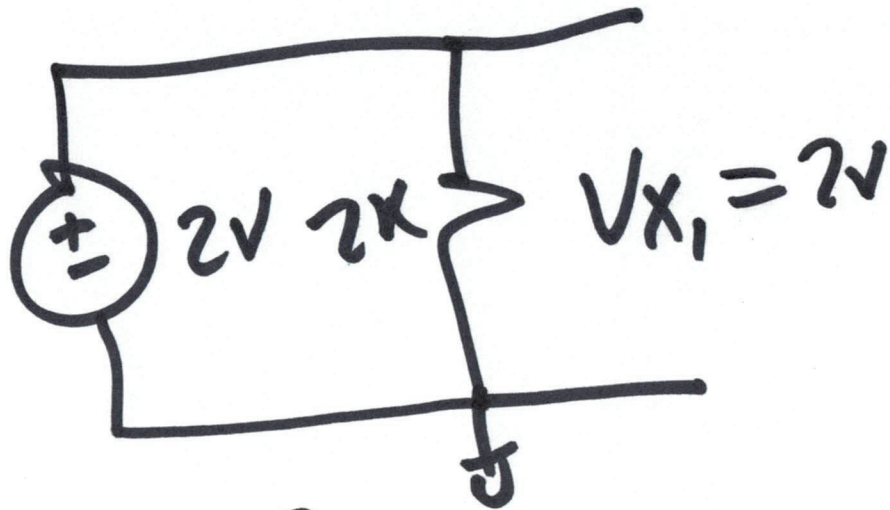

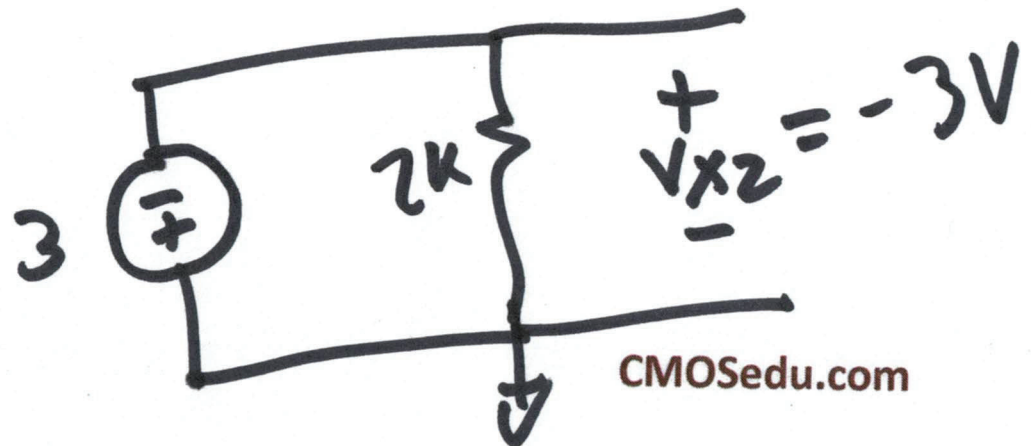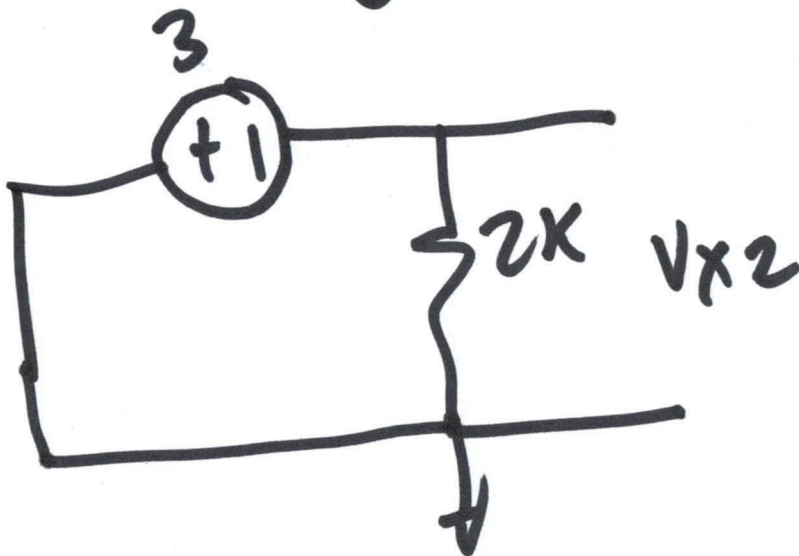
$$V_x = V_{x1} + V_{x2} = 2 - 3 = \underline{\underline{-1V}}$$



11)

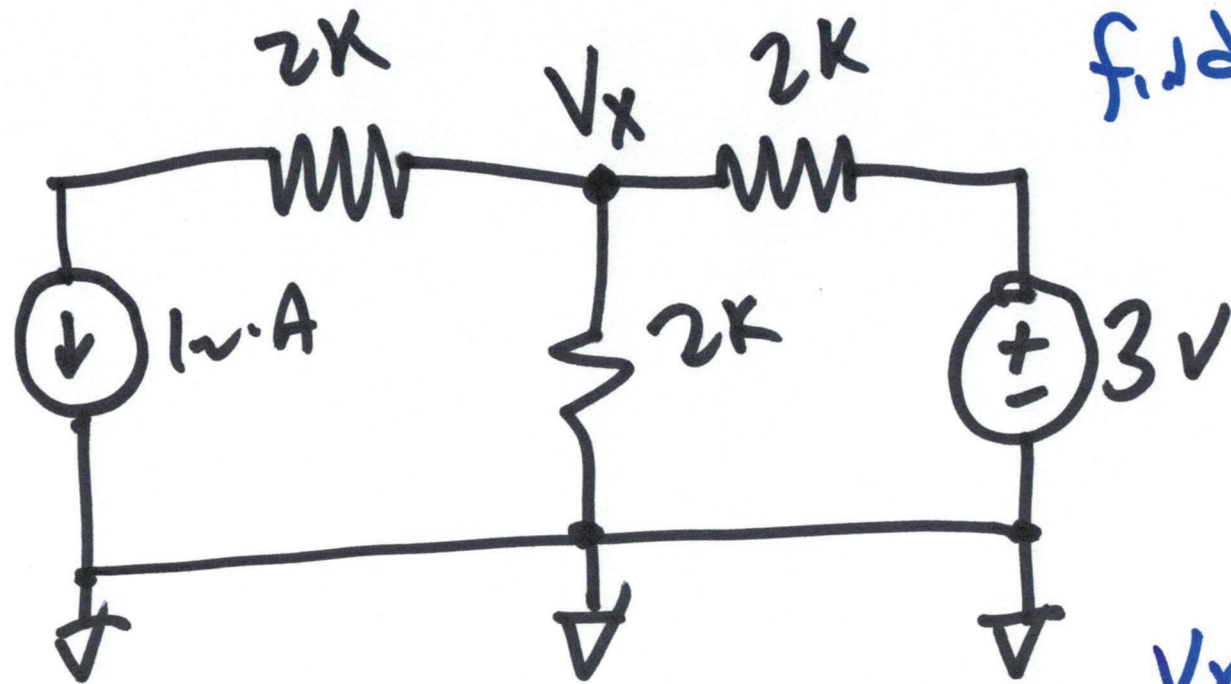



find V_x
using
superposition

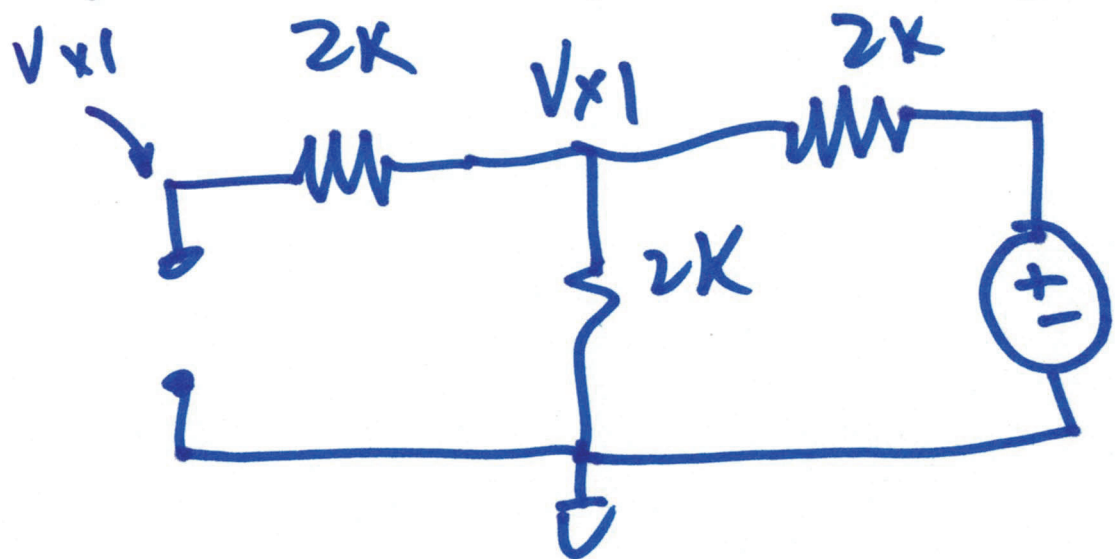


$$V_{x1} = 3 \cdot \frac{2k}{2k+2k}$$

$$V_{x1} = 1.5V$$

12)

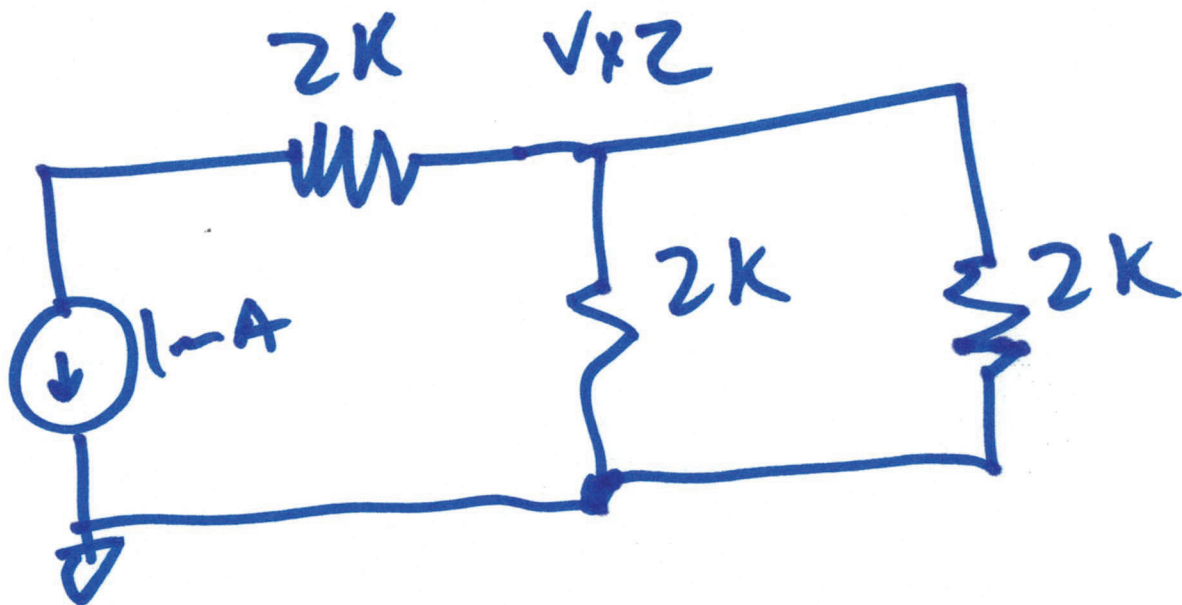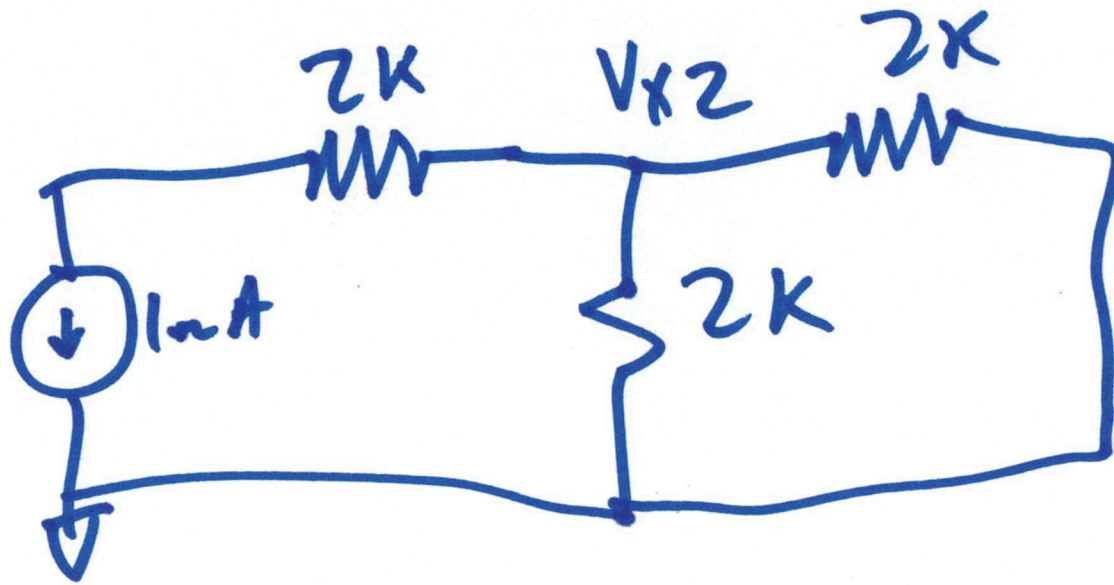

13)

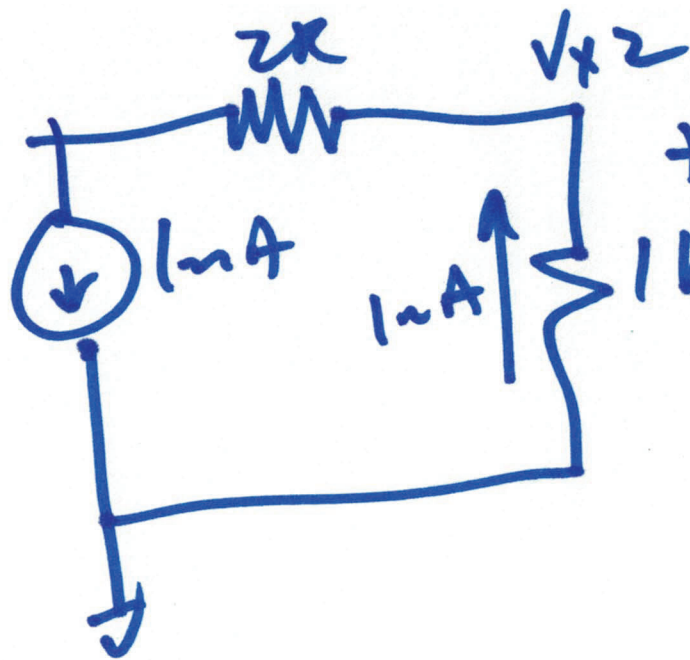

$$V_{x2} = -1\mu A \cdot 1K = -1V$$

$$V_x = V_{x1} + V_{x2} = 1.5 - 1$$

$$V_x = 0.5V$$