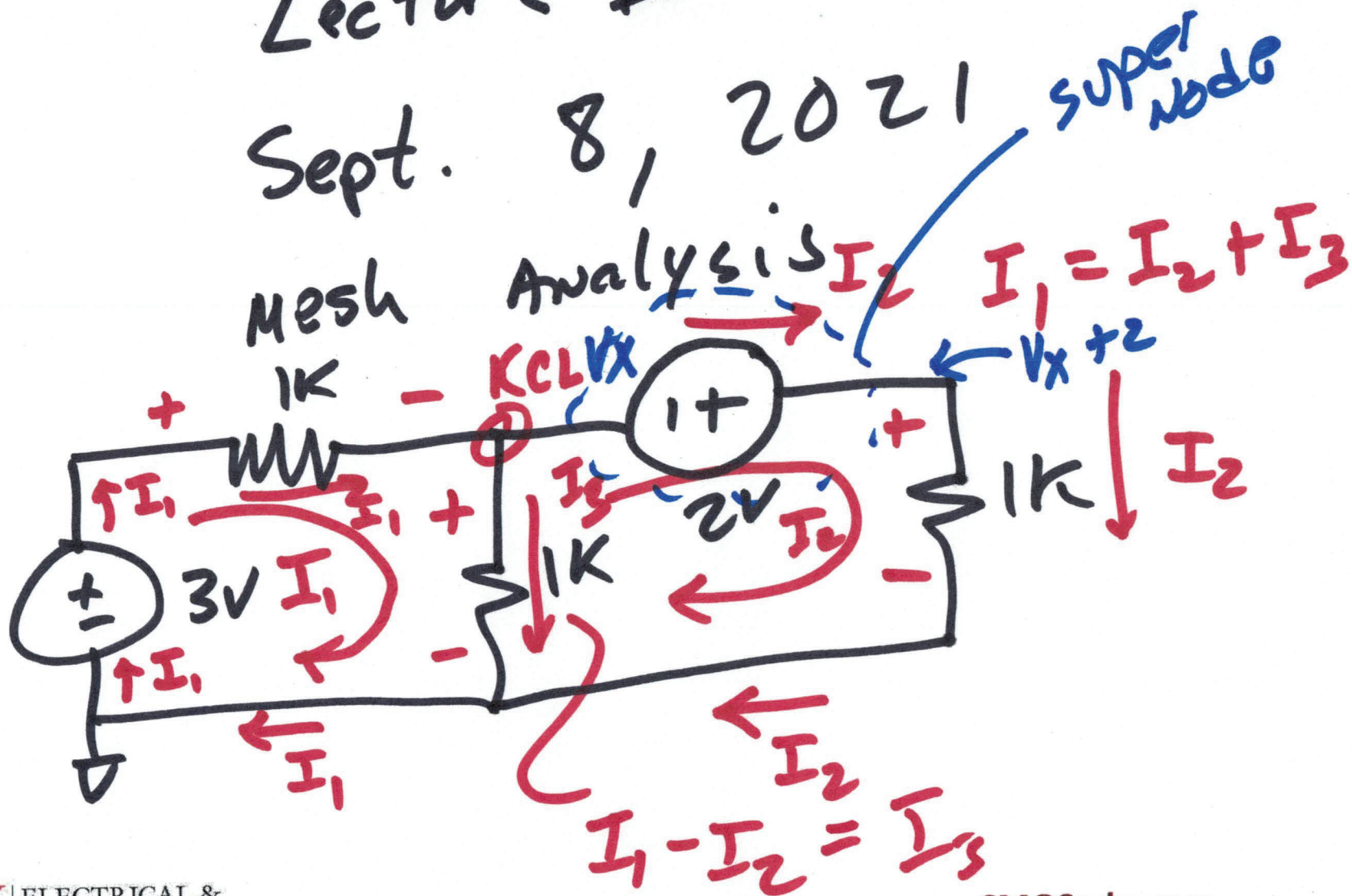



EE 220 Circuits 1

Lecture ~~5~~ 5

Sept. 8, 2021 ^{super node}



1)

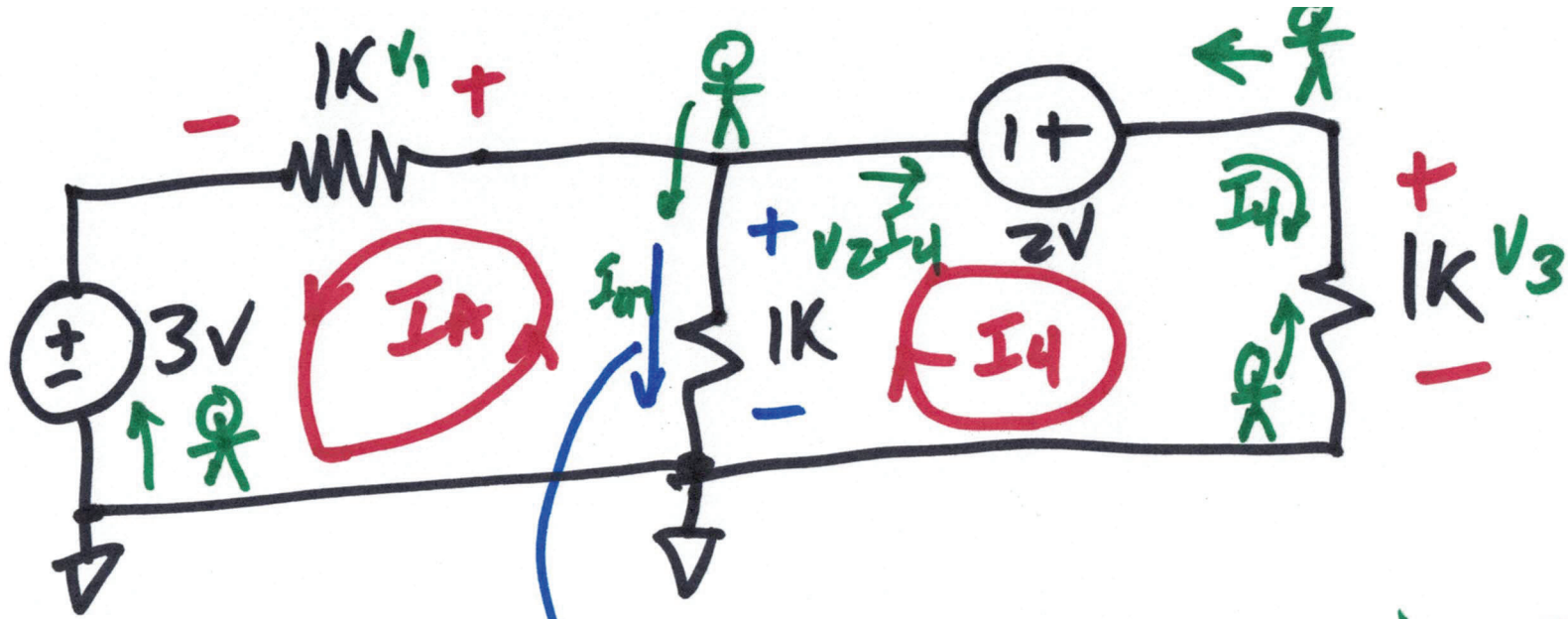

$$-I_A - I_4$$

$$V_1 = I_A \cdot 1K$$


$$-V_2 + V_3 - 2 = 0$$

$$V_3 = I_4 \cdot 1K$$

$$-V_2 + 3 + V_1 = 0$$

$$1K(-I_A - I_4) = V_2 = I_4 \cdot 1K$$

2)

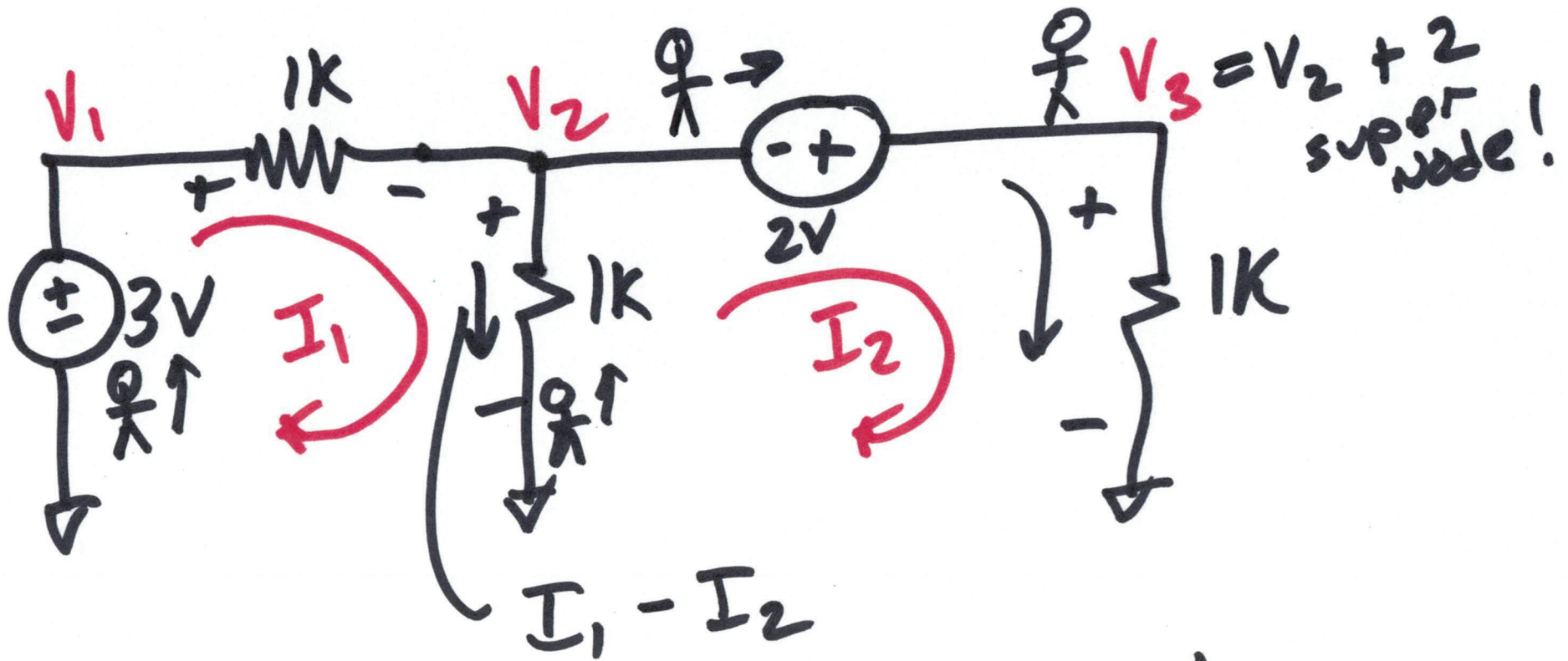

$$\begin{aligned}
 3 - I_1 \cdot 1k - 1k(I_1 - I_2) &= 0 \\
 2 - 1kI_2 + 1k(I_1 - I_2) &= 0 \\
 \rightarrow 3mA - I_1 - I_1 + I_2 &= 0 \\
 \rightarrow 2mA - I_2 + I_1 - I_2 &= 0
 \end{aligned}$$

3)

$$3 \text{ mA} - 2I_1 + I_2 = 0$$

$$I_1 = 1.5 \text{ mA} + \frac{I_2}{2}$$

$$2 \text{ mA} - 2I_2 + I_1 = 0$$


$$2 \text{ mA} - 2I_2 + 1.5 \text{ mA} + \frac{I_2}{2} = 0$$

$$3.5 \text{ mA} - 1.5 I_2 = 0$$

$$I_2 = \frac{3.5}{1.5} \text{ mA}$$
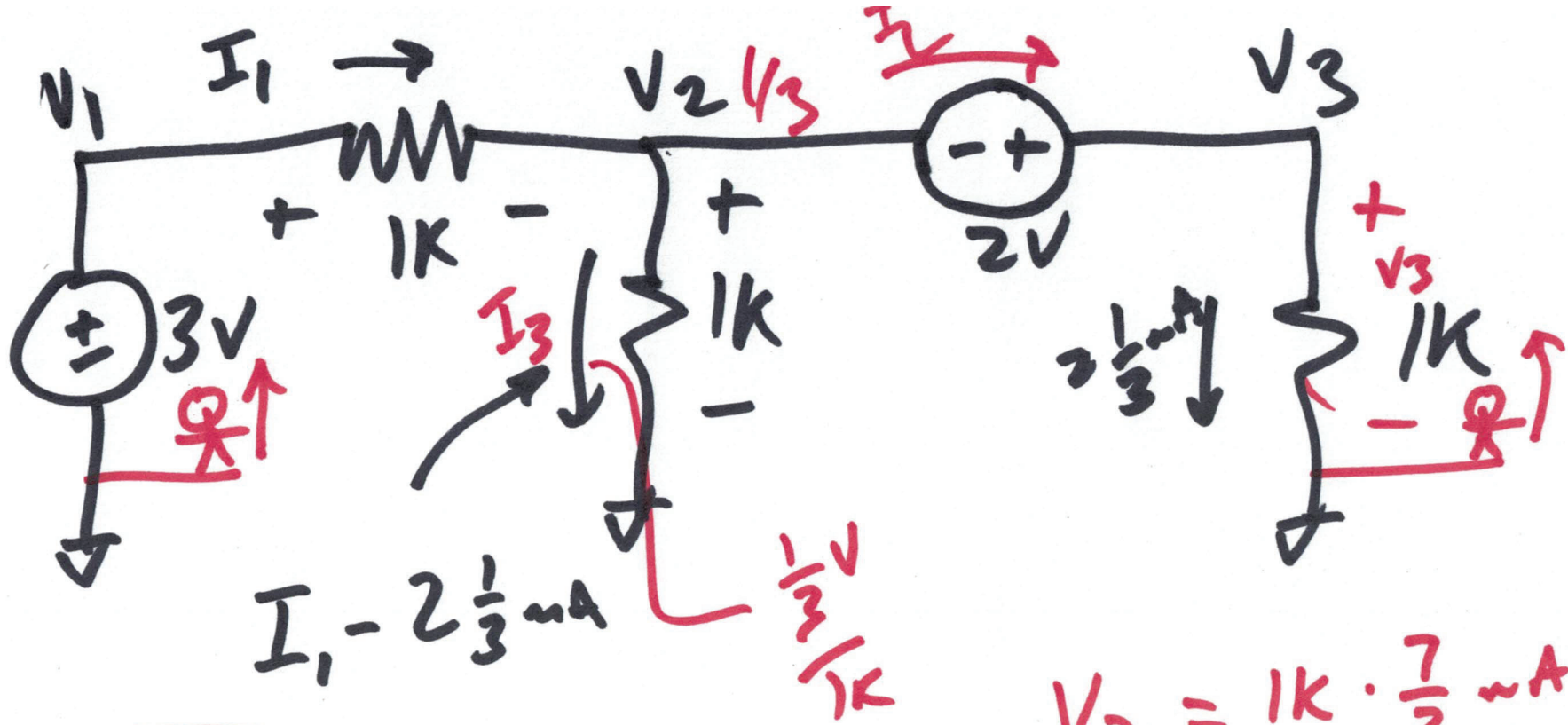
$$I_2 = \frac{7}{3} \text{ mA} = 2.333 \text{ mA}$$





$$V_1 = 3V$$

$$I_3 = \frac{1}{3} \mu A$$

$$V_3 = 1K \cdot \frac{7}{3} \mu A$$

$$V_3 = \frac{7}{3} V$$


$$I_1 = \frac{1}{3} \mu A + \frac{7}{3} \mu A$$

$$V_2 = V_3 - 2 = \frac{1}{3} V = V_2$$

$$I_1 = \frac{8}{3} \mu A$$

$$I_1 = 2.666 \mu A$$

9)

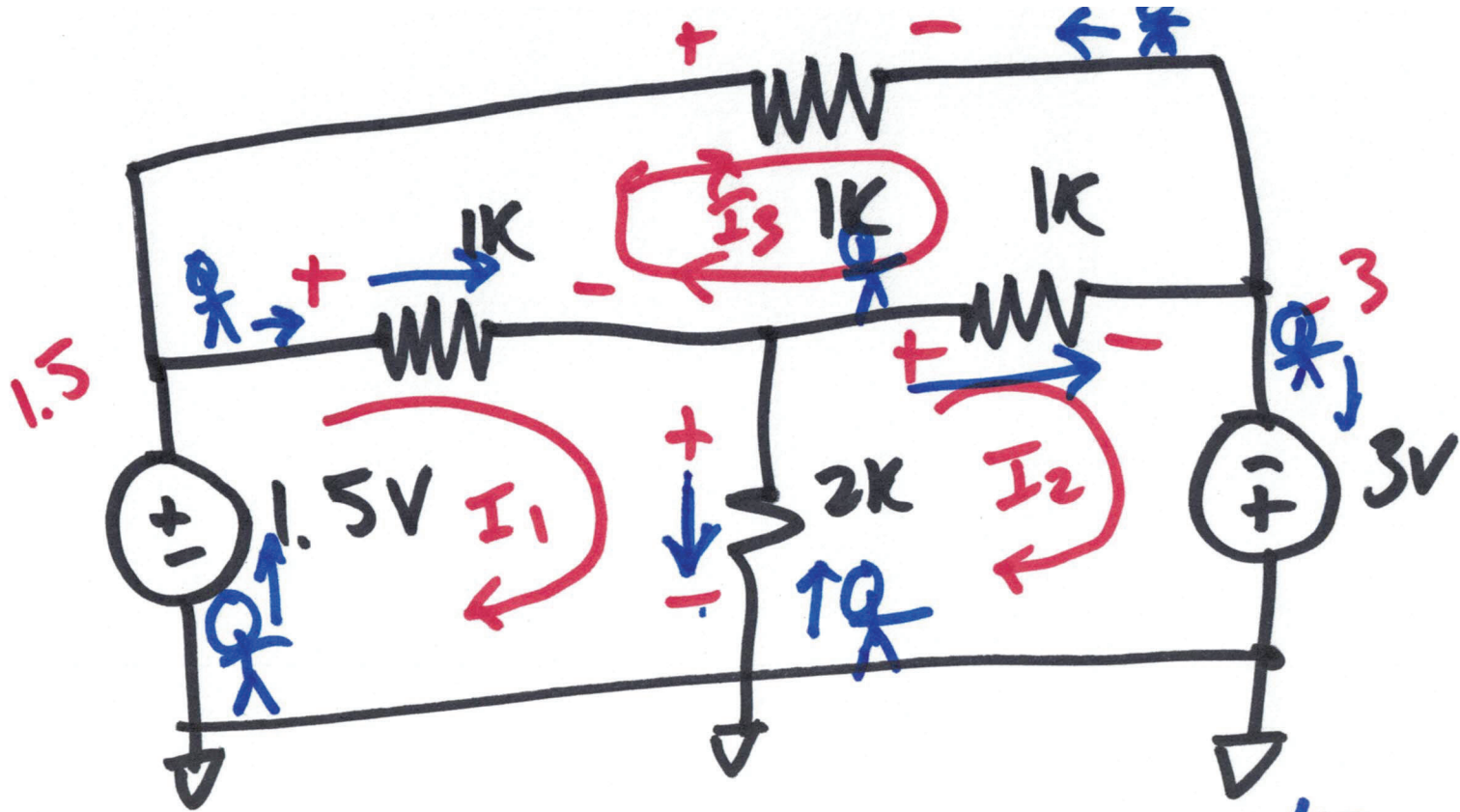


$$I_3 \cdot 1k - (I_1 - I_3) \cdot 1k - 1k(I_2 - I_3) = 0$$

$$-1k(I_1 - I_3) - 2k(I_1 - I_2) + 1.5 = 0$$

$$+3 + 2k(I_1 - I_2) - 1k(I_2 - I_3) = 0$$

6)

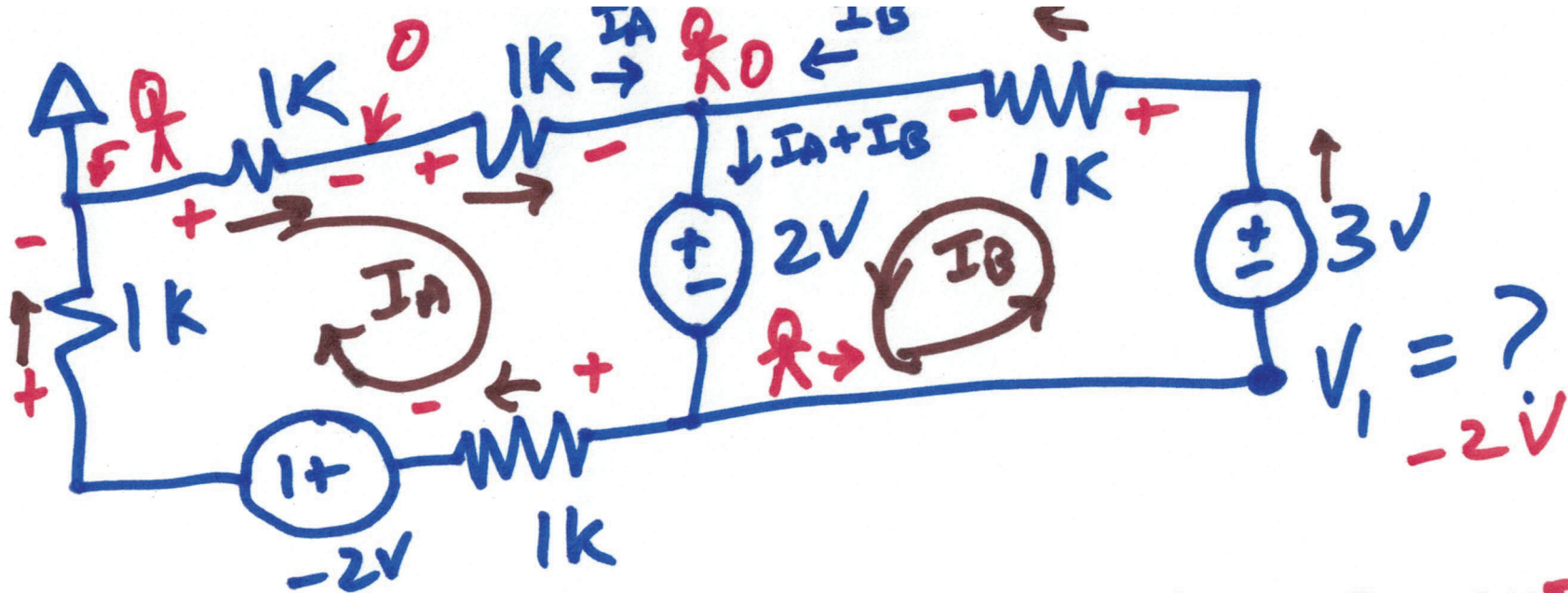

$$0 = +1k \cdot I_A + (-2V) + 1k I_A + 2V + 1k I_A + 1k I_A$$

$$0 = 4k I_A \rightarrow I_A = 0$$

$$+3 - 1k I_B - 2 = 0$$

$$I_B = 1 \mu A$$