
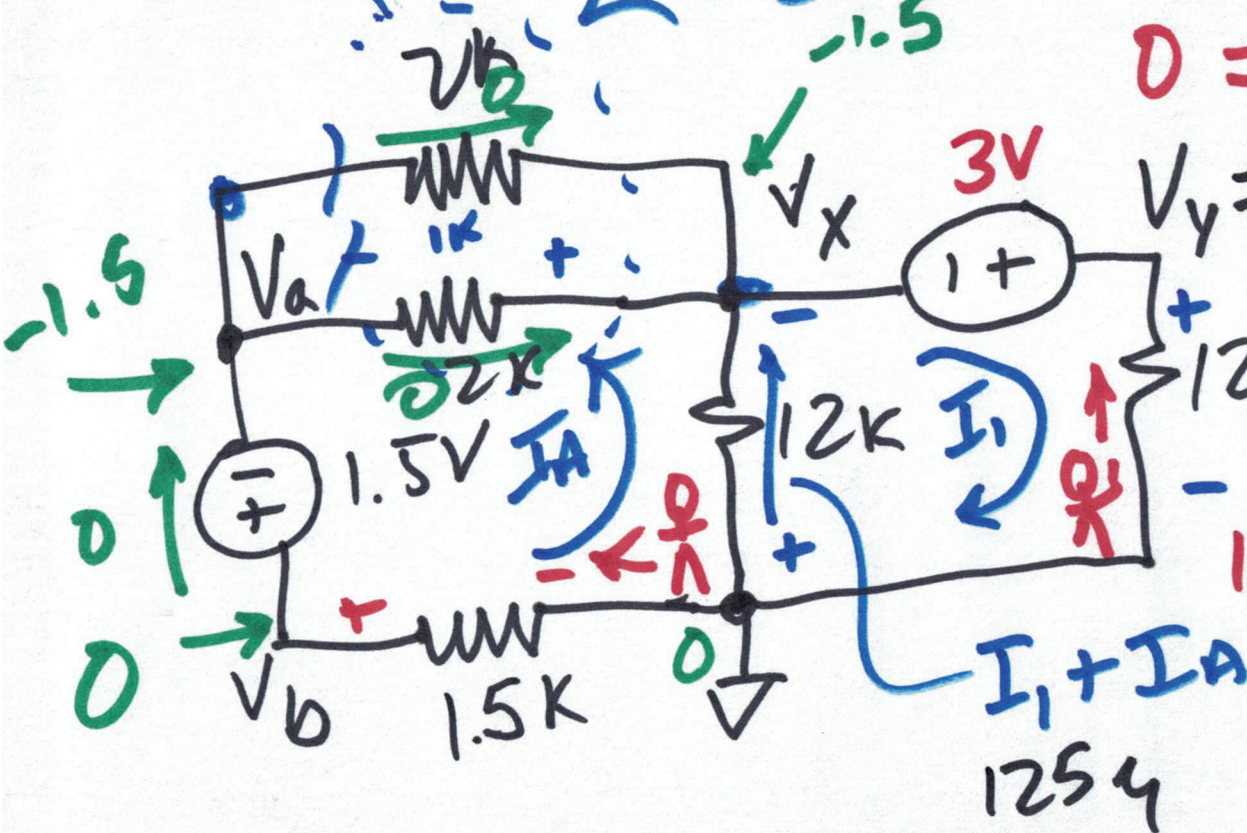


EE 220 CIRCUITS I

OCT. 3, 2022

Lecture 10

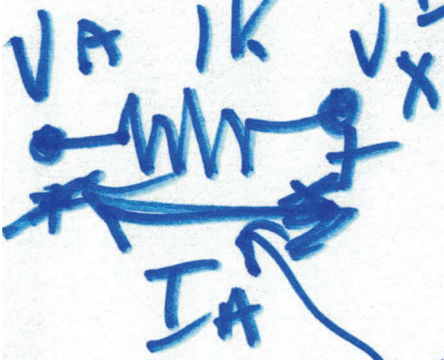

$$0 = 12kI_1 - 3 + 12k(I_1 + I_A)$$

$$V_y = 1.5$$

$$\frac{0 - 1.5}{12k} = 125 \mu A$$

$$1.5kI_A - 1.5V + 1kI_A$$

$$+ 12k(I_1 + I_A) = 0$$

125 μ

$$0 = I_1 - \frac{1}{4} \text{mA} + I_1 + I_A$$

$$-2I_1 = -250 \mu\text{A} + I_A$$

$$I_1 = 125 \mu\text{A} - \frac{I_A}{2}$$

$$0 = 1.5 \text{K} I_A - 1.5 + 10^3 I_A + 12 \text{K} I_1 + 12 \text{K} I_A$$

$$1.5 = 14.5 \text{K} I_A + 12 \text{K} \left(125 \mu\text{A} - \frac{I_A}{2} \right)$$

$$= 14.5 \text{K} I_A + \frac{12}{8} \text{mV} - 6 \text{K} I_A$$

$$1.5 = \cancel{14.5 \text{K}} 8.5 \text{K} I_A + 1.5 \text{V}$$


$$0 = I_A = \cancel{3 \text{mA}} = \cancel{353 \mu\text{A}}$$

2)

$$I_A = 0$$

$$I_1 = 1254A - 0$$

3)

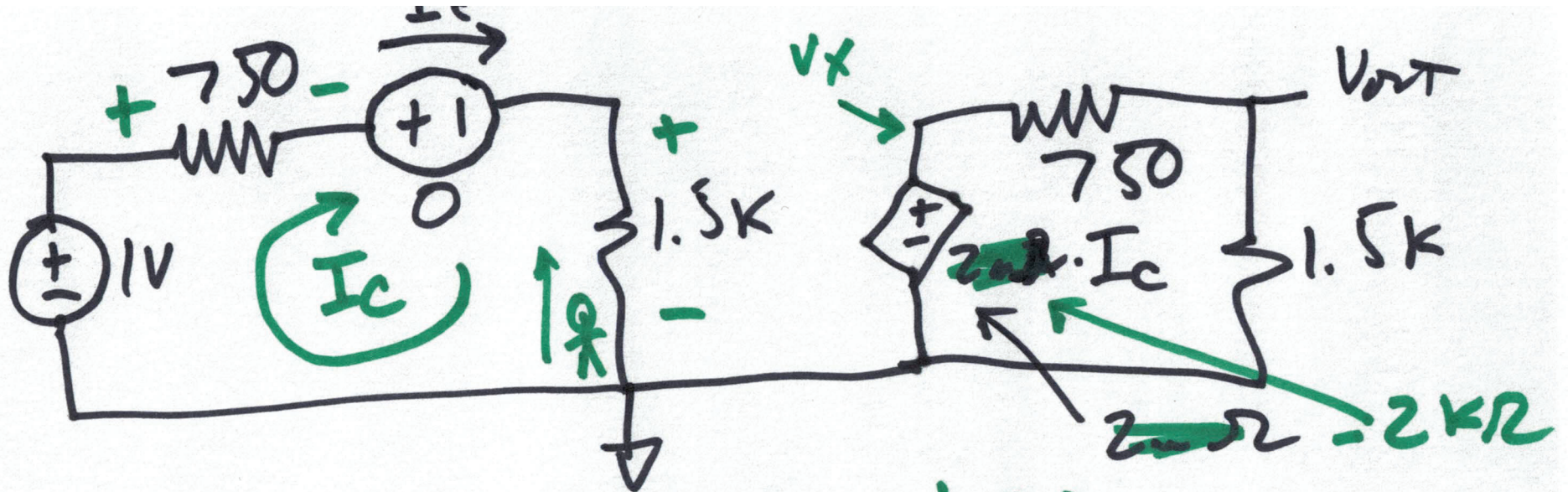

$$1.5kI_c + 0 + 750I_c - 1 = 0$$


$$2.25kI_c = 1$$

$$I_c = \frac{1}{2.25k} \text{ nA} = \frac{4}{9} \text{ nA}$$

$$V_x = -2k\Omega \cdot \frac{4}{9} \text{ nA} = -\frac{8}{9} \text{ V}$$

$$V_{out} = -\frac{8}{9} \cdot \frac{1.5k}{1.5k + 750}$$


4)

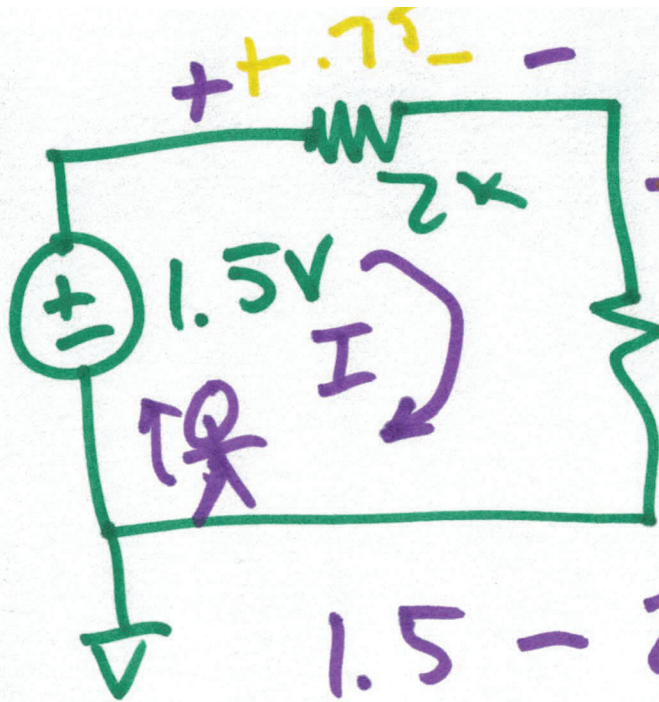

$$2kI = 2k \cdot \frac{1.5}{4k} = .75V$$

$$1.5 - 2kI - 2kI = 0$$

$$I = \frac{1.5}{4k}$$

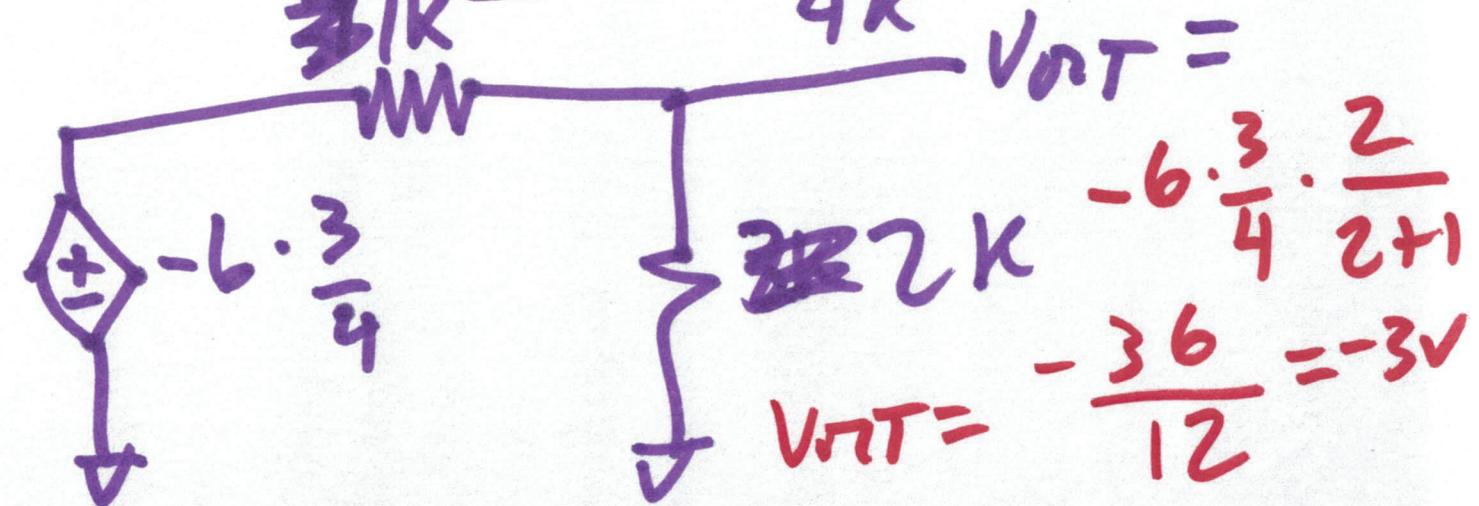


$$V_{out} = -6 \cdot \frac{3}{4} \cdot \frac{2}{2+1} = -\frac{36}{12} = -3V$$

Power is the use of energy over time

Watts
OR
 $\frac{\text{Joules}}{\text{s}}$


Joules CPU-Z

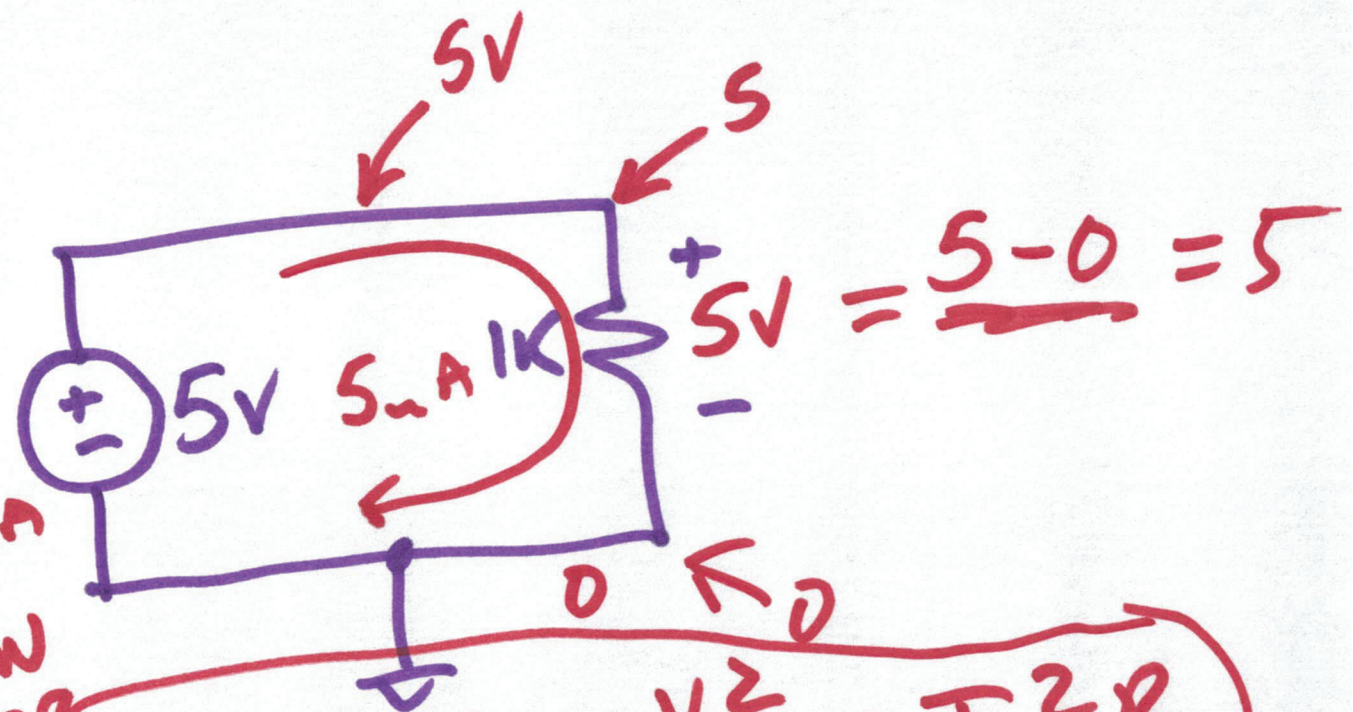

Power = $V \cdot I$
 $= 5 \cdot 5 \text{mA}$
 $= 25 \text{mW}$
 $I = \frac{V}{R} \Rightarrow V = IR$

$P = V \cdot I = \frac{V^2}{R} = I^2 R$

4)

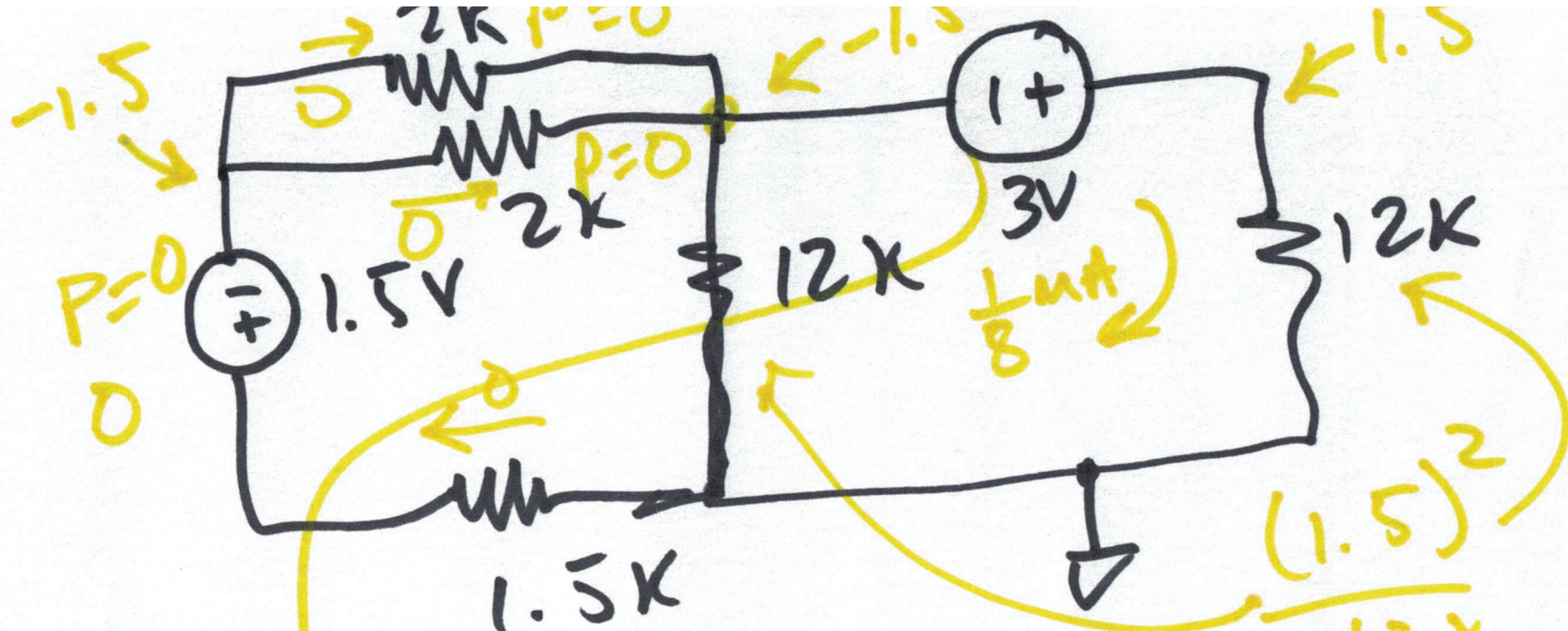

$$P = 3 \cdot \frac{1}{8} \text{ mA}$$

$$= \frac{3}{8} \text{ mW}$$

$$= -375 \text{ mW}$$

$$P = \frac{(-1.5)^2}{12\text{k}} = \frac{(1.5)^2}{12\text{k}} = 187.5 \mu\text{W}$$

