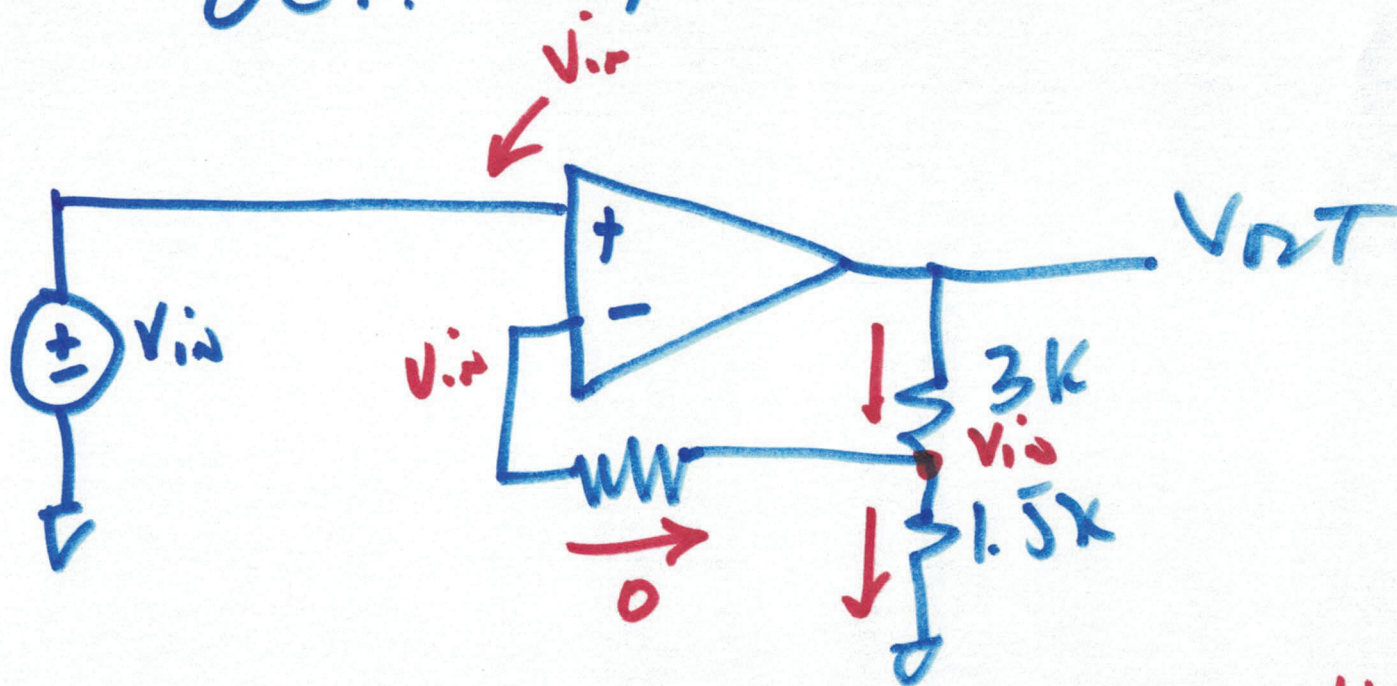


# EE 220 circuits I

## Lecture 13

OCT. 12, 2022




$$\frac{V_{in}}{1.5K} = \frac{V_{out} - V_{in}}{3K}$$





$$2V_{in} = V_{out} - V_{in}$$

$$V_{out} = 3V_{in}$$

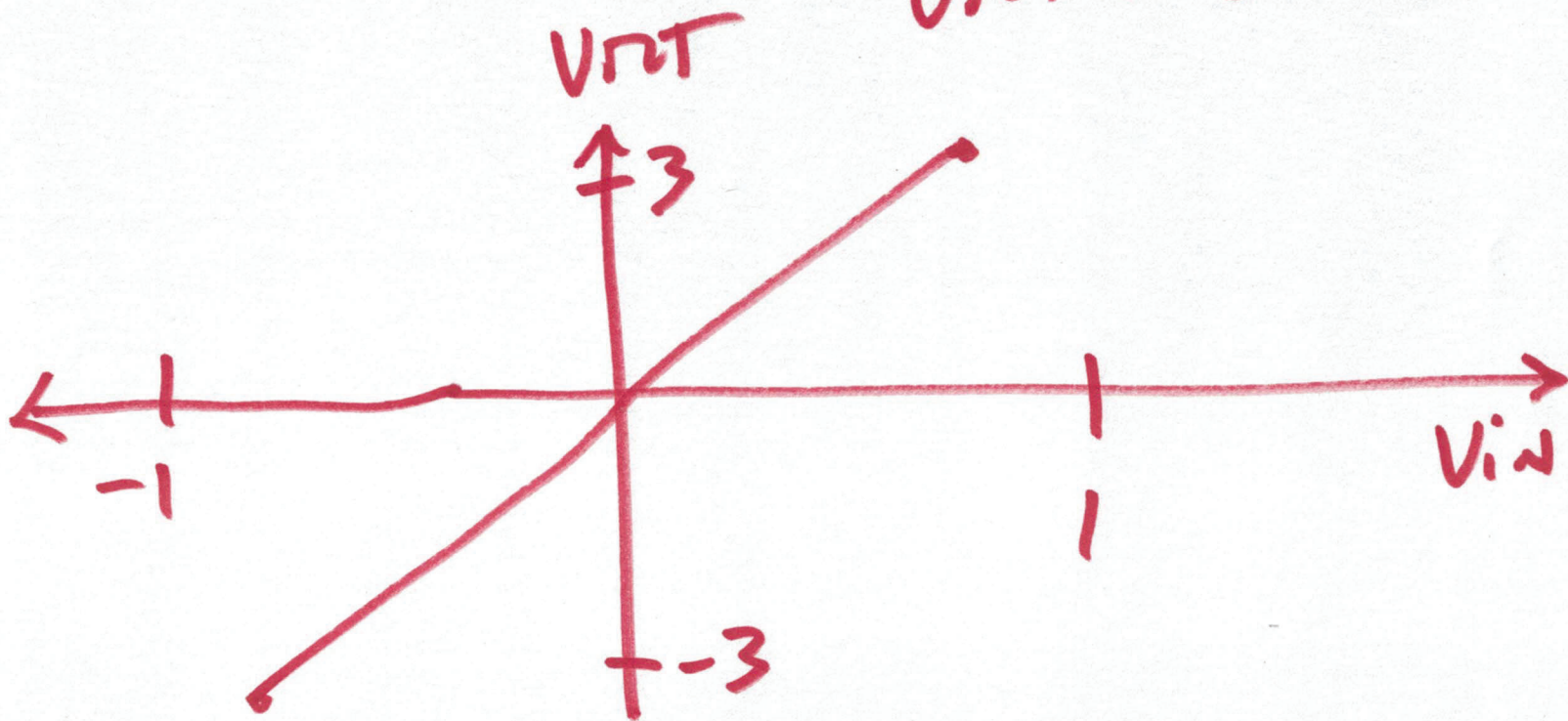



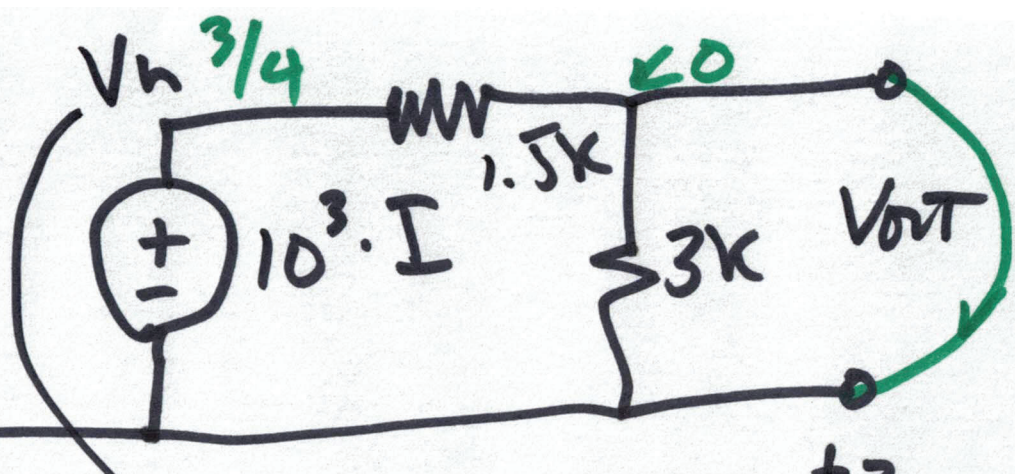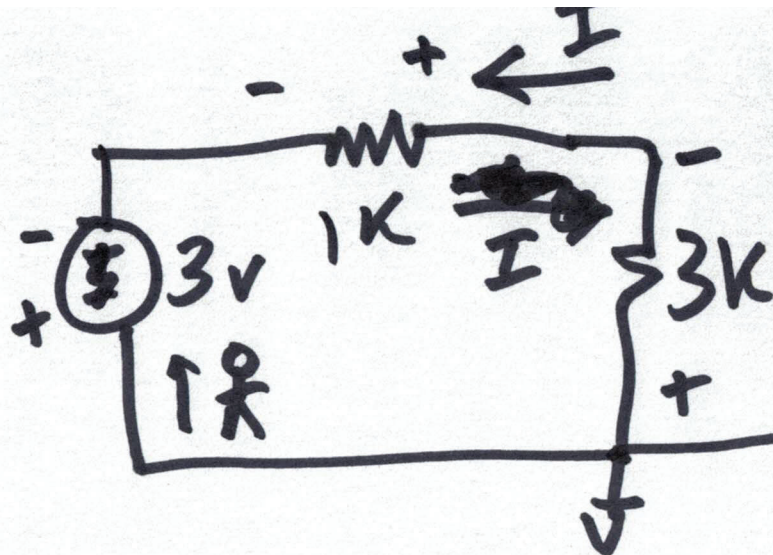


$$I = \frac{+3}{4k} = +\frac{3}{4} \text{ mA}$$

$$10^3 \cdot +\frac{3}{4} \text{ mA} = +\frac{3}{4} \text{ V}$$

$$V_{out} = +\frac{3}{4} \cdot \frac{3}{3+1.5}$$

$$-3 + 1kI + 3kI = 0$$

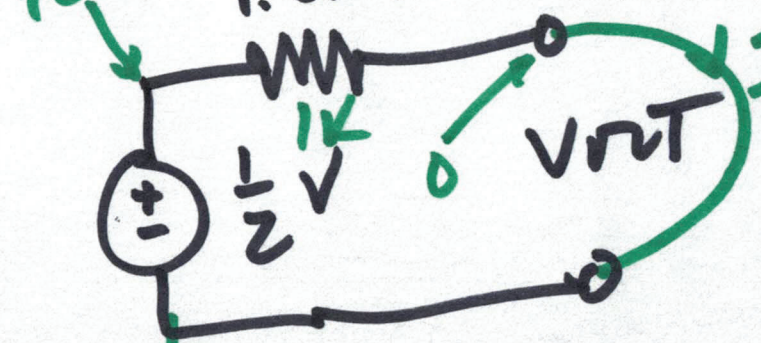

$$I_{sc} = \frac{1/2 \text{ V}}{1k} = \frac{1}{2} \text{ mA}$$

$$= +\frac{3}{4} \cdot \frac{2}{3}$$

$$= +\frac{6}{12} = +\frac{1}{2} \text{ V}$$

$$\frac{3/4 - 0}{1.5k} = \frac{3/4}{1.5k} = \frac{2}{4} = \frac{1}{2} \text{ mA}$$




NAME: \_\_\_\_\_

Closed book and notes.

Show your work for credit and put a box around your answers.

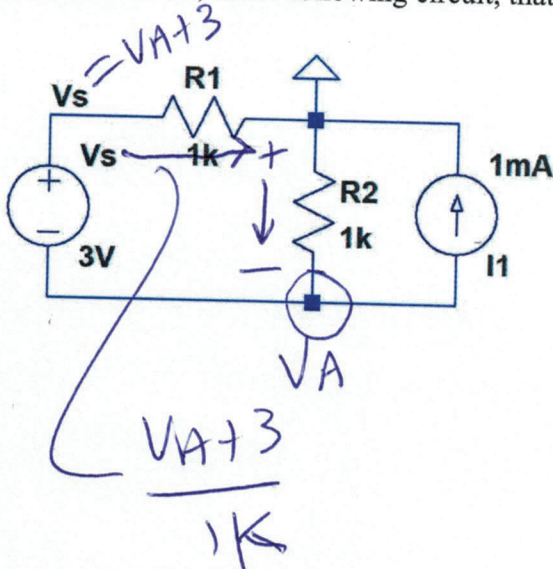1. Find the current, in the following circuit, that flows in R2. (10 points)





$$\frac{0 - V_A}{1K} = 1mA + \frac{V_A + 3}{1K}$$

$$-V_A = 1 + V_A + 3$$


$$-4 = 2V_A$$

$V_A = -2V$

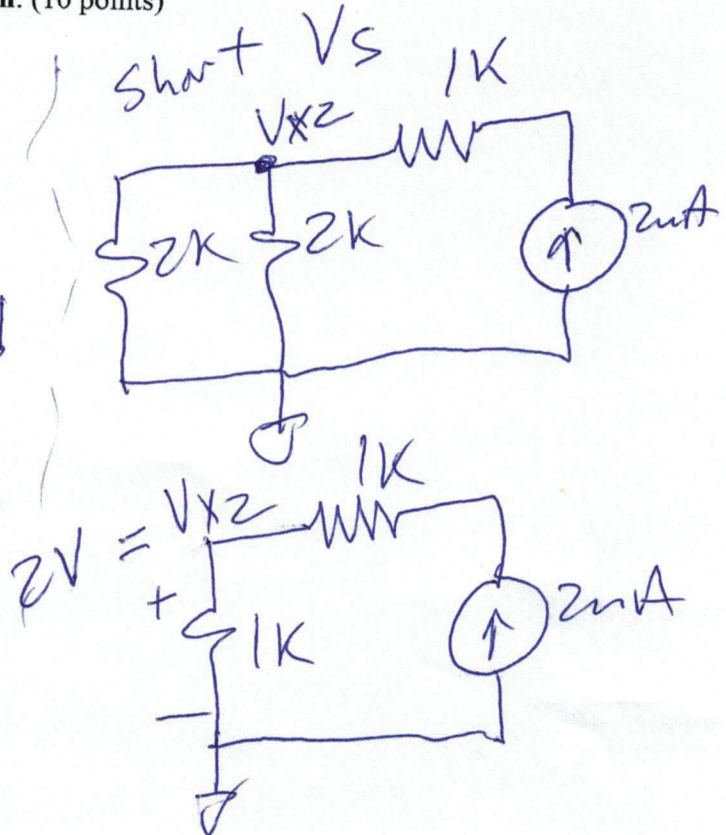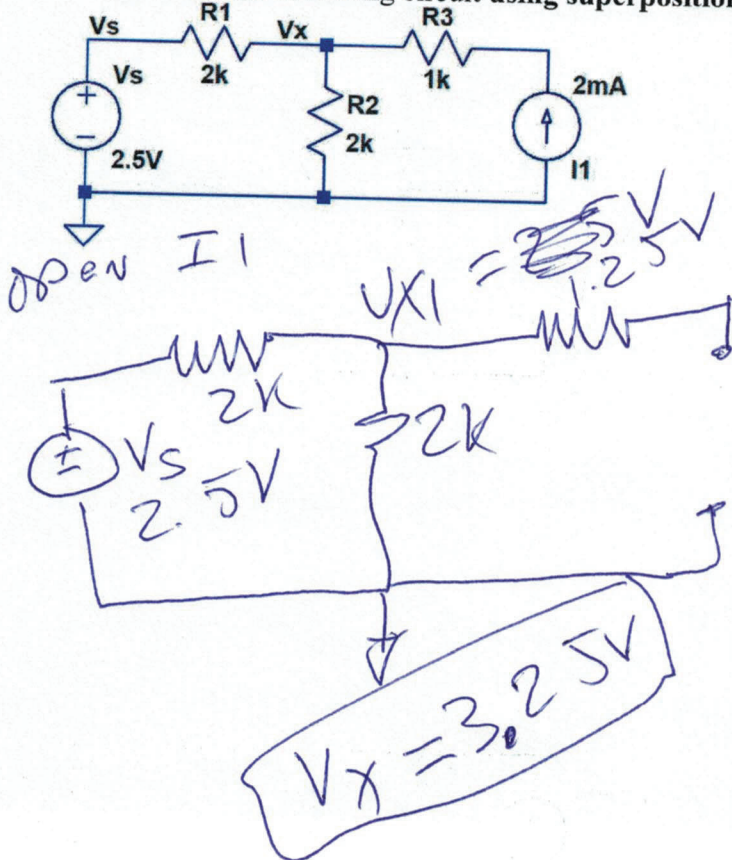2. Find  $V_x$  in the following circuit using superposition. (10 points)



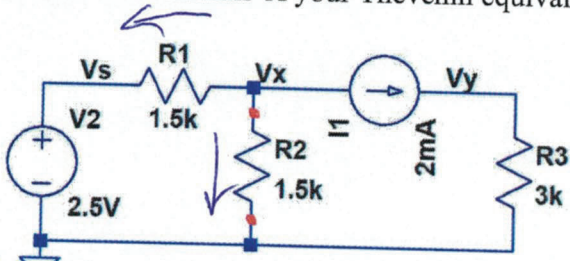3. Find the voltage  $V_x$  in the circuit seen below. Then find the Thevenin equivalent circuit, with  $R_2$  removed, at the terminals marked by dots. Show that your Thevenin circuit is correct by comparing the value you calculated for  $V_x$  to the one you get when you put  $R_2$  across the terminals of your Thevenin equivalent. (20 points)




$$2\text{mA} + \frac{V_x}{1.5\text{k}} + \frac{V_x - 2.5}{1.5\text{k}} = 0$$

$$3 + V_x + V_x - 2.5 = 0$$


$$2V_x = -0.5$$

$$V_x = -\frac{1}{4}\text{V}$$

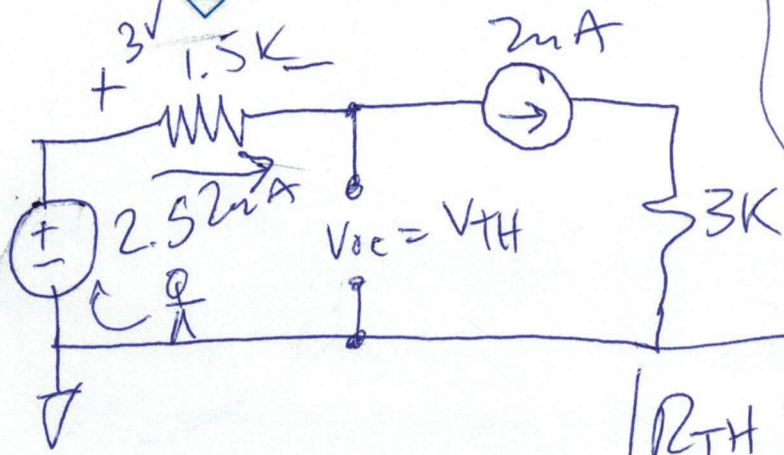

$$R_{TH} = 1.5\text{k}$$
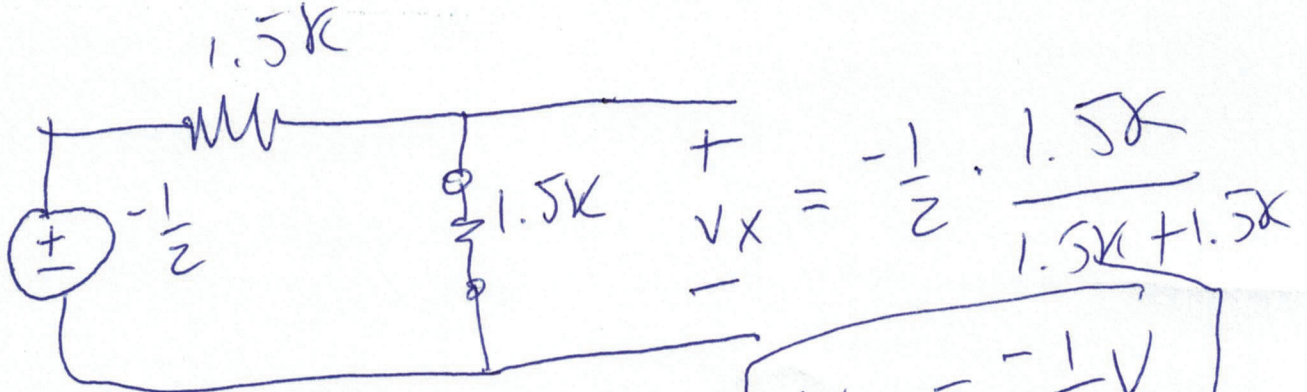
$$2.5 - 3 = V_{oc} = V_{th} = -\frac{1}{2}\text{V}$$




$$V_x = -\frac{1}{4}\text{V}$$

YAY!  
I ROCK!

5)



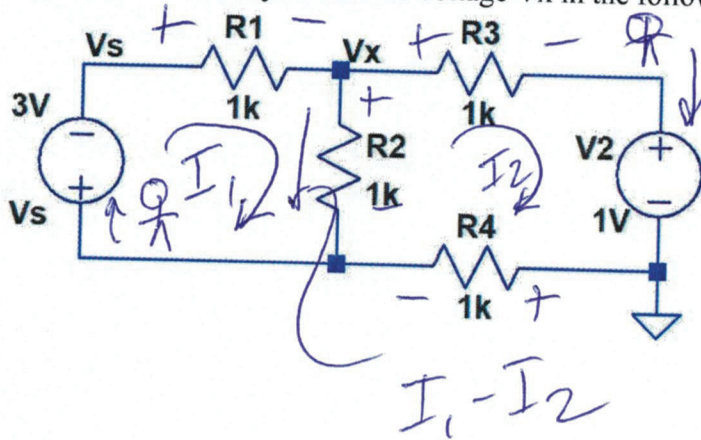4. Using mesh analysis find the voltage  $V_x$  in the following circuit. (20 points)



$$-3 - 1kI_1 - 1k(I_1 - I_2) = 0$$

$$-1 - 1kI_2 + 1k(I_1 - I_2) - 1kI_2 = 0$$

$$1kI_1 - 1 - 3kI_2 = 0 \rightarrow I_2 = \frac{1}{3} \mu A$$

$$\rightarrow 3 = -2kI_1 + 1kI_2$$

$$1.5 \mu A = -I_1 + \frac{I_2}{2}$$


$$I_1 = \frac{I_2}{2} - 1.5 \mu A$$

$$I_1 = \frac{1}{4} \mu A - 1.5 \mu A$$

$$I_1 = -1.25 \mu A$$

0)

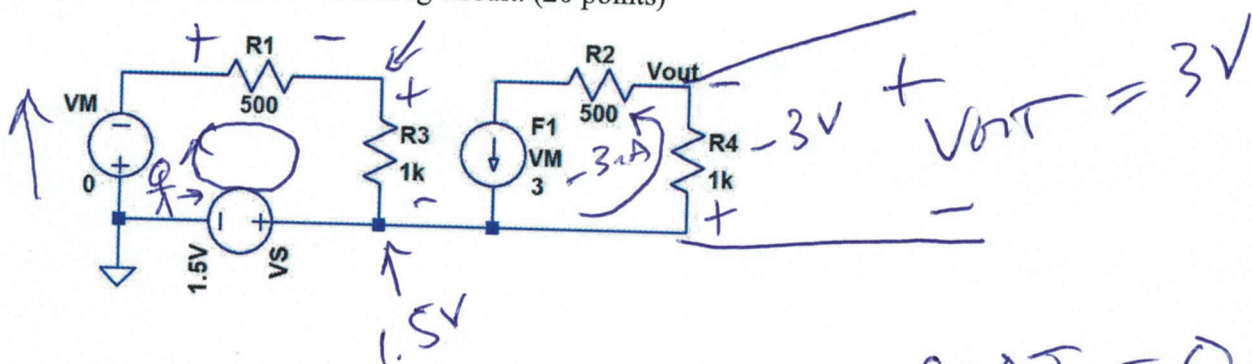5. Find  $V_{out}$  in the following circuit. (20 points)




$$1.5V + 1kI + 500I = 0$$

$$I = \frac{-1.5}{1.5k} = -1mA$$

→

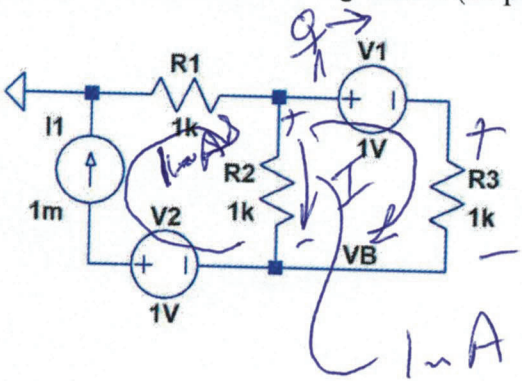
6. Find  $V_B$  in the following circuit. (20 points)



$$-1V - 1KI + 1K(1mA - I) = 0$$

$$-1 + 1 - KI - KI = 0$$

$$I = 0$$

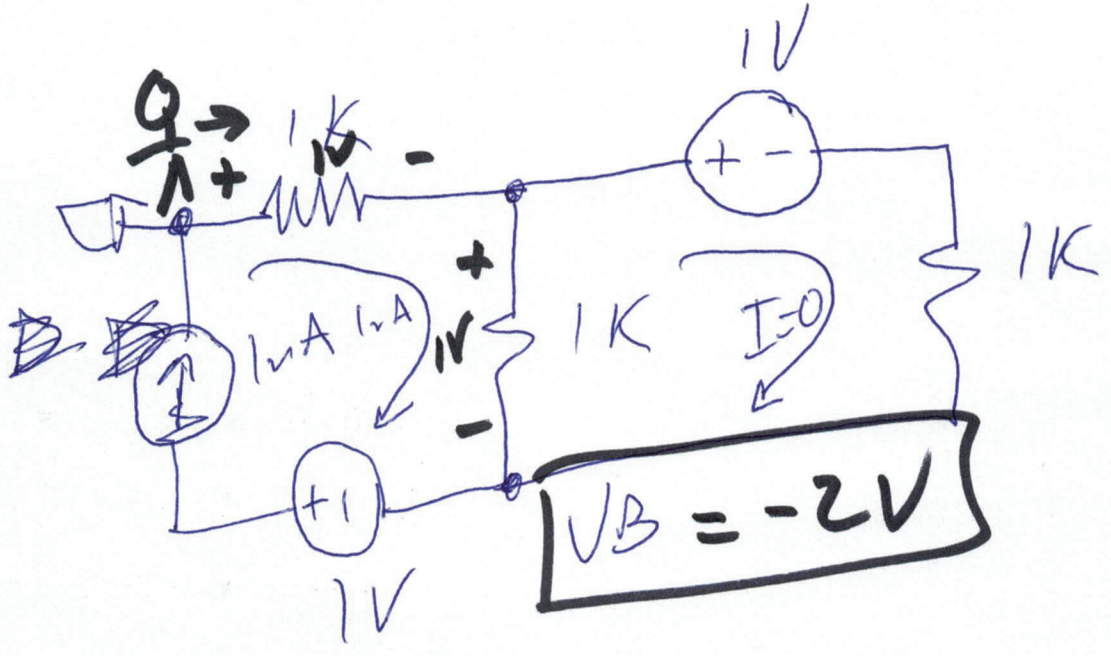

b)