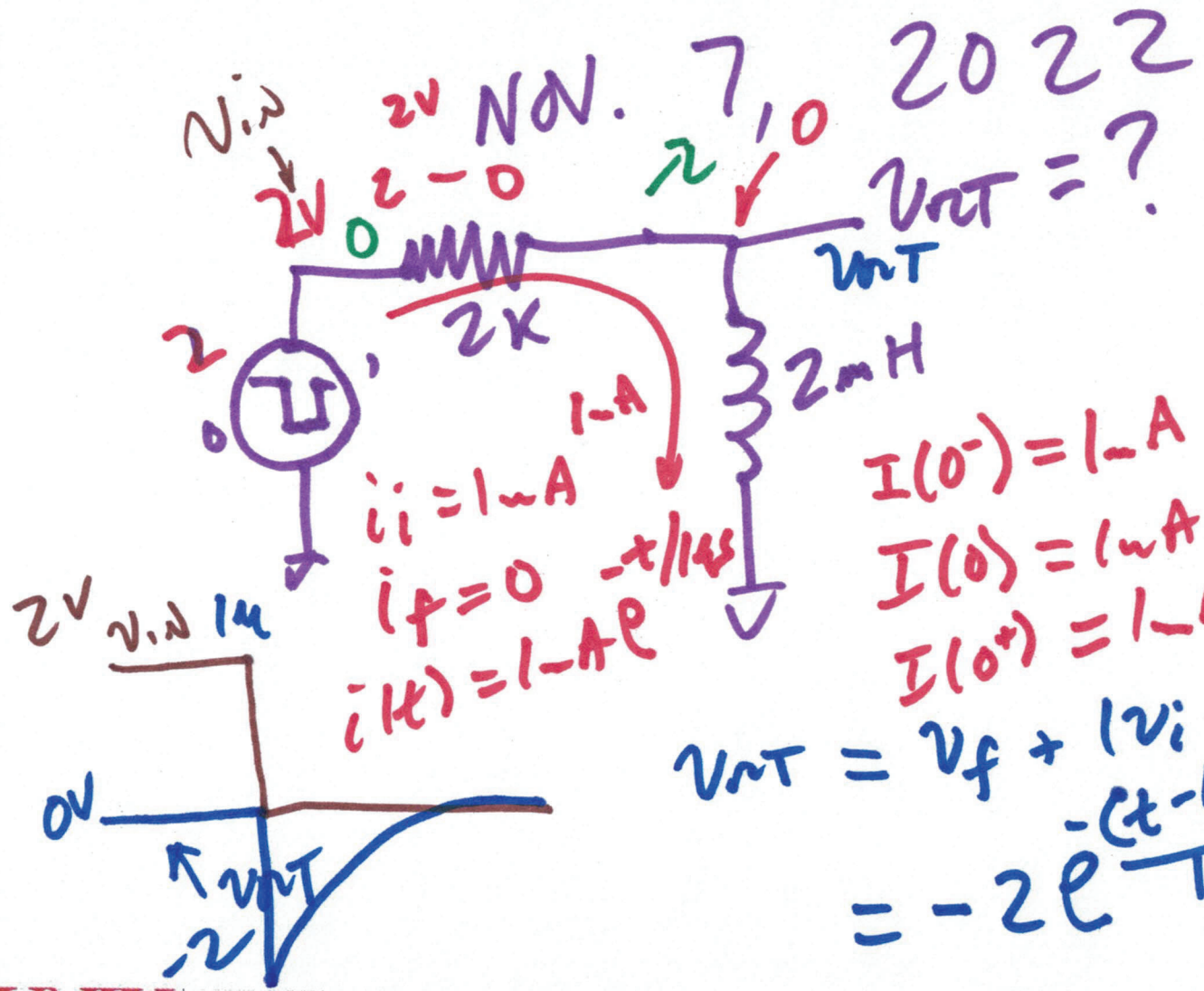


EE 220 CIRCUITS I

Lecture 19

$$\frac{-A}{B} = -\frac{A}{B} = \frac{A}{-B}$$



$$i = ?$$

$$\frac{L}{R} = \frac{2\text{mH} \cdot 10^{-3}}{2\text{k} \cdot 10^{-3}} = 145$$

$$I(0^-) = 1\text{mA}$$



$$I(0) = 1\text{mA}$$

$$I(0^+) = 1\text{mA}$$


$$v_{out} = v_f + (v_i - v_f) e^{-\frac{(t-145)}{145}}$$

$$= -2 e^{-\frac{(t-145)}{145}}$$

$$t \geq 145$$

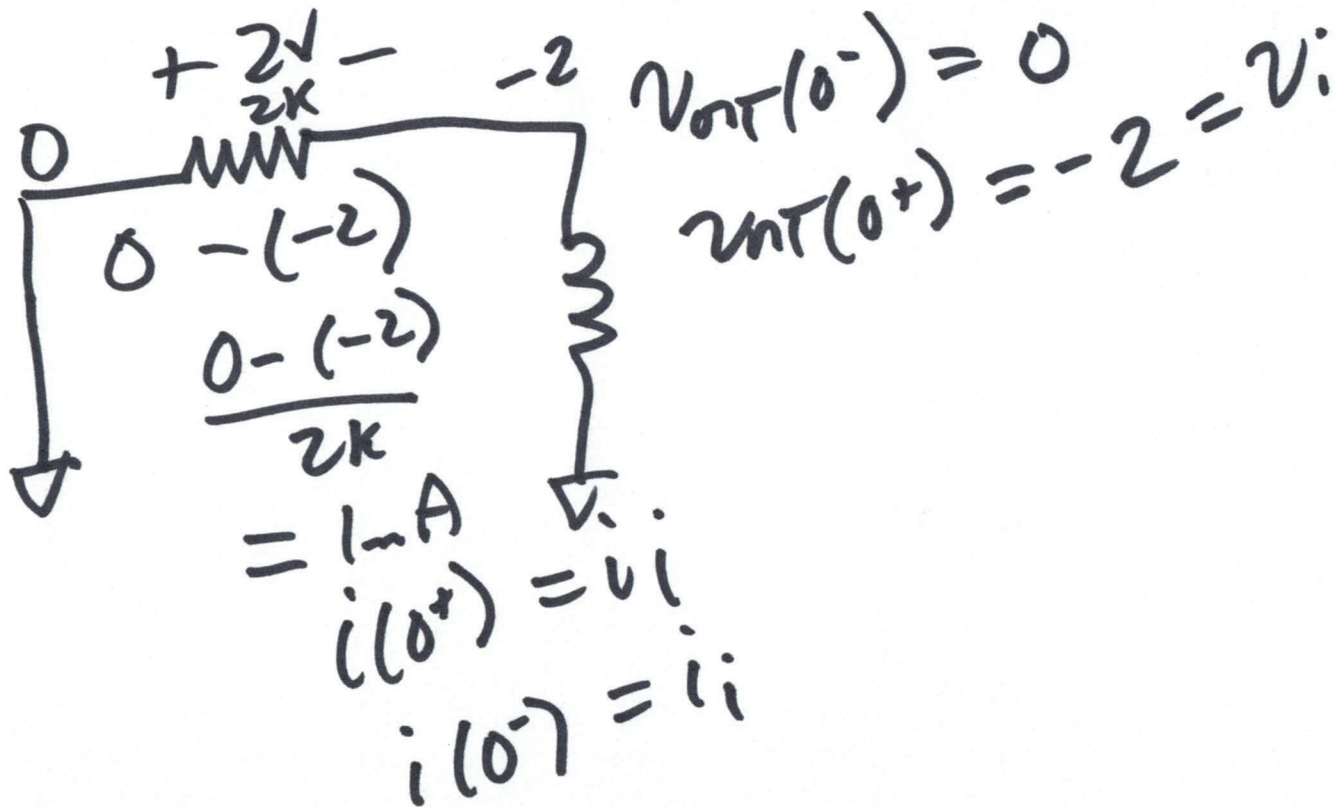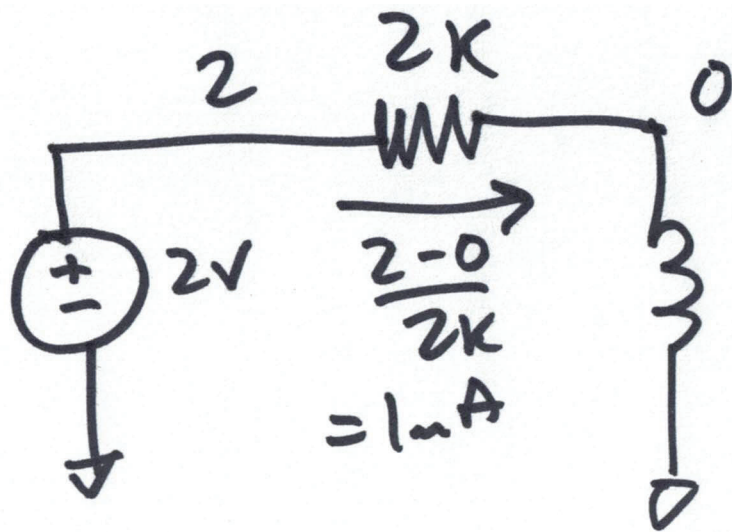

2)

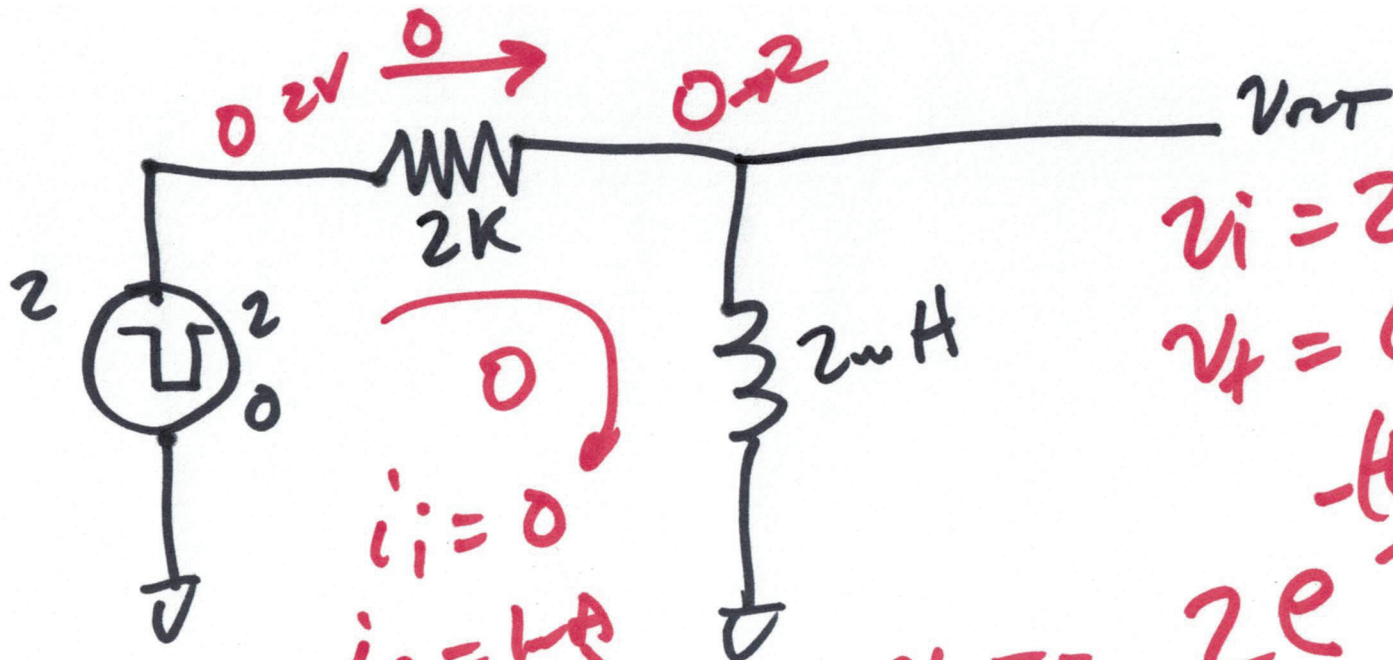

$i_i = 0$
 $i_f = 1\mu A$
 $(t-t_{ST})/1\mu$

$v_i = 2V$

$v_f = 0$

$- \frac{(t-t_{ST})}{1\mu}$

$v_{out} = 2e$

$i(t) = 1\mu A (1 - e^{-\frac{(t-t_{ST})}{1\mu}})$

$2 - 2e$

$2k$

$= 1\mu A - 1\mu A e^{-\frac{(t-t_{ST})}{1\mu}}$

3)

Energy, \mathcal{E}


$$\mathcal{E} = \int_{t_1}^{t_2} v(t) \cdot i(t) \cdot dt$$

$p(t) =$ instantaneous power, Watts
 $= v(t) \cdot i(t)$

inductor

$$v = L \cdot \frac{di}{dt} \left\{ \mathcal{E} = \int_0^t L \cdot \frac{di(t)}{dt} \cdot i(t) \cdot dt \right.$$
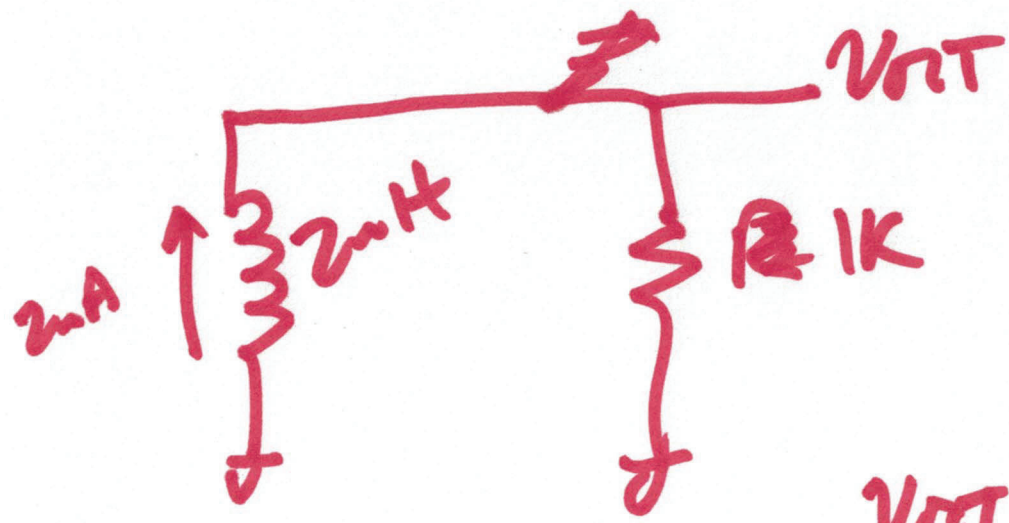
$$\boxed{\mathcal{E} = \frac{1}{2} L I^2} = L \int_0^I i(t) \cdot di(t)$$



$$V_i = 2V$$

$$V_f = 0$$

$$V_{out} = V_f + (V_i - V_f) e^{-t/4R}$$

$$\begin{aligned}
 E &= \frac{1}{2} L I^2 \\
 &= \frac{1}{2} \cdot 2mH (2mA)^2 \\
 &= 4 \cdot 10^{-3} \cdot 10^{-6} \\
 &= 4 nJ
 \end{aligned}$$

$$= 2e$$

10n

Capacitor

$$i = C \frac{dv}{dt} \rightarrow i(t) = C \frac{dv(t)}{dt}$$

$$\mathcal{E} = \int_{t_1}^{t_2} \underbrace{v(t) \cdot i(t)}_{p(t)} \cdot dt$$

$$= \int_{v_1}^{v_2} v(t) \cdot C \cdot \frac{dv(t)}{dt} \cdot dt$$
$$= \frac{1}{2} C v^2 \Big|_{v_1}^{v_2}$$

$$\mathcal{E} = \frac{1}{2} C (V_2 - V_1)^2 = \frac{1}{2} C \Delta V^2$$

$$\mathcal{E} = \frac{1}{2} C V^2$$

$$\mathcal{E} = \frac{1}{2} (10^3 \cdot 10^{-12} \cdot 10^{-9}) \cdot 5^2$$

$$\mathcal{E} = 12.5 \text{ nJ}$$