
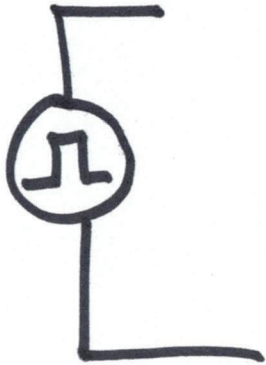


$$V_{PP} = 5V$$

EE 220 CIRCUITS I

11/9/2022 Lecture 20

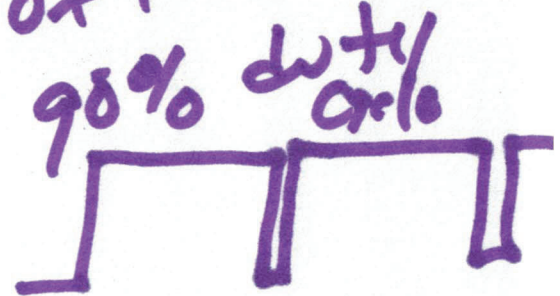

$$f = 10\text{MHz}$$


duty cycle

BNC connector

$$f = \frac{1}{T} = 10\text{MHz} = 10 \cdot 10^6 = 10^7$$


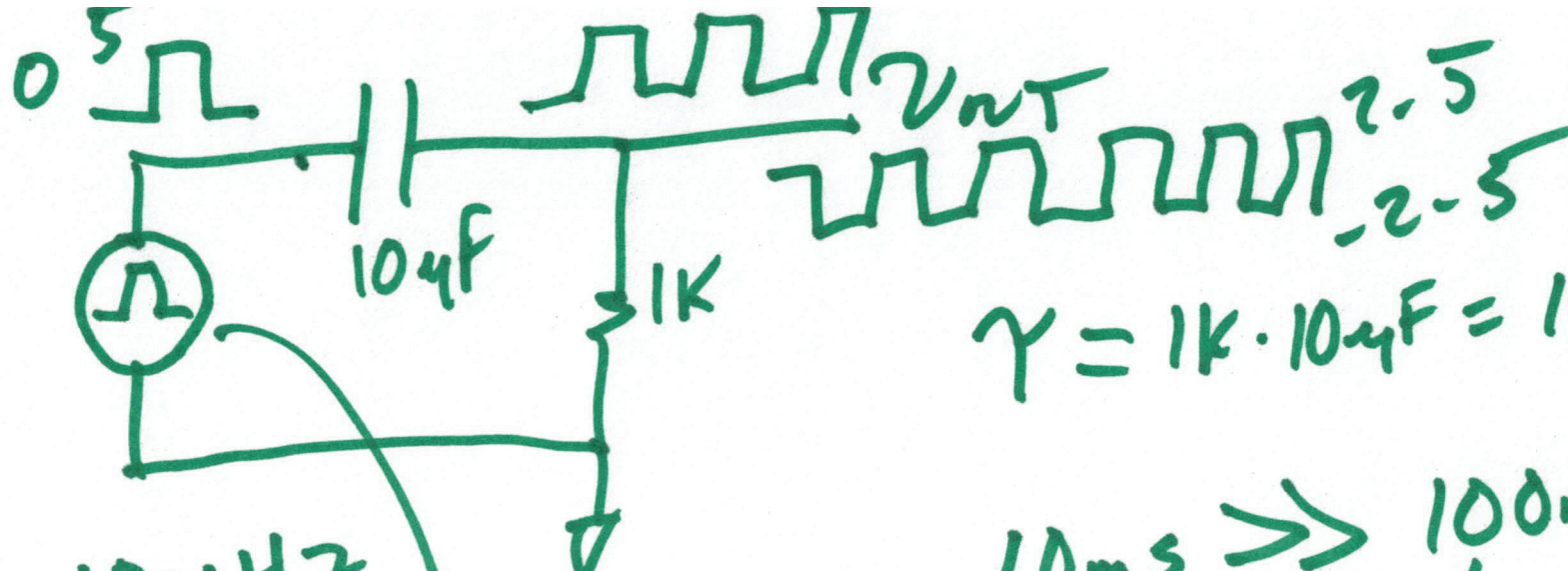
$$T = \frac{1}{10^7} = 0.1 \times 10^{-6} = 100\text{ns} = 0.1\mu\text{s}$$







$$\tau = 1K \cdot 104F = 10ms$$

$$10ms \gg 100ns$$

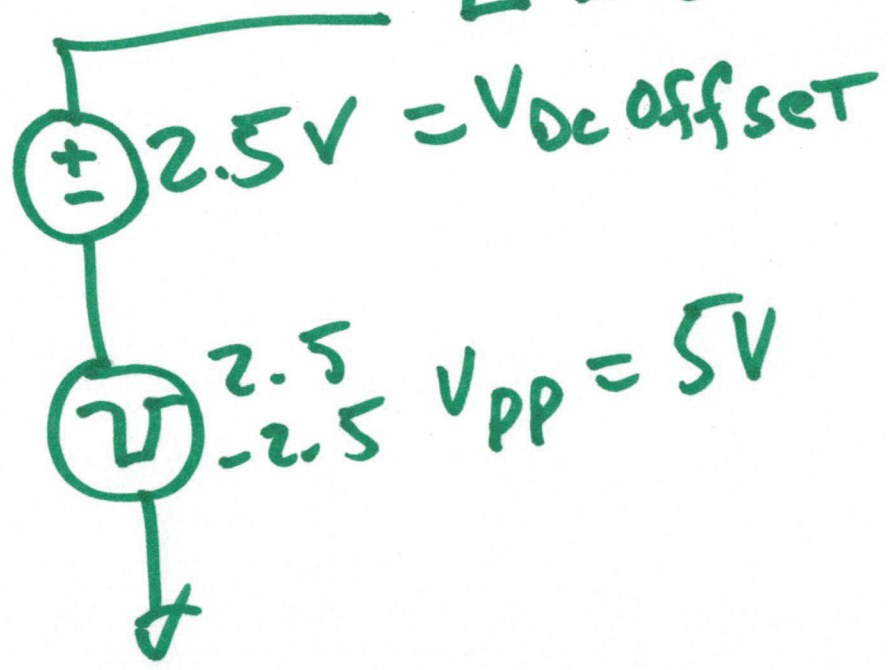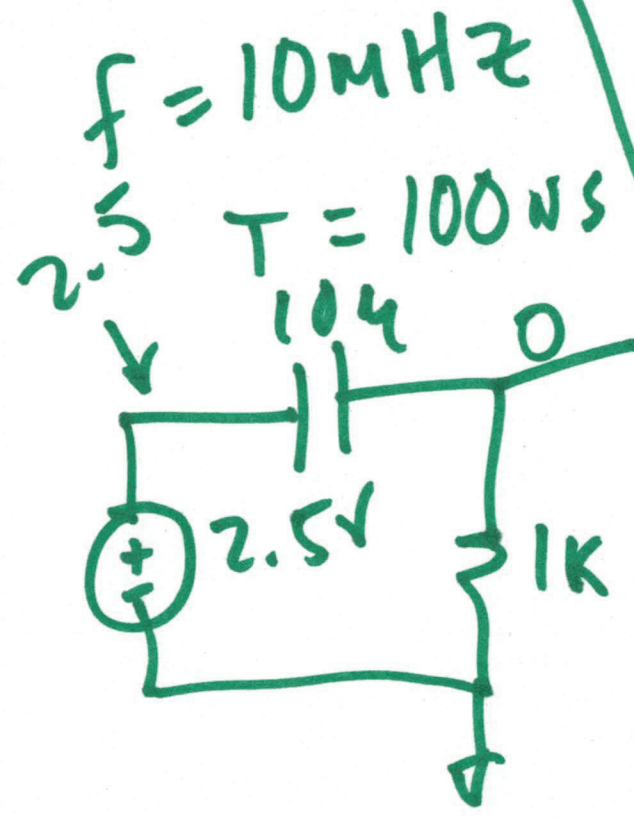


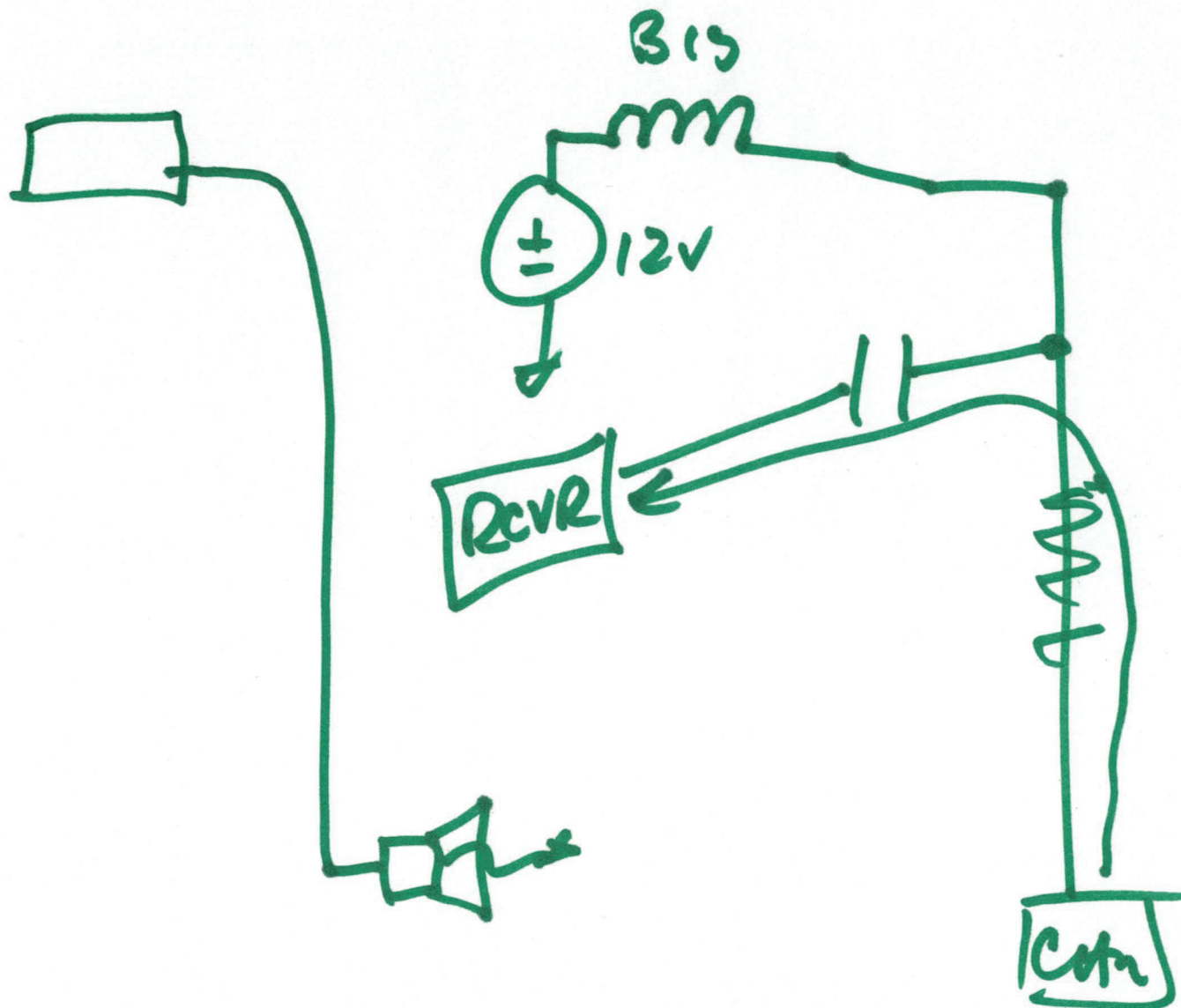


3)

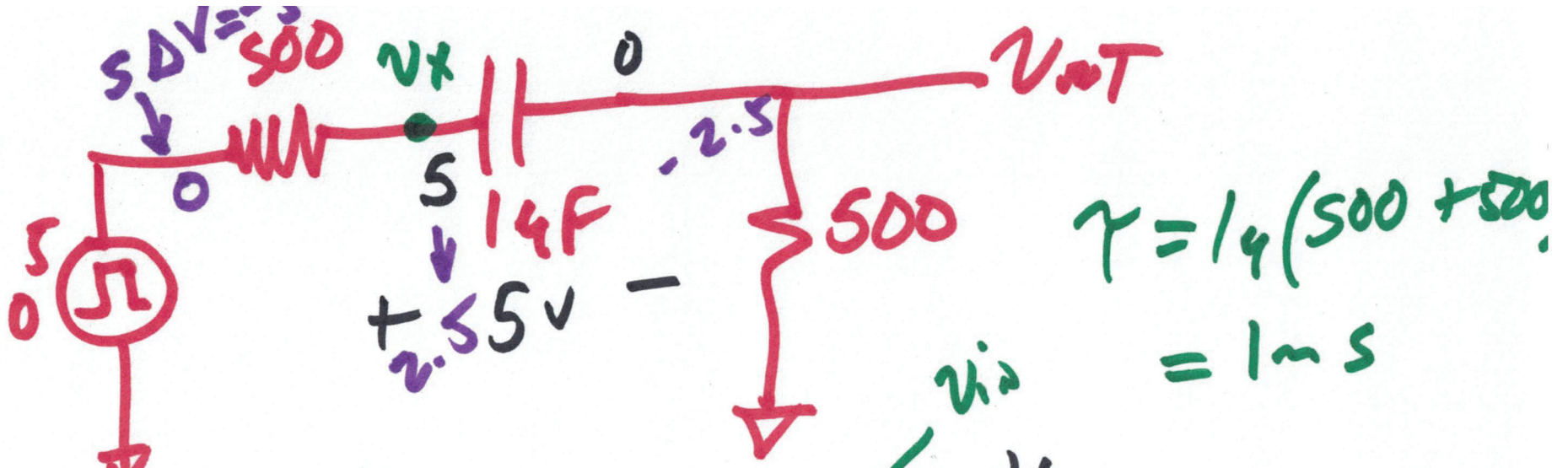


$$\tau = 14(500 + 500) = 1ms$$

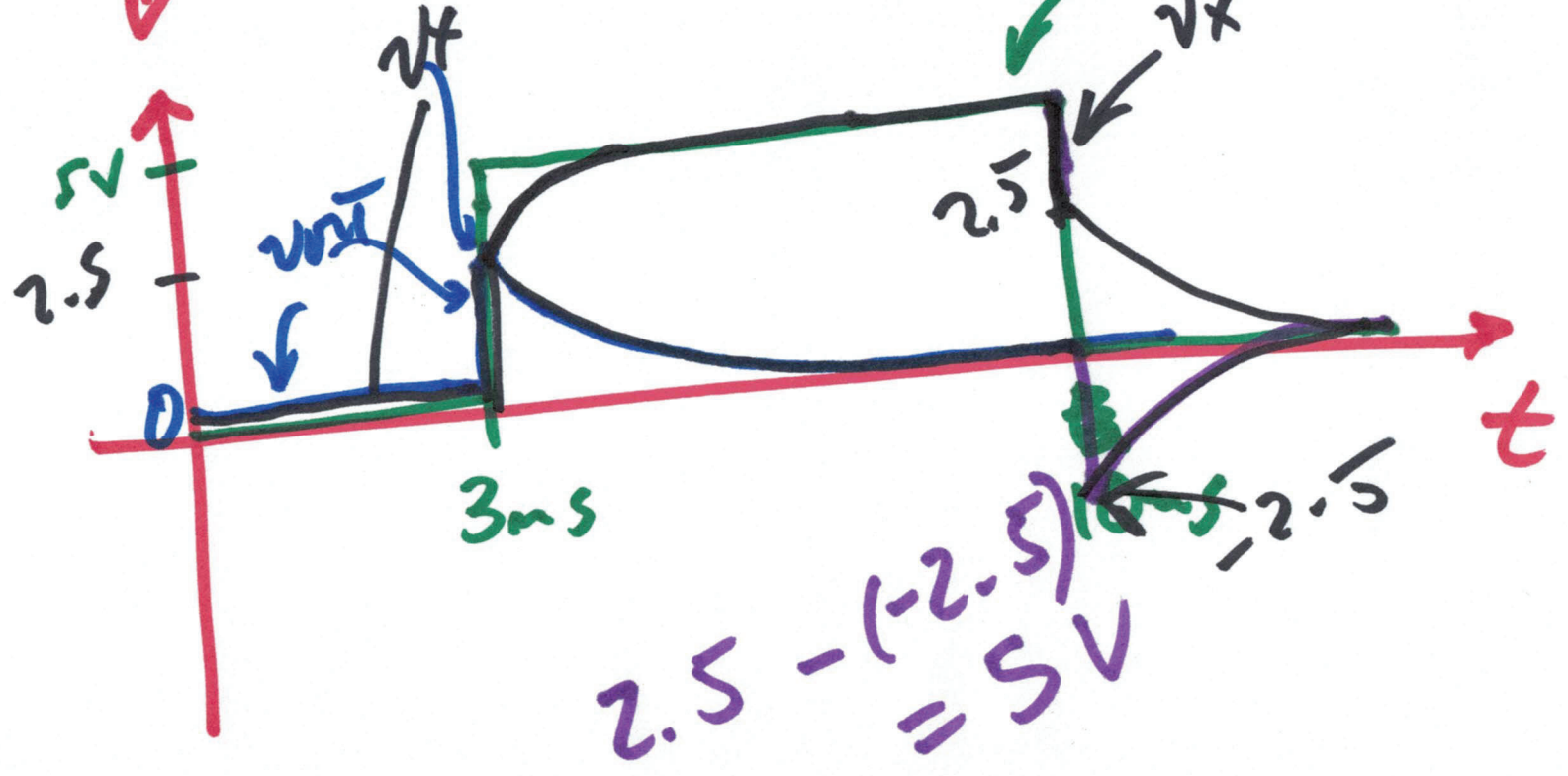

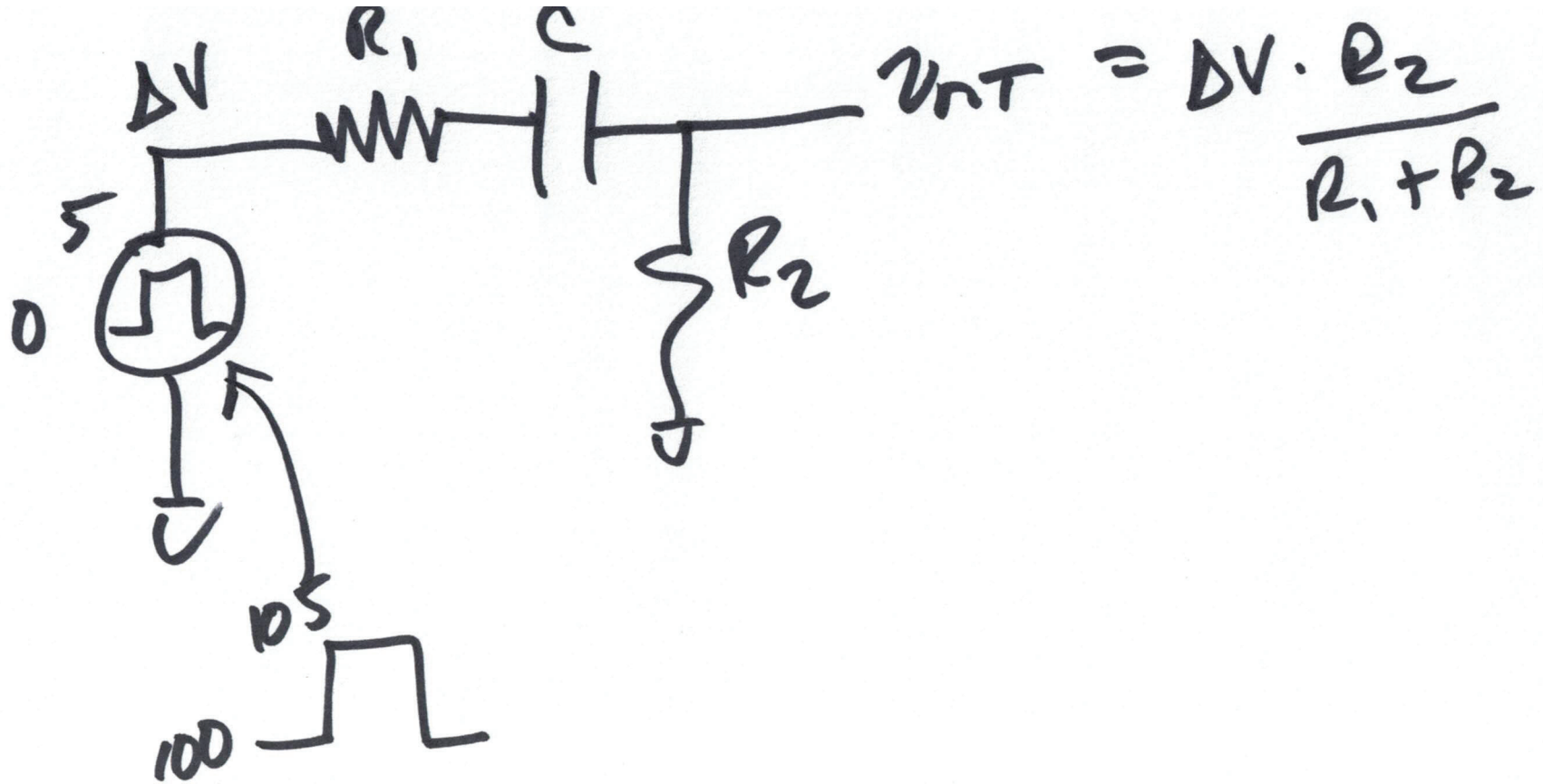

Integrations
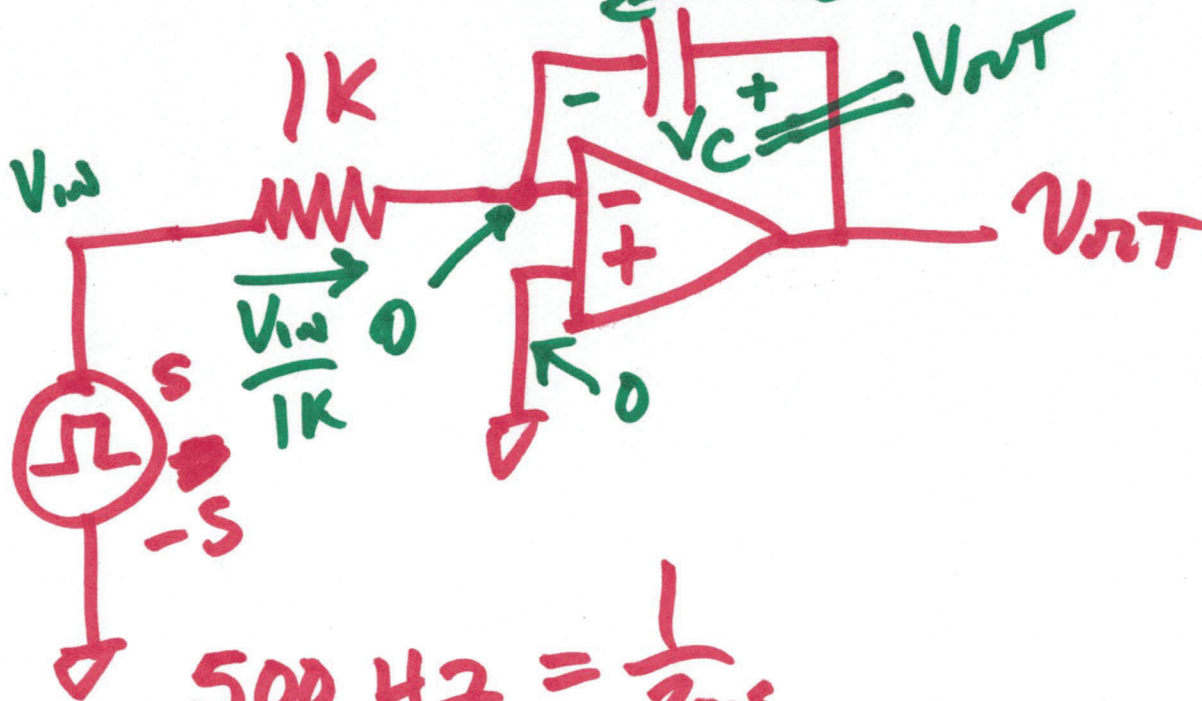
$$1\mu F \tau_c = C \frac{dV_{out}}{dt}$$



$$500 \text{ Hz} = \frac{1}{2\mu\text{s}}$$

$$T = 2\mu\text{s}$$



$$\frac{V_{in}}{R} + C \frac{dV_{out}}{dt} = 0$$

$$\frac{dV_{out}}{dt} = -\frac{1}{RC} V_{in}$$

$$dV_{out} = -\frac{1}{RC} V_{in} \cdot dt$$

$$V_{out} = -\frac{1}{RC} \int_{t_1}^{t_2} V_{in} \cdot dt$$

$$V_{out} = -\frac{1}{1\mu s} \int_0^{1\mu s} -5 \cdot dt = \frac{5t}{1\mu s} \Big|_0^{1\mu s}$$

