

EE 220 CIRCUITS I

NOV. 16, 2022



Lecture 21


AC - alternating current



60 Hz \rightarrow 16.67 ms


period
 $T = \frac{1}{f}$

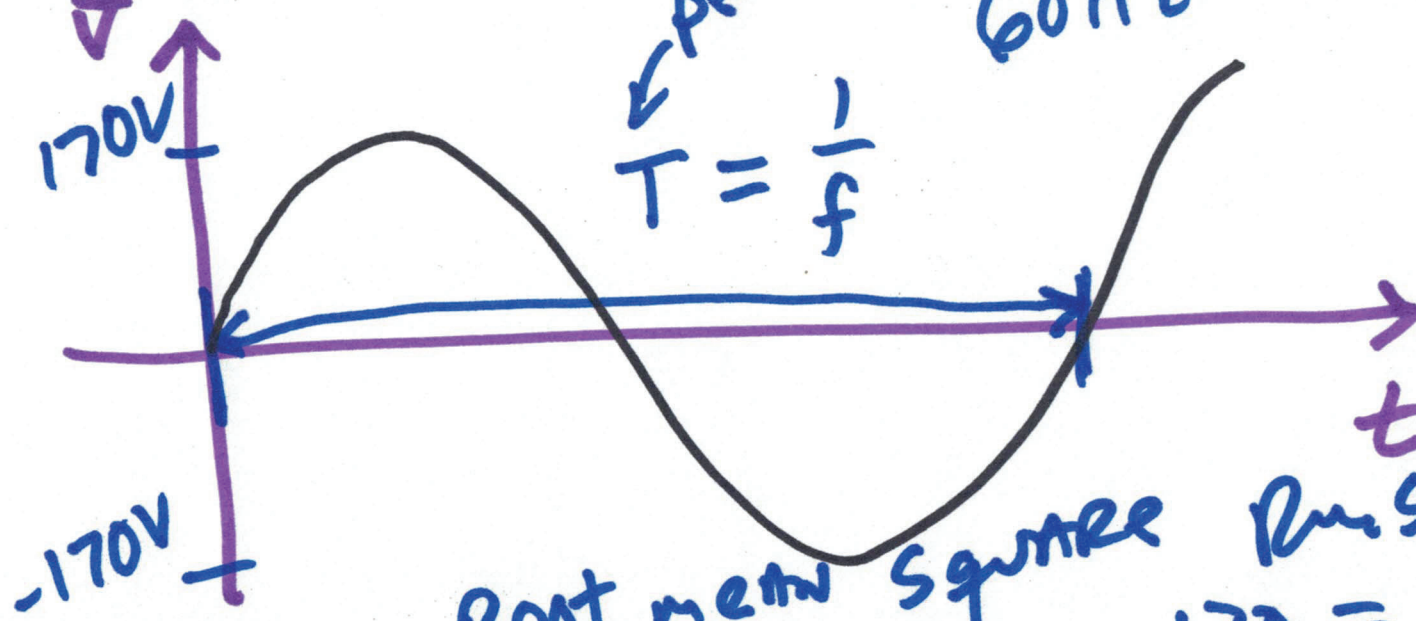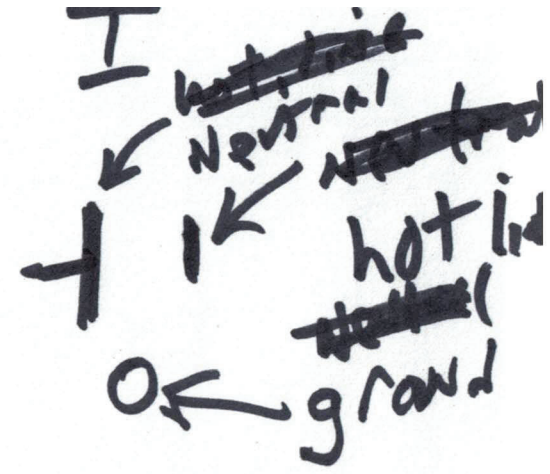
Root mean square rms
 $170 = \frac{170}{\sqrt{2}}$



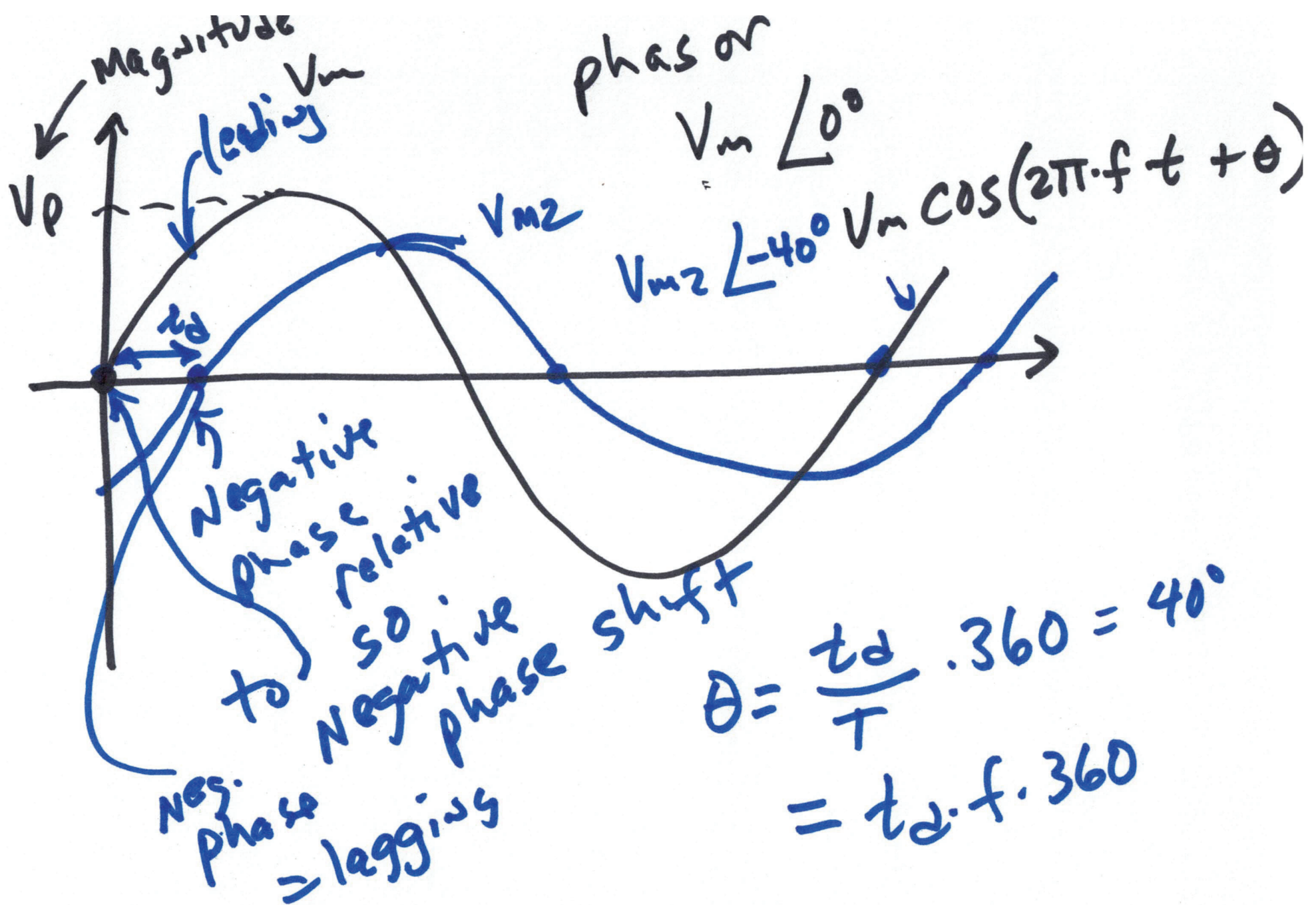

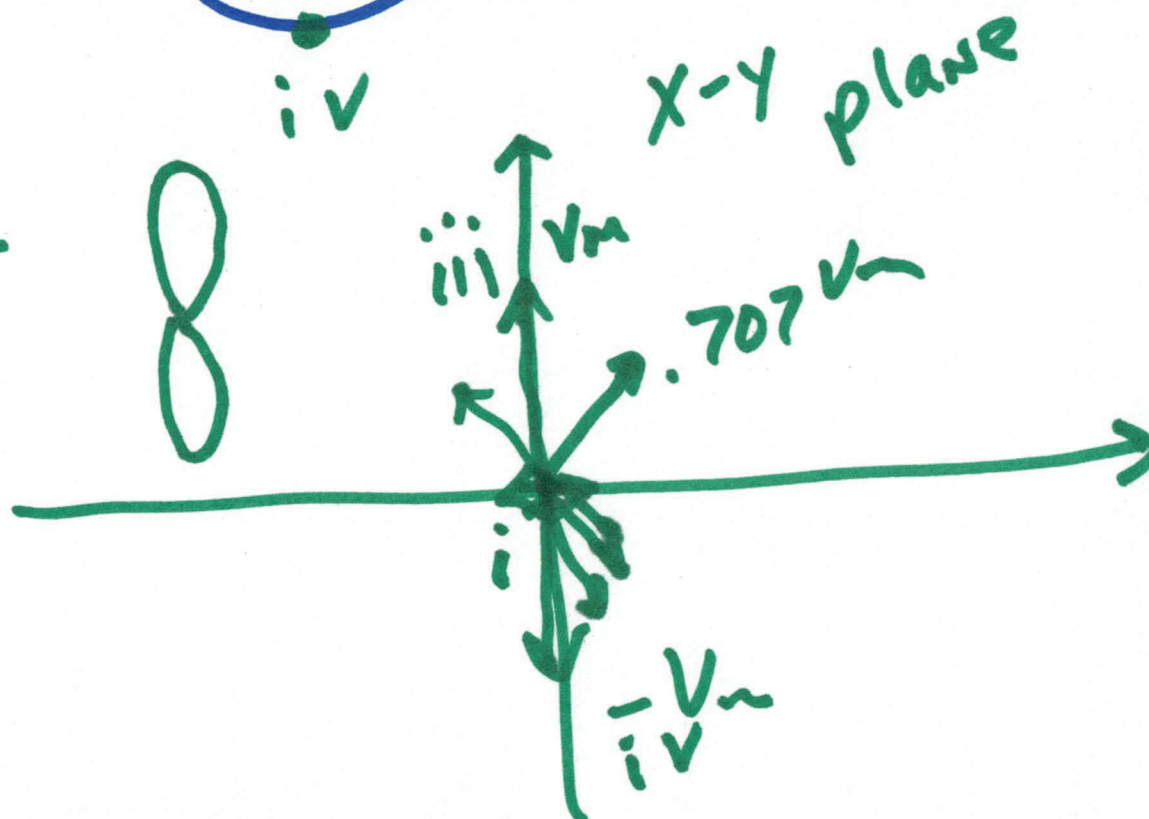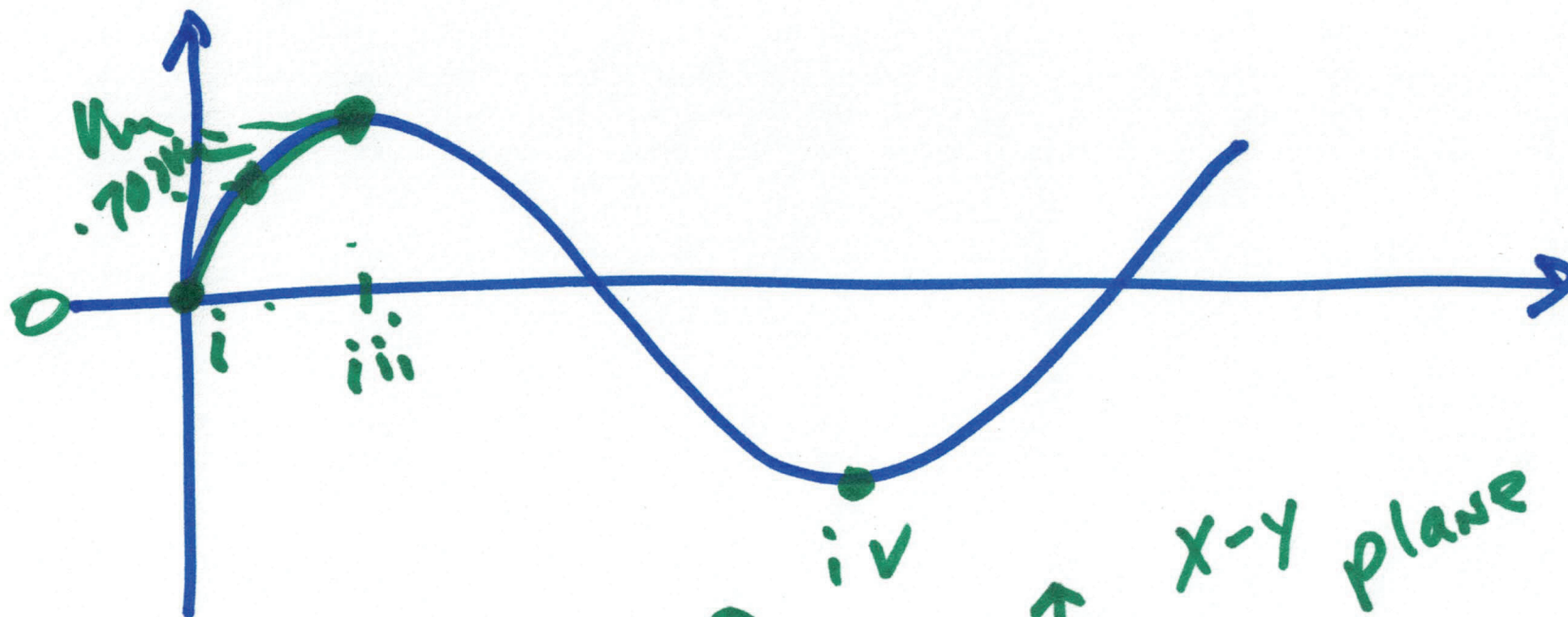

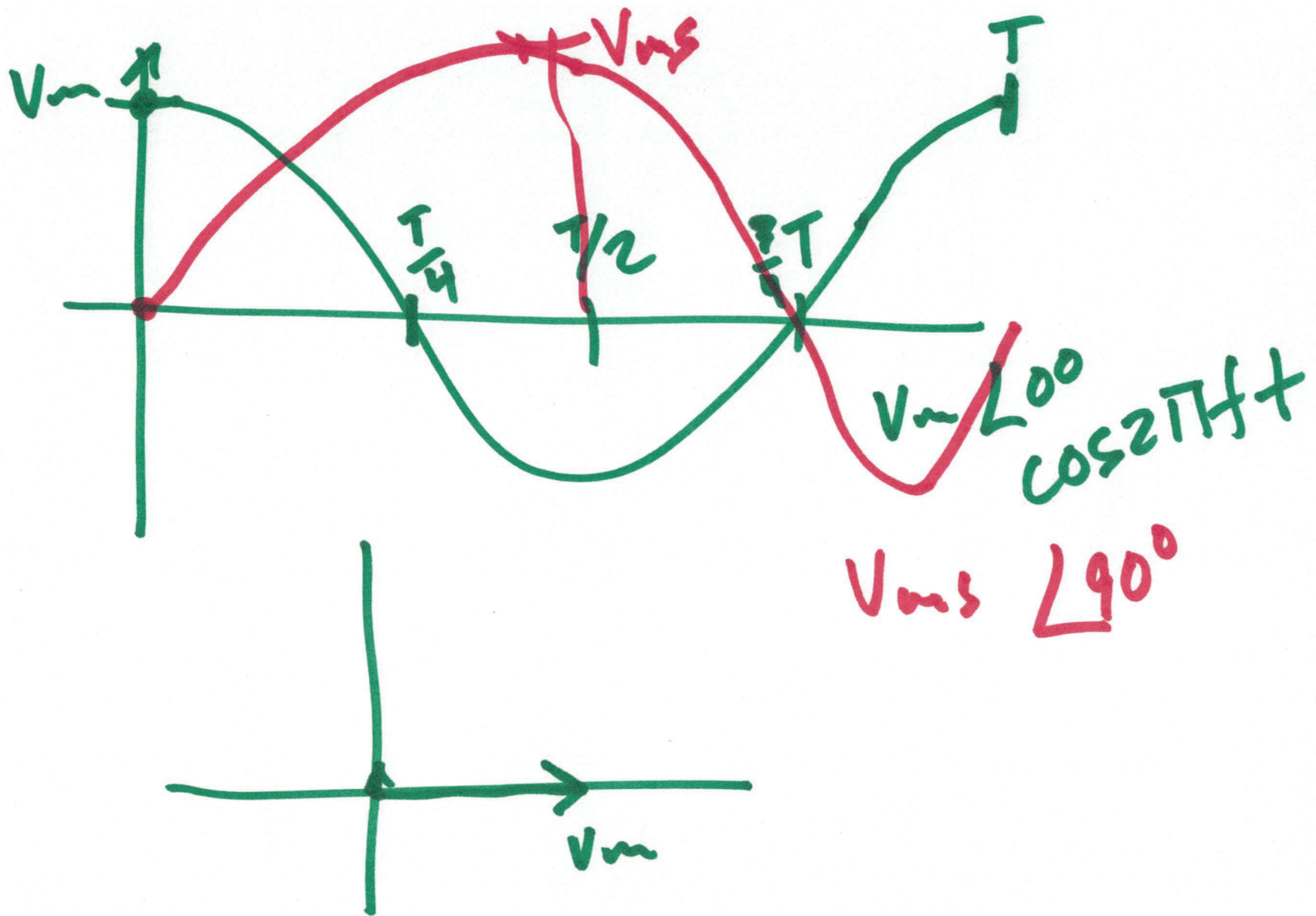

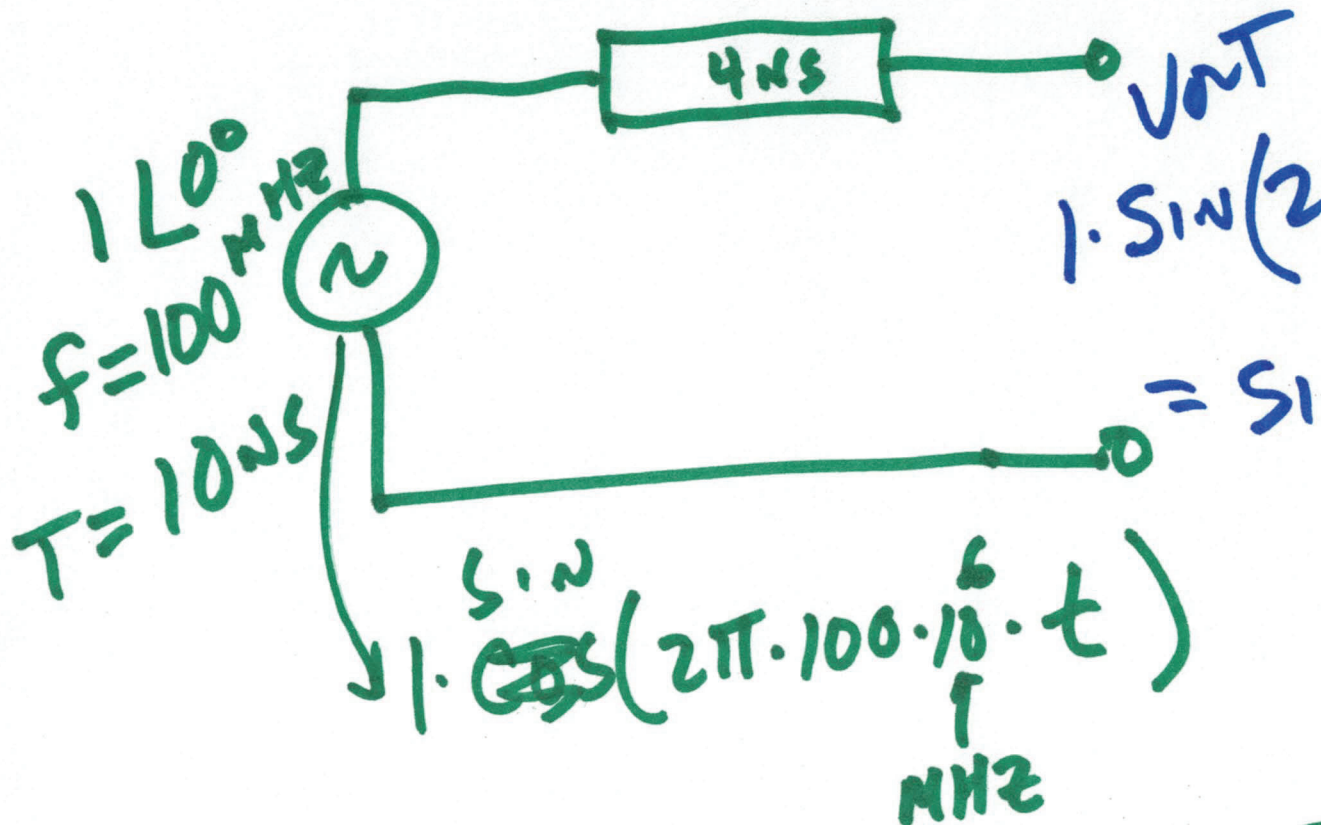


$$1 \cdot \sin(2\pi \cdot 100 \cdot 10^6 (t - 4 \text{ ns}))$$

$$= \sin(2\pi \cdot 100 \cdot 10^6 t - 2\pi \cdot 100 \cdot 10^6 \cdot 4 \text{ ns})$$

$$\theta =$$

$$2\pi \cdot \underbrace{100 \cdot 10^6}_f \cdot t_d$$

$$= 360 \cdot \frac{t_d}{T}$$

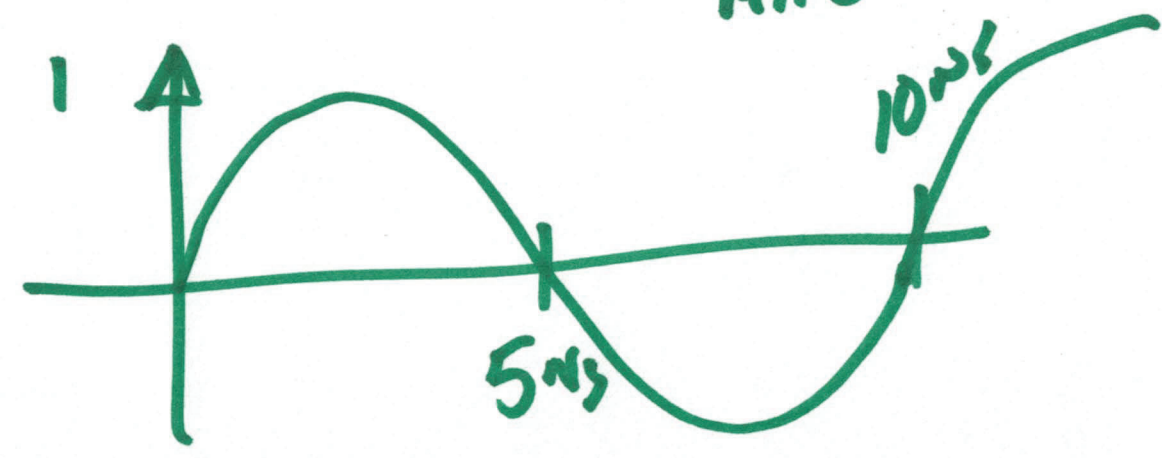

$$\theta = 360 \cdot \frac{4 \text{ ns}}{10 \text{ ns}} = 144^\circ$$

$$2\pi \cdot \frac{4}{10 \text{ ns}} \rightarrow \frac{2\pi}{360} \text{ degrees} = \text{RADIANS}$$

$$\frac{\pi}{180} \text{ degrees} = \text{RADIANS}$$

$$V_{out} = 1 \angle -144^\circ$$

Wang

$$V_{out} = 0. \cos(2\pi \cdot 100 \cdot 10^6 \cdot t) + j \sin(2\pi \cdot 100 \cdot 10^6 \cdot t - 144^\circ)$$

$$e^{j\theta} = \cos \theta + j \sin \theta$$

Euler's identity

$$\cos \theta = \frac{\text{Re}}{2}$$

$$\text{Im}\{e^{jk}\} = \sin k$$

$$\begin{aligned}
 & \sin(2\pi 100\text{MHz} \cdot t - 144^\circ) \\
 &= i \omega (e^{j(2\pi 100\text{MHz} \cdot t - 144^\circ)}) \\
 &= e^{j2\pi f \cdot t} \cdot e^{-j144^\circ} \\
 &\quad \downarrow \\
 & \quad e^{-j2\pi f \cdot t_d} \\
 & \quad e^{-j2\pi \frac{t_d}{T}}
 \end{aligned}$$

$$v = i \cdot j\omega L$$

$$i = C \frac{dv}{dt}$$

$$v = V_m \cos 2\pi f \cdot t$$

$x = \text{impedance of a CAP}$

$$i = C \cdot \frac{d}{dt} V_m \cos 2\pi f \cdot t$$

$$i \cdot x = v$$

$$i \cdot \frac{1}{j\omega C} = v$$

$$\omega = 2\pi f$$

$$i = C \cdot 2\pi f (-V_m \sin(2\pi f \cdot t))$$

$$i = C \cdot 2\pi f \cdot (+j)(+V_m) \cos 2\pi f \cdot t$$