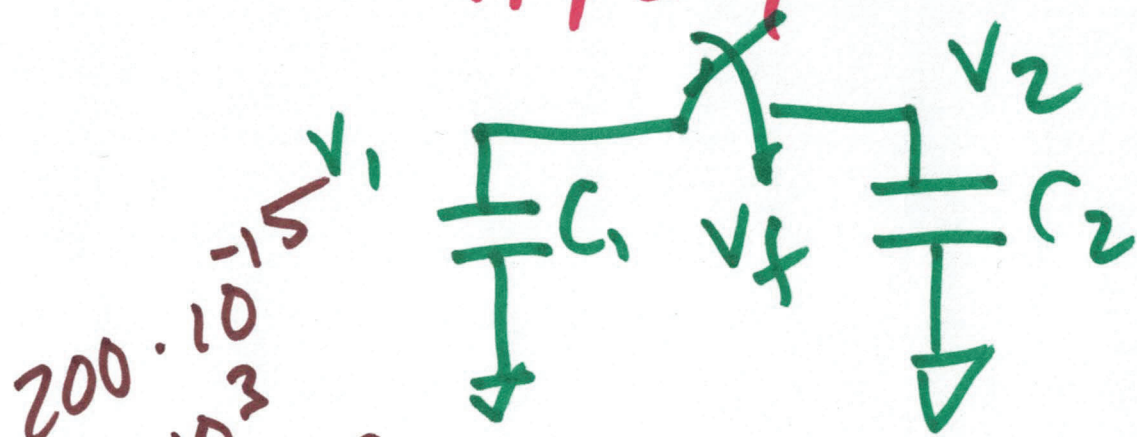


# EE 270 Circuits I

## Lecture 22

11/21/2022


$$CV = Q$$



$200 \cdot 10^{-15}$   
 $10^3$   
 $200 \cdot 10^{-12}$   
200PS  
0.2NS

$$C_1 V_1 + C_2 V_2 = (C_1 + C_2) V_f$$
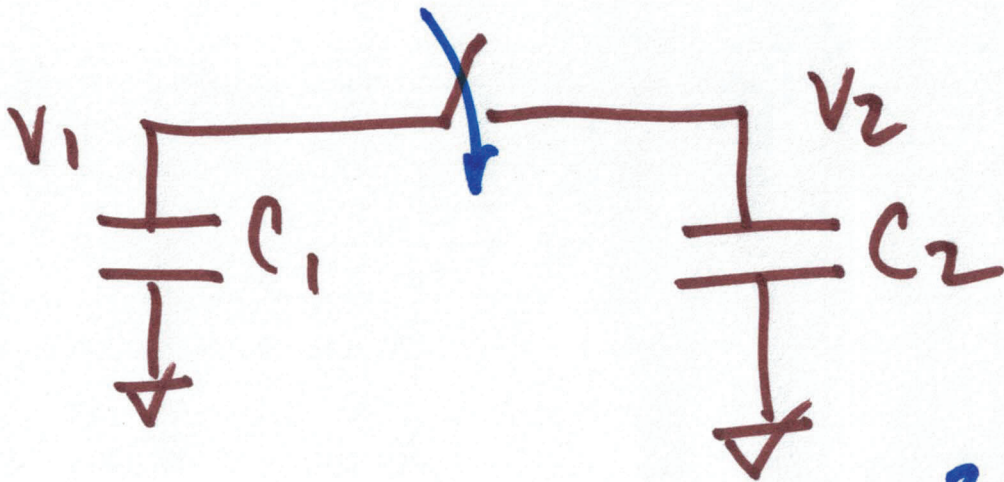
$$V_f = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$





$$\frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 = \frac{1}{2} (C_1 + C_2) V_f^2$$

$$V_f = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

$$\frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 = \frac{1}{2} (C_1 + C_2) \cdot \frac{(C_1 V_1 + C_2 V_2)^2}{(C_1 + C_2)^2}$$
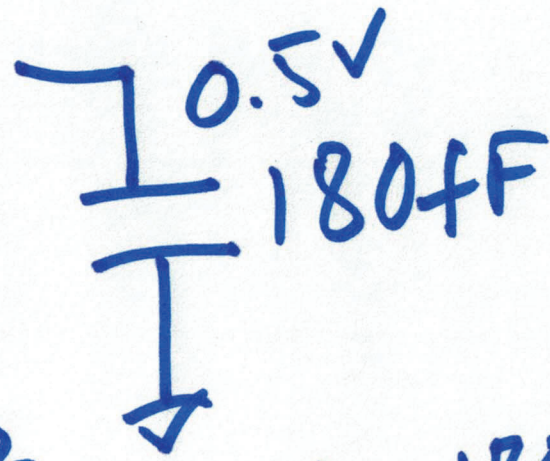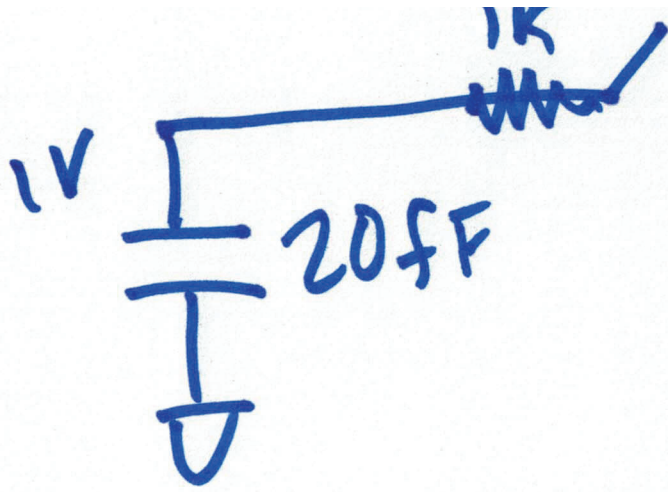
$$\stackrel{?}{=} \frac{1}{2} \frac{C_1^2 V_1^2}{C_1 + C_2} + \frac{1}{2} \frac{C_2^2 V_2^2}{C_1 + C_2}$$






$$E_{\text{before}} = \frac{1}{2} \cdot 20\text{fF} \cdot 1^2 + \frac{1}{2} \cdot 180\text{fF} \cdot (0.5)^2$$

$$E_{\text{diff}} = 32.5 - 30.25 = 2.25\text{fJ}$$

$$V_f = \frac{20\text{fF} \cdot 1 + 180\text{fF} \cdot \frac{1}{2}}{20\text{f} + 180\text{f}}$$

$$V_f = \frac{110}{200} = .55\text{V}$$
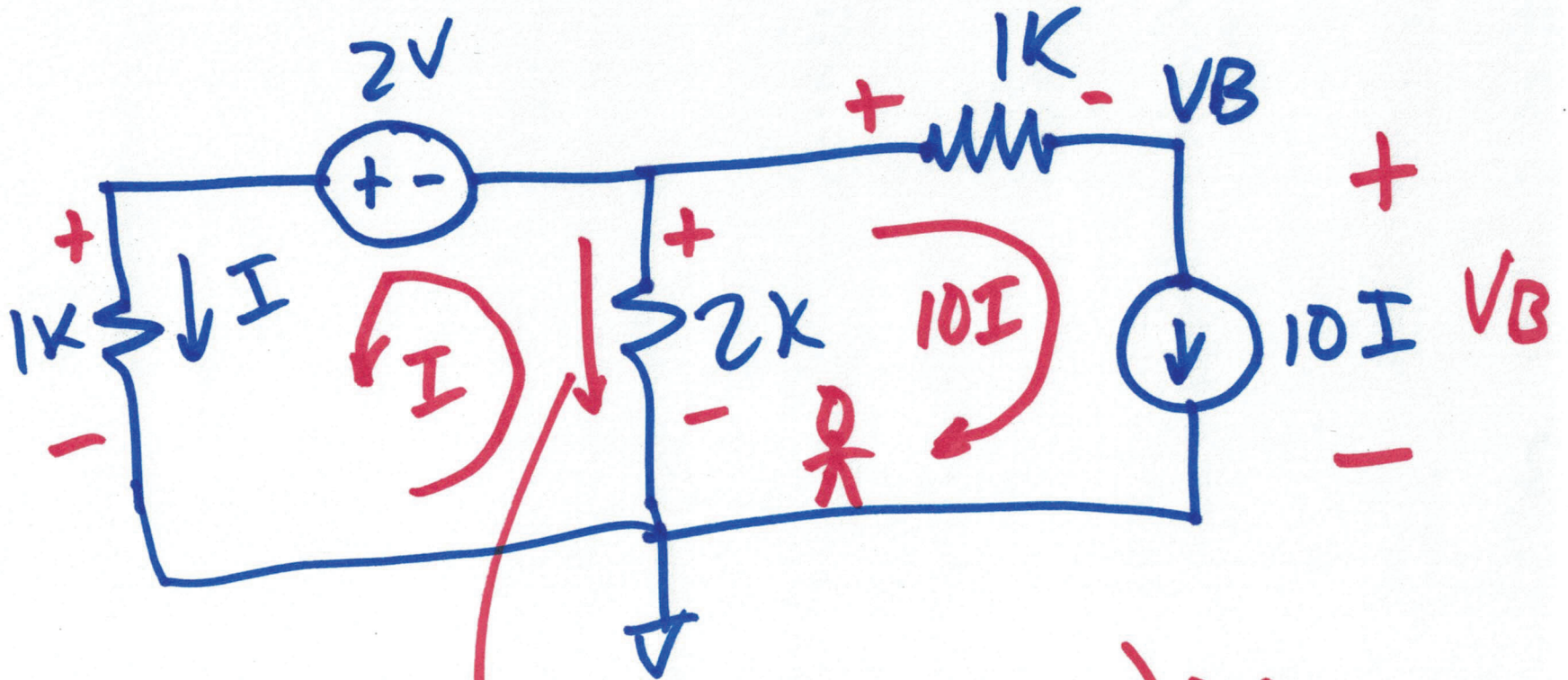
$$E_{\text{final}} = \frac{1}{2} (200\text{fF}) \cdot .55^2 = 30.25\text{fJ}$$




$$(-I - 10I)2k$$

$$V_B + 10I \cdot 1k - 2k(-I - 10I) = 0$$

$$2k(-I - 10I) + 2 - 1kI = 0$$



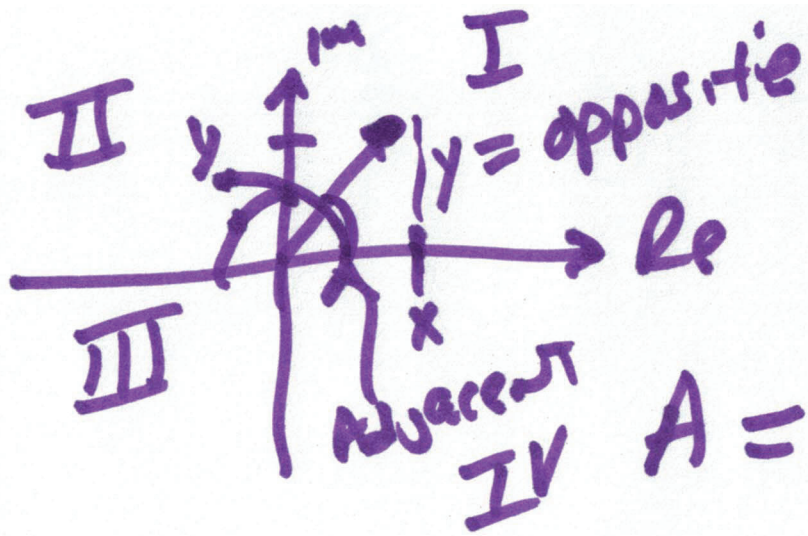

$x + jy = A \angle \theta$   
 rect.      Polar

$$A = |x + jy| = \sqrt{x^2 + y^2}$$

$$\angle \theta = \angle x + jy = \tan^{-1} \frac{y}{x}$$

$$\begin{aligned}
 a_1 + jb_1 + a_2 + jb_2 \\
 = (a_1 + a_2) + j(b_1 + b_2)
 \end{aligned}$$

$$A_1 \cdot A_2 \angle \theta_1 + \theta_2 = A_1 \angle \theta_1 + A_2 \angle \theta_2$$

$$\begin{aligned}
 A_1 \cos \theta_1 + j A_1 \sin \theta_1 + \\
 A_2 \cos \theta_2 + j A_2 \sin \theta_2
 \end{aligned}$$

$$\frac{x_1 + jy_1}{x_2 + jy_2} = \frac{\sqrt{x_1^2 + y_1^2} \angle \tan^{-1} \frac{y_1}{x_1}}{\sqrt{x_2^2 + y_2^2} \angle \tan^{-1} \frac{y_2}{x_2}}$$

$$= \frac{\sqrt{x_1^2 + y_1^2}}{\sqrt{x_2^2 + y_2^2}} \angle \tan^{-1} \frac{y_1}{x_1} - \tan^{-1} \frac{y_2}{x_2}$$

6)



$$\frac{1}{x + jy} \cdot \underbrace{\frac{x - jy}{x - jy}}_{=1} = \frac{x + j(-y)}{x^2 + y^2}$$

$$= \frac{x}{x^2 + y^2} + j \frac{-y}{x^2 + y^2}$$

$$\left| \frac{1}{x + jy} \right| = \sqrt{\frac{x^2}{(x^2 + y^2)^2} + \frac{(-y)^2}{(x^2 + y^2)^2}}$$

$$\frac{1}{\sqrt{x^2 + y^2}} = \sqrt{\frac{\cancel{x^2 + y^2}}{(x^2 + y^2)^2}}$$


$$\angle = \tan^{-1} \frac{\frac{-y}{x^2+y^2}}{x}$$

$$= \tan^{-1} -\frac{y}{x} = -\tan^{-1} \frac{y}{x}$$

$$\left| \frac{1}{x+iy} \right| = \frac{1}{\sqrt{x^2+y^2}}$$
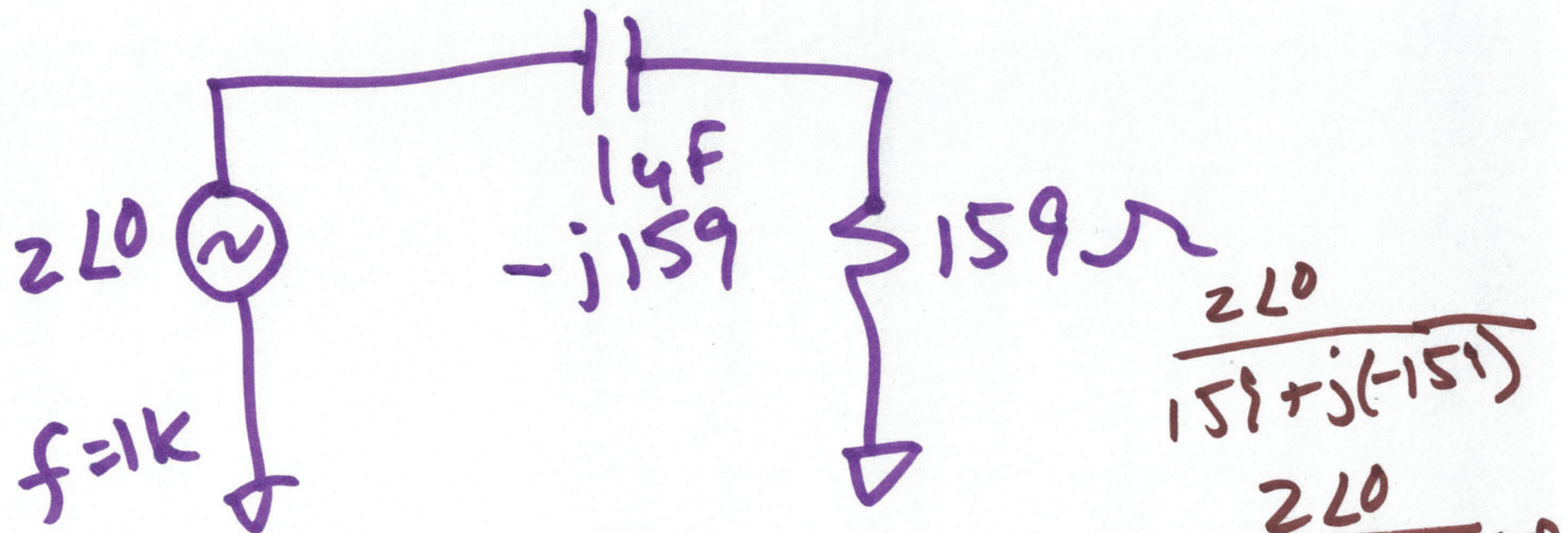
$$\angle \frac{1}{x+iy} = -\tan^{-1} \frac{y}{x}$$





$$Z = \frac{1}{j2\pi f \cdot C} = \frac{1}{j\omega C}$$


$$= \frac{1}{j \cdot 2\pi \cdot 10^3 \cdot 10^{-6}} = \frac{j159}{j} = -j159$$

$$\frac{2\angle 0}{159 + j(-159)}$$

$$= \frac{2\angle 0}{159 \cdot \sqrt{2} \angle -45^\circ}$$

$$\frac{2}{159 \cdot \sqrt{2}} \angle 45^\circ$$

8.9mA  $\angle 45^\circ$

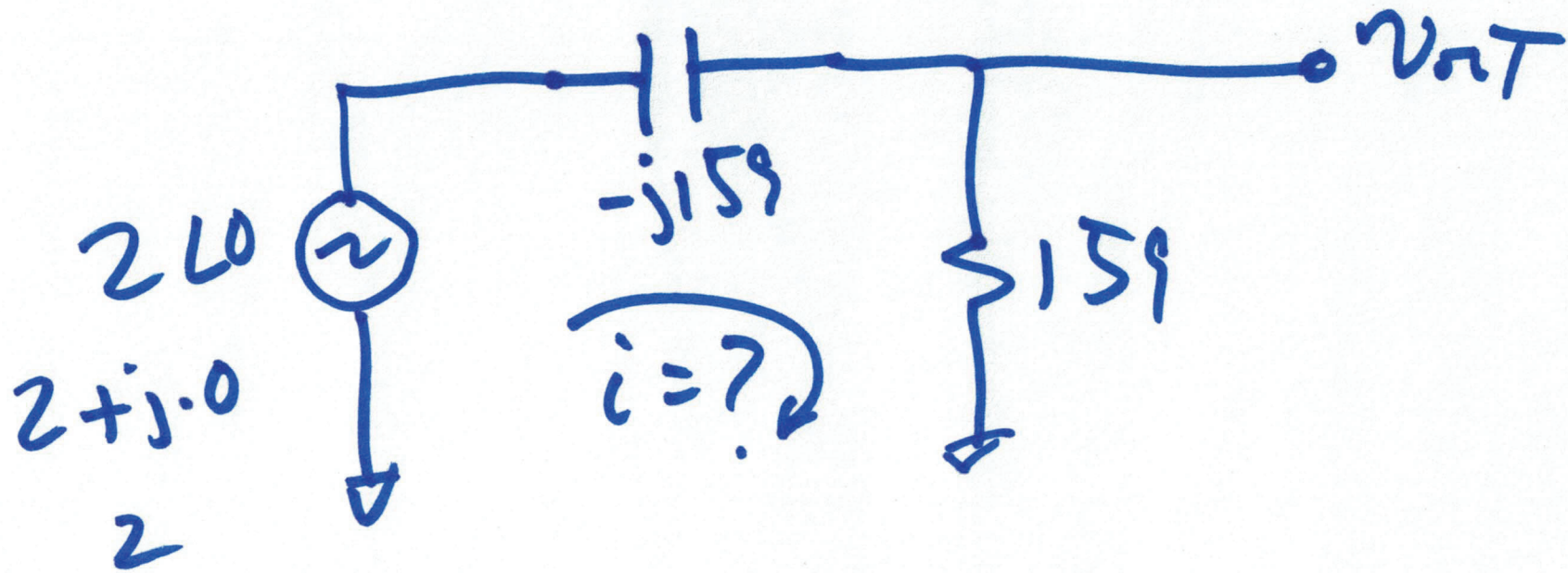

$$V_{out} = \frac{159}{159 + j(-159)} \cdot 2\angle 0$$

$$= \frac{1}{1 - j} \cdot 2\angle 0$$

$\angle -45^\circ$



$$V_{out} = \frac{1L0 \cdot 2L0}{\sqrt{(1)^2 + (-1)^2} \tan^{-1} \frac{-1}{1}} \quad -45^\circ$$

$$= \frac{2L0}{\sqrt{2} \angle -45^\circ} = \frac{2}{\sqrt{2}} \angle +45^\circ$$

$$= 1.41V \angle 45^\circ$$



$$\frac{t_d}{T} \cdot 360 = \theta$$

$$T = \frac{1}{1k} = 1\mu s$$

$$\frac{45}{360} = \frac{t_d}{1\mu s}$$

$$t_d = 0.125\mu s = 125ns$$